

World's Greatest Loudspeaker Values

RADIO

iblished by EXPERIMENTER PUBLISHING COMPANY, INC.

Publishers of "Radio News," "Science and Invention,"
"The Experimenter" and "Mater Camper & Turrist."

Editorial and General Offices: S3 Park PL, New York City

H. GERNSBACK, President. S. GERNSBACK, Trensver R. W. DEMOTT, Secretary, MEMBER: AUDIT BUREAU OF CIRCULATIONS

VOLUME 7

CONTENTS OCTOBER, 1925

NUMBER 4

In Our Next Issue

Further Applications in Vacuum

Tubes.

This is another of the serie farticles by Dr. Bazzoni show

of articles by Dr. Bazzoni showng the wide adaptability of the vacuum tube to human needs.

Straight-Line Frequency Dials, Explained by Sylvan Harris. This is perhaps the latest development that has occurred in popular radio applications this year.

Multiple Grid Vacuum Tubes.

Multi-grid vacuum tubes have attained wide popularity in

Europe, but are practically unknown here in America among the B. C. L.'s. An article by Theodore H. Nakken describes the application and use of these highly efficient tubes.

A Two-Range Receiver, Designed by Radio News Laboratories Staff.

This is another of the multirange sets designed to cover a range of 600 to 150 meters, at the same time eliminating the crowding of the stations.

In This Issue

Editorial.

By Hugo Gernsback 409

The Behavior of Radio

Waves, By Dr. E. F. W.

Alexanderson 410

Radio Stereophony.

By Ludwig Kapeller 416

Superpower Broadcasting.. 6
Parlor Magic With Your
Radio Set.

By Hugo Gernsback The Times Flies.

The Vacuum Tube And
Photo-Electric Cell.
By Gen. Gustave Ferrié 426

The Inventions of Reginald
A. Fessenden
New Ideas In Receivers.

By G. C. B. Rowe International Radio

By James Denson Sayers
Hard Tubes And Soft Tubes

As Amplifiers and Detectors.

By Dr. C. B. Bazzoni 434

By Dr. C. B. Bazzoni 434
The Luminotron.
By Theodore H. Nakken 436

- The Radio Hook at WRNY 438 \$370 Radio Play Contest.. 438 Radio Set Directory 439 The Balanced Interflex Cir-
- A New Super-Heterodyne.

 By McMurdo Silver 4
- Extending The Broadcast Range. By Sylvan Harris 44
- Does a Straight-Line Frequency Condenser Exist? By Sylvan Harris 447

 - th the Amateurs.

 By A. P. Peck 450
 - By A. P. Peck 450 e Radio Beginner. By A. P. Peck 451
- All About Filters.

 By Edward W. Berry 452

 Radio Wrinkles 454
 - ndard Hook-ups 45
- By John B. Brady 459
 Radio News Laboratories. 460
 Correspondence From Readers 462
- I Want To Know. By R. D. Washburne 463

ALDO KINN is positioned on the 10 of one processing matthe. Series were the content and principality of the "Feet" (v. C. the 1 werd on \$0 \) and we control the invasion of the content o

General Advertising De 53 Park Place

Western Advertising Representatives Finnesn & MrClure 720 Cass St. Otherne, III. New England Advertising Representative T. F. Magrane, Park Square Building, Besten, Mass. BADO MIN'S to fee take at all assembled to the Cailed Stage and Control.

1000° TO STEECHINE FOR KARDO NNN. Best year quee, either and
1000° TO STEECHINE FOR KARDO NNN. Best year quee, either and
1000° TO STEECHINE FOR KARDO NNN.
1000° TO STEECHINE FOR STEECHINE TO STEECH NNN
1000° TO STEECHINE TO STEECH NNN
1000° TO STEECHINE TO STEECH NNN
1000° TO STEECH NN
1000° TO STE

hamber to you; we stop our deliver to you on expiration.

Parific Coast Advertising Representative Exams City Advertising Representative Exams City Advertising Representative Deliver Heart Bilds. San Francisce. Colif. 15 W. Tenth St., Kansas City, Mo

Detreit Advertising Representative Roy Buell, Denovan Bldg., Detroit, Mich.

The Jan Wolf and what it brings to you with the Day-Fan Superadio

Day-Fan Superadio is like a great railroad station into which run a hun-

The train from San Francisco comes in on track 47. Pittsburgh's train rollsin on track 17. A long distance express from Nebraska comes in on track 13. A big New York special comes in at 65. These tracks belong to these trains.

They always come in on them. You know where to meet them. So for a hundred other trains from all over the United States.

Yes, you have guessed it. The trains are the music, the speeches, the songs that travel through space to your radio. The hundred tracks are the hundred lines on your Day-Fan dial.

Instead of running from track to track, know in advance where your train comes in. The Day-Fan Air Telephone Directory will tell you. No other set can do this. If you are using a Day-Fan 5 Tube Set it also has the newspaper numbers right on its dial. You need never again miss the "music train" you had planned to meet and enjoy. Day-Fan owners take distance for granted, just as they speak across the continent by telephone. They take selectivity for granted, and as a matter of course expect to cut out one station and get another. The thing that they are never able to take for granted is Day-Fan's sound beauty, for it is a second to the control of the course of the lin differs from a fifteen thousand dollar Stradivaries.

Magnificent as Day-Fan is in volume, exact as it is in its arrow-like flight to the music you'seek, masterious, its out-be in simplicities and the music to the m

Go hear a Day-Fan today and prove these things to yourself right away. If you do not know who is your nearest Day-Fan dealer drop us a line and we will tel lyou, or write us addressing Dept. RN and we will send you complete Day-Fan catalogue.



OEM 12, \$75.00 4 Tube



OEM 7, \$98.00 4 Tube Super-selective



Have the Day-Fan Air Telephone Directory malled to your home. A complete litt of all stations revised monthly from Government Reports. See all fifty cents in money order to The Dayton Fan & Motor Co. for six months' subscription.



Day-Fan 5, \$115.00 5 Tube Single dial control

Day Craft, \$145.00 5 Tube Self contained loud speaker and room for B batteries. With Legs, \$165.00 Legs Separate, \$20.00

Other Models, including consoles, to \$300.00

THE DAYTON FAN & MOTOR CO.

Dayton, Ohio
For more than 36 Years Manufacturers of
High Grade Electrical Apparatus



Radio Television Co., The 496

Randolph & Company......534

Rathbun Mig. Co., Inc......493

Rola Co., The509

Page

A.C Electrical Mfg. Co., The...549

Aero Products, Inc.467

Aerovox Wireless Corp.508

Alden Mfg. Co.484 All-American Radio Corp.529

INDEX TO ADVERTISERS

Kenman Electric Co., Inc.533

Kimley Electric Co., Inc.....566

Kinley Radio Co.554

Kirtland-Engel Co.506

Klosner Radio Corp.502

Klosner Radio Corp., The, Kodel Radio Corp., The, 406-407-551

L

DeWitt LaFrance Co., Inc.....532

Diamond Elec. Specialties Corp., 557

E

E. I. Company, The ...476-542-566

Eagle Radio Company474

Corp.544

Dubilier Condenser & Radio

| Amhassador Sales Co553 | Electrad, Inc | | |
|---|--|--|--|
| American Bosch Magneto Corn | Electric Specialty Co528 | Lancaster & Allwine | Saal Co., H. G |
| The404-405 | Electric Storage Battery Co., The519 | Lincoln Typewriter Co562 | Saturn Miss & Sales Co. Inc. |
| American Electric Co554 | The519 | Lincoln Typewriter Co | Saturn Mig. & Sales Co., Inc., The |
| American Hard Rubber Co491 | Electrical Engineers Equipment Co | | Service Battery Co |
| Amplion Corp. of America, The. 492 | Electrical Products Mfg. Co521 | M | Shipman-Ward Mig. Co550 |
| Amsco Products, Inc488 | Electrical Research Labs555 | | Silver-Marshall516 |
| Andrews Radio Co492 | Electro Thermal Co., The538 | | Smith, B. R558 |
| Antennaphone Co468 | | M & M Company, The565 | Smith Typewriter Sales Corp480 |
| Apex Electric Mfg. Co558 | Elgin Radio Supply Co486 | Manhattan Knitting Mills 476 | Southern Toy Co |
| Arrow Battery Co544 | Elite Stationery Co | Marshall Electric Co500 | Standard Aerial Base Co506 |
| Atwater Kent Mfg. Co473 | Erie Fixture Supply Co 500 Evans & Company, Victor J 546 | Martin Copeland Co | Standard Radio Co |
| | Evans & Company, Victor J540 | Massachusetts Radio School540 | Star-King Co |
| | | Mercury Electric Corp484 | Steger & Sons Piano Mfg. Co562 |
| В | P | Midwest Radio Co563 | Steinite Laboratories558 |
| | y | Miller Rubber Co. of N. Y546 | Sterling Mig. Co., The500 |
| Bakelite Corp399 | | Montgomery Ward & Co508 | Sylvania Products Co503 |
| Barawick Co | | | Dyframa Products Co. 11111111000 |
| Barkelew Electric Mfg. Co., The.532 | Fahnestock Eletric Co530 | Mozart-Grand Co., The545 | |
| Bastian Bros. Co | Fansteel Products Co., Inc475 | Multivider Co | T |
| Belden Mfg. Co513 | Ferbend Electric Co470-565 | Murdock Company, Wm. J554 | AND THE RESERVE OF THE PARTY OF |
| Bell Mfg. Co | Fishwick Radio Co472 | Music Master Corp471 | AND THE RESERVE OF THE PARTY OF |
| Benjamin Elec. Míg. Co 502 | Formica Insulation Co., The 495 | Musselman, A. J483 | Avenue of the second se |
| Benjamin Elec. Mig. Co502 | Frost, Inc., Herbert H553 | Mydar Radio Co474 | Telephone Maintenance Co550 |
| Big Three Radio Corp'n531 | | The state of the s | Thomas Battery Corp563 |
| Black Bros. Co | | 1-2 1 (S) | Thordarson Electric Mfg. Co505 |
| Bluebird Tube Co482 | G | N | Tower Mfg. Corp393 |
| Bodine Electric Co | G | the state of the s | Trimm Radio Mfg. Co482 |
| Boice, W. B. & J. E544 | TOTAL STATE OF THE | Actions Library and South | Tuerk Mfg, Co |
| Brady, John B498 | | Nagel Electric Company, The | |
| Branston, Inc., Chas. A510 | G & S Radio Lab530 | W. G536 | |
| Brant Battery Co540 | Gale Radio Labs558 | National Airphone Corp500 | U |
| Braun Co., W. C498 | Gearhart-Schlueter Radio Corp 554 | National Carbon Co., Inc469 | |
| Bristol Company, The481 | Gem Tube Company557 | National Radio Inst397 | |
| Brownlie, Roland486 | General Electric Co484 | Norden-Hauck, Inc | |
| Buescher Band Inst. Co566 | Goertz & Co., Inc., August510 | Months and the manner | Uncle Sam Electric Co565 |
| Buss Radio Service, Leo E502 | Golden-Leutz, Inc490 | | Union Fabric Co |
| | | | |
| Buss Radio Service, Les Liveries | Goodrich Rubber Co., The B. F487 | | Union Radio Corp468 |
| | Goodrich Rubber Co., The B. F487 Gould Storage Battery Co., Inc., | 0 | Union Radio Corp |
| C C | | 0 | Union Radio Corp468 |
| | Gould Storage Battery Co., Inc., The517 | 0 | Union Radio Corp |
| c | Gould Storage Battery Co., Inc., | | Union Radio Corp |
| C. E. Mig. Company, Inc 520 | Gould Storage Battery Co., Inc., The517 | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C. E. Mig. Company, Inc 520 California Radio Minerals 486 | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The517 | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Mfg. Company, Inc 520 California Radio Minerals 486 Carborundum Company, The 526 Carter Radio Company | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Mfg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Usion Radio Corp. 463 U. S. Naval Institute 478 U. S. Tool Company, Inc. 486 Utility Cabinet Co. 550 V Valley Electric Co. 400-401 |
| C C. E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C C. E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Usion Radio Corp. 463 U. S. Naval Institute 478 U. S. Tool Company, Inc. 486 Utility Cabinet Co. 550 V Valley Electric Co. 400-401 |
| C E. Mg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C E. Míg. Company, Inc | Gould Storage Battery Co., Inc., The | Dilo Samping & Engineering 10,00 | Union Radio Corp |
| C. E. Mig. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Engineering Co. The | Union Radio Corp |
| C E. Mig. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stompling & Engiovering Co., The | Union Radio Corp |
| C C. E. Mig. Company, Inc | Gould Storage Battery Co, Inc., The | Ohio, Sumoing & Engineering Co., The | Union Radio Corp |
| C E. Mig Company, Inc | Gould Storage Battery Co., Inc., The | Ohio, Stanging & Engionering Co., The | Union Radio Corp |
| C E. Mig. Company, Inc | Gold Storage Battery Co., Ec., The | Ohio, Sumoing & Engineering Co., The | Union Radio Corp |
| C E. Mig. Company, Inc | Goidd Storage Battery Co., 15, 17. The | Ohio, Stanging & Engionering Co., The | Union Kadio Corp |
| C E. Mig. Comeny. Inc | Gold Storage Battery Co., Ec., The | Ohio Stamping & Engineering 1. CA, The | Union Radio Corp |
| C E. Mig. Campany, Inc | Goidd Storage Battery Co., 15, 17. The | Ohio, Stanging & Engionering Co., The | Union Radio Corp |
| C E. Mig. Company, Inc | Gold Storage Battery Co., Ec., The | Ohio Stamping & Engineering 1. CA, The | Union Kadio Corp |
| C E. Mig. Comeny. Inc | Goidd Storage Battery Co., 15, 17. The | Ohio Stamping & Engineering CA, The 18th CA, 18 | Union Radio Corp |
| C E. Mig. Campsoy, Inc | Gould Storage Battery Co., Ecc., The | Ohio Stamping & Englowering Co., The | Union Kadio Corp |
| C E. Mig. Company, Inc | Gold Storage Battery Co., Ec., The | Ohio Stamping & Englowering Co., The | Union Kadio Corp |
| C E. Mig. Campsoy, Inc | Gould Storage Battery Co., Ecc., The | Ohio Stamping & Engiovering 1. CA, The 1.0 CA 1.0 C | Union Radio Corp |
| C E. Mig. Company, Inc | Goidd Storage Battery Co., 10.5, 17 Geyer Company, The | Ohio Stamping & Englowering Co. The | Union Kadio Corp |
| C E. Mig. Company, Inc | Gmidd Storage Battery Co., Ec., The | Ohio Stamping & Englowering Co., The | Union Radio Corp |
| C E. Mig. Company, Inc | Goidd Storage Battery Co., 10.5, 17 Geyer Company, The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C E. Mig. Company, Inc | Gould Storage Battery Co., Inc., The | Ohio Stamping & Englowering Co., The | Union Radio Corp |
| C S. My Company, Inc | Gould Storage Battery Co., Ec., The | Ohio Stamping & Englovering Co., The | Union Radio Corp |
| C E. Mig. Company. Inc | Gould Storage Battery Co., 10.5, 176 Coyer Company, The | Ohio Stamping & Engineering Co., The | Union Radio Corp |
| C S. My Company, Inc | Gould Storage Battery Co., Ec., The | Ohio Stamping & Englovering Co., The | Union Radio Corp |





Boys New Car With Earnings
Arrows, reparlies of any
extra transfer of the control of the control

Makes \$25 a Week NORE

Is Radio

It can making about \$25 a

Your Cutter, Michigan

You'r Letterdood, Mr. Bartyou'r Cutterdood, Mr. Bartyou'r Cutterdood, Mr. Bartyou'r Cutterdood, Mr. Bartsteel, W. ballid 4-stabe radio

Radio State of the state of the state of the state

Radio State of the state of the state of the state

Radio State of the state of the state of the state

Radio State of the state



Increase Pay 160 Per Ceat
I was just receiving E.O.
I was the part of the part of

Earn\$50 to \$250 a week in Radio

Home in Spare Time

Big Jobs Waiting In the Radio

F YOU are making less than \$50 a week
—if you want to get into the big pay
class in the world's fastest growing industry—get into Radio—NOW. Coupon
brings you full information.

Big jobs are open for trained men, in every section of the country. Radio manufacturers—distributors—dealers—broadcasts ing and receiving stations—arthroads and steamship companies and branches of the Government, need trained open everywhere for men to go into business for themselves a Radio Experts. The pay is hig, Thousands are now making \$50 o \$200 a week of Radio. This great industry is making new

Learn Quickly at Home by Tested Method

You can become a Radio Expert quickly, and easily, in your spare time at home, with the help of the National Radio Institute-America This Lamous, tested course makes Radio as simple as ABC—and so fascinating you will scarcely realize that you are master-quickly realized that you will be careful to the property of the

This Is the Course That Pays

We mean every word of it! We have developed the famus method that makes it unnecessary for your training to be an expense. Instead of making any man "scrimp" to get his training, your returns practically from rower way your course will pay for tixen, and more—much more! Get the details of these anazing methods.

Don't Worry About Age or Education

It makes no difference what your age is or what your previous training has been. Radio is a field in itself. It calls men of all ages from youth to settled middle age. Success does demand training in Radio and the N. R. I. course gives you training necessary to Success.

Up-To-Date Receiving Sets

You learn by doing—through the N. R. I. Course. All materials and equipment necessary are furnished you along with your course. You are sent receiving sets to build and install—real sets for experimental work and pleasure. This is a practical course that teaches you to get the practical results that be good to get the practical results that big pay jobs demand.

Helpful Employment Service

We are constantly in touch with openings for trained Radio men. The men we train get first chance at these fine jobs through our Employment Department—at no extra cost. When you complete our training we help you until you get

Mail Coupon Quick for FREE BOOK and Special Offer

The coupon below will bring you the most amazing book of Radio, ever written. It will open your eyes to the opportunities for you in this established, big pay field and fell you how to become a Radio Expert in your spare time at home. It has helped thousands of men to success in Radio.

Important: We have a Special Limited Offer for those who act quickly Mail the coupon or write a letter NOW. NATIONAL RADIO INSTITUTE

Dept. 13 MB, Washington, D. C.

Get this FREE BOOK

NATIONAL RADIO INSTITUTE, Deet 13MB Washington, D. C.

..... State.....

RADIO NEWS READERS' BUREAU

Time and Postage Saver

I N every issue of RADIO NEWS you undoubtedly see numerous articles advertised about which you would like to have further information. To sit down and write an individual letter to each of these respective concerns, regarding the article on which you desire information, would be quite a task.

As a special service to our readers, we will write the letters for you, thus saving your time and money.

Just write the names of the products about which you want information, and to avoid error the addresses of the manufacturers, on the coupon below and mail it to us.

DEADERS' SERVICE DUREAT

If the advertiser requires any money or stamps to be sent to pay the mailing charges on his catalogue or descriptive literature, please be sure to enclose the correct amount with the coupon.

We will transmit to the various advertisers your request for information on their products.

This service will appear regularly every month on this same page in RADIO NEWS.

If there is any Manufacturer not advertising in this month's issue of RADIO NEWS, from whom you would like to receive literature, write his name, address and the product in the special section of the coupon below.

TEAR ALONG THIS LINE

| DO NOT USE THIS COUPON FOR TECHNICAL QUESTIONS | | | | |
|--|------------------------------------|--|--|--|
| NAME | ADDRESS (Street — City — State) | List here specific article on which you wish literature. | of complete line is want ed, check in this column | |
| | | | | |
| | | | | |
| | | | | |
| Jse this space if you desire info NAME | ADDRESS (Street — City — Sta | The state of the s | month's issue | |
| | | | | |
| | | | | |
| Your name | Dealer | 's name | | |
| | His ac | ldress | | |

It's mahogany to the eye-but in fact it's Bakelite

So perfectly is the grain and color of mahogany and walnut reproduced in these Bakelite Radio Panels, that the eye cannot distinguish them from the natural woods.

By using a Bakelite Panel that matches the wood in the cabinet, your finished set will be far more handsome than if a plain panel is used.

Rigid and strong, Bakelite Panels support the weight of heavy instruments without sagging. They will not compress, or cold-flow, under pressure of binding screws. Because of their resistance to extremes of heat, cold and moisture, they will not warp nor split. These properties and their insulation value, color and finish are permanent.

Be sure to ask your dealer to show you these wood finish Bakelite Panels-obtainable under any of the following trade-names:

CELORON Dilecto Fibroc Micarta

A Bakelite Panel on a set is an indication that the manufacturer has used the best.

Write for Booklet 24

BAKELITE CORPORATION

247 Park Avenue, New York, N. Y. Chicago Office: 636 West 22nd Street



BARTIN.
In the registered intended of the optional state opti



THE MATERIAL OF A THOUSAND USES





Selectivity means more with the Valleytone

Potential Balance

exclusive in the Valleytone

The potential balance method of suppressing oscillation and preventing distortion is used for the first time and exclusively in the Valleytone Radio Receiver

tone Radio Receiver.

Reception is clear and mellow—free from the thin, hard, metallic sound and the howls and squeaks which have been the plague of radio.

Toroidal Coils

The Valleytone is the first manufactured set to use Toroidal coils. The Toroidal windingallows a greater coupling ratio between primary and secondary. The result is an appreciable increase in volume over the old solenoid winding.

Appearance

The Valleytone is mounted in a solid walnut cabinet, finished in two tones with inlaid gold stripes. It may also be procured in beautiful console models. Special Valley tables with built in loud speaker may be obtained for the cabinet model. Finer tuning becomes a reality , , , selectivity means more with the Valleytone Radio Receiver.

For instance: The Valleytone has regularly received and separated clearly and distinctly, radio programs broadcasted simultaneously from stations on wave lengths from four to five meters apart.

Such selectivity is attained in the Valleytone by the exclusive potential balance. The Valleytone circuit brings in stations sharply, clearly, and free from distortion.

With the Valleytone, you can enjoy radio as never before. You can get a station if it is on the air and transmitting strongly enough to reach you. You can choose your stations by the clock and hear them with the Valleytone.

The Valleytone is a five-tube set. It is manufactured by an old established company with the experience and the resources to assure you always the utmost in radio value. Before you buy a radio, see the Valleytone. Hear it. Let an authorized Valley dealer give you a demonstration. VALLEY ELECTRIC COMPANY, Radio Division, ST. LOUIS, U.S.A.

Branches in Principal Cities
Valleytone Valley

Valley Valley
Receiving Sets Battery Chargers B-Eliminators

Valley Electric

For radio at its best you need these, too



Valley B-Eliminator

The Valley B-Eliminator is made for receiving sets of from one to eight tubes. Binding posts and control rheostats are mounted on Bukelite punel. The unit is enclosed in a handsome black case.

It costs less at the start than wet B batteries and less in the long run than dry cells, too. Much more satisfactory than either.

Like new B batteries every night Here is a new and better way of supplying B voltage for radio reception.

B batteries wear out. They cannot be the same two nights in succession. As they decrease in strength, vol-

ume decreases, too. Furthermore, they become noisy as they wear out. The absolutely ideal B battery current can be obtained only by the use of fresh new B batteries every night.

The same ideal results can now be obtained by the use of the Valley B-Eliminator as your source of B voltage. In its performance, the Valley B-Eliminator is like a new set of B batteries every time you tune in and every second you are tuned in. The Valley B-Eliminator is more than a substitute for

B Batteries. It is a new and better way of supplying B voltage for radio reception. It operates on the house lighting circuit and provides B current at a constant voltage all the time.

Hence reception is always at its best. There is never any decrease in the strength of signals and none of the frying noises or hum which are due to low B batteries. Volume is maintained. Reception is uniformly good.

The charger with ten points of superiority

The Valley Battery Charger has a reputation for results. It is based on principles which were proven successful long before radio became popular.

It is the only charger needed for all radio batteries:—6 volt A bet-teries; 24, 48, 72 or 96 volt B batteries; and 2 volt batteries.

It has ten points of superiority

- 1 No bulbs. 2 No liquids.
- 3 Quiet in operation. 4 Cannot harm your battery.
- 5 Efficient. Takes about a dime's worth of current for a full charge. 6 Correct 6-ampere charging
- rate enables you to recharge your battery overnight. 7 Ammeter mounted flush with
- panel shows if battery is receiv-ing charge and if charging rate is correct.

Valley Battery Charger.

8 Special switch for B batteries. Voltages: 24, 48, 72, 96.

9 Has only two wearing parts, the contacts, which can be re-

two years. 10 Built in handsome black case with grained and engraved Bakelite pane and clear glass top which shows simple patented working parts. Harmonizes with

the finest receiving set. These features are all essential. Be sure of them by getting only a



Valley Battery Charger

VALLEY ELECTRIC COMPANY, Radio Division, St. Louis, U. S. A. Branches in Principal Cities

Valleytone Valley Valley Receiving Sets Battery Chargers B-Eliminators

Valley Electric



The Greatest Advances in Radio Design are Embodied in the

new **ULTRADYNE**

F the Ultradyne Model L-3 were merely another new receiver, its influence in the industry would be little felt.

But it is in reality the first step in the general revision of radio receiver design which is bound to follow its advent.

For the new Ultradyne Model L-3 is an entirely new type of receiver -radically different in appearance and method of operation-gives finer results from finer engineering. Employs 6 tubes, is completely

assembled and wired ready for the tubes and batteries. It has no dials-no panel-no needless controls. Two levers, an exclusive Ultradyne feature, give you control of the entire broadcast program. Its operation is practically automatic-simply slide the pointer to the station you want and adjust the volume control, soft

or loud as you like. Loud Speaker and "B" Batteries self enclosed in a beautiful cabinet

that is far from mechanical in design and an ideal mahogany furniture piece for the most charming home, This new Ultradyne Model L-3 gives you the best there is in radio

-truer reproduction than you have ever known before. Ask your dealer for a demonstration. The contrast between the

Ultradyne and other receivers is so marked that the desire to own one will be bred there and then.

Write for descriptive folder

ULTRADYNE

PHENIX RADIO CORPORATION 114 East 25th Street New York City





BOSCH BUILDS RADIO



THE AMERICAN BOSCH MAGNETO CORPORA-TION PRESENTS "THE AMBOROLA, THE BOSCH RECEIVING SET AND THE AMBOTONE." THE BOSCH REPRODUCER. THESE IN-STRUMENTS HAVE BEEN BUILT TO THE FAMOUS BOSCH LINE OF PRECISION AND ALL THE EXPERIMEN-TATION ON THEM HAS BEEN ACCOMPLISHED IN THE BOSCH LABORA-TORIES RATHER THAN IN THE HOMES OF THEIR PURCHASERS

THE AMERICAN BOSCH MAGNETO CORPORATION

BOSCH RADIO POLICY

- I. BOSCH PROTECTION FRANCHISE

 NO DISCOUNTS TO OTHER THAN
 AUTHORIZED DEALERS HOLDING
 THE BOSCH FRANCHISE.
- 2.BOSCH TERRITORIAL PROTECTION TERRITORIAL FRANCHISE DEFINED AND ALL RIGHTS PROTECTED
- 3. BOSCH PRICE GUARANTEE
 THE DEALERS PROFITS ARE PROTECTED BY GUARANTEE AGAINST PRICE REDUCTIONS UNLESS DEALER IS REBATED
- 4.BOSCH RATIFIES DEALER CONTRACTS
 ALL CONTRACTS MUST BE RATIFIED BY THE MANUFACTURER
- 5. BOSCH CO-OPERATION EXTENSIVE CONSUMER AND TRADE ADVERTISING IN NATIONAL PUB-LICATIONS. CLOSE LOCAL NEWS-PAPER CO-OPERATION
- 6. BOSCH STABILITY
 THE BOSCH RADIO POLICY MAINTAINS THE SAME ETHICAL STANDARDS WHICH HAS BEEN THE BOSCH PRACTICE FOR 15 SUCCESSFULYEARS
- 7. THE BOSCH DEALER
 THE BOSCH FRANCHISE IS A MAN
 SIZED, TWO FISTED OPPORTUNITY
 FOR ONE RECOGNIZED BUSINESS
 MAN IN A LOCALITY WHO IS
 ABLE TO CONDUCT AN INTELL
 IGENT SUCCESSFUL BUSINESS
 OVER A COURSE OF YEARS

ARE YOU THE MAN?

THE AMERICAN BOSCH MAGNETO CORPORATION SPRINGFIELD, MASS.

KODEL RADI The Emblem of Worth in Radio

Setting a New Radio Standard



Radio for years to come will not offer a better receiver than the LOGODYNE Big Five. Combining the utmost in performance with striking beauty of cabinet design, the LOGODYNE Big Five represents a triumph in radio engineering and artistry of manufacture.

No receiver could better express or exemplify the high standard to which the entire KODEL RADIO line is built-for KODEL RADIO is, without a doubt, the best that radio offers.

Free Send for the new edition of our free booklet "The Secret of Distance and Volume in Radio". Gives helpful interesting information on radio operation.

THE KODEL RADIO CORPORATION 501 East Pearl Street Cincinnati, Ohio

> WHRC ers of Kodel Broadcasting Station WKRC on the Alms Hotel. Send for program.









KODEL "Gold Star" Models-Radio's greatest set values: Three Tubs "Gold Star" Model, \$30 Two Tube "Gold Star" Model .. \$20

One Tube "Gold Star" Model ... \$12 "Gold Star" Crystal Set \$ 6



The New Improved
5 AMP. A & B
GOLD SEAL
HOMCHARGER
\$1950



Charges 150% Faster!

Better Because:-

New micrometer adjustment, hinged lid, and carrying handle. No bulbs to buy or break.

Can be used anywhere—contains no acids or other harmful liquids to spill.

Approved by underwriters trouble-proof, shock-proof and fireproof.

Beautiful cabinet in maroon and gold.

Free Write for new edition of our instructive booklet on radio operation "The Secret of Distance and Volume in Radio."

It takes only one-third as long to charge a battery with the New Improved GOLD SEAL HOMCHARGER. The big, healthy 5-ampere charging rate does away with the long bothersome waits that were necessary when the obsolete slow 2-ampere charger was the best that radio offered.

The New Improved GOLD SEAL HOMCHARGER charges 150% faster—will charge your battery overnight! And it charges both A and B batteries without additional equipment.

Don't let anybody sell you a slow 2-ampere chargerthey are obsolete—out-of-date. You need a modern charger with a full 5-ampere rate. Insist on the GOLD SEAL HOMCHARGER.

The Kodel Radio Corporation
501 East Pearl Street Cincinnati, Ohio

WKRC

Owners of Kodel Broadcasting Station WKRO



AN attractive cabinet can never make an Ozarka out of any other radio. Far too many radio buyers pay more attention to the outer appearance and not enough to the

assured that every purchaser of an Ozarka will have an experienced service man within his reach at all times. 3100 such men today comprise the Ozarka service organization - more are being added daily. Ozarka service does not add a single cent to the price you pay for your radio—then why not benefit by it?

handy man who can fix any-You send for a service man who is trained in repairing your make of car. To correct the fault is easy for him because he knows. Some other mechanic might have to tear the car apart

When your automobile runs as

the manufacturer intended it should, it is a real pleasure to drive it. But what do you do

when something goes wrong?

Do you immediately condemn

thecar?-no.Do voucall in some

thing? - no.

to locate the trouble. The same is true of radio, no matter what price you payyou will sometimes need the service of a service man. If he is factory trained and experi-enced he can and will deliver the kind of service you know you ought to have.

Ozarka instruments are only sold by direct factory representatives who are required to take a complete course of instructions of Ozarka service directly under Ozarka engineers. By so doing we are

addition to the appointments of the beautifully furnished home. Ozarka circuits have proved themselves high grade receiving sets. Whether you nign grade receiving sets. Whether you plan on installing a radio in your home, now or later, you deserve to hear the Ozarka. The Ozarka man will demonstrate the Ozarka to you right in your own home-under exactly the same conditions you will continue to use your set. Then there can be no disappointment later.

And remember, Ozarka is a radio in-strument built of the finest units, care-

strument built of the innest units, care-fully and correctly designed exteriorly and interiorly. Cabinets are ultra mod-ern, finely finished—a most attractive

Ozarka instruments are only sold in competition side by side with othersyou do your own tuning and therefore decide for yourself just what an Ozarka will do for selectivity, distance, volume and above all, tone.

Send for the book Ozarka Instruments No. 200; please give name of your county and we'll gladly have our

Ozarka representative arrange a dem onstration for you in your own home.

us see just what radio service is. We Need a Few More Ozarka Representatives

is even more important than the inside or

outside-your satisfaction depends on it. Let

RADIO offers a wonderful opportunity to men who wish to get into business for themselves. It is work that can be done, at the start, in the evenings and in your spare time. You can hold your present position and learn radio under our plan. Ozarka instruments have been on the market for four years—they have successfully met all competition. Ozarka representatives have made good, not only because Ozarka Instruments are right but because our training in both selling and service is the most complete possible

All we ask is that you are willing to purchase your demonstrating instrument and willing to learn what we are willing to teach you.

We have proven with 3100 men that with this training


We have proven with 3100 men that with this training you can make good in radio. The Ozarks sales course costs even a subject of the control of the cost of the co

Send Coupon for FREE Book

ZARKE INCORPORATED

| entlemen: Without obligation send book "Ozarka ents No. 200" and name of Ozarka representative. | Instru- |
|--|---------|
| ame | |

County.....State....

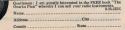

EDITORIAL AND GENERAL OFFICES, 53 PARK PLACE, NEW YOR

Val 7 OCTOBER 1925

ADVANCES IN RADIO

When E have always with us that element which tends to speculate on revolutionary discoveries in radio. As the writer has pointed out many times before, if there are revolutions in radio they surely will not be on the receiving end for some time to come, but will be, rather, on the broadcasting end.

Radio sets follow a close parallel with the phonograph and the automobile, where, to be sure, changes are made every year in minor improvements, but all three remain, roughly, the same. Last year's model, or the model of two years ago, whether phonograph, automobile or radio, will serve just as well this year and the year after. The next few years will see improvements in the physical appearance or radio set, as well as greater simplicity of controls. The tendency seems to be have as few thomass proposed or the controls of the controls of the controls of the controls of the controls.

other controls.

But out in the broadcast field great changes are coming about, and we may say that revolutionary changes will be effected in many phases during the next year. To be sure, none of these changes will affect the interest will be less that the will have been also also the will be less than the property of the proposes to do away with no of radio's greatest enemies of radio's products enemies the proposes to do away with no of radio's greatest enemies

-fading-by using a polarized wave—a brand new thing in radio. We all know how some of our most popular stations, if we are more than 100 miles away from them, will come in strong one second and will fade out almost entirely the next. The two pioneer statons, KDKA and WGY, are possibly the best examples of this fading unisance.

Then Dr. Alexanderson hopes, by a new combination, to do away with, or reduce static, one of the greatest hanes of radio today. Sooner or later the secret of "anti-static" will be discovered and we shall then be able to listent our sets in the summertime without having our reception spoiled by this greatest of nuisances. There is one remedy for static which is almost certain, and that is to bury the transmitting our reception spoiled by the present of the properties of the pr

On the receiving side this is not such a simple matter. If you are located in the country and can bury your antenna in a 75-foot insulated duct, the reception will be greatly improved. Unfortunately, such an underground aerial is also highly directive. If it points west, you will receive sta-

tions from the east at maximum strength, while those on the north and south and west will come in very poorly. The next best thing, then, would be to have a number of buried aerials radiating to the different points of the compass and connect all of them together. This remedies the directional effect, thut unfortunately it is too costly an anterna for the average broadcast listener, and besides, he doesn't have sufficient real estate, as a rule, to install such a system. Furthermore, in the city it is practically out of the question. Of the property of the companion of the property of the top a natura, but it is found that a loop antenna still picks up a good deal of static particularly when a thunderstorm is near, and while static is not as serious as with the outdoor aerial, still there is enough to spoil many a good program. The tendency of our biezer stations seems toward creater

poure. Underlyin low, rigger sactase stations averaged 500 vatts, with a few at 1,000 and 1,500 sprilled sparsely among them. During the summer, a number of 5,000-watters have made their appearance, and one of these has gone to 50,000 watts. The latter, WGY, of Schenectady, is now experimenting with this superpower. Several hundred miles away from this station its signals come in as loud as those of a local but still fade as before. This will probably be remedied sooner or later if the new Alexanderson polarized wave is used.

While superpower may help somewhat when there is little static, yet, even with stations of 50,000 watts or over, an approaching thunderstorm will be sufficient to spoil the program. What superpower does its omake it possible for the histener within a thousand miles to use a less sensitive set than the would need otherwise. With superpower the inthan the would need of the winder with the super-heterodyne did before. People with crystal sets within a radius of several hundred miles will be enabled to listen in, where heretofore 25 miles was the maximum.

The next important thing with which our engineers are rotubling themselves is the crowding of the stations. At the present time it is almost impossible to separate some of the stations on account of this crowding. Engineers are now hopeful of partly remedying this trouble by making the tuning at the sending end much sharper, so that each station will take up less room on the dial than it does now. As we all know, a radio station has its actual wave, then

there are side hands, and it is these side hands that cause heterodyning with other stations that are on the same wavelength. If the transmitting stations did not require any side bands at all and could operate on their exact waves, we should rarely have such a thing as interference from other stations. As a matter of fact, we could operate a great many more stations than we do now without interference, crainers are honeful that there is a remedy. Seem found, or

The Behavior of Radio Waves

By DR. E. F. W. ALEXANDERSON



Dr. Alexanderson, who has been associated with radio for many years, is an authority in this field whose name is well known to the reading public. RANO NEWS takes great pleasure in presenting this special authorized interview with him on a new and very interesting phenomenon in radio—the behavior of polarized waves.



In the future we shall point our radio transmitters at the receiving station we wish to speak with, and then fire them as we do our big guns today. We are constantly learning more and more concerning the nature of the propagation of radio waves, and as soon as our knowledge is more nearly complete we shall be able to determine just

complete we stall power, what type of antenna should be used for the greatest possible efficiency at any time of day or night and in any direction from the transmitter. This branch of radio science has been, in the past, very reluctant to give up its secrets. The engineers have, of ourse,

in the past, very reluctant to give up its secrets. The engineers have, of course, learned that under certain conditions a radio wave will do certain things. With this knowledge they have erected and put into operation the great industry we use so constantly.

But the point is that the physicists and the laboratory engineers whose business it is to investigate the natural phenomena withour reference to their practical applications have been unable to collect very much data concerning the why and wherefore of the action taking place in an artenian when it space and the exact nature of the action in that space, as the signal is carried to the receiving station.

Investigations of the last ten years have only been complicated by the work of Einstein and others by their taking away the ether, upon which so much of the previous theories had been founded. This deletion of the ether has not changed the actual operation of radio waves, of course. It has simply changed our conception of the prob-

THE ELECTRON, THE BASIC PROBLEM
At the foundation of the whole problem
is the electron. We know pretty well that

And here is as far as we may go with certainty. But in order to visualize to ourselves just what is happening, so that we may have some idea as to what actually takes place when we set a current in motion in an antenna and obtain a resultant force radiation, we must imagine, as nearly as possible, the purely physical reactions oc-



How polarized radio waves act when they are sent out into space from a horizontal multiple tuned

any passage of electrical current through a conductor is accompanied by a movement of the electrons in that conductor. This point is generally accepted among the scientists as fairly well proved.

The same thing occurs when the high fre-

The same thing occurs when the high frequency, high tension current is sent into an antenna. The electrons in the wire move in it according to the half-cycle passing through.

curring in the conductor and in the space. Since the deletion of the ether hypothesis, there has been a tendency among the physicists to accept the electron as a center of a field of force. Some-including Einstein -go further and say that the electron is nothing more than a field of force. However, to be a bit more conservative, let us suppose for the moment that the electron is as it has always been considered, the negative unit charge, with mass. The next step in the new line of thinking is that the elecbeing a center of force, drags a tentacle-like effect with it in its travels. is, when the electron moves, being the center of a force, it carries a field of strain with it. It must be considered that the strain always follows the electron.


So it should be quite possible for the electrons, moving in the antenna, to impart their force to the space around the antenna. In fact, this is probably what happens.

How this power travels through space must remain somewhat of an mystery untiwe discover something more of the nature of "space". At present, under the Einstein view and the hypotheses of other scientists over and the hypotheses of other scientists is in a matter of simply stirring up the site of the stirring of the stirring of the in the state, pending the further creation in that state, pending the further better the state, pending the further But we do know that we are gaining a

nore thorough knowledge of the immediate effect on transmission efficiency of certain types of antennae and their consequent wave

PECULIARITIES OF SHORT WAVES

The coming of the high frequencies or short wave-length has introduced a whole new field of investigation, which has brought us much more closely in touch with the problems and theories mentioned above. We now know that the short waves are effective almost entirely through the agency of their light under coldision. It is, their transmitted in the control of the control of the coldilative the antenna, travel upward into the higher strate of atmosphere and are re-

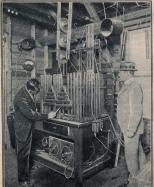



Dr. Alexanderson (on the right) in the laboratory where the transmitting apparatus for the short waves is housed.



The meter in the vertical leg of the antenna which is such an important factor in the generation of the polarized waves. In each vertical section of the antenna there must be an absolute balancing of the current for maximum results.

The portable receiving meter is
shown on the right
being inspected by
Dr. Alexanderson.
It is with a meter
of this type that
the polarized effects of waves are
studied.



THE ANTENNA

A word concerning the antenna: It is built to radiate at the shorter wave-lengths and consists of six tuned units. The end of the docted loop. In these high frequency leads there are two meters, one in each lead. In the erection of the antenna each lead, the three contents are the end of the content of the end of the

It is all these considerations which lead me to believe that the future will find us taking the bearing of the receiver, looking at the clock for the hour of day and night, and at both the transmitter and receiver, and that the engineer at the transmitter will then select the proper wave-length, the proper hour and the proper type of antenna for his work. It will be just as if he were pointing a big gun at the receiver.

flexied downward to the receiving station. This path is very much on the order of the path of the path

The exact nature of these waves, even, is not known. Along this same line of development and attack, which may throw a great deal of light on the action of waves, is the new horizontal polarization effect noted in the use of a horizontal loop. It has recently been observed that waves passed into space from a multiple tuned loop, supported in a horizontal direction, will radiate a pecu-

assumptions.

liar wave, polarized in the plane of the loop. The discovery of these waves may in-terest the reader. While we were engaged in some field test measurements, with different types of antennae, we noted one day that there was apparently no signal being radiated. The field test apparatus, which consisted of a short vertical antenna, was being carried around the station within a mile of the antenna. The meter in the receiving set, which registered the received current, showed that there was no radiation. Immediately we returned to the operating room to see if something had gone amiss with the generators. Upon arriving there we found that observation stations a couple of hundred miles distant were picking up the signals with ease.


This necessitated the postulating of the

This necessitated the postulating horizontally polarized waves.

Preliminary tests seem to show that as these waves travel further and further from the source, they change their plane in the manner of a cork-screw. This makes possible the reception of them, with the ordinary amerum, only at certain distances. This area not yet thoroughly understood. However, from the experimental station of the

General Electric Company, where the first of the experiments were tried and where the phenomenon was first noted, the distance for the first turn seems to be in the neighborhood of fifteen miles.


A very interesting point in connection with the construction of autenase was also brought the construction of autenase was also brought vertical loops were employed as radiators, vertical loops were employed as radiators, the loops was zero. The receiving station of the Radio Corporation of America at screening the Corporation of America at screening and little difference from the usual exception. This was surprising until we the horizontal waves, it happened that the vertical legs of the loops were neutralizing themselves while the horizontal portroom polarized type, cond ratiators of the new

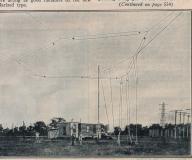

The antenna which is employed for the propagation of the polarized high frequency waves. Note the six sections of the horizontal loop.

Radio in Germany


By DR. EUGENE NESPER

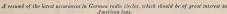



Salvee the time when, about a year ago, the regenerative circuits represently on the part of many of the part of amount of the part of the p

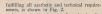In view of the fact that for the radio amateur time is no consideration and that he can consequently delve as deeply as he likes into radio technique, it is not surpris-



Among the numerous reflex circuits displayed at the exhibition, the two-tube reflex, Fig. 3, deserves special notice. The inductances are arranged to give very fine tuning over the largest possible range. Among the devices for fine adjustment the specially designed short-circuiting plug is to be noted, as indicated in the figure.

Special interest was aroused by the neutrodyne receivers. Most of these, as well as most of the other apparatus, are designed for wave-lengths of 200 to 700 meters.

A very interesting neutrodyne receiver is shown in Fig. 4. This is similar to the Halenz apparatus, but unlike the latter has its tubes protruding through the top of the cabinet. In addition, this set has a feature which should be embodied in all highly efficient sets, that is, measuring instruments by which the current and voltage may be continuously observed and so maintained constant.

While the sets so far described were mounted in the usual cabinet, the Cetthus exhibit also displayed a number of receivers cally in gramaplone style. One four-tube calls in gramaplone style. One four-tube is shown in Fig. 5. The tubes, dals and coils, etc., are mounted on a hard rubber panel, while the measuring instruments and low, within the gramaphone cabinet, are the batteries.

Still more flexible equipment is provided in an experimental receiver (Fig. 6) which, by means of a few switches, can set up a number of different circuits. In addition to these constructional and ex-

perimental activities, the Cottbus radio group maintains a short-wave broadcast station of about 90 meters and a capacity of 100 watts.

THE RADIO EXHIBITION

The first of September ushered in a new period in German broadcasting. On this day the regulations and prohibitions that had interfered with the free development



The exhibition hall built especially for radio in Betlin. The tower is the highest in Germany used for radio.

of the radio industry were abolished, and

with prohibition, have been relaxed as well.

The fact that, in spite of all these difficulties, the number of listeners in Germany has reached one million, of whom 38,000



Fig. 1. A regenerative receiver with two steps of A.F. amplification.

ing that it is just in the field of complex radio circuits that annaturus have achieved articles are considered in the consideration of the which the Cotthus Branch of the German Radio Clabs, under the leadership of Dr. 1925, displayed, therefore, very highly developed radio cignipment. There were at this exhibit seventeen neutrodynes and about which could not be surpassed, even by the which were built exclusively by amateurs and which could not be surpassed, even by the this, the exhibit acclusively by amateurs and developments in receiver construction. In particular the following sets were note-

THE EVER-POPULAR REGENERATIVE

The regenerative receiver with two audio frequency steps shown in Fig. 1 meets the demands of the commercial designs fully. This apparatus, in addition to being highly efficient, is very ornamental. Here special emphasis was also placed on delicate adjustments.

In connection with this apparatus, as with

all of those following, a schematic circuit diagram was displayed so that those interested could gain an immediate insight into the construction of the set. A four-tube Reinartz receiver, similarly



The 5 K.W. transmitter in the Konigswusterhausen station, one of the largest broadcast stations in the world.

are residents of Berlin and its suburbs, is a sign of the keen interest of the people in radio. It must not be overlooked that broadcasting altogether has been given free in Germany only since the end of 1923 so that Germany only since the end of 1923 so that she is the youngest among the big nations in radio. On the other hand, very early broadcasting did take place in 1920, from January till June, in Berlin. Here the opera "Madame Butterfly" was taken through microphones in the state opera house, transmitted by an ordinary overland line to the sender 27 miles distant in Königswusterhausen and thence broadcast with a power of sen and thence bloaders and on a wavelength of 2,800 meters. heard at a distance of 1,900 miles. Later private Sunday concerts were broadcast from this sender for some time. Though the annaratus used were property of the postal authorities, the whole enterprise may be considered to be the first amateur broadcasting as it was due exclusively to the initiative of the manager of the station. The same sender opened the official German broadcasting in 1923 and is, at present, working nightly with 10 k.w. efficiency on a wavelength of 1,300 meters. The organization of the German broad-

cast service is different from that of other countries in so far as all the transmitting The broadcast service is in the hands of private companies which are quite indepen-



5. This four-tube receiver, installed in a ograph cabinet and using the Flewelling it attracted much attention at the exhibit

dent in their programs. The post supplies the transmitting machinery and in return to the extent of half the shares. are, at present, nine broadcast companies in are, at present, nine broadcast companies in Germany with their stations in the main towns: Berlin (wave-length 505 meters), Breslau (418), Frankfurt (470), with re-lay transmitter Cassel (288), Hamburg (395), with relay transmitters, Hanover (296) and Bremen (279), Königsberg (463). (296) and Bremen (297), Kongsterg (485), Leipzig (485), with the relay transmitter, Dresden (292), Munich (485), with the relay transmitter, Nuremberg (340), Münster (410), and Stuttgart (443). A tenth broadcast company, with headquarters at Cologne, will be formed as soon as broad-casting is given free in the Rhinelands. The power of the individual senders varies

between 1 and 4 kilowatts, but preparations are being made to increase them to 8 k.w. and to interconnect them by cables so that, if required, the same program can be broad-cast simultaneously from several stations. Anybody may become a listener, the only formality being the payment of a license of two marks monthly at the nearest post



Fig. 6. Any number of different circuits n be connected by plugs and cords in t

150 feet, in the record time of three months, was quite an interesting architectural feat. The hall contains annexes for a special lecture hall, restaurant, recreation rooms, offices, etc. A special feature of the grounds is the enormous radio tower, a framework of steel 450 feet high, with an elevator to

Fig. 4. A neutrodyne receiver having two stages of radio freof audio fre-The indicating meters



office, of which amount the post retains 90 pfg. and hands 1 mark and 10 pfg. to the

companies.

The German radio industry is organized in an association, the "Verband der Radio-industrie" which forms a kind of learing house for the payment of the royalties to the owners of the different patents. They are charged according to the number of sockets built in the set, thus facilitating the most general application of patented devices to the best advantage of their owners, of the manufacturers and of the general public. There exists also in Germany quite a num-

ber of radio periodicals of high standing, the Deutsche Rundfunk having the largest cir-culation. It has its own laboratory and an advisory office where thousands of inquirers get assistance and advice.

PIRST EXHIBITION

Considering the handicaps under which the German radio world was suffering, the first radio exhibition in the fall of 1924 must be considered a great success. Twenty-four manufacturers exhibited and the number of visitors was 200,000, so that the radio association decided to repeat the exhibition every This year, after all restrictions have fallen, the products of the German radio industry can compete with those of other countries on equal footing, and special provisions have been made that this be done under absolutely fair conditions. Indeed standard acrials will be mounted in the hall and sound-proof cabins provided. The "Radio exhibition is being held again this fall, was built last year expressly to suit the special conditions of a radio exhibition. No steel or iron has been used in its construction. Brick and concrete and wood have been employed throughout so that no loss will be sustained through large masses of metal. The building of this hall, which is 400 by the top platform, in which will be installed a restaurant accommodating 200 persons. and receiving station are suspended.

Berlin is the center of the German elec-The majority of trical and radio industry. all concerns have their administration and shops there, which is one of the main rea-sons why Berlin has been chosen for this sons why bernin has been closed in this exhibition. Every manufacturer of consequence—dealers are not admitted as exhibitors—is represented, so that the exhibition gives a comprehensive idea of the development of the German radio industry. American radio experts who have recently visited the big wireless and broadcast stations at (Continued on page 544)



Fig. 2. A four-tube receiver employing the Reinartz circuit.



The Dife and Work of Lee DeForest



PART XIII

A FTER the patent rights to the threeclettrode amplifier had been duly sold for the sum of \$50,000, DeForest rashed back to his laboratory at High Bridge and started again his investigations, as of old. This had been his goal for some time, and back at the old routine again, wherein he could follow whatever lines of investigation he thought best, life some briefwester.

again brightened. As soon as possible, DeForest wired for Logwood to come on from California and did gladly. It was only a short time before the laboratory was in full working condition and things were again progressing as before. However, his fight with the ever-present experience of the control of the c

RALIO TELEPHONE CO. REVIVED

But as swiftly as possible he resuscitated the old Radio Telephone Company, opened

the our statio recipions company, opensating the control of the recently discovered oscillating audion. In the original discovery of the principle, of course, little had been learned of the characteristics of its operation, save that it was a generator of oscillating current. All the technique had yet ical and electrical details noted and put into shape for practical application. This was his first problem.

By the spring of 1914 things were again ship-shape and the laboratory was working on two very important developments in the radio field. The first was, or course, that just spoken of—the oscillating audion. The second was the construction of high frequency alternators with a quenched spark discharge for telephony. This latter part of the work was progressing with extreme randity and the laboratory engineers had



The first audion detector that the old-timers should remember.

succeeded in erecting a set which worked very well. The carrier frequency-the quenched spark discharge—was of such low frequency as to be audible at the receiver, but for the purposes of ordinary telephone, that is, the use of voice alone, an intelligible conversation could be carried on without the to operate at about 3,000 cycles.

For a number of months this field of investigation proved so profitable that some of the other engineers in the laboratory thought it held a great deal more promise than the audion in the rôle of generator. DeForest, however, did not think so. It held several important leads over the audion as it was developed at that particular time, though,

oevening at time pattern than time, toogge, of Cr course, the maintenance of the course of the conclusion and the treeping of are and other undamped of the treeping of are and other undamped on the course of the

In April of that year DeForest thought the time was ripe for submittal of the device to the Bureau of Standards. Accordingly, he sent them one of the instruments and it was put on exhibition.

Another step in the advancement and perfection of this development was reached when DeForest took two of them and set them into oscillation, at the same time connecting their output circuits to a load speaker. The two high frequencies which were generated, of course, caussed a beat note which could be plainly heard in the load speaker.

NAVY INSTALLS AUDION

It was shortly after a public demonstration of this stunt that the Navy became interested in the apparatus and desired complete data and information upon the construction and operation of sets using the
DeForest audions. The demonstrations were
a success and the Navy immediately ordered a
success and the Navy immediately ordered in
diversity as the socillators were called.

"diversity as the socillators were called.

With the constant advance of the mechanical staff in the manufacture of the conical staff in the manufacture of the conperior of the control of the control of the conference was able to take to London with him the first 110-volt Oscillion, as he called the oscillator and a husby tube for commercial work. It was so good that water had to be used for cooling it while in operation. Here a note must be made of a fact which

has been too little atreased all the way through this treatise. It is that DeForest allows—without a single exception—took each Nawy for their examination so that they could be included in the defense and arms, Nawy for their examination so that they could be included in the defense and arms, and still seems, to be a sort of religion with him. Though he has received little of the proper recognise of the comment the fullest co-operation in the use of his apparatus.

The case just cited above of his giving the Navy and Army all the help they desired in connection with the Oscillion is just another case in point of the property of the Navigary of the Navi

operation, a word might be added about the catering of the various DeForest Compaiors to the amateur trade. In each of the organizations—and DeForest had a number of different companies at different times—the commercial heads insisted that there was absolutely no money in such small mail order business, and each time the charge was made, DeForest tried to explain that the idea was



One of the first three-step audio frequency amplifiers.

not to make money, but keep the experi-

menters interested and to give them all the help possible in their hobby. The commercial entourage thereupon always showed the same lack of understanding, but allowed catalogue to be issued, just to please the Doctor. This was particularly the case after the commercialization of the audion. There was

to be issued, just to please the Doctor.

This was particularly the case after the
commercialization of the audion. There was
no end of trouble in manufacturing it and
the company had little capital to spare for
stock on hand. DeForest, however, put up
the usual fight and finally caused the directors to issue the usual catalogue.

PANAMA-PACIFIC EXPOSITION Another of DeForest's penchants was the

attendance of himself and his company at all expositions of world-wide interest. So, of course, plans were made—and rather complete ones—for the exhibit which was to be held at San Francisco, the Panama— Pacific Exposition. And thereby hange one of the most interesting episodes of the relations between DeForest and the telephone

But fet us parenthetically state that this diaction for expositions may be well discrimed by the state of the

Biography recorded by W. B. Arcin of Radio News, under the personal direction of Dr. DeForest. Copyright, 1925, by E. P. Co.

had made the accomplishment possible-the The most important publicity vessel of the booth was a little booklet entitled, Story of a Great Achievement." It set out simply how the engineers of the telephone company had been striving for a long term of years for the thing which had just been done, and then went into some mechanical details as to how the thing was done, giving not the slightest reference to the audion amplifier.

As one might well appreciate, this made DeForest furious. He took one of the books, that he need hope for little recognition or praise for his portion as inventor of the tubes. He had some business in Europe

He reached Paris a week before the scheduled time for the test. He set every agency at his command working to the result that when the tests were completed and the stories of it given the papers, the name of

the inventor of the oscillating audion was well up in the first few paragraphs. DEFOREST AIDS FRENCH

Of course the war was on at the time and communication was one of the most important things in the successful perpetration of a campaign. The radio engineers of the French Government came to DeForest for help and he gave them the fullest cooperation. It was during this period that one of the greatest Zeppelin scares was harrowing the hearts of the non-combatants at DeForest, knowing the characteristics of the transmitted sound of the Zep engines, set to work to find some means of protecting the cities and villages by the simple expedient of giving them warning long enough in advance to seek safety. Finding a microphone in his trunk, he fixed it in the small end of a huge megaphone and ran the leads of the "mike" to his three-





sat down that evening in his hotel after the closing of the exposition and wrote his own story of the great achievement. The following morning he paid the printer a visit and succeeded in getting his own book printed. The completed pamphlet was so similar to that given out by the telephone company that were almost indistinguishable—from -very different, indeed. It went into great detail as to the use of the vacuum tube as an amplifier of telephonic currents and told just the location of the various relay stations and explained thoroughly the problems which confronted the engineers for years and which same had been solved by the DeForest three-electrode vacuum tube. These were distributed as freely as those the telephone company. The day was

of the telephone company. complete, for DeForest had given himself at least an even chance.

This, however, did not complete the fight. Late in the summer, DeForest returned to New York. In the radio and engineering circles, there was afloat at the time a rumor that the A. T. & T. was contemplating and preparing for a telephonic test between Paris and Arlington. DeForest knew immediately that the one logical way for them to carry out such a scheme was through the agency of the oscillating audion. A further inquiry revealed the fact that the Western Electric Company had, during the past few months, manufactured more than 150 of these tubes.

DEFOREST IN PARIS Putting two and two together, he decided immediately that they were intending to use a bank of the oscillions for the purpose of creating the necessary carrier wave for the transmission of voice across the Atlantic. A further investigation at the source of the stunt, the telephone company, revealed noth-DeForest knew from past experiences with a swivel joint so it could be rotated This arrangement allowed the Zeps to be detected and located several miles further away than they had been before with only the agency of the horn. While on his trip and helping the engineers

of the Army, he found time to introduce the audion amplifier on the Continent for the first time. He had his standard one-, twoand three-step amplifiers with him and made

First work he and w to work on beterodyne most out point patent Page from DeForest's note-book with data on audion tube used as a detector,

public demonstrations before all the engineering societies and schools. He was in France until December of that year.

PROBLEM OF VACUUMS

At home, the work had been progressing very nicely. After the completion of the 110-volt tube, the problem of a vacuum had arisen. The engineers were constantly seeking to put more and more power through the tubes and found constantly that an increase in the voltage on the plate above a certain point invariably resulted in paralysis of the tube. This phenomenon was always accompanied by a bluish glow in the bulb This glow was attributed to ionization of the gases remaining in them after the ex-haustion process, so the only solution was the manufacture of tubes with a higher

Commercially, this was quite a problem. There were few plants in the country equip solved the problem by erecting their own glass-blowing plant and installing their own glass-blowing plant and installing their own vacuum pumps with the necessary equipment for making and mounting the elements of the tubes. Soon after this plant was put into opera-


tion some large oscillators were built. It was then that DeForest and his assistants first felt that the time was at hand when the vacuum tube would indeed turn the radio industry into a new and much advanced channel. The whole art was to be revised. the old technique was about to pass and a new era be ushered in. DeForest saw in the very near future the adoption and completion of his dream-radio broadcasting.



One of the first types of the DeForest un-damped wave oscilla-tor. A large number of these instruments were supplied to the U. S. Navy for use as local oscillators for dyne recept periments.

Radio Stereophony

By LUDWIG KAPELLER

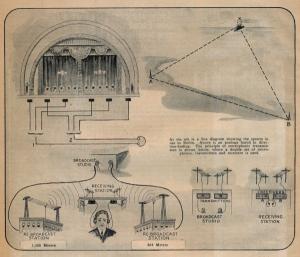

With most important goal in radio recipion is perfect reproduction. Many of the other tasks in reception have been accomplished, but a yet recopion in most perfect that is the perfect that it is the perfect that the perfect that is the perfect that the perfe

PLASTIC TONE REPRODUCTION

Many a radio fan recently, instead of referring to hook-ups and tube characteristic curves, has muffled his loud speaker with cloth or his headphones with wadding in cloth or his beadphones with wadding in cloth or his property of the property of

to the loud speaker and headphones simultaneously and, all at once, may have become aware of an incomparable improvement in reproduction. The music seemed to be more plastic and more alive—he had discovered for himself the principle of plastic tone re-

As a matter of fact, this invention is about furty-five years old—only four years younger than the felephone. On August 30, and the property of the property o

this absolutely modern arrangement only by

performance. However, this opinion is invalidated by the following lines in the patent: "This double listening to sound, received and transmitted by two different sets of apparatus, produces the same effects on the ear that the steroscope produces on the eye." That Ader was aware of the fact that this arrangement was the invention of sterophony is indicated by the patent draw.

Beitier, Ader points out certain features of the Ries merculosus, the special advantage of the Ries merculosus, the special advantage of the Ries and the Ries an

A number of European telephone companies provide special service connections to important music and opera halfs and theatres. These lines are permanently connected direct to the subscriber.

A ONE-FARAD CONDENSER

Comparative Sizes of a One-Farad Condenser and the Woolworth Building

HOW WOULD YOU LIKE TO OWN A 117.300 PLATE CONDENSER?



To tell the truth, whether a farad is large or small depends a great deal on the way one looks at it. When Gulliver went to the island of Lilliput he found the pygmies which he called Lilliputians. They looked exceedingly small to him, but to them, Gulliver was a giant of size heretofore unimag-

But when Gulliver went to the land of the Brobdingnagians he looked as small to them as the Lilliputians looked to him. So it is with the unit of capacity—the farad. The farad was defined originally as the capacity of a condenser which could hold a clarge of one coulomb of electricity and at the same time have a terminal voltage of one

Such a thing, however, is impracticable, so we have imagined the farad as divided into a million equal parts and have called each part a microfarad. Even the microfarad is rather large, so we have further subdivided it into another million parts, giving us the micro-microfarad.

We are accustomed to dealing with the microfarad in radio calculations, so the farad looks enormously big, just as the inhabitants of Brobdingnag looked to Gulliver. On the contrary, if we were accustomed to such a thing as the farad, the microfarad would certainly appear insignificant.

Take the 0.0005 microfarad condenser, for example. This is 1/2,000 of a microfarad, so that it would lake 2,000,000,000 0.0005 mf. condensers to make a farad of capacity.

On the other hand, suppose we wanted to build a one-farad condenser, and for the sake of argument made the area of each plate nearly equal to the ground area of the Woolworth Building shown here. Suppose also we wanted it to equal the height of this famous building.

In that case, there would be required 117,300 plates, if these plates were spaced 1/25 of an inch apart, and were 1/25 of an inch thick. The height of the condenser would be 792 feet, the same as the Woolworth Building, exclusive of the end-plates and dial.

It is well known that a sphere is a condenser. To show how extremely large the farad really is, it will be well to note that the capacity of the earth, assumed to be a perfect sphere of conducting material, is about 72/100,000 of a farad or 720 micro-



Superpower

POWER GENERATING PLANT.
These powerful generators supply the
power for the transmitting station at the
Schenetady plant of the General Electric Co. The buss bars for carrying the
current to the transmitter may be seen in

POR the past six months there has been a great deal of discussion in the radio and general per discussion in the radio and general per discussion. For the most part it was mere discussion, sprinkled hera and there with an account of some new station adding a few kilowatts which brought its total power to a possible five or six kilowatts.

At last we have the real thing in supersome solution and the first week in August the writer visited, with a number of other technical writers and correspondents, the new superpower station of the General Electric Company at Schenectady, New York.

SUPERPOWER STILL EXPERIMENTAL

Although the new, powerful transmitters are installed and in working condition—in foregraph and the property of the property o

It is the object of the technicians to settle these questions scientifically and finally through the new installations and the reports

of their operation.

The whole question of superpower is bound up with propagation formulas, wave forms and the comparative efficiency of the added power as compared with lower output. The limit of reception is set, strangely enough, by the noise level and the static level. The power of the received signal must, in all cases, be an appreciable per cent. above the societatatic level for the program to be re-

The second consideration, and probably the most important one, is the mathematical quantity in the transmission formula which is called the "attenuation constant" and governs the amount of effective signal at any office the second of the wave-length need and other constants. On the wave-length need and other constants the second of the wave-length need and other constants the wave-length need and other constants the wave-length need and other constants the transmitter of the best of the second of the

This is a field which is still more or less new—that is, there is not a great deal definitely known about it—and the new stations, among other things, hope to discover more about it.



Broadcasting



meters and is equipped to care for a maximum output of 50 kilowatts and a second one which broadcasts at 1,560 meters and is capable of putting 40 kilowatts into the

antenna. All programs for these stations will come through the regular WGV studio control and are transmitted from the Scheeckedly station are transmitted from the Scheeckedly station. South Schenectadly. Here the land line current is first steped up through a small amplifier and then delivered to the station modulator panel. This unit consists of three banks of modulators, each consisting of two annulier rules to brine the stimula to mooter. amplifier tubes to bring the signal to proper

As to the stations themselves, the accompanying photographs give a pretty thorough idea of the size and scope of the equipment. The transmitters are all of the master oscillator type and employ the 20-kilowatt, water-cooled tubes. The buildings containing the transmitter and the antenna are placed sev-eral miles out of Schenectady in order to minimize the interference in the shock excitation area around the transmitter. It is citation area atomic the transmission of fairly certain that all superpower stations erected will follow the same plan of erection at some miles from the populous centers which they are supposed to serve.

There are two main transmitters, which operates on a wave-length of 379.5 ANELS. At these panels the enormous power that used for transmitting is regulated.

intensity for placing it on the grids of the

large tubes.

By an extremely flexible arrangement of connectors, any one of these panels, any selection or combination of them or all of them may be used in conjunction with any one of the transmitters.

One of the accompanying illustrations shows this arrangement. The three rather open units house the water-cooled tubes and open units house the water-cooled tubes and the necessary transformers and step-up tubes, the connections and the grid-biasing leads. The two solid panels at the side are the ter-minal boards for the land lines coming in from the studio in Schenectady. All high frequency leads and con-nectors in oscillating or high tension circuits (Continued on page 558)



Parlor Magic with

ways arouse the suspicion of the party to

If a metallic chair is used, one wire from the loud speaker is run to one of the chair legs and connected with it. This may be legs and connected with it. This may be done under a rug or carpet so the connection will not show. In this manner, there will be no possible suspicion and the surprise effect in consequently heightnend. The other end of the cord from the loud speaker goes to of the cord from the loud speaker goes to the 'phone plug, as shown, while the other pole of the plug connects to a cord or wire, which may be wrapped around a spoon or other metallic object, in order to make good contact with the performer's hand. It will now be seen that if the performer kisses the lady's hand, providing the radio set is turned on and there is a station going, the instant he touches the hand, the music, or whatever

sue from the horn. In this experiment through the performer's body, thence through the lady's hand and arm, while her through the ladys nand an arm, while ne-other hand or arm is grounded on the chair, from which part of the current goes back to the loud speaker, thereby completing the circuit. It will be noted that music can issue from the horn only so long as contact is made between the performer and the one is made between the performer and the entertained, nor is the music or sound we ened, as a rule. So long as a good con is made, the high frequency currents readily through the body, almost as if the were a solid metallic connection through
As a rule, the lady being entertained
be skeptical that it is the contact between
the skeptical that it is the contact between the skeptical that it is the contact between the skeptical that it is the contact between the skeptical that it is the contact between the skeptical that it is the contact between the skeptical that it is the skeptical that it i

program there is from that station.

she is, just ask her to touch your face or your hand herself. At every contact thus made, music will, of course, be heard. An added interest is given the experi

by touching a sensitive part of the subj face, such as, for instance, her ear, or lips, lightly with the finger. If a 3-0

Using your radio outfit for parlor magic and novelty stunts is a brand new idea. In this article the author shows how your set can be used to entertain your friends in an entirely novel manner.

HOSE of you who think that a radio receiving set is good only for listening to the various broadcast programs are mistaken. Aside from giving its customary entertainment, a radio outfit, under certain circumstances, can become an excellent en been described before. Many variations may be made, and we now have a new source of entertainment from our versatile

In order to perform any of the experi-tents and entertainments herein described is necessary to have at least a 3-tube, or, it is mecessary to have at least a 3-tube, or, better, a 5-tube set. The first stunt, which never fails to evoke surprise, might be termed "The Radio Kiss" although this may not be an exact name for it. It is shown as our front cover illustration, as well as in illustrations Nos. I and IA.

In the first entertainment it is necessary have for the surprise element a metallic iron chair is of the garden variety, and while it is not so evident in cities, most country houses boast several of them. In order to make the experiment, it is necessary to have a metallicly conducting chair. Should it not be possible to get a metallic chair like the one pictured, then the next best thing would be to get an ordinary wooden arm-chair, and fit it with metallic handles, arm rests, or otherwise way at the presence of the coniron chair is of the garden variety, and while rests, or otherwise wrap tin—or copper-foil
—around the arm rests, although this is not
quite so good, because such a chair will al-









Your Radio Set

GERNSBACK Physical Society

tube set is used, a slight tingling sensation will be experienced, which, if the set is powerful enough, will sometimes be felt as har mless little shocks, such as are given off by a week shocking machine. This occurs only if the touch is very light. If the finger is pressed solidly against the skin this effect will not be noticed.

3f ourse the entire suggests of this way.

of course the entire success of this experiment hinges upon the "victim's" not seeing the one wire running to the performer's body. Variations of this can be made as

The performer may have a few short and it men through his shoes, in which case a like the performer may have a few short and it run through his shoes, in which case a like the performance of the mails. Then metallic plate may be put of the mails. Then metallic plate may be put of the performer has then only to step upon the control of the performer has then only to step upon the performer. The will be very mysterious and afford an are made good contact with the brass plate. The will be very mysterious and afford and make good contact with the brass plate. The will be very mysterious and afford and make good contact with the brass plate. The will be very mysterious and afford and make good contact with the brass plate. The will be very mysterious and afford and make the performer. It a wooden chair contact with the performer. The wooden chair arm extent and line and that the breath the performer than the performer than the performer than the performer. The wooden chair many the performer than the performer

in silent.

[Illustrations 2 and 2A show another valiety of the same idea. Here we have a number of persons connected in a chain in (Continued on page 559)

Fig. 3. When kid gloves become a radio head-set. In this experiment the performers grasp the two bare wires coming from the radio set, while their gloved hands are held over the histener's ears. She will hear the sounds as well as well as






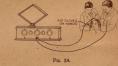


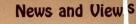

Fig. 4A

Fig. 4. Here we have a variation of the experiment shown under Fig. 3. Perhaps you do not believe that two sheets of letterhead for the property of the property of the property of the property of small if you don't believe it, try it and you will have the surprise or your life. Here we have the two performers granging the two wires coming from the raidle set, while their bare hands rest against we alterheads presented tiphily against the young below as the property of the property of the property of the property of through loud and clear with no distortion, and fully as well as with a good beadest. The principle, by the way, is that of











of Station WRNY

THE REMOTE CONTROL EQUIPMENT. In the suitcase on the left are the two microphones, phones for monitoring and "A" and "B" batteries, and in the right-hand value is the voice amplifier unit, for amplifying the signals before they are sent over land wires to THE Cobe plus on the left at WENY.

shows the power amplifier and transmitter.

THE TRANSMITTER AND CONTROL PANELS. In the transmitter can be seen

BATTERY-CHARGING PANEL. This panel, which was built by the station's staff

THE TRANSMITTER AND CONTROL PANELS. In the transmitter can be seen the large tubes and tuning apparatus and on the right is the panel on which is mounted the apparatus which controls the motor













The Times Flies

were two things that classified those two and set them apart from all other radio and editorial men I have ever seen. They had the worst bad luck followed by the best good luck and the greatest pro-

clivity for doing the unsuspected that ever blossomed in a couple of ordinary, every-How Michael H. Muldoon and Isadore Schwartzberg ever struck up the fellowship which kept them together for the long term of years I do not know. No matter what

the circumstances, they could not have been matched better had they had the same god-Of equal mystery is how they let themselves into radio.

thereby hangs this tale. But it does not alone hang on their falling into radio. Had it not been for the Old Man-otherwise the Skipper, officially known as the Publisher and Managing Editor of the Holden Times-and his enthusiasm, which was as unlimited as Einstein's space, and his unboly craving for something to fill the front page on Monday mornings, Micky and Izzy would probably not have pulled the stunt of the ages, as the head-ines called it, cost the Old Man the loss of his dignity and themselves three

good nights of sleep. Life had been rather uneventful-o uneventful-for some time and so Michael and Isadore were seriously considering a change of climate and working conditions. But before they could raise the proper will power and the money, radio came along. That is, the Old Man dealong. That is, the Old Man de-cided that radio would be a grand and glorious scheme for the increasing the circulation and thereby the

advertising rates. He informed Izzy and Micky they would be, on and after the following Monday, the editors of the paper's regular daily radio section and also the Sunday radio supple-This was, of course, nothing extraordinary, for most newspapers have radio editors recruited from all sources, including the copy boys and the linotypers.

But this pair differed very much from the usual run of pre-empted editors, for Izzy had a grander fund of usually useless information than any other man in nine states, and Micky could, under the proper stimulus, and Micky could, under the proper stimulus, do himself fairly noble writing about any-thing, whether he was conversant with the exact facts or not. Izzy could talk with fair case on anything from Pleistocene Man to the latest method of carbonizing steel. Micky could, likewise, tell a tale over the dinner table, after the coffee, which would

equal and ofttimes surpass anything of Jules Verne or Baron Münchhausen.

At once it becomes evident that they were the ideal journalists to edit a good, up-andcoming radio section.

Once they had started on the job they Once they had started on the job they became interested in it. The week-end after they had been given the assignment, Izzy spent several hours in the anottum of his room at Mrs. Brady's Elite Private Hotel with several heavy tomes, which, according to their prefaces, told thoroughly the tale of radio. After the had absorbed Flemming, a bit of Van Der Bijl and some miscellantermatics, he came into the office on Monday.

matics, he came into the office on Monday

morning with a new glow in his eye and a

new enthusiasm in his heart. With Micky, the situation was somewhat different. He read a couple of Jules Verne's accounts of exploits in the various sciences. He topped it off with some stories in the popular magazines and read one or two simone syllable, with a demi-tasse of Radio News. He, also, was under the impression that he was a thoroughly capable radio edi-

During the following week Izzv built exactly five radio sets. Four of them worked. The first ones were rather amateurish in their appearance and little more could be said for the operating characteristics. By the time he had completed and put into oper-(Continued on bage 514)



The Vacuum Tube and Photo-Electric Cell

By GENERAL GUSTAVE FERRIE



The author of this article is one of the world's foremost

authorities on radio tubes. In this article he describes several new and interesting applications of vacuum tubes.

HE developments undertaken to perfect radio electric devices, and in vacuum tubes, have found very effective and numerous applications in various

departments of science.

We shall describe briefly certain arrangements associating the properties of the three-and four-electrode tubes with photo-electric cells, particularly in connection with certain optical applications, and then discuss some

of these latter. It is not necessary to review here the characteristics of three- and four-electrode vacuum tubes, which are well known, but it will perhaps be useful to recall very briefly

the properties of photo-electric cells.

When light is allowed to fall on a surface covered with a light-sensitive metal and placed in a vacuum, it produces an emission of electrons whose intensity depends upon the quantity of violet rays in the beam di-rected on the surface. Potassium, in particular, gives very interesting results,

The apparatus utilizing this property, notably those which were designed by Mr. Rougier of the Strassbourg Observatory, were constructed as follows:

On the interior surface of a glass bulb, A, (Fig. 1) a layer of potassium is deposited except on that part of the surface forming a window through which the light enters. The wire, f, sealed in the glass, makes contact with the potassium. In the center of the bulb a wire loop, p, is mounted, insulated from the



a second wire, f, also sealed into the glass.
Under the influence of the light the potassium emits electrons. When it is connected central loop being connected to the positive pole, the latter attracts the electrons and a current is established in the battery surface. This current persists during the time that the cell is under action of light. In addition, this effect is instantaneous or at least takes place in an extremely short period.

The effect can therefore be used to determine the beginning of some luminous phenomena. The current of a very low intensity is increased by introducing argon gas into the bulb under a pressure of a few millimeters. The electronic current is then increased through ionization by collision. But even for very intense illumination it never reaches a current of a microampere. In order to utilize this current practically, it is therefore necessary to amplify it a great deal.

One means of amplification consists of in-

creasing the potential of the batteries con-







Fig. 2. How the photo-electric cell is used in conjunction with a standard three-element vac-uum tube for amplifying the variations in light

nected between the potassium and the anode of the cell. This method, however, is limited practically to about 150 volts, for above this value there is a risk of producing the glow discharge on the inside of the cell, and even of causing discharges capable of seriously damaging the cell. In order to achieve the



matically in white box, which can be seen through the of the passage. The light is then reflected to the floor above, where it is put

4 Relow

of the two-grid tube occurs when its plate current (with the photo-electric cell dark-ened) is about 0.5 milliampere; an intensity which falls to zero when the cell is powerfully illuminated. When the illumination is insufficient or when the variation in current is too feeble to actuate the measuring instruments, it is necessary to add a supplementary amplifier. Two or three tubes with three electrodes could be connected in parallel in case of necessity, instead of one,

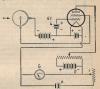


Fig. 3. By using a vacuum tupe naving too grid elements, a lower plate voltage can be em-ployed than with the standard three-element tube, so facilitating the use of the photo-electric cell.



With a three-electrode tube (Fig. 2), the anode, a, of the cell is connected to the grid of the tube. When the cell is illuminated, the electrons emitted by the potassium charge the anode connected to the grid.

Because of this charge, the grid acquires a small negative potential with reference to the tube filament which produces a large diminution of the plate current. It is this diminution which is utilized instead of the photo-electric current itself. Since the threeelectrode tube is not completely evacuated, the electrons emitted by the filament produce ionization by collision with the gaseous mole-cules which remain in it. The positive ions so produced will partly discharge the grid whose remaining potential will be consider-ably smaller than that considered above. In order to avoid this diminution of potential it is necessary to prevent the formation of positive ions, and to this end to reduce the positive ions, and to this end to reduce the plate voltage to a value below that of the ionization potential of the gas; that is to say, to about 20 volts. The consequence of this diminution in plate voltage is unfortunately a considerable reduction in amplifica-

The difficulty disappears on making use of four-electrode tubes, which do not require a plate voltage higher than 20 volts. The circuit is indicated in Fig. 3. A potential circuit is indicated in Fig. 3. A potential of 6 volts is applied between the first grid and the filament. Everything happens though the electrons were emitted by the first grid. The latter being extremely close to the second grid, the tube has a very high co-efficient of amplification. In order to obco-efficient of amplification. In order to obtain the best possible operation, it is necessary to use a potentiometer in connection with the battery, P, in such a manner as to enable an accurate adjustment of the plate voltage. The measuring instrument, G, is brought to zero by a battery, p, and a re-sistance, r. It is possible to obtain with such arrangement of a single amplifying

tube, in cases of intense illumination of the cell, sufficient action to effect measurements by means of a needle galvanometer giving a by means of a needle gavanometer, group a maximum deflection of one milliampere. (This arrangement of galvanometer, battery and resistance is the "zero shunt" described by Dr. Bazzoni in the July, 1925, issue of RADIO NEWS.—Editor.) It is generally necessary to increase the amplification by tube, connected as shown in Fig. 4. periments show that the maximum sensitivity

in order to still further amplify the cur-rent. Under the influence of a sudden illumination of the cell, the movement of the needle of the measuring instrument is always very sudden and rapid, while the return to normal position after the light is cut off is very slow. This is due to the negative charge collected by the second grid of the first tube, a charge which can be dissipated only slowly because of the high in-sulation. If this charge is very much re-

(Continued on page 540)



The giant telescope in the French observatory to which is attached the photo-electric cell apparatus used in astronomical observations and calculations.

he Inventions of Reginald A. Fessenden

HE financial difficulties of the Edison Machine Works at Schenectady and of the Edison Light Companies, which were the cause of their inability to continue to pay for the solution of commercial problems by the Edison Laboratory, were not straightened out until 1892, when Mr. C. A. Coffin, a man who had demon-strated very exceptional business ability, first as a shoe manufacturer and then in connection with the Thomson-Houston Comany, combined the Edison and Thomson-Houston Companies to form the General Electric and quickly transmuted the semibankrupt aggregation into an extremely sound and profitable organization. VACUUM BOILED VARNISH

But, in the meantime, a number of us had

to look for work elsewhere, and the date of my wedding with Miss Helen Trott had been set for Soptember, so it was necessary to act quickly. About a year before, Mr. had come to Edison in connection with some trouble he was having with blackening of varnish gums. Edison, busy, had sent him down to me. In connection with my work on elasticity, referred to in my preceding article, I had distilled great numbers of flexible and elastic substances, including fossil gums, in vacuum and under pressure, and had formulated certain conclusions as to their behavior, decompositions, etc. So I was able to show Mr. Pratt at once how to remove the blackening of the gums, and also how he could use the cheaper Zanzibar fossil gums in place of the more expensive copals, and at the same time get clearer, tougher harder varnishes.

About a month later Mr. Pratt had called again, after consultation with his partner, to offer me a one-third interest in his com pany, guaranteed at not less than \$10,000 per annum. This was a munificent offer, for \$10,000 then was equivalent in purchasing power for rent, clothes, food, etc., as my house account books show, to \$40,000 now, and I suppose any sensible man would have accepted it. But I wanted to continue my work with Edison, and have never regretted times it has seemed to me that it might have been more fair to my wife if some of them had been accepted, but, on the whole, I think not. The richness and fullness of life depends on the amount and character of its experiences. My dear mother used to say that the only difference between a rut and the grave was that the rut was longer. And I am quite sure that the years of good, clean hardship, of wide experience and varied in-terests, together, effect a welding between husband and wife which is the best personal thing that life can give; and that early mar-riages and simple living are best.

WESTINGHOUSE COMPANY

The position in the varnish works had, of course, been filled by the time the Edison companies difficulties came to a head, and though arrangements could no doubt have been made with some of the other varnish companies, there was the feeling that more practical experience in the design of dynamos and other electrical machinery was to be sought, to round out the mathematical studies. A position as assistant to J. F. Kelley, electrician for the United States



A quaint instance of the type of electrical machinery employed at the time shortly preceding the period of which Professor Fessendem writes in this article. Company, the eastern branch of the Westof nitrocellulose for lamp filaments.

inghouse Company and which handled all the D.C. work of that company, offered the opportunity. Zimmermann was the general manager, a very able man. Nassoy, the shop superintendent, was also very capable Kelley was brilliant and remarkably well up in his subject. He would have made a name for himself had he not been interested almost solely in sociology and rather disin-clined to take trouble. He seldom came into the laboratory, leaving me entirely to plan and carry out the experimental work.

SAWYER, MANN, MAXIM, WESTON, CHESNEY, STANLEY The incandescent and arc lamp work had

been taken to Pittsburgh, so part of the sold the Westinghouse Company a type of are lamp, applied for a portion of the space, to develop an arc light machine. While not an inventor himself, Stanley was a very good business man and had several very able assistants, notably Mr. C. C. Chesney, now head of the General Electric Works at

The laboratory, of which I was given charge, was one of traditions, for Sawyer and Mann, Maxim and Weston had worked there. Sawyer and Mann had been among the first to use carbonized paper for incan-descent lighting, but failed to make a practical lamp, and, still more important, failed to discover the method of "subdividing the electrical light," which formed such a problem to the early workers, and which Edison solved by making the lamp have a very high resistance, so that but little current was needed per watt, and so the amount of copper needed for the distributing mains was reduced to a practicable amount.

Maxim, later the inventor of the first practical rapid-fire gun and of cordite, the first practical nitrocellulose rifle powder, and who did some very important work on fly-ing was. I believe, responsible for the

Weston, the greatest of them all, had worked out a system of electroplating which was long, and still is, used. Also an efficient type of dynamo and an extremely efficient arc lamp. But his great work was the invention and perfection of electrical instru-ments, in which field he occupies the eminence that Edison does in that of electrical measuring instruments prior to his work is almost inconceivable now. I think it safe to say that the average error then amounted to 7½ per cent, in commercial instru-ments. By elaborate research and experiment Weston produced a type of iron alloy which, after "aging" by a method he dis-covered, would retain its magnetic strength unchanged by shock or temperature variation. He then produced copper wire in a pure state, and free from the minutest trace of iron. Then by refinements in construction, a new type of jeweled bearing, etc., he finally gave electrical engineers D.C. voltmeters and ammeters which could be depended upon to within to of one per cent. instead of the 5 to 10 per cent. previously obtainable.

MANGANIN AND THE WESTON CELL Since the resistance of the copper wire

changed with temperature, the circuits of his instruments had to be kept at the same resistance by some means. He did this by discovering an entirely new alloy with hitherto unheard-of and at first unbelieved an entirely new alloy with properties, i. e., one whose resistance diminished with temperature instead of increasing This he called manganin, but it should be called "Weston." Then as a standard of voltage he invented a standard cell which did not change its voltage with change of temperature. Later he produced the first satisfactory A.C. instruments.

This work made possible, for the first time, the accurate commercial measurement of electricity, and it is of interest to note that all the steps are due to one man.

This autobiography copyright, 1924, by E. P. Co. All rights, including that of translation, strictly reserved.

The first thing done was to put the laboratory, which had been allowed entirely to run down, into shape so that quantitative measurements could be accurately made, for quantitative work is one of the main secrets of success in inventing. Then after solving some bearing metal problems, the matter of insulation came up. Shellac and nitrocellulose varnish and japan were in use then, and the dynamos would not stand up, as the shellac, etc., cracked and became hydroscopic-Here my researches on oils and gums came It had been of course evident to many linseed oil would be suitable if it could be dried quickly and would still insulate. But the raw oil took weeks to dry and when driers were used it would not insulate. So at the Edison laboratory our practice had been to dip cloth in oil, hang up for two or three weeks in a warm room, and then cut

the cloth into strips for use.

But dynamos in those days were not coil
wound, so this could not be used in place of
the shellac, japan, etc., as the dynamos could
not be held up for weeks for drying.

The first step, obviously, was to see why, the chemical driers, lead oxide, etc., spoiled the insulation of the linseed oil when used. This was soon traced down to the formation of hydroscopic or water soluble metallic soaps, by the union of the driers with the oil. All the driers used appeared to form such soaps. It was then noticed that one or two substances which had not been used commercially the control of the driers with the oil.



Fessenden's early theory of the structure of matter explained the hysteresis of iron by the irregularity of the stores filling the interatices bethe hypothetical structure of carbon steel. The irregularity of the carbon atom is here supposed to hinder the free magnetic alignment of the iron (Te.) atom.

cially as driers, particularly borate of mangamese, acted, even in minute quantities, very actively. From the work done in developing my electrostatic doublet theory of cohesion the conclusion had been reached that cohesion and chemical union differed only in the presence or absence of ionic charges, and that, to quote from my paper before the Newark Electrical Society in 1890:

The difference between cohesion and chemical combination is that in cohesion the atoms are charged similarly in every way substances short-circuit the atoms they become chemically combined. This is the explanation of a law which will probably be found on the combination of the combination of the comsistence can combine without the presence of a third, thus making all chemical combinations the result of catalysis; plexed forms of the substances being capable of

Borate of manganese then (and others of this type discovered later) was simply a powerful catalyser for coxygen, and might give a dried oil having high instalation. It dynamos could be wound and soaked with this borated oil and placed in a drying oven and the oil would dry in a comparatively few hours. By the addition of suitable gums in proper proportion, determined by experihistly instalating cloth and take was obhistly instalating cloth and take was ob-



On the basis of Fessenden's theoretical considerations, it was shown that iron alloyed with some element whose atoms were larger than the iron atoms and which were nearly spherical street, and the street was the street and the street was street. That the conclusions derived from Fessenden's theory were valid is evidenced by the high magnetic efficiency of silica iron.

tained, similar to what is now known as Empire cloth, which proved very durable, samples now 35 years old still being apparently unchanged.

The results were in a way almost too good, for Nassoy came in one day and complained that it was cutting down the profits of the repair department as of all the dynamos insulated this new way during the past year only two had come in for repairs, and one of these had been an built up covered this loss many times over and orders came in so fast that there was difficulty in filling them.

INSULATION FOR DYNAMOS FOR MAKING ALUMINUM

Hall had invented the first practical method of making aluminum by electrolysis, the method which is used today. We got orders for the dynamos. These were low voltage, about 30 volts if I remember, and which was a large dynamo in those 200 hp., which was a large dynamo.

The overload was at times excessive, amounting to a short circuit, and the mechanical stress on the windings was very high. It was clear that no organic insulation would I had noticed some years previously if cord made of pure asbestos was soaked in silicate of soda, dried and heated, the whole turned to a sort of opaque glass but retained a certain degree of flexibility, and of fair insulating quality. I gave instructions that the large copper straps, three or four inches deep and about a half-inch wide, should be insulated in this way and laid in their grooves in the armature sheets, and the dynamos shipped so. This horrified the testing department, accustomed to measuring dynamo insulation in megohms, espeof several hundred lamps would light up between adjacent windings. However, an inventor must never be intimated by what appear to be facts, when he knows they are not, so the dynamos were shipped and nothing heard from them, except orders for two more, and the report that they worked all right, but that the brushes used to get red

JOB ORDER SYSTEM. BALDWIN LOCO-MOTIVE WORKS


The new types of dynamos and motors were parting on the develooper problems which could not be solved on the develooper problems which could not be solved or give the development of th

and the quite undesired result was that in a very short time they were sending me all over the country to doctor up financially sick plants, and this cut very badly into the time available for scientific work in the laboratory. About this time also I introlatoratory, about this time also I introoffice, what I called the "lob Order" system, which later came into general use in works, as it enabled jobs to be kept track of much better than with the old classical system of

accounting.

The discounting certaide jib was at the Definition of the discountive tworks, which had in-stalled our motors on some new 100-ton careas, much larger than anything previously used, and had hought some compound dynamics of the discounting the

he save it? Looking things over and making a few calculations on the emissivity of the steam pipes used in carrying steam to the great number of small engines scattered all over the plant and on their efficiency, etc., I told him that the only way was for him to throw out all his steam drive system, as two-thirds of the steam energy was being lost from condensation and from the inefficiency of the small engines, and that he should put in motors driving groups of machine tools and furnished with electricity from large dynamos and engines located next the boilers. He asked how much it would cost. I made careful estimate, an appalling amount But Vauclain was game, and asked me to work out the details, offered me the job of superintendent of motive power for the works at four times the salary I was getting, and when this, with real regret, was declined, told me to take the matter up with my company and to tell them he wanted such a plant put in. This was installed a few years later and I had the satisfaction of seeing Vauclain's statement, in his paper on the working of the big electrical drive on the working of the one of the which he had had the nerve to put in, that it had saved him over 60 per cent. of the (Continued on page 555)

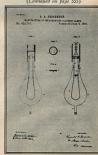

One of Fessenden's important inventions is the use of silicon iron wire for leading-in conductors in incandescent bulbs. The illustration is a reproduction of the drawing for this patent.

New Ideas In Receivers

By G. C. B. ROWF

The two receivers described in this article are the latest in modern radio engineering design. These illustrate the first attempt to get away from the use of the ordinary dials such as me now use.

7 ITHIN the last year there have been improvements beyond number in the design of radio receivers. The work of the radio engineers has however, been concentrated mainly on improvements in the circuits used and the apparatus and instruto the outward appearance of the cabinet, However, in the receivers that will appear How the "dial-less" receiver is tuned. The cover turns on a The cover turns on a shaft at 1 and on the rim of the cover is space provided for the stations' call letters. This receiver was invented by Mr. C. C. Blackmore.

cover. Once the rheostats are set, they need the cover. On the side of the set are two handles: one controls the volume and the other is

an adjustment for the variable condensers. The volume control lever, when placed on the left side of the slot, disconnects the "A" battery from the filaments of the tubes, and when moved across to the right side, opercontrols the fila-

How the set operates. The spindle, 1, turned by the cover rotates gear, A, This turns the

second lever moves

pper condenser and siso the lower conden-er through the float-ing gear train B and C. Lever 4 equalizes of the two variable condensers

gears so that the movable plates of the con-densers can be placed in such a position that they compensate for any changes in the the radio frequency

plates of the other, the settings remain in a fixed relation throughout the whole range As has been mentioned above, the top

cover of the receiver rotates, and is fastened to the shaft on which is mounted the gear train that operates the two variable condensers. Around the perimeter of the cover is a flat, gilded strip on which may be written the call letters of the different stations. As each station will come in at a different point on the perimeter of the cover, there sufficient space for a great number of call letters

The apparatus is mounted on the under side of the wooden panel, which is, in turn, covered by the revolving lid. The receiver is 16 inches in diameter and is 81/2 inches in height. the opposite side of the set from the control levers for the antenna and ground connections and also two jacks for phone or loud speaker connections.

There are numerous radio engineers that have been working for many months to get the correct combination of circuit and cabinet. One receiver, which is the result of the work of Robert E. Lacault, is shown in some of the accompanying illustrations. It seems that the goal of the designers last year was to make the tuning of a receiver as simple a matter as possible and, there-fore, Mr. Lacault has his receiver tuned with but two controls. These controls are through a system of two levers that project through the front of the cabinet and travel around the central grill work, which covers the horn of the loud speaker that is inclosed in the cabi-

on the market this fall, not only are the circuit and its necessary instruments im-proved, but more attention than ever before has been given to the appearance of the set

A departure from conventional receiving equipment design is shown in the set illustrated in the accompanying photographs. The main feature that is stressed is that there are no dials to turn in order to tune in different stations, there being but one adjustment to make.

This adjustment is made by rotating the cover of the set. Attached to the knurled knob shown in the center of this movable cover is a pin attened to a rotating shaft which controls two variable condensers that tune the one stage of radio frequency amplification and the detector unit. There are five tubes used. As mentioned above, there is one stage of radio frequency amplifica-tion, detector and three stages of audio fre-quency amplification, the last two of these

The rotating cover is removable. Under this there is a sub-panel of wood on which is mounted an adjustable resistance and the top of a rheostat. As may be seen, the vacuum tubes are inserted through this panel with their tips just clearing the movable transformer or the fixed coupler. When the movable plates of one condenser are set in relation to the

The revolving cover is supported by the plate, 1, which is at-tached to the shaft to tached to the shaft to which is fastened the variable conden-ser gears. The point-er, 2, indicates the call letters written on the rim of the cover. The controls.

Photos on this page Courtesy Ohio Stamping and Engineering Co.





Rear view of Lacault's receiver, showing the gears that drive the variable condensers. Gears 2 and are on the shaft attached to the levers and those numbered 1 and 4 are on the condenser shaft.

the exterior of the cabinet, the periphery of this grill work of bronze is marked off by a scale so that the operator of the receiver can at all times get a station that be wishes by the method of logging the set. by the method of logging the set and knob, by the control of the set and which, when turned full to the left, disconnects the "A" battery from the filaments of the

vacuum tubes. There is also a telephone jack for the use of head-phones, if the oper-

ator wishes to try for DX. The amount of current that is supplied to the filaments of

the tubes is regulated by automatic filament controls, so that the operator does not have to worry about their adjustment. The receiver employs six tubes of the storage battery type, three of them functioning as radio frequency amplifiers, the fourth as a detector and the last two as audio frequency amplifiers. Two of the radio frequency stages are tuned, but the third stage stages an innovation is introduced in the way of two resistances in the grid circuits of the tubes. These resistances prevent these circuits from "spilling over," or oscillating, at resonance points and at the same time increase the selectivity of the whole radio frequency amplifer unit.

The variable condensers used in this receiver are of the straight-line wave-length type, which adds a great deal to the simplicity of turning, as the points at which the levers are set to pick up the stations are separated more widely than they would be with the ordinary type of condense man the with the addiction of the property of the with the addiction frequency amplifier, so that the impedance is the same. By this means distortion is eliminated to a considerable ex-

The cabinet is 24 inches in length, 14 inches wide and is the same height. There is space, inside the cabinet for "B" batteries and the antenna and ground connections are made to terminals at the rear of

The lond speaker system is the result of careful research work, not only m connection with the unit, as has been mentioned above, but also in connection with the horn, the contour being adopted after many trials. This horn is of a special composition which reduces to a minimum all extraneous vibrations and renders the music and speech output of the highest grade.

There may be used with this receiver either an indoor or an outdoor antenna system. By an indoor antenna is meant a short stretch of wire inside the room, not a loon antenna. An antenna of the loop type will operate satisfactorily on local reception, but will not give the results on DX work that the other type will.

The two types of receivers described above are designed especially for the person who "knows nothing about radio," for they are

Front view of the receiver. The loud speaker unit on the left leads to the bell of horn. A. The levers, I and 4 are shown connected to the shaft carrying the gears that operate the variable condensers. The position of the volume control is indicated at 3.



Front view of the sixtube receiver that has tube receiver that has the two tuning controls, indicated at 1 and 4. These levers move along the periphery of the grill work, on which is engraved a scale to be used for logging. The number 3 indicates the volume Photos control. Photos control. Radio Corp. made in such a manner that tunnie in startions is reduced to the freset possible actions. Such radio receivers as are herein dements that will tend to make radio a greater infore sport than it already is. As quiebly, as designers and manufacturers learn that the present-day radio fan whele as et that the present-day radio fan whole a set that perparance of the room in which it is placed, the sooner will the industry be placed on a more stable foundation. A great deal of mented along the lines mentoned above, he cause it is only by careful research works cause it is only by careful research works and experimenting that radio will finally take it registrated place among the great inventions of





Radio in China being under government con-trol, broadcasting i s permitted only under special license. Changes in legislation permitting a lifting of the radio equipment embargo are daily ex-pected. Only in two treaty ports is there any broadcasting. In Hong Kong there is a 1,500-watt government station oper-

ating on 350 to 360 meters. The Hong Kong Hotel Company operate a 100watt station, the wave-length of which we do not know. There is some phone transmission by


department stores and hotels, but it is The Ministry of Commerce has been working for a year on regulations which may be acceptable to the Chinese powers-When these regulations are completed to the satisfaction of all parties concerned, China may be expected to couple its interest (at this rather late

date) to that of the rest of the world in this field of endeavor. RECENT RADIO PROGRESS ABROARD COLOMBIA

The development of a radio market in Colombia which has no broadcast station, is largely dependent upon the com-pletion and satisfactory operation of the proposed broadcast stations in

Peru and Costa Rica. AFRICA AND FAR EAST INDIA

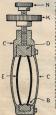It is necessary in India for one desiring to import radio apparatus to obtain an import license from the Indian Gov-ernment. Contrary to previous reports. once this license is obtained, there are no restrictions whatever on the quantity of receiving sets which the licensee may import. Further, the purchaser of a re-



The main difference between the type of English condenser shown in the accom-panying sketch and panying sketch and others on the market is that the pressure is applied to the movable plates in a vertical direction. The metallic denser forms one plate of the condenser, the other being the two mica-covered plates, E. These plates are sprung into position sprung into position by the plates, B and D. When the acrew, the plates, B and D. When the acrew, ceiving set must have a license from the government permitting him to operate it. but this license need not be obtained prior to the importation of his receiver. These regulations also apply to Burma. NEW ZEALAND

New Zealand is well supplied with broadcast stations and offers a good market for receiving apparatus. American radio manufacturers and exporters



The new type of English inductances with

worth of their goods during the first quarter of 1925,

SYRIA Radio enthusiasts residing in Syria are dependent upon distant broadcast sta-tions for their entertainment. It is practically impossible to determine what the possible market for radio apparatus in Syria will be but it is certain that, until broadcasting stations are erected and placed in operation within a relatively short distance of Syria, only high-priced receiving sets will be worthy of consider-

TUNIS

There is one broadcast station in Tunis -located in the city of Tunis-but radio fans are not dependent on this station for their entertainment as they can readily receive from several European cities. Permission to erect and operate a broadcast station in Tunis must be obtained from the government

It is not required that individuals owning and operating receiving sets procure a license from the government, but they must notify the Postal authorities of their

The principal radio dealers in Tunis the electrical firms. Most of the are the electrical firms. Most of the receiving sets and radio parts offered for sale and in use in that territory are of French origin. The average price of a 5-tube set in Tunis is 1,500 francs, approximately (\$75.00), and load speakers retail at approximately (\$600 francs (\$30.00) each. French manufacturers and exporters of radio apparatus are in an advantageup sosition, relative to those advantageous position, relative to those

of other foreign countries, to develop the" Tunisian market. These advantages are: admits French radio aparatus duty free, the pres-ent favorable rate of exchange and the nearness of the two countries to one an-



ENGLAND



Many more radio experimenters would use inductances of the honey comb and similar types, if the construction were more solid. As made at

the present, these coils stand up very well at first, but tend to loosen in their windings when used for a considerable period. In addition, they are easily affected by mechanical damage, for instance when they are dropped or otherwise roughly handled by the

An English maker has now brought out a new style of inductance coil, which is claimed to be more solid than any other type, and is not likely to suffer from mechanical break-

Fig. 1 on the left shows a coil of the new design; the winding is contained in the in terior, and is protected by the stout hard rubber discs shown in the illustration. central portion of these discs is engraved with circular lines, so that the coil is easily held and not liable to slip.

The interior construction and the method of fitting the plug-in pins in the lower ends of the hard rubber discs is clearly shown in Figs. 2 and 3.

-C. A. Oldrovd. An attempt was recent-

Underwater Transmis. sion

ly made by engineers of the British Broadcastine Co. to broadcast from

under water. The experiments were made in one of the large tanks in the London Zoo Aquarium. The aim of the experiment was





to ascertain, not whether fishes speak, but whether they actually communicate by means of any special sounds. The results of this most interesting experiment have not, as yet, been divulged to the eager thousands who were not so fortunate as to hear this pro-



SPAIN

Broadcast ve

On page 99 of the July number of "El Exportanumber of L. dor Americana," the Perifonia Spanish issue of The American Exporter, appears an interesting article discussing the Spanish translation of the English word

broadcasting and its derivatives. It is pointproacasting and its derivatives. It is pointed out that the distinguished Spanish philologist, D. Julio Casares, published a treatise on the question in the Spanish newspaper, A B C on June 6, 1924.

It is said that the Spanish word "radiodi-fusión" has made little headway toward re-placing the English "broadcasting." The English term is so much mutilated in print

and speech in the Spanish-speaking countries that the "purists" are crying for an author-ized Spanish form. The Spanish Academy, slow and conservative, has not acted. Casares proposes perifonia and its derivatives. Perifonia is composed of the Greek elements peri, around, in every direction, and fone, sound. It would make a better international word than the English term, it is claimed. The English forms would be: To broadcast, perifone; by broadcast, by perifone; broadcaster, perifonist, etc. (The words are analogous to our words

Since Esperanto is winning recognition as

the world radio language, perhaps a more generally acceptable international word for broadcast would be the Esperanto: disaudioi -dis, to scatter in all directions; audi, to hear; ig, the suffix which means to cause to be done, thus: disaudigi, to cause to be heard in all directions, pronounced: Dees-ou-dee-Derivations: disaudigi, to broadcast; disaudigado, broadcasting; disaudiganto, etc.-J. D. Savres.

ADJUSTABLE SCREW AND LOCK NUT TO ADMIT ANY SIZE CRYSTAL



The feature of this English crystal detector is that both the crystal and the catwhisker can be adjusted. The crystal is held between two jaws and can be rotated so that any part of it may be presented to the catwhisker, which is held in a chuck attached to the handle that works in a ball-and-socket joint.

PRESENT ANY FACE

TO CAT WHISKER

Esperanto Broadcast Lessons By JAMES DENSON SAYERS*

PART I ALPHABET

The five vowels have the international sound, practically the same as Spanish or German: a, ah; e, eh; i, ee (always as i in machine); o, oh; u, oo (as u in Those consonants which have only one

sound in English are the same in Esperanto: b, d, f, k, l, m, n, p, r, t, v, z. The r should be slightly trilled.

q, w, x, y are not used.
c, tso; \(\bar{c}\), cho; g, go; \(\bar{g}\), jo; h, ho (same as English); h, hho (as the German or Scotch ch, strongly aspirated; appears in health the strong of the strong

but few words); j, yo (as j in hallelu-jah); j, zho (as s in pleasure or measure, pan): J. 200 (as s in pleasure or measure, or French j in je); s, so; ŝ, sho.
aj as ai in aisle; ej as ei in vein; oj as oy in boy; uj as uj in hallelujah; aŭ as ou in house; eŭ, eh-oo said quickly

ACCENT

Always accent next to last vowel: Es-pe-ro, Es-pe-ran-to, ju-na, Eŭ-ro-po. There are three combinations of letters which need a little special attention for English-speaking students: Kv. kvar, kvin kvieta. Kn. knabo, knedi. Sc. scio (sts-ce-o), sceno (stse-no), eksciti (eksee-tee)

As it is of first importance in the study of any language to correctly master the pronunciation at the beginning, I cannot overemphasize the need of each student following me closely in all the Esperanto text, diligently pronouncing after me all words and text which I indicate for that purpose.

WORD ENDINGS

Each class of words in Esperanto has its distinctive letter ending, so that you know at once to which class a word be-longs: Nouns (names of things) end in longs: Nouns (names of things) end in opatro, father, domo, house; adjectives on patro, father, domo, house; adjectives bona patro, good father; granda domo, large house; verbs (infinitive) end in it kuri, to run, vidd, to see; adverbs end in e: rapidly, rapide, slowly, malrapide; present tense of verbs end in ast: kuras, runs, vidas, seex; past tense in is; kuris, runs, vidas, seex; past tense in is; kuris, ran, vidis, saw; future tense in os: kuros, will run, vidos, will see; imperative in u: Portu al mi la libron, Bring me the book, Ni iru kun li, Let us go with him;

* President New York Esperanto Club.

The following is the first of a series of three condensed lessons in Esperanto, prepared especially to be broadcast from WRNY by Mr. Sayers in order that all read ers of RADIO NEWS, wherever situated, may have ORAL PRAC TICE in correct pronunciation of the World Radio Language. After these three lessons students following them will be well prepared for reading, writing and beginning conversational practice. This first lesson will be given from WRNY at 10:00 P. M SEPTEMBER 24, on 258.5 meters. This will be fol-lowed by a lesson a month later till the series of three is completed.)

subjunctive in us: Se mi estus sana, mi estus feliĉa, If I were well, I would be

When more than one of anything When more than one of anything is indicated it is called the plural. The plural is shown in Esperanto by the ending i; patroj, (pah-troy), fathers, domoj (dohm-oy) houses. Adjectives describing plural nouns must also take the plural ending: bonaj patroj, grandaj domoj.

Pronouns are: Mi, I; ni, we; li, he; vi, you; (ili, they; ŝi, she; ĝi, it; oni, one, they, people (abstract); ci, thou (used familiarly in family or with intimate friends); si reflexive pronoun; see below.)

To form the possessive with any pro-noun, add the adjective ending a: Mia libro, my book; miaj libroj, my books; lia domo; ŝia patro; iliaj patroj.

Oni is used for one, they, people, when

words are used indefinitely: Oni diras ke li estas riĉa, One says (or, they si is a very valuable pronoun in Es-

preventing ambiguity such often exists in national languages. It always refers back to the subject of the sentence. In "John loves his brother and his children" we can't tell from the English text whose children, but "Johano amas sian fraton kaj siajn in-fanojn" we see at once means the chil-dren are John's, not his brother's.

Mem is used to emphasize pronouns Li batis sin mem. He struck himself (hi own self); Si mem venis, She herself The sign of the accusative, n, in Esperanto is of first importance. Many persons, not understanding its usage, denounce it, but once understood and used easily, its great value is seen. It is of such importance because the syntax, or sentence structure, of different national languages differs greatly. Therefore, in a universal language, the German may put his verb wherever he pleases, anyone can place the subject at pleases, anyone tan place the sale of the sentence, but as long as the "n" is used to indicate the object in the sentence it is clear. "La patron morthe "I is used to indicate the object in the sentence it is clear. "La patron mor-dis la hundo" means, with instant clar-ity, "The dog bit the father"; La bildon pentris la pentristo, The painter painted the picture.

N renders clear such ambiguous Eng-N renders clear such ambiguous Eng-lish structure as: "John loves Mary more than George," "Johano amas Marion pli ol Georgo" which can mean nothing but "John loves Mary more than George (loves Mary)."

The accusative n is not used after prepositions: Sur la tero kuŝas ŝtono, On the ground lies a stone; Antaŭ la domo staras arbo, Before the house stands a tree. But if motion toward something is to be indicated, the accusative of motion is used: Li iris en la domon, He went nto the house. ĝis, till, as far as, until, up to, al, to. towards, and tra, through, can mean nothing but motion, therefore it is not necesing but motion, therefore it is not neces-sary to use n following them: Mi iris ĝis la rivero, I went as far as the river: Li venis al mi. He came to me: Ni voja-ĝis tra la mondo, We traveled through the

Names of days of the week and months of the year (usually written with small letters as is the custom in most countries) are: Dimanĉo, lundo, mardo, merkredo, jaŭdo, vendredo, sabato, Januaro februaro, marto, aprilo, majo, junio, julio, aŭgusto, septembro, oktobro, novembro, decembro.

NUMBERS

Cardinal numbers: 1, unu, 2, du, 3, tri, 4, kvar, 5, kvin, 6, ses, 7, sep, 8, ok, 9, naŭ, 10, nulo, 11, dekunu, 12, dekdu, 15, dekkvin. Multiples of ten are simply "ten" plus the desired multiple of ten, thus, 20, dudek, 40, kvardek, 90, naŭdek.

(Continued on page 482)

Hard Tubes and Soft Tubes As Amplifiers and Detectors

By PROF. C. B. BAZZONI, Ph. D. * The first part of an article telling about the fundamental characteristics and functions of



HE three-electrode tube is the heart of the radio set. Every radio user knows that these tubes contain a filament which can be heated to glowing by a current passed between two of the plugs in the base, a metal plate connected to a third plug and an intermediate wire grid con-nected to the fourth plug. These details of construction can be observed easily by peering through thin places in the silvery lining of the tube, especially when the filament is glowing. Very few amateurs, however, even those expert in making and operating sets, hook-ups, and still fewer are familiar with the scientific principles underlying the design of the tubes. The experimenter interested in the advancement of radio performance ought, nevertheless, to study these matters diligently, since improvements in any device can be made only after an adequate understanding

The fact that the tubes of today are in all essentials, except degree of vacuum, practically identical with those introduced by DeForest back in 1907 might be thought to indicate that room for improvement exists in this field. Let us consider briefly certain of the fundamental characteristics of presentthose characteristics which belong, not only to the three-electrode tubes, but also to the two-electrode and four-electrode tubes used in certain special connections in the radio

of its present construction and operation has

HOT CATHODE AND COLD CATHODE TUBES

The practical uses of vacuum tubes depend on the movement through them of streams electrons-those elementary particles which constitute negative electricity. movement is maintained by an electric field between a positively charged electrode in the tube called the anode and a negatively charged electrode called the cathode. One method of classifying vacuum tubes is based on the nature of the cathode: 1, cold cathode tubes, where the cathode is merely a metal plate or wire and, 2, hot cathode tubes, where the cathode is a filament which can be heated to incandescence. It is evident that all the ordinary radio tubes belong in class 2. However, readers of this periodical will recall that the September issue condifferent types of electron tubes. from escaping through it. If now heat be

tained (page 293) a description of a new cold cathode tube which has been used as a rectifier in a "B" battery eliminator and for other radio purposes

HARD TUBES AND SOFT TUBES In hot cathode tubes electrons are pro-

duced continuously from the hot filament itself (the so-called thermionic emission) and, being drawn over to the anode, produce a relatively heavy current through the tube, which would be maintained even if the air or other gas were completely re-moved. In cold cathode tubes, on the other the cathode. The electron stream on which the current flow depends is built up through an electrical "break-down" (ionization) of the gas atoms in the tube. Cold cathode tubes must, therefore, contain a certain amount of gas.

A second useful classification of vacuum tubes is made on the basis of degree of tubes is made on the basis of degree of vacuum, that is, on the amount of gas in the tube. From this point of view tubes are either "soft" that is, with a considerable amount of gas in them or "hard" with as good a vacuum, i.e. as little gas, as is possible with present-day air-pump facilites. plain from what we have already said that cold cathode tubes must be soft, while hot

HARD VACUUM, HOT CATHODE TUBES The hard vacuum, hot cathode tube is in rinciple the simplest of all vacuum devices although, on account of the mechanical difficulties of producing and maintaining the attain any sort of perfection. The 201A and 301A tubes are examples of this type. In the filament of such tubes, as in all electrical conductors, there are many millions of free electrons, that is, of electrons which circulate freely amongst the atoms of tungsten which make up the filament. These free high average speeds-say about thirty miles per second—on paths rendered very short, broken and irregular by frequent collisions with the tungsten atoms. Each time an electron hits an atom it stops or bounces off in another direction, but the speed averaged over a second is nevertheless high. At the surface of the filament certain skin forces act sufficiently to prevent any electrons which come up to the surface with these velocities applied to the filament the electron speeds fact, merely the energy of motion of the electrons and atoms-and some of them will then be able to work out through the surface of the filament into the surrounding space, The hotter the filament the more electrons will work out in each second.

THE THERMIONIC EMISSION


These electrons make up the thermionic emission, so named by O. W. Richardson, who first explained the effect in 1903. If there is no positively charged electrode in the neighborhood of the emitting cathode, the electrons will merely form a cloud around the hot wire and will act to repell the electrons coming up to the surface back into the filament, thus putting a stop to the emission after a certain density of the cloud is reached. This, for example, is the condition in an incandescent lamp where we have a glowing wire but no second electrode. radio tubes the plate is kept 45 to 90 volts positive, referred to the filament, by the "B" ing out of the filament as a result of its high temperature, fly over to the plate making up the "plate current." If the filament is made the "plate current." If the filament is made very hot, as for instance when a tungsten filament is raised to 2,000 to 2,500 degrees Centigrade (as is usual in radio sets), an enormous number of electrons is given out in each second; enough, at the highest temperatures, to make up a current as large as filament. Under these conditions there will be a very large number of electrons on their way over in each unit of volume of the space between filament and plate at any instant.

SPACE CHARGE

This distributed cloud of electrons is, of course, a distribution of negative electricity and is referred to as "negative space charge" or merely "space charge." charge, being negative, will evidently act to repel fresh electrons coming out of the filament so that when it becomes dense enough. it will stop or, rather, limit the thermionic emission. For any given plate voltage a definite upper limit is thus put on the plate not become greater as the filament rheostat is turned out, since the space charge prevents



Fig. 1. The Thermionic Emission. S-S is the sur-face of the filament wire. The circles enclosing the letter T represent tungsten atoms which are roughly stationary and have a dis-meter of one-one-hundred-millionth of an inch. The dots represent electrons, which move about at 30 miles per second and whose diameter is one one-hundred-thousandth of an hundred-thousandth of an atom. Fig. 2. Space Charge. The electrons at any instant in the volume S repel electrons coming

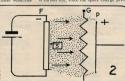

any more electrons getting away from the filament in any case. If now the space charge be in any way reduced while the the performance of the performance of the pervalue, the person will immediately increase, due to the extra electrons which are thus enabled to get away from the filament. This simple fact is the fundamental principle which explains nearly all of the mysteries of the radio trans-

ACTION OF THE GRID

The write of the grid serve servely, to increase of decrease the space charge and thus to alter the strength of the plate current distribution of the server server

THE NECESSARY VACUUM It is seen that the theory of the "hard tube" involves no mention of gas. Gas must, in fact, be reduced to a point where the num ber of gas atoms between filament and plate is not large enough to offer any serious impediment to the passage of the electrons In first-class hard tubes the air is pumped out by efficient air pumps while all the metal and glass parts are being heated and then the residual air is taken up by cer-tain chemicals called "getters," which com-bine with the gas atoms to form solid compounds. It is the action of these chemicals which produces the silvery film s.en on the inside of the glass in commercial tubes. By this means the gas pressure is reduced to per one ten-thousand-millionth (1/10,000,-000,000) of the normal atmospheric pressure. Now there will still be about one thousand million of atoms in each cubic centimeter of the space at this pressure so that such a vacuum, nearly the best attainable at present, is very far from perfect.

However, the atoms are so small and the electrons so much smaller that the chance of collisions occurring is really very slight at each of collisions occurring is really very slight at each of the collisions occurring is really very slight at each of the collisions occurring the collisions occur

THE PURE ELECTRON DISCHARGE

An electron discharge of this character in which gas plays no important part is called a "pure electron discharge." We have here the simplest, most easily controlled and best understood type of electron current. It is possible to design tubes using this type of discharge so that they will amplify weak signals into intense ones without introducing irregularities or distortion. For straight amplification work the hard tube has, there

fore, the widest use at the present time.

The widest use at the present time survive as an ownlife it leaves much to be desired when used as a detector in radio crients. It is, in the first place, entirely too modern practice. Compared to galvaneers and similar detecting devices used for modern practice. Compared to galvaneers and similar detecting devices used for table detector must be ranked very low in the detector must be ranked very low in the deed in sensitivity. Numerous attempts have been made to remetely this defect. The The gas-filled or "soft" detecting time is

SOFT VACUUM TUBES

The "soft" or low vaccinis the was the type in general use for all radio purposes prior to 1914. The soft tube was used in those early days merely because, with the air the soft tube and the soft days may be a soft to be a manufactured. They were in subsequent texts, so that the present generation of radio properties, different results of the soft tube, have some really valuable to the soft tube, have some really valuable to make use of by deliberately introducing as into otherwise hard tubes. This new line of development is one with which the soft tubes have some or with which the soft tubes are some soft tubes and tubes. This new line of development is one with which the STRUCTURE OF GAS ATOMS.

In order to understand the effect of gas on the electron current through a vacuum tube we must first bring up a few facts about the construction of the gas atoms themselves. Atoms are extremely minute particles of matter, far too small ever to be perceptible even under the most powerful microscopes. yet they are known to have a beautifully omplex structure-being composed of electrons, the elementary particles of negative electricity, and of protons, the elementary particles of positive electricity. The electric charge on a proton equals that on an electron but in mass they are very different—the proton weighing about 1,800 times as much as the electron. Most of the atoms in a tube from which the air has been pumped and which has been treated with a "getter" are probably nitrogen atoms. Each nitrogen atom consists of a small central part, the nucleus, containing fourteen protons and seven electrons (and having, therefore, a net positive charge of seven units) and of an outer shell containing seven electrons.

saggregation is seen to be neutral, electrically, it is held topether by electrical forces of a definite character and has consequently a definite definite structural strength. This means that a certain definite amount of work must be done on the atom in order to break it apart of the structural strength. This structural is amount of work must be done to knock off or plack away one of the seven exertion of or plack away one of the seven exertion cleartons. This particular amount of work is the smallest that could produce any effect parts would evidently be more difficult and would therefore require more would the structural structural structural to the smallest structural s

ELECTRON PROJECTILES

Now an electron drawn over from the filment to the plate by 30-90-01 "By battery packs up considerable speed and therefore as packs and the state of the speed of

The positive ion will be very heavy compared with the negative ion. Since the nucleus contains seven protons, as stated above, the positive ion will be, in fact, more than 12,000 times as heavy as the single electron knocked off. As soon as these ions are formed they will begin to move, the positive ions falling toward the filament and the negative ions toward the plate. If there are a great many atoms in the tube so that many considerably to the strength of the electron current. The positive ions, on the other hand, are very heavy and therefore clumsy, so that they do not move as fast as the negative ones, yet they will exert a most important influence since, by their presence the space between the filament and the plate, they will neutralize the space charge and thus cause an increase in the electrons getting away from the filament.

DETECTING ACTION

If the potential across from filament to plate is not great enough to give the electrons the energy necessary to ionize the atoms then the discharge will go on very much like the pure electron discharge described above but, if the potential rises, then at the instant the critical value is passed and ionization begins the two causes mentioned—the contribution of the negative ions

(Continued on page 551)


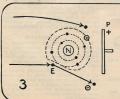


Fig. 2. The ionization of nitrogen. No is the nucleus: E, electron projectile fall-ing toward plate, P: circle edition of the property of the plate plate, provided and circle enclosing r is the plate plate. The plate plate

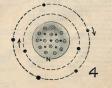

The Luminotron

By Theodore H. Nakken*





Bottom view of the apparatus used for the transfer of light energy into electrical energy.

NE of the most neglected and yet most interesting branches of re search can be found in the subject of photo-electricity, photo-electric cells, and the possibilities of their application in different apparatus.

The possibilities of a satisfactory photo-electric cell would be extremely far-reaching, as, after such a cell has been constructed, the solution would be given for quite a number of problems that now await their complete answer and satisfactory solu-Of the problems that might be solved I will name only the following

1. Automatic registration of light intensities at various moments.

2. Automatic signal apparatus. 3. Automatic apparatus for lighting buoys. 4. Measurement of the intensity of dif-

ferent light rays. 5. Reproduction of sound photographed upon a film.

6. Talking motion pictures.
7. Telegraphing photographs, etc., at high speed by wire or by means of radio.
8. Television.

As is generally known, the element selen-ium exhibits to a marked degree the peculiar property of lowering its electrical resistance when it is illuminated by light rays. This property seemed to promise at once the complete solution of the various problems named, and it may be said that if the selenium cell had only fulfilled its original promises, most of these problems would have electrical details of the apparatus involved the greatest ingenuity.

The selenium cell, however, has a sharply defined frequency limit. Cells made in the most careful manner are scarcely able to follow light modulations faithfully in variations above a thousand a second. Even if cells of much better quality are produced, the limit remains far below the frequency which would be required for most of the above problems.

A second disagreeable property is the so-called inertia of the cells. By this it is

*Research Engineer, Radiall Co.

interesting to students of television. meant that the cells, after being illuminated, do not return immediately to the resistance they possess when in complete darkness. Means for circumventing this property have been devised, but these, at best, constitute

Another drawback is the fact that for no apparent reason they can suddenly change their properties, so that they are, therefore, entirely unable to act as the controlling member in apparatus of which a certain reliability must be demanded.

It was with these facts in view that much thought and labor have been given to some kind of photo-electric cell that would be able to take over the functions of the selenium cell.

THE HALLWACHS EFFECT

The most beautiful line of attack was Hallwachs effect. This effect may be brief-ly described as the property of metals to emit electrons when light, especially ultraviolet light, falls upon them while charged negatively. This emission of electrons

negatively. This emission of elections to be practically instantaneous. The alkaline metals, like potassium or rubidium, show this phenomenon to a marked degree and even emit electrons when illumi-nated by the visible spectrum.

We are indebted to the German scien-tists Elster and Geitel for much of our knowledge of the actual properties of these metals and their amalgams and hydrides which possess the Hallwachs effect to a still

The photo-electric cell, as built by Elster was silvered over a great part of the sur-face on the inside, so that only a small aperture in the silver coating was left open. contact was brought through the glass bulb so that the silver coating could be brought so that the surver coating could be brought into electrical contact with a terminal on the outside of the cell. A platinum wire was fused in the glass where it was free of the silver coating and formed the second contact (see Fig. 1). After the glass build had been prepared, pure potassium, or rubi-dium, was distilled into the bulb, and upon condensation the entire silver-coated inner surface was covered with the metal. After a sufficient deposit of alkaline metal had



ORIGINAL ELSTER AND GEITEL PHOTO ELECTRIC CELL FIG. I An early photo-electric cell.



LATER FORM OF THE CELL CALLED LUMINOTRON FIG. 4

By varying the intensity of light on the plate of this cell, the potential of that plate can be varied through wide limits.

been secured, the bulb was filled with hydrogen, which caused potassium or rubidium

To bring this layer to its highest point of sensitivity, an electrical discharge was then caused to pass through the tube, usualmen caused to pass through the tube, usually by means of a spark coil. This discharge caused the hydride to assume a reddish, bluish or greenish color, depending upon the alkaline metal used and the degree of intensity of discharge. After this process had been completed, the tube was evacuated and an inert gas, like helium or argon, was introduced into the tube at very low pressure, which again seemed to serve to increase the sensitivity and also to make the cells more

stable in performance. To obtain the best results from these cells the platinum wire in the opening (see Fig. the piatinum-wire in the opening (see Fig. 1) was made positive and served as anode, while a negative potential was applied to the coating. To secure the greatest response it was at all times necessary to bring the potential difference to the highest pos-sible point. This practice was very dangerous, as the potential was always held to the point of breakdown. Consequently, the one operating the cell had, to say the least, to have great experimental ability. There-



FIG. 2

1, glass container; 2, filament; 3, photo-electric plate; 4, cathode terminal; 5 and 6, filament terminals.

fore, the use of the cell for other than purely scientific purposes, for instance, the measurement of the light intensity of stars, has very rarely been attempted.

The cells had an additional disadvantage in that they were subject to fatigue. It seems that the photo-electric properties of such surfaces depend upon the presence of what might be called free electrons, i. e., electrons that can be easily loosened from the atoms to which they belong.

On the other hand, it may be said that the cells had apparently no appreciable inertia, as it has been proven experimentally by Wilson that they possess the capability of following up to 1,500,000 light fluctuations

WORKING PRINCIPLES

In his work upon the improvement of photo-electric cells, the author paid the greatest attention to the above properties of the alkaline cells and built upon this foun-The underlying thoughts were the following:

Some kind of cell must be devised in which it is possible to retain all the desirable qualities of the alkaline hydrides.

2. No attempt should be made to use the

actual photo-electric currents, as these require tremendous amplification to be of any appreciable use.

3 Manny must be provided for constant-Means must be provided for constant-ly supplying free electrons to the sensitive

The very first cell constructed in the course of the experiments is shown diagrammatically in Fig. 2. glass container (1) in which is inclosed a glass container (1) in which is inclosed a filament (2), and a photo-electric plate (3). Contacts 4, 5 and 6 were brought to the outside. This tube was connected as shown in Fig. 3, where we see the tube connected to a battery (7) for lighting the filament, which can be regulated by means of a rheostat (8). If we connect the sensitive plate by means of a wire (10) to the stem of a sensitive electrometer (9) we see that the gold leaf (11) takes a position, depending upon the electronic charge which accumulates mon the photo-electric plate (3), as a result of the thermionic emission from the filament. If light now falls upon the cell the photo-electric emission will come into play and therefore the plate will lose some of its charge, with the result that we ond position as indicated by the dotted line. As soon as the light source is removed, the As soon as the light source is remove can make this effect even stronger by interposing between the filament and the sensitive plate a grid, which is held at a constant positive potential, as is shown in Figs, 4 and 5

In the patent obtained on this invention (U. S. Patent No. 1,522,070), there are indicated other forms worked out to a higher degree of perfection than the figures given above, but in practice it was found that the cell as described is perfectly capable of all that is necessary to conduct different experiments successfully. The cell in it forms was called the Luminotron. The cell in its various

If we take a cell of the form as shown in Fig. 4 and connect the sensitive plate directly to the grid of an ordinary ther-mionic valve, it will be clearly seen that if we cause the plate of the photo-electric light, we shall thereby vary potential of the grid in the valve, which in turn will vary the magnitude of the plate current, according to the well-known pronerties of these valves

WHAT HAS BEEN DONE We have now succeeded in doing the fol-

lowing: If the filament of the photo-electric cell is lighted, it emits electrons, which, by the action of the positive grid, are projected upon the sensitive plate, which therefore assumes a negative charge. Here, it may be added, this constant electronic bombardment, taking place within the tube, seems to have the very useful effect of constantly resensitizing the photo-electric surface. It


Nakken's photo-electric and vacuum tube am-

vacuum plifier.



was pointed out that the original alkaline cells were made highly sensitive by means of an electric discharge through the tube. which really amounts to an electronic bom bardment. The same sensitizing seems to be going on constantly in the cens of this construction; in fact, it was often found that cells which were only slightly sensitive after they had been constructed needed lighted filament to reach the same degree of sensitivity as the very best specimens.

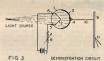Now, when light of varying intensity is projected upon the plate, the latter will, of



charge of electricity is carried from the late (3) by a wire (10) to an electrometer (9), thich causes the gold leaves (11) to spread.

its own accord emit electrons and emission is greatly facilitated by the fact that the grid is held at a positive potential and therefore acts as an anode with regard to the sensitive plate. of the filament remains constant, of course, and therefore the potential of the plate varies in direct proportion with the inten-

sity of the light rays. As was pointed out, the electronic emis sion is absolutely instantaneous, as is testified by the measurement of the possible number of fluctuations that can be followed by a sensitive plate of this description. thermionic valve, the plate current in the latter will be an exact electric reproduction

of the varying intensities of the light source It is the conviction of the author that in these cells there appears a phenomenon that has not heretofore been established. a photo-actinic plate under the influence of light rays emits electrons, it may be safely concluded that such a plate under the same circumstances should show a tendency to resist the depositing of electrons on its surface from outside sources. i.e., the filament. If this be true, we should see a second reason for the great sensitivity of the cell. Not only does the actinic plate emit electrons and thus lose part of its charge, but the plate resists the ten-dency of the filament to instantly replace that charge, which should be of the greatest benefit to the sensitivity of

At some future time the au-

ther hopes to go more deeply into this hypothesis to see whether or not this novel effect actually exists

It is evident that it is a fairly easy mate ter to combine the different functions of valve in one and the same tube Different ways of doing this have been given in the patent referred to above, but all the cells described there function only as light detectors by means of the varying potentials of a photo-actinic plate, which at the same


The author wants to express here his The author wants to express here his great appreciation for the work done and the assistance given in this development work by his friend, Prof. Chr. Ries, in Munich, Germany, who was so good as to undertake the actual construction of the cells, and who, as one of the greatest experts in photo-electric phenomena, assisted

in all phases of the experiments conducted.

This is the first of three articles, the following of which will deal with the appli cation of the described photo-electric cell to a system for recording and reproducing sound, leading up to the final application in talking motion pictures, while the third article will deal with a system of telephotography, either by wire or by means of radio, in which article the author will also deal with the problem of television.

RADIO REACHES THE PHILIP. PINES

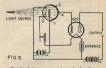Radio has finally reached the Philippine Islands in both its commercial and popular forms. Two rival organizations are fight-ing for control of local commercial and broadcast rights. With the advent of broadcasting the total number of fans listed in the Islands jumped from about 100 to about 2,000. No definite estimate of fans can be



Circuit of the apparatus shown in the photo-

secured, but it is believed that the craze is now started and that broadcast listeners will soon be legion, despite the difficulties of reception in that climate.

At the end of 1924 the Bureau of Posts and Telegraphs reported that there were 41 private radio stations, 39 amateur wireless licenses and about 85 radio receiving sets in operation. Of the latter class, 50 receiving sets were said to be located in and around Manila.

the cell.

The Radio Hook at WRNY





the judges on the right indicate their disapproval by the noise-making implements. But the performer hears nothing.

FEW things have made such a great hit as the radio hook at Station WRNY, now used on all Amateur Nights. The radio hook is the invention of Mr. Hugo Gernsback, editor of RADIO NEWS, and it works follows: On Thursday nights, during the presenta-

tion of the Amateur Night feature, the radio hook is applied just as the old-fashioned hook, that yanked the amateurs off the stage on the Bowery, was used in the good old days, except that the radio hook is more humane, in that the performer never knows that it is being used on him.

Its modus operandi is as follows: Several hundred feet away from the WRNY studio, securely locked into a room, there are anywhere from six to ten musical and literary critics. The critics are never twice the same people, but are usually recruited from the desks of newspaper critics. These critics are seated and wear telephone head receivers, with which they listen in to the front of them a regular broadcast microphone, which is on the air at all times, the same as the studio "mike." Anything that the critic says, or any noise that he makes,

goes on the air along with the amateur's performance. The critics have all sorts of weird noise-making contrivances, such as cowbells, Klaxon horns, rattles, horns and will become apparent later.

The amateur goes on the air and does his stuff. If it is good, the radio audience hears only the undiluted program of the amateur. But let it be bad, and immediately the critics begin their noise-making inferno, which drowns out the poor amateur who, blissfully (Continued on page 551)

\$370 Radio Play Contest

IN connection with Station WRNY, owned and operated by the publishers of Radio News, the following should be noted by playwrights and all those competent to write playlets. During the fall and coming winter, Station WRNY will organize its own group of players, who will, once or twice a month, broadcast a number of RADIO playlets.

There are, of course, many broadcast plays at the present time, but this is not at all what is wanted. Station WRNY requires radio playlets. In other words, theme must have something to do with radio. It may be of scientific, or other radio interest. It may have to do with broadcasting itself, or it may incorporate any other radio feature. But it is quite essential that radio itself be played up big in some way or other.

It should also be noted that the tech nique of a play broadcast is wholly different from that of the usual play. Where the entire play appeal is to the ear only it is necessary, in order to create the illusion, to resort to all sorts of sound effects, which it is left to the ingenuity of the playwright to employ to the best advantage. The more of these there are, the better, as a rule, is a play of this kind. Furthermore, when the audience can-

not see the play, the cast should always

confined to very few players. more players there are, the more difficult it is for the audience, who can distinguish the players only by their voices, to follow their actions. There should not be

more than five players in any event. When submitting manuscripts for radio

CASH PRIZES 6150.00

| Second | " | | | | | 75.00 |
|---------|---|--|--|--|------|-------|
| Third | | | | | | 50.00 |
| Fourth | " | | | | | 35.00 |
| Fifth | " | | | | | 25.00 |
| Sixth | " | | | | | 20.00 |
| Seventh | " | | | | | 15.00 |
| me deve | | | | | - | |
| Total | | | | | . S. | 70.00 |

playlets, the playwright should bear in mind that each playlet must be so ar-ranged that it may be played in not more than twenty minutes to a half hour.

Remember, in this particular competi-tion, that there must be a good deal of the radio element interspersed through the action, and the greater the number and diversity of musical sounds and

and diversity of musical sounds and noises there are, the better.

This competition is open freely to all, with the exception of the employees of The Experimenter Publishing Company and their families.

RULES OF THE CONTEST

All manuscripts must be typewritten, or in ink. Pencil matter cannot be considered.

All manuscripts must be delivered flat, not rolled.

A number of prizes are listed here-with, which will be paid to the winners at the close of the contest. In case of a tie, identical prizes will be given each

Manuscripts cannot be returned unless return postage is enclosed.

The publishers have the option of pro-ducing any play submitted, even if it does not win a prize. But they will pay the sum of ten dollars (\$10.00) each for any playlets produced that do not win

This competition closes on October 15. by which time all manuscripts must have been submitted

Address all correspondence to Editor, Radio Playlets, in care of this magazine, 53 Park Place, New York.

RADIO SET DIRECTORY

R ADIO has now arrived at the stage where receiving sets have become stabilized to a very high degree. Inasmuch as there is continuous discussion as to various features of sets produced in the United States, Radio News has taken the initiative to present, month by month, a complete picture of the entire set industry.

List Price: \$130

Trade Name: Airo Mas-ter No. 150, Console

ter No. 150, Conso Highboy Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside Loud Speaker: Built-

Manufacturer: AJAX ELEC. SPEC. CO., 1926 Chestnut St. St. Louis, Mo. Trade Name: Ajax Mar-

veltone Circuit: Tuned radio

Gircuit: Tuned radio irequency Batteries: Storage rec-ommended Antenna: Outside rec-ommended Load Speaker: None iurnished Controls: Three List Price: \$45

Trade Name: Ajax-A.C.S. Crystal Set Circuit: Crystal Batteries: None Antenna: Outside or socket

socket Loud Speaker: None Controls: One List Price: \$5

Trade Name: Ajax A.
C.S.T. Junior. Crystal Set
Circuit: Crystal
Batteries: None
Antenna: Outside or

Loud Speaker: None

Manufacturer: ALAD-DIN MFG. CO., Muncie, Indiana Trade Name: Aladyne Plain Cabinet Circuit: Non-oscillating tuned radio frequency Batteries: Storage Antennas: Outside Loud Speaker: Separate Controlas: Two List Price: \$75

Controls: One List Price: \$3

de Built-in

In presenting the various sets in a directory of this kind, it is naturally only possible to touch the high points, and we have there-fore listed all outfits under a simple classification that will, we hope, be of great service to the public, as well as to the trade. We have

attempted in this issue to list every set manufactured in this country, and although we have written a number of letters to all manufacturers, not all have replied. In order to make the directory complete, all sets manufactured by any one manufacturer listed have been included.

The Directory will be kept up to date, month to month. All manufacturers are invited to send monthly corrections as to the various features of the sets which they produce.

Manufacturer:
A-C ELECTRICAL
MFG, CO.,
E. Fourth St., Dayton,
Ohio
Trade Name: A-C Dayton XL-10
Circuit: Tuned radio
frequency
Batteries: Dry cell or storage Antenna: Outside Loud Speaker: Separate Controls: Three List Price: \$115

Trade Name: A-C Dayton glass-encased Circuit: Tuned radio frequency Batteries: Dry cell or

Batteries:
storage
Antenna: Outside
Loud Speaker: Separate
Controls: Three
List Price: \$125

Trade Name: A-C Day-ton Phono-Set Circuit: Tuned radio frequency Batteries: Dry cell or storage Antenna: Ontside Loud Speaker: Phono-graph graph Controls: Three List Price: \$95

Trade Name: A-C Day-ton XL-15 Console Model Circuit: Tuned radio frequency Batteries: Dry cell or

storage Antenna: Outside Loud Speaker: Built-in Controls: Three List Price: \$185 Trade Name: A-C Day-ton XL-5 Knock-

ton XL-5 Knock-Down Set Circuit: Tuned radio frequency Batteries: Dry cell or storage Antenna: Outside Loud Speaker: Separate Controls: Three List Price: \$72.50

Manufacturer: ADLER MFG. CO., INC., 881 B'way, N. Y. City Trade Name: Adler-Royal Model 199 Greatt: Neutrodyne Batteries: Dry cell (All batteries enclosed) Antenna: Outdoor or

Loud Speaker: Separate Controls: Three List Price: \$125

Trade Name: Adler-Royal Model 201A Circuit: Neutrodyne Batteries: Storage Antenna: Outdoor or Loud Speaker: Separate Controls: Three List Price: \$125

Manufacturer: AIRO MASTER CORP., 227-239 W. 17th St., New York City Trade Name: Airo Mas-ter No. 60 Chest Circuit: Tuned radio

Trade Name: Aladyne Semi-Console Circuit: Non-oscillating tuned radio frequency Batteries: Storage Antenna: Outside Loud Speaker: Built-in Controls: Two List Price: \$100 Manufacturer: AMERI-CAN RADIO & RE-SEARCH CORP., Medford Hillside, Mass. Trade Name: Amrad Model T-5 frequency
Batteries: Storage
Antenna: Outside
Loud Speaker: Separate
Controls: Three
List Price: \$60

Trade Name: Airo Mas-ter No. 75, Concert Circuit: Tuned radio Batteries: Storage cells fair)
Antenna: Outside
Loud Speaker: Separate
Controls: Two
List Price: \$85

Circuit: Tunes
irequency
Batteries: Storage
Antenna: Outside
Lond Speaker: Built-in.
Controls: Three
List Price: \$75 Trade Name: Amrad Calcinette Circuit: Neutrodyne Batteries: Storage Antenna: Outside Loud Speaker: Built-in Controls: Two Trade Name: Airo Mas-ter No. 130, Conzole Table Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside Loud Speaker: Built-in Controls: Three Controls: Two List Price: \$185

Trade Name: Amrad Jewel Circuit: Neutrodyne Batteries: Storage Antenna: Outside Loud Speaker: Built-in Controls: Two List Price: \$285

Manufacturer: THE
AMERICAN SPEC.
COMPANY
135-165 Holland Ave.,
Bridgeport, Com.
Trade Name: "Electrola" Model 40
Circuit: Tuned radio
frequency.
Batteries: Storage
Attention Outdoor, or

Antenna: Ostroor or indoor Loud Speaker: Separate Controls: Three List Price: \$85 8 8 8 Trade Name: "Electro-ba" Model 60 Circuit: Tuned radio frequency frequency Batteries: Storage Antenna: Outdoor or indoor Loud Speaker: Separate

Controls: Five Manufacturer: AMSCO
PRODUCTS, INC.,
416 Broome St.,
New York City.
Trade Name: Meloo Su-

preme 5 Circuit: Tuned radio Circuit: Tomed ratio
frequency
Batteries: Storage
Antenna: Either (indoor
recommended)
Loud Speaker: Separate
Controls: Three
List Price: \$165

Trade Name: Melco Supreme 25 Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Storage Antenna: Either (indoor recommended) Loud Speaker: Separate Controls: Three List Price: \$150

Manufacturer: ANDREWS RADIO COMPANY, Tribune Tower, Chicago, Ill.

Trade Name: Andrews
Deresnadyne Model M
Circuit: Deresnadyne
Batteries: Storage
Antenna: Outdoor or indoor Loud Speaker: Separate Controls: Three List Price: \$125

Trade Name: Andrews Deresnadyne De Luxe Model Circuit: Deresnadyne

Antenna: Outdoor or Indoor Loud Speaker: Separate Controls: Three List Price: \$165

Manufacturer: APEX ELECTRIC MFG. CO. 1410 West 59th Street, Chicago, Ill. Trade Name: Apex Super Five Circuit: Tuned radio

Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside Loud Speaker: Separate Controls: Three List Price: 895 without accessories Trade Name: Apex De

Circuit: Tunes refrequency
Batteries: Storage
Antenna: Outside
Loud Speaker: Built-in
Controls: Three
List Price: \$135

Trade Name: Apex Baby Grand Console Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside Loud Speaker: Built-in Controls: Three List Price: \$225

Manufacturer: ARGUS
RADIO CORP.,
25 West 18th Street,
New York City
Trade Name: Power
Electric Radio Stand-

Electric Radio Stand-ard
Circult: One stage un-tuned, two transform-er-coupled radio freq-Batteries: Direct from A.C. or D.C. current Antenna: Outdoor or indoor.

Antenna: indoor Loud Speaker: Separate Controls: Two List Price: \$160 Trade Name: Power Electric Radio Model

Circuit: 1 stage untuned 2 transformer-coupled radio frequency Batteries: Direct from A.C. or D.C. curent Antenna: Outdoor or indoor Loud Speaker: Built-in Controls: Two List Price: \$235

Trade Name: Power Electric Radio Model 300 Circuit: 1 stage untuned 2 transformer-coupled

radio frequency
Batteries: Direct from
A.C. or D.C. current
Antenna: Outdoor or Antenna: Judoc Indoor Loud Speaker: Built-in Controls: Two List Price: \$300

Trade Name: Power Electric Radio Phono Radio Panel Circuit: 1 stage untuned 2 transformer-coupled Batteries: Direct from A.C. or D.C. carrent Antenna: Outdoor or indoor Loud Speaker: Senarate. Loud Speaker: Separate Controls: Two List Price: \$145 Manufacturer: ATWA-TER KENT MFG. CO. 4700 Wissahickon Ave., Philadelphia, Pa. Trade Name: Atwater Kent Model 10 Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor or

Loud Speaker: Separate Controls: Three List Price: \$80 Trade Name: Atwater Kent Model 12 Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor or

Loud Speaker: Separate

Trade Name: Atwater Kent Model 20 compact Circuit: Tuned radio irequency Batteries: Storage Antenna: Outdoor or

Loud Speaker: Sepa-Controls: Three List Price: \$80

Trade Namet Atwater Kent Model 20 Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor or indoor Loud Speaker: Separate

Controls: Three List Price: \$80 Trade Name: Atwater Kent Model 24 Circuit: Tuned rad frequency Batteries: Storage Antenna: Outdoor or radio

indoor Loud Speaker: Separate Controls: Three List Price: \$100

Trade Name: Atwater Kent Model 19 Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor or indoor Loud Speaker: Separate Controls: Two List Price: \$60

Manufacturer: AUDI-OLA RADIO CO., 430 So. Green Street, 430 So. Green Street, Trade Chicago. II. 120 Chicago. III. 120 Chicago. II. 120 Chicago. III. 120 Chicag

Trade Name: Audiola
"Midget"
Circuit: Special non-regenerative
Batteries: Dry cell WD-Antenna: Outdoor Loud Speaker: Head-set

Controls: One List Price: \$10 Trade Name: Audiola "Sealed Five" Circuit: Tuned radio

frequency Batteries: Either (storage preferred) Antenna; Outdoor Loud Speaker: Separate Controls: Three List Price: \$60

Manufacturer: BALTIMORE HUB WHEEL
& MFG. CO.,
222 N. Gay Street,
Baltimore, Md.
Trade Name: Hubco
Baby Grand—portable
Circuit: Tuned radio irequency Batteries: Dry cell or

storage Antenna: Outdoor only Loud Speaker: Separate Controls: Three List Price: \$60 Trade Name: Hubco Super Five—Portable Circuit: Self-balancing neutrodyne Batteries: Dry cell or Antenna: Aerial only Loud Speaker: Sepa-

Controls: Three List Price: \$150 Trade Name: Hubco
Baby Grand
able De Luxe
Circuit: Tuned radio
frequency
Batteries: Dry cell or

Antenna: Aerial only Loud Speaker: Sena Trade Name: Hubco Baby Grand Console Circuit: Tuned radio

frequency Batteries:Dry cell or storage
Antenna: Aerial
Loud Speaker: Built-in
with space for "A"
and "B" batteries
Controls: Three List Price: \$100

Manufacturer: BILT-MORE RADIO CO., Jamaica Plain, Boston, Mass. Trade Name: Biltmore Master R.F Model T.5

T-5 Circuit: Tuned radio frequency Batteries: Dry cell or Antenna: Outdoor or loop Loud Speaker: Sepa rate Controls: Three List Price: \$68

Trade Name: Biltmore Master R-F Model T-5-C Circuit: Tuned radio frequency Batteries: Dry cell or storage Antenna: Outdoor or loop Loud Speaker: Built-in Controls: Three List Price \$160

(Continued on page 566)

The Balanced Interflex Circuit RY HUGO GERNSRACK Member American Physical Society

Rear view of the Balanced Interflex. (1) and (6), aperiodic primary; (2) and (7), secondaries of main inductances; (3) and (8), adjustable lossers; (5), (11), (14), and (16), tubes and societs; (17) automatic resistances; (12) and (18), automatic filament control jacks; (10) crystal detector; (13) and (13), audio frequency transformers; (4) and (9), traphybline frequency condensers, linearly condensers, l

N our August issue I described the In-terflex Four. This, as will be recalled, constitutes a circuit wherein a crystal detector is placed right in the grid circuit of a vacuum tube.

Excellent as this circuit is for quality, quantity and DX ability, it still has two controls; namely, the condenser tuning control

N this article me describe the first real single-control tuned radio frequency set described so far. It has but one dial or one single control -no compensation of any kind. Its volume is tremendous. It does not howl or squeal, and brings in the distant stations, all merely by turning one lone knob. It is a set which should be particularly popular with the old folk who do not wish to be bothered with more than a single knob. Stations can be logged with a single row of figures.

and the potentiometer control. Ordinarily, in radio parlance, the Interflex Four would be called a 1-dial set. Where two controls are used, however, it requires a stretch of the imagination to call two controls one

It has always been my secret ambition to roduce a multi-tube circuit which has but a single control, not just a single tuning control and then, stuck away in some obscure corner, some potentiometer or some com-pensating condenser control, or what-not. The Interflex Balanced Single-Control

Set described here is the result of ideas on single-control sets which I have cherished ever since I wrote an editorial on the subject, which appeared in the February, 1923, or later all sets will have to come to honest-to-goodness single control which I mean just one knob, and nothing

The ideal set should not oscillate; that is, it should not howl and produce shrieks from meters up to 600 meters. Stations should come in without any disturbing noises, and all the time there should be only one control or one knob to accomplish this.

these things and quite a good many besides. THEORY OF THIS SET The Balanced Tuned Interflex Four-A

comprises one stage of tuned radio frequency, crystal detector and three stages of audio frequency amplification, of which the two last stages are transformer coupled. In all tuned radio frequency circuits, if the set howls and squeals on regeneration, it is necessary to provide losses. There are several methods of obtaining such losses, but denser in such a way that there are certain absorption losses. But it is apparent that this is a very crude way of accomplishing these losses. In the first place, moving the coils even 1/64 of an inch closer to or further from the condensers will make a tre-mendous difference in signal strength. Fur-

thermore, the losses are not always fully

realized, and in spite of some constructors' claims, the majority of the sets thus made soneal and howl most annoyingly.

The coils could, of course, be made adjustable so that they could be moved toward or from the condenser. This however, would necessitate a number of extra controls, which are not wanted. Furthermore, no two sets ONE NIGHT'S PERFORMANCE OF

WJZ WQJ WTAM WSAI WGR WGRS WGBS WAHG KDKA WTAS WPG WCAU WMAK WJAZ Richmond Hill, N.Y. Pittsburgh, Pa. Elgin, Ill. 252 233 233 224 215.17

New te-Paterson, N. J. Chicago, Ill. inced Interflex takes broadcast range differences of tubes, differences of conden-sers, differences in coils, and a hundred other points which are apt to throw the set out of balance, with no means of rebalancing it. I have thought of overcoming all these defects by using an original method which, to the best of my knowledge, has not been described before

WIBJ Chie The Balanced

Granted that we must have certain losses

in order to do away with excessive oscillations, and that a set provide beet just below the control of the cont

Referring again to Fig. 1, it will be noted that the circuit from the grid of the tube to D, through coil 4 and through conscillatory circuit, while the losser circuit is independent and does not enter directly into the workings of the regular circuit. The time the workings of the regular circuit. The just as well be disconnected from the closed collatory circuit, if this, were desired, and although the results will then not be quite mains the same

In this particular circuit, if the tickler coils, of which two are used in the Balanced Interflex, are correctly adjusted, this set does a most surprising thing. The ticklers can be adjusted at the lowest available wave, say 200 meters, so that the circuit is on the point of oscillation. If correctly adjusted, impossible as this sounds, the same condition will prevail through the entire broadcast range up to 600 meters.

In other words, stations of 200 meters up to 545 meters will come in with the same intensity, with the stations in between as

In Fig. 2 the complete circuit is shown. It will be seen that we have two ticklers, 3 and 8, shunted with .005 fixed condensers. In order to produce a circuit with but a single control it was necessary to link the



Note the pristine appearance of the real one-control Balanced Interflex. No makebelieve controls stuck away in a corner here. 'Phone and loudspeaker jacks left and right respectively.

two variable condensers, as is shown in the photographic reproductions. The connection is also indicated in the dotted line, S-1 in Fig. 2. Reverting to Fig. 2, it might be thought that the tickler 8, with its condenser 19,




Fig. 1. Theoretical circuit of the Balanced Interflex. L 4 and 2 constitute varicocupler. 2 and C-3 represents the adjustable losser grounded to the filament. Crystal detector D is in the grid circuit, making the first tube a detectorcoupled amplifier. Tuning is accomplished by condenser C-2.

should be grounded to the filament of the second tube at I.7. The connection exists, although it is not immediately apparent. You may trace the connection from condenser 19 through connecting wire A to the necessary of the control of the connecting links of the two condensers S-1 to the rotor of condenser 4. Thence the circut goes down through ticklet a, which you will notice is grounded on the filament I7. Tecklet's mingli, herefore, be said to be in


The photographic illustrations show this as it appeared when completed. The variocouplers used here are factory-made his own, I have shown in Figs. 3 and 4 how the variocoupler can be built at little expense. It should be remembered, as will be seen further down, that once the ticklers are adjusted they are never touched again Hence, the construction of the ticklers need not be extraordinarily good, because they are used only when the set is first put into operation. The illustrations 3 and 4. I believe, are clear enough to give all the de-Ordinary well-seasoned cardboard tubing, which has been either shellacked ing, which has been either shellacked or dipped in hot paraffin, should be used. The tickler construction is very simple. Merely use a 1½-inch piece of tubing, through which passes a threaded 6/32 or 8/32 rod, ings can be punched right into the cardboard out, because the ticklers are not used enough. as has been mentioned. Flexible leads go from the rotor to binding post, as shown in Fig. 3. I believe the drawings are so complete that nothing else need he said about

THE DOUBLE VARIABLE CONDENSER We now come to the next important consideration, and that is the double variable condenser. In the Balanced Interflex I found it advisable to use a straight-line frequency condenser, which for many reasons is the most desirable. Two of these were coupled on one shaft, as will be seen by the photographic illustrations. Of course, you can use either a straight-line frequency condenser or any other condenser, for that matter, to suit your needs. In Fig. 5 I have shown the means of coupling the two condensers. The only piece which you will need is the connecting sleeve, which any machinist will be glad to make for you at small cost. When buying the condensers it is necessary to be the alert to see that you select one in which the shaft extends not only on the side which carries the dial, but on the opposite side as well, because if it does not, you cannot make a connection to the second con-

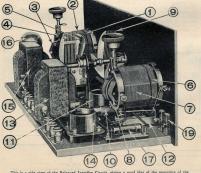Quite a few condensers on the market have a shaft that is extended, and which usually has a slot at the end. If it has not, you can



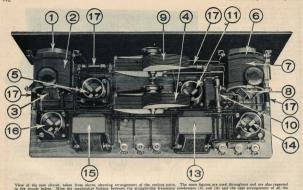This is a side view of the Balanced Interflex Circuit, giving a good idea of the mounting of variocouplers and the adjustable lossers. The figures used are the same for all illustrations. (



easily provide one with a hack-saw so that it will fit the tennon of the sleeve, as shown. The set-screw is quite important, for reasons which will be apparent later.

There are also on the market today condensers in gangs of two that you may buy ready-made, and if you use them, it is, of course, not necessary to provide any connecting sleeve, because such double condensers are usually built upon a single shaft. The adjustable sleeve method is the better, however, as you will see below.

The two condensers shown in the illustrations are supported by means of a bracket between the two. In other types of condensers it would be better to have an end bracket, as some of these condensers are rather heavy and should be supported from the end. The set shown here was made with a panel

and make a compact set. I do not, however, recommend these measurements to the average builder, because there is too much cramping: the panel should be at least 7 x 21, with a sub-base 7 x 20, if possible. Or even 7 x 24 panel with base 7 x 23 can be used. It will be noticed that the variocouplers are mounted right on the panel. This necessi-

tates drilling holes in the front panel, which have to be filled up afterward. If this fea-ture is not desired, the variocouplers may be placed upon the baseboard, but in that case we must use the larger baseboard, because with the smaller size there would be no room left. The set can then be wired as shown in our wiring diagram.

This wiring diagram, by the way, also shows a new wrinkle: the connecting lines are drawn in a peculiar manner, with a purpose in mind. As connections are made, a colored pencil is run over the lines, which will show you which connections are com-pleted. If you follow this procedure, you will leave out no connecting wires.

A front view of the set is also given, which shows the simplicity of the set. There is only one knob and the turning of this knob will not only bring in the locals, but the DX (distant) stations as well, without

(Continued on bane 547)


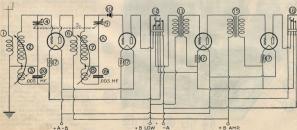


fig. 2. The complete circuit of the Balanced Interflex. (1) is the aperiodic primary; (2) secondary; (3) adjustable losser; (4) and (5) mechanical confessers; (6) untused radio frequency primary; (7) tuned regions yecondary; (9) digitable losser; (10) greaters; (12) and (13) and (14) and (15) automatic flashment control jecks; (13) and (14) and (15) accounted flashment control jecks; (13) and (14) and (14) fixed constants resistance, (14) and (15) and (16) fixed constants resistance, (15) and (16) and (16) fixed constants resistance, (15) and (16) and (16) fixed constants resistance, (15) and (16) and

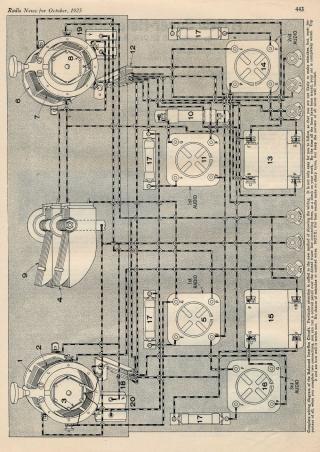

A New Super-Heterodyne

By McMURDO SILVER, A.I.R.E.



In this article is described a super-heterodyne receiver of a new type, which can be built in a very compact style.



THIS latest six-tube super-heterodyne has been called the "super-autodyne" since this name is justified by the use of but a single tube functioning as both detector and oscillator rather than the custector and oscillator rather than the cus-tomary separate detector and oscillator tubes heretofore employed. This tube is termed the "autodyne" tube, whereas the separate oscillator is generally called a "heterodyne" tube. From the the desired to the control of the tube. From this the derivation of "super-autodyne" follows logically. The entire cir-cuit is still of the "supersonic" type, since the frequency of the incoming signals is changed to that of the long-wave inter-mediate R.F. amplifier.

The circuit of the super-autodyne is shown in Fig. 1. The first tube, marked VI, is the combination detector-oscillator, connected in a balanced bridge circuit. Tubes V2 and V3 are the two intermediate frequency amplifiers, functioning at sixty kilocycles, and feeding into the second detector, V4, and then into the customary two audio amplifiers,

V5 and V6. AUTODYNE FREQUENCY CHANGER The first portion of the circuit that appears to be radical is the autodyne frequency pears to be radical is the autous of changer, the circuit of which may best be considered when isolated in Fig. 2. The problem the prevention of the oscillator section of the circuit from reacting upon the loop or antenna circuit. This is somewhat difficult, since the two circuits must be arranged to feed into the same tube, which must oscil-late at one frequency and "detect" at another, the actual separation of these two frequencies being but sixty kilocycles throughout the broadcast range. In terms of length, the oscillator must be operated at ten meters away from the loop circuit at 200 meters, and about sixty-five meters away at 550 meters in order to produce the necessary beat for the long-wave amplifier.

The solution of the problem by the use

of a bridge circuit is due to a Signal Corps engineer, Jackson H. Pressley, and is very effective. Condenser C1 tunes the oscillator grid circuit, made up of coils L2 and L3, which are really a continuous winding tapped at the center. This circuit is caused to oscillate by means of the tickler, L1, coupled inductively to L2, L3 in the usual fashion. The grid condenser and leak R1, C3, aid detection, but do not interfere with the oscillator circuit. The loop or antenna circuit, represented by B1, B2, tuned in con-denser C2, is connected to the mid-point of L3 and at the joint between CX and If we assume a condition of balance to exist between what may be considered the bridge elements, L2, L3, CX, CX, then energy induced into this circuit from BI. C2 will divide equally across the arms of the bridge, all going to waste except the voltage drop across condenser CX, across which is connected the tube's grid and fila-ment. Further, since the loop circuit is con-nected to the bridge circuit at points of neutral potential, the bridge or oscillator circuit will not react upon the loop system. With this arrangement, radiation due to

the oscillator energy feeding into the loop

ficiency to be made up, since in the autodyne circuit less than half the signal voltage is applied to the tube, the balance being lost in the bridge USE OF REGENERATION

That this efficiency is made up is evident in a comparison of the autodyne freq changer with a standard separate detector and oscillator frequency changer, for the signal strength is equal from either system and frequently in favor of the autodyne The actual manner in which this occurs appears to be due to regenerative amplification caused by the tickler, Ll, the original purpose of which was to cause the bridge to oscillate. However, at the same time as it accomplishes this, it feeds a portion of the signal energy back into the bridge circuit

Panel view of the six-tube super-het-erodyne receiver, which is remarkab-



circuit is automatically eliminated, since the system is so balanced that this cannot occur, unlike the usual "super" circuit where separate oscillator feeds directly into the detector grid circuit. With a properly designed super, radiation at its worst is not a very serious problem, however, since the oscillator-to-loop coupling is, for best results, so loose as almost to preclude radia-tion from the loop or antenna system.

So far this system looks excellent, except for the single point brought out above, vis. that the incoming signal is divided and only a small portion used to cause detection. Since the detecting efficiency of a tube is proportional to the square of the applied signal voltage, it is vitally important that maximum potential be delivered to the tube terminals. How, then, is the apparent dewhere it reinforces that portion of the sig-nal in the bridge circuit used for rectification, resulting in an even stronger signal than would at first glance be expected from the system

Were this regenerative amplification to be carried out to the limit, it would be necessary only to feed the signal energy in the plate circuit back into the loop circuit diseries with L1, but coupled to the loop or sult of such an arrangement, carefully carried out, is a tremendous increase in the sensitivity of the receiver as a whole, as well as an increase in selectivity. ter condition is due to neutralizing, in the usual fashion, the loop circuit resistance by regeneration, a condition which does not occur in the original balanced circuit of Fig. 2, since the loop circuit is so balanced as not to react or be reacted upon by the oscillator circuit. Hence, any regenerative amplification obtained in a balanced condition is merely through the reinforcing of that portion of the original signal in the bridge circuit utilized for rectification.

Having decided to use regenerative amplification in the autodyne, we see that a second tickler is necessary, or some other means of feeding the signal in the plate circuit back into the loop circuit. A simple method at once presents itself—a slight unbalancing of the bridge, allowing a por-tion of the signal energy feed from L1 into the L2, L3, CX, CX circuit to get into the loop circuit. Of course, along with this soope ercuit. Of course, along with this comes a portion of the oscillator energy, but it is indeed a simple matter so to adjust one of the balancing condensers, CX, CX, that just the required value of unbalance be obtained

This results in sharpening up the loop tuning condenser and considerable strengthening



This top view of the receiver shows how the gang vacuum tube sockets are placed in relation to

of the received signal, at the expense of a slight (but entirely negligible) tendency to The tuning, as a whole, is broadened slightly, due to reaction of the various circuits, but this is easily controlled by one of the balancing condensers, and is rather desirable, since the system is astonishingly sharp when perfectly balanced."

The only other unusual feature about the super-autodyne illustrated is the intermediate amplifier, which uses but two intermediate stages rather than the conventional three. This is made possible by the use of exceptionally efficient intermediate transformers, operating in a highly regenerative condition. This two-stage amplifier gives practically the same over-all voltage gain as could be obtained from three stages, though it would be possible to obtain proportionately the same results from any good transformers.

THE OSCILLATOR COUPLER AND

The oscillator coupler may be made by winding two sections separated 1/16 inch on a 21/4-inch tube, each section containing 28 turns of No. 28 D.S.C. wire. The rotor coil also consists of 28 turns of the same size wire on a 11/2-inch tube, rotatable within the stator tube.

Constructional data on the intermediate transformers and filter may be found in Fig. 3. It is suggested, though, that unless the builder has adequate measuring facilities that he purchase these already tested and

In wiring the receiver, a well-tinned iron should be employed in conjunction with resin-core solder. A small amount of paste

may be used on each connection if desired. but not on any of the fixed condensers. Here, connections may be soldered to lugs

Circuit diagram of the six-tube su

or to the condensers directly.

Fig. 1.

OSCILLATOR COUPLER ROTOR All Coils No. 28 DSC Wire CONSTRUCTION DETAILS TOP VIEW OF COUPLER Showing Disposition

onstructional details of the oscillator counter. These plans should be carefully followed to obtain maximum efficiency.

The under side of the shelf that sup-ports the gang tube sockets and the in-termediate and au-

panel alone. These are a connection between the rheostat and potentiometer and one between the potentiometer and S1. Busreaches the other lug to which it is to be soldered. Each piece should be bent to fit properly, cut to size and then soldered in


The "A" battery should be connected to

its lead, one tube inserted in a socket, switch closed, and rheostat R4 just turned on. If the tube lights, it should be moved from socket to socket to see that all "A" connections are correct. The positive battery lead should then be connected to the B-45 and B-90 posts. If the tube lights, the wiring or assembly is faulty and should be checked. The tube should light only when checked. The tube should ngm only the "A" battery is connected to the leads.

dio frequency transformers. This method of arrang-ing the instruments makes for s h or t The remaining batteries may be cor nected and the loop leads run to posts B1, B2 and B3. If the loop is spiral, B1 goes to the outside lead, B2 to the center tap and B3 to the inside end. Any standard

The tuning is quite simple. The tubes should be adjusted to proper brilliancy by means of the rheostat, and the potentioneter set just to the positive side of that (Continued on page 532)

illator, then come two

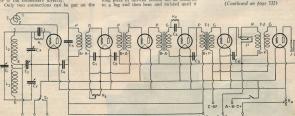

super-heterodyne receiver. The first tube on the left is the combi-tubes used as intermediate amplifiers, a detector and two A.F. tubes.


bar should be used, straightened, carefully bent and cut to proper length before any attempt is made to solder it in place. A

long piece of bus-bar should not be soldered

Extending the Broadcast Range

By SYLUAN HARRIS Rather than bemoan the inability of his set to cover the complete broadcast range, let the

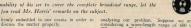radio fan read Mr. Harris' remarks on the subject.



that there will be considerable consternation on the part of many radio fans when the broadcast wave-lengths are lowered. There is also no doubt that the wave band will be lowered. There is nothing else to be done to clear up the conges-

HERE is not a shadow of a doubt



A curve taken in a three-circuit tuner, showing the change of inductance with frequency.

tion which now exists in the ether. Everyone is expecting it to happen soon. RADIO NEWS, in its May issue, first made the an-

nouncement of the extension. There will probably be a great hue and cry when the extension comes. People will say: "It has been difficult enough up to now to cover the range of 550 to 220 meters. How will it be possible to cover a range of 550 to 150?"

There will be many arguments pro and con, but in the end, no matter how much arguing is done, ways and means will be found to overcome the difficulties. At least, if the total range cannot be covered in a single step, as is now done, it will have to be done in two or more steps.

In the July issue of RADIO NEWS, a means In the July ISSUE OI KADIO MENS, a Decay of overcoming this difficulty was presented in the form of a three-range receiver, in which a total wave range of 600 to 140 meters was covered in three steps by means of a single switch. These ranges were, approximately, 600 to 400, 420 to 220, 240 to 140 meters.

This not only made possible the covering of the whole range conveniently, but at the same time, completely eliminated the crowding of stations on the dial, thus simplifying tuning considerably,

As to the possibility of covering such a wide wave band-that is another question. wide wave band that is another the point Let us look at the problem from the point of view of the variable condenser, which is there are three ideas which we must get


THE BASIC PRINCIPLES The first of these three is the idea of capacity ratio. This is very simple. It is merely the maximum capacity of the condenser divided by the minimum. words, if the maximum capacity of the con-

denser is 500 micromicrofarads and the minimum capacity is 20, then the capacity ratio of the condenser is 500/20 or 25 to 1. This is generally written 25:1.

The next idea, that of wave-length ratio, is just as simple. It is merely the longest wave-length we are considering, divided by the shortest. If we are considering a range of 600 to 200 meters, the wave-length ratio is 600/200 or 3:1.

The third, and—thank goodness—the last of these ideas needed here, is that which of these fleas needed here, is that which considers the relation between the capacity in the tuned circuit of a receiver, and the wave-length to be received. This is generally known; the wave-length is given by the formula

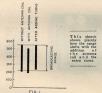 $\lambda = 1884 \text{ VL} \times C$ in which L is the inductance in the circuit in microhenries, and C is the capacity in



microfarads. The point that is of importance in connection with all this is that the wave-length is proportional to the square

root of the capacity in the circuit. That is to say, we shall have to quadruple the capacity to double the wave-length, or increase the capacity nine times to triple the wave-length. Or to look at it another way, we may regard the capacity as pro-portional to the square of the wave-length; to double the wave-length we shall have to

quadruple the capacity, etc.

Having assimilated these basic ideas, let us now co-ordinate them for the purpose of

considering a wave-length range of 600 to 200 meters. This is a wave-length ratio of 3 to 1. Since the capacity is proportional to the square of the wave-length, we should then require a capacity ratio in our tuning condenser of 9 to 1 to completely cover the

It is a relatively simple matter to cover 3-to-1 wave range with a coil and condenser isolated in space. But when the coil is coupled to another coil, as our secondary the mutual inductance between the antenna coil and the secondary reduces the effective inductance connected across the tuning con-

This was shown recently in RADIO NEWS LABORATORY. A simple single-layer coil was connected in series with a condenser and connected in series with a condenser and thermo-galvanometer. This coil had a pri-mary of a few turns wound directly upon the secondary winding. The circuit was then excited by a small oscillator, and the wave-length range of the coil and condenses noted for both the maximum and minimum settings of the condenser.

This was done by placing the condenser at the desired dial settings and measuring the wave-length with a wave-meter at which the galvanometer deflections were a maxi-

The primary coil was then connected to the antenna and ground, and without making any other changes in the circuits, simimeasurements of the wave range were taken. These measurements are given in the following table:

Maximum Minimum Capacity Capacity Without antenna 550 With antenna 198

This was not done for the purpose of ex pounding a new theory. The principles have been known for a long, long time. But it



How to keep from growing old! Separating the abort-wave stations.

is surprising how much the antenna-coupling coil can affect the wave range

Now, it was noted above that the antenna coupling has maximum wave-length to 507 meters. This will not permit us to tune in stations above 507. The present wave band extends to 550 meters. Suppose we band extends to 550 meters. Suppose we add a few turns of wire to the coil to make up for this deficiency. What will happen?

To begin with, we shall reach our 550 meters, of course. But, at the same time, we shall raise our lower wave-length limit and instead of being able to tune as low as (Continued on page 506)



consisted merely of an oscillator, on the left, and

Does a Straight-Line Frequency Condenser Exist?


By SYLUAN HARRIS

RTICLES dealing with the straightline frequency condenser were presented exclusively to our readers in the August and September issues of News. These articles by no means type of condenser. In fact, some of the lifficulties have already arisen, in spite of





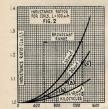coil having capacity as shown in (A) is aivalent to the circuit in (B), the inductance (B) equal to the true inductance in (A) d the capacity in (B) equal to the coil capacity in (A).



How the apparent inductance of a coil depends on the coil capacity is shown in this chart.

A radio fan came to me a few days ago and asked if it would be possible for the straight-line frequency condenser to elimi-nate what he called heterodyning between stations. By this he meant the interference which occurs from the overlapping of the side bands emitted by two stations. Every-one knows that broadcast stations are alloone knows that broadcast stations are allo-cated in channels separated by a frequency of 10 kilocycles. That is, their carrier waves differ in frequency by 10 kilocycles (or 10,000 cycles). If now, the slide bands of two stations separated by 10 kilocycles ex-ceed 5 kilocycles each, it is evident that some of these modulation frequencies will overlap, and some frequencies will be received simultaneously from both stations.

No condenser-in fact, no tuning appa-

contemporary radio periodicals in which it is stated that "there is not at the present time (and never will be) any such instrument." The writer of that article bases his statement on the fact that the characteristics of coils, which are used with the condensers in tun-

ing circuits, vary considerably.

Well, without going much further, I might say that this is a serious misstatement. this is so will be shown as we proceed. For the moment, however, I might say that the design of a straight-line frequency condenser does not depend at all upon the coil. If the calibration of the condenser departs from calibration of the condenser departs from the linear because of coil capacity, then the trouble is with the coil, and not with the condenser. In such case, why blame the con-denser? The poor condenser has already been blamed for enough trouble.

However, we are not interested in such pedantic quibbling. We are entirely inter-ested in the practical side of the matter, and it is this side that we shall consider here in detail. Let us state the problem, first recalling a few essential facts that were ex-plained in our August issue. The design of an S.L.F. condenser is based upon the as-sumption of constant inductance in the cir-cuit. It is based upon the formula:

$$f = \frac{159.3}{\sqrt{LC}}$$

in which f is the circuit frequency in kilo-cycles, L is the inductance in microhenries and C is the capacity in microfarads. By assuming L constant, we can take the square root of L and divide it into the number 159.3 and obtain a constant, K. Then if C is pro-portional to 1/d³, in which d is the dial readng, we have

and this formula plotted on graph paper will give a straight line.

Now, remember that this involves the assumption of a constant inductance. coil which is used with the condenser has some capacity (distributed), the inductance will not remain constant. We may conwill not remain constant. We may con-sider the coil having capacity as equivalent to a coil which does not have capacity con-nected in parallel with a small condenser equal to the coil capacity. For example, in Fig. 1 we have shown at A a coil which has will not remain constant. considerable inductance and a small distributed capacity. As measured between the terminals a and b, the coil has a certain inductance which is called the "apparent" inductance. This is to be distinguished from the "true" inductance, which is the induct-ance the coil would have if it did not possess

distributed capacity.

In B of Fig. I we have shown an equiva-lent arrangement. We have taken the true inductance of the coil at A (which is the inductance we should measure between the terminals a and b if the coil had no capacity) and have shunted around it a condenser having a capacity equal to the coil capacity Such an arrangement would give a measured inductance across its terminals a' and b', exactly equal to that across a and b, if the measurements were made at the same fre-

The arrangement at A in Fig. 1 is con verted into the equivalent circuit at B simply for purposes of convenience. We can easily perform computations with circuit B. We shall now consider how the apparent inductance between the a' and b' varies. We shall call the true inductance of the coil L, and the capacity of the coil C.

We shall now introduce a new idea to our of the "resistance ratio" that is considered in studying the high frequency resistance of conductors. It is the ratio of the resistance of the conductor at high frequencies to its of the conductor at high frequencies to us resistance at low frequencies, and is symbolized as R/Ro. So we can have the "inductance ratio," which is the ratio of the "apparent" inductance (as measured at high "apparent" inductance (as measured at high frequencies, taking account of the coil capacity), to the inductance as measured at low frequencies (where the effect of coil capacity is negligible). We may symbolize this as La/L, where La is the apparent in-ductance and L is the true inductance. The

formula showing the relation between these La 1 - 39.48f2 LC × 10-9 in which f is the frequency in kilocycles and C is the coil capacity in microfarads.

(Continued on page 562)

two quantities is:



The calibration curve of an S. L. F. condenses is bent slightly by the circuit capacity.

Another Three-Range Receiver

Ry the Staff of Radio News Laboratories

Here is described another receiver with a multiple range. It will tune from 40 to 555 meters and uses two stages of radio frequency.

N an article by W. B. Arvin in the June issue of Radio News, our readers were advised of changes in the broadcast wavelengths which may be considered, and which, fact, are necessary to obviate the difficulties we now have in tuning, due to the

great congestion in the ether. RADIO NEWS, realizing the great importance of familiarizing its readers with ways and means of building sets that will cover the whole range, from 600 to 150 meters, at the same time eliminating the crowding on the dials, started a series of articles in the June issue, describing sets which will meet the renuirements. The first of the series was the three-range receiver described in that issue, which is a three-circuit tuner. The arrangement of coil and condensers in the circuits is such that by means of the special switch described, it is possible to separate the whole range into three portions. This has the effect of spreading the whole range out over three circumferences of the dial. Furthermore, the whole thing is accomplished by means of



one switch, which is a very novel idea.

Multi-range receivers have been designed in the past, but as far as the writer knows, them have required a number of

The problem is rather simple when there is only one tuned circuit to consider, but when we try to make a tuned radio frequency amplifier tune over several ranges, it quency amplifier tune over several ranges, it means that a great deal of convenience and beauty of design will be lost. This is because the coils used must be either tapped or replaceable. If they are to be tapped, this means a multitude of switches, for it is obvious that all the taps cannot be brought into one switch. If they were, there would be considerable coupling between the stages which would result in decreased amplifica-



If the coils are to be replaceable, as they used to be in the days when so many experi menters used the honeycomb coils, there is the same inconvenience that applies to manipulating so many switches in the case of the make the operation of the sets as simple as possible, and certainly a half-dozen switches or coils does not by any means add to the simplicity of the set.

How the problem will finally be overcome in the commercial form of set is problematical. Of course, there is the possibility of using several switches behind the panel, all operated by a long shaft, or in-terlocked in some way by wires or toothed racks so as they can be operated simultan-eously by a single knob or lever. This method, however, is a little complicated for the average person to build, but I believe that manufacturers of sets may have to adopt it.

RADIO NEWS will bring out sets in the near future employing these methods of

range control. There are many experimenters who are laboring under the impression that the wave range can be increased merely by lowering the minimum capacities of the tuning condensers. The wave range certainly can be lowered by doing this, but it can be lowered only a very little. If you don't believe me, try this yourself. Connect two variable con-densers in series, and set both of their dials at zero. Having the two minimum capaci-ties in series will give a minimum capacity somewhere near half what it was. It will be found that if the set operates at all satisfactorily, the wave range will be lowered only by a few meters.

The set described in this article is the usual radio frequency amplifier connected to a detector and two stages of audio frequency amplification. Regeneration is controlled by a potentiometer, as shown in the wiring dia-

gram Fig. 1. The three wave-length ranges are obtained shown in the accompanying photographs. These coils are of the basket type, which anyone can wind himself very easily.


method of winding is shown in the accompanying sketch. When finished, the coils are mounted onto an ordinary tube base, which can be heated and removed from an old burnt-out electron A bit of sealing wax suffices to hold

the coil in place. Coils made in this fashion may be bought at the radio stores, if the reader does not wish to go to the trouble to "roll his own." The dimensions of the coils are all the same, these dimensions being given below

They differ only in the number of turns employed. The primary and secondary coils are wound and tied together by the lacing string. The method of winding inductance coils

that is described below will be found to be one of the easiest for the home set constructor.

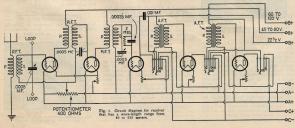The set, as described, will give a total wave range of 40 to 555 meters, and will be divided into the following ranges with a 0.0005 mfd, condenser:





This figure illustrates the method of winding the rectangular coils which are shown in the photograph below. The pegs are not laid out in a circle as is usual, but follow a rectangular path, as suggested in the text.

Coil No. 1...... 40-180 meters. Coil No. 2......100-300 "

Primary, Secondary.

Coil No. 1. 4 8

Coil No. 2. . . . 8 16

Coil No. 3. . . . 10 40

As a result of this dividing the range into three parts, it will be a very easy matter to time to the short-wave stations, where the control of the control of the control of the ent time. Many stations will be tuned in which it was heretofore impossible to hear. It is advisible to use straight-line frequency condensers in this set, as well as in any stations. The set is remarkally selective and sensitive, as all multi-stage tuned R.F. receivers should be. We take great pleasure in recommending this credit to our readers in recommending this credit to our readers receivers. All those parts of the receiver which have not been described in detail in this article are the same as those in the usual tuned R.F. set, so that no one should have any difficulty in following the wiring allowers are the support of the support of the different, the audio frequency amplifer; has been mounted directly behind the radio frequency amplifer, instead of on a line with set within small space limits and, furthermore, utilizes a considerable amount of space of the baseboard which generally goes to

METHOD OF WINDING COILS

Refined to winding colling.


The coils used in this receiver are more or less rectangular in shape. The reason for this is that in the set for which they were designed the apparatus was arranged as compactly as possible, in order to have the leads connecting the different instruments at a minimum heapth; if the coils had to be a compactly and the construction of the construction of the construction of the construction of the transformer of the construction of the transformer of the construction of the transformer of the construction of the

the transformers in the transformers in the transformers in the property of th

The Laboratory Staff of RADIO NEWS has developed another reciving set that will tune to the lower wave-lengths as well as the present broadcast band. The receiver described in the following article tunes from 40 to 555 meters, which is one of the broadest tranges RADIO NEWS has ever presented to its readers.

The receiver is not difficult to construct, as there are no complicated switches incorporated in its make-up, the variation of wavelengths being obtained by interchangeable colls that are easily constructed—EDITOR.

The primary and the secondary of these radio frequency transformer are wound on the same form and should have the number the primary and the secondary are wound, they are then bound together with this. So that the cold will retain strong string, so that the cold will retain placed in the top of an empty tube socket and the leads soldered to the prongs of the tube socket. The col is fastened in place from an old discrated "B" business."

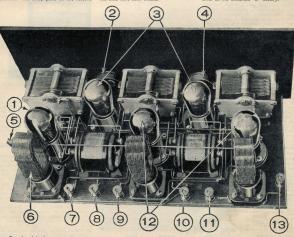

Rear view of the three-range receiver. 1 is the detector tube; 2, a potentiometer; 3, radio frequency amplifier tubes; 4, a rheostar; 5, the gridleak; 6, removable coll for different wave-lengths; 7, +45 volts; 8, +"A" and -"B"; 9, -"B"; 10, +90 volts; 11, antenna binding post; 12, audio frequency amplifier tubes; 13, the ground binding post; 12, and 12, and 13, and 14, and 1



Ham Co-operation—Is It Dead?

HERE, oh, where has the type of transmitting amateur gone that some of us were familiar just before the recent World War Is there some Sargasso Sea of the ether to which these souls have been irresistibly drawn and taken away from the ham game, or is there some limbo to which they have strayed? A few moments listening in on the air any evening during the present time will quickly convince anyone who has been in touch with amateur activities for a period of ten years or more that some such abode must have robbed the game of the best men that ever kept the ball rolling by good operation and co-operation. Of course, this is not to say that there are not any good operators today and that there is an absolute lack of co-operation among the active amateurs.

There are some good fists left, but evidences of co-operation are few and far be-Co-operation throughout this editorial is to mean not only co-operation between individual amateurs who are in per-sonal contact with each other, but co-operation on the air as well. In the good old days before the war, the writer at one time was making plans for the erection of a new aerial mast. As things went along he spoke and many meritorious suggestions were put forward. When the plans were finally completed, and the day for the erection of the dozen other hams on hand to aid. The mast went up in jig time and with little, if any, trouble. Compare this with the present-day situation. The writer again had occasion to design a mast for another ham and supervise its erection. Several days before the date slated for raising the mast, many hams were asked both personally and via the air to assist. Some of them assented and others excused themselves. Possibly a total of ten said that they would be on hand. On the day of the raising, just two of them came around to assist and they seemed to be a lot more willing to stand around and give advice than actually lend a hand. Before the mast was put up they stood around and discould be constructed; rather than the onlong part in particle. Finally, after much argument and discussion, the mast was not being part into particle. Finally, after much argument and discussion, the mast was not put forth created so much hard feeling among those present that the writer decided that man in such works as this. He would rather so out and hire a couple of hardy diffilation of the surface feelings would be hart during the work.

all kinds is of great help. When a new ham starts up, go over and offer to help him get started right. We are sure that he will appreciate your offer and some day he may reciprocate to your own advantage.

Another instance that will strike nearer home to the radio amateur fraternity in general is the case of the little private war that is going on at present within the con-fines of the second district. It seems that recently some of the Jersey boys became Council was being run and instead of exerdraw from that governing body. The writer has talked with several hams, both mem-bers of the council and of New Jersey clubs. It seems that mob rule is the only thing that is responsible for the secession of the clubs from the council. Certainly not one of the club members has been able to state any single valid reason why the clubs should Their representatives certainly do not seem to be performing their duty correctly if they cannot uphold the clubs whom they represent at the council meetings. Those the outsiders for incompetence are, as far as it is possible to find out, performing their duties to the best of their ability.

council is an up-and-going organization and certainly has done much for amateur radio in the eastern section of the United States.



A typical European transmitter showing a Mullard 7/50 transmitting tube.

Imagine what would happen if the inhabitants of a town-located in any one of the states of the Union were to decide suddenly that they did not like the way the state was being run, and that they were going to withdraw from the rule of that state. If this mob rule were to spread, another Civil War would undoubtedly ensue. (Continued on page 528)

A characteristic curve of the vacuum tube is supplied with every tube, so that the purchaser will know exactly how to operate his receiver or transmitter.

At Last-Individual Tube Ratings

MANY users of tubes have by this time become acquainted with the great variations that are often found in them. Sometimes the second of the second acquainted with the second of the sec

Since the advent of many independent manufacturers of electron tubes into the radio market some unreliable tubes have come to our notice. There is no way in which defects in tubes can be detected at the dealer's counter, and the purchaser has been applied to the product of the product. All that he claim to the of the product, All that he say essay some continuous products of the products of the products.

he Radio Beginner

How Does Your Set Get Its Power?

By A. P. PECK

HEN you sit listening to a con cert as it comes in on the loud speaker, do you realize where the there certainly is some power coming from the speaker. Enough of it, in fact, to set the atmosphere of the room into vibration with the sound of the voice or music, and this is no mean quantity. But the power which comes into the antenna is almost in-

Let us take some illustration which will show by comparison just how much energy is received by the set and how much is

"R" BATTERY SMALL MOVE -MENT OF HANDLE OPENS COCK ALLOWING LARGE FIG 2

An hydraulic representation of the grid action is given above.

given out by it, so that we may appreciate just what the set is adding to the incoming

signal. The ordinary antenna, at average distance The orumary antenna, at average distance from a broadcast station of the standard Class "B" type—that is, a station with an output rating of, say, 500 watts—will pick up and deliver to the first tube of the set less than ten microwatts. An appreciation of this power may be gained when we say that it isn't sufficient to raise an ordinary human hair a thousandth of an inch in one second. Very little power, to say the

But when the signal comes out of the loud speaker, a great deal of power has been gained in the passage of the signal through gained in the passage of the signal through the tube. In fact, at the terminal of the speaker, the power is on the order of 15 watts, which by comparison is some power. Following the example given above as to what this power is able to do, a little figur-ing will show that the loud speaker power is sufficient to raise a pasteboard box containing twenty cigarettes one foot in one

second. This illustration is taken from an ordinary commercial five-tube set and is nothing extraordinary.

THE TUBE A TRIGGER

Now let us see where all this power has been picked up in the travels of the signal through the set. Almost every one knows without being told that it comes from the vacuum tube. These little instruments work very much like a gun. A hunter of big game knows that he can pull a small trigger exerting very little power and bring down the largest lion or tiger. He knows also that with his finger alone he would not have the slightest chance of killing the beast. His finger and the little force it exerts on the trigger of the gun simply serve to release the power held in the cartridge of the gun. The case is the same in the vacuum tube. The infinitely small power picked up by the antenna simply serves to "trigger" the power which the tube is able to release.

We may compare the trigger of the gun to the grid of the vacuum tube, and the cali-bre of the gun to what the engineers call the amplification factor of the tube. The the amplification factor of the tube. The than to go into the wilds of an African than to go into the wide of an Artican jungle armed with a .22, because he knows that the trigger, pulled ever so hard, would not release sufficient power to kill some of not recease swith which he is sure to come in contact. He takes a larger gum—one which will surely do the desired work. Simply stated, the amplification factor of the tube means how hard it will shoot when the grid is "triggered." In the ordinary

type of tube, the so-called 201-A or 301-A type, this power ratio is 5 or 6. That is, if we put so much power into it at the grid, we shall receive five or six times that much power at the output or plate end of the tube.

Now in our set which gave power sufficient to raise the pack of cigarettes we had five tubes. Into the first one we placed an infinitely small power. After it passed through the first one, the resultant power which came out at the plate and was delivered at the grid of the next tube was five

GRID IN PATH OF FLOW



This illustration shows graphically how the grid stands in the path of the heavy "B" bat-tery current.

or six times what passed into the first one. At the second tube, this increased power was again amplified five or six times, thus each of the following tubes the power was again multiplied by the amplification factor so that when we passed the final output through the loud speaker we had 3,000 or 4,000 times the original power, depending on what the engineers call the efficiency of the

An instrument which will increase power in such proportions certainly is an interesting device. Last month, in this place, we told you of what the engineers and radiotricians call the "characteristic" of the tube. But at that time we did not tell how the tube worked. After showing what the tube is able to do in the line of increasing power, we may as well explain how this amplification is performed. In other words, we shall

(Continued on page 494)

the grid are enabled to control a current of many times their own magnitude.



NEGATIVE GRID NO CURRENT FLOW




POSITIVE GRID GREAT CURRENT FLOW

FIG. 4

All About Filters

By EDWARD W. BERRY

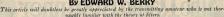



EPHONY has today reached such a state of development that not only must the voice be carried in an intelligible manner, but it must also be a true reproduction of the original, free from distortion and unaccompanied by disturbing Even the modern practice of telegraphy is beginning to demand the pure wave. Consequently, it has become necessary to provide, as nearly as possible, a pure direct current for excitation. To accomplish this filters have been employed. At the present time the most practical source of plate sup-ply in general use is either the D.C. gen-erator or chemically rectified A.C.

In a previous article-Radio News for 1924-the writer undertook the August. study of the wave forms of the predominant ripples in the generator. Here we found that the composite ripple consists of its two fundamental waves, slot ripple and commu-tator ripple. The slot ripple frequency was


$$Fs = \frac{\text{No. of slots X R.P.M.}}{60}$$

and the commutator ripple was equal to:
No. of segments X R.P.M.

That is, a generator having 16 armature slots and 48 commutator segments revolving at a speed of 3600 R.P.M. would have a slot ripple frequency per second of 960 and a commutator ripple of 2,880. We also learned that the composite wave form could be greatly changed by various brush settings in the case of the double commutator machine, the brushes might be so set that one commutator ripple tends to neutralize The slot ripples at both commutators always remain in phase with each other and no amount of brush shifting will The use of the uneven number alter them. of slots doubles the frequencies and also re-duces the amplitude of the various ripples duces the amplitude of the various ripples. Besides these well-defined ripples there is present a small amount of disturbance due to the sliding contact of the brushes on the commutator. These latter impulses have no definite form and are, in the properly functioning generator, very minute in compari-son with the main ripples. The sum of all the disturbing impulses in a well-designed generator is small usually a fraction of one

per cent, of the total voltage of the machine. The chemically rectified A.C. is an en-tirely different proposition. The proper use of an even number of tubes in so-called selfrectifying circuits eliminates the half-cycle interruptions in transmission. That is, tubes alternate, one tube or group of tubes working, while the others are idling. Every tube is idle for half a cycle. The ripple in this case is one frequency only, disregarding, of course, harmonics which in modern power supplies are negligible.

DIRECT AND RECTIFIED SUPPLY The D.C. generator and the rectified A.C. supply present the following propositions: In the D.C. generator supply there is a large D.C. component with a small A.C. com-ponent superimposed. Our aim here should be to pass as much of the D.C. as possible and to completely block out the A.C., or, more exactly speaking, the fluctuating volt-age. If in the case of the A.C. supply we blocked the ripple, there would be no supply

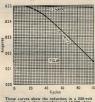

These curves show the reduction in a 250-volt ripple, with a plate impedance of 10,000 ohms.

This means that first it will be necessary to obtain a D.C. component that does not drop to a small fraction of the maximum not drop to a small fraction of the maximum or peak voltage every half-cycle. We must smooth off the peaks and fill in the valleys, so to speak. This is accomplished by the "smoother" type of filter, to be described below. Having obtained an effective D.C.



working knowledge of the functioning of condensers and inductances and therefore will not burden him with it here. If he has it may be obtained from any one of a number of standard textbooks. Further-more, a knowledge of complicated formula and higher mathematics is not necessary to



effectively filter plate supply from either a transformer or a generator. A knowledge of the results obtained by different combinations is a great help in intelligently applying filters. We shall, then, discuss filters more


standpoint.


In Fig. 1 we have what we might call a "raw" supply. There is no attempt here at any filter. Both the direct current and the ripple current are flowing in the plate cir-cuit. The resistance of the path between cuit. The resistance of the path between the plate and the filament is so large that it will allow only a small amount of direct current to flow. The ripple current is subject to this same resistance. If we had a constant voltage of 1,000 volts at the supply and the resistance of the path between the filament and the plate were 10,000 ohms the plate current would be .1 ampere. It the ripple voltage had been 10 volts, the ripple current would have been .001 ampere. Right now it would be well to settle one thing; that is, that there are not two kinds of current flowing through the plate. Fig. 2a is the conventional method of showing a constant voltage. In this case, it is our D.C. plate supply of 1,000 volts. Fig. 2b shows, in addition, a fluctuating voltage of 10 volts. This is the ripple voltage. These two are in series and the actual voltage across the plate is the sum of the two as indicated in Fig. 2c. The voltage in our example keeps ig. 2c. changing from 1,000 volts to 1,010 (Fig. 2c) Likewise, the current through the plate cir-cuit keeps changing from ,100 ampere to 101 ampere. It is this fluctuating current, 001 ampere, that is called the ripple current Removing this ripple current means remov-ing the voltage fluctuation across the plate Ing the voltage internation across the place. There are two ways of going about this. Remove it in the supply, or reduce it after it has left the supply. That is, there will it has left the supply. That is, there will still be the fluctuation across the supply ter minals, but the fluctuation across the plate itself will have been reduced by the addi-tion of a filter between the two. With the A.C. supply in any of its forms such as "raw," chemically or mechanically rectified "raw," chemically or mechanically rectified, reducing the ripple of the supply is out of the question. With the D.C. generator the proper application of filters will not only reduce the ripple across the plate but in the

CHOKE COILS

machine as well

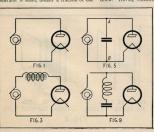In Fig. 3 we have placed an inductance in series with the plate. This inductance is no more or less than the common variety of choke coil familiar to the newest of ama-teurs. Its resistance is usually fairly small.



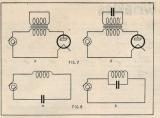

7a and 7b show two schemes using the primary of an A. F. transformes for a filter. Fig. 8a is a series reso-nant circuit, and 8b is a parallel resonant circuit.

Therefore, it makes but a small voltage drop in the direct current circuit. But to the small fluctuating ripple current it is a big hindrance. Before it can force its way through the coil, the ripple voltage has dropped and is trying to force it back again. The actual amount of the ripple current that does pass the coil depends upon the frequency of the ripple and the inductance of the coil. The inductance of the coil in this case is, we may say, a measure of its choking effect. Without worrying our heads over the "whys" of the matter, this slowing up of the varying current is accompanied by a reduction of the fluctuating or ripple voltage across the plate. If it is reduced in the choke, then only the remainder can pass through the plate. Which is which, is as immaterial to the functioning of the hen or the egg to the digestion of a good omelette. That is, each comes from the

The curves of Fig. 4 indicate the reduction in a 250-volt ripple, such as might come from the chemical rectification of a 500-volt supply, plotted against frequency For convenience, we have assumed a plate impedance of 10,000 ohms. Here it is particularly noticeable that the inductance used alone does not discriminate. That is, it does not suppress any particular frequency or band of frequencies. It simply tends to lower the ripple current more and more as the frequency increases. At the lower frequencies, such as 60-cycle, the one-henry choke, as seen from the curves, is a very poor excuse for a filter. Even the 10-henry choke does not make an effective filter. Besides the suppressing action, there is another characteristic peculiar to chokes, more espe-cially the larger types. They store up energy while the ripple is rising to a peak and tend to discharge it as the ripple voltage tends to decrease. In this way, figuraage tends to decrease. In this way, nigratively speaking, they take some of the current from the peaks and use it to fill in the valleys. That is to say, the chokes not only stop some of the ripples, but also iron out some of the kinks in the ripple that do get through. Even with this second char-acteristic the choke used alone cannot be classed as a filter.

CONDENSERS

In Fig. 5 a condenser has been placed across the supply. This condenser is also across the plate or load. Let us forget for a moment the supply and consider that the ripple remains constant, regardless of what takes place in the filter or plate circuit. The condenser, of course, is able to pass an alter-nating or fluctuating current. The amount which it passes depends upon the frequency and the voltage of the ripple and also upon the canacity of the condenser. When the direct current comes to point A, it finds but one path to travel. That is through the one path to travel. That is through the plate. The condenser does not affect it in any appreciable way. When the fluctuating current comes to point A it finds two paths— one through the plate and the other through the condenser. Some of the ripple current will be bypassed through the condenser. A and B are still at ripple potential. Then, in spite of our bypassing some ripple current as long as there is more where it came from, there will be no reduction in ripple current. One of the most common examoles of this is the lighting system in a house In a properly wired house, the lighting of one light will not dim one that is already lighted. For the condenser to have any filtering effect from bypassing, it will be necessary to bypass so much current that the source of supply begins to show signs of weakness. This is what takes place in the case of the generator.

To get a better understanding of this let us consider a generator with a ripple of 10 volts, a plate impedance of 10,000 ohms and a 1 mid. condenser across the generator terminals. The impedance of the path through A-B at zero frequency, or direct current, is infinite. By impedance we mean the resisting properties that the condenser has to both A.C. and D.C. By infinity we simply mean a very enormous number. impedance of this condenser decreases very rapidly with increase in frequency. So rapid is this decrease that the 1 mfd. condenser at 100 cycles will have an impedance of only 1,595 ohms. This would mean that the im-


pedance through the plate would be about six times that of the condenser. In other words, at 100 cycles there would be six times as much ripple current flowing through the condenser as through the plate. is being bypassed, but it is not affecting the ripple through the plate unless it is lowering the ripple voltage across the generator terminals, which in this case is also the voltage across the plate. The ripple frequencies in most generators are very much higher than 100 cycles with the result that the ripple than 100 cycles with the result that the 1100 cycles with the condenser may tend to become even larger than D.C. plate current.

All this time we have been considering that the ripple voltage has remained constant.

In a generator the great load caused by the condenser has a short-circuiting effect on the fluctuating voltage. This action is quite similar to the drop in the secondary voltage of an overloaded transformer. This then is a very important step for filtering generators. In the case of the rectified A.C. supply with its very much larger percentage ripple, this breaking-down process, due to the large load required by the filter to do it and the resulting inefficiency of the complete set, would be out of the question. There is, however, a characteristic shown by the condenser quite similar to the second charcondenser quite similar to the second char-acteristic of the inductance that we have overlooked. The condenser will store up energy on the peaks and deliver it to the load when the ripple voltage is at the bottom of the valleys. In the case of R.A.C., the condenser, like the inductance, does not make In the case of R.A.C., the a satisfactory filter when used alone.

Let us sum up the actions of these two when working alone in a circuit. The inductance is actually suppressing a certain per cent. of the A.C. component dependent per cent. of the A.C. component dependent upon the frequency and the value of the inductance. The ratio of this suppressed current to the A.C. current that would flow if the inductance were omitted may be called the efficiency of suppression. The curves of Fig. 6 show this for a 10-volt ripple on one of the smaller tubes wine a one-lawer and of the smaller tubes, using a one-henry and of the smaller tubes, using a one-nearly and a ten-henry choke. For comparison the ratio of bypassed ripple current to total ripple current with a 1-mfd, condenser under the same conditions has been plotted on the same sheet. It is rather difficult to compare the curves for inductance and for capacity on the same sheet as that for the inductance shows actual per cent. efficiency. The insert curve shows that, at about 8 cycles per sec-ond, the bypassed current has become equal to the plate ripple. At 100 cycles the curve shows that 92 per cent. of the total ripple

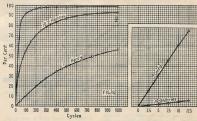current flowing is passing through the con-denser. From the foregoing we may con-(Continued on base 466)



Curves showing the ratio of the suppressed part of the A. C. component to the total A. C. This may be called the efficiency of suppression.

Radio Wrinkles

SPREADING DIAL READINGS

To most of the fans experienced in tuning the old-style condensers with most of station wave-lengths jammed in the first quarter of the dial, the arrival of the straight-line frequency condensers is a great relief. However, many set owners have two things to consider; there may be some of the old-style condensers on hand that are money for new condensers; even though they will facilitate tuning, may not always be possible. While the resulting condensers described below are not absolutely the straight-line frequency type, they will do the construction.

To make an 11-plate condenser, that size being needed in a special circuit built by the writer, a 17-plate condenser was cut down As will be seen later on, the extra number of plates are necessary, in order to give the desired capacity, to compensate for the material that is removed from the rotor plates. The rotor plates of the condenser were re-moved and taken off the shaft. Then, with



LOW WAVE SIDE HIGH WAVE SIDE ST PLATE

ROTOR PLATES ASSEMBLY FIG. 2

By trimming off a portion of the movable plates, a circular plate condenser may be con-werted into a straight-line wave-length type.

a small pair of shears, a file and emery paper to finish off, pieces were trimmed in sizes as follows

1st plate was left full size. 2nd plate sector removed equal to 15 dial

3rd plate sector removed equal to 27 dial divisions.

4th plate sector removed equal to 37 dial 5th plate sector removed equal to 45 dial

6th plate sector removed equal to 52 dial 7th plate sector removed equal to 58 dial

8th plate sector removed equal to 63 dial

It might be said here that more time and closer calculations might produce a truer curve, but the idea is the same and can be worked out for any size condenser for any

The rotor is then assembled and the unit replaced. The edges of the high-wave side will be even, while on the low side the edges will fan out and mesh in the sequences of the above table. This gives an eccentric rotor in which the smallest capacities are on the low waves and load up progressively in inverse proportion to the frequencies producing the straight-line effect

In tuning: From 0 to 15 is a 3-plate vernier condenser, from 15 to 27 is equivalent to a 15-plate condenser with only an 11-plate range, thus the kilocycles are spread out on the low waves and close together on the high, with fairly equal divisions over the whole range of the condenser, which remains the same total capacity of the oldstyle 11-plate condenser. It should be noted that great care must be taken in the preparation of the plates. Do not bend them. Also be sure, when replacing the plates, that the same number of washers are in the same Contributed by Chas. H. Stago.

AN EAR-PHONE CONDENSER

Procure an old receiver of the moulded type-the metal shell type will not do in this case-and remove the magnets, etc., from the Insert a piece of copper A into the shell, so that it fits firmly in the back, as shown in the diagram, leaving a lug on this plate long enough for the screw D to pass through. This screw will form one terminal of the condenser.

Next obtain a piece of sheet mica B, the ity which is desired in the condenser. thinner the mica, the greater will be the capacity of the condenser; about .002 of an capacity of the condenser; about so that inch serves well. Cut the mica so that it entirely covers the copper sheet A, to which it should be fastened by means of a

little shellac.

The movable plate C may be a piece of aluminum which is drilled and tapped to take a 1/4-inch machine screw with countersunk head, which screws into a tapped hole in the end of the adjusting screw E. Be sure a shade below the surface of the plate C as it will otherwise bear on the mica and keep the plates further apart than is intended, thus causing the maximum capacity of the condenser to be considerably less than is desired By means of the machine screw, screw

tte C tight against the end of screw which should be turned off square. Then run some solder around the joint on the upper end, so that it will not work loose The center hole in the ear-piece of the

receiver should then be enlarged, if necessary, and tapped out to take the brass bush-ing F, which is screwed on the outside and tapped inside to suit the thread on the ad-justing screw. To obtain fine adjustments, All the pieces should then be assembled

is shown in the diagram, particular care being taken here to make sure that plate C is absolutely parallel to plate A. important.

The diagram shows a type of panel mount-



form of an old receiver should be

ing in which X is a piece of insulating material, such as hard rubber or bakelite, with a hole cut in it, into which the phone should be a "push in" fit. This sub-panel is attached to the main panel by means of four machine screws and spacing washers, as shown, one at each corner of the sub-

A condenser such as this, if carefully made, will be very useful about the laboratory or work bench and will well repay the trouble of constructing it. may be used in any number of experiments, and its maximum capacity may always be readily calculated for different thicknesses of dielectric that may be used. Contributed by T. A. Vincent

GROUNDING A LIGHTNING SWITCH

Many radio fans use an ordinary doublepole, single-throw knife-switch for connecting the antenna and ground to their receiving set. Then another switch is employed between the antenna and ground for lightning protection. Now why not let the double pole switch serve also as a lightning switch? This would be an advantage as the lightning switch is sometimes forgotten-and the cost of a lightning switch is saved, as well.



By adding a strip of copper or bronze to a D.P.S.T. switch, an efficient lightning switch can be made.

A small strip of phospher bronze or copper about ½ or ¼ inch wide and about 1/32 inch thick is bent to the shape shown in the illustration and soldered to the ground-point of the switch, so that the strip will just touch the antenna blade when the switch is in the open position. It is easily seen that this will interfere in no manner with the proper functioning of the switch. It is well to round off the edges of the strip so that the blade will make an easy sliding contact with

When the switch is left in the open position, which it ordinarily is, the antenna will be grounded, but when the switch is closed, the ground circuit is automatically opened. Contributed by Oliver Kirchner.

ELIMINATING VIBRATION FROM THE TRANSMITTER

While installing a local transmitter, siderable annoyance was experienced the vibrating of the transmitting panel when the motor-generator unit was set in operation. After numerous experiments with several types of cushioning, including felt, hair, soft rubber, rubber sponges, and so

forth, the novel system sketched here was tried and proved to be all that could be de-sired. It did completely eliminate all traces of vibration from the transmitter and was less expensive than any other style used. Small motor-generator units can be cushioned in the same way, employing more balls, of course, because of the added weight.



The lowly rubber ball can be used efficiently for removing vibration from a set, as shown

The turned wood sockets for the balls are much cheaner than the cast-lead or glass caster-holder type, but, for best results, one the latter types is advised, inasmuch as hold their form better and have no tendency to split (which is not the case with the wood sockets unless a very hard wood is used in construction). However, for the average amateur, either type will be found very serviceable. The rubber balls may be secured in any novelty store at from five to ten cents apiece, but inspect each closely for by signs of puncture or rotting cracks.
When this system is assembled and in place it will be found to be all that could

Contributed by Louis A. Cummings.

A RADIO FREQUENCY TRANSFORMER

For those fans who want to experiment with a combination of tuned and untuned to a reduction of the number of controls on their receivers, here is an untuned radio frequency transformer that can be made easily,

quickly and cheaply, and mounted anywhere The only materials required are a tallow

andle—regardless of previous condition of servitude—and a spool of enameled copper wire, any size from No. 24 to 30. Cut off a piece of the candle, preferably a large-sized candle, to about three inches in length. Now cut two adjacent slots, as shown in the illustration, all the way around the candle, to a depth of about half an inch, being careful not to cut the candle in two. nor to break down the quarter-inch partition between the slots.



candle cut as shown above, a simple and iner pensive coupling device will be constructed

Now wind from 150 to 175 turns of wire in each slot, bringing out the terminals through small knife cuts at either end of the piece of candle. After winding, light the piece of candle that was left over and drop the hot paraffin over the knife cuts and over the windings, to serve as a binder. Some experimenting may be required to determine whether or not the leads to one side of the transformer should be reversed, but this is easily effected. To mount this transformer, hold a match under one end of, it until it begins to melt and then stick it onto any part of the baseboard that is

Contributed by Frank Savage.

METHOD FOR SUPPORTING

Any experimenter who makes his own variocouplers or variometers knows that it is a difficult job to make a rotor that is firm and will not slip. As these parts of the in-struments are most essential, the following idea is recommended for making a rotor as strong as necessary,

All rotors have two windings that are divided in the middle for anchoring the shaft, except the 180-degree type of couplers. For the average rotor, make one hole be-tween the windings in the center and another in line with it about 1/4-inch away. holes should be of a size to accommodate the average bus bar. Then bend a piece of bus bar in a U shape, the distance between the two holes in the rotor being equal to the bottom part of the U end of the bus bar to the middle of the other side, after passing the wire through the holes, and solder the other end to the shaft to which is attached the dial for rotating the rotor.



Another easy method of mounting the rotor of a coupler. This scheme employs only bus bar and a shaft.

This method gives a firm connection and makes it impossible for the rotor to slip when the dial is turned. With other types of couplers the bus bar can be connected outside the windings in the usual manner.


Contributed by Dr. C. R. Doyne.

HOME-MADE R. F. TRANSFORMER Radio frequency transformers can be

easily wound on certain forms, but the main trouble is that few experimenters are lucky enough to possess a lathe for turning the forms. A substitute for the usual form may be devised from a porcelain insulator of the type shown in the sketch. There should be five ridges around the circumference and a hole through the center for mounting purposes; this type of insulator may be pur-chased in almost any electrical shop. Be sure that the diameters of the different sections are approximately the same

The primary winding, consisting of 80 turns of No. 40 S.C.C. wire, is wound in the second and fourth sections as shown, i.e., there are 40 turns of wire in each section The secondary winding consists of 169 turns of the same size wire wound on the other three sections, with 56 turns in the first and last sections and 57 in the center one. The inside ends of the primary winding are connected and the inside ends of the two outside coils are attached to the ends of the coil wound in the middle section. The transformer may be mounted as shown in the sketch and the four leads may be brought out to the top of the small panel to binding posts.

This type of transformer will be found

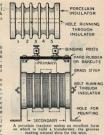

to operate in a very satisfactory manner and the cost of it is much less than any other which may be obtained on the market today, Contributed by Edward Geroux.

FASTENING A PRIMARY COIL The fan who builds his own is often con-

fronted with the problem of winding small, untuned primary coil over the secondary coil and fastening the ends so that they will be permanently fixed. Cut from heavy paper a strip like that shown in the sketch Make it as wide as the primary coil will be and leave several half-inch strips attached to one side. This is fastened to the secondary coil with collodion, the tabs extending to one side. Wind on two turns of wire before starting to wind the coil, these being the leads. After winding the first turn, bend the strips back over it and then wind on the rest of the coil over the strips which should be previously coated with collodion. After finishing the coil, wind on two more turns for leads. Bend the tabs back

STRIP FOLDED BACK AND PASTED



One of the best methods yet devised for fasten ing a primary coil that is wound over a sec

over the coil and fasten them down as shown In a few minutes the wires in the sketch can be clipped loose at the ends and the coil
will be complete, with long leads. Contributed by Clyde D. Williams.

AN EXTERNAL VOLUME CONTROL

Many of the sets purchased to-day have the internal wiring sealed so that there can be no changes made in the circuit and, sometimes, there is poor provision made for (Continued on page 504).

WHY THE OCEAN'S NEAR THE SHORE

-Radiotics-

OUITE A FEET



The radio section of the New York Evening Journal on July 23 advises the un-

A HELUVA SET!

Santa Barbara Daily Santa Barbara, Cal., y.2., shows a hook-up SUPER - HOT re-"Ah, this must be which the Master of



HOW DO THEY GET THAT WAY?

UNREASONABLE

age and never fall



Contributed by Salina M. Weller THE WOMAN'S INFLUENCE AGAIN

The July Radio World

YOUR NOSE KNOWS

advertisement from aves will suffer much om "skin effect" in get-ng through these conden-

Contributed by Thomas Gilmon

FOR "BOOTLEG" TUBES?

Contributed by John F. Inderdohen.

HORSE-PLAY!

entributed by J. L. Donaldson

NESOME anuary, 1925, is-News ap-ad-"LONESOME" PLEASE NOTICE

Contributed by William Francey

MUST BE AUTO-SUGGESTION
An advertisement in the April Ranto Naws announcement of the tight is "AU-

Cash for Radiotics

LaSh TOF Kadlofics
If you happen to see any humorous misprints in the press, we shall be glad to have
KADIOTIC. Will be accepted unless the
printed original giving the name of the
printed original giving the name of the
will pay \$1.00 fee seek RADIOTIC accepted and printed here. A few humorous
unit pay \$1.00 fee seek RADIOTIC accepted and printed here. A few humorous
company esk RADIOTIC. The most
humorous ones will be printed. Address
aft RADIOTICS to

Editor RADIOTIC DEPARTMENT, c/o Radio News.

MUST BE RHEO-STATIC In the Philadelphia (Pa.)
Inquirer of March 15 is the

husband, who is putting up considerable resistance
Contributed by J. F. Cullen FOR CLEANER RADIO

Contributed by Joseph F. Greatheart. FOOD FOR THOUGHT



A HOT ONE!

Contributed by W K Klingenemith



In the April 4 issue the Sun Radio Section, I York, N. Y., appeared

the ether, and not stone dead, geologically speak

Contributed by H. C. Baxter FOR INSPIRATION

the inspirator alone be worth the price of admission!

Contributed by A. R. Poirier.

THE "GOLD DRAIN"



IN NEW ZEALAND, BUT NOT HERE



WHAT A COIL! WHAT A COIL!





By JOHN B. BRADY

(1,541,845, M. I. Pupin. Filed December 11, 1915; issued June 16, 1925. Assigned to Westinghouse Electric & Mig. Co.)

Electrical wave receiving system in which the antenna circuit is connected with the receiving



circuit through a recurrent network of simila sections. The network contains damping residences in each section. The object of the inven-tion is to exclude from the receiving circuit al waves which are not intended to be received.



of a resonance wave-coil with an adjustable grounded metal tube operatively associated with the wave-coil. A secondary take-off circuit is coupled with the wave-coil for operation of re-

(1,537,609, J. V. L. Hogan, Filed May 19, 1922; issued May 12, 1925, Assigned to Westinghouse Electric & Mfg. Co.)
Are transmission system, wherein the purpose is to increase the radiation of the system, A non-imunoidal generator is employed and the frequency



of the main wave multiplied and the multiplied frequency fed in phase with a harmonic of the output of the generator to the antenna circuit. In this way the full power of the several frequencies is radiated,

(1.543,325, F. Dietrich. Filed December 8, 1923; issued June 23, 1925. Assigned to C. Brandes, Inc.) Head-band for telephone head-sets wherein lead-band for telephone head-sets wherein mless fabric webbing is provided over the e members which form the head-band. The



(1,544,136, F. Dietrich. Filed November 5, 1923; issued June 30, 1925. Assigned to C. Brandes,



from the telephone conductors which lead into the telephone receiver casing,

temposite receiver civing.

(1,543,47). W. S. Lemmon. Filed January 14, 1920; issued June 23, 1923.) Resonance ownerter for producing socillations for Resonance ownerter for producing socillations for a current source is provided and industance and capacity elements connected across the terminal expect of the control of the current source is provided and industance and capacity circuit tuned to the frequency of the afternating current to be produced industance and expactly elements and arranged to cooperate with the interrupter for producing societ.



lations which may be impressed upon the signaling

(1,538,466, Louis Cohen and J. O. Mauborgne, Filed October 25, 1920; issued May 19, 1925.) Electrical signaling for the reception of signals without interference arising from static. The re-



ceived energy is caused to act upon an ungrounded antenna system and pass through a wave-cool for producing a wave development on the wave-cool. The wave-coil is operatively associated with adjustable metal tubes which are changed in position along the wave-coil for the best signal reception.



Stray elimination in radio receivers, in which a baffle circuit tuned to the signal frequency is provided with a by-pass circuit including a re-actance and an intensity selector co-operating to divert preferentially stray energy from the re-ceiving system. The receiving apparatus is con-nected with the baffle circuit.

Phener No. 1,500,60, W. F. Grines. Filed June 7, 1823; issued. March 10, 1923; ...
Radio signaling system in which the signaling frequency of a transmitting station may be manitained constant. The antenna circuit of the transmitter is coupled with a pair of balanced circuit of the transmitter is coupled with a pair of balanced circuit condition. In the event that the frequency of the transmitter shifts, the control circuits become



operative to adjust the antenna circuit to the normal frequency. (1,538,472, P. Crosley, Jr. Filed May 23, 1921; issued May 19, 1925.)



Condenser of the book type in which one plate is hingedly mounted with respect to another plate by means of a cam actuated by a shaft member extending through an instrument panel.

(Patent No. 1,530,129, E. H. Loftin and H. H. Lyon, Filed April 5, 1920; issued March 17, 1925.)



Radio signaling system utilizing low extended antennae. The optimum length of the low horizontal antennae is described as being of the order of one-tenth the wave-length of an operating signal and adjusted in resonance with the signaling wave. The invention is described with reference to underground and underwater antenna systems.

(Patent No. 1,534,720, E. W. Kellogg and C. W. Rice. Filed May 18, 1921; issued April 21, 1925. Assigned to General Electric Company, New York.)

New York! Radio receiving system employing a uni-directional horizontal receiving amenia for the receiving and the receiving attached with a transmission like running parallel with a release of the receiving autenna to a distant receiving station.

*Patent Attorney, Ouray Building, Washington, D. C.

460

RADIO NEWS LABORATOR

WHE WILL SHOW I WI

ADIO mandaturers are invited to send to RADIO NEWS LABORATORIES amples of their products for test. It does not matter whether or not they advertise in RADIO NEWS, the RADIO NEWS LABORATORIES being an indicated prove to be built according to modern radio engineering practice, they will each be awarded a certification of merit, and "with the products of the provers of the pages and to modern radio engineering practice, they will each be awarded a certification of merit, and "with they are also as those given below will appear in this department of RADIO NEWS. If the appearant does not pass the Laboratory published on these pages, and only apparatus which has been tested by the Laboratories and found to be of good mechanical electrical construction is described. Hansmoch as the service of the RADIO NEWS LABORATORIES is tree to all manufactures of the respective of the RADIO NEWS LABORATORIES is tree to all manufactures and the accepted by the Laboratories and between the accepted by the Laboratories, each present the accepted of present the present

LOUD SPEAKER
This loud speaker, submitted to
e Radio News Laboratories by
e Peter Grassman Co., 366 Madi-



son Avenue, New York City, gives very fine reproduction with regard to both quality and volume. It is well made and presents an attractive AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 853.

HARCO SHELLAC This shellae, submitted by the Harco Laboratories, 312 Quincy Ave.,



Long Beach, Calif., comes in hand AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE MERIT NO. 851.

BRANSTON VERNIER DIAL The vernier dial, shown in the astration, was submitted by Chas. Branston, Inc., 815 Main St., affalo, N. Y. This dial is well use and can be used satisfactorily



in all cases where a vernier dial is required.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 868.

C-B CRYSTAL SET
This crystal set, submitted to the
Radio News Laboratories for test
by the Crain Brothers, 2304 Tele-



graph Avenue, Oakland, Calif., is shown in the illustration. This set operates satisfactorily on local stations and for short distance work.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 863.

ROVIM PHONE POST This phone post was submitted by the Rovim Mfg. Co., 318 Friendship St., Providence, R. I. It is de-



signed to accommodate the tips usu-ally found on the end of receiver cords. It presents a good appear-ance on the panel, and is very cer-tain as regards electrical contact. The phone posts are easily mounted.

AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 900.

ERLA RHEOSTAT The precision rheostat, submitted y the Electrical Research Labora-ories, Inc., 2500 Cottage Grove tyrenue, Chicago, Ill., has a reby the tories.



made and will arradio receivers,
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 842,

KANT-BLO SIGNAL The illustration shown below is of e Kant-Blo Signal which is deressive current flows from the tery, the bulb lights up, indicat-that something is wrong in the . It is made for panel mounting

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 866.



AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE OF MERIT NO. 844.

WINDHAM WIRE-FORMER

The Windham Wire-Former, furnished by the Goyer Company, Wil-limantie, Conn., to the Rabio News Ladonarosites, is shown in the illustration. This wire-former can be used satisfactorily in the construction of radio sets, provision being made for forming loops in the wire, for cutting and for stripping issual-

tion.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 859. BELDENAMEL AERIAL WIRE



The Stranded Enameled Aerial Wire, submitted to the Rano News Lanonarousins for test by the Belden Mfg. Co., 2300 S. Western Acc., Chicago, Ill., is shown in the illustration. It consists of seven strands of No. 22 copper wire. It can be used satisfactorily for an an be used satisfactorily for an according to the strands of No. 22 copper wire. tenna construction.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 360. UNCLE SAM TUNING COIL



er type, hav-ry and tickler very satisfacrily in three-circuit tuners.
AWARDED THE RADIO NEWS
ABORATORIES CERTIFICATE
F MERIT NO. 863.

SPARTAN LOUD SPEAKER
This loud speaker, submitted to
the Rabio News Labonaronius for
test by the Spartan Electric Corp.,



99 Chambers St., New York City, is shown in the illustration. It affords very good reproduction of radio concerts, without disturbing dissortion and with sufficient volume for all ordinary purposes.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 871.

This bezel was submitted to the Rapio News Laponaronies for test by the Electrical Research Labora-



The second of the panel and adds to be appearance of the set.

AWARDED THE RADIO NEWS.

ABORATORIES CERTIFICATE

OF MERIT NO. 834.

int of this resistance. This is ac-mplished by attaching an ordinary tostat to one side of this resist-ce, thus making it variable. AWARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 895.

LOMPARDI CONDENSER



SITTMANN CONDENSER



SUPERSPEAKER



very satisfactority annual policy of distortion.

ARDED THE RADIO NEWS PRATORIES CERTIFICATE IERIT NO. 891.

"NIETY" LEAD-IN

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 903.



ALL-HENRY COIL



AWARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 902.

POLYGRID AND CONDENSER

d and safely carries uired of it, THE RADIO NEWS IES. CERTIFICATE



LABORATORIES CERTIFI-VALLEY BATTERY CLIP

KEYSTONE



SCHAFFER CRYSTAL



adjusted.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 911. AERO-LOOP



SUB-BASE SOCKET



illustration. It is fitted with a threaded ring so that it can be mounted on a sub-sanel from beneath, permitting the wiring and terminals to be hidden from view.

AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 925.

DEPERCTION VERNIER DIAL

This dial, on, was sub adio Mfg. enser. WARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 921.

ABOLLO LOUD SPEAKER





WARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 800

POLK BINDING POST

rtain. AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE F MERIT NO. 922.

AMALGAM SOLDERING PASTE



AWARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 913. (Continued on page 565)

Correspondence from Readers

ABOUT RADIO TURES

Editor Pape News

I cannot help but comment on your article C Willerson This article relating to high vacuum, giving to Messrs. Langmuir and Arnold credit for high vacuum. I must

I have been in the incandescent lamp in-I have been in the incandescent lamp in-dustry for the past thirty-eight years, or since 1887, and all of my work has been along the line of exhaust, not only for in-candescent lamps, but for radio tubes and thermos bottles also. I cannot understand Mr. Wilkerson's article giving Langmuir and Arnold credit for having the only methods for producing high vacuums.

The first real high-vacuum tube made was The first real high-vacuum tube made was probably produced by Crookes or Roentgen along about 1894, in the production of the now well-known X-ray tube. Mr. Wilkerson forgets the fact that previous to the experiments of Roentgen and Crookes, Geissler had produced very high vacuums,

fact, the Geissler pump today will produce a will probably take a little longer than with the so-called Langmuir method, but a very high vacuum is produced nevertheless Another very good pump that was known long before Langmuir and Arnold was the long before Langmuir and Arnoid was the Sprengle continuous fall mercury pump, also

the Bobo and Goede rotary mercury pumps.

I have no doubt of the possibilities of Langmuir or Arnold procuring a patent on the methods of producing high vacuum by use of mercury vapor. I am, however, inclined to believe that even this is not new, because you will find in the first book of physics, generally used by first year pupils at high school, that the method used by Langmuir is demonstrated, and this book that I mention was published more than twenty years ago. In later editions of this first book, you will find that both Langmuir and Dr. Goede are given credit for mercury vapor

The writer did a lot of experimenting with mercury vapor, arsenic, various and sundry oxides, phosphor, iodine, magnesium, thalium and the like, more than twenty years ago, and you will find that the phosphor method was patented along about 1896, by a Magaleny or some such Italian name.

Mr. Wilkerson's article further states that the General Electric Company has all claims on thoriated tungsten filament. I believe this is an error. If you will look up the patents of the General Electric Company, you will find that their patent calls for pure. homogeneous tungsten, and their sole right is in incandescent electric lamps. Tungsten and thoriated tungsten were thought of and used back in 1902, and there are several German patents on such, whereas the Gen-Electric Company purchased the and Hannaman patents sometime about 1907

The article further states that the independent tube manufacturer will probably have some trouble in getting this thoriated tungsten. The mere fact that the only two concerns outside of the General Electric Company who manufactured tungsten filament are now out of business is no good reason why some others, when they realize the magnitude of the market, will not go into manufacturing it. In the meantime this material of a very good quality can be purchased in abundance in Germany, Switzerland and other countries.

Now, my real object in writing this letter as I do and taking exception to this article written by Mr. Wilkerson is that it seems to me that RADIO NEWS has tried to scare the independent tube manufacturer as this article would lead one to believe that this article would lead one to believe that an infringement on various patents; this

The writer is an engineer for one of the The writer is an engineer for one of the largest independent tube manufacturers in the United States, and he wishes to state that they are not using the Langmuir mercury vapor for high vacuums in any sense. and are producing a tube as good as the Langmuir mercury vapor system. Articles of this nature lead one to believe that no one except the large corporation may go into the manufacture of tubes—which I be-lieve to be erroneous. In a periodical such as yours, read by so many, I believe that a little more thought should be given the subject before it goes to press, and some of the facts looked into, as, in my opinion, such statements have a tendency to retard the industry

W. R. ARMSTRONG. 4049 Diversey Ave., Chicago, Ill.

(Ranto News is sever responsible for the statements made by its authors. Such state-ments are usually made in good faith, but if ments are usually made in good faith, out if NEWS is always ready to correct it.—EDI-

THREE-CIRCUIT PEGENEPATORS AND NEUTRODYNES

Editor RADIO NEWS .

Batter, RABIO News:

In regard to Mr. Sarec's letter on the advantages of the Neutrodyne and the short-comings of the regenerative set, I should like to stand up for the three-tube, three-circuit set of the two variometer, coupler and condenser type. I have experimented and concenser type. I have experimented with nearly every type of set in use for the last three years, and find that outside of the super-heterodyne class there is not a set to compare with a three-circuit set

to compare with a three-circuit set.

During the summer, signals from WEAP,
WBZ, WGY and other such stations have
been heard 900 feet away from a Magnavox loud speaker of the A3 type. During
this winter England, France and Spain were this winter England, France and Spani were heard and nearly every night in the week signals from KPO have come in through KDKA at 10 o'clock when KPO has been broadcasting stock market reports. And all of this on a loud speaker.

The set is absolutely distortionless and clear and, regarding simplicity, only the

grid and plate variometers are used in tun Nearly 300 stations have been logged in about 10 months of operation. It might be well to state that no power or radio fre-quency amplifiers were used at any time and that all of the above statements can be amply

G. HERBERT RILL, IR., Buckwood Avenue Catonsville, Md.

RADIO BROADCAST ANNOUNCERS Editor, RADIO NEWS

As a constant reader of your excellent magazine, I am taking the liberty of sending you this letter. No doubt, in the past you have received several letters regarding the many radio station announcers' shortcomings in giving the station's call letters properly.

I have just finished reading Mr. Carl H.
Butman's article, "What'll I Do When I
Can't Get the Call?" which appears on page

1442, the February issue. His article is very clear and no doubt he expresses 90 per cent, of the radio andi-

ences' opinion. Undoubtedly, some change will be absolutely necessary in the very near future for better call letter identification.

However, his idea of the "Dit Dah Dah" seems practically useless to me. One could say WNYC practically five times over while someone gave the same letters in the "Dah radio audience may be somewhat hard of hearing or have radio sets that are not now erful or selective enough to bring in the DX and though they may hear a hand concert and though they may hear a band concert from a far station fairly loud enough to know that it is a band concert, they get peevish at the announcer for not yelling his head off when he tells the station's call let-It would take some announcer to give ters. It would take some announcer to give all letters with a voice of the same power and volume that a band can give! Why not give him a megaphone? The other day I heard one of Thomas A. Edison's phonographs of the 1890 model using evlinder records, while I was at the home of a friend Everyone who has had one of these relies will remember how the selection was announced. There was no feeling in the words spoken, and the voice seemed as if spoken by someone in a trance, or under the in-fluence of some of the stuff our bootleggers peddle around in this era of Science and Invention! There are many announcers in our hest broadcast stations today who announce their call letters and programs with the same dead feeling as the announcers on the old Edison records

In my estimation, a good announcer is 70 per cent, of the radio program If he has a pleasant voice and can talk understandable English, the radio audience can overlook some of the terrible stuff put on the air occasionally. I have heard that there has been a complaint made about Roxy's announcing. He is original, his style is well liked, and this is the first time I ever heard of any complaint against him. Roxy has a personality all his own, and his announcing personality all his own, and his announcing is what saves those programs which would otherwise be a failure. I would suggest that Mr. J. A. Halman, Broadcasting Manager of WEAF, take a trip to Zion, Ill., where the "blue laws" are still in effect, and all those who support them are welcome there Let Roxy announce in his own good way, as everyone loves a breezy and cheerful an-nouncer. Let's have more of them

As I don't want to hurt anyone's feelings, I will not say here who is and who is not a good announcer. However, I am glad to say there are more good ones than bad ones. I should be happy if you could find enough space in Radio News for this letter so that

we may hear from others on this subject. Best wishes to Rapio News and three cheers for Roxy

E. Pendergast, 22 Harris St., Webster, Mass.

MR. HOWE HAS STARTED SOMETHING

Editor, RADIO NEWS:

Permit me as a one-time member of England's largest radio magazine to criticize one or two of the points in Mr. Howe's letter which appeared in your May issue.

Mr. Howe sets out from the beginning to condemn British broadcasting, and if we are to believe him I really don't understand why the B.B.C. should continue its efforts why the B.B.C. should continue its efforts having, as it appears, so dismally failed in what it set out to do. First of all, let it be understood that America had some two years' start over England and perhaps there (Continued on page 536)



Conducted by R. D. Washburne

THIS Department is conducted for the benefit of our Railo Sperimenters. We shall be glad to answer here questions for the benefit of all, but we can publish only such matter as is of unificient interest to all.

1. Department is conducted for the benefit of our Railo Sperimenters. We shall be glad to answer here questions brief.

2. Only one side of the sheet should be written upon all must be only the state of the sheet should be presented as the state of the sheet should be presented or sheet written or sheet written in all. No strettlends paid to penciled matter.

3. Satisface, Sagrama, etc., must be on separate places. The present of questions. It herever, questions sental condicabile research work, intracts calculations, patter research, etc., a special charge will be made. Refer we manter such questions, correspondents will be informed to the price charge. Mr. Washburns answers Padio questions from WRNV every Thursday at 8:30 P. M.

A MODIFIED REINARTZ SET (2143) Mr. R. W. Adams, Muskogee, Obla-

Q. 1. Is the enclosed diagram a satisfactory me? This appeared in a foreign publication and exceptional results were claimed for it.

exceptional results were claimed for it.

A. 1. We have modified the schematic circuit somewhat, as you will see (Q. 2143). Better optertion results when the 2001-unn choke coil is used. This may be wound with No. 30 S.S.C., or S.C.C. o denser—this is characteristic of Reinartz receivers. This modified Reinartz will be found one of the inext sets for all-round good operation. It is easy trouble to the control of the control of the treepond. Oscillation control is positive and easy the set of the control of the control of the control in the control of the control of the control of the instance of the control of the control of the instance of the control of the control of the control of the instance of the control of the control of the control of the instance of the control of the control of the control of the instance of the control of the control of the control of the instance of the control of the instance of the control of the contr

The 16-turn aerial coil serves a double purpose t couples the aerial to the grid, and the plate to be grid.

the grid.

A simple coil construction is shown in "Q113. A simple coil construction in shown in "Q113. A simple coil consects to the £6003 mit fixed grid condenser. A single connects to the £6003 mit fixed grid condenser. A single coil consecution is a single consecution of the consecution of the

rubber.
Q. 2. How can a Diode be used in place of a crystal, in a reflex set?
A. 2. Circuit "Q.2143-B" shows how to use the 2-telement "Fleming Valve" sppe of rectifier.
The same coil construction is followed in this receiver, as in the one described in your first in-


quiry above, with the exception that aerial coil quiry above, with the exception that aerial coil "A" will necessarily consist of a good many turns, "A" will necessarily consist of a good many turns, unistend of an aperiodic, or untuned one, winding "A" (having leads Nos. 3 and 4, with "4" being the aerial connection) will have about 45 or 50 turns and coil "B" will contain the same

A. 3. Whether you have a 2-amp, or a 5-amp, tube charger, you should find no difficulty in following circuit "Q.2143-C."

The voltage distribution in the auto-transformer

is shown.

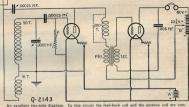Knowing the charging rate of your "B" battery,
you may determine the size lamp required to pass



An excellent two-tube diagram. In this circuit the feed-back coil and the antenna coil are com-bined in one winding. Any convenient form of coil winding may be used.

count, connection "!" being the grid connection. The second radio frequency unit (C and D) has a primary of about eight turns, the exact value to be determined by experiment, with "4" being the plate lead. The secondary, "D" will have about 45 or 50 turns, with "!" connecting to the plate of the 2-dement tube. the correct charging current by a glance at this table:

45-60 A.E. CHOKE OMED 00 SEC PRI SEC 200 OHMS 006 Q-2144

O. 3. How are "B" batteries charged from an "A" battery charging tube rectifier?

This diagram shows two sugges of tuned radio frequency amplification and three stages of stead of the usual tube detector. The second radio frequency tube circuit is reflexed for one stage of audio frequency amplification. The Double Selector Multiflex circuit of Victor Greiff, audio frequency amplification, using a crystal detector is

THE DOUBLE SELECTOR MULTIPLEX (2144) Mr. Virgin Aldrich Beauer City Nob

464

Q. 1. Some time last year Victor Greiff devel-oped a peculiar reflex circuit using a crystal de-tector and a "losser" control of circuit oscillation. Please give the constants of this circuit. A. 1. The Double Selector Multiflex circuit

A notentiometer will furnish the necessary 200

The three radio frequency transformers are An A.F. transformer secondary, or a Ford spar-coil secondary will work admirably as the A.F.

noke.

A variometer may be substituted for the first
coil radio frequency transformer.


The value of "G.L" will be about 50,000 ohms,
with "C" butters should be used and a bigher

grad back resistance. Tumbeh have deturn secondaries to be used for Tumbeh have deturn secondaries to be used to the property of the detailed of the property of the detailed of the detailed

R.F.T. The crystal detector "D" may be fixed or Be sure to maintain a non-inductive relation of

40 TO 205 METER RECEIVER

40 TO 205 METER RECEIVER
(2145) Mr. A. R. Leyque, á Ox, prês Muret,
Hte, Garonne, France, asks:
Q. 1. Please describe the construction, and show
the circuit, of a receiver designed to cover the
entire amateur wave-length operating band.
A. 1. We are not prepared to furnish such a
diagram, particularly since the amateurs have A. 1. We are not prepared to finally and a few properties of the properties of minds and a been literated to prepare to finally and the left literated to prepare to marked-paths as low receiver would require a great deal of experimental work and we do make of around the properties of the properties

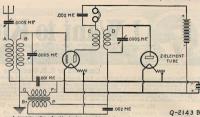

In this circuit a two-element tube supplants the usual crystal detector or etector. The descriptive text is quite complete. Battery potentials and condense values should be verified for best consultations.

THE TYPE 4DL REFLEX SET (2146) Mr. P. Raia Chett. Rangalor City (2146) 2 India, asks:

ndia, asks:

Q. 1. How is the Inverse Duplex form of reflex irreuit different from any other kind of reflex irreuit? I am particularly interested in the Inverse Juplex circuit as incorporated in the Grimes Type DL Inverse Duplex reflex receiver, a set having



Exterior view of the Renaissance Model, Grimes Inverse Duplex Receiver, incorporating the

tube detector, two stages of tuned radio fre-sency amplification and three stages of audio equency amplification, using only four dry cell A. 1. The schematic diagram of the connec-tions of a Type 4DL Grimes Inverse Duplex receiver is shown in "Q. 2146." This is one of the most up-to-date and efficient reflex circuits wated for best results.

Keeven to be raid out. By "efficient" we main the reproduction in bad (fakes are three stages and the reproduction in bad (fakes are three stages and the stages of the stage


The Principle

The Principle

The Principle

The Principle

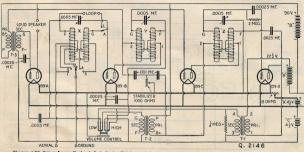Detail Q. 2146-A represents four radio vacuum tubes used in a standard reflex circuit, wherein a tube detector is used. The amplification sequence is as follows: three stages of radio frequency (Continued on page 476)



The type 4-DL Grimes Inverse Duplex (reflex) circuit. This is one of the latest developments of the reflexed principle. There is wide room for experiment in this field. Note the "C" battery blassing all amplifier tube grids, resulting in low "B" battery consumption.

NOTE—The Viking Receiving Set has been tested and approved by Radio News Testing Laboratory.



We trust you! Just fill out the order blank below and we will send this wonderful VIKING 6 TUBE RADIO RECEIVER to you express collect. Simply put he express office the atomishing low prices of \$20.5 is, supply and the express office the atomishing low prices of \$20.5 is, supply to the express of

pack it up and return to your express office. They will return your \$29.50 to you without question or quibble. No two men seem to agree as to just what a radio instru-

No two men seem to agree as to just what a radio instruent should do. There is only one wy for any man to ustify mentation of the property of the seem of the seem

or 6 Days FREI

Remember you run a solutely no risk! If you decide any time within 6 days that the VIKING 5 TUBE RECEIVER is not just what you want a radioto be, set your money back from your local express office. You will find it hard of upper the control of th

Radio Laboratories Don't Send 435 N. LaSalle St. CHICAGO a Penny ILL.

Use this Order Blank VIKING RADIO LABORATORIES,
435 N. La Salle Su, Chicago, Ill.
Gentlemen:—I want to place my short progression of UBE RADIO INSTRUMENT (with-

1 Upon receipt of this order you are to ship on VIKING \$19.50 — FIVE TUBE INSTRU MENT, completely wired, without accessories express collect, C. O. D. When this instrument of the collect of the collect

as ollows:

keep my money for 6 days. If at any time within 6 days I am not satisfied with the VIKING for any reason whatsoever, I will return it, packed the form of the first of the firs 3

4 Please ship as soon as possible and advise me when you have shipped.

City and State...

I-mfd. condenser across the terminals is at both the higher and the very low fre-

quencies superior to a 10-henry choke used

THE BELL "Shockproof" Socket

Fourteen points of contact on the side of each prong in this new socket. A straight push seats the tube; no twist needed. Tube is supported by contact springs (not the socket shell). It "floats" on springs, perfectly shockproof. Suitable for sub-panel or base mounting.



The 2-in-1 Vernier Dial

A sensitive, easily controlled dial giving coarse or 15 to 1 vernier tuning without lifting the hand from the big knurled knob. Handsome polished bakelite, with enclosed dial scale.



The BELL 3-Phone Plug


With this plug you can hook up one to three head sets in series. Plainly marked connections show how to plug in phones without confusion.

> Dealers-Write for prices and information.

BELL MANUFACTURING CO. 11 Elkins St.. Boston, Mass.

Makers of the famous BELL TIMER

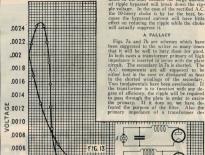All About Filters
(Continued from page 453)




0 100 200 300 400 500 600 700 800 900 1000 1100 1200 Cycles per Second

Curve A shows the by-pass effect and B the change in voltage across the plate in the circuit shown in Fig. 12.

This graph shows how the voltage across a condenser rapidly changes with the frequency


.0004

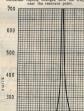

creases with the load on the secondary. If a test were to be made with the secondary open and with the secondary shorted it would be found that the ripple would actually increase when the secondary was shorted. The above also applies to 7b. Fig. 7a will not be discriminate while 7b will be discriminate. That is, 7b will intensify the ripple when a resonant combination in the secondary is

reached.

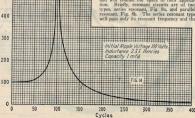For the reader who wants to know the "whys" and "wherefores" it would be a good thing if, at this point, he reviewed the sub-thing if, at this point, he reviewed the sub-thing if, at this point, he reviewed the sub-thing if, at the point is the point in t





transformers and an antennae coupler with a uniquely constructed variable primary for governing the selectivity of the antennae circuit.

can have it!

The sensational favor which Chicago and New York showered upon the AERO COIL has prompted its designers to make it available to every fan in the Nation. Vigorous plans are, therefore, under way to place the Aero Coil where every city and village can see it and witness it was the second of the Aero Coil where every city and village can e it and witness its markedly superior performance.

Declared by Chicago and New York the most SELECTIVE, most POWERFUL Inductance Ever Designed!

Enjoy the "knife-edge" selectivity with which Aero Coils cut through the tangled mass of Chicago and New York broadcasting at will! Enjoy the uncanny sensitivity with which sets built of Aero Coils pick up the far off, small, low-wattage stations that you never thought existed! Be thrilled by the amazing volume with which Aero Coils amplify for the loud speaker, reception which you have always had to listen to on the head phones! Build a 5-Tube Tuned Radio Frequency Set with Aero Coils the true low loss inductance system.

PATENTS PROTECT ITS SUPER-EFFICIENCY Its lower circuit resist-Build Your Set Now!

ance, its lower high frequency resistance, its lower distributed capacity, and the fact that its dielectric is 95% air are the reasons why the Aero Coil tunes so sharply into resonance-and why it actually uses the energy which other types of inductances waste. Hence, Aero Coil is the inductance of today-and tomorrow, and you can be assured that it is-for the construction which makes it the ideal

inductance is patented, and no induc-

Engineers recog-nize cylindrical winding to be su-perior to any other. The Aero Coil is

95% Air dielectric

No dope on
windings — All turns
air-spaced—Solonoid
(cylindrical)windings

Variable primary

them cost a bit morebut, performance considtheir price is low. \$12.00 for a set of three complete with nickel plated mounting brackets which fit any condenser. Go to your dealer's today and obtain a set of three, A circular containing complete hookups for building the most selective, most sensitive, most pov

The construction which

makes possible the far su-

perior results obtained from Aero Coils also makes

tance can be made so good as Aero Coil erful five-tube receivers ever designed unless in violation of these patents! is enclosed in each package. If your dealer has not yet obtained his stock of Aero Coils, order direct, enclosing price with your order.

Free Booklet showing new circuits and giving full constructional information of help to any fan or set builder — mailed on request.

Write for the Aero Booklet.



SUCCESSORS TO

HENNINGER RADIO MEG. CO.



Use AERO COILS

Wherever An Inductance Is Required THE ONLY AIR DIELECTRIC COILS HAVING VARIABLE PRIMARIES IN ANTENNAB

The Aero Coil 3-Circuit Tuner

tion of the pat-ented protected Aero-Coilconstruc-tion and for that

The Aero Coil Radio Frequency Regenerative Kit



Consists of one AERO COIL 3-Circuit Tuner and one AERO COIL Antennae Coupling

The Aero Coil Wave Trap Unit Also for Crystal Sets By reason of the characteristics made possible by the Aero Coil construc-tion, this unit makes a very efficient wave trop or crystal set. Price \$4.00

The Aero Coil Oscillator for Super Heterodynes



eved through use of the Aero



-for experimental hook-ups

-for permanent circuits

UNION RADIO TIP JACKS

Only 25c a pair

Handy for temporary connections, ideal for permanent mountings.

The superiority of Union Radio Tip Jacks over binding posts appeals to all set builders. Easy to attach, positive in their action. Nickel plated and substantial, nothing to chip, break or get lost. Firmly grip any size wire from No. 11 to No. 24 B & S gauge. Easily reamed to hold antenna or loading coils. These Jacks have been adopted as standard equipment by leading set manufacturers.

Three sizes for all mountings.

TYPE A for panels $\frac{\pi}{16}$ " to $\frac{1}{12}$ " thick.

TYPE B for panels, cabinet walls, partitions $\frac{5}{16}$ " to $\frac{1}{2}$ " thick.

TYPE C for panels up to 1/8" thick. Other Guaranteed Union Radio Parts

TUBE SOCKETS-Moulded condensite highly polished. Phosphor bronze contact springs. Reinforced bayonet slot. For all standard tubes.

Price 70c

DIAL ADJUSTERS - Necessary for fine tuning. Make minute dial adjustments easy. Price 69c

> At your dealer's or sent on receipt of price


RETAILERS-WHOLESALERS

Send for literature and samples of our reasonably priced Guaranteed Radio Products. Get details of our attractive proposition. Ask for illustrated pamphlet C.

UNION-RADIO-CORPORATION (
124 ~ SUSSEX ~ AVENUE - NEWARK-N.)
NEW-YORK-OFFICE - 116-WEST-322-STREET

parallel resonant type will tend to pass all frequencies except resonant frequency. The resonant frequency is equal to:

f = 159.3

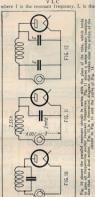

inductance of the choke in microhenries and C is the capacity of the condenser in micro-farade

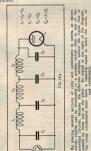


Fig. 9 shows the series resonant circuit across the line. This would be very effective for bypassing one particular frequency. As this type will pass very little current



A NEW Two-Inch Radio Panel Voltmeter of WESTON Standard Ouality

THESE Model 506 instruments fill a long felt need for small Panel Voltmeters for radio receiving sets. They have all the precision, craftsmenship of assembly and ruggedness of the famous Weston line.

Made in single and double ranges for measuring filament and battery voltages, they have an exceptionally high internal resistance—125 ohms per volt. Regularly made with a black finish and narrow flange type of case; fastened to the panel with a special type of clamp supplied with each instrument.

For further information address

Weston Electrical
Instrument Corporation
Weston Ave. Newark, N. J.





Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. EXPERIMENTER PUB. Co., 53 Park Pl, N. Y. City



Announcing The Wilson"B" Ladiopower Unit

This new unit will eliminate all "B" battery troubles. It is guaranteed not

to set up the slightest hum.

Supplies uniform voltage at all times, insuring better reception. Nothing to adjust. No moving part to get out of order. No acid to spill. Will not affect your neighbor's set. Requires no attention whatever, except to switch it on and off as you want to use your receiver. In handsomely finished solid walnut case. Price \$35.

The Andrews Paddlewhool-Coil



The coil of ideal characteristics. Has high ratio of induct-ance to resistance. Losses are negligible.

Gives maximum range and volume with entire freedom from distortion. Increases selectivity and greatly improves tone qual-ity. This coil is employed in such wellknown receivers as the Andrews DERES-NADYNE and the BUCKINGHAM and can be used in all standard hook-ups where a high grade transformer-inductance is required. Provided with nickel plated bracket for mounting. Price \$3.00. Our Technical Dept, will answer questions rela-tive to the Paddlewheel Coll and its use in any hook-up. Get blueprints of well-known receiver and circuits from your dealer or write direct.

Duo-Spiral Tolding Loop

Handsomely finished in silver and mahogany. Neat and compact. An ornament to your set-not an eyesore. Folds readily and can be used




anywhere. Ideal for portable sets. Has silvered dial gradu-



Price \$8.50

Write direct if your dealer is unable to supply these standard braducts.

Radio Units Inc. 1301 First Ave. Maywood, Ill PERKINS ELECTRIC, LTD.,
Winnipeg above and below resonance, it would not be adaptable to changes in speed caused by changing load and would not be practical for the generator. Neither would it be prac-tical when used alone for rectified A.C. as the load of the filter at resonance would probably be far greater than that of the tube and the actual reduction of the ripple would be very small.

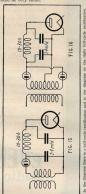

PARALLEL CIRCUITS

Fig. 10 is the parallel resonant circuit in series with the plate. This will, of course, tend to pass all frequencies except resonant frequency. For this one frequency it will be a dead stop, except, of course, to supply the losses in the filter. For the D.C. generator it is not at all practical, as it would be necessary to have one for slot ripple and another for commutator ripple, neither of which would effectively take care of the



Fig. 17. To the circuit of Fig. 16 a parallel resonant circuit has been added in order to suppress any ripple that might get through to it.

moving contact disturbances. Used alone for rectified A.C., it would tend to have too great a stopping power. Used in conjunc-tion with a smoother type filter, which has ironed out a good share of the ripple, it is ideal in removing the small A.C. component that remains.

Fig. 11 is our first approach to a good ter. It is the series resonant combination, filter. so applied that its action is two-fold. forms a series circuit which will readily bypass its resonant frequency. The choke tends to stop other frequencies and the condenser bypasses those that do pass through. There is another very important action that takes place in this type, an intelligent dis-



12-Cell - 24-Volt Storage'B'Battery

brings you this genuine AMPL-TONE Loud Speaker Unit Ten days' free trial. Your Three Dollars

unconditionally returned if at the end of ten days you are not perfectly satisfied with this Phonograph Attachment and do not find it to be of exceptional value fo volume and clear re

production. Reverse the

graph people spent years per Take advantage and use UNION FABRIC CO.

(Makers of the French Headset) DERBY, CONN.



FERBEND ELECTRIC CO



is easy to get with the right kind of set. Profits are easy to get with the righ kind of goods. Dealers write for fac HUDSON-ROSS-116 S. Wells S






TYPE 60

Five Tubes. Two stages of radio frequency, detector and two stages audio frequency. Selective, good volume and distance. Brown mahogany art 360 finish cabinst. Price



TYPE 175
ix Tubes. Special Music Master Circuit,
ery selective, long distance and splended
one quality. Built-in Music Master Reoducer. Solid mahogany cabinet in
cown mahogany art satin finish \$1.75
rice

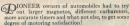Ten Models - \$50 to \$460 Guaranteed Unconditionally



degree of motoring satisfaction:

Pioneer owners of radio receiving sets likewise experimented with different tubes, more powerful batteries, condensers and all sorts of "loud speakers," trying to balance the power of the set with the quality of the amplifier. And they found that, no mixter how good their set might be, Music Master Reproducer made any good set better.

Music Master Receivers provide efficiency of radio reception equal to the quality of Muses Masters reproduction. Mustc Masters makes no claim to have developed new and sensational radio "book my. "Standardizations in the accepted principle of a result of the standard principle of the standard principle of demonstrated principles of radio research and electrical science. An authorized Muses Mastral's power of distance, claimy home if you wish—Mustc Mastral's power of distance, claimy and volume, ease of operation—and above all, it is faitful ireturation of the standard principles of the standard principles

production and superb musical tone quality.

See MUSIC MASTER—hear—com-

pare—before you buy ANY radio set. Music Master Corporation

Makers and Distributors of High-Grade Radio Apparatus

128-130 N. Tenth Street
WYORK CHICAGO PHILADELPHIA PITTEBURGH
Canadian Factory: Kitchener, Ontorio



re Tubes. New Music Master cuit, involving special adaptana to radio frequency. Vective, good volume and discetive, good volume and dissective, solid mahogany cabinet in wan mahogany art \$100 in finish. Price \$

> Canadian Prices Slightly Higher)

Music Master

Rouse Your Bigger and Better Self to Action !

I'll help you prove

Vill Fascinate You! -Will Thrill You! -Will REWARD You!

undreds of COYNE-Trained Men Earn

0 to 3200 a Week

vanced education, knowl-edge of higher RAILROAD FARE athematics.or TO CHICAGO experience in order to learn at COYNE. Earn While You



..........

little into the theory of A.C. circuits. The D.C. resistance of a good condenser is very large, usually many million ohms. Now let us consider that in Fig. 12 there is a D.C. voltage of 100 volts impressed across E. The reactance of the condenser is infinite so that, practically speaking, there is no curcurren lowing through the inductance, there will be no IR drop through the coil and the voltage Ec will be the same as E or 100 volts. The resonant frequency for this combination 2.55 henries and 1 mfd. is 100 cycles. Now in the place of the D.C. voltage, let us substitute 100 volts A.C. Keeping the 100 volts constant, let us slowly increase the frequency. As the frequency begins to increase the condenser begins to pass current. Very little at first, but as the resonant frequen 100 cycles, is neared the current rises rapidly until at resonance it has become very great As we pass beyond resonance, the current through the condenser rapidly decreases. It finally becomes even less than the very minute current that did flow when the 100-volt D.C. was applied. As resonance is ap-proached the voltage across the condenser proacned the voltage across the condenser becomes many, many times that of the orig-inal voltage. Reaching its peak at resonance, it rapidly decreases as resonance is passed As the frequency is increased beyond resonance, the voltage across the condenser continues to decrease, soon reaching a value The curve of Fig. 14 shows how this voltage across the condenser changes. It is at the point marked X that the series resonant circuit may be used as an effective filter.

If the load is connected across the condenser, If the load is connected across the condenser, as shown in Fig. 11, the decrease in the ripple voltage across the condenser means a decrease in the ripple across the plate. It is evident from the curve 14 that the effective application of this type requires as low a resonant frequency as possible, consider-



Fig. 18. The sections shown above are easier of construction than the circuit shown in Fig. 17.

ably lower than the frequencies to be filtered out. Supposing that in Fig. 11 we desired to filter out a bothersome 90-cycle ripple. The values that we have used here would not be at all practical. For at 90 would not be at all practical. For at 90 cycles the ripple voltage across the condenser, which, of course, is the same as the ripple across the plate, is much greater than the ripple of the supply. That is, instead of the supply is the same across the plate of the supply. ripple of the supply. That is, instead of reducing the ripple we are increasing it. It would have been much better if 20 to 30 henries had been used and at least 2 mid. condensers. This particular type of filter is equally effective for both rectified A.C. and the D.C. generator. When so designed that the resonant frequency is far below that of any frequency to be eliminated, it is known as a "smoother" filter. It tends to reduce all frequencies above a certain point. The larger the inductances and the capacities, the better will be the filtering. The addition of a load across the condenser will change the shape of the curves of 14-but the general results will be the same.

In Fig. 12 we have added a condenser for our filter. This gives us practically the same per than the same per than the same per than the unhindered short-circuit effect of the first condenser. With the generator this helps materially in the breaking-down process of the ripples in the generator. In the rectified A.C. this first

At Last!

-an indoor aerial that works even better than an outside wire!



Add hundreds of miles to your best distance records with this scientifically designed antenna. Consists of 100 wire strands insulated from one another and from mole

Cuts Down Static Gives Londer Signals Greater Selectivity Equipped with special fixed condensers, EFFAR-SEE gives range and vol-ume of long aerial-selec-tivity and freedom from interference of short an-tenna, Write f-

Type INL (large) \$4.00 Type BXL (small)... At any radio dealer

FISHWICK RADIO CO. 500 Edwards Bldg... Cincinnati, O.



Simplifies wiring, tuning and operation. Permits the use of any type of tube or any combination of tubes. Tested and used by more than 50 set man acturers and in every popular construc-

RADIALL COMPANY

Dept.RN-15, 50 Franklin St., New York City Write for

Hook-ups

The "SELF-ADJUSTING" Rheastat



ATWATER KENT **RADIO**

don't open the box"



Dealers, did you know-

THAT the farmers of the country have

set down in writing their preference for Atwater Kent Radio? The Meredith Publications and the Capper Publications recently asked the farmers: "What make of radio set do you

Kent was FIRST. If you have prospects in rural districts, there's a tip for you.

DEALERS have been telling us what they most like about Atwater Kent Radio.

"This sums it up," one of them said: "We send the sets to our customers' homes without opening the boxes. We know they're all right. 'Inspected' means inspected when Atwater Kent says it." Other dealers gave similar testi-

mony. Although we advise all to open the boxes and make sure there has been no accident in transportation, it is gratifying to know that they regard it as unnecessary. The word "Inspected" on the

pink tag attached to the bottom of every Atwater Kent set is a certificate of character. It means that every set has been subjected to no less than 140 gauge and physical inspections and nineteen electrical tests. All along the line of manufacture the smallest defect is a death warrant.

Even after the "final" inspection we are constantly picking Receivers from the finished array and testing them again.

Visitors at the factory sometimes think we are too fussy. That we regard as a compliment. Every dealer knows that "fussiness" at the plant relieves the customer from fussing in the home, and makes Atwater Kent Radio easy to sell.

"It is not our fault that we sell most of that make," a dealer told us. "The people take them away. Atwater Kent Radio has a good name, fastened to the people's mind with the glue of quality."

We believe in being fussy and shall continue to be.

Write for illustrated booklet telling the complete every of Atwater Kent Radio

ATWATER KENT MEG. COMPANY 4713 WISSAHICKON AVE. PHILADELPHIA, PA.

ence of the Atwater Kent Radio Artists, who broad-cast from ten stations every Thursday evening from

WEEL . wcco .























Big Money Radio Expert \$3,000 \$\times 10000 a year

Yes—\$3,000 to \$10,000 a year! These are the opportunities. The chance of a fifetime. Investigate the first interest investigate the first interest interest

We wantambitious men everywhere to learn Radio operation, construction, installation, repairing and selling. Be our representative in your neighborhood. Find out how you can qualify in a few short months, and receive our marvelous 1000 Mile Radio Outfit given as part of your training.

Train at Home-In Three Months

Find out how, in your spare time at home, by mail, without giving up your present position, mail, without giving up your present position, present position, given the present position of the present position, and the present position of the present position, which was the present position of the present position of the present position of the present position of the present position present position present position present position present position present present present present present present present graduates of this well-known copart.

"I pledge my personal attention to every member enrelling in our Association at this time.

"I pledge my personal attention to every member enrelling in our Association at this time.

questions will be answered by man, and I will work with you at every stage of the course, guiding you till fully trained, including you till fully trained, including for Operator's license."

A. G. MOHADTP

a. G. MOHAUPT Mr. Mohaupt, head of Radio Association of America, is a Graduate Electrical Engineer, University of Wisconsin; former Radio Instructor for the U. S. Government; author of "Practice and Theory of Medern Radio."

1000-Mile Radio Outfit

May From Farty Syllogar.

May From Farty Syllogar.

May From Harmation. Let us prove to you that Rodio is easier to learn and offers blager to learn and offers blager soon that you can get into. Don't wait. Act while our Special Offer of a 1000-mile Act Syllogar S

Name

Address State

condenser acts as a bypass for ripple, and bor returns energy to the circuit during the advanced and the control of the contro



There are a countless number of composite filters that can be made by using the various types of sections. The limit in variation is governed by the pocket-book. However, the more complicated may not, by any means, be the most efficient. The writer has purposely avoided mention of several other popular types of sections which, while good, have not worked out in practice as well as the "pi" type of section described above.

PEACTICAL APPLICATIONS
Figs. 15 to 21 show some practical applications of the foregoing. In 15 we have the cycle rectification. In 12 a parallel resonant circuit has been added. The resonant free this peace of the cycle rectification. In 12 a parallel resonant traction of the peace of the p



than one section. Fig. 19 shows the "pir type of filter used with a generator. Here, of course, it is not necessary to have such alenge values of indictance and capacity as the ripples are all of fairly high frequency, usually above 500 cycles. As effect of the moving contact noises. If the Heising system of modulation is to be used, large condensers across the supply will tend to shortcreative the phiere voice frequencies. This The difficulty may be overcome by the addition of an audio frequency choice, as shown



last word in tuning devices

When a micrometer control is so delicately geared that it seeks out and brings in the most elusive stations within the scope of your set with deadly accuracy, and with case, we feel that it fully deserves to be referred to as "the last word in tuning devices". Such is the Accurature. Incidentally, it can be quickly substituted for ordinary dials without alteration of your set.

MYDAR RADIO CO.
7 CAMPBELL ST., NEWARK, N.J.

ACCURATUNE

DATENTS

To the Man with an Idea

I offer a comprehensive, experience, efficient service for itsi encode, efficient service for itsi encode, efficient service for itsi education of the encode efficient of the proposition. Send sketch, or model and described the encode of th

PATENT LAWYER

2 Owen Building, Washington, D. C.
41A Park Row, New York City

The EAGLE Neutrodyne RECEIVER is "King of The Air"

Write for literature.

Insure your copy reaching you each month

Insure your copy reaching you each month. Subscribe to RADIO NEWS-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

Balkite Radio Power Units the ideal power supply for any radio set

A" CIRCUIT



Price \$19.50



The Balkist Trickle Charger Charge both 4, and 6 vole radio "I balteries at about 5 ampera-charge with a low capacity storage charger with a low capacity storage baltery for sets now using dry cells, few these particles are set of the few tubes. Farnishes more current than used by 0 dry cell or 2 storage in operation it meed be used at no other time. (3) As a "reack" or baltery sets of as many as 8 tubes, buttery sets of a storage of the sets of cycle current of cycle current sets of the sets of the decrease of the sets of the sets of the with sets of the sets of the sets of the with sets of the se The Balkite Trickle Charge

Price \$10 Vest of Rockies, \$10.50 In Canada, \$15 Balkite Radio Power Units are the ideal power supply for any radio set. They simplify and improve radio reception. They reduce the amount of attention you must give your set. With their use your current supply is always exactly what is required for each circuit.

For the "A" circuit there are the Balkite Chargers. Because of its obvious advantages the Balkite Battery Charger is the most popular charger on the market. Entirely noiseless - it is the only charger commonly used while the set is in operation.

For sets of smaller "A" current requirements-any dry cell set or sets of few storage battery tubes—there is the Balkite Trickle Charger, With a low capacity storage battery it enables owners of sets now using dry cells to make a most economical installation.

For the "B" circuit there is Balkite "B"-the outstanding development in radio. It eliminates "B" batteries entirely and supplies plate current from the light socket.

It fits any set of 5 tubes or less. For sets of six tubes or more there is Balkite "B" II, the same popular model offered last year.

Noiseless—No bulbs—Permanent

All Balkite Radio Power Units are based on the same principle. All are entirely noiseless in operation. They have no moving parts, no bulbs, and nothing to adjust, break or get out of order. They cannot deteriorate through use or disuse—each is a permanent piece of equipment with nothing to wear out or replace. They require no other attention than the infrequent addition of water. They do not interfere with your set or your neighbor's. Their current consumption is remarkably low. They require no changes or additions to your set.

An "A" battery, a Balkite Charger and a Balkite "B" constitute the most advanced power equipment on the market, one that is economical, unfailing in operation, and eliminates the possibility of run-down batteries.

Manufactured by FANSTEEL PRODUCTS COMPANY, Inc. North Chicago, Illinois

Radio Power Units



U. S. Patent



Price \$35 In Canada, \$49.50



Price \$55 In Canada, 875

The Unipower, manufactured by the Gould Storage Battery Company, is equipped with a spe-cial Balkite Radio Power Unit,

Practicosi



AMERICA'S GREATEST KNIT JACKET VALUE



in Fig. 20. A small radio frequency bypass condenser should be used, as shown. Fig. 21 shows the application of the filter to the

double commutator generator.

The basic principles for an effective filter for either the generator or rectified A.C.

supply are:
1. Use a low-pass smoother filter with a resonant frequency as low as possible, at least one-third of the lowest frequency to be filtered.

2. Have the inductance as large as is practical from an economical and resistance standpoint 3. Add another smoother section, if necessary, rather than a tuned section to a smoother filter.


0000 The application of the fil

The rapidly increasing popularity of the distributed field winding type of generator, which is usually separately excited, perhaps warrants a last-minute note on seg excited generators. The separately-excited generator adds several more ripples to the plate supply. These are slot and commutator ripple of the exciting machine and the re-sultant beat wave of the four ripples. Bonding the two negative terminals of the generator and exciter and grounding will help. A bypass condenser should be placed across the fields of both generators for protection. If the exciting generator is coupled to the high voltage generator shaft so that the two slot ripples bear the same phase relation to each other at all times, the resulting beat ripple may be materially changed by revers-ing the polarity of the exciting field. This is especially noticeable where both machines have the same number of slots in the armature. The proper setting of the coupling and the polarity of the field will reduce the ripple an amazing amount.

I Want to Know

(Continued from bage 464)

amplification (shown in dotted lines) detection, three stages of audio frequency in the first stage of audio frequency in the supplied cation of free has been assigned. That is, one volt on the grid of the first tube becomes two constants of the tube being (assumed) two. Two volts on the grid of the second tube becomes four volts on the grid of the second tube becomes four volts on the plate of that tube. (The two volts

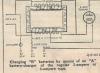

grid luput, amplified by the 'maplification con-ordinate and the property of the con-of voting at the plate). It must be under the con-trol to the control of the control of the and Q. 126-D are not actual values secured in and Q. 126-D are not actual values secured in the control of the cluster condition certains in four types of refer cross-secured and properties of the control of the control of the con-propersion is being used for certain propersion is being used for certain progression is being used for certain the con-trol of the control of the control of the con-trol of the control of the

desired manner.

RADIO HOOK-UPS



3rd Edition

Completely revised rewritten and enlarged.

16 Pages of the Latest Hook-ups Added

The most complete, practical and up-to-date radio hook-ups book obtainable. Revised and rought up to the minute by one of the foremost radio engineers in the industry.

Contains only practical, effi-cient hook-ups. Crystal sets, one tube sets, reflex, regenerative, radio frequency, and super cir-

Gives complete wiring diagrams and full instructions each and every set so that nothing further is needed in the way

of patterns or diagrams.

One of the finest books to have on hand at all times for reference as to the various types of hook-ups and the most prac-tical way of constructing each.

Send for or buy a copy today, All Orders Filled Within 24 Hours You Can Obtain a Copy at All Reliable Radio and Newsdealers



Prepaid

E.I.Company CONSRAD COMPANY, Inc.

Selling Agents 233 Fulton St., New York

Selling Customer Satisfaction

When you sell a set of both "A" and "B" Willard Radio Batteries you have given your customer:

- 1 Batteries which with an occasional recharge will last for years.
- 2 Batteries which maintain their voltage throughout the charge, and can be easily recharged.
- 3 Batteries which are an absolutely even source of power.
- 4 Batteries in which there is practically no electrical leakage from cell to cell or from cell to ground.
- 5 Batteries which are easy to hook up, for Willards have standard Fahnestock clips.
- 6 Batteries which are entirely free from shelf wear.

The Right Selling Plan for Radio Dealers

Your local Willard Service Station will act as your jobber on Willard Radio Batteries.

This means a quick source of supply of strictly fresh, well charged batteries which you can turn over to your customers in the pink of condition.

No servicing problems for you, Your local Willard Service Station assumes the responsibility for service.

Willard Radio Batteries will be advertised more extensively than ever this fall. Have your local Willard Service Station show you

WILLARD will be adverted tensively that fall. Haveyour Service Station

BATTERIES

In addition you have made a clean sale which will not involve further attention or service on your part.

Read the details of our new and practical plan for merchandising storage batteries through radio dealers. These are given in the small print at the side of this advertisement.

Willard Storage Battery Co.

Cleveland, Ohio

this advertising and explain the details of this new and practical plan for selling radio storage batteries. The advertisements will be signed:

Sales and Service thru
The Willard Battery men
and their
Associate Radio Dealers

Appropriate signs and window cards will identify you as an Associate Dealer. Booklets and other valuable selling helps will also be furnished.

Your Nearest Willard Service Station is Your Nearest Willard Jobber



Perfected with specially designed RCA Tube

The Super-Ducon replaces the "B" battery, operates from the light socket (110 to 125 volts 60 cycle A.C.) and is absolutely noiseless when properly installed.

Every radio man knows the results he gets when his "B" battery is at its best. The Super-Ducon gives him this topnotch volume all the time.

As now furnished, the Super-Ducon has a specially designed R.C.A. tube-Rectron U.V. 196, which has an average life of more than 1,000 hours.

Tested and listed by the National Board of Fire Underwriters

Write for descriptive booklet. Address 4377 Bronx Blvd., New York City

ROBISON'S RADIO TELEGRAPHY and TELEPHONY Revised

Price \$8.50 Postpaid

Send checks or money orders to Secretary-Treasurer, U. S. NAVAL INSTITUTE, ANNAPOLIS, MARYLAND, U. S. A. SPECIAL OFFER: Send \$2.00 additional and the "Storage Battery Manual, Including Principles of Storage Battery and Design, 1920," by Lieut-Comdr. L. C. Dunn U. S. Navy, will be sent postpaid. This book of 391 pages ordinarily sells for \$7.00,

RADIO BOOKS AND PATTERNS

The Consrad Company has a complete line of radio books and patterns for every man who owns or operates a radio receiver or transmitter. WRITE FOR FREE CATALOG

The Consrad Company, Inc., 233 Fulton St., New York City

even that the last amplifies table, the third freed but fir, it everythe the animans rather freedom-tion, the load dan to the ancessive and complex load, the load dan to the ancessive and complex to the last state of the animal complex and the state amplification by the same first two tables, later amplification by the same first two tables, and the last state of the last state of the later and later amplification. The last state of the later and later amplification by the same first two tables and later amplification. The later amplification of the later amplification by the same first two tables and later amplification by the later amplification of the first amplification by the later amplification of the later amplification of the later amplification by the third amplifier table is to great as to cause inself-ted amplification of the later amplification of the later amplifies the later amplification of the later amplifies the l









The sequence of amplification in four different circuits is depicted above.

the amplifier tubes, of which there are three, car-ries the minimum radio frequency current and the maximum audio frequency current; the last ampli-fier, the third tube, carries the maximum radio sier, the third tube, carriers the maximum radio frequency current and the minimum and/or fre-frequency current and the minimum and/or fre-lated in the control of the control of the con-location of the control of the control of the load imposed on the tubes. On the control of the control of the con-location of the control of the control of the load of "malanced suppliers of the control of the control of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the control of the control of the con-trol of the control of the con-trol of the control of the contro

The Schematic Diagram

This is Q. 2146. The first radio frequency am-diffier tube is "199-B," reflexed as the second audio requency amplifier tube. The second radio fre



TYPE A \$ 60 No. 1050





TYPE B De Luxe 75 No. 1080

De Luxe Mode

The Marvelous Tone Inexpensive Receivers in Solid Mahogany Cabinets

The combination of Rico Celluweld Low Loss Coils and Variable Condensers is made mechanically perfect. The Coils are welded firmly to the support of the rotor plates, a new principle. (Patents Pending.)

Selective and non-oscillating, the Rico "Auto-Balanced" Tuned Radio Frequency Set accomplished by carefully setting the neutralizing angle of the Coils at the factory; remains permanent due to the Celluweld process.

These and other features are all combined to give the radio buyer the very finest in improved 1925 Receivers.

Type A RICO-DYNE STANDARD

The Rico-Dyne Standard embodies all the features listed above and is enclosed in a beautiful solid mahogany cabinet, presenting a beautiful appearance in any home.

Type B-RICO-DYNE DE LUXE

The De Luxe Model is also enclosed in a beautiful mahogany cabinet, but extra space is provided for the wonderful "Melotone" loud-speaker unit and all batteries—what more could one ask?

The Masterpiece of Them All



Melotone Unit

ing unit—for loud speakers, phonographs, etc.—is a standard Rico-Dyne product that is guaranteed by the complete success of thousands now in use. Melotone is known throughout the radio trade. It is used everywhere. It has all the qualities of \$10 and \$12 units.

Price - - - \$7.50

Rico-Phones None Better—

None Better—
Don't pay more—
A headset of real value.

Price - - \$2.95



DEALERS JOBBERS DISTRIBUTERS
Wire immediately for our interesting new sales proposition

RADIO INDUSTRIES CORP., 131-133-137 Duane Street, New York, N. Y.

The HAMMARLUND Straight-Line-Frequency Condenser

These New Features Maintain Hammarlund Leadership

Straight - line Frequency, spacing stations equally over Single-hole mounting.

Only one small strip of ghest quality insulation, aced outside of electro-atic field.

Distributes Stations Evenly Over Your Dials

THE great radio development for 1926 is the S-L-F Condenser. It was inevitable, owing to the multiplicity of broadcast stations and the inability of old-type condensers to separate them properly.

The public erroneously classifies radio stations accord-

a ne public erroneously classifies radio stations according to wave-lengths, whereas they operate actually on particular frequencies allotted by the Government, ten kiloeycles apart. The peculiar shape of the S-LF Condenser plates is designed to separate and evenly dis-

censer plates is designed to separate and evenly dis-tribute these frequency groups over the dials. The new Hammarlund S-L-F Condenser is an engineer-ing masterpiece, with that superior neatness of design and electrical efficiency always distinguishing Hammarlund workmanship.

It is more compact and will stand more abuse than any condenser of similar type.

Made in all standard capacities Write for descriptive folder

HAMMARLUND MANUFACTURING COMPANY 424-438 West 33rd Street

For Better Radio PRODUCTS

10000000000000

Aeriola X Crystal Set \$12 Complete

ft. serial wire, 25 ft. groupd and in wire, serial insulators, porce-tube, lead-in strip, ground clamp, -tite knobs, set head phones. (With-secessories, 36,08.)

MONEY BACK GUARANTEE Send for FREE Descriptive Beeklet.

CRAIN BROS. RADIO SHOPPE 2304 Telegraph Avenue : : Oakland, Calif.



Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

quency tube, "199-C," acts also as the first undi-frequency amplifier. "P and a single property amplifier to be used only on weak signals, strong signals casily overload this tube, causing considerable dis-cipation of the signal of the si

The Audio Frequency Circuit

The definition of the state of



A standard two-coil unit. This may be used in a great many different circuits and sets. This is a convenient coil for tapping or otherwise altering.

The one-quarter megohm leak connected across the secondary of "T-1" may need to be of a dif-ferent value. Making this resistance variable re-sults in a flexibility much to be desired (in an

The Radio Frequency Circuit

cucriment recover).

The Radis Presency Circular Value Try Radis Value Try Radis Value Try Radis Value Try Val



THE new Super Unit is a diaphragm of broad pitch range, especially designed by Bristol engineers. It reproduces the high and low notes with equal truthfulness, and,

therefore, evens up the entire musical scale of either voice or instrumental music. Often the harmonics of a wonderful ensemble have been destroyed by the persistent loss of high or low notes, and the annoyance attributed to a faulty receiver when, in fact, the trouble lay wholly with the loud speaker. The Bristol Audiophone Loud Speaker with its new Super Unit of broad pitch range, and its exceptional voice of scientific devel-

opment, tells the whole tonal truth and nothing but the truth.

There are four Bristol Loud Speaker models both horn and cabinet type, priced at \$15.00 to \$30.00.

If your dealer does not carry the Bristol line, send for our illustrated folder 3025-S. We will also send free a most instructive booklet. "How To Select Your Loud Speaker."

The Super Unit with the new Low Pitch Diaphragm.

Model S Audiophone

Rubber horn 141/2 inches in diameter. Black mat finish with silvered base decora-

Models S and C (the Cabinet Model), are equipped with the new Super Unit:

BRISTOL AUDICIPHONE Loud Speaker





RIMM Entertainer is a high quality speaker at an intermediate price. Its full throated Volconite Horn tapers gently from a diameter of 1/2 inch at the opening to that of 12 inches at the bell. The diaphragm of the unit is extra large, and this combination insures that all the tones, from high of violin to low of organ, are reproduced with a fidelity comparable only to those of the concert being

broadcast.

TRIMM Superior Reproducers HEADSETS Professional - - \$5.50 Dependable - - 4.40 PHONODAPTERS Giant Unit - - \$10.00 Little Wonder - 4.50 SPEAKERS Home Speaker - \$10 Entertainer - -

Cabinette - - -

Concert - - -Chello - - -

Excellence of performance is an out-standing mark of a TRIMM product. That it is guaranteed to you for a lifetime means full protection. Be sure to investigate the complete TRIMM line before purchasing any reproducer.

RMA

dway Dept.N New

ON ONE TUBE

Vesco Radio Co., OAKLAND, CALIF.



Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

of this radio receiver that proper design of the component can overcome, in great part, the object. Now for the data: Privary, No. 28 oct. wire. Secondary, No. 28 cannoted. Winding directions of the component o



The method of oscillation control used in the type 4-DL reflex set.

The method of occillation control used in the control may be a control of the con

Some of the property of the Renaise of the Renaise

Esperanto Broadcast Lessons

(Continued from page 433) 100, cent; 1,000, mil; 1,000,000 miliono.

1,000,000,000, billono, etc. 123, centdu-dektri; 294, ducentnaŭdekkvar, 1925, mil naŭ cent dudek kvin. Ordinal numbers simply add the adjective ending a, to the cardinals: Unua,



with the characteristic curve inclosed The MUSSELMAN Certified Tube is OW science has taken the last

vestige of guesswork out of tube buying. No longer need you select your radio tubes with your shut. You may today choose tubes with an exact knowledge of such important factors as mutual conductance, plate flow, amplification constant and output impedance-if you buy MUSSELMAN Certified Electron Tubes. No other tube offers you so large a measure of satisfaction or of known value for your money.

called "the tube with a pedigree" because you will find inclosed in the carton a characteristic curve slip which gives the exact operating data on that particular tube. You do not need to take the dealer's word for the tube's quality - it's right on the curve slip, an individual record for every tube that leaves our factory. This curve shows graphically the record of the tube in the five all-important tests which determine tube efficiency.

No tube ever carried so strong a guarantee as the MUSSELMAN Certified Tube, Your dealer is authorized to return money instantly, without question or quibble, if this tube does not prove even



Over 14 years' experiis back MUSSELMAN Certified Tube. Care and pre-cision heretofore undreamed of in the manufacture of radio routine MUSSELMAN

better than we claim. MUSSELMAN Tubes cost a trifle more. They are worth more. Go to your dealer today and secure one or more of these tubes. Pay your dealer \$1.00 each for them. If, after a thorough test you are not satisfied they are the best tubes you ever tried, return them to your dealer and receive your money back. pparison with your very best tube of the vast difference in favor of this ith its "pedigree" attached.

A. J. MUSSELMAN

The Van Horne Company

547 Washington Blvd., Chicago

to type Our 3VB corresponding

understanding tubes these t to replace them purchasing rom Washington

was unable to obtain



Partners for Power



If you want distance and clear tone from your radio set, your storage battery must have its partner-the Tungar Battery Charger.

Two clips and a plug to connect to the house current. That's all there is to it. Or you can make permanent connection and just throw a switch.

The Tungar is a G-E product developed in the great Research Labora-tories of General Electric. The new Tungarcharges 2, 4, 6 volt "A" batteries; 24 to 96 volt "B" batteries, in series; and auto bat-teries, too. No extra at-tachments needed. Two ampere size (East of the Rockies) . \$18.00 60 cycles-110 volts

The Tungar charges while you sleep-it makes no disturbing noise-keeps your batteries at top notch. For power there is nothing like a good storage battery-with a Tungar to keep it good.



Tungar-a registered trademark-is found only on the genuine. Look for it on the name plate.

Merchandise Division General Electric Company, Bridgeport, Conn.

GENERAL ELECTRIC

PLIODYNE-6

\$60,00 RADIO PARTS CO., LABS., BS. AUSTIN BLVD.

SPECIAL NOTICE

We are franchising dealers for territorial rights under Sidson A. C. Receiver, the new Super-Hetro Magnetic, tuning from 5 meters to 1500, and the Harold Belevedere Receiver. Give us MERCURY ELECTRIC CORP. 2030 Grand Avenue New York, N. Y.

NA-ALD

No.old Dollars Sockets are the only ones Na-ald DeLuxe Sockets are the only ones with these three exclusive features—lowest loss, lowest capacity and positive side-scraping contact. Send for booklet and laboratory test. Alden Manufacturing Company, Dept. K10, Springfield, Mass.

FREE MONEY

in extra profits if you enjoy our dis-Also for a copy of the Salespeaker. HUDSON-ROSS-116 S. Wells St

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

first, sepa, seventh, deka, tenth, centra, hundredth, la cent-kvardek-kvina psalmo, the 145th psalm, la cent kvardek oka paĝo, the 148th page, thus adding a to last word only of a compound group. Adverbs of numerals are formed thus: firstly, unue, secondly, due, fifthly, kvine, tenthly, deke, etc. Fractions by suffix on: duono, a half, kvinono, a fifth,

dekono, a tenth, etc.

The definite article "the" is la. There is no indefinite article "a" or "an"; birdo, a bird, mi vidas domon, I see a

Words used and explained in above lesson will not be in the following vocabulary.

VOCABULARY

legi, to read; letero, letter; se, if, mono, money; infano, child; ol, than; post, after, after, affair, matter, nun, now; after, after, after, matter, nun, now monorit, to show; doni, to give; kaj, and ke, that; libro, book; veni, to come; havi, to have; est; to be; familio, family; iri, to go; alveno, arrival; preta, ready; tuta, whole, entire; nova, new; birdo, bird; pardoni, to pardon; tre, very; morgati, tomorrow; multo, much; kanbo, boy; pli, or morgati, to be able to, care diskutt, discuss; povi, to be able to, care diskutt, discuss; povi, to be able to, care (diskutt, discuss). vesto, coat, dress; akvo, water; diri, to READING EXERCISE

Mi legas la libron. Li skribis du leterojn. I-liaj patroj venos morgaŭ. Mi mem vidis vin en la domo. Se mi havus multan monon mi estus rica. La knabon mordis la hundo. Dekkvin infanoj estas en la familio. Pli ol duono iras al la lernejo. Unue, post via alveno, ni dis-lutos la aferon. Se vi estus preta, ni povus diskuti ĝin nun. La tuta grupo de sep personoj iras en la domon. Montru al mi vian novan veston. Donu al la birdoj akvon. Ni iru al li kaj mi par-donos lin. Oni diras ke li estas tre riĉa. Tri estas duono de ses, ok estas kvar kvinonoj de dek. (To be continued)

Esperanto-English Vocabulary (Continued from April, 1925, issue)

Natural oscillation, fundamenta oscilo. negative, negativa.

neon, neono; neon tube, neona tuba, node, nodo; current—, n. de intenseco; potential—, n. de tensio.

non-inductive shunt, neindukta, senindukta, ŝunto. note magnifier, sonfortigilo, malalfrekvenca, amplifikatoro.

Ohm, omo; megohm, megomo. operate, to, funkciigi; wireless opera-

tor, senfadenisto, radiisto. open radiating circuit, nefermita radianta cirkuito.

oscillate, to, oscili. oscilation, oscilo; to break into—, eko-scili; fundamental (natural)—, fundamenta o.; self- -, mem-o.; -transformer. oscila transformatoro; open- circuit

nefermita oscila sirkuito; closed—circuit, fermita o. cirkuito. oscillator, oscilatoro, oscililo. outer primary (of transformer), eliro de

primario. outer secondary (of transformer), eliro de sekundario.

output, elmeto. overload, troŝarĝo.

Panel, panelo; control-, kontrolpanelo

"as Good as Zenith"


"I WANT a radio set which will give me the same true quality of tone—the same selectivity the same volume without distortion—the same long distance range as Zenith." That is the expressed desire of thousands and thousands of radio enthusiasts.

The reason for their ambition is simply this: Zenith radio sets are never offered to the public until all laboratory experiments have been carried to a satisfactory conclusion—until in side-by-side tests with other radio sets Zenith supremacy has been completely demonstrated.

Zenith radio sets will never be produced on a quantity basis at the sacrifice of quality.

But—which is better: to be distinguished merely for volume of production—or to be distinguished for a degree of excellence so high that it sets the standard throughout the industry? Ask your nearest Zenith dealer for a demonstration.

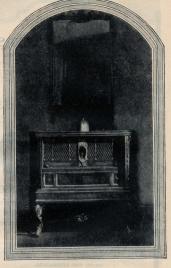ZENITH RADIO CORPORATION Straus Building, Chicago



Super-Zeniths are priced at from \$240 to \$2,000. Each instrument is sold under a quality guarantee. Above is shown the De Luxe Italian model.

Again Commander Donald B. MacMillan has chosen Zenith exclusively for his expedition to the Arctic. When human lives may depend upon the reliability of radio performance, only one reason can explain his choice: Zenith has proved to be the best obtainable, at any price.





Model 8

An efficient condenser made with new and patented one-piece stator, guaranteed to give sharp tuning at the lower broadcasting wave lengths,

Model 9

Same as Model 8, but with Vernier and Kurz-Kasch Dial. Capacity, Max. .00025, Min. .0000076, Max. .00030, Min. .000008, Max. .00035, Min. .0000086, Max. .00050, Min. .000011,



MULTIPLE CONDENSER



For Single Control Receivers

Simplify your receiver by operating two or more U. S. Tool Condenser units with only one dial-the greatest step thus far in radio reception.

Made under Hogan Patents, Jan. 9, 1912-Pat. No. 1.014.002.

WRITE FOR LITERATURE II.S.TOOL CO.INC. AMPERE N.J.

See These New Models at Your Dealer's

ELGIN SUPER-REINARTZ

New 1926 Model ELGIN RADIO SUPPLY CO. Dept. C, 207-E Chicago St., Elgin, III.

SPECIAL CATWHISKERS Twenty-five Cents Package of Ten

ama briary PREE SAMPLE CALIFORNIA RADIO MINERALS
HARRY GRANT, JR.
Oak Greve Avo... Burlingame, Calif
Tested and Approved—POPULAR RADIO

Increase Distance, Volume, Clarity Colytt" adjustable grid leak improves rece reper value of leak in grid circuit, and hold \$ 100 complete Make of teach of the complete o R. N. COLYTT LABORATORIES S6S Washington Bird., Chicago

YOU CAN GET BROWNLIE VERNIER DETECTOR \$2.00 At your dealer or Direct.

ROLAND BROWNLIE & CO. 20 Saunders St. Modferd, Mass

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

connected in-, konektita paralele, parallel, parallel, perikon, perikono.

phase, fazo, plate, plato, anodo; -circuit, plata cir-

kuito. plug, ŝtopilo; coil—, bobena ŝ. plug-in, to, enŝtopi; plug-in coil, en-ŝtopa bobeno.

pole, poluso. polyphase, multfaza.

porcelain, porcelano. positive, pozitiva. potential, tensio; —loop, ventro de t.;

potentiometer, potenciometro. power factor, faktoro de potenco.

primary, primario, primaria.

Quenched spark, estingita sparko:

-gap, estinga sparkilo. Radiate, to, radii, radiadi; radiating,

radianta. radiation, radiado. radio, radio; -amateur, r.-amatoro, radiulo; -"fan", radiamanto; -operator radiisto; — -telegraphy, r.-telegrafio; — -telephony, r.-telefonio; —station, r.-

stacio, radicio. radio frequency, radio frekvenco, alta frekvenco.

radiogoniometer, radiogoniometro. range, trafpovo.

ratio, proporcio. reaction, reakcio. receiver (person), ricevanto, ricevisto. receiver (object), ricevilo, ricevaparato;

balanced __ kompensita r.; continuous wave-, r. por kontinuaj ondoj. receiver arrangement, riceva arango, receiving apparatus, set, ricevilo, rice-

vaparato reception, ricevo, ricevado, recorder, recording apparatus, mem-skribanta aparato, mem-skribilo.

rectifier, rektifikatoro, rektifilo. rectify, to, rektifi, reflex, refleksa,

regeneration, reakcio. regulating resistance, reostato de kampo.

rejector (adj.) rejeta. relay, to, relaji. relay, relajo; high tension—, altatensia r.; key—, r. de la manipulatoro, senda

klavo. resistance, rezistanco; grid-, krada r.;

high, low-, alta, malalta r.; insulation izola r.; regulating-, reostato de kampo; variable, varia r., reostato; starting starta reostato. resonance, resonanco; -curve, reson-

anca kurvo. resonator, resonatoro rheostat, reostato: filament- filamenta

ripple, subondeto; -elimination, subondeta elimino.

root mean square (value), efika (val-

rotary spark gap, turna sparkilo. rotor, rotoro, turnbobeno.

Saturation, satureco. screened, ŝirmita.

secondary, sekundario, sekundaria. selective, selektiva; selectivity, selektiveco

self-excited dynamo, mem-ekscita dinamo self-capacity, mem-kapacito.

self-induction, mem-indukto. self-oscillation, mem-oscilo.

- -better color -lasting
- 1 -lower free sulphur -no discolor-
- 3 -higher softening point -no warping



RUBBER is the best Material electrically for Radio Panels

This is a known fact, but-

Due to discoloration in certain makes of hard rubber panels after a period of time, some people have the idea that age impairs their high electrical qualities.

An excess of the sulphur necessary in compounding hard rubber will cause discoloration and does ultimately lower electrical efficiency.

Goodrich Silvertown Hard Rubber panels will not discolor or lose their electrical efficiency. They contain less than one per cent of free sulphur.

Distinctly superior to other hard rubber panels. Specify them for maximum range and selectivity. Also the following for greatest all around satisfaction—

Goodrich V. T. Sockets — Goodrich Variometers unwound — Radiophone Ear Cushions — Spaghetti Tubing — Battery Mats.

THE B. F. GOODRICH RUBBER COMPANY
ESTABLISHED 1870

Akron, Ohio

Goodrich

Rubber Radio PRODUCTS

"Best in the Long Run"



Solved! The space problem of the straight-line frequency condenser. The new AMSCO Allocating Condenser is ingeniously designed to save room in the cabinet, yet spreads the stations evenly around the dial, according to frequency. Greatly improves the selectivity of the set, and simplifies tun-Three sizes, Single or Siamese. Ask your dealer or write Dept. F

AMSCO PRODUCTS, INC. Broome and Lafavette Streets, New York City MAKERS I MELCO SUPREME RADIO RECEIVERS

Half a Heart is the secret. Half a Heart is the shape of the rotor plates.



JUST THE BOOK YOU WANTED

"Radio News"



Volume No. 1 (Fourth Printing)

Chock full of radio constructive and learnershe printles from everyday language which everyone can understand. Section 11 coveryday language which everyone can understand. Section 11 coveryday language which everyone can understand. Section 11 coveryday language which everyone can understand. Section 12 coveryday language which everyone can understand the language langu

EXPERIMENTER PUBLISHING CO., Inc. 53 Park Place, New York

send out waves, to, elsendi ondojn, sending apparatus, sendilo, sendapar-

serkling key, manipulatoro, senda klavo. (adj.), seria; connected inkonektita serie.

sharp tuning, akuta agordo, shellac, ŝelako.

short circuit, mallonga cirkuito. shunt, sunto; highly inductive, altindukta ŝ.; non-inductive-, neindukta, senindukta ŝ.

signals, signaloj; balancing-, kompensitaj, ekvilibritaj, s. sliding contact, ŝova kontakto.

smooth, to, glatigi. solder, to, soldi, brazi. span, vantaro.

spark, sparko; quenched-, estingita s .: rotary-, turna s spark, gap, sparkilo; multiple-, mul-

topa s.; quenched-, estinga s

sparking distance, sparka distanco. specific inductive capacity (dielectric constant), dielektrika konstanto. spindle, spindelo.

spreader, apartiga stango. stable, stabila; stability, stabileco; stabilizer, stabiligilo. standard, normo; to standardize, nor-

migi. starter, startilo. static, atmosferaĵoj. station, stacio. stator, statoro, fiksbobeno.

storage battery, akumulatoro, strays, atmosferaj perturboj, atmosfe-

strength, firmeco, forteco; dielectric-, stress, streĉo; dielectric-, dielektrika

super-heterodyne, super-heterodino. super-regeneration, super-reakcio.

supersonie, supersona sustained wave, kontinua ondo. switch, to, (general term), salti, (change over) komuti, (cut out) interupti. switch (general term), ŝaltilo; changeover-, komutatoro, komutilo; cut-out-, interuptoro, interuptilo; automatic-cut-

out, aŭtomata-i.; charging—, ŝarĝ-i.; field break—, i. de kampo; high tension—, altatensia i.; double-pole—, dupolusa k.; double-throw-, duvoja k.; wave-chang-ing-, ondŝanĝa k.; rotary-, turna k. switchboard, ŝalta, komutatora, interuptora, tabulo.

synchronous discharger, sinkrona spar-

synthetic, sinteza, syntonization, sintonizo, agordo. syntonize, to, sintonizi, agordi. syntony, sintonio.

Tap, to (a coil), spili, tapi; tappings, spilaĵoj, tapaĵoj. tapper, frapilo. telautograph, telautografo; telegraph,

telegrafo. telephone, telefono; -receiver, telefon-

ilo. tension, tensio; high, low-, alta, malalta t; high - relay, altatensia relajo, terminal, binding post, borno, klemo, tetraode (four-electrode valve), tetraodo.

thermionic, termiona thermo-couple, termo-kuplo.
Thomson's formula formulo de Thom-

three-electrode valve, trielektroda val-

vo. triodo. tickler, tiklilo. transformer, transformatoro, transfor-milo; air-core—, aerkerna t.; high fre-quency—, altfrekvenca—; low frequency

malaltfrekvenca; high ratio-, altproporcia t.; low ratio—, malaltproporcia t.; oscillation—(jigger), oscila t. (ĝigero); plug-in-, enŝtopa t.

after all....

HOW WELL YOU CAN HEAR" is the only thing that really counts

FOR a few weeks after we get a new radio set we all have the "logged 57 varieties of stations last night" feeling in our blood. Then we get tired and want to sit back and have some real entertainment. For, after all, "How well you can hear" is the only thing that really counts-no matter whether the entertainment is coming from a local station or one a thousand miles away.



Acme M A-2 Audio Frequency Transform-er-more amplification without distortion.

"How well you can hear" IN THIS "how well you can hear" proposition is where quality comes in-and so does Acme. The

Acme Apparatus Company, pioneer radio and transformer engineers and manufacturers, have long made both transmitting and receiving apparatus of only the highest efficiency. Specialists in amplification, even before the days of broadcasting, this company has perfected "amplification without distortion."



Acme "Double Fre-edge Cone" Lond Speaker-for reproduc-tion without distortion.

Make this test with your set DISTORTION does not mean merely squeals and

howls. Any thing which fails to give you an exact reproduction of the human voice is distortion. Here is how vou can test vour own set. Start your radio and at the same time keep up a conversation with two or three Unless you can understand

the voice over the radio as



Amplification

easily as that of a friend several feet from you, and without any more concentration and effort than is ordinarily required in talking with him, then you have distortion.

The reason you have to concentrate when listening to a The reason you have to concentrate when listening to a voice speaking over the ordinary radio (an action unnecessary in ordinary conversation) is simply this. The individuality of the voice is lost because distortion has blurred out the overtones which give this vitality and individuality. Monotones are always hard to understand.

The whole story of distortion and how it can be over-come is carefully and fully explained in "Amplification without Distortion," a book on radio reception which is invaluable because it is written by a famous radio engine in language even the radio novice can completely underin language even the radio novice can completely under-stand. Over two hundred thousand radio enthusiasts can vouch for the service it will give you. Thousands have written us their thanks. The 9th edition is just off the written us their thanks. press. Send for your copy.

CLAUDE F. CAIRNS President, Acme Apparatus Co.

9th edition of this famous book just off press -send for your coby.

A 40 PAGE book-over 200,000 of which have been sold at 10c a copy—gives the complete story of "Amplification without Distortion." Use coupon.



| | ACME APPARATUS CO., Dept. K8, Cambridge, Mass. Enclosed find 10c (coin) (stamps) t 40 page book, "Amplification withou | to cover mailing t Distortion." | of on | е сору | 0 |
|---|--|------------------------------------|-------|--------|---|
| ı | Name | | | | |
| | Street | | | | |

UNIVERSAL PLIO-6

The Only Set That Tunes All Wave Lengths.

35 To 3600 METERS

AR Melbourne 480-WGY 109-2FL Sydney 770-WKAQ San Juan 360-2BL Sydney 350-CFF Amsterdam 2000 Karachi-Bombay-KOP-WGY 1660-6KW Tuinucu 346-Bankok-4SF Hilversum 1050-WLU-KDKA 64-KYW-3NO New Castle 400





Six tube, 2 Stages Non-Regenerative Tuned Radio Frequency Amplification, Detector and 3 Stages Distortionless Radio Amplification. Receiving range from 1,000 to 12,000 miles depending upon location, station transmitting, wave-length received and other variable factors. FULL DETAILS NOW AVAILABLE FROM MANUFACTURERS

GOLDEN-LEUTZ INC.

476 BROADWAY :-: NEW YORK CITY on Patent 1,014,002-Other Patents Pending CADI ES "EXPEDINES" NEW YORK

CARTER New "IMP" Rhoestat (Pat. Pend.)



IN COME

Smallest rhootat made. Diameter only 1½ in. Projects only ½ in. back of panel. One hole mounting. Complete with pointer hole. New exclusive Carter method of contact. Positive, amonth, silent. Same high Carter quality and standard of workmanship you know so well. See one at your dealer's today. Write for information on other Carter original Build. Carter original Radio products.

In Canada, Carter Radio Co., Limited-Terento

Parter Radio (to.

Any dealer can supply

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year
Experimenter Publishing Co., 53 Park Place, N. Y. C.

transmission, sendo, elsendo, sendado,

elesendado. transmit, to, sendi, elsendi. transmitter (person), sendanto, sen-

disto. transmitter (object), sendilo, sendaparato

transmitting apparatus, sendaparato, sendilo.

trembler, martela interuptoro. triode (three-electrode valve) tube (valve), valvo, tubo, lampo,

to, agordi, sintonizi; to re-tune, tune, reagordi; to tune out, foragordi, malagordi. tuned, agordita, sintonzita; flatly-

neakute a.; sharply-, akute a.; untuned, neagordita tuner, agordilo, sintonizilo,

tuning, agordo, sintonizo; coarse-, kruda a.; fine-, delikata, (or subtila); flat—, neakuta a.; sharp—, akuta a.;
—coil, agorda bobeno.

turn (of a coil), volvo (de bobeno).

Undamped wave, kontinua ondo.

Vacuum tube, vakua tubo. valve; valvo, tubo, lampo; 2-electrode-, diodo; 3-electrode-, triodo; 4-elec-trode-, tetraodo; bright emitter-, hela

v.; dull emitter—, malhela v. variable, varia, variigebla, algustigebla, variometer, variometro; vario-coupler, vario-kuplilo.

vary, to, varii velocity, rapideco.

vernier, verniera. w

Watt. vato; kilowatt. kilovato. wave, ondo; carrier—, portanta o.; con-tinuous waves, kontinuaj ondoj; damped, —s, amortizaj o.; electromagnetic —s, elektromagnetaj o.; Hertzian -s, Hertzai o.; undamped -s. kontinuai o.

wave frequency, ondfrekvenco. wavemeter, ondometro.

wire, fadeno, drato; bare—, nuda f.; flexible—, fleksebla f.; insulated —, izo-lita f.; solid —, solida f.; stranded —, dividita f. wiring (collection of wires), fadenaro; (method of wiring), fadenarango; (action),

fadenado. wireless, senfadena.

X's atmosferaĵoi.

Lessons in Esperanto

(Concluded from July, 1925, issue)

In concluding these lessons in Esperanto, I want to urge upon all who have auto, I want to urge upon all wno nave followed them (and from the correspondence I have received, I believe a satisfactory proportion of the Radio News readers are studying Esperanto) the highly important follow-up activity of a wide correspondence in Esperanto. is not a suggestion intended only for the idler who has no activity, who has little interest in anything serious in life, but it is meant more for the already active radio fan and others who wish to gain more valuable knowledge, and to extend their perspective in many ways. It is intended for the person who wishes to write pro-fessionally, for from all corners of the you can gather unusual features that your home paper or magazine will want, and you can, by the same correspondence, get

The latest developments in low-loss parts

Built of this special insulation made to order for radio



NOW you can get a complete line of low-loss parts made of Radion, the special insulation which our engineers created for radio purposes exclusively. These parts embody the very latest developments in radio; they are as efficient as the wellknown Radion Panels.

From the earliest days of radio, the experience of thousands of amateurs has proved that Radion Panels give the most satisfactory results. The complete line of Radion parts have the wonderful Radion finish smooth and high-polished. This finish eliminates those losses caused by moisture gathering on the surface of ordinary insulation, causing leakage paths. The high-resistant characteristics found only in Radion Panels also mark these new parts.

Radion Panels, made in Black and Mahoganite come cut in standard sizes for whatever set you wish to build. And, in addition, you can now get the new Radion Sockets, Radion Dials, Radion Loud Speaker Horn, Radion Tubing, Radion Binding Post Strips, Insulators, etc.



Radion Built-In Horn

IN any set you build, you may put in a Radion Horn, which takes up small space, gives clear rounded tones, and eliminates the bother of an unsightly awkward horn outside the set. Price \$3.00 including cap to fit most makes of headphones or loud speaker unit.

Radion Close-Tuning Dial No. 10 THE new No. 10 4-inch Radion Dial



This is Radion No. 2 Socket designed for both new and old tubes.

Send for Booklet OUR booklet, "Building Your Own Set," gives wiring diagrams, front and rear views, shows new set with slanting panel, sets with the Radion Built-in Horn, lists of parts and directions for building the most popular circuits. Send coupon with 10 cents today.

is built to conform to the fingers, helping you to get close tuning. May be used for single mounting condensers. We believe it is the most beautiful dial yet designed. Nine other styles of Radion Dials, in several sizes to meet your requirements.

New Radion Sockets for the new style tubes In line with our policy of keeping all Radion parts abreast of the very latest developments, we announce new Radion Sockets No. 4 and No. 5 for the new style tubes. Neither of these sockets has collars or side bosses. No. 4 is equipped with binding posts. No. 5 without,

> Universal Sockets for both new and old tubes

Radion Sockets No. 2 and No. 3 are designed to take the old or standard tubes, as well as the new tubes just on the market. No. 2 is equipped with binding post. No. 3 without.

All Radion Sockets are highly efficient, due to the principle of their construction and the low-loss characteristics of Radion. Ask your dealer to show them to you.

AMERICAN HARD RUBBER COMPANY Dept A10, 11 Mercer Street, New York City



-----AMERICAN HARD RUBBER COMPANY, Dept. A10, 11 Mercer St., New York City. Please send me your booklet, "Building Your Own Set," for which I enclose 10 cents in stamps.



Amplions chosen & reproduce Papal Ceremonies throughout Saint Peters, Rome

Of ALL loud speakers, Amplions enjoy the

honor and high compliment of having been installed throughout the famous Cathedral of Saint Peters, Rome, that important ceremonies conducted by His Holiness the Pope may be clearly audible to great multitudes of people. Supreme clarity of reproduction was the prime

requisite. It is only logical that The Amplion -creation of the actual originators and oldest makers of loud speakers-should have been chosen. Amplions outsell any other loud speaker throughout the world, chiefly because of unrivaled clarity of tone. "The clearness of the reproduction of the Pope's voice was an outstanding writes a witness to the first ceremonies.

Hear The Amplion in comparison with any or all other reproducers. Prove to your entire satisfaction that it is the world's finest loud speaker. Amplion Loud Speakers, \$12.00 up. Phonograph units in two sizes. Write for inter-esting literature and dealer's address. THE AMPLION CORPORATION OF AMERICA

Executive Offices: Suite W, 280 Madison Ave., New York City Canadian Distributors: Burndept of Canada, Ltd., Toronto Alfred Graham & Co., London, Eng., Patentees

The World's Standard Loud Speaker





Andrews . Jeresnadyne Radio Receiving Set

ANDREWS RADIO CO. Tribune Tower Chcagoi



TODAY for big 48 - page catalog of latest radio goods at Wholesale Live dealers and agents wanted DARD RADIO CO., 108 East 13th, Kansas City, Mc same of the most interesting

the photographs to illustrate those features. I speak on this point from per-sonal experience. It is intended also for the collector of stamps, or of souvening cards, or of any kind of curios, of folk lore and of people's customs of different lands. Whatever be your hobby or your main interest in other parts of the world and other peoples, you will find Esper-auto correspondence a marvelous tool, ready and easy, even delightful to use. Don't be afraid that your letter won't

be understood. Put the words on paper according to the simple rules you have learned here, and be sure it will be easily learned here, and be sure it will be easily understood, just so it is written legibly. One student of these lessons living at Hannibal, Mo., after six weeks' study, using additional reading text, has written me letters that any Esperantist, even students like himself, of any other nationality could instantly read and comprehend.

HOW TO GET CORRESPONDENTS

There are thousands of others, like yourself, in all countries who wish to cor-respond in Esperanto. You can get in touch with the kind you will like best to touch with the kind you will like but of correspond with, those who have similar hobbies to your own, by inserting a little ad in any one of the leading international Esperanto publications. Such an ad will cost about 25c and will bring you any where from ten to one hundred offers of correspondence. You are morally obligated to reply, at least by one postal card. telling those with whom you do not wish to carry on correspondence, that you can-not keep it up. But out of those who write, you will find the kind you will wish to become better acquainted with. Y can word your ad something like this:

2 East Court St., Pendelton, Oregon, U. S. A., deziras korespondadi kaj inter-anĝi PM, PI kaj L. pri radio-aferoj. PM is abbreviation for "Poštmarkoj", stamps, PI Poštkartoj ilustritaj, illustrat-ed poste-or souvenir cards, L., leteroj,

There are many excellent Esperanto publications of wide circulation in which an ad similar to the above could be inserted with excellent results, but the two leading ones of most general, world-wide ESPERANTO, 12 Boulevard du Thea-

tre, Geneva Switzerland. It is monthly beautifully printed in best Esperanto, and is the official organ of the Universala Esperanto Asocio, the world organizaon, \$2.00 per year.
HEROLDO DES ESPERANTO, Hor-

rem bei Koeln, Germany, semi-weekly newspaper, illustrated, excellent Esper-anto, \$1.00 three months, \$4.00 yearly. For Esperanto literature and up-to-date For Esperanto literature and up-to-date information about the Esperanto-radio movement of Europe, write British Esperanto Association, 17 Hart Street, London, W. C. 1., England.

It will be of interest to every student f these lessons and all Esperantists in North America who see this to write me giving at least names and addresses. Ad-dress Box 223, City Hall Station, New

The following reading exercise with which we close these lessons, is taken from an illustrated Esperanto technical article on Radio, sent out by the Inter-nacia Radio Asocio, 97 rue Royale, Versailles. France, as a feature of their service for Esperantists interesting them-selves in radio who have not in their native languages adequate technical in-formation on the subject. For the radio terms in this exercise, see the Esperanto-

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



RATHBUN STRAIGHT LINE FREQUENCY CONVERTER

THE modern radio receiver has abundant tone, volume and power—now it may have perfect, simplified control.

The Rathbun Straight Line Frequency Converter is adapted for use on your receiver—every



Stations indicated in kilocycles and wavelengths showing crowding with an ordinary capacity condenser.



Stations partially separated and tuning alightly improved with a Straight Line Wave Length Condenser.

distinct reading at a uniform distance from the next. Real logging becomes a fact. The stations are distributed with flawless precision over 360° – one complete revolution of the Dial. There is no limitation or crowding as on controls using only half a dial. Radio control is simplified.

The Rathbun Straight Line Frequency Converter provides straight line frequency tuning with ordinary capacity condensers. It is interchangeable with any condenser—on any receiver. It is sold with the guarantee of reliability and satisfaction attached to all Rathbun Radio Apparatus.

See and Try it—at Your Dealer's

If your dealer cannot supply you, send
Money Order (\$3.50 each) and your
order will be shipped promptly by

Rathbun Manufacturing Co., Inc.
Jamestown New York

Parcel Post prepaid.





Complete and equal separation o. station over the entire dial with the Rathbun Straigh



You'll never know how much difference a dial can make until you actually get your hands on the new Mar-Co. It splits a single degree into hair's breadth divisions. It responds to your slightest touch with no suggestion of backlash.

Smooth-precise-and strikingly handsome -built for your present set and for your next year's set as well-it is what you'd expect of Mar-Co-see it at your dealer's.

MARTIN COPELAND COMPANY Providence, R. I.

Nickel

Gold

he Radiophan Adapter A "2 in 1" Crystal Detector proves Reflex and Crystal Sets

Prices

For You



TUERK MFG. CO

Boys and Young Men-You can earn dandy prizes and liberal commissions by selling and delivering our popular magazines in your spare time. No experience or money is necessary. We furnish all supplies and tell you just how to start. Write to-day.

E. J. FOLEY, Department RN-10, Experimenter Publishing Company, 53 Park Place, New York City

vocabulary published in April News. The following vocabulary Radio News. The following vocabulary not yet used in these lessons.

WVOCABIILADY kunveno, convention, meeting,

ingeniero, engineer. firmo, firm, klarıgis, explained. principo, principle. interesa, interesting. longa, long. generale, generally,

uzi, to use (uzata, being used).

taugas, fit for, suitable, bedaurinde, regrettably. prezentas, presents. ĉefa, chief difektas, defects genante, troubling.

amtempe, at the same time. najbara, neighbor. aŭskultanto, listener.

delikata, delicate, ambaŭ, both, malhelpis, hindered. enmeto, putting in. malfacilaĵo, difficulty.

venkis, conquered. sola, single, lonely. efektivigis, brought about, realized. efika, efficacious.

facile, casily. cetere, moreover, besides. sendube, doubtless

siaflanke, for his part, PRAKTIKA AMPLIFO ALTREKVENCA

Dum la januara kunveno de la «Société des Amis de la T. S. F.» s-o Rouge, ingeniero de la firmo "G. M. R.", en Parizo, klarigis la principon de tre interesa ricevilo por amatoro). Por la mallongaj ondoj, nun ĝenerale uzataj en radiotelefonaj sendoj, altfrekvenca amplifo per rezist-ancaj amplifikatoroj ne tre taŭgas. Multe pli taŭgas rezonancaj amplifikatoroj, sed, bedaŭrinde, ili prezentas du ĉefain mal-bonaĵojn. Unue, kiam ili enhavas kelajn ŝtupojn, kontinuaj osciloj estiĝas en la cirkvitoj, kiam la sinsekvaj ŝtupoj estas agordo de ĉiuj ŝtupoj. S-o Rouge forigis ambaŭ tiujn malbonaĵojn. La estiĝon de ante samtempe najbarajn aŭskultantojn. Due, tre delikata estas la samtempa agorditaj laŭ sama ondolongo, kaj tio difektas la aŭdadon de radiotelefonio, ĝenkontinuaj osciloj en la cirkvitoj li malhelpis per enmeto de rezistanco en la oscilan cirkviton de ĉiu ŝtupo. La malfacilaĵon de samtempa alĝustigo de ĉiuj ŝtupoj li venkis, arangante la aparaton liel, ke per unu sola butono ĉiuj ŝtupoj estas sam-tempe alĝustigeblaj. Tiel li efektivigis aparton samtempe tre efikan kaj tre facile uzeblan de radio-amatoroi.

Amatoroj cetere povas provi mem tiun prnicipon, el kiu ili sendube ricevos tre


bonajn rezultatojn. Siaflanke, S-o Scott-Taggart provis tiun sistemon kaj favore rekomendis ĝin en "Modern Wireless" de oktobro 1924.

Where Does Your Set Get Its Power?

(Continued from page 451)

explain just how a vacuum tube acts as a trigger to add a lot of power to a very weak signal so that, in the end, it is audible to a large number of people sitting in a room.

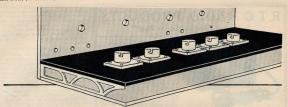Put in the simplest possible terms, the tube simply controls the flow of current from the "B" battery. This battery is in



You need Quality in the Base Panel

THE use of a base panel makes possible shorter, neater and more efficient wiring. But the panel must be an insulator of the first quality that will not deteriorate with time. It must be free from any tendency to absorb water to function properly in damp, humid weather. It must not warp or distort, disturbing the angle of the coils and the arrangement of the apparatus.

There is one panel material in which you are sure of getting all of those essential qualities—and that is Formica.

For years it has been accepted by the vast majority of leading radio manufacturers, as mechanically and electrically the best available material for radio panels. It also is the most handsome, and its finish is entirely permanent. It does not check, crack or lose its lustre with time.

Formica is evidence of quality, durability and genuine worth in any radio apparatus.

VERI-CHROLIE PANELS

By the purchase of a controlling interest in the Verl-Chrom aboesteries, the financial and production resources of the Formical instalation Company have been seed behind this remarkable new process for all the production of the production in cost of the production in cost barge. Write the configuration of the production in cost is large. Write for prices on complete panels finished in this way in quantity.

Dealers: Home set builders who want the best results want Formica. It has been for years a highly profitable line for thousands of dealers.

THE FORMICA INSULATION COMPANY

4618 Spring Grove Avenue, Cincinnati, Ohio

- 1 Formica is used by nearly all the leading set makers and has for years been used by more set makers than any other material.
- ? Formica is unaffected by weather and time it lasts forever.
- 3 Formica in appearance is the finest of all panel materials and always remains so.
- 4 Formica's electrical qualities of every kind far exceed any possible requirement.
- 6 Formica will not sag from heat or cold flow under pressure.
 It retains its dimensions. Everything you fasten to it stays tight and precisely where you put it.
 7 Formica panels are sold in neat craft paper envelopes which assure you that you are getting the genuine. 8 Formica is one of the most widely approved materials in radio.

SALES OFFICES

| 50 Church Street | New York, N. Y |
|------------------------|-----------------|
| 9 South Clinton Street | Chicago, II |
| 516 Caxton Bldg. | Cleveland, Ohi |
| 327 Cutler Bldg | Rochester, N. Y |
| 422 First Avenue | Pittsburg, Pi |
| 6 Beacon Street | Boston, Mas |
| 55 Calle Obispo | Habana, Cub |

| 026 Second | Avenue | Minneapolis, Minn. |
|-------------|-------------|---------------------|
| 25 Bulletin | Bldg. | Philadelphia, Pa. |
| 08 Title Bu | ilding | Baltimore, Md. |
| 85 Mission | Street | San Francisco, Cal. |
| 19 Ohio Bu | ilding | Toledo, Ohio |
| 109 Plymou | th Bldg | New Haven, Conn. |
| Whitney Ce | ntral Bldg. | New Orleans, La. |
| Whitney Ce | ntral Bidg. | New Orleans, La. |

5 Formica has high mechanical strength and will not break in use.





Hear the Formica Orchestra over WLW every Tues-day evening from 9 to 10 Central Standard Time.

RTC RADIO PRODUCTS

"Always First - Always Best"



RTC "B" Battery Eliminator

To obtain the best results from a raillo set a steady constant mappy of take voltage is necessary. The RIY Eliminates meets its necessary. The RIY Eliminates were set as the results of t

the size of the unit is less than B Batteries. Size 44x74x44 inches. Model RT-40 "B" Battery Eliminator

\$35.00



RTC "B" Battery Eliminator Kit

Model RT-40K "B" Battery Eliminator Kit

\$20.00



RCT Tube Re-Activator Are your tables mr. down and toporturely. Hat your out credit of your failure for the failure

Model RT-20 Tube Reactivator - - \$6.50 THE RADIO TELEVISION CO.

9410 St. Catherine Avenue

CLEVELAND, OHIO

Full information on request. Prices F.O.B. Factory. MONEY BACK IF NOT SATISFIED



Radio Tubes

\$1.50 Each ACME PRODUCTS CO., 903 Broad St. No Newark, N. J.

WADE SQUARE LAW CONDENSER AND DIAL

Frequency, 00005 mfd. . At your dealers, otherwise send purchase price and you will be supplied postpaid.

WADE NFG. Co., Inc., 1819-A Breadway, N. Y. City



HEATH RADIO & ELECTRIC MFG. CO., 206 First St., Newark, N. J. FAMOUS"BH"TRANSFORMERS

TABUUS DE I MANOUMERA DE I MANOUMERA DE MANO

Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 65c. Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, N. Y.

the same relation to the set that the powder is to the hunter's gun. The amplification of 3,000 or 4,000 times obtains its current from this battery. Without this source of supply, the set could do nothing. Referring to the hunter again-po matter how hard he might press the trigger, the gun would be worth-less unless there were powder in the cartridge.

A FEW "BRUTE FACTS"

How the grid controls this power of the "B" battery is a very interesting story. We shall explain it in the easiest possible manner. At some points we shall make several statements which Sir Oliver Lodge has so aptly classified as the "brute facts of aptly classified as the "brute facts of science," those things which are found by the physicist and mathematician to be true, but for which we have, at the same time, no thorough explanation. In other words, they are just facts which we know do exist, but do not know why. We shall label all these brute facts and the reader will simply have to take them for truths founded on proofs and theories which are too long and compliand theories which are too long and compi-cated to be completely detailed here. First, we shall say that a current is always flowing through the tube from the filament

to the plate so long as the filament is lighted and the "B" battery connected properly with its positive pole to the plate and the negative pole to the filament.

This current is important, but the most

important point is the fact that the little grid which is placed between the filament and the plate has complete control over it. The grid may stop the current entirely or allow all of it to pass. It may even cause more than the ordinary amount of current to take the path from the "B" battery through the tube -through the space between the plate and the filament-and then down the filament lead



The skeleton view of The skeleton view of the elements of a vac-uum tube shown here-with will give the reader a clearer idea of the relation be-tween the various parts.

As we said above, this is the all-important characteristic of the tube, this ability of the grid to control so easily the passage of the current of the high voltage battery.

How this is done is an interesting process It all depends upon the way the current passes through the tube. Ordinarily, we think of current as passing along a wire or some

other metal path. But, in the final analysis. the current passes through a tube just as it passes along the copper leads from the light company's mains in the street to the lamps

which light your home.

We will not go into great detail as to just how a current travels, but will simply say that whenever there is a movement of current in any direction, there is a flow of electrons accompanying it. That is, there is a real and measurable stream of these little particles of matter flowing in a definite direction and at a definite speed through the conductor or in the space through which the current is passing.

A word of explanation here as to just



combines volume with a velvet tone

SAAL Jr.
The same in every respect as the Saal Soft Speaker, except it

\$20



The Saal Soft Speaker Unit is example of the care with whice example of the care with whice tured. The disphragm is conceted to the armature by an which transmits the action of the care of the care

IN buying a radio reproducer you need no longer choose between volume and tone quality. You can now buy a speaker with both. The Saal Soft Speaker combines volume with a velvet tone. And tone quality is what counts after you have owned a set a while.

The Saal has no blare, no blast, no metallic ring. It is not a fad. It is a faithful reproducer of radio programs. It is properly constructed for the accurate reproduction of sound. It is not straightnecked like a trumpet. The neck is curved like a swophone, the most melodious of all instruments. From the reproducing unit to the edge of the bell is one unbroken taper—one even, unbroken enlargement of sound.

The reproducing unit of the Saal Soft Speaker is of all-metal construction, and cannot be harmed or "blasted" by the loudest receiver. It maintains its tone with any volume. There is no ad-

justment knob to complicate tuning. The Saal Soft Speaker is made to last a life-time. The neck is of aluminum, a procus and non-wibrant metal with no timyr ing. The bell is of genuine Bakelite, the most perfect and most resonant of all radio materials. There is no wood, no tin, no composition, It has nothing to warp-rack, wear out or deteriorate. It is guaranteed to give you satisfaction.

In appearance the Saal, with its large black bell, black crackle throat and graceful lines is the aristocrat of horns. Also funnished with a brown bell and gold or silver stippled throat at \$5 extra. Hear it at your dealer's today.

VOLUME WITH TONE QUALITY

Manufactured and guaranteed by H. G. SAAL COMPANY, 1800 Montrose Ave., Chicago, Ill.

Just like having Radio Batteries fresh every day!

I MAGINE the high quality in reception if your radio batteries were always brand new! Imagine having radio batteries that never need replacement!

The man who owns a Cooper A-n-B has just such radio power at his disposal. Using the same light socket as an electric lamp, it supplies, year in and year out, the exact current requirements of any radio circuit.

The Cooper A-n-B never wears out. Its usefulness is constant -its current precisely the same whenever you pull the switch of your set.

For a 5-tube receiver an entire evening's entertainment costs about five cents for current.

Having a Cooper A-n-B is just like having radio batteries fresh every day.

The COOPER CORPORATION CINCINNATI, OHIO Founded - 1004



The advantages of the Cooper A-n-B aretoo an advertisement We bave explained its benefits in an interesting booklet. May



Special Library of Information RADIO PATENTS

TRADE MARKS

JOHN B. BRADY

Ouray Building Cable address: RADIOPAT

Washington, D. C. Telephone: Main 4806



exactly what these little electrons are may not be amiss. Those who have studied the latest ideas in physics and chemistry will, of course, find this a repetition of what they already know, but those who are not so well acquainted with these sciences will need this explanation to understand the operation of the tube.

All matter is composed of electrons and protons. Just what the electrons are is hard to say. Some scientists think that they are simply small charges of electricity, while others think that they constitute the last indivisible foundation of matter carrying an electric charge. In either case, all we need to know is that the electron is negative electricity and that the proton is positive electricity and that the two of them compose the atoms of matter. Now, as in ordinary electrical work, unlike charges attract each other and like charges repel. That is, a positive and a negative particle of electricity will rush together with great haste and force while two positive or two negative particles will rush apart with just as great enthusiasm.

THEORY OF MATTER All matter is, of course, made up or atoms

which are, in the last analysis, nothing more nor less than an orderly array of electrons. According to the latest view the proton is at the center of the atom and the electron revolves around it in much the same fashion as the moon revolves around the earth.

How and why this is so is one of the brute facts of science spoken of above. It must be taken for what it is worth without further worry. It may be difficult at first for the reader to accustom himself to thinking of matter in this way, but time will give

him the proper conception.

Nevertheless, all matter is composed of these tiny particles, and thereby hangs the tale of the vacuum tube's operation. Now, in a metal like copper, all the atoms

are composed of the same number of elec-trons and protons. But, at the same time, between them there are a number of loose electrons not attached to any particular proton. Ordinarily, all the electrons have their particular nucleus of protons, or protons and electrons, around which they revolve and which they never leave, except under some extraordinary circumstance. The passage of electrical current through a wire may, of course, be considered an extraordinary happening, so far as the electrons are concerned and they are what we are concerned with

Now in copper-and this is another of the brute facts of science-there are some of the loose electrons spoken of above. Also, the passage of a current through copper may rob some of the nucleii of their electrons and make them (the electrons) travel along in some particular direction in the wire, depending upon which is the positive end of the wire, or rather to which end of the wire is attached the positive pole of the generator or source of current. In case the material substance has all its

electrons tied tightly to their nucleii, so to speak, so that a current may not move them, we have an insulator instead of a conductor. The passage of a current along any sub-stance depends on the flow of electrons alone. The nature of the conductor has nothing to do with the passage of the current, except as it contains electrons which may be easily dislodged and moved from place.

Now, with a clear idea as to the necessity for moving electrons for the carriage of current, it does not look so preposterous for a current to flow through a vacuum tube when we learn that there is a constant stream of electrons flowing through it.

How this necessary stream is created and kept up in the vacuum tube is another in-teresting point. It is accomplished very simply by heating the filament until it "boils

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



Plays No Favorites

Amplifies both Low and High Tones

YOU want more from your loud speaker than noise, distortion, howls and squeals. You want pure tones, clear and mellow, whether high, low or of medium pitch. You expect faithful reproduction.

Such reproduction is made possible by resistance coupling amplification. Lower initial and operating costs, simpler assembly, and superior results make this method of amplification most popular.

"ELECTRAD" 3-STEP RESISTANCE COUPLED AMPLIFIER KIT No. 1-C —A big \$6.75 value. Contains the necessary Resistor Couplers, Certified Mica Condensers, Condenser Mounting, Certified Grid Leaks and Resistors. Nothing else needed except sockets, rheostat and bus bar.

> Ask your dealer or write for FREE Resistance Coupled Amplification Folder

ELECTRAD, Inc.

428 Broadway New York City

Variohms, Audiohms, Lightning Arresters, Lead-Ins and many other "Electrad" radio products are on sale at your dealers. Sent direct if he can't supply.

"ELECTRAD" LAMP SOCKET AN-TENNA—Price 75c. Plugs in on any light socket. Reduces static and other interference. No outdoor aerial needed.

ELECTRAD



"The Six Point Pressure Condenser" THE "Electrad" Certified Fixed Mica Condenser is a revelation in accuracy and design. Ingenious, rigid binding and firm riveting fasters parts securely at Six different points insuring positive electrical contact. Impervious to temperature and climatic variations. Exerts even pressure upon the largest possible surface—can't work loose. Binding strap and soldering lug in one piece. Accuracy and quietness assured always. Value guaranteed to remain within 10% of calibration. Standard capacities, 3 types. Licersed under Pat. No. 1,181,623, May 2, 1916, and applications pending. Price 308 to 75 is neaded dust and moisture proof packages.



For use with UV-201-A, C-301-A, UV-199 and C-299 types of vacuum tubes. A promoter of good reception.

A tube and time saver for the set owner.

A money maker for the radio dealer and serv-

Pocket Meters

Panel Meters Potentiometers Battery Chargers Microcondensers

The Sterling Manufacturing Company Cleveland, Ohio 2831-53 Prospect Ave.,

National Airphone Corp. MANUFACTURERS OF Somerset-the Ultimate in Radio Frequency Receivers 18 Hudson Street - New York City



"Lighting Fixtures" READY TO HANG (Direct (Direct from Manufacturer)
upleteely wired including glassware
Send for new Catalogus No. 27
(Just reduced prices) Special Proposition to Dealers ERIE FIXTURE SUPPLY CO. Authorized Cockaday Coil PRECISION COIL CO., Inc. ists in the manufacture of all type off" the electrons. Here we come again to the construction of matter from electrons. When a metal is heated, the scientists have found that it throws off these electrons in much the same way as water throws off steam when it is heated. This "boiling" of electrons from an incandescent filament makes

the working of a vacuum tube possible.

As said above, all electrons have a negative electrical charge. And of course they will be attracted to anything which has a positive charge. And further, all those who have had anything to do with a radio set know that the plates of the vacuum tubes know that the plates of the vacuum tubes must be connected to the positive pole of the "B" battery. As a matter of fact, the "B" battery is used as much to put a positive charge on the plate as it is to furnish the current which is triggered off by the

Now we must make another explanation regarding the flow of electrons before we get too far away from the subject. Just above we told how the passage of current depended upon the free electrons in the wire or conductor for its path. Somewhat the same is the situation with the filament. Some elements have an ability to throw off electrons with greater ease than others. that reason they are selected for use as filaments. With the smaller type tubes, for instance the 199 and the 299 types, the filament is made of a special so-called thoriated This name comes from a certain compound of thorium which will throw off electrons at a very low temperature. With ordinary tungsten it is necessary to heat the wire to bright red.

THE GRID ACTION If we had only a filament and a plate in

a tube, the flow of current through it would be constant. That is, the positive plate would have an uninterrupted attraction for the electrons constantly being boiled off the filament and, there being nothing to stop them or change the number of them reaching the plate, the current would be almost constant through the tube. That is, it would vary little, if any, in quantity from second to second.

But here, for the uses of radio, we inter-pose a grid between the plate and the fila-ment to control the flow of electrons. It ment to control the flow of electrons. It was the grid which Dr. Lee DeForest invented which has made radio, as we know it today, possible, for it is through the use of this grid that we are enabled to control the flow of current from the "B" battery in accordance with the incoming signal which

we wish to receive. It is very necessary that we begin to think of the tube merely as a sort of valve which controls the flow of current from the "B' battery in accordance with the incoming sig-nal. The battery is the reservoir and the tube is the controlling outlet. The incoming signal acts as a workman turning the valve.

The explanation of how the grid is enabled to control all this power is simple in one way and quite complicated in another. The mathematical part of it is very com-plicated, and may be studied only by those who have a thorough foundation in the higher branches of that complicated science. Luckily, however, the mathematical reasons may be put in simple language that anyone may understand.

An examination of a vacuum tube will show that the grid is very close to the fila-ment—much closer than the plate. This placement of the grid must be taken into consideration in figuring out how it controls the flow of electrons. It is perfectly plain that the speed of the electron should increase as it approaches the plate. Maybe it is not so plain, but it is a brute fact of science, anyway, and will have to be taken for granted. It is easily seen, however, that as the electron approaches the plate, the

Ow! CH Quality at a New Low Price

The Perfected C-H Rheosta



had faith in these foremost engineers and millions of their radio parts in the orange and blue boxes have helped build receiv-

Consistently from the earliest days has the C-H trade mark been synonymous with proper design and unequalled precision. Radio builders everywhere justly

name Cutler-Hammer has held an enviable position in radio.

ing sets of quality.

Better Sets at Lower Cost These millions of sales have brought down

manufacturing costs and today this quality carries no premium. Demanding the C-H trade mark now not only insures satisfaction, but provides a saving. Dealers everywhere are ready to serve you. If yours has not yet stocked any C-H part you desire, send us his name and we will see that you are supplied.

THE CUTLER-HAMMER MFG. CO. Member Radio Section, Associated Manufacturers of

MILWAUKEE AND NEW YORK



CUTLER-HAMMER - Buy Your Radio Parts by Name

Vital Parts of Leading Radio Sets

Nowhere is the axiom "an article is no better than the parts it contains" more true than in the radio world. So it is not surprising that leading manufacturers of radio sets choose the accessories for their hockups only after gaining a full technical knowledge of their make-up. and the results they give

In full consideration of this, the choice of Benjamin Radio Products, above all others, by the manufacturers of many of the finest modern radio sets, bespeaks eloquently of their as practical radio parts made by one of the oldest manufacturers of electrical goods

Each has been made a super radio part—to secure for the owner of the set the purest, loudest and clearest radio signals possible. Used together, their total efficiency spells the acme of selectivity, tuning range, the climination of disturbance and distortion, and the reduction of radio losses. And, the logical total of these many worthy features is "Better Radio. 120-128 S. Sangar St., Chicaro





241 W. 17th Street New York

448 Bryant Street San Francisco

Low Resistance - Low Distributed Capacity Wires are space wound, adjacent coils are parallel, air insulated and so separated that while caracity is reduced to a minimum, inductance is maintained at a high noint of efficiency.

Tuned Radio Frequency Transformers Greater Tuning Range - Greater Selectivity

These coils are very uniform, both in inducance and distributed especity, so that if desired they may be guared for single counted of the three tunes to days. A minimum amount of material is used in the field of the coil, and an anti-copacity connent is used only where the wirse cross. Coils are coupled so as to reduce expective coupling to a minimum. Green double slik covering provides high insulation and

Benjamin Cle-Ra-Tone Sockets

enjamin Cle-Ra-Tone Sockets prevent the transnission of outside vibrations into microphonic dis mission of outside vibrations into microphonic dis-turbances. Four delicately adjusted double springs support the socket—"float" it above the base—and absorb all jars and shocks. An absolute necessity in portable sets. Used by leading manufacturers and recommeded by radio engineers in their most popular hookups. There are no rubb parts to deteriorate. Bakelite is used wherever possible to insure sturdiness, long life and high insulation. Handy lugs make soldering easy. Stiff bus

Benjamin Low-Loss, Long-Range Condensers

Straight line type. Definite and positive control of Straight time type. Definite and positive control of minute changes in condensor capacity. Spreads the broadcast range on the higher frequencies, and eliminates bunching of stations on the lower side of the dal. Add sheep using side increase selectivity. Mar-non insulance is used and leakage must go through long paths conside of morgan field. Ungelabed silver plan freak.



DRING STERRINEN

TUBES REPAIRED OR EXCHANGED

when the body to the recommendation of authority of a sulfield relies coenters. Don't the authority of a sulfield relies coenters, but the authority of the sulfield relies and the sulfield relies an

SAVE YOUR TUBES

Don't throw away "dead" radio tubes You can rejuvenate them quickly at home and without expense by a very simple process. Send 10 cents in coin and a self addressed stamped envelope for full and complete directions. LEO E. BUSS RADIO SERVICE



UILDING A SET?

KLOSNER RHEOSTATS KLOSNER RADIO CORPORATION 1024 East 178th St. Rheastat Specialists, N

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

power of the plate over it will become greater and greater on account of the nearcrease in speed of the electron as it comes closer to the plate is called its acceleration consider the closeness of the grid to the filament and the comparatively large distance to the plate. That is, the distance is extremely large compared to the size of the electron. (The writer has tried to keep away from any reference to the size of the electron because it is so small that there is no clear example which can be given in explanation of it. Just let us say that it is so small that several billions of them would be required to stretch across the finest needle point ever made.) Mathematically, these mites travel very

slowly at first, gradually attaining speed. Of course, their power is directly proportional to their speed. This point may be illustrated by reference again to the gun. The power by reference again to the gun. The power of the bullet to penetrate an object is cal-culated by multiplying the weight of the bullet by the speed at which it is traveling. The same is the case with every moving thing. This is one of the first laws of mechanics. We shall state it again: The power or energy of any object is

equal to the weight of the object multiplied by half the velocity at which it is traveling. This law is stated in order that the reader may get a clearer idea of how the grid This is done because we commented in the first few paragraphs on how extrememinute the incoming signal really ly minute the incoming signal really is. The reader might become confused as to how this minute current can control the great attractive power of the plate for the

We have seen what gives the electrons their force. This force is controlled by the amount of positive charge on the plate of ment and the plate. We have also seen that the power of the electron increases as it approaches the plate, and we have seen how the grid is placed as close to the filament as is consistent with mechanical problems involved in the manufacture of the elements and the electrical properties of the tube.

When the electron is first boiled off the


filament, it has little preference as to which way it will go. That is the case when there is no charge on the plate. If a battery is connected to the plate so that there is a positive charge to attract the electrons, they will, of course, lay their path toward it, immediately they are free of the filament. Now the manufacturers of tubes specify certain voltages for the plates of their tubes.

This is done so that the pull of the plate just throws the slightest attraction for the electrons, so that it is just sufficient-meas-ured at the surface of the filament-to start the electrons toward the plate. By measured at the filament we mean, of course, that the attraction of the positive plate for the negative electrons at the outside of the filament wire is just enough to start them in the general direction of the plate. We must constantly keep in mind that the power of the plate to attract the electrons is, as the mathematicians say, a function of the dis-tance. Simply stated, this means that the further away from the plate we go, the less the attraction becomes.

When the electron is first released it starts toward the plate very slowly. For some time it travels with very little power, gradually picking up speed and power as it comes closer and closer to the plate. The grid is so placed that it intersects the path of the electrons before they gain any appreciable change in the grid to effect a mighty change in the current at the plate.

The grid, of course, controls the electrons in the same way that the plate does. The

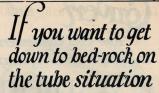A type for every need or preference: S 01-A S-99 Large Base S-99 Small Base



HIS tube or that tube—a cheap, questionable product that quickly wears down "B" batteries and gives little that is worth while in return or a downright quality product that brings out the best in your set—its an important question many fans are asking themselves today.

If you want to quit speculating with radio tubes—if you want to get down to bed-rock and get all out of your set that its possible for a tube to get—then install Sylvanias. Immediately you will notice a big difference in performance: better tone, greater sensitivity, more volume, longer life.

There is no compromise in Sylvania performance because there is no compromise in Sylvania manufacture. There is one standard only—the best it is humanly possible to produce. Yet the price is no more than you will pay for any other tube.

A Note to Dealers

§ Sylvania tubes are made by a close-knit organization that knows, from long years of experience, the intimate relationship of quality to profits. You should, by all means, get full particulars about the dealer franchise now. You are invited to investigate the Company's responsibility through any of the commercial agencies. Write or



Sylvania Products Company

Emporium, Pa.



No more crowding of stations at low-wave lengths. The SLF VERNIER DIAL separates stations at low wave-lengths just as easily as at high wave-lengths.

The strong, positive and ingenious mechanism contained in the knob gives small increases in capacity at low wave-lengths and progressively greater increases at higher wave lengths while knob and pointer revolve at uniform speeds.

A standard 12-to-1 VERNIER DIAL giving SLF characteristics to any ordinary condenser. Hairline pois Write for prices

JOBBERS AND DEALERS: Deliveries September 10th. Orders filled in rotation as received. Catalog copy and cuts ready August 15th WALBERT MANUFACTURING COMPANY 933 Wrightwood Avenue, Chicago, U. S. A.

C

Heavy gears

Allabakelite

The JEWEL Lightning Arrester

has been approved by the underwriters for indoor and outdoor installations (No. E-5403) as complying with their radio code.

dio code.

"Each lead-in wire shall be proxited with an approved protective device properly connected and located (uside an approved and located (uside practicable to the point where the wine cuter the building. The protective when the process of the process of

Install an approved Jewell Lightning Arrester and avoid possibility of having your entire insurance policy questioned. Buy from Dealer

Price, \$1.10

504

Jewell Electrical Instrument Co.

1650 Walnut St., Chicago

small incoming signals place a small posi-tive or negative voltage of the grid in ac-cordance with the transmitted voice or music. This voltage is infinitely small, as we said in the beginning, but on account of the posi-tion of grid in connection with the filament and plate these minute voltages are able to deflect or help the electrons in their path

The working of the grid is just the same as that of the plate. A positive charge on the grid will help the electron stream along by overcoming the resistance offered to it within the tube and the filament. When the grid turns negative on account of a negative signal, it at once repels the electrons and acts as an effective bar to their passage, thus shutting off the flow and therewith the

current. Now we understand that the grid, by becoming alternately positive and negative as the incoming signal becomes alternately positive and negative, controls the flow of cur-rent from the "B" battery because it is much closer to the filament than the plate and because there is a balance between the voltage on the plate and the construction of the tube.

We shall explain the reason for the vacmum. Everyone knows that there is a nearvacuum in the electric lights we use in our homes. Were it not for this exhaustion of the air in the bulb, the filament would be burned up as soon as it was lighted. This is also one reason for the vacuum in the vacuum tube—to keep the filament from burning up.

The second and most important reason is that the molecules of the air, if left in the tube, would impede the progress of the electrons in their flow from the filament to the plate. The so-called "hard" tubes are the plate. those which have a high degree of exhaustion, that is, the very last vestige of air pos-sible has been taken from them so that there will be the least interference possible offered to the electrons.

The degree of vacuum in a tube is ver much higher than in the ordinary electric lamp. In fact, the exhaustion of the air and other gases from such tubes is one of the stiffest problems now confronting manu-facturers. They have developed all sorts of special pumps and other apparatus for this purpose, and there are no end of patents on them. The company which controls the best pumping apparatus will be in a position to put out the best tubes, all other things being

equal. Last month we explained the "characteristic curve" of a vacuum tube. In order to tie that explanation up with this one, it will only be necessary to say that the character-istic curve is nothing more nor less than the Bertillon measurement of the particular tube simply the engineer's method of telling on paper what the tube will do. From the char-acteristic we can obtain the proper plate voltage to use on it, the amplification factor -or the calibre of the tube-and many other interesting and extremely important concerning what the tube will do when it is hooked up to a radio set.

Radio Wrinkles (Continued from page 455)

varying the intensity of the output of the The apparatus here described may be applied to any set, as it is placed across the phone terminals or connected to a plug

the phone terminals or connected to a plug that is inserted in the phone jack.

The apparatus needed for this control can be found in nearly every junk box. There are needed a resistance, which may be varied from 500 to 1500 ohms, two single-circuit jacks, and a mounting panel or small box. The parts are connected as

Unconditionally Guaranteed RSON HORDA

AMPLIFYING TRANSFORMERS

Standard on the majority of quality sets

EDY

Writes:

"We are cranks on audio-frequency transformers and our engineers are constantly running comparative tests on them. The

fact that we continue to use Thordarson's exclusively, in ever increasing numbers, simply means that we believe that it is the best available at this time."

Thordarsons are Absolutely Uniform! They always "match up perfectly

One reason that leading builders of fine sets use more Thordarsons than all competitive transformers combined is because Thordarsons run absolutely alike, absolutely uniform: always "match up" perfectly.

Daily we hear from fans who paid high prices for musically named, fancy-looking transformers only to discover that their old stand-bys-Thordarsons-were the real musical instru-

ments. For the benefit of others we therefore repeat "when better transformers can be bought they will be Thordarsons.'

Few, if any, transformers actually cost as much to make as Thordarsons. Why, then, pay more? Follow the lead of the leaders build or replace with Thordarsons. Any store can supply you. If dealer is sold out, order from us.

Thordarson Types and Prices



Thordarson Super Audio Frequency Transformers, sub-panel or top mounting types: 2:1, \$5; 31/2-1, \$4; 6:1, \$4.50.

Thordarson Power Amplifying Transformers give best results when preceded by two stages using 3½-1 Thordar-son A. F. Transformers, Pair



The Thordarson INTERSTAGE



Power Amplifying Transformer,
Provides two stages of POWER
amplification when inserted in
circuit between Input and Output Power Amplifying transtransformer and output the quality of the reception
more than repay of the provided of the
Thordarson builds a transformer
of this type. Each \$8.

Thordarson AUTOFORMER

the All Frequency Amplifier, amplifies clearly the lowest notes of any instrument as perfectly as the lighest notes. Autoformer the lighest notes. Autoformer mimpedances, resistances and capacities—developed and perfected by Thordarson. Write for the Autoformer Hookup Bulletin, Autoformer are \$5.00 each.



Write for latest Thordarson bulletins on amplification, Thordarson Dealers Everywhere.

THORDARSON ELECTRIC MANUFACTURING CO.
Transformer specialists since 1895
WORLD'S OLDEST AND LARGEST EXCLUSIVE TRANSFORMER MAKERS
Chicago, U.S.A.

KENNEDY RADIODYNE Thermiodyne GLØBE Deresnadyne ADLER-ROYAL MURDOCK MU-RAD r-Marshall



Newport

SUR-PANEL MOUNTING THORDARSONS ON SALE

They permit a neater assembly, the shorten-ing of leads and the concealing of wiring— as in factory built sets. Same ratios—same prices—as standard type Thordarsons. If dealer cannot supply, order from us.

Super-Het Builders

For the "Best" 45,000 Cycle Super-Heterodyne "Radio" and other leading authorities recommend in highest terms the Thordarson 2:1 Ratio Transformers. Take no others.

SUCCESSFUL RADIO ADVERTISING

HE difference which makes your radio product better than another is technical. Yet an advertisement which confines itself to statement of the technicality cannot yield sales. Nor can an advertisement which ignores the technical difference.

The radio advertising which we prepare is successful for two reasons:

We know Radio, and therefore understand our clients' radio products.

We know Advertising, and consequently are able to interpret into impressionable language, the technical individualities of the radio products about which we write.

If you are interested in finding out how much more effective your advertising can be made when it is prepared by an advertising agency which is able to appreciate your product technically, we invite your correspondence.

This advertisement is directed to reputable, established manufacturers

KIRTLAND-ENGEL COMPANY ADVERTISING

646 North Michigan Boulevard, Chicago

Standard Adjustable AERIAL BASES



Pat. Pend.

Ask your dealer to install your aerial with these new Standard Aerial Bases. Get the best and the cheapest at the same time. STANDARD AERIAL BASE CO. 227 W. 240 St. POMONA. CALIF.

Price \$2.00

shown in the sketch. Such a control as this may be used as a remote control for the volume, as a long lead may be run to the control panel, which may be close to



By the use of two plugs and jacks and a variable resistance connected, as shown above, in the output of a radio receiver, the volume of the signals received may be varied to any intensity desired by varying the amount of resistance.

the loud speaker. In this way it will not be necessary to make several trips between the receiver and the loud speaker to adjust the volume by means of rheostats.

Extending the Broadcast Range

198 meters, we may be able to go only to, say, 220 meters, or even 240 meters. How low we shall be able to tune depends upon how closely the antenna is coupled to the secondary, and also upon the other capacities existing in the circuit, and whether or not the inductance of the coil changes with the

This is illustrated graphically in Fig. 1. The vertical back column on the left indicates the range of wave-length obtainable without connecting the antenna and ground without connecting the antenna and ground connected, the wave-length range is low-ered to 507 to 198 meters. When the antenna and ground in the second of the wave-length range is low-ered to 507 to 198 meters. This makes it impossible to reach the longer wave-lengths, although we can reach the shorter ones. This is indicated by the middle block column

When we add a sufficient number of turns to the secondary coil to make up for this loss of inductance, the wave-length is raised to 550 to 240 meters. We are now able to tune to the upper wave-lengths as before, but are not now able to tune to the lower ones.

The reason for this is that the coupling of the antenna circuit to the secondary lowers the upper limit more than it lowers the lower limit, whereas the addition of the lower limit, whereas the addition of the extra turns of wire changes both limits to hearly the same extent. This is indicated by the right-hand vertical column in Fig. 1. NNDUCTANCE VS. PREOUNENCY CHANGE

When a coil has considerable capacity, as is the case with multi-layer coils, the inductance changes as the frequency for wavelength) changes. See Fig. 2. Over the longer wave-lengths, say from 600 to 300 meters, the inductance does not change appreciably, but it is likely to increase very ratio of the control of the co

Now let us consider what difficulties we shall meet when we try to get down to 150 smeters. The total range of 600 to 150 meters represents a wave-length ratio of 600/150 or 4 to 1. As has been explained above, this would require a capacity ratio of 16 to 1. In the old case, where we covered a range of 600 to 200 meters, there would have been no difficulty in covering the range, although there are many sets on the market which



No storage-battery radio is complete without a RECTIGON!

Westinghouse Rectigon Battery Charger

WESTINGHOUSE ELECTRIC & MFG. COMPANY South Bend, Indiana







cannot cover it. The secret of the problem lies in employing loose coupling between the primary and secondary, and in using coils with low distributed capacity. The two cases are compared in the table below.

 Wave-Length Range
 Wave-Length
 Capacity Ratio

 Desired
 Ratio
 Required

 600-200
 3:1
 9:1

 600-150
 4:1
 16:1

 On account of the high capacity ratio re

quired to cover the 600-130 range, it will hardly be possible to cover the range with the J005 microfarad condenser which was the formal to the first part of the first pale. This condenser has a maximum of 500 and we cannot count on a minabout 25 micromicrofarada, because of the subtional part of the first pale of the first pale is not well to use the condenser at the very low dall settings, as it is very medicant at the condense of the first pale of the first pale increases to very high values at the low dial settings.

The capacity ratio was, therefore, 500,75 or 20 to 1. It is very interesting to note that although we require a capacity ratio of 9 to 1 to over the 600-200 meter range, and although we have condensers having not been able to cover the range completely. It is quite a mystery to the writer why this has been so difficult. He has constructed many radio receivers, and has not had any castillar range in covering the continued continued to the contraction of the continued of the cont

But to take care of the range of 600-150 meters we should have to keep things in the same proportion. So, if we could cover the range 60-200 with a 20-to-1 condenser, requiring only a 9-to-1 ratio, then to cover a range 600-150, requiring a capacity ratio of 16 to 1, which is about twice the 9-to-1 ratio of about twice 20 to 1, to 60 feet. This high capacity ratio is not obtainable in the small-sized condensers. A 0,001 in the small-sized condensers. A

microfarad condenser may fill the bill, however, for this can be counted on to have a capacity ratio of at least 40 to 1. Thus, a condenser having a maximum of 1000 micromicrofarads and a minimum of 25, will have a capacity ratio of 1000/25 or 40 to 1. There will be difficulties involved here.

There will be difficulties involved here, bowever, which will make it necessary to go to other means of extending the range. The main difficulty lies in the great cought of the state of t

We come to the end of our journey, therefore, with the tentative conclusion that the only way in which the difficulty can be tapped colls in the tuned circuits. A very good example of this will be found in the three-range receiver described in the July entirely necessary to use three ranges. Two entirely necessary to use three ranges. Two ranges will be satisfactory for most purranges will be satisfactory for most purranges will be satisfactory for most purture to the control of the control of the the stations as much as practicable is, of course, the climination of crowding.

Much ingenuity will have to be exercised in keeping down the number of switches and controls. But difficulties such as this will be overcome, for there is scarcely anything for which a suitable switch cannot be designed.

Book Review

MANUAL OF RADIO TELEGRAPHY AND TELEPHONY FOR THE USE OF NAVAL RADIOMEN. By Commander S. S. Robison, revised by Commander S. C. Hooper, both of the U. S.

Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 65c. Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, N. Y.



Rola

Re*Creation — the triumph of genius

Re*CREATION could not come in a day. Nor in a year. Mere mechanical skill could not produce it. Just as no wonderful painting can be turned out by any machine. For re*creation is something intangible—subtle.

Mechanics and acoustics enter in, but artistic genius, itself, must guide the creation of an instrument capable of re*creating the tonal arts of the world. That instrument must be in intimate sympathy with every expression of music and voice.

Rola is the one Re*creator. And once you hear it, you too will say: 'Here is a truly marvelous thing. Now I can get all I have longed for from the miracle of radio.' The Rola Company, 4250 Hollis Street, Oatand, California. Marketed nationally through Baker-Smith, Inc. Head offices, Call Building, San Francisco. Branch offices in principal cities.

A Set Is As Good As Its Dials



trol is accurate to a hair's breadth. There is positively no backlash or lost motion.

PRICE \$350



The New Fynur tuning dial operates on beveled wheels instead of gears, so that forward or backward there is not the slightest break or in-

O BACKLASH is possible in the new Fynur Vernier Control. There are no gears to mesh, so there can be no lost motion, and the movement is always smooth and

If you want the utmost accuracy in reception, and unless you have it you cannot expect the best results from your set, use Fynur dials. They'll give you perfect selectivity and a greater and more lasting satisfaction than any other dial on the market. Simple in construction (can be mounted without dissembling), beautiful in appearance, (black or mahoganite Bakelite). If your dealer cannot supply you, write us.

Your set can be no better than its dials, so have the best set by having the best dials.

AUGUST GOERTZ & CO., Inc. 270-286 Morris Ave., Newark, N. J.

SET MANUFACTURERS will find that Fynur dials will improve the appearance as well as the efficiency of their products. In-

FYNUR VERNIER CONTROL

BRANSTON RADIO

Hetorus-the Final Achievement! A new and improved type of tuned R. F

transformer with isolated field coils. IT DOES THREE THINGS:

Increases selectivity for precise tuning.
Improves tone and volume of distant stations.
Reduces static and interference to a minimum.



Because: The Hetorus Coil has no pickup quality of its own and amplifies only the signals to Being "fieldless" there can be no interaction either between the coils themselves or adjacent apparatus. They can therefore be mounted in any position or angle:

tuned R. F. Receiver using Hetorus Coils. It is giving phenomenal results equal or superior to any 5-tube receiver on the

Whether you give your present set the advantage of this latest forward step in radio or build a new receiver, Hetorus Coils will afford you results in keeping with the best radio developments of 1926. Write at once for free information on this outstanding sens

Chas. A. Branston, Inc. 817 Main St., Buffalo, N. Y.

Prices For You

Boys and Young Men-You can earn dandy prizes and liberal commissions by selling and delivering our popular magazines in your spare time. No experience or money is necessary. We furnish all supplies and tell you just how to start. Write to-day,

E. J. FOLEY, Department RN-10, Experimenter Publishing Company, 53 Park Place, New York City

Navy. Buckram cover, 7 x 10 inches, 895 pages, illustrated. The sixth revised edi-tion, published by the United States Naval Institute, Annapolis, Md., is dated 1924. Institute, Annapolis, Md., is dated 1924.
Although this book is not generally well known, and the state of th

THE RADIO GUNNER. Stiff paper cover, 5 x 71/2 inches, 318 pages, illustrated Published by Houghton Mifflin Co., 2 Park

Street, Boston, Mass. Price \$2.00.

Published by Houghton Miffin Co., 2 Parts. Street, Boston, Mass. Price S. 2001.

For any or and the future, the result of the street, in the state for the street, in the state for the street, in the state for the street, in the street, in

meaning the state of the first of the first

RADIO YEAR BOOK. Second Edition.

RADIO YEAR BOOK. Second Edition, 1925. Over 1000 pages, cloth-covered cardboard covers: Price 30 Iranes, 17 General to the publication, 140 Trans. If ordered before publication, 40 rus de Seine, Paris, France.

The Reals Year, Book, which is published in Paris, France.
The Reals Year, Book, which is published. The second edition, 1923, will deves of all the trens associated and selling radio apparatus in every country of the world, the second of the published trens associated and selling radio apparatus in every country of the world, the second of the published trens associated and selling radio apparatus in every country of the world, the second of the published trens associated and an experiment of the second of the published trens associated and the second of the published trends and the second of th

RADIO MANUEL. By Orrin E. Dunlap, Jr., Radio Editor of the New York Times. Hard cloth cover, 5/4x74 inches, 267 pages. Diagrams and illustrations. Pub-lished by Houghton & Mifflin Co., 2 Park

lished by Houghton & Mifflin Co., 2 Park Street, Boston, Mass. Price S2.00.
There are always arising certain little circum-tree to be a second of the control of the control of the two large question marks, one following the query Why? and the other "Where can I find it in questions. Of corres, we do not any that every-thing pertaining to radio is treated in the munual, and the control of the Mr. Denlap first bits some of the high spots in the history of radio's development and then in

The Newest and Best Thing In Radio Utmost Simplicity!



NO DIAL

Brings them in

5 Tube Receiver Using Storage or Dry Batteries

Years ahead of other radio receivers by its patented design but already hailed by scores of happy users as the ideal radio set for every home—this great achievement of design and work-manship is now available to you! Think of a receiver without dials-so simple that any child can operate it; fool-prooftrouble-proof: That's NO-DIAL, the newest thing in radio:

Features You Have Waited for

Greatest Simplicity without sacrifice of other desirable features has been attained by NO-DIAL engineers through the most careful correlation of all parts. Adjustments which the listener, himself, in ordinary sets must make are in NO-DIAL completed at the factory.

Better Tuning is made possible because the condensers are permanently kept in step. The cover of NO-DIAL is rotated, bringing in station after station loud and clear, far and near. That is all the listener need do - even filament control is automatic.

No Log Book Necessary! The entire edge of the cover is a Station Register, on whose ample surface dozens of call letters, wave length and station names can be written in either ink or pencil, without crowding. Stations always come in at the same places where you locate and mark them.

Sensitivity of NO-DIAL is equal to that of highest priced receiver. In many tests it has received stations from coast-to-coast with loud speaker volume and fine tonal quality. Tube for tube, it recognizes no superior.

We Stand for Conservative Statements in Radio Advertising

Tone Quality - powerful yet silky - smooth throughout the entire musical scale-is due to the superior design and workmanship of NO-DIAL'S audio frequency transformers. High and low notes of voice and any musical instrument are reproduced with life-like fidelity. NO-DIAL does not re-radiate.

Cabinets of NO-DIAL Receivers are of spun aluminum, finished in mahogany brown crystalline, matching the most beautiful loud speakers and harmonizing with distinctive furniture in any home. Since NO-DIAL has no dials it needs no panel; consequently it is compact and damage-

Circuit of the five-tube NO-DIAL is the latest and newest radio hook-up, a most remarkably efficient combination of tuned radio frequency and resistance coupling.

> USE THE COUPON IF YOUR DEALER CANNOT SHOW YOU NO DIAL OF FOR FURTHER DETAILS

OUR GUARANTEE

We guarantee NO-DIAL Receivers against defects in workmanship or material, and will promptly replace any receiver which in our judgment is defective, or

refund the purchase price

No-Dial is licensed under Blackmore patents and patents pending Hogan patent No. 1,014,002. The OHIO STAMPING & ENGINEERING COMPANY

DAYTON, OHIO, U. S. A.

A Radio Cabinet of Beauty and Elegance Direct to You at Lowest Cost

Lid splined both ends to prevent warping. Nickeled piano hinge. Nickeled lid support of artistic design. Anti-vibration cushion feet (not visible in cut).

Edges of lid moulded to match bottom.

Shipped securely packed in strong carton.

Prompt shipment.

Hardwood Solid Rubbed Black Mahogany American Fields Walnut

CASH WITH ORDER or C.O.D. if % of price is sent with order. Prices F. O. B. Hickory, N. C. Order express

FREE WITH EACH CABINET a glued-up stock non - warping 1/2-

Free Catalogue.

Ivey Loud-Speaker In Cabinet Form At a Reasonable Price

We have at last perfected a Reproducer that
should mean something to you. SOLID BLACK,
we honestly believe has an superior as to EFF. WALNUT CARRET highly finished. The
CIENCY, PRICE AND BEAUTY. We make
that the product of the prod most powerful telephone unit ready to attach to your set. F. O. B. Hickory, N. C. SEND FOR FREE CATALOGUE

THE SOUTHERN TOY CO., Dept. N. Hickory, North Carolina

What Is the Radio Dealer to Do?

THAT is a question thousands of radio dealers,—real business men, all over the country are asking themselves to-day. They are wondering, and they have a right to wonder, if the radio business is a fair one-whether it is safe-whether it is honest. to wooder, if the radio business is a fair one-whether it is ande-whether it is homes. The fine denie work brast all I fail and Whether -makes some more one york to find, in a market at prices much less than his com. Not only done he lose on his inventory, the result of the process of the second with the result of the process dealer more, his best part on the result of the market dealer more, his best part of the process dealer more, his best part as a certain price may now be bought at half off or more. Ladway Heyment & Company has always fifst the dealers transhes very knowly because our Company self only to dealers, and radio is a man line with us,—not because our Company self only to dealers, and radio is a man line with us,—not were the contraction of the co

a side line. We use the dealers, for their own safety and profit, to watch the lines they carry. We usuge the dealers, for their own safety and profit, and the lines we determine the lines we carry. Ladvey from the Company carries only lines that are quick moving. Hash have Ladvey from the Company carries only lines that are quick moving, that have ladvey from the company carries only lines that we will not knowledge and the company carries and the company carry a line or recommend by them or which he will lose meny because of factory damping, price of which he will lose meny because of factory damping, price of which he will lose meny because of factory damping, price of the company that on which he will lose meny because of factory damping, price of the company that on which he will be seen the company that t It is to the advantage of every dealer to tie up with Hommel. Our illustrated catalogue 366 S is free. Ask for it.

Boys and Young Men-You can earn dandy prizes and liberal commissions by selling and delivering our popular magazines in your spare time. No experience or money is necessary. We furnish all supplies and tell you just how to start. Write to-day.

E. J. FOLEY, Department RN-10, EXPERIMENTER PUBLISHING COMPANY 53 PARK PLACE NEW YORK CITY a cleer and mon-technical style exclaim the theory of claer waves and have recognition. Even the tions of the functions of different pieces of appa-ratus used in the reception of broadcast signals are done in a similar interesting manner. There there is no similar interesting manner. There there is no similar interesting manner. There are done in a similar interesting manner. There are no similar to the control of the control of the transmission and chapters on radio beacons and how time signals and weather reports are broad-cast. A dictionary of radio terms concludes the

cast. A dictionary to result of the book.

Mr. Dunlay's experience in radio has made him capable of answering beforehand many unaked questions. The phases of radio reception asked questions, and the book of the most arise many times daily and, as a deference, we can recommend this radio manual.

40 Non-Technical Radio Articles

ry month for the beginner, the layman those who like radio from the non-mical side.

SCIENCE & INVENTION, which can be bought at any newsstand, contains the largest and most interesting section of radio articles of any non-radio magazine in existence.

in existence.

Plenty of "How To Make It" radio articles and plenty of simplified hook-ups for the layman and experimenter. The radio section of SCIENCE & INVENTION is as good that many RADIO NEWS readers buy it solely for this feature.

Interesting Radio Articles to Appear in the October Issue of

"Science and Invention" Hints to the Radio Builder, Part II. By Leon L. Adelman, Assoc. I. R. E. Superpower—Is It Here To Stay?

By Jack Milligram.

Converting Tuner to Short Waves. By Herbert E. Hayden. The Radio Constructor—How to Build a Low-Powered C. W. and Phone Transmitter.

By A. P. Peck, Assoc. I. R. E. Radio Hazards-How They May Be Avoided.
Radio As An Aid To Humanity.

DRY BATTERY RADIO ON AIRPLANE

The following was recently printed in the New York "Times": Radio history was written at the Great Lakes station today when a message was Lakes station today when a message was flashed from apparatus on a navy airplane to Prof. C. M. Jansky in the department of electrical engineering at the University of Minnesota, who replied to it.

Officers in charge of the experiments

said its success marked a new radio triumph, in that it is the first time such a message has been sent on a machine which works without a generator and simply on dry batteries.

They pointed out that this is extremely important to the army and navy, since with the old form of machine messages might be sent only while the plane was in the air and while its propeller furnished the power for a

while its properier turnished the power for a generator, while now an operator may send messages when the plane is on the ground. Immediately after the test Licut. Com-mander E. F. McDonald, Jr., who had a hand in perfecting and building the new instrument, announced that he will take such an outfit with him when he goes in June on the polar expedition into the Arctic regions with Daniel MacMillan.

The following letter was printed subsequently in the "Times":

To the Editor of The New York Times: The writer notes with interest the article in this morning's *Times* entitled "Dry Bat-tery Radio Works on Airplane." The statement is made that this is a new radio triumph in that it is the first time that such a message has been sent on a machine which

works without a generator and simply on dry batteries. Permit the writer to state that as far back as 1905 he was manufacturing a dry



Important Facts

about Beldenamel **Aerial Wire**

It is endorsed by leading radio engineers as the most efficient type of outdoor aerial.

It offers maximum surface to radio-frequency oscillations.

It is not a trick aerial, but a real, scientific development.

It is furnished in 100 and 150 foot lengths to provide sufficient length for lead-in without joint.

-use a Beldenamel Aerial

THE volume and range of your radio set depends largely upon the condition of your aerial. An ordinary bare copper aerial wire soon corrodes, due to the smoke and fumes in the atmosphere, and its resistance increases rapidly. When this happens, less energy is transmitted to your detector and you lose volume and range. It cheats your set!

A Beldenamel Aerial is coated with many layers of baked Beldenamel, which protects the copper surface from corrosion, and the aerial resistance does not increase. A Beldenamel Aerial insures maximum range and volume, year in and year out. It lasts indefinitely!

Mail the Coupon for Free Illustrated Booklet

BELDEN MANUFACTURING CO. MELDEN MANUFACTURING O 2314E South Western Ave., Chicago


Beldon

There's a Position for YOU in RADIO



THE Radio Industry today holds forth more and better opportunities than ever before. Radio operating and manufacturing companies are constantly employing new radio operators, mechanics, assemblers, testers, repairmen and designers. Truly, this is a radio era.

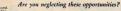Guglielmo Mar as he appears to Signor Marco Honorary Chair of the Radio Insti-







Our Home Study Department permits those who cannot attend classes to study at radio at home in spare time. Check the course in which you are most interested

former Radio Init: radio at nome in spare time. Check the tate of America course in which you are most interested and mail the coupon to the

RADIO INSTITUTE OF AMERICA Formerly Marconi Institute Established in 1909

324 Broadway

New York City

RADIO INSTITUTE OF AMERICA, 32 Broadway, New York City,
Please send me fullilationmation about upon the most basis Course of saids instruction.

| an interessed in the complete course, including code instruction, which qualifies for the U.S. Government Commercial or America Sender Leaves.

| I am interessed in the exchanical course for radio desires, jobbers and assermen.
Name.

......



"B" BATTERIES

A dependable battery that will solve your "circuit power problem on multi tube sets or and for all. It holds its charge for months.

STORAD "A" BATTERIES
Full capacity reliable storage batteries made of highest grade materials and having rubber case and rubber insulated connectors.
Made in three sizes:—R-3-60 amp. hr.; R-4-80 amp. hr.; R-5-100 amp. hr.

Ask your dealer about Storad products or write direct for literature. Distributors territory still available.

THE CLEVELAND ENGINEERING LABORATORIES CO. 2138 Superior Viaduct, N. W., Cleveland, Ohio

Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will.

Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, New York

battery set using a one-inch spark coil and six dry batteries, and that amateurs in those days were successful in transmitting from

There was even a case of an amateur on the Pacffic Coast transmitting ninety miles with such a set.

This, as you will note, took place exactly twenty years ago.

H. GERNSBACK, Editor Radio News.

The Times Flies

ation his first neutrodyne and spent a profitable evening neutralizing the condensers, he began to take a real interest in radio. By the middle of the following week he was building super-heterodynes with crystal oscillators and in less than another two weeks he was discussing the phase angle of the voltage and current with the town's chiefradio engineers.

Before the third of the radio supplements had come out, Micky was writing the most weird and imaginative stuff the town had ever seen.

Then the Old Man began to take an interest in radio other than as a circulationgetter. He began to imagine himself as the director of the destines of a great broadtaken in his mind than it was put into practice. There was a more or less indigent radio merchant in the town who had, when the craze first started, erected a station, the time of the control of the control of the time because the broadcast studie's staff found is necessary to eat occasionally.

The control of the co

the man that agreet failing of the manner of

It was a good set, only it was so sharp in tuning that the Old Man ruined his temper and almost sent his wife into a nervous breakdown before he was able to hear even a local.

Once started on the road to bugdom, he

was entirely belghess in combating the bacillus. Gradually he became more and more addicted until, as the station became of some consequence, it soon reached a more important place in his mind—and the minds of his employees, perforce—than anything else, even including the feature section of the Sunday.

And as he took more interest in radio it behoved the clitors of the radio section of the paper to look to their copy. It became incumbent upon them to produce more understand the intricacles of the art he turned down a great deal of the stuff they had been printing before. This cut greatly into the radio celliors' loading time. They they have been printing before the stuff they had been printing before. This cut greatly into the radio celliors' loading time. They they have been printing before the stuff of the printing has its compensations, though, and



Crosley Super-TrirdynSpecial 800.
Crosley Musicone \$1750

Better Results from 3 Tubes Than from 5

Sounds improbable doesn't it? But it is a scientific truth, first demonstrated in the Crosley laboratories and then confirmed by the performance of thousands of Trirdyns the country over.

Employing but 3 tubes, the Crosley Super-Trirdyn consistently equals, and in fact surpasses, the more costly 5 tube sets in performance.

These astonishing results are simple to explain. Instead of passing the incoming signal once through each of 5 tubes, Crosley design passes it through two of the three tubes several times, each time building up its strength and adding to its volume.

Even the technically uninitiated can see the advantages: simplicity instead of complexity; fewer dials to adjust; sharper accuracy in selecting stations; greater clarity; greater volume.

Yet that is not all. Simplicity of

turing costs lower and bring about a lower cost to you. This, combined with the economies of gigantic production, makes the Super-Tirridyn lower offered. For Crosley is the world's largest builder of radio sets—owning and operating parts factories, cabinet woodworking and assembly plants.

Listen to a Crosley Super-Trirdyn under the most exacting conditions. Make an unbiased comparison with the most costly receiver you have ever heard. Forget the radical difference

in price.

Then will you understand why the Crosley Super-Trirdyn represents a genuine achievement in radio performance and value which all America was quick to recognize and reward with increasing sales.

Write for attractive illustrated catalogue. Authorized sales and service stations everywhere.



Add 10 per cent to all price West of Rocky Mountains
Crosley manufactures receiving set which are licensed under Armstro.
U. S. patent No. 1,13,140 an priced from 89,75 to \$60.00 with not accessful.
Crosley owns and operates W. L. W. first prepare control super-power first prepare control super-power.

EROSLEY

Better-Costs Less

RADIO

THE CROSLEY RADIO CORPORATION - CINCINNATI, OHIO



BOYS! We Will Pay You Liberal Commissions and Award Dandy Prizes —For Your Spare Time.

Y OU can easily earn all the money you want by becoming a member of our Young Men's Sales Association. It's easy. Simply sell and deliver our four popular magazines—Radio News, Science and Invention, The Experimenter, and Motor Camper & Tourist—in your neighborhood.

There are many boys just like you who are turning their spare time into cash by taking advantage of this pleasant way of making money. You can do the same. No experience or money is necessary. There is no obligation.

Take your pencil now and fill in your name and address on the coupon below. Then mail it to-day. It will bring you everything you need to start making money and earning dandy prizes right away.



Thomas Lathrop of Michigan, one of the many members of our Young Men's Sales Association, who earns all the extra money he needs through selling and delivering our four popular magazines.

| Use | Scissors | Here- | | |
|---|----------|-------|------|--|
| E. J. FOLEY, Department R-10, Experimenter Publishing Co., 53 Park Place, New York City | | | | |

| ther of your Young Men's Sales Association. | Please tell me how I | can do so and become |
|---|----------------------|----------------------|
| | | |

| Address | | | | | |
|---------|--|------|-------|------|--|
| City | | | State | | |

they found that larger and larger expense accounts for parts, labor and what-not would pass unquestioned. The result of the Skipper's interest, on the whole, was simply about four wights of extra work for the boys and a couple of new suits each—which they sorely needed.

After the first spurt, other things gradually made the Old Man pay a little less attention to radio and so only the four nights of work a week were necessary—no more. Few of his demands on them could not be fulfilled.

Periodically, he desired a new set which had to be the ne plus ultra in radio, but there were always new circuits which could be a some and the second of the second of of great colm, as they say, simply forbode a storm of equal intensity, and it certainly worked out in the case of the Odd Man. One worked out in the case of the Odd Man. One of the feature section for the Sunday me, (which was printed on Thursday) he conceived a brilliant idea of having the radio editors find consenting which would furnish

collors find sometiming which would turnals. Now as all good offiers know, the Monday morning edition is the base of editoral of the collection of the collection of the collection of news—and it invariably seems that people generally are better behaved on the people generally are better behaved on the the work. Also, since the European countries worthip the same delry, they jilevaise tres worthip the same delry, they jilevaise tres worthip the same delry, they jilevaise ters as Labor Government and the juternational delt. This lowers quite a hole on the free to the collection of the collection of the lab night's sleep if the could rest confident that the Radio Department would furnish at the collection regularly, a safe for the Mostay edition regularly, a safe for the Mostay edition regularly.

The Old Man gave orders and expected them to be carried out. Therefore, Micky found it necessary to visit Henri's every Sunday. Henri's, be it known, sold some stuff in tea-eups which gave Micky the in-spiration for the ideas which he promptly repeated to Zey, who just as promptly supplied the technical details to make the scheme plausible and interesting reading to

the radio fan.

The first Monday after the order was given, the front page column told of a new method for catching all the boolegagers in method for catching all the boolegagers for finding device. The next week the column told how radio could be used to lighten the work of doing the family wash. From that time on the syndicates began to ask for the work of the first page are distributed by the first page and the stories which appeared regulatify our Monday morning.

Then the Old Man had the grant idea. Ever since he had been the owner and mansaging either of the Timer he had been been the water had been the control of the action of the Timer had been the desired and across the river. He wanted to outself he serves the transport of the transport of the transportation, to atthough both Holden and transportation, to atthough both Holden and transportation, to atthough the Holden and transportation, to atthough the though and the transportation of a stable to agree on the terms of joint responsibility in the building of a bridge. As a result, a slow terry service of carrying papers, and the necessity for a couple of extra handlings took minutes out of the Timer and seconds count in selling of the Timer and seconds count in selling

Considering the imagination Izzy and Micky had shown in the other exploits they had attempted, the Old Man was perfectly justified in believing they could carry another one through successfully. So when he got the grand idea of beating the Argus

Continuous, unfailing "A" Power

-in a single compact unit .. that automatically replenishes itself

THE new Gould Unipower asks for a place in your set on this basis—that it will contribute more than anything else to the convenience, perfection and economy of operating your set—that it will give you the most that your money can buy—that it will lansish "A." battery failure, the most frequent cause of poor radio recention.

Here are the facts about Unipower.

A new kind of "A"

Unipower is a single compact "A" power unit that fits inside most radio cabinets. It takes the place of dry "A" batteries or of separate storage battery and chareing units.

Unipower is quickly and easily installed, Just connect two wires to your set, plug in on your light current, and the job's done! Unipower is equipped with an exclusive Bulkite charger of special design. Unipower will last you for years, and there are no tubes, bulbs, lamps or working parts that require frequent and expensive replacement.



With Uniposeer, you insure your set again
"A" battery failure—the most freque

Off when it's on-On when it's off

A unique feature of Unipower is the single master control switch that governs the operation of your entire set. When the witch is ON, Unipower feeds your set rich, quiet power that gives ideal reception, with neither hum nor noise. When the switch is OFF, Unipower automatically replenshess tested on a low trickle charge and with a minimum consumption of current—a few cents a month.

The most your money can buy

When you also consider that Unipower banishes the cost and inconvenience of dry "A" battery renewals, or the bother of charging a storage battery, increases the life of your tubes, and in addition, gives you the finest kind of continuous, unfailing" "A" power, you see how economical Unipower really is. You'll

economical Unipower refind that it pays for itself over and over again.

Decide to see the new Unipower today. The nearest radio dealer has it. Ask him for a demonstration. Then make your decision! The Gould Storage Battery Company, Inc., 250 Park Avenue, New York.



comfortably inside most set cabinets. It is quickly and early installed. Just connect two uses to your set, plug in on your house current and you have continuous, unfall ing "A" power in-

Unipower Off when it's off—On when it's off



A Revelation In Tone-Volume-Clarity

Here is a "loud speaker" that brings the artists into your very room so realistic is its reproduction.

Piano music, the most difficult to reproduce, sounds so natural that you are carried away by its beauty.

Vocal selections retain all of the colorings of the artist.

Orchestra music is a treat; every instrument can be heard, clear and full.

Magnetic diaphragm control-used exclusively in the Kellogg Unit-is the new principle that performs these wonders in radio

No excess vibrations, no chattering, every tone true. The Kellogg Unit is available for use with a phonograph and

will reproduce voice or music with a full, sweet, clear tone. A popular instrument. The Kellogg Symphony Reproducer is a revelation in Tone—Volume—Clarity. At your dealers for \$20.00-Hear one today.



"Not Merely a Loud Speaker."

KELLOGG SWITCHBOARD & SUPPLY COMPANY, CHICAGO, ILLINOIS

Kellogg Symphony Reproducer



The Preferred Aerial

More and more the users of today's popular types of radio sets are turning from unsightly, inconvenient outside aerials to the more selective, easily controlled,

Reception is astonishingly improved through the exclusive basket weave method of winding the silk-insulated stranded wire. There is a Bodine Loop that will give

perfect service with your particular set. The Bodine is exceptionally fine for the Remmler Superheterodyne and Grebe Synchrophase. Consult Dealer. Price, \$8.50-\$10. VOUL

BODINE ELECTRIC COMPANY 2256 W. Ohio Street. Chicago, Ill.

C. L. PARKER atents, Trade Marks, Copyrights, Patent Litigation for Improved Reception -

out of half of its circulation, and raising his own advertising rates proportionately, he called on his two radio editors to perfect the mechanical details of his scheme. The idea was simple in the extreme to an ordinary radio engineer who was thoroughly trained and sober. Izzy was always that and Micky fulfilled requirements some of the time-but not always. There was the

The Times was the better paper by far. It had more wire news, a better equipped printing shop and a higher class staff. But all of this was of no avail when the river. and the lack of a bridge providing fast and to make the trip simply prohibited the Times getting to Hyattsville with the news while it was still news-was considered. As a matter of fact, the people of Hvattsville had to read the less desirable Argus because of the two-hour lapse. By the time workers were going home in the evening, the Argus would have the complete box scores while the Times, on the newsstand beside it, still concluded its accounts of the games in the fourth or firth iming. The Times would easily sell if it could get on the streets an hour or so sooner. Although the distance between the towns as the crow flies was less than forty miles, it was more than two hundred by rail, because the connecting line ran down the river a hundred miles to the nearest bridge, and then back up to Hyattsville after passing a junction point. The papers could likewise not be sent across the ferry both on account of the extreme expense and the time limit.

The Old Man, scientist as he had become therefore decided to carry the papers in the only way by which he could be sure of a speedy, direct service at the proper time. He would transport them by airplane.

But that was only half of the idea. Since he had become such a thorough radio bug he bethought himself of some method through which he could gain a little 'house advertising at the same time he inaugurated the service. Even in that part of the West, airplanes with pilots were more or less common. Everyone had seen airplanes. In fact, there was a fellow out at the park who made his living taking people for rides in one of them.

But a riderless, radio-controlled airplane was a thing apart for any community and could be calculated to attract plenty of at-

And that is what the Old Man visioned after reading one of Micky's Monday morning dreams. Such a plane would, of course, be controlled from one end of the flight or the other, or possibly both. The stunt would have to continue for only a week or so, in order to get the publicity value, then a regu-lar airman could be engaged to carry the papers. So the Old Man called on Micky and Izzy to make the necessary arrangements The evening after the Skipper had made them privy to their little job, they adjourned to Henri's around the corner to figure out a few ways and means.

"Izzy, me buck, this is the largest order yet," said Micky. "Now the question is: "are we going to do it?"

"You mean, can we?" said the ever-serious

"No, I mean, will we? If we can't, of course we won't. If we don't, we look for some nice newspaper that needs a couple of good radio editors.

"Well, it can be done, and if we can't do it, we can make it cost the Skipper so much he will tire of his stunt.

It was a very few minutes until Micky was drawing weird diagrams and handing them to his accomplice. Izzy looked them

over, shaking his head at the first dozen or so. Then his face lightened.
"You've got it," he said and immediately



With MACMILLAN in the ARCTIC

ONCE again that intrepid explorer, Donald MacMillan, has gone into the Frozen North. And once again—for the fourth time—the relied on Exide Batteries to serve him, without flinching, through the extreme rigors of the Polar region.

Each item of equipment on such an expedition is chosen with utmost care, for life or death hangs in the balance. On previous voyages to the Arctic with MacMillan, Exide Batteries have been through shipwreck, bitzard and incredible cold and never in once have failed.

On this latest adventure all the storage batteries are Exide—for radio sending and receiving, for electric light aboard ship and on shore, for operating the sensitive scientific instruments. The three U. S. Navy airplanes that accompanied MacMillan's two vessels are equipped with Exide Batteries. Wherever radio must not fail,

> ways find Exide Batteries have been installed—in government and commercial plants—on the giant ship Leviathan, on the Navy dirigible Shenandoah, on the new British airship R33; on every continent and the seven munication throughmunication through-

> > outthe modern world.

you will almost al-

The same qualities that make Exide the choice where lives are at stake are built into the Exide Batteries that you can have with your own receiving set. Staumch and dependable, the Exide gives uniform current through a long period of discharge and assures the clearest reception of which your set is capable. There is a type for every tube and a size for every tube and a size for every tube and a size for every did and a size for every did and a size for every the and all Exide dealers.

THE ELECTRIC STORAGE BATTERY COMPANY Philadelphia

In Canada, Exide Batteries of Canada, Limited 153 Dufferin Street, Toronto





Exide 6-volt "A" batter in one-piece case There are also Exide "A" bat ies for 2-volt and 4-volt tubes i "B" batteries, 24 and 48 volts 6000 milliampere capacity. T



NAVY MODEL C-10 Super-Heterodyne The Highest Class Receiver in the World

Wave length range 50-600 meters with removable Coils. Panel Dimensions 28 3/16 in. x 8 in. x 1/4 in. Only two major tuning adjustments.

Total amplification almost 2,000,000 times.

For any Circuit
Prompt shipment can be
made on tested, standard
apparatus of the following manufacture:

E. I. S., Inc. General Radio Willard

Benjamin Electric
Allen Cardwell
Dubilier Formics
Western Magnavoz
Jewell Amer Tras
Western Electric
Radio Corporation
Music Master
Cutler Hammer Fros

A high powered 10-tube Broadcast Receiver capable of receiving over 3.000 miles under favorable conditions, and having a degree of selectivity far in advance of others.

We believe the Navy Model C-10 represents final superiority over any receiver now being manufactured or even contemplated for broadcast reception.

Attractive illustrated literature gladly mailed upon request. Write direct to

NORDEN-HAUCK, INC.

1617 Chestnut Street, Philadelphia, Penna.

began making sketches of his own. The plan was simple. The broadcast station was in a pretty straight line between the two landing fields in the towns. This would save the Qld Man money. The distances to be covered were short and the half-kilowatt of the triasmitter could be used for the long trip between the two fields, while small short-wave transmitters could be used at the

two landing fields.

The old army differential loop beacon system would be employed to keep the plane on its course. One side would be set to transmit dashes, great long ones, and the other one would have an automatic lighter on the plane would be sufficient. The output of the power amplifier would be control to the power amplifier would be con-

nected to two relays.

Both of them would have time relays controlled by an air leak valve. This would make it possible to keep the plane within a ten-degree course. It could not get far enough off the line of flight to be out of control of the small transmitters, which were

to be installed at both the landing fields for bringing the plane down and controlling the take-off.

The time relay selector idea appealed to both of them as a stroke of genius. If the plane went too far to that a stroke of plane went too far to that a stroke of connecting the small motor to the horizontal rudder. This would bring the plane back into course and, as soon as the center point was reached where the dots and dashes were

of equal strength, the connector would be beld in a neutral position. A couple of gyroscopes in the plane would attend to the matter of equilibrium. The special short-wave receiver. This receiver would, in reality, be five different waveeach working on a slightly different wavevertical path of the plane; a second would control the contact; the third would cut out the beam receiver and the other two would control the side-to-side course, of the slip all work direct to motor relays, doing away

with the complication of switches. The short-wave transmitters would have wave-

changing devices which would give instant control.

Many nights they worked over the technical plane. In a couple of weeks they had drawings with the flourishes to show the control of th

The plane was an easy matter. The fellow at the park was not doing a land office business and was willing enough to be rid of the thing. This detail completed, Izay and Micky started immediately upon the construction of the sets necessary. At the first test, nothing at all happened.

At the first test, notting at all anapeneo. The Skipper was ready to give them both the so-called gate when Micky remembered that the hald left the ignition of the plane as it was. Each of the spark plugs was sending out its own brand of static, so that the short waves had no effect whatever on the relays and the plane-operating devices. The Old Man went home to dinner thoroughly disgusted with radio. Izzy and

ougnity disgusted with radio. 1222 and
Micky spent a pleasant evening putting yards
of copper screening around the engine and
grounding it to the engine frame and the
frame of the plane.

The party offerseen the plane table of

The next afternoon the plane took off beautifully, fulfilling the dreams of even the enthusiastic Micky.



Best by Test

Three types—one quality—the BEST!

"CeCo" Tubes prove their worth by performance! Clarity of tone, rich volume, long life
—CeCo has them all to a degree that will

Serve equally well as radio frequency amplifiers, detectors, oscillators and audio fre-

quency amplifiers.
CeCo Tubes make any good circuit better.
Every tube backed by a guarantee that's

backed by a company of established reputation and responsibility.

C.E. MANUFACTURING COMPANY, Inc.

C.E. MANUFACTURING COMPANY, 702 Eddy Street, Providance, R.I. Trade Supplied through Jobbers Only!

Jobbers-Write for details and prices. Set Manufacturers-Ask us about our SPECIAL MATCHED tubes.



TO THE RADIO DEALER

Let us explain how you can make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade.

EXPERIMENTER PUBLISHING COMPANY, 53 PARK PLACE, NEW YORK CITY





DYMAC Type E Headset The same quality headset with improved headband at low price to meet popular demand. 2,200 or 3,000 ohms as preferred. List, \$3.00



DYMAC Vernier Dial

Same as on DYMAC Selecto Five Receiver. Provision for both coarse and fine tuning. 4" diameter; ver-nier ratio 12 to 1. Easily mounted on any condenser. Adds much to the performance and appearance of any List, \$1.50

Other DYMAC Accessories and Parts

Loud Speaker Unit, \$5.00

Audio Frequency Transformers \$2.50 to \$4.00 Soldering Set (standard), \$2.50 Sub-Panel Socket, 75c Jacks, 50c to 90c



A Marked Contribution to Radio Reception The DYMAC Selecto Five

This is the new set that has surprised by its performance even radio engineers who have been striving for years for improvement in reception. The DYMAC Selecto Five is a

new type receiver made by the manufacturers of the DYMAC guaranteed radio products. It is not a neutrodyne; it is not a super-heterodyne; it is not a regenerative set. In rigid tests, under difficult condi-

tions, it has outperformed them all for accurate rendition of tonal values.

For best results with the DYMAC Set, use a DYMAC Speaker (\$8.50) and DYMAC Type G Ear Phones (\$5). These DYMAC accesso-ries improve the reception of any set.

PRICE \$75 But let it talk for itself. Put it in your home on trial. If you have had difficulty in getting satisfactory results because of peculiar local conditions, you are the one we most want to try it. For through the Selecto Five you get the fullest enjoyment of the

improved broadcasting. Encased in a handsome mahogany cabinet finished in walnut, with ebon ized panels and base, and with DYMAC black and silver finish dials, the DYMAC

set will harmonize with the finest interiors. If unable to obtain quick delivery of a DYMAC Selecto Five from your dealer, write us. We shall see that you are supplied promptly.

Every DYMAC product guaranteed for one year

ELECTRICAL PRODUCTS MFG. CO.

New York Office: Metropolitan Tower Export Office: Ad. Auriema, Inc., 116 Broad St., New York City

RHODE ISLAND

DYMAC

PROVIDENCE.

Factory Sales Agents

The// SUPER-HETERODYNE



Here's the finest, most complete book of data and information ever compiled on the Standard Super-Heterodyne.

This is the big book of instruction and information on the various standard "supers" in common use today; a complete, up-to-the-minute, impartial 64-page book covering all the builder or user of this type of set might want to know. The Super-Heterodyne is written by a radio authority who not only has years of trade and practical experience but is constantly designing modern radio apparatus. It is a handy, useful size, 5½ x 7½ inches, printed clearly, profusely illustrated, easy to read and bound with a handsome two-color cover. This is the very latest of the complete library of Experimenters' Handbooks on radio. These books are complete practical guides to almost every important phase of radio transmission and reception.

You can get any of these books at your radio or news dealer or direct from us.

The CONSRAD COMPANY

233 Fulton St. New York, N. Y.

Then the war began between the two tleman of the old school, a hater, with all his heart, of the fads of modern civiliza-tion. The first edition containing the an-nouncement that the *Times* would be delivered in Hyattsville by a radio-controlled plane simply served to send him to his sanc-tum in high wrath. The wrath, however, became tinged with a pink fear when the business manager came running into his office with a huge placard which stated that at last Hyattsville was to get its news on time and that the very latest scientific device would bring it.

The gentleman of the Argus had distinct feelings on the subject of science generally, and radio in particular. He classified the latter as simply the latest device of a jazzmad age to beat up its flagging emotions and mental powers. Radio, he said, was simply a fad, had been since its inception, and would remain that as long as there were fools left to sink thousands of dollars in useless broadcast stations and other fools to listen nightly to the drivel they flooded God's good, clean Furthermore, he put his thoughts into an

editorial, with the result that the advertis-ing manager told him a day later, when the tallies were made, that he had cut off several thousands of his circulation and permanently eliminated several cash-paying radio adver-

This served only to force the old warorse to renewed efforts to quash this latest device of the devil. The same day another editorial appeared and another drop in circulation was reported in due time. apparent that the readers had their own

But there was at least one man in the Argus organization who believed that radio would be successful in spite of the editorials which said that the stunt with the plane, "announced by our contemporary across the marshes," would be a great and ignominious The chap who believed in radio was one

Taylor, a cub of the rankest sort, who had been on the paper less than a month-been with newspaper men briefly enough still to hold the old ideas concerning newspaper men generally, and star reporters particularly.

He knew that the plane would fly, and being assigned to the Argus' staff in Holden, bethought himself of ways for turning the behought himself of ways for turning the Timer stunt to the glory of the Argus. The Timer, the thought, liad no business to attempt to take the circulation of the Argus in Hyattsville. Lost circulation, lost revenue, lost job. This was his sequence of thought. The day of the premier flight was less than two weeks off. And then Taylor lad a grand idea. It would be quite simple to iourner over to his own town, ston 2+ his. a grand idea. It would be dute simple to journey over to his own town, stop at his office, get fifty or a hundred of his own be-loved Argus, wrap them in a bundle similar to the Times, carry them to Holden, slip them into the plane while no one was look-ing and so send the Argus back to Hyattsville by the Times plane.

Of course, if on the opening day of the service, with the Old Man making his grand speech, they should haul forth a few copies of the Argus instead of the Times, there would be a grand howl of derision and the entire scheme would appear extremely ridicu-

As the time grew near, the Old Man of the Times grew more and more enthusiastic. He wrote a long speech which he planned to deliver at the first landing of the plane in Hyattsville. He would tell the multitudes who would gather to witness the stunt that at last they were to get their news on time, etc., etc., and ad infinitum. It would be the valedictory of science as against "mossbackism." In fact, it would be the greatest victory for the Times in years.

Pacent Engineering Achievements

More Improved "PACENT" Essentials for the Season's Better Receivers

RHEOSTATS and POTENTIOMETERS

The Pacent Genuine Bakelite Rheostat and Potentiometer are the last word in resistance devices. The finger-fitting, fluted, mushroom knob of genuine Bakelite conveys the velvety feel of the smooth running positive edged contact without click or noise and is a joy to the eye. The Pacent two unit construction simplifies installation and preserves the accurate factory adjustment. Every rheostat adaptable to one or two hole mounting. Made in all standard ohmages and supplied with silvered dials and black knob or with gold dial and mahogany knob. PRICE. \$1.00

Pacent Porcelain and Moulded Rheostats and Potentiometers made with Porcelain Base, edge contact and 3/16 inch shaft, or Black Moulded base, side contact and 1/4 inch shaft -provided with elongated mounting holes to accommodate varying spaced panel borings. Two Unit construction, Pacent type knob. Made in all standard ohmages and




Pacent Radioglass sockets-for UV199 type tubes and for standard 201A types. Made of glass specially prepared for radio purposes and used when low dielectric losses are desired. One piece direct contact members with exclusive Pacent self-cleaning feature. Special pieced and formed soldering lug ends for easy soldering. PRICE either size. . 40e Also made of Pyrex for UV199 type tubes. PRICE......\$1.00

RADIOFILE and RADIODYLE

The Pacent Radiofile provides a new and convenient means of recording stations by name, wave length and frequency. With this device several stations of the same wave length can be permanently logged without difficulty. Insulating disc and mounting pins are supplied, and by grounding one mounting pin an electrostatic shield is provided. Made to fit standard 3 and 4 inch dials and to accommodate all standard condenser shafts. Beautifully finished in Satin—Silver or Gold. PRICE—Silver or Gold finish for 3"

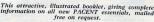The Pacent Radiodyle is one of the finest and most practical dials on the market today. It presents a beautiful appearance. There is a pleasing contrast of the fluted black knob with the silver-finished metal back. The knob is made of genuine Bakelite,



MANUFACTURERS, JOBBERS and DEALERS Write or Wire for Particulars and Prices

Pacent Electric Co., Inc. 91 Seventh Avenue · New York, N. Y.

OFFICES: CHICAGO-MINNEAPOLIS-BUFFALO-BOSTON-PHILA.-WASH., D. C .-SAN FRANCISCO-ST. LOUIS-PITTSBURGH-JACKSONVILLE-DETROIT CANADIAN LICENSEE-WHITE RADIO LTD., HAMILTON, ONTARIO












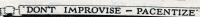



To insure the right hook-up:

GET a PREMIER S-Wire Battery Cable. Keeps wires neatly concealed, untangled and out of the way. Five different colored wires insure proper battery and set connections. With a flip of your finger you can un-\$1.00 hok "A" battery and hook on the charger. In attractive carton..... At your dealer's or swite

Crescent Braid Co. Inc. Providence R. I. Makers of Premier "Blue Ribbon" Extension Cords, Premier, Jr.

Important Back Issues of "Radio News" available

The back issues of "RADIO NEWS" contain many important and valuable articles on Radio Circuits and General Information. Here is a list of important back issues on hand.

JULY, 1924 ISSUE How to Make and Use a Waverneter.

By L. W. Hatry
A Local V.T. Transmitter
Roflex Receiver with Neutrodyse Centrol.
By A. D. Cowper

AUGUST 1924 188UF e Seledyne Principle. By Dawding & Rodgers Trepadyne Circuit. By Clyde Filed Brying a Tuned Radio Francesy Reselver SEPTEMBER, 1924 ISSUE Neutrodyne Reseivers, By Graves
A 5-Tube Reseiver of Advanced Design. OCTOBER, 1924 ISSUE

A.R.F. Seledyne Receiver.

By Dowding and Rodgers NOVEMBER 1934 ISSUE A 100-Watt Master Oscillator Transmitter, By J. E. Fetzer A Cascade Regenerative Receive

DECEMBER, 1924 ISSUE A Short Wave Adapter for the Broadcast Re-

Colver.

JANUARY, 1925 ISSUE

Experimenting with 5 Meters, By W. A. Bruns
An Ideal Lew-Loss Broadcast Receiver.

By Clyde Fitch

EERDHARY 1925 ISSUE A Good Short Wave Receiver.

MARCH 1015 19911E How to Build an Ultra Short Wave Recei Some Super-Heterodyne Notes, Some Super-Heterodyne Notes.

By W. Taylor
The Radio "Uni-Set." By H. M. Towns

APRIL. 1925 ISSUE Law Less Short Wave Set.

MAY 1925 ISSUE MAY, 1925 1850...

The Monophase Circuit. By F. H. Dalet A 5-Meter Transmitter. By W. B. Arvin An Efficient Crystal Detector. By R. Hetchison By D. E. Learned By D. E. Learned By D. E. Learned

JUNE, 1925 ISSUE

JULY, 1925 188UE New Uses for the Vaccum Tube. By C. B. Bazzoni A 3-Range Receiver.

Price 25c Each PREPAID

EXPERIMENTER PUBLISHING CO., Inc. 53 Park Place New York, N. Y.

Hyattsville was literally covered with posters telling of the great event.

The editor of the Argus behaved like a mad bull. He wrote scathing editorials on his event his attacks become actually libel-

Each morning the Skipper, just as emphatically, wrote another story, telling that the plane would mark a new era. The good citizens of the two towns heartily enjoyed the fireworks. They saw the battle as an-other form of the old defying the new. and opinion hung pretty much on the result of the flight

Micky and Izzy enjoyed it all fully. Every day they spent at the hangar. Aside from a trial trip now and then, just to keep their a trial trip now and then, just to keep their hands in, they had nothing to do and en-joyed it immensely.

The cub, Taylor, was so nervous and ex-cited over his well-planned coup that he passed up two or three small stories he was

supposed to get

Then the great day arrived

At the pressroom, long before time, Tavfor stood waiting at the door for the cirfor stood waiting at the door for the cir-culation manager to appear and give him regular early editions. But, being a hard-boiled gentleman, the circulation manager paid no attention to the cub when he did paid no attention to the cub when he did appear, and Taylor began to fear for time. While no one was looking he grabbed a bundle of fifty papers wrapped for delivery and piled on a long bench. He ran out, jumped into a friend's car and set out for the landing field at Holden and the Times

plane. Fearing detection, he slipped the papers into the plane at the first instant possible, on top of the Times bundles. He went on to Henri's, drank two cups of "coffee" in celebration and talled more loudy than necessary to his field boss. He then sped back to Hyattsville to watch the tim from a safe distance. He selected a point near the platform from which the Old Man was to make his speech. The Old Man was on the platform and

Izzy was at the short-wave landing-control
set. Everything was in readiness. The plane was to start at high noon In his excitement, Micky, at the Holden

station, pulled the wrong switch to start. The plane would not take off; one of the tuning inductances had been thrown off at the early morning test. The crowd at the field-it was a small one-became nervous. There were a few swift strokes at one of the relays and a test. It seemed to work but there was nothing steady about it. It was the left turn relay.

was the left turn relay.

Micky moved the starting point of the
plane a little further to the right and so
avoided the necessity of using it again on
the start if it should fail. A second try
and the plane took off beautifully. By breaking the contact just as it was being straightened out, he caught it with the beam transmitter and held it in line after making a quick shift to release the short-wave land-ing control. At the Hyattsville end, the crowd was enormous. All the chief citizenry had been issued special invitations and were in attendance. They had come early. The Old Man was anxious. The platform was the only place he could stay. He could not get down and consent to mere talk. He wanted to see the plane. It would probably not arrive before a quarter of one.

The spectators were beginning to look at The spectators were beginning to look at their watches and then turn to the sky. At five minutes of one, they were beginning to shift from one foot to the other and show signs of laughter. The Old Man was upset. He tried to go over the first lew paragraphs of his speech. It would be the final blow to the old fossil at the Arpus who had contended that the whole thing was a Joke. A little twinge of fear seized him. It was



condemned radio music as false and distorted, approved the re-sults of Karas Harmonik amplification with great enthusiasm. Prominent radio engineers subected Karas Harmoniks to exhaustive laboratory tests-and pronounced it a technical masterpiece. Technical editors who promoted the season's most successful hook-ups specified Karas Harmoniks in their circuits. The triumph of the Karas Harmonik was complete!

But, for all of this, the enjoyment of Karas Harmonik amplification was too greatly confined to one class of radio enthasiasts. Home set builders bought Karas Harmoniks by the tens of thousands. They were free to pick and choose. They were most exacting in their demands for the newest and best developments.

It was the owners of factory-built sets who missed the

your mind to do it now—at once. (In large cities, most good dealers carry Karas Harmoniks—and in many small towns. If your dealer is out of them, order direct from us Send no money. Just use the coupon below?

Karas Electric Co.,

4039 N. Rockwell St., Chicago, Ill Karas Electric Co.,



No Need to Hunt for the Sensitive Spot The Carborundum Detector Unit is Fixed—Permanent

PROM the first moment you hook up the Carborundum Detector Unit in your Reflex or Cynstl Set you get a positive sensitivity that is permanent. §There are no adjustments. This is one Detector Unit that retain is sensitivity indefinitely. It will not burn out. §The Carborundum Detector Unit comes to you laboratory tested and it's made with a special Carborundum created for Radio use. §It will give you clear, true, tones—increased selectivity—greater volume and distance.

Sold under a Guarantee by All Dealers
MADE ONLY BY

THE CARBORUNDUM COMPANY, NIAGARA FALLS, N. Y.
New York, Chicago, Boston, Philadelphia, Cleveland, Detroit, Cincinnati
Pittiburch, Millenuke, Grand Ramoda

Carborundum Detector Unit



"Doubletoroids" make more selective sets possible, since they do not form miniature loop aerials. "Doubletoroids" hold static and other disturbances to a minimum since no current from an external source

can intuence them.

Outstanding Features of the Doubletoroids.

Both primary and secondary are true toroids.

The magnetic path is shortest.

It is the most compact.

RADIO FOUNDATION, Inc.
25 West Broadway New York



The Noncles Gridfeak improves recotion because it can be adjusted for every station. Pits standard brackets. Absolutely noiseless. At all dealers and in the better sets. NONOISE GRIDLEAK



DON'T LOSE YOUR RIGHTS

Young Men—Turn Your Spare Hours Into Money!

Bers hig notes, prizes, and swareds calling RADIO NEWS, SCIENCE AND INVENTION, THE
EXPERIMENTER, and MOTOR CAMPER, & TOURIST in your neighborhood. We train you as
our salesman and pay you liberally for your time. Write at once and we will help you. REIDWELL

THE EXPERIMENTER PUBLISHING CO., 53 Park Place, New York, N. Y.

one o'clock and the plane was not yet in

sight.

Suddenly Izzy began to work frantically with the slapt-twave set. In a few seconds his work was seemingly rewarded. There was the faintest hint of a roar. In another two minutes the piane was in sight and the goods had forgotten their jokes and the property of the sight paragraphs of the talk.

graphs of the falls, and the fall was replicated that ever. It was strying to get the plane out of the path of the beam transmitter. He threw the indicates to the left and closed the key. The discarce of the left and closed the key. The something and then settled back into its something and the settled back into its something and the right and again depressed the key. The same result followed his attempt. He showed that the thresh we working only on half a load. The plane was wiftin two hundred that the thresh we working only on half a load. The plane was wiftin two hundred bad of the plates, carring little whether he load of the plates, carring little whether he

Again the key was depressed and the plane almost fell because of the sharpness of the turn it made. At last it was safe from the beam transmitter and the landing relays were working. He drove it around a huge circle and, with a little maneuvering, it landed as easily as if it had been in the hands of a pilot. The throng waiting for the papers thought it was just a grand-stand stunt and commented on the excellence of

melted them down or not.

Izzy's workmanship.

There was a final volplane and Izzy released the contact with another depression of the key. Several men rushed out to

bring the plane to a dead stop and fetch the papers. An involuntary cheer went up from the throng,

The papers in bundles were thrown at the Old Main's feet. There were several yells, one or two grunts. He started on his speech and while growing more and more cloquent reached down to the topmont hundle for one at the climax of his talk. He was just reaching his climax, when—he had not yellowed at the paper—he unfolded it to full size, gripping it in his hand at his side. He was about to raise in for the gaze of the was about to raise in for the gaze of the yes, the caught the line across the top of the first page. It read, the Hystirtelli drapust for the grant of the caught the fine across the top of the first page. It read, the Hystirtelli drapust for the grant of the g

He dropped it like a hot cake. The climax of his speech had been ruined, the victory of science had been turned into defeat by some crude horse-play. He thought fast. He thought of feinting a faint, of suicide, of murdering the person responsible.

Izzy saw something was wrong and from the edge of the platform reached for the paper. He scanned the front page. A smile lighted his face. Jumping in front of the Old Man, he held the paper up for all to see. There was a titter at first, now and then a gasp and finally a roar of laughter. Beneath Feh Hystirstille Argus in letters

Beneath The Pryatismile Argus in letters filling almost the top of the page there was a banner reading, "Paper Plane Fails in First Flight." And below, in almost as large letters, "Publicity Stunt a Deserved Failure."

The Old Man was sputtering about in an attempt to learn the cause of the commotion. As he was behind largy, he could not control to the control of the country of the could not be a country of the cou



today

Write

for your FREE copy of this valuable book

Every radio fan, every owner of a receiving set and, above all, everyone who is contemplating the purchase of a set this fall, should have a copy of this new book on radio storage batteries.

It explains fully just what service storage batteries perform in the operation of a set and which types of batteries are best suited to the various kinds of radio sets on the market.

You naturally want to secure the kind of batteries that will give you the best results. Then this book will be indispensable to you, for it gives the information you need to make a wise selection. The book also explains the best methods of caring for storage batteries to insure their long life, how to charge batteries properly, how to connect batteries to a radio set, and how to arrange them so that recharging is reduced to a very simple, easy matter.

Write for this FREE book today. The facts it contains will save you time and money and add greatly to your enjoyment of radio. A post-card will bring it to you by return mail.

THE PREST-O-LITE CO. Inc.
DEPT. 107 INDIANAPOLIS, IND.
New York San Francisco

Prest-O-Lite "A" and "B" Batteries offer truly remarkable savings. Although standard in every respect, they are low priced. They will last for years and are all easily rechargeable. See them at your dealer's.





23 M R R "A" Battery




69 W H R "A" Batter



48 L R R "B" Battery



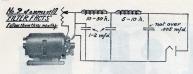

The "pi" type of filters described in numbers 7 and 8 of this series while excellent for C. W. and some forms of phone modulation are not suitable for Heising modulation. The large condensers tend to short circuit the modulating frequencies. This may be overcome by the addition of a small choke, 5-to henries, in the plate lead directly after the filters, followed by a small con-

Bulletin No. 237-B lists over three hundred motor-generator combinations that will give the maximum miles per watt. Write for your copy to-day.

ELECTRIC SPECIALTY COMPANY TRADE "ESCO" MARK

211 South Street.

Stamford, Conn. This complete series with other valuable motor-generator information may be obtained in namphlet form. Write for your copy

100 Volt Storage "B" Battery for \$1000!



BATTERY Cleveland, Ohio withBulb \$14.50

LEARN THE CODE AT HOME OMNIGRAPH



THE OMNIGRAPH MFG. CO., 15 HUDSON STREET, NEW YORK CITY

Young Men — Turn Your Spare Hours Into Money!

Earn big profits, prizes, and awards selling RADIO NEWS SCI-ENCE & INVENTION, THE EXPERIMENTER, and MOTOR CAMPER & TOURIST in your neighborhood. We train you as our salesman and pay you liberally for your time. Write at once and we will help you to get started. M. BRIDWELL

THE EXPERIMENTER PUBLISHING CO.

53 Park Place, New York, N. Y.

The best part of it was missed. Two or three times he started to finish. No one paid any attention to him It was not until Izzy jerked at his coattails, almost pulling him off the platform, that he finally came to himself again. Once down on the ground and listening to Izzy's

explanation he was again the swift-thinking managing editor. The victory of science was secondary to a good story.

Izzy explained: "Taylor, a cub on the Argus did it," he said. The cub intended to put his first regular morning edition in

the plane, not knowing that the Argus editor, mad as a hornet, thinking that the whole thing would be a flop, had had the special article written telling about the failure of the plane set up, and a special run of the r made.

paper made.

He was following the regular newspaper custom of telling about an event before it happened, keeping the specially printed copies in the office until the news was flashed, then turning the papers out for circulation. The Argus had them on trucks all the time the Prime had them on trucks all the time the plane was in flight, waiting for official word that the plane had failed, which of course it didn't, and which of course caused the joke on them. They took 'em off the trucks as soon as the plane landed. They had a special special course of the plane landed.

cial reporter here.
"Micky heard one of the Argus men-Taylor's boss at the Holden office-talking about it while the plane was in the air and he sent me a message just as you were open-ing the bundle. I had to wait a second to get myself organized before I jumped on the platform.


"Serves the old fossil right," cut in the Old Man. "Hurry back to Holden fast as you can and write a page one, line story on this business and be sure you tell the Argus story. Say that such procedure is often done in prize fights and the Kentucky derby-the extra copies-but say, and be sarcastic, that the result always happens in such case. And tell the Argus staff to train their cubs. Don't mention his name in the story, though. Now git!" And Izzy got.

Ham Co-operation-Is It Dead? (Continued from page 450)

The A. R. R. L. may be likened to the national government of this country, wherein the district councils would correspond to the states and the separate clubs to the cities. Amateur radio is due for one grand explosion if the separate clubs persist in their short-sighted methods. The district councils are just as necessary for the promotion of amateur radio activities as the states of the Union are for the self-government of the people. If the amateurs cannot be represented in this way, they will never be rea resented at all. One point that proves this is the activity of the Second District Coun-cil representative at Washington at the time the White bill was under consideration. Thousands of letters from individual hams could never have exerted the pressure that

necessary at all, inasmuch as legislators did not concern themselves particularly with the amateur. Today, however, with the millions of broadcast listeners throughout the country, many of whom misunderstand the amateur and his activities, representation for the ham is a crying need. If we do not have it, we shall soon go the way of the dodo, and ham radio will be as extinct as that bird. If in every district

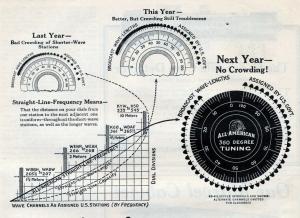the personal appearance of this one repre-sentative accomplished. In the future, the mateur is going to need representation of this type more than ever. Years ago it





LL-AMERICAN STRAIGHT-LINE-FREQUENCY

UNING

All-American Straight-Line

Frequency Condensers pe C-35 Max. 350 micromicro arads (Min. 10.5 mmf.).... pe C-50 Max. 500 micromicro arads (Min. 11.8 mmf.)

All-American Toroid Coils Type T-1 Antenna Coupler \$3.50 Type T-2 R.F. Transformer 3.50 Set of 3 Coils complete . . 10.50



Ease and certainty in tuning - no more crowding of shortwave stations-no need to buy vernier dials-no gears or other back-lash makers-body capacity absolutely not distinguishable - electrical efficiency unsurpassed - on one-half the panel space: that is the ALL-AMERICAN Straight-Line-Frequency Condensers.

New power for distance reception through close coupling -tuning of arrow-like sharpness-elimination of all oscillation worries through the self-enclosed endless magnetic field - non-radiating reception: that is ALL-AMERICAN Toroid Coils - Antenna Coupler and Radio Frequency Transformers. See them at your dealer's.

A new edition of the famous RADIO KEY BOOK, together with complete information about the new ALL-AMERICAN Straight-Line-Frequency TUNING, is yours for 10 cents, coin or stamps. Send for it today sure!

ALL-AMERICANRADIO CORPORATION, E. N. Rauland, President, 4207 Belmont Ave., CHICAGO

OWNING AND OPERATING STATION WENR-266 METERS MERICAN Pioneers in the Radio Industry



The G. & S. Silk Core Detector

A Greatly Improved Crystal Detector

TO give this detector a thorough and gruelling tests, we sent samples to the leading testing laboratories of the United States. We asked the engineers out or buff the G. & S. Silk Core Detector. NOT ONE WAS ABLE TO HURT IT! They reported it to be unscalled in volume, tone and selections of the sent of the

heat expansion and provides a greater capacity and larger surface for picking up the waves.

Money Back Guarantee
Try the G. & S. Silk Core Detector at
our risk. If not satisfied, return it and
your purchase price will cheerfully be
refunded. Sent C. O. D. or on receipt

of money order for \$1.50. DEALERS WRITE

1269 Cochran Avenue

tinsel, which allows more DEALERS WRITE

G. & S. RESEARCH LABORATORY

: : Los Angeles, Calif.

Our Marvel Cabinet



See our other Styles. 9 styles for 14 sizes of panels

If you want to see the prettiest line of radio cabinets at "Factory to User" prices send for 1925 catalog

UTILITY CABINET CO.

'PHONE 721

WAUKESHA, WIS.

Any Radio Map a Month Old Is OUTOF DATE Unless it has a monthly supplementary service THE AIR-LINE RADIO MAP AND LOOP THE AIR-LINE RADIO MAP AND LOOP THE MAP AND LOOP T

sable mile-scale. Lists stations by call letters and waletribs. LOG shors location; difference in time; pownecers and killecycle; Spaces to list dial settings; thiheard; distance and signal strencts. Wheeler you o outdoor aerial or loop; direction of loop; phises or lopositer. It enables you to have a complete and individual Log for Every Station

PRICE 50 CENTS
At your dealers, or sent pertbald. Dealers and Jabber
With at once.
MULTIVIDER COMPANY, Asnows City, Misson

FAHNESTOCK CLIPS "Popular Wherever Rodio Is Used."

PRESS
DOWN
HERE
nestors are used by
nestors are
nestors ar

"THE IDEAL CONNECTOR"

FAHNESTOCK ELECTRIC COMPANY
Long Island City, New York

there should be organized an efficient and active district council, and if every club would belong to that council and have a voice in the doings of it, amateur radio would be far befter off. Organizations of this type are an absolute necessity, so let's have

This phase of amateur radio is just another instance of the lack of co-operation among us. Can we not do something about it and get ham activities on an organized basis, where everyone will co-operate and pull together for our mutual benefit?

For our own protection and for the advancement of han radio in general, we must organize! The time is coming when we shall need this protection. Broadcast promoters are casting longing eyes at the upper ham band between 150 and 200 meters. If we want to keep this good old space in the ether, we may have to fight for it, and to fight we need organization and co-operation. Let's get it now and keep it!

Now that we have considered two cases of more or less personal co-operation, let us for a moment consider the type of comus for a moment consider the type of com-munications that we bear over the air every night. Listen in at any time and you will probably hear something like this. "9XXX, 9XXX, 9XXX u 2YYY, 2YYY." This will be repeated for about ten minutes and then possibly 9XXX will respond, asking 2YYY if there is anything doing. Nine hundred and ninety-nine times out of a thousand the 2 station will come back with some-thing like this: "No OM. Nil hr. QSB? QSA?" The ninth district station will then give him the desired information, whereupon the 2 will probably come back with: "Tks OM Cul 73 Gn," And if you listen in on that same 2 station for a while, you will probably hear him go through the same process half a dozen times or more. sort of thing helping ham radio at all? De-cidedly not. It is permissible for an operator after retuning his apparatus, to call body to get a report on his note and other characteristics of his wave. But why must this be done a dozen times a night and every night, week in and week out? And then again we have the CO hound. His sole mission in life seems to be to raise DX and, incidentally, hell in general, among the amateur wave bands. Does this seem to be co-operation, particularly when a man will sit down at the key and pound off a continuous CQ for ten minutes at a time with-out even signing? The rules call for three COs and three signs repeated three times and then followed by a period of listen-ing. If this procedure were followed by everyone, there would be less jamming on the air and more room for those few loyal hams who actually try to handle some traffic. Two things are the backbone of the ama-

teur organization and are the only reasons for its existence. They are experimental work of a constructive nature and the handling of traffic. Those amazeur stations who do not accomplish either of these feats stations of other owners and do not contribute anything toward the advancement of radio, as applied particularly to the ham. So let us all try to get together and do the following things. They will help greatly bound for-

First, promote personal co-operation among nearby hams, by assisting each other whenever possible and necessary.

Second, promote good feeling between the local clubs and the district council and the A. R. R. L. You will have to do this if you want to keep ham radio going.

Third, promote co-operation on the air. Eliminate the interminable CQ hound and the "Nil hir OM" type of operator who never seems to have any traffic to start or to relay. The more hams that handle traffic, the more ham radio in general will be keet

You Don't Need a New Set

You Don't Need Straight Line Frequency Condensers

All You Need Is the New

Gets Straight Line Trequency Results from May Type Condenser

If your set dissatisfies you because it is no longer selective— If it fails to bring low

wave stations—
If it crowds many sta-

tions between 0 and 50—

And "gets" very little between 50 and 100—

If it requires nerveracking, hair - trigging tuning—

Then you need SLF Dials!

\$350 Each
Gold or Silver Face

Radio Fans

S L F Dials are being stocked by America's Best Retailers with vision to see the waiting market.

Dealers and Jobbers write or wire for details

ordinary vernier dial. S. L. F. works
on an entirely different
principle.

SLF Dials should not be confused with the

Patented VARIABLE DRIVE makes for sharper tuning and better dinance. Syreading of status spreems for the status spreems of the statu

There are ONLY Two Ways to Bring a Set Up-to-Date!

1--The Expensive and Impractical Way Rewire entire set and replace old condensers with costly straight line frequency type.

2-- The Inexpensive and Simple

Just remove old dials and replace with the Marvelous S.L.F. Dials.

BIG THREE RADIO CORP'N

16-22 HUDSON ST., NEW YORK, N.Y.

532

AT LAST YOU CAN TELL WHAT YOUR TUBES WILL DO

SUPERADIO VACUUM TUBE DYNOMETER

HIS revolutionary Meter measures easily, with positive accuracy, the power of any vacuum tube on the market. No more do you have to buy a "pig in the poke." Now, you can get that "best" audio or radio frequency amplifier or that "right" detector tube. And you can always duplicate bes when it comes to renewals. Insist on TESTED TURES

Every Set or Tube Manufacturer, every Jobber and Dealer will want this necessary Meter. Reliable Representatives wanted. Write for details.

SUPERADIO KIT \$17.50

Here is the ideal Kit to build, the new Super-heterodyne. Marvelous results. Contains I An-tenna Coupler, I Succeeding of Special Herman Coupler, I Special Special Special Special Special Special Matched Intermediate Transformers and all mecessary hardware with diagrams, Iayouts and complete Super-heterodyne Treatise by Louis C. Billotte. Write today for information.



DE WITT LA FRANCE CO., INC. 54 Washburn Avenue, Cambridge, Mass

Boston Representative
MARTIN, HARTLEY & FOSS, 99 Bedford St. WILLIAM A. WELTY & CO., 36 So. State St.



Standard Tipe shown below will run on the A CORD TIP that requires no solder, no wrap-ping of the insulation and no tools other than a pen knife and a small screw driver. Any-one can attach it quickly and have a factory finish. The internal thread of the Universal Sleeve "A" draws inside all loose ends of insulation.

The Wood screw "B" inserts in the wire core of the cord until the head seats (see B-2) making an excellent electrical contact. This screw also wedges the cord out into the internal thread of "A" making a firm mechanical joint.

All parts are of brass, nickel plated.

Nº 632 PRICETIO

(DIN Expose to of here wire, broom word ware "B" looking wire to See our Bulletin No. 36 at your Dealers. If he hasn't his copy, we have one for him The Barkelew Electric Mfg. Co. 1700 Middletown, Ohio, U. S. A. turns on any of our mand-ers Grap Tops shown at left

WIRFLESS COURSE

LESSON

by Universal Sience "A" his an

B C

DIN CO

Let's go!

The Standard Radio Text Book

12th EDITION

264 Pages of Radio-500 Illustrations. Size 6 x 9 Inches-DeLuxe Binding. Genuine Gold Stamped-Round Corners.

PRICE \$2.00

Experimenter Publishing Co., Inc. New York, N. Y. 53 Park Place

before the public and the greater will be

the benefit to those most interested.

In experimental work more than in any other phase of the ham game does co operation become necessary. we be if there were not an exchange of ideas between us? The development of the short wave bands, for instance, would not be pro-gressing with the speed that it is if a few of the more enlightened and ambitious did not go a little out of their way to provide their ham brothers with the results of their work. Would that more of the hams were of this type! Sometimes it is as hard as pulling teeth to get information from a ham. And then he is usually not sure of his stuff. He has probably followed in someone else's footsteps and so, of course, has only a superficial knowledge of what he is discussing. Let's get away from this sort of stuff, fellows. It only retards the game. Study radio so that you have at least a basis to work on. Then get away from the beaten track and try to do something original. Better still, bring co-operation into play and get together with one or two other hams and conduct experimental work. You will soon find that the results of pooling your thoughts will be much better in the long run than individual work could ever be. And then, try to help others who may not know as much as you do. Show them the right way to go about doing the things that they are trying to accom-plish, rather than look down on them just because they do not know as much about radio as you do. Remember, we all had to start somewhere; not one of us was born with a full knowledge of radio. By letting the other fellow in on what you know, you will experience that feeling that comes from

A New Super-Heterodyne (Continued from page 445)

doing a good deed and, at the same time,

adjustment where a "plunk" is heard as turned to the right or negative side. it is properly adjusted, no squeals at all will be heard—when improperly adjusted, many will be heard. Reference to the tuning chart will show approximately how the dials should be set for different wavelengths.



Fig. 2. The autodyne frequency charger, part of the circuit which oscillates at one frequency and detects at another.

Balancing is done by first setting both small condensers all the way in. Then, as the tuning dials are rotated, clicks will be heard. If one of the balancing condensers is turned out, a point will be found where no clicks can be heard. The condenser conno cheeks can be heard. The condenser con-nected from grid to filament will generally have a low setting, while the other balanc-ing condenser will be all the way in. Once the receiver has been balanced, it should be tuned for several days and then gradually

COMPARE! KENMAN 5—MODEL 1926

Since 1913, twelve years, we have been manufacturing the finest grades of radio apparatus. This is the reason why you, as a discriminating radio buyer, should prefer the Kenman 5 Receiver.

the reason why you, as a discriminating radio buyer, should prefer the Acmian 3 Accevers.

For arthitic design ... See it.
For the fine quality of its engineering ... Examine it.
For Power, selectivity, and distance ... Try it.

Then for price, with any other 5-tube set-Compare it

For clearness without howls, squeals or distortion

Compare the Kenman 5 1926 model with any 5-tube receiver at any price. Under equal conditions, its performance will compare with or excel any receiver of its kind on the market. You can pay more but you cannot buy more.

Your Money Back If Not Satisfied

Any Kenman dealer will be glad to demonstrate the exceptional properties of this receiver without any obligation on your part, or if your dealer cannot supply you we will ship you direct on receipt of price with a full money back guarantee if you are not satisfied.

Features of the Kenman Re-

Gremins Westinghouse Bakeitie throughouse Bakeitie throughouse Bakeitie throughouse Condensers, allow the Condensers, allow the Condensers, and with the high standard we have set. The cabe work of art, not alone work of the Condensers of the Cond

tortion. Rheostats con trol voltage and vol ume, also filament con trol jack for phone use



Dealers Needed to Distribute Sets Already Sold

We have on hand many customer orders for which dealers will be required for distribution. Write for complete details and terms. *29 75
"A little buys
a lot"

Hear it.

KENMAN ELECTRIC CO. Inc., 296 Broadway, New York, N. Y.

Radio Manufacturers Since 19



and Others.

Furnished to manufacturers, completely engraved and machined, ready for use.





RANDOLPH & CO., Dept. 459 Washington, D. C.

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, New York City.

unbalanced by adjusting one of the con-densers (CX). If this is done on a weak station, an increase in signal strength will be noticed. If the set is too far unbalanced, however, the selectivity will suffer.

CONSTRUCTION The practical construction of a receiver embodying the super-autodyne circuit, with either a balanced or slightly unbalanced bridge circuit, is extremely simple and will readily be understood by reference to the various photos and diagrams accompanying this article. The actual list of parts necessary is given below. They may be of standard manufacture, but should be carefully selected to conform with the general specifications, since for the design illustrated the electrical and mechanical requirements

| 2 (C1, C2) | .0005 condensers. 4-inch moulded dia |
|--------------------------|--|
| 1 (R4) | vernier type pr ferably. 6-ohm rheostat. |
| | eter. Insulated top bin |
| 1 (R3) 3 (B1, B2, B3) | 240-ohm po |

1 (C5, 211)

2 (210, 210)

2 (T1, T2)

2 (C7, C8)

2 (C3, C4)

2 (C9, C10)

2 (Cx. CX)

1 (C6)

1 (R1)

29

1 (L1, L2, L3)

Insulated top binding posts. 1-spring jack

60 K.C. filter with matched tuning 60 K.C. matched in-termediate trans-

formers. Coupling unit 6 gang 199 or 201A socket shelf.

31/6:1 audio transformers. .5 mfd. by-pass con-

.00025 mica condensers with leak .002 mica conden-

.0075 mica condensers. .000025 balancing

condensers. 5- or .5-megohm leak.

2-megohm leak. On-off switch. S.P.S.T. switch 5-lead color cable. Pair shelf brackets. Panel 7x18x1/8 in. 6/32 R.H.N.P. 34-inch machine

6/32 R.H.N.P. 11/2inch machin

6/32 N. P. nuts. length spaghetti lengths bus-bar. soldering lugs.

Tools required: 1 hand-drill with drills and countersink; 1 soldering iron with resincore solder and non-corrosive paste; I sidecutting pliers; I screw-driver, hammer and centerpunch.

As soon as the material has been procured, each item should be carefully examined to see that all screws and nuts are tight, and lugs placed as shown in the photographs, so that those on the various instruments will point in the best directions for short leads. Socker springs should be bent up to make good contact with the tube Condenser bearings should be adusted to give the desired tension.

The front panel may be laid out with the



A Super Pattern for Super-Heterodyne Set Builders

The simplest, greatest and most revo-lutionary Radio Pattern ever designed The complete super-heterodyne a Ine competee super-neteroayne as shown above can be built with this pattern by anyone. The secret of the marvelous simplicity is the gigantic blueprints that are drawn the full size of the super-heterodyne itself. The blueprint of the picing diese. blueprint of the niring diagram measuring 19½" x 44" is drawn by a master radio engineer, every conceinable measurement is given right on the pattern so that you need not the pattern so that y

measure a single wire.
The price of the complete pattern comprising two blueprints, size 1915, x 44", and a 16 page booklet size 8' x 12" and enclosed in an extra heavy cardbeard box printed handsomely it two colors is only \$1.00.

Here is the most wonderful opportu-nity for every radio amateur to have the finest set yet designed for radio GET YOUR ORDER IN EARLY OR SEE YOUR DEALER TODAY



PRICE \$1.00 At All Radio or News Dealers

The Consrad Company, Inc. 233 Fulton St., New York City







The Greatest Condenser value in the world

COVERS 200 to 600 Meters

This new PILOT Straight-line FREQUENCY Condenser is presented only in the universallyrecommended 13-plate model (.0003 maximum capacity), as specified by all authorities for use all tuned radio frequency circuits. The PILOT Condenser is superior to similar condensers being offered at many times the price.

"UNCROWDS" THE DIAL

CY Condenser.

PILOT Straight-line FREQUENCY Condensers spread the stations evenly over your dial, eliminating the present congestion in the lower wave-lengths, making it easy to tune in DX (i.e.: KDKA at 53 instead of at 17). It will pay you to replace your present condensers

Rigid, accurate, precise construction.

Extra - heavy plates, .032 inches thick. Genuine bakelite in-

sulation. Pierced end-plates to minimize eddy cur-

rents. Braced rotor - plates prevent shorting. Low loss, minimum insulation.

MADE, BOUGHT, SOLD IN VOLUME

Quantity production in America's greatest Radio Parts factory, plus direct mass purchases by the ensurances S. S. Kreuge Co.'s nation-wide organiza-makes possible the production of this finest-pull-Straight-line FREQUENCY condenser to retail at PILOT Straight-line FREQUENCY condenser to retail at PILOT Straight-line FREQUENCY condenser is being used as standard equipment by a large number of manufacturers of high-grade radio receivers.

PILOT PARTS USED EVERYWHERE

Manufacturers, amateurs and experimenters every-where are using PILOT Radio parts. They have learned it is not necessary to pay more for perfect performance. PILOT parts are superior because they are designed by leading engineers and built by ex-perts. PILOT parts are low in price because PILOT produces more parts than any other Radio manufac-ture parts than any other Radio manufac-

ON SALE AT ALL S.S.KRESGE CO. STORES



This new PILOT Straight-line FREQUENCY Condenser can be purchased complete for \$1.00 at any S. S. KRESGE CO. store. Or if no Kresge store is convenient send \$1.00, plus ten cents postage, for each condenser ordered in cash or Money Order direct to

PILOT ELECTRIC MFG. CO., Inc. 323 Berry Street

Brooklyn, N.Y.

PILOT PARTS for PERFECT

Made By America's Greatest Radio Parts Manufacturer

Do You Need More Money?



A busy Pennsylvanian who increases his income regularly every month through spare-time, money-making plan.

Sell Us Your Spare Time At a Big Profit!

HOUSANDS of busy men and women in all sections of the country are turning their spare time into money-easily earning from \$5 to \$25 a week through our practical money-making plan. What they are doing, you can do

No experience or investment is necessary, Age, education or where you live does not matter. All you need do is take orders for renewal and new subscriptions to our four popular magazines-Radio News, Science and Invention. The Experimenter, and Motor Camper & Tourist.

We furnish all supplies and instructions absolutely free. You begin earning money just as soon as you start. All particulars will be sent you immediately on receipt of the coupon below. Simply fill in your name and address, clip out and

---- Mail To-day ----

E. J. Foley, Box R-10, Experimenter Publishing Co

53 Park Place, New York City. Please send me immediately, without obligation, full particulars about your spare-time, money-making plan.

Name Address City..... State..... aid of a rule and scriber, after which the hole locations should be punched with a center-punch or nail, and a hammer. After drilling the holes, the panel may be grained with fine sand-paper and oil, rubbing in one



INTERMEDIATE TRANSFORMER. 36 SSE WIFE WHOE . B' , OUTSIDE . PLATE" WEIGHT, OUTSTON - TERIO



CORE 007 SILICON STEEL I PIECE AS SHOWN . I PIECE WITHOUT CENTER PROJECTION MOUNT WITH PROJECTION UNDER PRIMITY COL IMPREGNATE IN FOSIN REESWAY COMBILINO



FILTER "36 DSC WIRE INSIDE -'B' OUTSIDE - PLATE SECONDARY ISON TURNS . 36 DSC WIRE INSIDE-A", OUTSIDE-"GRID" PAPREGNATE IN ROSIN-PAFEMAN

Fig. 3. Details of intermediate frequency trans-formers and filter.

direction until the original polished finish direction until the original polished hinsh has disappeared. After wiping the panel off with alcohol, indicating marks for the dials may be scratched as in Fig. 1 and filled with Chinese white. The sub-panel should not be grained.

Correspondence from Readers

(Continued from page 462)

would be some excuse if the British apparatus was not so efficient. However, this is not the case. We in England were able to profit by American experience when we took up broadcasting on the other side just about two years ago.

about two years ago.

I saw one and one-half years of broad-casting in England before coming to this country and I have done my share of listen-ing-in over here during the last eight months. Most of my listening in England was done from a spot some twenty-five miles out of London while here, as you will see, I am a little closer to the locals. In England I made it a point not to use more than two tubes for DX work, a straightforward radio frequency and detector circuit. Here I am using four tubes at present. There was nothing special about my circuit over there, and it was long before the low-loss craze was the vogue. The radio frequency coupling was of the tuned plate type, the tickler of the R-F tube. My aerial was about 100 feet in length, 25 feet high and my house

in a valley—the Thames valley.

In spite of the low aerial and the fact that I was using only two tubes, I managed to log KDKA, WGR and WMAS (the latto log KDKA, WGR and WMAS (the lat-ter at Dartmouth, Mass. I may have the call wrong) in—if I remember correctly— October, 1923. Reception of these stations was verified. This speaks very well of the broadcasting but without question the appa-ratus at the receiving end must necessarily have been pretty efficient to receive at this

Hundreds of amateurs on the other sidefans, you would call them-have received American stations on only one tube during



Test accurately and safely

There's no substitute for high resistance in a voltmeter for testing radio batteries, tube voltage, or experimental work. 60 ohms per volt is the Nagel standard, assuring accurate readings and safety against battery drainage under touch contact or continuous service. your dealer or write The W. G. Nagel Electric Co., 512 Hamilton Street, Toledo, Ohio.

If you own a "Super-Het" you can test your "A" and "B" batteries with one in-

RY CELL TESTERS AMMETERS IGH-RESISTANCE VOLTMETERS VOLTAMMETERS · BAKELITE HOT MOULDED INSULATIONS

GET A Handy Binder

for your RADIO NEWS

Holds and preserves six issues, each of which can be inserted or removed at will.

Price 65c. EXPERIMENTER PUBLISHING CO., Inc.,

BOOK DEPT 53 Park Place, New York



Ouick Shipment Transportation Paid

Lowest Prices

Revolutionary Method to "Build Your Own"



SHALL WE SEND YOU ALSO New 1925 "Rasco" Catalog No. 12

This Free Book Tells

DON'T EVEN THINK OF BUYING A SET OR KIT BEFORE YOU SEE OUR KIT CATALOG

Book explains what you want to know

"No Sod et

RADIO SPECIALTY CO.



Used by the United States Navy and Signal Corps for over nine years. Dilecto is the strongest, safest radio panel that can be made. Look for the identifying "Red Stripe" that sets apart Dilecto from its

THE CONTINENTAL FIBRE CO. FACTORY: NEWARK, DELAWARE Service on Dilecto, also Contex, Conite, and Vulcanized Fibre, from:

NEW YORK SAN FRANCISCO
220 Park Ave. To Fressat St.
CHICAGO Bids.
Farmers Bank Bidg. 207 So. Hill St. Offices and Agents Throughout the World



Y. M. C. A. Radio Institute Courses in Radio Operating and Radio Construction. Expert In-structors-Thorough Courses. Employment Service, Dormitories-Restaurant-Club Privileges

Write for booklet "Opportunities in Radio" 158 East 86th Street, New York City

CLASS 25¢PINS CATALOG FREE VICTOR BASTIAN BROS. CO.

the past winter. Both broadcaster and receiver must be pretty good to accomplish

this. Some pretty good crystal records have been made over there, too, which all points "efficient transmitting gear." to "efficient transmitting gear.

Mr. Howe overlooks the fact that conditions on both sides of the Atlantic may differ, although it may be the same day of

the week. The fact that he sailed down the middle of the Atlantic and received American stations and not British stations proves nothing. I have at times received WGR in England better than Berlin. On occasion I have sat up and listened to American transmissions for hours, but in attempting to do so on the following evening, have failed to detect even a faint carrier wave, although apparently atmospheric conditions were O.K. WBZ has been heard in London every day for a week this last winter and on the fol-lowing week another American station al-

together would come in well, to the total ex-clusion of WBZ. There are too many unknowns in radio vet to criticize one another's apparatus by individual results. apparatus by individual results.

Some weeks ago the R. C. A. relayed 5XX about five times better than I ever heard KDKA relayed in London. That—if I took Mr. Howe's attitude—would prove that 5XX and that Apparatus the SXXX.

is better than KDKA and that American receiving apparatus is not consistently satis-factory because it failed to get 5XX the following week. But instead—I think that it was the finest piece of radio work ever accomplished. It required the best of apparatus and operators at both ends.

When I came over here I brought British tubes with me and these I used until they

one day came to an untimely end. I sub-stituted them for American tubes and have noticed not the slightest difference. As I said above, I am using a four-tube set. My aerial is 200 feet in height-not badly screened, but I have failed in eight months to get out further than Dallas, Tex. I don't blame American apparatus—it is fine, the same as is the British—but I blame local conditions which cannot be helped. Mr. Howe may be interested to know that

I spent eighteen months answering on an average 2,000 questions a week addressed to the radio publication for which I was working and no charge whatever-not even postage-was made for this service. The American method of mounting the

tubes and so forth on a baseboard behind the panel is rapidly spreading over on the other side. We must all live and learn, Mr. Howe's remarks re the British tube socket -which I'll admit I don't care for as much as the American socket-are grossly exaggerated and only the clumsiest person would burn out his filament when inserting the tube, People often judge from their own experi-He adds, or rather gives the impression,

that a good pair of phones sell for \$15. I paid \$2 for a very good pair before leaving London

American radio fans are probably advanced technically than their advanced technically than their British brothers—taken as a whole, that is, owing to the fact that they have had two years more experience at the job. Very few ama-teurs in England use more than four tubes and the super-heterodyne is hardly ever seen on the other side.

I hope that these few remarks will in-

I hope that the terest you-Mr. Howe.
L. W. CORBETT,

N. Y. Representative, Popular Wireless. 106 West 81st St., N. Y. C.

IT IS, AT THAT! what is meant by three stages of

"Oh, that's when your mother and two of her neighbors get together."

Contributed by William A. Heitler.

ORCHESTRION De Luxe

WONDERFUL REPRODUCTION! rediscrited in Level is a sareth suised instrument for wear the sareth suised instrument to wear the sareth sareth

RADIO CABINET COMPANY

2123 Olney Street Indianapolis, Indiana
Radio News Laboratories Certificate et Merit No. 370

What Your Father Should Know

If Your Father Is 40 Years or More of Age. You Should Call His Attention Immediately to This Important Message Which Will Help Him to Live Longer and Happier

Was Help Him to Live Longer and Happier Man. As a route as setting of 100, 107 of distinct to 100, 107 of the control of 100, 107 of the control of 100, 107 of the control of 100, 100 of

The "Windham" Wire Former

A Handy Tool for Electricians, Radio Fans and Mechanics This rugged little t

not only makes accurate loops or eyes for No. 4, 6, 8 and 10 screws but will make either sharp or easy radius right angle bends and the sharp cut-ter will cut the toughest wire as well. It is drop forged of the very best steel and care-fully tempered in oil. Retails for \$1.25. Dealers and Jobbers send for full information. Desirable ter-

THE GOYER COMPANY

Willimantic, Conn.



BURIED TREASURE can still be found in



Good Chemists Command High Salaries

CHEMISTRY



and you can make yourself independent for life by unearthing one of chemistry's vet undiscovered secrets.

Do you remember how the tales of pirate gold used to fire your imagination and make you want to sail the uncharted seas in search of treasure and adventure? And then you would regret that such things were no longer done. But that is a mistake. They are done-today and everyday-not on desert islands, but in the chemical laboratories throughout desert islands, but in the chemical lanoratories intrugious your own country. Quietly, systematically, the chemist works. His work is difficult, but more adventurous than the blood-curdling decid of the Spanish Main. Instead of meeting an early and violent death on some forgotten shore, he gathers would be able to the contributions to however the contributions to have the contribution of the contribution of the contribution of the contributions. weath and honor through his invaluable contributions to humanity. Alfred Nobel, the Swedish chemist who invented dynamite, made so many millions that the income alone from his bequests provides five \$40,000 prizes every year for the advancement of science and peace, C. M. Hall, the chemist who discovered how to manufacture aluminum made millions who discovered how to manufacture aluminum made millions. who discovered how to manufacture aluminum made millions through this discovery. F. G. Cottrell, who devised a valu-able process for recovering the waste from flue gases, James Gayley, who showed how to save enormous losses in steel manufacture, L. H. Baekeland, who invented Bakelite—these are only a few of the men to whom fortunes have come through their chemical achievements.



I have not written since I received the big et. I can still say that it far exceeded my nticipations. Since I have been studying with



Experimental Equipment Furnished to Every Student

CHEMICAL INSTITUTE OF NEW YORK, Inc.

66-R-WEST BROADWAY NEW YORK CITY

Now Is the Time to Study Chemistry

You Can Learn at Home

Easy Monthly Payments

Special 30 Day Offer

DON'T WAIT-MAIL COUPON NOW!

INSTITUTE OF NEW YORK



Charges all Storage Batteries Quickly, Quietly, Safely

The New TWIN BULB

Chargers as well as other radio equip ment have been improved. That is why we have the New Twin Bulb Handy Charger. It is the last word in battery chargers. Regardless of make or voltage it will charge your "A" and "B" Stor-age Batteries at a fast rate and without the slightest noise. The Twin Bulb Charger cannot discharge or overcharge our battery, therefore it is particularly adaptable to overnight charging.

The "push-pall" method of charging is employed by this new Twin Bulb HANDY, using both halves of the AC wave. This advanced principle accounts for the fast rate of charge. See your near-tradio dealer about this new charger.

INTERSTATE ELECTRIC CO. 4341 DUNCAN AVE. . . ST. LOUIS

SAUE \$1000

\$35 to \$50 a Week

After short course in RADIO. LI-CENSES a specialty. Instruction in all branches. FALL term begins SEPT. 14th. Positions secured for graduates. Send for free Sample Code Lessons. Scholarships for a few lucky ones, catalogue and full details from

MASS, RADIO SCHOOL

18 Boylston Street Boston, Mass.

your copy reaching you each month, to RADIO NEWS - \$2.50 a year, ster Publishing Co., 53 Park Place,

The Vacuum Tube and Photo-Electric Cell (Continued from page 427)

duced (as in the case of slight illumination of the cell), this dissipation may, on the charge.

In these circuits the insulation of all parts play an important rôle. In particular, if the exterior grid of the two-grid tube is not perfectly insulated, a time will be reached when the quantity of electricity so lost will equal the quantity of electricity carried by the photo-electric current. The potential adjusts itself to a value corresponding to this state of equilibrium, and from this results a limitation of the system. well insulated tube, a condition could be established in which, during the instant following illumination, the maximum current produced by positive ions arriving at the exterior grid is of the order of 10-13 ampere. It is necessary to note that if the photo-electric current is only slightly greater than effective current is only stigntly greater total 10⁻¹³ amperes, the variations in potential of the outer grid are slow because of the capacity of this grid. This is also true of the variations of the inner grid current. The value of the current to be measured is therefore determined, not by the total variation of current between the inner grid and fila-ment (since this variation will be the same in all cases, the current reaching zero), but by the speed of variation of this current. One notes, for example, the variation of current during a time, t

Here are some brief indications of the applications to which this new device has been put. The realization of these applicabeen put. tions is due chiefly to Mr. Jouaust, for it after having taken an important part in establishing the basic principles.

It is of very great interest in astronomy and in geodesy to be able to register with very great precision the instant when a pendulum passes a particular position during each of its oscillations. Generally an elec-tric contact is employed for this purpose; a metal strip or a drop of mercury, with which the pendulum makes contact at each oscillation. Now a material contact, light as it may be, between the pendulum and another body, causes a disturbance in its oscil-lations. If it is a clock movement which closes the electric contact, experiments have shown that variations of about a hundredth a period are produced. By placing a small mirror on the rod of a pendulum, in such a manner that at each oscillation a luminous ray is reflected during an extreme ly short time onto the photo-electric cell connected, as has been described, to amplifiers, a graphic register of the photo-electric current is easily obtained by means of a recording instrument. A sudden indentation of the line drawn by the recording pen of the instrument is produced at each oscillation of the pendulum.

The first application of this device was made jointly by Colonel Perrier and Captain Schmerber, of the Geographic Service of the French Army, on a geodetic pendulum for the measurement of the gravitational constant. This application was communicated at a meeting of the International Geodetic and Geophysical Union in Madrid in 1924. Another application was made on a mas-ter pendulum at the International Time Bureau (Paris Observatory) situated in a shaft at a depth of 27 meters. Fig. 6 represents the optical arrangements of the stallation designed and constructed with the assistance of Mr. L. Joly. The cell and the amplifying devices could not be placed in the shaft because of dampness. It was necessary to arrange them at the top of the shaft.





X-L VARIO DENSERS FOR GREATER DISTANCE, VOLUME and CLARITY

ned and Used by the Foremost DEL N-Capacity range 1.8 to , for balance in Roberts two , McMurdo Silver's Knockout, X-L RADIO LABORATORIES





FIXED DETECTORS-ARE LOUD AND CLEAR.



THE KEYSTONE PRODUCTS CO.

Build Better Radio Sets with Ragemco Tools



SEND FOR THIS FREE TOOL CIRCULAR.

OU cannot do good work without the proper tools. We ship, direct to your door, any of our tools especially made for radio uses. Many of these tools are different from any you have ever seen.

Tools of Every Description for Every Conceivable Purpose

Long Sharp Nose Side Cutting Plier Side Cutting Nipper Combination Plier Wire Bending Tool Set of Three Screw Drivers Three-in-one Nut Wrench Screw Starter Driver Tool Users Book Scriber and Marker

Hollow Handle Tool Set "Yankee" Hand Drill "Hollow Handle" Hand Drill Circle Cutters Bench Vise Radio Drill Set Electric Soldering Iron

SAVE MONEY AND TIME

Send for our Special Tool Circular "A". You will be astonished at the remarkable tools we have for your work, that simplify set building, and you will be delighted at our low prices.

SAVE TIME AND

MONEY

Radio Tools of every description for every purpose

THE RADIOGEM CORPORATION, 66 W. Broadway, New York, N. Y.



Every Circuit a Separate Color

The new Consrad Patterns contain every pos-sible idea that will be of assistance to the user of these patterns while con-structing the receiver. The latest innovation is the printing of the wir-ing diagram on the new patterns in four colors; thus, GREEN for the Tuner-Oscillator circuit, YELLOW for the low potential wiring or "A" battery circuit, RED for the plate and "B" battery circuit and WHITE for the grid circuit.

The TROPADYNE

The Superadio—the Only Receiver with "Tunable" Intermediate **Transformers**

The new Tropadyne circuit is spreading like wildfire. Front pages of many radio magazines and newspapers are featuring this circuit. The secret of its tremendous popularity is in the TUNABLE Intermediate transformers called Tropaformers. Tropaformers enable you, after the set is built, to tune the intermediate transformers so that you have no worries about balance.

They take a big question mark out of your Super-Heterodyne.

Consrad is again right up to the minute by publishing in its usual complete form a pattern on the authentic Tropadyne circuit. This pattern contains two extra large sized blueprints (19 by 22 inches). The blueprint of the wiring diagram is printed in the latest Consrad method explained else-where on this page. With these blueprints comes a large 16-page booklet complete in every detail, fully illustrated and written in plain understandable English.

Altogether every modern aid toward making a radio diagram easy to understand and easy to follow is incorporated in this latest Consrad Pattern.

SOLD BY ALL RADIO AND NEWS DEALERS

PRICE 50c EACH Published and Distributed by

The Consrad Company, 233 Fulton St., New York, N. Y.

The

SUPER-HETERODYNE

USE THIS BLANK TO ORDER

Just elip out this coupon, check the patterns or books you want and mail it to us with full remittance.

The Constrad Co., Inc.

233 Fulton St., New York, N. Y.

Gentlemen: I have checked below the patterns and books I desire. Enclosed find \$....., the full price. Kindly send me the items checked postpaid.

rice. Kindly send me the items checked postpaid Consrad Patterns—50c each

No. 2. How to Make a Two-Stage Amplifier.
No. 4. How to Make a Reinartz Receiver.
No. 5. How to Make a Reflex Receiver.
No. 6. How to Make a Cockaday Receiver.
No. 7. How to Make a Neutrodyne Receiver.
No. 8. How to Make the Autoplex Receiver.

No. 8. How to Make the Autoplex Receiver.
No. 9. How to Make the S. T. 100 Receiver.
No. 10. How to Make the Ultradyne Receiver.
No. 11. How to Make a Five Tube Cockaday Receiver.

... No. 12. How to Make a Portable Receiver.
... No. 13. How to Make a Harkness Receiver.
... No. 14. How to Make the Original Genuine SuperHeterodyne. List \$1.00

Heterodyne. List \$1.00.

No. 15. How to Make a Low Loss Receiver.

No. 16. How to Make a Tropadyne Superadio.

A. Radio Map of the U. S. on Cloth.

B. 20 Radio Diagrams and Hook-ups. New Edition
C. All About Aerials and Their Construction.
D. Radio Amateurs Practical Design Data.

Radio Books-25c each

No. 1. Tips for the Radio Constructor. No. 2. How to Make Practical Radio Receivers.

No. 2. How to Make Practical Radio R No. 3. Radio Questions Answered. No. 4. Radio Frequency Amplification.

No. 5. Loud Talkers and How to Build Them. No. 6. How to Tune Your Radio Set. No. 7. One Hundred Radio Hook-ups, New Edition.

No. 8. All About Radio Parts.
No. 9. History and Operations of Vacuum Tubes.

. No. 10. The Neutrodyne and All About It.
. No. 11. How Radio is Received.

.. No. 12. How to Locate Troubles in Your Radio Set.


... No. 13. Reflex Radio Receivers. ... No. 14. The Super-Heterodyne Theory and Construc-

Special Books

Radio News Amateurs' Handibook. \$1.00
Radio Log Book 50
Wireless Course in 20 Lessons—Leather Binding 2.00
The Radio Instructor 1.00
The Radio Listeners' Guide & Call Book 51
The Radio Review, 35 the copy \$3.50 the year

Name

CityState.....

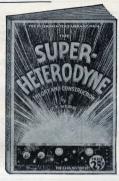

Here's the finest, most complete book of data and information ever compiled on the Standard Super-Heterodyne.

This is the big book of instruction and information on the various standard "supers" in common use today; a complete, up-to-the-minute, impartial 64-page book covering all the builder or user of this type of set might want to know. The Super-Heterodyne is written by a radio authority who to only his years of trade and practical experience but all the properties of the p

This is the very latest of the complete library of Experimenters Handbooks on radio, a list of which is printed on this page. These books are complete practical guides to almost every important phase of radio transmission and reception.

The famous Constad patterns are also listed on this coupon for your convenience. They are radio's finest patterns for the building of the most successful standard receivers.

You can get any of these books or patterns at your radio or news dealer or direct from us by using the coupon attached to this page.

The CONSRAD COMPANY

233 Fulton St. New York, N. Y.

L₁, L₂, L₃ and L₄ represent lenses, M and N, mirrors, D₁ and D₂, screens provided with narrow slits, F₁ and F₂. For the requirements of the International

Time Bureau which must compare the movements of six pendulums by means of hourly telegraphic signals transmitted by the Eiffel Tower station and by stations at Lyon, Bor-deaux, Saigon and Annapolis, U. S., etc., it is necessary to dispose the amplifying apparatus in such a manner that it is possible to record the illuminations due to the oscillations of the pendulum and to listen by teletions of the pendulum and to listen by tele-phone to the tick produced by the currents generated by these same rays of light. By this means it is possible to use the method this means it is possible to use the method comes necessary (Fig. 7). This arrange-ment presented no serious difficulty and the system was put into regular use at the end of January, 1925. Measures are being taken to verify, with a high degree of precision, the isochronian of the successive illuminations due to the pendulum.



All the timing instruments of the International Time Bureau will be provided with optical recording devices such as that described. Although the pendulums of these time-pieces sustain only the extremely small force of the spring maintaining the vibrating clock movement, it is certain that this force cook movement, it is certain that this force cannot be rigorously constant, and is the cause of little irregularities in the period of oscillations. We have therefore developed a pendulum in which the clock movement is eliminated and which consists simply of a pendulum on the rod of which is fixed a small mirror designed to train a small ray on the photo-electric cell. The current of this latter after amplification actuates an electromagnet which maintains the pendulum in vibration. The oscillations of the pendulum are therefore maintained without any material contact other than at its point of

In the case of the geodetic pendulum for the measurement of the gravitational constant, the amplified photo-electric current, which serves to record the oscillations of the pendulum, can be employed at the same time to actuate a small electric pendulum which serves to count the number of oscillations, as in the preceding device.

The astronomer, determining the time by means of a meridian telescope, observes the instant when a particular star passes the cross-hair of his telescope, and at each such instant closing an electric contact with his hand would send the current through the recording instrument (chronograph) on which, at the same time, the oscillations of the clock pendulum are recorded. There is evidently an interval between the instant when the star passes the cross hairs and the instant when the record is made on the chronograph. In addition, this interval is varia-This, then, is a source of serious error.

We have tried to record, by the action of the light of the star itself on a potassium cell, the instant when the star is eclipsed by the cross-hairs of the telescope. Interest-ing results have already been obtained with

Results and Prices never before achieved. -

SENSATIONAL NEW MODELS BY

\$3850 to \$15000

The Richardson Console



A beautiful mahogany console, artistically and unostentatiously constructed, that will enhance the appearance of any room.



Two-tone mahogany cabinet with sloping panel and enclosing loop for set,



\$75 with the 3-dial, 5-tube

\$95 with the 2-dial binocu-lar coils, 5-tube tuned radio frequency set.

\$150 with the 7-tube, 2-dial control, binocular coils, 3 stages of tuned radio frequency, detector, 3 stages of audio frequency amplification and self-contained loop set. (Neutralized by Boyd Phelps method)

Richardson Imperial

\$75 with the 2-dial control, binocular coils, 5-tube tuned radio frequency set.

125 with the 7-tube, 2lar coils, 3 stages of tuned radio frequency, detector, 3 stages of audio frequency amplification and self-contained loop set.

(Neutralized by Boyd Phelps method)



Sloping panel cabinet, mahogany finish shows same care and result of skill applied to all Richardson products

The Richardson Sophomore -a year ahead

\$38.50 A 5-tube, tuned radio frequency set with 3-dial control, rigidly constructed and wired with the famous Richardson "Can't go wrong" wiring system.

RICHARDSON RADIO INCORPORATED

LOS ANGELES PHILADELPHIA CLEVELAND Executive Office and Factory-128 University Place, New York City, N. Y.



Every Radio Fan Should Have This Book

Price Only

Elik E a little radio encyclepredia, this I.C.S. Radio
Handbook is packed with
Handbook is packed with
useful to everybody — from
useful to everybody — from
useful to everybody — from
useful to example to the
Elik pages
Pocket Size

Elik E a little radio encyclepredia price
Handbook is packed with
Han

mical diagram.

You may dip into it at random, or hunt up special information you want, or leaves to see the second to second to

Tenhatedly
P. B. DOAK
T. P. B. DOAK
T. P. B. DOAK
TOTS; electron tubes, etc.

Just mail the coupon with a doâte ball and you use 1. C. S. Radio Handbook by return mail. Note to other good books listed below and the low prices.

INTERNATIONAL CORRESPONDENCE SOMOOLS

22: 1 entering the property of the p

understood that if I am not entirely anticled a ground of the control of the cont

Get Boice Prices Before You Buy!

At the Works's largest outdoors or binan series of chires, boile offers greater values at lower prices up a positive seens-back guizantee. Whatever you be there's a Boiler-trans Broth Machine to do your work. Cit-time and Saway.

Lathes, Joint the Barry of the Barr

W. B. & J. E. Boice, Deat Toledo, O. To the Radio Dealer

Let us explain how you can make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade. EXPERIMENTER PUBLISHING CO. 53 Park Place : New York City brilliant stars (Vega) with a telescope of 28 centimeters diameter. The deflection of the recording instrument due to the passage of the stars has an amelinate in its obposed that the new devices under construction which are provided with more amplifiers and better electrical instalation will give countly good records with stars less brilliant than Vega.

Radio In Germany

Nauen and Königswusterhausen have expressed their appreciation at the quality of the equipment and the smooth working of



Fig. 3. A two-tube reflex that attracted great

It has been the special endeavor of the management of the Berliner Messe Am to make the exhibition in every respect a live affair, full of practical demonstrations—the whole process of broadcasting is shown in all details from the studio of the broadcast station to the home listener or the load speaker in a big hall.

MORE RADIO SHOWER PRIZES

The D. X. Instrument Company, whose invitation to participate in the RABIO NEWS Shower Party was unfortunately miscarried in the mail, announces at this time a contribution of twenty-four prizes to the Shower Party. These prizes, which will be distributed among the twelve zones, are twelve Fil-ko variable grid leaks and twelve Fil-ko resistors.

Radio Stereophony

LAWS OF ACOUSTICS

The physical has of acoustics were investigated some time ago. We will give a very brief caphantion and frave an example termine the positions of a ship on the ocean, wireless may be used. From two different position, Ago and the contract of the contraction of of the contractio





Conform to Bureau of Standards specifications for lowest losses. Automatic bearing take-up and rugged construction assure permanent alignment. All capacities—plain, vernier. Fully guaranteed.

Duplex Matched Condensers Afford Uniform Dial Settings

Or eliminate logging — Dial by call letters or wave lengths. Specially tested and guaranteed. Matched, packed and sealed, to remain unopened until used. Literature on request

Literature on request
DUPLEX CONDENSER & RADIO CORP.
52 Flatbush Ave. Extension, Brooklyn, N.Y.

Lack some of the refinements of the Duples Standard but are best at the price. Idealforportable sets. All capacities—plain and vernier.





Insure your copy reaching you each month Subscribe to RADIO NEWS-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

point in question and two different points, the distance between which is known; i. e., we construct a triangle similar to that referred to above, by means of which we can compute the unknown distance. Now we can imagine that every observation we make with our two eyes represents such a series of measurements. Each eye receives a cer-tain picture and automatically determines the angle its axis has to be turned to look the angle its axis has to be turned to look at a certain point. Then, a busy slide rule in our brains quickly computes the distance to that point by the aid of the triangle whose base is the line between the two eyes. and whose vortex is at the point under ob-servation. This computation never comes to consciousness; we are only aware of the final result: plastic seeing, i. e., we have an idea of depth in space, because we determine the distances by intuition, that is, we feel the perspective.

Our ears determine distances and directions in a similar way, but here three different phenomena are at work to form the impression of "plastic" hearing in the brain. First, there is an extremely small interval of time between the instance when the two ears receive the sound waves. For instance, if the sound comes directly from the left side, the left ear will receive it earlier than the right one, the right ear receiving the sound as much later as the sound requires to travel from the left to the right ear, a distance of approximately eight inches. That is, the velocity of sound is 1,090 feet per second. This time interval will be .66 foot (8 inches) divided by 1,090, or .0006 of a second. This difference in time represents the maximum and decreases if the source of the sound approaches a position directly in front of us. In this position, the distance of the source is the same from both ears.
As a matter of fact, in order to locate the origin of a sound, we always turn the head into such a position that both ears are equal-ly distant from the source.

Sound travels in waves, the length of which depends upon the pitch of the tone. Sup-pose we have a source of sound on the left side, then the left car at some instant might receive a wave at its maximum amplitude while the right ear, being eight inches more remote, might receive it at its minimum amplitude. This difference of phase offers a new method to the ear for determining distance and location of the source of sound, intensity, one ear will feel differences in intensity compared with the other ear, thus enabling the brain to get the impression of

plastic hearing. The photographic camera can be considered as a crudely constructed human eye. If we take a picture using two similar "eyes" of this simple model placed at a distance from each other corresponding to the distance of the human eyes, we get a stereoscopic picture. That is to say, we see a plastic or depth-effect in the picture because the camera "saw" the object under the same circumstances as the human eve would have

The microphone corresponds to the human r. Suppose we placed two microphones in ear. Suppose we placed two microphones in front of a sound-producer and at distances from each other corresponding to the dis-tance between the human ears. Receivers connected to this system of microphone will connected to this system of micropione wingive a "plastic" impression. This procedure is called Stereophony. In theory, it would therefore be best to place two distinct microphones at the proper distance from each other and at considerable distance away from the stage above the orchestra seats. This, of course, would be very inconvenient and the sound would necessarily need amplification at the receiving end, because one would be obliged to dampen the microphone in order to avoid an interfering echo

INSTALLATION AT THE OPERA HOUSE So they placed the following installation



Phonograph

Loud Speaker Unit Type A . . . \$4.00 Type B . . . 6.00



Mozart Radioceive Superior Headset Price \$5.00



Baby Grand Loud Speaker

Complete with Unit A \$9.00

Complete with Unit B \$12.00

TS extraordinary reproducing qualities, its low center of gravity with resultant steadiness, its general beauty of outline, and, the fact that it will harmonize perfectly with any furnishings from the simplest to the m o s t pretentious, have maintained for it a worthy place amongst all that is superlative in Radio necessities today.

Our Baby Grand "Appreciation" folder cheerfully mailed on request.

Miller AMPLIFYING HORNS 41 Different Models



The Proof of Quality and Service

Miller Amplifying Horns carry the seal of approval of this country's largest and finest radio manufacturers. These concerns use Miller Horns as standard equipment. Surely this fact is sufficient proof of Miller superiority.

No radio company that has built up a nation-wide reputation for making a product of high quality would risk that reputation by equipping their product with anything but the best. Such companies we fuller Horns and depend upon Miller to make deliveries according to their requirements. They know that our vast experience and tremendous production facilities have made it possible for us to offer amplifying horns of highest quality, at a competitive price. Write us today for complete information.

The Miller Rubber Co.

Akron of N. Y. Ohio



EVERYTHING IN RADIO
AT ATTRACTIVE PRICES
SETS OR PARTS
Mail order only
ALL RADIO COMPANY, 417 North Clark St., Chinge

in the Berlin Opera House: At the edits of the stage six microplones are placed as A, A, B, B, C, C, Three of these A, B and C are connected to one pair of wires and A, B, C, to another pair. From each pair of wires there is a cable leading to the receiver, where one supplies the receiver right ear. From each set there is a cable leading to the subscriber, each receiver of the pheadphone being connected to a separate

Whoever has an opportunity to hear this stereophonic transmission is arrayried by the effect. The sound seems much fuller and sharper in every detail. The different voices of a chorus become notably more distinguishable from each other and from the orchestra. The simple method of transmission can never produce these effects, just as a photo can never reproduce the perspective of a landscape.

DIFFICULTIES

However, we cannot overlook the difficulties of the stereophonic transmission. impossible to furnish every hearer with two separate cables going into his home. Such increase of wires would become an unbearable burden on the telephone system of a big city like Berlin. We see, however, that one city like bernit. We see, nowever, that there is a possibility of improving the radio service of today by using stereophonic trans-mission. The transmission is certainly posmission. The transmission is certainly pos-sible. There could be two microphones in the broadcast studio instead of one, connected to two distinct transmitters which broadcast the performance stereophonically on two different wave-lengths. In the receiver, each phone of the head-set could be connected to a distinct receiving system tuned to the two stereophonic transmitters. It is needless to say that this arrangement gives rise to numerous difficulties and makes reception considerably more expensive than does the simple method. The difficulties are apparently not insurmountable. The Berlin broadcast station has already transmitted stereophonically on waves of 430 and 505

In the United States this system of transmitting has been tried with fair results at Yale University in New Haven, Conn. Two transmitters of about 20 watts power were employed to broadcast stereophonically, the wave-lengths being about one hundred meters apart.

This subject of stereophonic broadcasting is referred to on page 233 of the March, 1924, issue of the Journal of the AI.E.E., a particularly pertinent paragraph of which

is quoted below: "In picking up material for broadcasting, that is, in getting the sound energy into electrical energy, the general requirement would seem to be to get to the high quality microphone the sounds in the form in which a skilled listener would wish to hear them if he were free to choose his location with respect to the source of these sounds. In this respect, the skilled listener would be largely governed by hearing the sounds under the accustomed conditions with all undesir-able noises, echoes and abnormal reverberations removed. In considering the pick-up of material for broadcasting it should be noted, however, that it corresponds to listening with one ear, that is, the binaural sense of direction, which is normally obtained in hearing the sounds directly, is lacking. binaural audition, it is possible to concentrate on one sound source and to disregard somewhat the effect of other sounds coming from different directions or distances. ecause of the monaural character of broadcasting it is necessary, therefore, to go even further in reducing noises and reverberation at the transmitter than would be the case for an observer using two ears at the same location."-Funk.



At your dealer's. If he cannot supply you send his name with your order to YAXLEY MFG. CO., Dent. N. 217 No. Dexplaines St., Chicado.



Stop Trying to Wind Your Coils on Your Finger Tips— IT CAN'T BE DONE!

Astenatic Adjustable Feeder, Significant Feeder, Significant Specific Peeder, Significant Feeder, Significant Feeder, Significant Feeder, Significant Feeder, Significant Feeder, American Specific American Specific American Feeder, Adjustable Feeder, Adjustable

The WIZAID WIRE WINDER, a light, denshle an well-disabed device, nickeled throughout, has read with disabed device, nickeled throughout, has read the second of the second

Subject to meany back guarantee.

DEALERS INVESTIGATE

WIZARD WIRE WINDER CO.

3812 Central Ave., Los Angeles, Cal.

PATENTS WRITE for our Found Guide Books and "REC ORD OF INVENTION BLANK" before disclosing inventions. Send

model or sketch and description of your investion for our INSPECTION and INSTRUCTIONS FREE. TERMS REASONABLE. Electrical and Radio Cases a specialty.

VICTOR J. EVANS & CO.

919 NINTH ST., WASHINGTON, D. C.

Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park Pl., N. Y. C.

The Balanced Interflex Circuit

(Continued from page 442)

any other control whatsoever. The 'bloom jack for head-phones is at the left, while jack for head-phones is at the left, while When through using the set, the listener pulls out the plug, which automatically disconnects all the vacuum tubes. There is no switch on this receiver. OPERATION OP THE SIT AND SPECIAL

This is a world in which you camon hope to get anything for nothing. By this I mean or seven control in your set to get anything for nothing. By this I mean and will expect to get exactly the same results, if not better, than with the old constitution of the control of the co

is not supposed to do, and does not do it the detector is well chosen.

You will understand, of course, that the "B" battery minus goes to plus "A." This saves one binding post in the set when you



SIDES OF COIL SHOWING CONNECTIONS~

Fig. 3. This shows the constructional details of the variocoupler, which can be made readily by any experimenter.

As will be seen, no rheostats are used in the set. These are supplanted by automatic resistances or Amperites, which work very nicely. If the set is completely wired as per instructions, and if the correct materials have been used, we are now ready to

time the set.

It will be found that on locals the set, if the connections are right, will work immediately, although it may squeal and howl. If the set of the set o

Tune in the lowest possible station, say around 210 or 220 meters. Adjust your tickler controls in such a way that the station comes in loudly without souncaling. By turning both tickler controls VERY slowly you will find a point which is just below the oscillation. That is the correct point.

Logged 204 stations with the Harkness Counterflex,

USING a two-foot loop as antenna, Mr. E. F. Cassel of Washington, D. C., reports the reception of 204 stations with the 3-tube Harkness Counterflex. He writes:—

"My log shows 204 stations, approximately one-third of them on the loudspacker and I am not a DX chaser. The stations include everything from Denver east and from Montreal south. Most of the log has been received from eight to ten in the evening when the heterodynes and multi-tube sets but I know of no set in this town that has been giving the consistent satisfactory reception of mine."

The Counterflex Circuit was developed by Kenneth Harkness, whose knock-out Reflex was the sensation of 1924.

The remarkable results obtained with this set are due to a novel principle which enables tremendous amplification to be secured and eliminates the squeals of selfoscillation.

After experimenting with the Counterflex for more than a year, Mr. Harkness has now written a booklet giving a thorough explanation of its fundamental principles and a complete description of different models of Counterflex receivers. We will send you a FREE COPY of this booklet on request. Just mail the coupon below, enclosing 10 cents to cover postage and cost of mailing.

KENNETH HARKNESS RADIO CORPORATION



With this complete kit of genaine Harkness parts you can assemble the 3-tabe Counterflex in just a few moments—with only a screwdriver. A series of special step-by-step diagrams shows how to wire the set. It is not mecessary to understand or follow the usual type of circuit diagram.

COMPLETE 3-TUBE KIT - - - \$36.00

CENUINE

HARKNESS


RADIO PRODUCTS

Mail this coupon for Free Book now/ KENNETH HARKNESS RADIO CORP. Dept. A-2, 727-739 Frelinghuysen Ave., Newark, N. J.

Please send my free copy of your booklet explaining the new Harkness Counterflex Circuit. I enclose 10c. (coin or stamps) to cover cost of mailing.

lame

Address

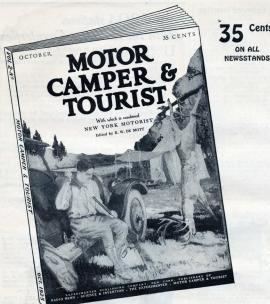

Now Bigger and Better than ever—

COMBINED WITH THE NEW YORK MOTORIST

MOTOR CAMPER & TOURIST, the only national magazine for the man on tour, has acquired the NEW YORK MOTOR. IST and combined it with MOTOR CAMPER & TOURIST. The number of pages of interesting reading matter and beautiful pictures has been greatly increased and many attractive improve-

ments have been added.

The art work is the finest that can be obtained and the entire magazine is printed in colors.

New departments have also been added, together with a larger and more varied number of articles on camping and touring.

MOTOR CAMPER & TOURIST is a bigger and better magazine in every way. A helpful, interesting and essential magazine for every motorist. Buy your copy today, it is a complete guide for every tourist.

GERMOTT PUBLISHING CO., Owners

Licensed Publishers—EXPERIMENTER PUBLISHING COMPANY, Inc., 53 Park Place, New York, N.Y.

It will be found that, as you turn the con-denser tuning control, the stations will snap in with a startling loudness without being actompanied by any squealing or howling throughout the entire range of 200 to 545 meters. If there should be howling or squealing at any of the higher stations, the ticklers are not adjusted correctly. It may be neces-sary to turn one tickler all the way around and try working it back the other way. Sounds should come in not only loudly but without distortion of any kind. If distortion exists, the ticklers are incorrectly adjusted.



~CROSS SECTION OF COIL SHOWING ROTOR CONSTRUCTION~ Fig. 4. Constructional details of the adjust-able losser described in the article which can be readily made by any constructor. It will take you a little while to become

familiar with this adjustment, but once you "get the hang of it," you will be astonished at the power and selectivity of the set. If, despite everything, the set still howls, then the trouble lies in the coupling between the two condensers. In other words, the condensers do not balance the inductances. In that case the condenser sleeve, as shown in Fig. 5, should be loosened and one of the rotors of one of the condensers advanced or retarded 1/4 of an inch more or less. This or retarded 3% of an inch more or iess. Inis can best be determined by experiment. In the set which we see illustrated here it was found that for best operation the outside rotor was almost 3% of an inch out of step with its mate. With a little experimenting you can find the correct point, after which the sleeve may be tightened. This should stop all squealing, and the set may now be said to be perfectly balanced.

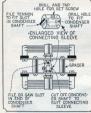


Fig. 5. Full instructions on how to link the two tuning condensers described in this article. Note particularly instructions in the article.

There may be other reasons for squealing and before attempting to adjust the condensers, please bear the following important considerations in mind: No two tubes are alike. It will be found necessary in most cases to switch around the four tubes; this often remedies the trouble. Also, as stated before, the fixed crystal detector may be at before, the fixed crystal detector may be at fault. A detector that is too sensitive causes howls. You will also notice that as you in-sert a new detector into its holding brackets, you have to retune the set slightly.



Just Listen to It!

THE A-C DAYTON asks but one thing - a



100 to 1 Vernier Dia At last, a 100 to 1, 4 in. genuine bake

lite vernier dial that matches up with all standard dials on the market. En-tire mechanism fitted into a small metal case in the knob. Nothing complicated about it, but extremely fine readings can be obtained.

The Proudfoot 100 to 1 Vernier Dial fits all condensers - both screw and locknut mounting types. Easily attached. See one at your dealers. he cannot supply you, write \$3.00 Complete



ave Length Low

CRUVER MANUFACTURING CO. 2456 W. Jackson Blvd., Chicago, Ill.



13 Still Lasts Indefinitely—Pays for Itself END NO MONEY Just state puribe

WORLD BATTERY COMPANY Wabash Ave., Dept. 75 Chic



Insure your copy reaching you each month. Subscribe to RADIO NEWS - \$2,50 a year.

The detector may work better if reversed. Try this and you will find that when it is operated in one position, reception is louder.

Of what good is the crystal detector? It gives an amplification factor of about 8 to

This may not be so apparent on locals, but if you short-circuit the detector on dis-tant stations, you will find that the signals are in all cases practically killed. Besides,

the detector in the grid circuit makes for great clarity of signals. Another important point is the detector diage. With the set shown here, the particular voltage for best results was 21.

means that you should use a tapped "B" battery on the detector side. Forty-five volts on this particular set practically killed all signals, except powerful local stations.

Try reversing aerial and ground. Very often this makes a big difference. If your aerial is 100 feet or longer, it is quite necessit

sary to place a .00025 fixed condenser in s with the anten

The set may be said to work normally when, by turning the tuning control, the stations snap in with a loud clucking sound at their full power. There should be no howl or sough through the entire broadcast range. When the set is finally adjusted and works at its best, it may be noticed that during the month it develops a squeal. This is a sure sign that the batteries are running down. With a new battery the ticklers may need a slight returning. If new tubes are used or tubes are switched around, retuning of the ticklers is, of course, necessary.

A complete list of materials for the Balanced Interflex: 2 Straight-line Frequency Conden-

Variocouplers Amperites

Audio Frequency Transformers, 31/2 to 1 Sockets

Fixed Detector .005 Fixed Condensers

Vernier Dial Automatic Filament Control

Baseboard

6 Binding Posts RESULTS

This particular set, on a 60-foot aerial, brings in KDKA at a dial setting of 50, and the volume is tremendous - stronger than e of the locals. This in midsummer. with lots of static prevailing and transmitting conditions notoriously poor. The locals, of course, come in with tremendous volume over the entire range. Distant stations that have been heard on a single evening are given in the list. This should by no means be considered a record, because receiving conditions in New York are poor. Besides, the log represents that of a sultry August night, with a great deal of static which made it impossible to get the calls of many more stations that otherwise could have been logged.

This receiver should be of particular a peal to those who wish the simplest possible control of a radio set.

The policy of Radio News is such that it is impossible to recommend certain parts that go into the making of any set. writer will, however, be glad upon receipt of a stamped addressed envelope, to forward a list of the particular parts used in the set described here. The writer will also be glad to give his attention to correspondence from those readers who have constructed the Interflex-Four, or who wish to have further particulars about it.



MARVELOUS NEW LOOP Folds to any position-Wires always taut **GUARANTEED FOR LIFE!**

The newest addition to the line of quality Radio Accessories. Made of the highest grade materials throughout in a new and masterly design. Specifications: Length, 24 inches, Normal Ht., 20 inches, Wavelength; range 120 to 600 meters. The AALCO is different both in appearance and operation. You will find that this new loop adds cannot supply you send money order, as will ship direct. LIST PRICE, \$15.00. JOBBERS: Write for our proposition

AALCO RADIO LABORATORIES 6346 Cottage Grove Aven



The Famous Truly Portable TELMACO P-1 Receiver Four Tubes Do the Work of Seven

ty, distance, volume, workmanenip and policy of the state of the state

P-1 Kit Saves You Money! lmnco P-1 Receiver in hit form has lastic reception. This contains all us, including case, drilled and en-i illustrated instructions. \$80.00 or write us. Descriptive folder free.

Radio Division Telephone Maintenance Co. 20 So. Wells St. Dept. B Chicago, III. SELMACO

Quality Radio Exclusively N Established 1918





Address

The Radio Hook at WRNY (Continued from bage 438)

ignorant of all this, goes on to the end; that is, if the announcer lets him. If the amateur is palpably bad, the announcer, who listens in to the din from the critics' room by means of his head-phones, politely informs the amateur that the critics would like to give someone else a chance. Immediately the next amateur goes on.

Why do the critics wear head-phones? Simply because if they had a loud speaker in the critics' room this loud speaker would talk into the microphone and the radio audience would hear nothing but a howl. Hence the head-phones are needed.

A patent is pending on this arrangement-

The Experimenter

has come back! If you are one of the one hundred thousand readers of the old ELECTRICAL EXPENDENTER, you will no doubt be glad to bear that the EXPENDENTER has come back BIGGER AND BETTER THAN EVER.

Experimental Radio

Nothing but experiments, written by the foremest radio authorities, also a monthly ure section to brighten up the magnine. But best of all for you radio readers, is the big radio section of over twelve pages of some fifty radio experimental articles—and mind you, NOTHING BUT EXPERIMENTS.

INTERESTING ARTICLES TO AP-PEAR IN THE EXPERIMENTER FOR OCTOBER, 1925

Thermit Fusions for Experimenters By T. O'Conor Sloane, Ph.D. Audio Frequency Amplifying Transformers By Theodore H., Nakken A Broadcast Type Microphone By A. P. Peck

Remote Control

Meters and Their Use

By Leon L. Adelman Maps of Electricity on Airplanes
By H. T. Wilking Electric Water Tank Heater

Hard Tubes and Soft Tubes (Continued from page 435)

to the electron stream and the simultaneous reduction of the space charge by the posi-tive ions—will together produce a most marked increase in the current passing through the tube

These facts explain the extreme sensitiveness as detectors in wireless of tubes con-taining a certain amount of gas. If the grid potential is set so that the driving po-tential on the electron stream is just too small to produce ionization and the grid is then connected to an aerial any potential surge in the aerial, even if extremely small, will cause ionization to set in and the plate current will leap up to a value much higher than would be reached if a hard tube were connected to the same aerial.

INSTABILITY OF GAS TUBES

Practically, the trouble with these tubes has always been instability of the critical voltage point for the setting in of ionization. This point depends on the number of atoms present, that is on the pressure, and, if the gas is merely the residual gas from the evacuation of the tube, the pressure does not remain constant while the tube is in use. It follows from this that although a tube may display extraordinary sensitivity at a given moment it may slip off and be almost



To the Radio Dealer:

Let us explain how you can make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade.

The Experimenter Publishing Co.

53 Park Place, New York City



Developed for Those Who Demand the Best

Apex Vernier Dials Apex Vernier Diats are constructed on ephanistival tested and truly scientific principles and are engineered truly scientific principles and are engineered exceptable to the separations of the average radio user, consequently they more than meet the expectations of the average radio user, it yanged to the service of the service of the service and provide control and accuracy essential to full radio engineers. It is under the service of t byal Brass Finish, 4in. \$2.00; 3½ in. \$1.65 tin Silver Finish, 4in. 2.50; 3½ in. 1.90 eLuxe Gold (24K)4in. 3.00; 3¼ in. 2.50

Apex Rheostat Dials

APCA ARICOSTAT J/1318
are little brothers to Apex Vernier Diala. Accurate, handsome—a necessity to attained to the control of APEX ELECTRIC MFG. CO. 1410 W. 59th St., Dept. 1006 : Chicago



TOWN CRIER Radio's Most Beautiful Speaker

Xou will be delighted with the gorgeous colors . . the handsome, stippled finish, and the novel design of the Town Crier-the Speaker with the voice that thrills. Ask your dealer to show you a Town Crier Speaker. Write today for beauti-fully illustrated circular describing the Golden Polychrome and Green Poly-

List Price \$17.50 GALE RADIO LABS. CHICAGO

THE LATEST parts and sets are always featured in our Salespeaker. If you are a live-wire dealer, write for your copy, now.

HUDSON-ROSS-116 S. Wella St Chicago

your copy reaching you each month, e to RADIO NEWS-\$2.50 a year, enter Publishing Co., 53 Park Pl., N.Y.C.

couraging, and later wrote that if true it would account for Michelson and Morley's results on light and ether drag. (Still later he forwarded one of the papers to the Royal Society for publication, but could not get it in.) So the paper was not published till 1891, and then much abbreviated.

The theory was rounded up, meanti the tensile strength of some metals which had never been measured was predicted, c.a., of cadmium, which was later confirmed almost exactly by Thurston. Also the true nature of solution was worked out and given; which became accepted later, and also Van der Waal's equation was modified into a simple form which has also been accepted, by Sutherland and others.

STANLEY-KELLY-CHESNEY LABORATORY Stanley owned part of the electric light-ing station at Pittsfield, Mass. Chesney, who had had a thorough electrical training and was a fine designer, had worked out new types of transformers which should be (and later turned out to be) better than anything on the market. Kelly had a brilliant idea of neutralizing the inductance of motors by winding a compensating winding in grooves in the pole pieces. was thought that the silicon iron would be of use in the transformers and A.C. motors and Chesney had found that the idle current of transformers could be neutralized comof transformers could be neutralized com-mercially and the all-day losses greatly re-duced if my new type of condensers was used. So I was asked to join them. Zim-mermann offered me the position of chief electrician and a much higher salary if I would stay, but, perhaps wisely, perhaps unwisely, I went.

Superpower Broadcasting (Continued from page 419)

are carried overhead and consist, for the most part, of copper tubing. The two transmitters and the modulator units, together with the kenetron rectifying units, are housed in Building No. 1 at the experimental field.

THE TRANSMITTERS Aside from the two main transmitters, there are several others. One is built to ransmit on 90 meters, another to work at 20 and 40 meters and still another to work at 5 meters. These are all distinct from the main WGY station, which is situated in the center of the General Electric Plant in Schenectady. The 90-meter set will usually work at about 5 kilowatts, though the installation is capable of a much greater output. This station is in a building of its own and the other short-wave installations are situated in still another building. The power supply for the whole outfit comes

from one source, however. The 5-, 20- and 40-meter work is still very The 5-, 20- and 40-meter work to much of an experiment, in that there is no regular broadcasting on these bands. The work being done with them is solely for the purpose of collecting data as to the be-havior of radiations at the extremely high

frequencies. The two large installations are in standard form and are permanently installed. The condensers, as can be seen, are composed large aluminum plates, which are made up in a very novel manner: the surfaces are formed of two pieces of spun aluminum which are snapped into the holders like which are snapped into the holders like watch crystals. They are spaced rather far apart, even for transmitting sets. However, when it is considered that in some of the sets the voltage on the plates runs in the neighborhood of 10,000 the reason is ob-

The water cooling system is worthy of detailed description. The plate of the tube in the case of the twenty-kilowatt tubes

22½ Volt Un-Acid Everlasting Recharge-



Steinite 1500 MILE oday's Greatest 1-Tube Set Regenerative Licensed Under Armstrong Patent 1113149

Sharp Tuning Easy to Operate FREE 10 Day Trial

201 Radio Bldg., Atchison, Kan. Write for Free Literature. Complete Line

To the RADIO DEALER

Let us explain how you can't make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade.

EXPERIMENTER PUBLISHING CO. 53 Park Place, New York City



LARGE CONCERT UNIT The Heart of the Speaker

Large size of this unit gives great range with tone of most pleasing quality which, combined with the amplifying properties of the Burns Horn, produces remarkable results.

Horn is of distinctive de-

sign with pyralin flare in several handsome finishes. It pleases the eye as well as the ear. Made by American Electric Company

CHIGAGO, U.S. A.



How to Build the SUPER-FIVE

Write today for the WOLDER of the BOOK. It will bring you a new radio experience. Profusely illustrated with photographs, drawings. It takes you arep-by-step through the making of the SUPER-FIVE, acceptional 5-Tube Receiver developed by engineers of the Gearhart-Schluster Radio Corporation. bring you a new radio ex ely illustrated with photo Corporation.

Inclose 28c and you'll have it by return mail.

Gearhart-Schlueter Radio Corporation

Dest. 711

Fresno, California

Young Men-Turn Your Spare Time Into Money!

Carn big profits, prizes, and awards seming ADIO NEWS, SCIENCE & INVENTION, PIE EXPERIMENTER, and MOTOR CAMPER & TOURIST in your neighborhood. We train you as our salesman and pay you liberally for your time. Write at once and we will help you to get started.

M. BRIDWELL

THE EXPERIMENTER PUBLISHING CO. 53 Park Place, New York, N. Y.

plification constant and the plate resistance. It must be understood, of course, that each tube is put through its paces separately. The characteristic curve is measured and all the other data found separately for each individual tube. And the best part of it all is that the tubes measured in the Laboratories of Ranto News were found to have values of these quantities in accordance with the values given by the manufacturer on these graphs furnished with the tubes. The tubes which were tested were selected at random from a batch of 100 furnished by the

A RE you interested in motoring, tour-ing or camping? If you are, do not fail to read the October issue of

MOTOR CAMPER AND TOURIST

Here is a magazine that tells you thin in connection with your car—things that you never even suspected. Are you just running around the country or are you getting the full benefit of your car? MOTOR CAMPER & TOURIST shows you the way. On all newsstands.

CONTENTS FOR OCTOBER ISSUE Hunting with the Automobile.

By Capt. Paul A. Curtis

Why Motorists Like Wisconsin.
By May L. Bauchle Springs in Missouri.

By Mabel Henderson Malone What I Wear When Camping.

By A. Pearl McPherson

A Trip to the Berkshires. By Louise A. Haadin unting a Good Place to Camp on a Ninety-Day Ramble

By B. F. Clark The Bluenose Trail.
By Lorraine Wallace Gould

The Behavior of Radio Waves

(Continued from page 411)

Some of these things have been brought out from time to time in Radio News in the forecasts of the future. These prophetic articles are extremely interesting to me and should be to all those who have imagination and are interested in the future of the world's youngest science.

And one point which should not be over-looked by the other sciences in the advance looked by the other sciences in the advance of radio is that before all the present enig-mas are solved, there will be a wealth of material found in the exploration of radio that will throw no end of light upon problems now confronting the workers in other

One of these which seems to be of great importance is in this same wave work which we have been describing. Before all is known concerning the nature of propagation of waves from an antenna, the physicist will find a great deal of data valuable to him in finally reaching a thorough explanation of the passage of currents over ordinary conductors, a problem which is by no means settled as yet.

Already radio has taught us a great many things concerning the electron, and it certainly will tell us much more as time goes on.

HOT DOG!

HOPE: So that radio friend of yours doesn't approve of your crystal set?

LESS: No, that DX hound even barks at Less: No, t Contributed by Moses M. Allen.



Hear the Murdock Neutrodyne

COMPARE the Murdock
Five Tube Neutrodyne for
the quality of its tone; for the
beauty of its cabinet; and for
its reasonable \$100, price!
There is space in the cabinet
for the "B" batteries. The only \$100. with built-in making radio apparatus.

WM, J. MURDOCKCO.
Dest. At, Washington Ave
Chelsea, Mass. \$92.50 MURDOCK

NEUTRODYNE

NEUTRODYNE The MOLLIFORMER



Volume — Utilizes greater

Guaranteed to Give Complete S Your Money Refund PRICE \$22,50 60 Cycle Unit.... Complete Kit— 25 Cycle Unit....

24.50 C. E. JACOBS, Sole Mnfr.

Build a Single Control Receiver Don't Use a Multitude of Dials



The KINLEY

Tuned Radio Frequency Unit

GIVES BETTER RESULTS WITH ONE DIA

PRICE \$16.00

Send for descriptive circular.

KINLEY RADIO COMPANY
45 Elmhurat Ave. : : : Detroit, Mich.

The Inventions of Reginald A. Fessenden

(Continued from page 429)

power formerly used, i. c., just a little better than my estimate.

A.C. MOTOR. SILICON IRON FOR LOW

A.C. MOTOR. SILICON IRON FOR LOW A.C. LOSSES Meantime, whenever there was a chance, my experimenting was going on. Alternat-ing current work was coming up and the mathematics of this as given by Kapp and others was carefully studied. Some work was done on an a.c. motor, a commutator type run by a.c. currents. This was a dead failure. The sparking was cut down pretty well, but it got altogether too hot.
This was traced to the high hysteresis and
eddy current loss, with a.c. currents. The thing to do, therefore, was to get a kind of iron with lower hysteresis and higher ohmic resistance. Here the electrostatic doublet theory of cohesion came in useful again. I am not dead sure now that this particular application of the theory was correct, but it gave the results, which was the important gave the results, which was the important thing then. Why did iron have hysteresis? But first, what happened when iron was magnetized? Ewing's book on magnetism had been published and it then seemed fairly certain that the iron molecules aligned themselves in some way when magnetized Hysteresis meant loss of energy, so it seemed that elements which caused iron to have large hysteresis, when alloyed with it, hinlarge hysteresis, when alloyed with it, hin-dered the iron molecules from aligning freely. Looking back at the figure given for the explanation of the contraction of chemical compounds it will be seen that if the inter-space filling element was small or irregular in shape it would do this. Also an irregularly shaped element had a high melt-ing point, and mercury had a low melting point because its atoms were nearly round.

Now the carbon atom was small and with sharp corners and carbon had a high melting point, so this would explain why high carbon steel had high hysteresis. The thing to look for then was some element whose atoms were farger than the carbon atoms and which did not have too high a melting point and which was cheap and easily alloyed with iron. Silicon seemed to be what was wanted, as its atomic volume was considerably larger than iron and it melted at a lower tempera-

ture and was easily obtained.
So, through the shindness of Mr. Perrine,
Former electrician for the company and thes,
Former electrician for the company and thes,
samples of low carbon iron alloyed with different amounts of silicon were obtained. They
were tested and found to give low hysteresis
result may have been pure lock and that the
rotation is of a more complex nature to
the result has been of so much use to the
the result has been of so much use to the
the result has been of so much use to the
the result has been of so much use to the
the result has been of so much use to the
the result of the result of the result of the result has been
if any the result is the result of the result is a single size.

If any the result is the result is the result of the result is
the result in the result is the result in the result is the result in the result is
the result in the result is the result in the result in the result is the result in the result in the result in the result in the result is the result in the

ELECTRODELESS GAS LAMPS

When fixing up the laboratory platenates and correcting in for older of source, some vacuum tubes which were bying about were efficient vacuum tubes might be made by making the tube long enough, because the effects of the control of the tube long of the laboratory of the laboratory



Amazing new receiver

NOW anyone can build it in an amazingly short time this new easy way. Experts assemble it at factory. You simply wire. Note revolutionary new principle it contains.

NO excuse now for not having a fine radio, At a surprisingly low cost, too. For a remarkable plan is showing thousands a new way to build their own. It is so easy that anyone can do it in all hour's time. So fascition to the source of the s

And in addition to the fun and pride of building your own, the finished receiver actually contains a phenomenal feature not yet found in the most expensive sets; that brings results otherwise impossible.

This feature follows the discovery of a new inductance principle that overcomes many vital weaknesses of present day sets. It is based on an entirely new type coil—the Erla *Balloon *Circloid.

Circloids are the backbone of the Erla kit and are largely responsible for the striking improvements this kit alone offers. Note these four advantages in particular:

 Greater distance. Circloids have no measurable external field to affect adjacent coils or wiring circuits. This makes possible higher amplification in each stage, with increased sensitivity and greater range.

2. More volume. Higher r.f. amplification enables Circloids to bring in distant stations scarcely audible in

Dealers—Exclusive franchises are available to high class dealers in localities still open. Write or wire immediately.

ordinary sets with volume enough on the loud speaker to fill an auditorium.

3. Increased selectivity. Circloids have absolutely no pick-up qualities of their own. Only signals flowing in the antenna circuit are built up.

4. Finer tone quality. The self-

enclosed field positively prevents stray feed-backs between coils. Hence no blurring or distortion. Tones are crystal clear, Circloids are sold singly and in sets

of three; also in kits containing three Circloids and three, 60035 condensers. Write for free information a hit—also book See how a few minutes of (an alligative you the newest and most nearly perfected set known to radio science. Examine it at any Eria dealer's, or send the coupon for full information, illustrations and diagrams contained send the coupon of rull information, in the containing the sensational new Circloid principle. Enclose 106 for mailing and postage on book.

*Trate Mark Engintered.

Electrical Research
Laboratorica,
2506 Cottage Grove Ave.,
Dept.17-A, Chicago, U. S. A.

☐ Send me free information on kit. ☐ Enclose the street England to give the standards were to go routing for book. All one company to give "Better Radio Reception." complete value service. Name

| Address | | |
|---------|---------|--|
| | _County | |

The Sensational Buy of the Year—Radio Set, Lot, Subscription
A GENUINE

| HARKNESS | COUN | TERFLEX | KIT |
|-------------------|-------------|-------------------|--------|
| 3 Tube Reflex and | Better Than | the Average 5 Tul | oe Set |

Instruction booklet illustrates and explains assembly and wiring step by step.


SECOND: A FREE Warranty deed for a LOT 20 x 100 at or near Port Jefferson, Long Island, New York.

THIRD: A year's subscription to this magazine—RADIO NEWS.

\$36.00 c. o. d.

THE REGULAR PRICE OF THE HARKNESS' LATEST MASTERPIECE

| KEWOL RADIO COMPANY. 205 Brendway, New York City. Gentlemen — I am erobating check or manay order for Gentlemen — I am erobating check or manay order for KIT along with the FREE WARRANTY DEED an Year's Subscription, to Radio News. |
|--|
| Name |
| Address |
| City State |

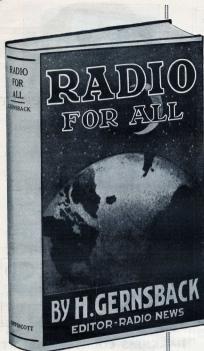

PRICE \$2.00

Mail all orders with money order or cash direct to

The EXPERIMENTER PUBLISHING CO., Inc. New York City 53 Park Place

RADIO'S

Most Complete Book of Information

By H. GERNSBACK

Editor of RADIO NEWS, SCIENCE AND INVENTION, THE EXPERI-MENTER, and MOTOR CAMPER

What the novice in radio needs the book in the second of the secon

WHAT THE BOOK IS

A combination of a radio course for the portion of the property and telephone with a reference book for the more ox perfecced amateur. Half a dozen book in one.

FOR THE BEGINNER

Herr to make your own receiving set costing from \$3.00 to \$50.00. coming reflit \$3.09 to borrow. Here to read diagrams: for every pic-ture diagram there is a corresponding technical diagram using the symbols instead of drawings. How to time sharply and eliminate inte-ference from other stations.

FOR THE MORE EXPERIENCED

AMATEUR

How the radio compass works. How the radio cempass works.

All about underground aerials, loop perials and directional aerials. Permulae for finding wave length; mis-cellaneous formulae for finding capacity of condenser and other instruments. Tabbes of wire resistances, wave lengths and their corresponding frequencies, approximate wave lengths for different section, tuning cell data, and much more approximate lengths to the lengths of the lengths and much more properties.

SPECIAL FEATURES

Detailed description of Washington weather signals and their translation. Description of a modern broadcasting sta-tion and its operation.

IN OTHER WORDS

and important to that you codinarily have to dig out of government publications, text-books, purpolists, etc., is handly combined in this one book.

the next thought was, why not do away with the electrodes altogether and make the gas the secondary of a transformer and so do away with all electrode drop and loss? This was suggested to Mr. Westinghouse, but nothing came of it at the time, so the work was dropped.

FIRST PATENT, SILICON IRON WIRE In the vacuum tube experiments platinum had to be used for the wires sealed into the glass and leading the current to the electrodes. This was expensive even then. What could be used in place of it? Evidently something having the same approximate coefficient of expansion as glass and which would "wet" the melted glass, ie, have if possible a negative capillary coeffi-cient with respect to melted glass. Iron has a low coefficient of expansion, and glass is mainly oxide of silicon so wire made from the silicon iron alloys which had been obtained for the magnetic work suggested obtained for the magnetic work suggested itself and proved satisfactory. Other alloys were tested and my first two patents applied for, with the permission of Mr. Westing-house. I. c., U. S. 452,494, Feb. 18, 1891. covering alloys of silicon with iron, nickel, cobalt, etc., and U. S. 453,742, Feb. 18, 1891, covering the method of keeping the joint clean by sealing in vacuum, driving off occluded gases by passing current through the wires, so that iron or nickel alloys could be used without addition of silicon, the oxide formed being forced to combine with, and dissolve in, the glass. Nothing was done with this at the time, but it saved done with this at the time, but it saved Westinghouse the loss of the contract for lighting the Columbia Exposition at Chi-cago in 1893, and the method is apparently coming into use again.

VACUUM-BOILED OXY-CELLULOSE CONDENSERS

The condensers used for the A.C. motor experiments, though of the purest cellulose and parafine and boiled in vacuum, heated badly, i.e., had high dielectric hysteresis. On the electrostatic doublet theory this must be due to short-conducting paths in must be due to short-conducting paths in the material, of perhaps only molecular dimensions. Cross and Bevan, and I think some others, had found that a molecule of water could be split off from cellulose by prolonged heating at a certain temperature. Possibly this water molecule was what formed the conducting path, and caused the high hysteresis. So the paper was heated in high melting point for so many hours, until the water molecule had come off, and then boiled in vacuum. It worked; the hysteresis was reduced to a small percentage of the previous loss and could no longer be meas-

PURELY SCIENTIFIC WORK

Passing over other experimental work on circuit-breakers, projectors, etc., the purely scientific work had not been entirely neg-lected. The money allowed me for Pullman fares on my trips was (with the knowledge of the company) used for buying scientific books, with, I believe, no loss to the efficient carrying out of the company's work. Also there was a remarkably fine public library in Newark, much ahead of the times. Alter-Hertz were thoroughly worked over. A paper on the electrostatic doublet theory of cohesion was read before a little local soci-ety, the Newark Electrical Society, in 1890, cty, the Newark Electrical Society, in 1890, and a copy was sent to the Philosophical Magazine for publication. But it was too new. One of the editors said that it could not be correct because it did not obey Maxwell's fifth power law quarilosity the first. not be correct because it did not obey Max-well's fifth power law, overlooking the fact that I had pointed out that it did. Another objected that electrical charges could only exist on the surface of conductors, and so could not account for the cohesion of the metals. Fitzgerald, an extremely kind man and a mathematical genius, was more en-



Dubilier Micadons -Standard Fixed Radio Condensers

Nearly all of the leading manufacturers of radio sets have adopted the Micadon as their standard

A layman might be fooled. Not so these manufacturers. They need fixed condensers with accurately matched and permanent capacities, and they know which are the best,

Send 10c for 32-page booklet, "Applications of Dubilier Condensers in Radio Circuits." Address Dept. F-2.

Dubilier

4377 Bronx Boulevard, New York City



Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year Experimenter Publishing Co., 53 Park Place, N. Y. C.

Developed for Those Who Demand the Best

Apex Vernier Dials truly scientific principles and are engineered to meet the precise requirements of experts—consequently they more than meet the expectations of the average radio user. They bring in distant stations with alactic properties of the experts of the e

Royal Brass Finish, 4in. \$2.00; 3½in. \$1.65 Satin Silver Finish, 4in. 2.50; 3½in. 1.90 Del.uxe Gold (24K)4in. 3.00; 3½in. 2.50 Apex Rheostat Dials
little brothers to Apex Vernier Dials,
urate, handsome—a necessity to satisory operation, beauty of appearance.

APEX ELECTRIC MFG. CO.

1410 W. 50th St. Dept. 1016 . Chicago





Town CRIER Radio's Most Beautiful Speaker

You will be delighted with the gorgeous colors . . . the handsome, stippled finish, and the novel design of the Town Crier— the Speaker with the voice that thrills. Ask your dealer to show you a Town Crier Speaker. Write today for beauti-fully illustrated circular describing the toolden Polychrome and Green Poly-

List Price \$17.50 est of the Rockies \$18.50 GALE RADIO LABS.

THE LATEST

parts and sets are always featured in our Salespeaker. If you are a live-wire dealer, write for your copy, now. HUDSON-ROSS-116 S. Wells St.

your copy reaching you each month, to RADIO NEWS-\$2.50 a year, enter Publishing Co., 53 Park Pl., N.Y.C.

couraging, and later wrote that if true it would account for Michelson and Morley's results on light and ether drag. (Still later Society for publication, but could not get it in.) So the paper was not published till 1891, and then much abbreviated.

The theory was rounded up, meantime, the tensile strength of some metals which of cadmium, which was later confirmed almost exactly by Thurston. Also the true nature of solution was worked out and given; which became accepted later, and also Van der Waal's equation was modified into a simple form which has also been accepted, by Sutherland and others.

STANLEY-KELLY-CHESNEY LABORATORY Stanley owned part of the electric lighting station at Pittsfield, Mass. Chesney, who had had a thorough electrical training and was a fine designer, had worked out new types of transformers which should be (and later turned out to be) better than anything on the market. Kelly had a bril-liant idea of neutralizing the inductance of motors by winding a compensating winding in grooves in the pole pieces. was thought that the silicon iron would be of use in the transformers and A.C. motors and Chesney had found that the idle current of transformers could be neutralized comof transformers could be neutralized com-mercially and the all-day losses greatly re-duced if my new type of condensers was used. So I was asked to join them. Zim-mermann offered me the position of chief electrician and a much higher salary if I would stay, but, perhaps wisely, perhaps unwisely, I went.

Superpower Broadcasting (Continued from page 419)

are carried overhead and consist, for the

most part, of copper tubing. The two transmitters and the modulator units, together with the kenetron rectifying units, are housed in Building No. 1 at the experimental field.

THE TRANSMITTERS

Aside from the two main transmitters, there are several others. One is built to transmit on 90 meters, another to work at 20 and 40 meters and still another to work at at 5 meters. These are all distinct from the main WGY station, which is situated in the center of the General Electric Plant in Schenectady. The 90-meter set will usually work at about 5 kilowatts, though the installation is capable of a much greater out-put. This station is in a building of its own and the other short-wave installations are situated in still another building. The power supply for the whole outfit comes om one source, however,

The 5-, 20- and 40-meter work is still very much of an experiment, in that there is no regular broadcasting on these bands. The work being done with them is solely for the purpose of collecting data as to the be-bavior of radiations at the extremely high frequencies

The two large installations are in standard form and are permanently installed. The condensers, as can be seen, are composed of large aluminum plates, which are made up in a very novel manner: the surfaces are formed of two pieces of spun aluminum formed of two pieces of spun aluminum which are snapped into the holders like watch crystals. They are spaced rather far apart, even for transmitting sets. However, when it is considered that in some of the sets the voltage on the plates runs in the neighborhood of 10,000 the reason is ob-

The water cooling system is worthy of detailed description. The plate of the tube in the case of the twenty-kilowatt tubes

22 Volt Un-Acid Everlasting



26 page radio goods catalogue 10c. Same day shipments B. R. SMITH, 31 Washington Ave., Danbury, Conn



Inday's Greatest 1-Tuhe Set \$6 Regenerative Licensed Under Armstrong Patent 1113149 Sharp Tuning Easy to Operate FREE 10 Day Trial

STEINITE LABORATORIES, Manufacturers 201 Radio Bldg., Atchison, Kan. Write for Free Literature. Complete Line

To the RADIO DEALER

Let us explain how you can' make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade.

EXPERIMENTER PUBLISHING CO. 53 Park Place, New York City

forms the bulle of the tube. That is, the filament and grid are inside it. The leads from the elements are taken out through a glass seal at the top. Around the plate there is a metal container which carries the water circulation. The water is led to the sheath through rubber hose. A large radiator at the rear of the building keeps the water at approximately atmospheric temperature all

the time. The water lead—the hose—is coiled on large wooden drums so as to make the water column long enough to raise its resistance to cent from the tube. The system may seem rather peculiar and ineffective at first sight, but practice has proven that it works very well, or at least with as good efficiency as

do the other parts of the circuit.

The plate current for the verice of the plate current for the plate current

TYPES OF ANTENNAE

There are several types of antennae available for use on any of the sets. At the being used. It consists of two excitons, each of which is tumed to the entired wave-length, others which may be used. Just now the entired wave-length others which may be used. Just now the entired wave-length of the property of the entired wave-length of the entired wave-length of the entired wave-length of the entire the entire the entire that t

This description is the first released on the new superpower work, and represents practically the first step in the inauguration of of this new plase of radio broadcasting. Our knowledge as to the behavior and efficiency of such installation is extremely hazy, but now that investigation of a wide type has been started, there will no doubt be much of interest on the subject to make its appearance within the next few months.

Parlor Magic With Your Radio Set

(Continued from page 421)

series with a load speaker and a see. It is order to have sound come from the load speaker it is necessary that a complete, undered chain the exhibited. Any nummore there are, the weaker the sounds will be it will be noted in this experiment were proposed to the contract of the contrac



We have all the new, advanced types of parts at prices which save you REAL MONEY! "Straight Line Frequency"

Condensers, "Toroidal" Coils, "All-Frequency" Audio Transformers, new "Vernier" dials and all the other newest type park. Also Kits and sets of latest improved designs. All clearly illustrated and fully described in our new, big FREE Catalog and Builder's Hook Un Guide.

Get this big Free Book today! You need it! You can't afford to be without this hom a fide money saver and sure guide to success. Send for it now—at once, before you buly another part of any kind! Before you bull another set! Simply send name and address and name of friend interested in Radio. Send today!

THE BARAWIK CO. 102-142 S. Canal St., Chicago, Ill.

One of America's Oldest Radio Institutions

GLIMINATE Your STORAGE A *** BATTERY *** A. C. POLARIZER Use Electric Light Current—awa your recharging tests and before. First usual set of Blus is had.

Use Electric Light Current—saves your recharging easts and bether. First small east of Bax is lated, Nothing to act out of order. Thousands are always giving satisfaction. Order yours TODAY.

SEND \$1.BILL along with yours and SEND \$1.BILL along with yours and the second of the second seco

BLAX WILL SELL

BLACK BROS., Inc.
BLACK BUILDING
Los Angeles

Potter CONDENSERS

—Prevent "B" voltage fluctuation —Allow undistorted amplification —Make possible full bass tones —Improve reception with "B" Supply Units,

Made in 1/10, 1/1, 1/2, 3 and 4 Microfarad sizes
At Your Dealer's
POTTER MANUFACTURING COMPANY
North Chicago, Illinois

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year.

Experimenter Publishing Co., 53 Park Place, N. Y. C.

RADIO LISTENERS' GUIDE and CALL BOOK

Suide and (

Radio Set Owners Book

fall Issue

Worlds' Greatest Book of Information with the Latest Complete List of Radio Stations and Call Letters

Here is the latest and greatest radio book of its kind published for the Broadcast Listener. It is a National Radio Guide Book of the United States in that it gives you, completely and comprehensively, the location of radio stations on the air. It lists all stations of the United States, both Broadcast and Amateur, giving size and location of each station, its wave-length, etc., with ample space for tabling and logging those you receive.

Then just as an Automobile Guide Book tells you how to care for your car, this book explains the complete care of your radio set by explaining the fundamental operation of all principal parts. And also it gives foreign radio stations, time signals and a multitude of

similar, valuable listings. 116 pages filled to the brim with valuable data,

PARTIAL LIST OF CONTENTS

Selecting a Radio Receiving Set. Reaching the Shorter Wavelengths. by States. How Broadcast Stations Operate. Radio Broadcast Stations of Canada. Locating and Eliminating Trouble in

All About Radiologs.
The Function and Care of Vacuum
Tubes.

Loud Speakers-How to Select Them. Fundamental Principals of Radio, The Care and Operation of Storage Bat-

Basic and Modern Radio Circuits Aerials, Loops, Ground and Lightning Arresters How to Understand Radio Circuits.

Radio Broadcast Stations of the U. S., by Call Letters.

Radio Broadcast Stations of the U. S.,

Special Land and Experimental Radio Stations of the U. S Foreign Radio Broadcast Stations, by

American Radio Relay League and Directory. Amateur Radio Stations of the U. S., by

Foreign Amateur Radio Stations. Table for Making Time Transitions. Radio Broadcast Maps of the United States and Canada.

Time in All Parts of the World.

Sold and Distributed by

The Consrad Company, 233 Fulton St., New York

Consrad

35c the copy-Sold at all Newsdealers and Radio Stores

IF YOUR DEALER CANNOT SUPPLY YOU, ORDER DIRECT, USING THIS COUPON

THE CONSRAD CO., 233 Fulton St., New York City

Herewith find 35c for which send me Fall Edition of Radio Listeners' Guide & Call

Name

skin of the hands. If, however, the hands are slightly moistened, the loud speaker will come on with full strength as a rule.

In the chain experiment as shown in illustrations 2 and 2A, lots of amusement will be created by the operator asking one of the girls to stick out her tongue and having the next partner touch it with the tip of her finger. The tongue, being very sensitive and moist, will naturally carry a high amount of current. If the set is of the 5-tube variety, I can vouch that the same girl will not try it twice. Although the shock is not at all serious, it is somewhat disagree-able when experienced for the first time. This particular experiment, by the way, does not work unless the polarity is right. You may have to reverse the connections at the plug in a previous experiment to find out which is the correct polarity.

The next is a most interesting experiment, as interesting as it is surprising. Even your average radio engineer, if told that you can make a perfectly good head-set with a pair of glores will probably laugh at you. Nevertheless, the following shows how to do it. As shown in illustrations? As shown in illustrations 3 and 3A, it requires two performers and one person to be entertained. The two performers must put on kid gloves (cotton or silk gloves do not work.) One pair of gloves will do; namely, a right and a left. The gloves should be put on the usual way, buttoned up, so that the palm of the hand and the stretched part of the glove become a diaphragm, which when held with a spread hand, will be stiff.

The two performers now grasp leads or wires leading to the plug of the radio set. No loud speaker is connected in this case. The two hands with the gloves are put over the ears of the listener. Be sure that the the ears of the listener. gloves actually touch the ears. In the case of a girl, the hair must be pushed aside, as the experiment will not work well over the hair. If the station is tuned in, she will hear the selections as loud as with a good head-set. This may seem surprising, but it is simply a variation of the good old condenser telephone, invented by Professor Dolbear in 1876. In this case, the hands of the performers form the two plates of the condenser, while the gloves are the dielecthird plate. The leather diaphragm vibrates under the influence of the high frequency currents, and the sounds are heard. This is a very pretty experiment and one that always arouses considerable astonishment, not only from the layman, but also from those

who know something about electricity.

A clever variation of this experiment is shown in illustrations 4 and 4A. This is a duplicate of the preceding one, except that in this, no gloves are used, merely two pieces of stiff bond paper, such as used for letterheads. The two pieces of paper are pressed with the bare hands against the listener's ears, while the performers grasp the metallic ends of the wires coming from the phone plug in the two free hands, as in the glove experiment. If the choice of the paper is right, the listener will hear the sounds as loud as with a good head-set.

In both of these experiment it is assumed that the strength of the signals is good. If they are weak as for instance, those coming from a distant station, the results will be very poor. The louder the signals received, the better the results.

The reader will, of course, be able to make many variations of the experiments described herein, and with a little ingenuity a good deal of entertainment can be pro-vided.

I have in my notebook a number of other experiments of the entertainment kind, and experiments of the entertainment kind, and if you should care to see more of them, I shall be glad to hear from you. If there is enough response from our readers, I shall soon publish a second installment of Parlor Magic With Your Radio Set.



The Bridge to Amplification Without Distortion

Daven engineers were pioneers. They blazed the way for others to follow. They designed and built the first Resistance Coupled Amplifier offered the public. They found resistance coupling in an experimental stage. They perfected it.

Daven Resistance Units, Amplifier Kits and Super-Amplifiers are accepted by authorities as standard. The Daven Super-Amplifier, for use in any known set or circuit, is priced at \$15.

A NEW TUBE BY DAVEN

To meet the exacting requirements of Resistance Coupled Amplification the Daven Radio Corporation has created a new product—the DAVEN HIGH MU VACUUM TUBE. Type MU 20. It is designed for one specific purpose only—to increase the amplification of the Daven Resistance Coupled Amplifier so as to

exceed that of ordinary audio Use this free coupon



exceed that of ordinary and frequency coupling. The Daven High MU is a 6-volt, 1/4 Daven Radio Corp. 183-169 Summit Street Newark, New Jersey Laurent High MU is a 6-volt, % ampere tube with an amplification constant of 20. The price is \$4.00. Daven Power Tube Type MU 6 is for last or output stage. Price \$5.00

DAVEN PRODUCTS ARE SOLD ONLY BY GOOD DEALERS

25c is enclosed.

Complete Catalog (free).

| Address-

For Dealers: Sendyour re turning co Coupled on The sur
DÂVÊY RÂDÎO CÔRPORATUÔY letterhead or card, or this coupon and see will have our nearest

Bar II S Pat Of NEW JERSEY cute with you. BIG LITTLE THINGS OF RADIO

Just the Book You Wanted

"RADIO NEWS" AMATEURS' HANDIBOOK

Cuck ful ét rails constructive au l'autentier articles fron cove a course. Witten by common au la mattein forme de la common au l'autentitée, in plais crevique la geneges which evergine can méteration. Sections include articles on Receiving Sets and Smulph Apparatus, Transmitters and Account and Common autentier de la c

Price \$1.00

EXPERIMENTER PUBLISHING CO., Inc., 53 Park Pl., New York



The S-C CAPACITY ELEMENT

Offers an easy means of obtaining simple tuning.

Be up-to-date!

Make your set a single control. This device can be easily applied

to Roberts, Browning-Drakes, Superheterodynes or any set with two controls. Furnished complete with instructions, template and Martin-Copeland

vernier dial, \$15.00. Without dial, \$13.50 4-TUBE "SUPERUNIT" with

loop and S-C Capacity Element, \$55,00. Three styles. Type A for stand-

ard base, type B for 199's, type C for UX tubes.

HANSCOM RADIO DEVICES WOONSOCKET, R. I., U. S. A.

A GENUINE REMINGTON NO 10

CUT TO \$7065 LIKE NEW



30 DAYS FREE TRIAL

Save more than half your cost on a literally like new! This is the latest Model No. 10, with the exclusive Remington "Selfstarting" feature, the most popular typewriter ever built.

ever built.

The best buy of the year—the biggest typewriter value ever offered. Actual cash asving, \$64 on new machine—\$20 to \$45 on rebuilt. Like new; perfect appearance and working condition. All late improvements: column selector, 2-color ribbon (automatic reverse), back spacer, variable plates release, latest style paper fingers and guide. Up to date in every way, Standard keyboard; \$4 characters. All visible. Will write on a postage stann. Guranteed 5 years, 38 days FREE TRIFAL. Satisfaction or memory refunded. Write for de-tails. A postered will 36.

Cut Prices on All Standard Makes LINCOLN TYPEWRITER CO., Inc.

America's Leading Independent Typewriter House 298 Broadway, New York City Dept. 56 Insure your copy reaching you each month. Subscribe to RADIO NEWS-\$2.50 a year. Experimenter Publishing Co., 53 Park Pl., N.Y.C.

Does a Straight-line Frequency Condenser Exist?

(Continued from page 447)

To make things easier to comprehend values of the inductance ratio were computed from this formula and are shown in Fig. 2. Three curves are shown, all of them applying to inductances of 100 microhenries, one curve for a coil having a capacity of 10 micro-microfarads, one for a coil of 20 and The horizontal axis (at the bottom) calibrated in kilocycles, and the vertical axis (at the left) is calibrated according to the

inductance ratio. Thus, a coil of 100 microhenries having a distributed capacity of 20 micro-microfarads, at a frequency of 1,000 kilocycles (300 meters), would have an in-ductance ratio of 1.087. (Point "a," Fig. 2.) That is, its inductance under those condi-tions would be 1.087 times its true inductance, an increase of 8.7 per cent.

For the purpose of exaggerating conditions, we have assumed rather large coil capacities. It is difficult to conceive of any coil of any of the types now in general use that will have as high a capacity as 15 micro-microfarads. But when we consider the effect of other apparatus in proximity to it, and the additional capacity of the connecting wires, it is probable that it may, in some cases, run as high as 20 micro-microfarads. For this reason we shall consider from now on, for the sake of argument, coils of 100 microhenries having coil capacities of 20 micro-microfarads. Now, remember that the frequency of a circuit is given by the formula:

159.3

as explained above. If we consider L to change, we can easily find out the variation in the frequency that will occur as a result of this change. In Fig. 2 the limits of the broadcast frequencies have been indicated by the vertical broken lines, viz., 550 to 1350 kilocycles. Consider the 20 Auf curve. The values of the inductance ratio at these limits are shown at b and c, and have the values 1.024 and 1.168

In other words, the inductance of the coil changes in the ratio of 1.168/1.024 (or 1.142) in the frequency range 550 to 1350 kilo-cycles. That is, if the inductance of the coil at 550 kilocycles were 100 microhenries, its inductance at 1350 kilocycles would be 100 x 1.142, or 114.2 microhenries. Now suppose, instead of using L in the above formula, we use its new value, which is 1.142 L. The equation will then be:

159 3 = 0.936√1.142 LC It will be noted that the form of the for-mula has not been changed. The part in brackets is the same as that with which we started, the only difference being that we now obtain a frequency which is 0.936 times

the frequency we obtained when we assumed instance, if we happen to have our radio receiver so designed as to tune to 1350 kilocycles at exactly 100 on the dial, without considering the change of inductance, it would actually tune in 1350 x 0.9336 or 1263

This same procedure has been followed out for various values of frequency lying within the broadcast range. A perfectly linear condenser calibration has been assumed for the sake of argument, in the solid line drawn

Motors



Only \$10 Each Ideal for home-made phonographs,

experimental purposes and combination PHONOGRAPH-RADIO sets. We have a limited number of small motors which are greatly under-priced for quick clear-ance. You will never again equal this low price when this lot is sold.

They are universal motors, 110 volts, cycle single phase, complete with turntable, cord and socket for immediate use. 1400 R. P. M. Motor has 1º pulley with flange for ½° flat belt. Housed in highly polished, nickel-plated that

Don't lose out on this remarkable offer. Order your motor today. Tomorrow may be too late. DO IT NOW! Price \$10.00 f. o. b. Steger, Illinois,

Industrial Division Steger & Sons

Piano Manufacturing Company Dept. 60, Steper Building CHICAGO, ILLINOIS

Three "E" Straight Line Rheostat



6-15-30 Ohms. Your Rheostat Reception

detector tube. For there is only one femperature at which efficient reception is obtained and this point is very critical. The THREE "E" STRAIGHT LINE RHEOSTAT g this critical point as no other can. It gives straight variation, runs smoothly, is absolutely NOISELESS. 100 May 100 M

ELECTRICAL ENGINEERS EQUIPMENT CO. Radio Division
708 W. Madison St., Dept. 6,
Chicago, III.
Circulars on Request

The Aristocrat of Rheastats

THREE

PERSONAL STATIONERY 200 SHEETS and \$1.00 Drinted with your Name

Clear, white bond paper, with enrel name and address printed in beautil both paper and enrelopes, and sent only \$1.00. (West of Mississippi U. S. \$1.10.) If incorrected to sen ship C. O. D. Moser returned if y AGENTS MAKE BIG MONEY taking orders

7056 Main Street STATIONERY COMPANY Smethmart, Pa

Insure your copy reaching you each month Subscribe to RADIO NEWS — \$2,50 a year. Experimenter Publishing Co., 53 Park Pl., N.Y.C.

in Fig. 3, by assuming a frequency of 550 to be tuned in at zero on the dial, and a frequency of 1350 kilocycles at 100 on the These points are shown at a and b of Fig. 3, and a straight line was drawn con-necting them. This line represents a perfectly linear calibration.

The points computed as explained above, assuming the coil and associated circuit to have a total capacity of 20 micromicrofarads, were also plotted in Fig. 3, giving the broken curve. There is no doubt that this curve is a curve-it is not a straight line.

But the main point in this connection is that it is not very far from a straight line. The curvature is not sufficient to cause anyone any trouble in separating the many stations, which is the prime reason for the existence of the straight-line frequency condenser, anyway.

HOW CONDENSERS ARE DESIGNED

Let us go a bit further. Suppose the designer of the condenser first determined the approximate shape of the plates by the theoretical method outlined in my article in the August issue of Rapio News, and then put the condenser into an oscillatory circuit. He then measured the frequency that was tuned in at every dial setting and plotted a curve. If the curve was not perfectly straight, he would grind away some of the plate, or build a new set of plates having a slightly different shape. Finally he arrived at a set of plates which gave him a perfectly linear calibra-

The roil he had been using in the measuring circuit was a good one, having low distributed capacity. The problem now is: What will happen if this condenser is used in a circuit with a coil having greater distributed capacity?

The answer is easy. The calibration curve will be less curved than the one we have shown in Fig. 3. The curve ab in Fig. 3
was drawn for a condenser associated with a coil which had no distributed capacity, and we are comparing it with the curve applying to a condenser associated with a coil of con siderable capacity. Certainly there will be an improvement.

The reader must not be misled by the state ments made by those who measure the capac-ity of a condenser at various settings and then calibrate the frequency dial-setting curve from these measurements. It is absolutely impossible to judge the straightness of the calibration curve by this method as, I venture to say, the majority of the condensers will be made by the cut-and-try method, as described immediately above.

There is one other point that may prove interesting to many. Purchasers have in the past been accustomed to demand from the dealers condensers which have low minimum capacities. In the straight-line frequency type of condenser the straightness of the calibration curve will often be destroyed by cutting away the plates in the attempt to obtain a low minimum capacity. This was explained in detail in the September issue of Radio News where an experimental course obtained on a straight-line frequency condenser was prevented.

EFFECT OF CAPACITY

It has been shown above that the curve will be bent downward when the condenser is used in a circuit with a coil having appreciable capacity. It is apparent, then, that the tendency will be to straighten out the curve somewhat, thereby counteracting, to some degree, the upward curvature due to the low minimum capacity

In conclusion I should like to say that, in spite of the fact that we are not able to have anything "perfectly perfect" in this universe of ours, the straight-line frequency condenser is about the best thing that has come





Other Miraco Long Distance Sets 13"

All the Proof you want is waiting for You!

NAME..... ADDRESS.....



100 AMP. RADIO BATTERY Rubber Case

THOMAS WITHERBEE

Shipped direct from factory to you.

Send No Money

This is an actual 100 amp. Radio Storage Battery honestly built of purest materials by real battery builders. Solid Rubber Compartment cases—not wood (non-leakable)—will outlast the hattery itself. Lead coated carrying handle. Wing binding posts.
Will operate the average 5 tube radio set from three to four hours daily for a month to six weeks. NO DEPOSIT or Advance Payment Required

THOMAS BATTERY CORP., 511 West 58th St., New York, N.Y.



along, as yet, in the way of helping us tune in the many concerts on the air. Despite some curvature in the calibration curves, most of them, when actually plotted in a radio receiver, will be substantially straight, and furthermore, it would require a great deal more curvature that we actually do get to cause the confusion among the short-wave stations that has existed heretofore with the use of circular plate condensers.

Radio News Laboratories

(Continued from page 461)

G & S SILK CORE DETECTOR



The G & S silk core detector shown in the illustration was submitted by the G & S Radio Research Laboratory, 1269 Cochran Avenue, Los Angeles, Calif. It is of the adjustable type, arranged for panel mounting. When mounted on the panel it presents a neat and inconspicuous appearance. It would be suitable for use in any radio receiver which requires a crystal detector.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 889.

ERLA CIRCLOID COILS



These coils, submitted by the Electrical Research Laboratories, 2500 Cottage Grove Avenue, Chicago, Ill., are shown in the illustration. They operate satisfactorily as radio frequency amplifiers, covering the complete broadcast wave range.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 888.

KEYSTONE RHEOSTAT



This rheostat, furnished to the Radio News Laboratories for test by the Keystone Radio Company, Greenville, Pa., is rigidly built and may be used satisfactorily in any kind of radio receiving circuit.

AWARDED THE RADIO NEWS LABORA-TORIES CERTIFICATE OF MERIT NO. 927.

ZENITH RADIO SET



The set shown in the illustration was submitted by the Zenith Radio Corporation, 332 South Michigan Avenue, Chicago, Ill This set operates very satisfactorily over the whole broadcast range, reproducing with satisfactory sensitivity, selectivity and quality.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 887.

HALOWAT RECEIVER



The Halowat Receiver, submitted by the Hallock & Watson Radio Corp., 192 Park St., Portland, Ore., is shown in the illustration. This receiver is of the five-tube type of radio frequency amplifier and will satisfactorily bring in stations on the broadcast wave-lengths. It produces a fair degree of selectivity and sensitivity and reproduces without appreciable distortion.

AWARDEL THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 893.



Now-Plate Voltage for any Set—and You can afford it.

First Cost Economy now makes it possible for EVERYONE to obtain efficient "B" current supply right from their electric light socket. Now one of the biggest improvements in modern-day radio reception is placed within the reach of all. Think of it! A perfect, always efficient source of plate voltage for any set for \$9.75! It marks a revolutionary step forward and will be welcomed by millions of radio enthusiasts lions of radio enthusiasts.

Maxmin B"Battery Eliminator

The price of this remarkable new unit is spectacular in more than one way. Besides saving you from \$15 to \$45 it is amazingly low considering the quality and superiority. You may ask "how could it be possible to build such a unit for the ridiculously low price of \$9.75?" True mechanical genius and resourcefulness alone are representable. But the logical ways to approximate the logical ways to approximate the second of the processing the second of sponsible. But the logical way to answer this question is to equip your set at once with this marvelous unit and be convinced.

ASK YOUR DEALER—OR SEND DIRECT

FERBEND Wave Trap

This company also manufactures the famous Ferbend WAVE TRAP —the instrument which has been widely imitat-ed but never equaled. It is the only original and genuine.

Until nation-wide distribution is completed it is possible that your dealer hasn't stocked the MAXMIN "B" Battery Eliminator as yet. So you will not have to wait, we will make prepaid ship-part direct to you work your regist of \$2.50. ment direct to you upon receipt of \$9.75, or C. O. D., plus postage. Remember, superior results are guaranteed or your money back. Be one of the first to own and use the Ferbend MAXMIM "B" Battery Eliminator.

Use the COUPON NOW!

Complete, nothing else to buy.

Operates at maximum efficiency at all times on either direct or alternating current, any frequency.

Delivers unlimited current to any receiving set regardless of number of tubes.

Delivers 100 volts to ANY set.

Cost of operation less than 50c a year.

It lasts indefinitely.

All parts are specially designed and manufactured by us for this purpose only.

Unconditionally Guaranteed

to be equal and superior to any eliminator now on the market, regardless of price.

Ferbend Electric Company

25 East South Water Street Chicago, Ill.

FERBEND ELECTRIC CO. 25 E. South Water St., Chicago Send Postpaid. I am enclosing \$9.75.
Send C. O. D., Plus few cents postage,
Send Literature,

INSULATORS



Perfect your entire installation by insulating your antenna-ground system. Your set is not responsible for energy lost thru a poorly insulated aerial. Use M & M Low-Loss Lead-in and Wall

CLEVELAND, OHIO

CLE



LOW BABY COIL
Smallest Tuning Coil in the World

Size 21/8 x 21/2 in.

FREE Ask your dealer or send us four cents in stamps for wiring diagrams of circuits in which these units can be used.

UNCLE SAM ELECTRIC CO. Plainfield, N. J

Power - Ronomy - Performance pped ready to use! No costly bulbs! No acid funce! its for 110 volt A.C., D.C., or farm plants. Write Distributors! Everybude! Kimley Electric Company, Inc.



Numerous tests have shown that James Blue Bullet will out-perform any fixed crystal for distance, volume and quality of tone. For an idea of 1 lasting qualities read this

the plate steadily for a month. Of other crystals, the first burned out in 8 hours and another in 18 hours. The Blue Bullet has outside them all and is still going atrong, superior to any crystal Five ver had, fixed or otherwise—and I've tried them all."—Kennedy, Oakland, California. James Blue Bullet has been under 180 volt

Ask your nearest dealer for a James Blue Bullet or send to us direct. Postpaid or C.O.D., \$1.00.

STAR-KING COMPANY 200 Davis Street



asiest of all instruments in and one of the mountains. Three first leases at free give you a quie eay start—in a few week you can be playing populations.

Free Saxophone Book BUESCHER BAND INSTRUMENT CO.

Enerothing in Faud and Orchestra Instruments

973 BUESCHER BLOCK - ELKHART, INDIANA

Radio Set Directory

(Continued from base 439)

Trade Name: Biltmore V Reflex Circuit: Reflex Batteries: Dry cell or storage outdoor or loop Loud Speaker: Sens. rate Controls: Three List Price: \$100

Trade Name: Biltmore Master Reflex Model V-C Circuit: Reflex Batteries: Dry cell or Storage Outdoor or loop Loud Speaker: Built-in Controls: Three List Price: \$185

Trade Name: Biltmore Master Reflex Model VI Circuit: Reflex with re-sistance amplification Batteries: Dry cell or storage Antenna: Outdoor or loop Loud Speaker: Separate Controls: Three List Price: \$115

Trade Name: Biltmore Master Reflex Model VI-C Circuit: Reflex with registance amplifica-

Ratteries: Dry cell or storage Antenna: Outdoor or loop Loud Speaker: Built-in Controls: Three List Price: \$200

Manufacturer: BLUE SEAL MFG. CO., 1406 S. Michigan Blvd. Chicago, Ill. Trade Name: Blue Seal tuned radio fre-

quency Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Outdoor or indoor Loud Speaker: Separate Controls: Three List Price: \$135

Manufacturer: G.
BOISSONNAULT
CO., INC.
365 Canal Place
New York City
Trade Name: White-Circuit: Tuned radio

frequency Batteries: Storage Antenna: Outdoor or indoor Loud Speaker: Sepa-

rate Controls: Three List Price: \$35

BRONX RADIO EQUIP. CO. 687 Courtlandt Ave., New York City Trade Name: Breco B. S-3 Circuit: Straight Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

rate Controls: Three List Price: \$80 Trade Name: Breco B.

R. 5 Circuit: Radio fre-quency detector and audio frequency Patteries: Storage Batteries: Storage Antenna: Outdoor

Loud Speaker: Separate Controls: Three BROWN RADIO

BROWN RADIO

MFG, CO.

675 Wyoming Ave.,
Kingston, Pa.

Trade Name: Thorobred Console B-66
Circuit: Tuned radio
frequency
Batteries: Storage or
dry cell

dry cell Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$225

Trade Name: Thoro-bred Model B-88 Circuit: Tuned radio frequency
Batteries: Storage or Antenna: Outdoor Loud Speaker: Sepa-

rate Controls: Three List Price: \$130 Trade Name: Thoro-bred Model B-77 Circuit: Tuned radio frequency Batteries: Dry cell or Antenna: Outdoor Loud Spraker: Sepa-

Controls: Three

Manufacturer: CHEL-SEA RADIO CO., 150 5th St., Chelsea, Mass. Trade Name: Chelsea No. 122 Circuit: Armstrong Regenerative 3-circuit
Batteries: Either
Antenna: Outdoor
Loud Speaker: Sepa-

rate Controls: 1 List Price: \$25 Trade Name: Chelsea

Super-5 Circuit: 2 stages tuned radio frequency de-tector, 2 audio am-plification plification Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

List Price: \$50

Trade Name: Chelsea Console No. 130 Circuit: 2 stages tuned radio frequency, de-tector 2 audio ampli-fication Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price \$125

Trade Name: Chelsea Super-6 tuned radio Super-to tuned radio frequency tuned radio frequency, detector 3 special audio ampli-iner Batteries:

Antenna: Loud Speaker: Sepa-Controls: Three List Price: \$60

Manufacturer: CON-CERT RADIO-PHONE CO. 19:88 Euclid Ave., Cleveland, Ohio Trade Name: Concert Ir. Crystal Set Circuit: Single slider Batteries: None Antenna: Outdoor

Controls: One List Price: \$3.50 (Continued in November issue)



FOR "FANS" OUR new 64 - page Radio Catalog in-cluding all the best and latest Kits, Parts and accessories for broad-cast receiving sets. Lowest prices in the

FOR "HAMS" New 32-page booklet of army and navy transmitting apparatus and miscellaneous specials for "hams" such as W. E. Choke Coils,

More than 1,000,000 fans and hams make our store Walte for olther or both



509 South State Street, CHICAGO, II.I.

The Vacuum Tube Explained



How it was invented. developed and its modern function in the radio receiver.

This book serves an integering study of the fundamental principles, placetand of the fundamental principles, placetand of the version of the serves of the s PRICE 25c

Sold by all Reliable Radio and News Dealers

The E. I. Company 233 Fulton St., New York, N.Y.

E.I.Company

U BRI NICH B PPORTUNITY AD-LETS

Commin. Ten per cent discount for 6 insues, 20 per cent discount for 6 insues, 20 per cent discount for 12 Classified advertising rate twenty-to-cents as west for each insertion. Ten per cent discount for 6 insues, 20 per cent discount for 12 Classified advertising the company and classified advertisments unless placed by an accredited advertising agency. No advertisement for less than 10 words accepted.

Objectionable or mislating advertisements not accepted. Advertisements for the December issue must reach us not later than Oct. 1st.

CIRCULATION LARGER THAN THAT OF ANY OTHER RADIO PUBLICATION

EXPERIMENTER PUBLISHING CO., INC., 53 Park Place, New York, N. Y.

Acents Wanted

Agents Wanted in every city and town to sell st red radio apparatus. Attractive discensis gives. If is sted write us at once stating age and radio experi-tifimington Electrical Specialty Co., Inc., 405 Dela The state of the s

emark, N. J. \$359,00 Monthly selling Radio Direct from fact holesale prices. United Radio, Box 625-A. Gary, Ladii Excellent opportunity for Radio Plan in each County r oppresentative. Good Pay. Pleasant Work, No. deposit required. I Manager, P. O. Ber

Business Opportunities

Make \$100 Weekly in Spare Time. Sell what the red ants—long distance rudb receiving sets. Two cales wee rys \$100 preds. No big investment, no caswasing. Sha Coherado made \$505 in one nuclean, country—write to core. This plan is measured to contry—write to the control of the control of the control of the control of the listen.

Meser.

Quick Soles, Big Profits, selling Little Wooder Haddo
ts at \$2.40° Fully gasaranteed to give wondered results
monor refunded. Great oppertunity, write quick, territer limited. Sens \$1.25 for sample and judge for yourfully for the profit of the control of the content of the control of the control of the content of the control of the control of the content of the control of the control of the content of the control of the control of the content of the control of

Chemistry

Learn Chemistry at home. Dr. T. O'Copor Sicane, not ligator and selessific authority will teach you. Our how only correspondence course fits you to take a position result. See our full page and on page 559 of this issue bentical Institute of New York, 06 W. Broadway, Nerk City.

Correspondence Courses Fee "Home Study Courses" (by mail), write Carnegle

Educational

died Correspondence School courses save over half. Ba in catalogue 1000 courses free. Used courses bough dents' Exchange, Dent. A. 47 West 62d St., New Yor

200-20,000 meter Receiver Zadiots \$25.00. Smill, 12

For Advertisers

24 Words 355 Rural Weeklies \$14.20. Admeyer, 4112-B

Hela Wanted Men to build radio sets in spare time. Lesn Lambert, Detectives needed everywhere; large salaries; free part

Helb Wonted (Continued)

All mea-women, 18-65, wanting to qualify for Government Partition, \$150-500 monthly, write Mr. Ozment, 231, St. Louis, Mo., immediately.

Detectives Needed Everywhere. Travel. Experience uncoccusary. Wife, George Wagner, former Government Detective, 1985 Broadway, N. Y.

Instruction

Learn Chemistry at Home. Dr. T. O'Cence Situane, not-becater and selectific authority, will teach yeu. On most study correspondence course fits yeu to take a possible chemist. See our full page ad on page 353 of the sun. Chemical Institute of New York, 65 W. Broadwa, ew York City. Miscellaneous

Beautiful registered bull pups cheap. Bulldags, 501 orknood, Dallas, Texas. orkwood, Dallas, Texas.

Pearls and Slugs. Pearl hunters should send their pead d slugs by registered mall or express to Herbert H. V. ces, Pearl buyer, Pittsfield, Ill. Lightning Electrolyte, Charges storage batteries in Make it yourself. Guaranteed formula \$5.00. W free circulars. Murphy, Chemist, Talunca, Calif.,

Motorcycles, Bicycles

Old Coins United States 2s Breaze, and bargain Price List 10c. Arcy, Box 483, Muskopes, Okla.

Old Money Wanted

Patent Attorneys

centers—Should write for our Free Guide Books and erd of Invention Blank" before disclosing inventions, middle or shetch of your invention for our Free Innec-and Instructions. Radio, Ricerrical, Chermical, Mo-cell and Problemsk species, Person reasonable, Viktor runs & Co., 22° Ninh, Washington, D. Erans & Ca., 227 Ninth, Washington, D. C.
Patests, Send drawing or model for examination as open to patentallity. Advice and backlet free. High treference. Best results. Prospects se successes source as the Common Patental Lawyer, 644 G Street, N Washington, D. Vashington, D. C.

Patents for Inventions. Long experience, highest gn ork, rates reasonable, best references. Advice as to p stability. Wm. Ashley Kelly, 41 Park Ress, New York Patent-Sense—As one of the oldest patent firms in America we give inventors, at lowest consistent charge, a service need for results, evidenced by many well-known patents of extraordinary value. Book, Patent-Sense, free. Lacey, 62:1–78; W., Washington, D. C. Estib. 1849.

Patente

Inventions Commercialized. Patented or unpatented. Write Adam Pisher Mfg, Co., 278 Enright, St. Louis,

Personal

Lonely Hearts Exchange letters; make interestin, nes lends in our jelly club, Eva Moore, Ber 25s, Jacksonville, orida, Exclose stame

Printing Outfits and Supplies

Bays! Den't Overlook This. The "Rases" Baby D x Greatest decetor ever foreight out with molded Pully adjustable. See throught out with molded Really adjustable. See throw attentioned in this location, or our catalog, the property of the plette See, the same detector with Radicelte Crysta, Te aid. Send for yours today, Radio Specialty Co 96-98 Park Place, New York City.

Make Yeur "B" with Edison Elements. They fetime. Pair 5 cents; welded, 7½ cents postpaid. hazelle. Woodburn, Ore. nagelle, Woodhurn, Ore.

Veory Radie Panel: Grained white "Ivorylite" makes'
santiful set of all. Guaranteed satisfactory. Any
(16 in. thick. 3c per square inch. Sample free. It
te Radie Panel Co., Dept. N, 3222 Ave. F, Fort W. Texas.

Barpaiss Naty Receiving Pubes \$1.00. Shorage Batteries

Body angewer \$4.00, Editon Batteries \$5.00. 221 Neth

Polits in Analyse Strage "6" Batter elements. 9s

Editon Ahaline Strage "10" Batter elements. 9s

Editon Aha Write Lambert first! Dan't buy one until you've rea The Treth About Hadio." Sent free, Write Leon Lam ert, Wichita, Kansas.

Solid Mahogany Radio Cabinets for sale cheap, owen by insteen panel. Address "Factory," Broda, N. C.

Wanted—A 540 watt Transmitting Statles. Give deficition, service embedding process condition and price or 255, Radio News.

Box 233, Radio News. Supersensitive Galena Crystals, pound \$1.60, prepaid Alkemits, All-sensitive Crystals, 56c, Buskett Joslin Ma. Salesmen Wanted

daily selling "World's Greatest Fost-Comfort" to men or boys. Quick sellers everywhere. Just take orders, we mall sbess direct. Bis and repeats. Territory protected. Best season quick, Dept. 231, Easy-Wear Shoc Co., I spolis, Ind.

Oil or Coal.—"The Burning Question," interesting be let, diseases high efficiency low priced residence oil burn Copy free. Write E. L. Miller, Masufacturer Cli Burners, 50 Climax Bidg., Kansas Cliy, Mo.

Skat Sales Agents Wanted. All or Part Time for Ska Hand Soap, Metal Polish, etc. Strictly Commission. To Skat Company, Hartfeed, Com.

A Salesman wanted in every town or city within 25 of a broadcasting station to sell Rediogen, the cor ratio receiving set that retails for \$2.50. With Rad general receiving apparatus, 1,000 cits phose, and avial The changest ratio outlik on the market-year as practite the most expensive. Big success to the right most. Big success to the right most apparatus of the Raddegen Copy, 66-R Broadway, New York City, 1986.

Scenery to Rent

Settings for Opera, Plays, Minstrels, Plush Drops, Ad

Song Writers

Songwriters: Let me furnish the music for ye guaranteeing you absolute satisfaction. Courtight Submit your scripts for estimate and free at. W. Newcomer, 1874 Broadway, New York,

Telegraphy

Telegraphy—Both Morse and Wireless taught ig salaries. Wonderful opportunities. Expe-sance to earn part. School established fifty years ree. Dodge's Institute. Cour St. Valouraine To-

Wanted to Buy

Full Value Paid for Old Gold, Jewe

Put One

Into Your Set



HAVE you been troubled with distortion, due to faulty audio-frequency transformers? If so, slip a Bradley-Amplifier into your set and experience a new thrill in radio reproduction. No special wiring is necessary, because the Bradley-Amplifier is wired, ready for instant use. Send for new booklet "Amplifies without Distortion" today! It explains, fully, the principles of audio frequency amplification and how to improve tone quality.

ALLEN-BRADLEY CO., 287 Greenfield Ave., Milwaukee, Wis.

pact three-tube audio amplifier of the resistance coupled type.

Aside from its faultless tone quality and perfect reproduction, the Bradley-Amplifier is amazingly small in size. All circuits, resistors, and condensers are securely soldered within the base, leaving no exposed parts.

Another outstanding feature is the use of Bradleyunits (Molded Resistors) which do not deteriorate with age nor are they affected by temperature and moisture. The Bradley-Amplifier requires no attention or adjustment.

Bradley-Amplifier

Resistance-Coupled PERFECT AUDIO AM

PRINTED BY GILES PRINTING CO., LONG ISLAND CITY



1-Bradleystat-Noiseless Rheostat for ALL radio tubes.

- 2-Bradleyswitch-Compact Switch for receiving sets.
- 3-Bradleydenser-Low Loss Condenser for sharp tuning.
- 4-Bradlevometer-Perfect Potentiometer for all circuits.
- 5-Bradleyohm-Adjustable Resistor for every application.
- 6-Bradleyleak-Adjustable Grid Leak of highest efficiency. 7-Bradleyunit-Fixed Resistor for Resistance Amplifiers.
- 8-Bradleynier-Vernier Knob, easily attached to any set.



It's a *genuine* UV-201-A only when it bears the name Radiotron and the RCA mark

WD-11, WD-12, UV-199, UV-200, and UV-201-A are the type names of Radiotrons. They belong to Radiotrons only. To be sure you are buying the genuine, look for the name Radiotron and the RCA mark on the base. Then you are sure of quality.

Radio Corporation of America hicago New York San Francisco

Radiotron

REG. U.S. PAT. OFF

AN RCA PRODUCT