RADIO'S GREATEST MAGAZINE



MARCH 25 Cents

Over 200 Illustrations







The AC roay is the modern

UNNINGHAM

0327



X326

For better reception with any AC set, use

#### CUNNINGHAM AC Tubes CX 326 and C 327

These tubes eliminate batteriesjust plug into your house lighting circuit and enjoy modern radio re-ception. It is just that simple.

E. T. CUNNINGHAM, Inc.
New York Chicago San Francisco



"MEN! Here's the 'dope' you've been looking for-

HOW TO GET INTO THE RADIO BUSINESS

# BIGMON in WorkThat is Almost Romance

If you're earning a penny less than \$50 a week, clip coupon now for FREE BOOK! New Book, 64 pages, profusely illustrated, tells all about the Radio profession, thousands of opportunities-in work that is almost romance! YOU can learn quickly and easily at home, through our tested, improved methods, to take advantage of these great opportunities! Why go along at \$25 or \$35 or \$45 a week, when you can pleasantly and in a comparatively short time learn to be a Radio Expert, capable of holding the big pay jobs?

#### Clip Coupon for Free Book

Don't envy the other fellow who's pulling down the big cash! Our proven home-study training methods make it possible for you, too, to get ready for a better job, to earn enough money so you can enjoy the good things of life. One of the most valuable books ever written on Radio tells how-interesting facts about this great field, and how we can prepare you, quickly and easily in your spare time at home, to step into a big-pay Radio job. You can do what others have done through our training. GET THIS NEW FREE BOOK. SEND COUPON TODAY.

J. E. SMITH, Presiden Dept. 3S NATIONAL RADIO INSTITUTE
WASHINGTON, D. C.

Coupon Brings

> Free Book Mail It NOW!

INCLUDED IN COURSE

Instruments shown here and others sent to

our students free of extra cost. CLIP COUPON NOW-find out all about this big unequalled offer while you still have time to take advantage of it. Our training is in-

tensely practical—these instruments help you learn to do the practical work. Receiving sets, from simplest kind to thousand-mile receiver. Many other big features

My Radio Training Is the Famous "Course That Pays for Itself"

Spare time earnings are casy in Radio when you know it the way we teach you. Increase your income almost from the start of your course thru practical knowledge we give you. We show you how to hold the job, then our Employ-ment Department helps you get one. Free book, "Rich Re-

ment Department helps you get one. Free Book, Aucuwards in Radio, "tells how.
Howard B. Luce, of Friedens, Pa., made \$220 in 7 weeks during his stime. D. H. Sultt. of Newport, Ark., write, "While taking the ol carned in spars time work approximately \$900. Was weeking at Radio
Learned in spars time work approximately \$900. Was weeking at Radio
paper time only. Striventer Sense, 507 Elia Street, Kaukanan, Wee, made \$300

THIS COUPON TODAY

Published by EXPERIMENTER PUBLISHING COMPANY, Inc., Publishers of "Radio News," "Science and Invention." "Radio Listoners' Guide." "Amarine Stories" and "French Humer." H. GERNSBACK, President
Member: Audit Bureau of Circulations

Editorial and General Offices. 2 30 Fifth Avenue, New York City

VOLUME 9 MARCH, 1928 NUMBER 9

#### Contents of This Issue:

Custom-Set Building, By Hugo Gernsback 985 A.C. to D.C. and How An Unusual Nine-Tube Peridyne 1018 Encircling the World with a Two-Tube Full-Band Tuning in Radio Receivers, Set. By Armstrong Perry 096 By G. C. B. Rowe 1019 How to Kill Vagrant Radio Noises The Silver Screen-Grid Superheterodyne, What Constitutes Tone Quality? By Ernest R. Pfaff 1020 By Robert Neil Auble 990 The All-Electric Everyman Four, The Listener Speaks 992 By Fred C. Ehlert 1025 Radio-The Alarm Clock of a Nation, The Knowles Screen-Grid Four. By Julia Shawell 996 By Hugh S. Knowles 1028 Radio Novelties About the Globe People and Radio as Seen by the Camera 999 The Pacent Distant-Signal Amplifier, By Gerard J. Kelley 1031 Roasted by Radio, By C. Sterling Gleason 1000 This is 2LO, London, England, Calling, Letters from Home Radio Set 1031 By Dale Pollack 1002 Wisdom for Radio Widows, RADIO NEWS LABORATORIES 1036 By Larry Triggs 1003 Radiotics 1028 The United States, A Broadcast Studio, I Want to Know. By C. W. Palmer 1039 By Joseph Riley 1004 Bridge by Radio, By G. C. B. Rowe 1005 Radio Wrinkles, Close of Prize Contest 1062 Caring for the Socket-Power Units, Australian Broadcast Stations By Charles Magee Adams 1006 The "Screen-Grid" Tube 1074 Broadcastatics 1008 The Girl on the Cover, Caroline Andrews 1075 List of Broadcast Stations 1000 What's New in Radio 1010 A Novel System of R.F. Stabilization A Loud Speaker with Linen Diaphragms 1913 World-Broadcasting-A British Proposal 1078 The Radio Beginner-"Standing By" for Radio "Bugs" "Contact." By L. B. Robbins 1014

#### In Forthcoming Issues:

By Clyde A. Randon 1015

A SHORT-WAVE RECEIVER WITH R.F. AMPLIFICATION RADIO TELEVISION IN THE HOME RADIO RECEPTION AND LISTENER PSYCHOLOGY By G C R Rowe

Repairing Simple Ailments of Radio Re-

By W. Francis Goodreau By Charles Magee Adams

Book Review

ceivers.

HOW TO SUBSCRIBE FOR RADIO NEWS. Senditance to Experimenter Publishing Co., 239 Fifth.

Why Vacuum Tubes Become Paralyzed 1081

The contents of RADIO NEWS are indexed in the industrial Arts Index, copies of which can be found in every library General Advertising Dept., 230 Fifth Avenue, New York City

L. P. McClure, 720 Cass Street, Chicago, IR. ADVERTISING REPRESENTATIVES HARRY DAVIES, DILLON & KELLY, 15 West 19th St., Kunsas City, Mo. T. F. MAGRANE, Park Square Blog., Boston, Mass

NEW

401 Dry Cell Type

BANDBOX

**JUNIOR** 

\$35

# The radio leadership of 1928



Double Unit

170 to 185 volts on the plate of the 171 power output tube. Other radios show from 100 to 110 and 130 to 140 volts on the plate of the output tube. The 171 power tube should have around 180 volts. This better than 40% superiority in one case and 25% in the other is the difference between today's radio and yesterday's.



MUSICONE Type-D \$15

Crosley Musicones are favocess for their taker. This new style is no exception. Its loss price of \$15 is in beeping with Crosley traditions. It instantly demonatested its soundness by im-

# 4cBANDBOX

The Bandboxes are genuine Neutrodyne receivers. Totally and completely shielded, their acute sensitivity and sharp selectivity is amazing. It has a single illuminated dial.

Contributing much to the success of this 1978 wonder radio is the Mershon Condenser in the power element of the set. Not being paper, the danger of its blowing out is entirely removed, so that the desired heavy voltage can be used to produce the acoustic and volume results so greaty desired. IT IS SELF HEALING. It does not have to be replaced as is the case with

paper condensers. The capacity of smoothing condensers in The capacity of smoothing condensers sin Crosley power units is 30 mf. Other sets use only a fraction of that condenser capacity. Undersize condensers, transformers, etc., are used in order to build down to a price. Crosley builds up to a standard. The AC Bandbox is purposely made in two models—the 602 in a double unit—the 704 self-contained. This is to provide maximum

adaptability in all sorts of surroundings and uses.

The 602 double unit provides console cabinet installation in ALL kinds of consoles.

The 704 is for those who want the entire set in one cabinet. The two sets are identical in elements, design, and performance. The physical difference

design, and performance. The physical difference is solely to meet the human differences of task on necessity, and price! The size of the 704 is 17% inches long by 12% inches wide, and is 6% inches high.

Battery Type Bandbox \$55

This celebrated model needs no picture, for in

Battery Type Bandbox \$55

This celebrated model needs no picture, for in appearance it is identical to the 602 receiver pictured above. Its amazing performance has won the radio world this season, and its value is as outstanding NOW as the day it was first presented!

SELF CONTAINED SELF CONTAINED

Approved Console Cabinets manufactured by Showers Bros. Co., of Bloomington, Ind., and Wolf Mfg. Industries, Kokomo, Ind., are sold to Crosley dealers by H. T. Roberts Co., 1340 S. Michigan Ave., Chicago, Sales




Crosley is licensed only for Radio Amateur, Experimental and Broadcast Reception THE CROSLEY RADIO CORPORATION Powel Crosley, Ir. Cincinnati, Ohio Montana. Wyoming, Colorado, New Mexico, and West, prices alightly higher Witte Dept. 22 for descriptive literature

"You're there with a Crosley"

CROSLEY RADIO

#### INDEX TO ADVERTISERS



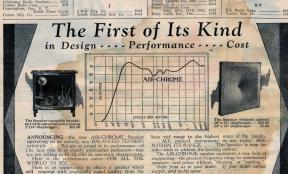

THE AIR-CHROME STUDIOS 168 Coit Street Irvington, N. J.



# \$7500 a week in Your Spare Jime

Do for You

1-Enable you to earn \$3 an hour

upwards in your spare time.

2-Train you to install, repair and build all kinds of sets.

3-Start you in business without

4-Train you for the \$3,000 to \$10,000 big-pay radio positions.

5-Help secure a better position at bigger pay for you.

6-Give you the backing of the Radio Association.

A MEMBERSHIP NEED NOT

COST YOU A SINGLE CENT

capital, or finance an invention.

OINING the Radio Association enables you to cash in on Radio now! Follow its success-proven plans and you can earn \$3 an hour, in your spare time, from the very first. Over \$600,000,000 is being spent yearly for sets, supplies, service. You can get your share of this business and, at the same time, fit yourself for What a Membership Can

#### the big-pay opportunities in Radio.

Founded on a New Idea Members of the Association do not wait for months before they make money out of Radio. Without quitting their jobs, our members are earning \$25 to \$75 a week spare time by building "tailored" radio sets, serving as "radio doctors," selling ready built sets and accessories, or following one of the many profitmaking plans of the Association.

Earned \$500 in Spare Hours Hundreds earn \$3 an hour as "radio doctors." Lyle Follick, Lansing, Mich., has already made \$500 in spare

time. Werner Eichler, Rochester, N. Y., is earning \$50 a week for spare time. F. J. Buckley, Sedalia, Mo., is earning as much in spare time as he receives from his employer.

We will start you in business. Our cooperative plan gives the ambitious man his opportunity to establish himself. Many have followed this plan and es-tablished radio stores. Membership in the Association has increased the salaries of many. Scores are now connected with big radio organizations. Others have prosperous stores.

A year ago Claude De Grave knew nothing about Radio. Today he is on the staff of a famous radio manufacturer and an associate member of the Institute of Radio Engineers. He attributes his success to joining the Association. His income now is 350% more than when he joined.

#### Doubled Income in Six Months

"I attribute my success entirely to the Radio Association," writes W. E. Thon, Chicago, who was clerk in a hardware store before joining. We helped him secure the managership of a large store at

a 220% increased salary.

"In 1922 I was a clerk," writes K. O. Benzing, McGregor, Ia., "when I enrolled. Since then I have built hundreds of sets from 1-tube Regenerative to Superheterodynes. I am now operating my own store and my income is 200% greater than when I joined the Association. My entire success is due to the splendid help it gave.

#### Easiest Way Into Radio

If ambitious to become a Radio Engineer, to fit yourself for the \$3,000 to \$10,000 opportunities in Radio, join the Association. It gives you a comprehensive, practical and theoretical training and the benefit of our Employment Service. You earn while you learn. You have the privilege of buying radio supplies at wholesale. You have the Association behind you in carrying out your


ACT NOW-if you wish Special Membership Plan

To a limited number of ambitious men, we will give Special Memberships that may not—need not—cost you a cent. To secure one, write today. We will send you details and also our book, "Your Opportunity in the Radio Industry." It will open your eyes to the money-making possibilities of Radio.

RADIO ASSOCIATION OF AMERICA,	
4513 Ravenswood Ave., Chicago, Ill.	Dept. RN-3
Gentlemen: Please send me by return mail full d Membership Plan and also copy of you tunity in the Radio Industry."	etails of your Special book, Your Oppor-
Name	
Address	
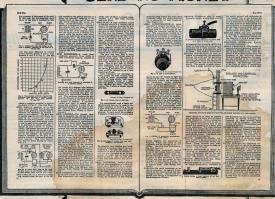
# 20,000 Sold to date

Let me send you a copy
If you do not like it - return it /
SEND NO MONEY



JUST MAIL THIS COUPON ENCLOSE NO MONEY

SIDNEY GERNSBACK, 230-5th Ave., New York. Send me one copy of Södne Gerssbuck's First Radio E cyclopedia in one volume: advertised. I will pay postma \$2.09 plus postage on deliver

Addres

own....

The First Radio Encyclopedia greatly reluced

The Sints Radio Encyclopedia Ever Published

Edited by Sidney GERNSBACK, Editor of "Radio Listeners" Guide and Call Book
(Radio Review)." Author of "Wireless Course in Twenty Lessons".—"One Thousand
and One Formulas".—"Practical Electricity Course"—etc.

The most of shannels was very considerable to the constraints when the constraints was used in the constraints was used to be constraint of the constraints and constraints and constraints and constraints and constraints was constraints of the constraints and constraints was constraints of the constraints of the constraints was constraints when the constraints and constraints was constraints of the constraints which constraints and constraints was constraints when the constraints was constraint to the constraints which constraints was constraints which constraints was constraints which constraints was constraint to the constraints which constraints was constraints which constraints which constraints was constraints which constraints which constraints was constraints which constraints which constraints was constraints which constraints was constraints which constraints was constraints which constraints which constraints which constraints was constraints which constraints which constraints which constraints was constraints which constr

#### REMEMBER

described and illustrated in this volume can be found in any dictionary, or any other encyclopedia.

S. GERNSBACK - 230 Fifth Ave., New York, N. Y.

# ACHIEVE SUCCESS IN RADIO

### New course gives finest instruction obtainable You can learn at home!

Good pay from the start, rapid advancement, and phenomenal success-a life profession of fascinating brain-work—that is what Radio holds for the man who knows his subject thoroughly. Right now on Mr. Duncan's desk there are letters from hig radio companies offering employment to RIA graduates.

Since 1909 Radio Institute of America has trained thousands to become successful in the many branches of Radio. Are you going to plod along at a thirty-five dollar a week job when REAL MONEY is waiting for you in radio?

#### New course finest ever

Prominent radio men have enthusiastically greeted RIA's new course as the most complete and up-to-date offered today. All this first-quality equipment is furnished FREE WITH THE COURSE-parts for making many practical radio

circuits and the Peerless Signagraph for code instruction.

#### RIA backed by RCA, G-E and Westinghouse

You get all the benefits of instruction conducted by RCA and sponsored by RCA's associates, G-E and Westinghouse. Our employment department is at the service of graduates.

#### Study at Home

Moreover you can STUDY AT HOME - when you please and as long as you please.

> This new informative booklet describing the course is just off the press. If you want to learn more about the well paying positions in this fascinating

profession send the coupon now for your copy. No obligation.

RADIO INSTITUTE OF AMERICA, 326 Broadway, New York City

Dept. A-3

Please send me your new catalog. I want to know more about your new radio course

326 Broadway, New York City t. A-3



Mr. R. L. Duncan, Director

port of the Radio Corporation of America in your work of

(Signed) J. G. HARBORD.


Radio Corporation of America

President.

Dear Mr. Duncan You have the heartiest sup-

radio instruction.

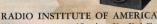FREE WITH COURSE all this first-quality equipment for experimental work—all the parts to build many practical radio circuits, the Peerless Signagraph for code instruction.



"Try this on your piano"

only

Here it Is!

The Loudsbeaker Sensation of 1928 of course

it's an



Simply attach the ENSCO piano unit to your piano and the cord to your radio set--it only takes a minute--and you have a marvelous, resonant loudspeaker.

This wonderful device makes use of the perfect sound-reproducing qualities of the piano soundboard. It took years to develop the piano to its present state of perfection, and you can now enjoy perfect radio reproduction by using this sound-board.



It doesn't show-it does not mar the piano in any way or interfere with its use as a piano. Fits any piano, grand or upright, and works on any radio set.

The reproduction is simply marvelous. The sonorous bass notes, the rolling notes of the middle register, and the thin, sharp tones of the upper treble—all perfect—and the voice sounds natural. The famous ENSCO drive mechanism the rugged direct-drive, distortionless unit developed by Clyde J. Fitch, makes this possible. It is new, and the results will surely astound you.

#### MANY NOVEL APPLICATIONS

Musical furniture is now a reality. Imagine the dinner table, surrounded by guests, bursting forth into glorious song, a chair or bridge table telling a bedtime story, or a door or panel singing a baritone solo! All this is made possible by the ENSCO piano unit. It is made by the makers of the famous ENSCO cone speaker kits under U. S. Patent No. 1630199 and others pending.



The Best \$10 You Ever Spent!



If you do not have a piano, use it on the table or a panel, or door. It works!

Sold under money-back guarantee. You must be satisfied or your money will be refunded. Price only \$10.00. Complete with 20-foot cord. Ask your dealer or send order to our nearest office. Shipped prepaid on receipt of check or money order or C. O. D. with postage added.

Price in Canada—\$11.50

25 CHURCH STREET NEW YORK

ENGINEERS' SERVICE COMPANY 28 E. JACKSON BLVD. CHICAGO, ILL.

331 BAY STREET TORONTO, ONT



Editorial and General Offices, 230 Fifth Avenue, New York

Vol. 9 MARCH, 1928

## Custom-Set Building

By Hugo Gernsback

DVER since radio became popular, the vogue of the home-built set has shown a gradual but healthy increase. When to buy read-scating first starfed, it was impossible, in many cases, to buy ready-made sets, because at that time there were none to speak of on the market. It took several years for set manufacturers to develop the multi-tube set and, in the meanwhile, radio constructors and amateurs all over the country were making their own.

When ready-made sets did finally come along, in overwhelming numbers and at practically all prices, home set building naturally took; as et-back. The incentive for people to build their com was now in horm alone and the properties of the properties of the now is horm alone as the "exastonest buildier," has not vanished, by any means. Quite the contrary; his tribe is increasing steadily. For reason is not difficult to explain. In the first play, it should be understood that the rabbe contrary; his tribe is increasing steadily. For the properties of the properties of the properties of the tenders of the properties of the properties of the properties of the fermin, and of said. In the teve classes of the custom-set buildier builds not only for himself built rather, for the friends, and for said. But the vectoses of the custom-set building, whether for profit or for one's own amusement, remains practically, the same.

Bul, particularly in the radio art, which is comparatively so new, practiculty every day, brings along new inventions and improvement of the properties of t

If a new circuit is described in Rasso News, or other rando publications, there are upwards of 20,000 olividebals in this country in the property of the property of the country of the property of the property of the property of the who also know about the latest improvement and clear to have such sets, but have nother the time nor the inclination to load as the property of the property of the property of the such sets, but have nother the ince nor the inclination to load as the butter who as a radar relate a profit from the transaction. It is easy to see that there is an excellent committee justification market of such as the property of the property of the property of market of such as a property of the property of the property of market of such as a property of the property of the property of market of such as a property of the prop

For instance, as very frequently happens, a man has a special coincia, a bookers, a phoneparty mondo, or a special deset, in which he does not be a special coincide of the sp

special radio installations and, in this respect, the custom-set builder performs the same duty as the body builder when a rich man gishes a special automobile built to fit his requirements.

A number of case that have recently come to my attention might very well be mentioned. There was one of a militonier on Park very well be mediated and the same of the second of the saw wired that every room could have an outlet for a radio loud pedaler. But that was not all, the requirements were that more of the same a single receiver could not do this; so a custom-set builder was a safel receiver could not do this; so a custom-set builder was called in, and one set was installed in a Louis XIV islaid cubined, in the library, and had to be built into a sectional bookcase. As withing arrangement was provided, so that every boul speaker. This was a special requirement, and unusual; but the custom-set builder did a notal job.

builder did a nest Job.

In a well-known New York restaurant, a custom-set builder was called in to she another unusual job. The requirements included as well that lone would show. Furthermore, complete year was recorded to fill the entire restaurant, which is of a tremendous ties, with a good volume of music. It was cherical, forthermore, consignation of the contractive state of the contractive state on the market could possibly have been used, because of the environment of the contractive state on the market could possibly have been used, because of the environment of the contractive state of which had also to be amplified to a high degree to deliver randicard unit, in the certain of the custom-state builder who

completed the Job, be accomplished a most satisfactory installation. Then, or course, there is always—and this applies more to the country than to the edy—and by the property of the country than to the edy—and property of the country than the edy—and the property of the country than the edy—and the country of the countr

Mr. Hugo Gernsback speaks every Tuesday at 9.30 P. M. from Stations WRNY (356 meters) and 2XAL (30.90 meters) on various radio and scientific subjects.

# ENCIRCLING the WORLD WITH A TWO-TUBE SET

A LL who have been holding records for long-distance reception of broadcasts, and those whose imaginations have plons, now can retire from the limelight. Walter Rodman Pierce, Jr., a 17-year-old boy of Saunderstown, Rhode Island, seems to have all the other known DX artists backed completely off the beards with a When Pierce's friend and brother 'hann,"

Franklin B, Rowell (IAMU) of Pawtucket, told me at a recent New England convention of the American Radio Relay League that Pierce was receiving broadcasts from Japan, the Philippines, Australia and other countries in all parts of the world, on two tubes, it sounded like the result of a superheated inagination. But Pierce appeared to be an honest young man; and he gave me from memory the call letters and locations of so many stations that he said he had logged, that I knew he must have either heard most of them many times or else spent most of his time memorizing the call.

spent most of his time memorizing the call books.

He said that he had letters and cards from many of these stations, verifying his reception. Still, his record was so remarkable, so nearly incredible, that I decided

to visit his home and see the evidence before making any unqualified statement. Several months later I visited Saunderstown. Pierce's home, I found, was a farm back in the woods. A grocer on the highwith him and with members of the boy's family while I waited for the boy to come home from school. The house is in a good radio location, on a hill that rises west of Narragansett Bay, opposite Newport. Pierce's receiver is a Radiola III, a twotube set which was well known a few years

Frere's Federics is a frauma if, a twotube set which is now entired or ago, but which is now entired or ago, but which is now entired or in the living room; it was booked up to three dry fells and two 45-volt "B" batteries. He was using tubes of the 198 Literles. He was using tubes of the 198 Literfor which the set was designed.

#### ELABORATE GROUND SYSTEM

From the looks of the outfit, I would have said that New York would have been DX for it; but outside the window there was something unusual. The wire that led from the ground eminection on the receiver out through the window cutout at a point party wires led to the same number of pipes or other pieces of metal embedded in the ground (see Fig. 1). Pierce said that he found that each new ground connection increased selectivity and rethered the effect another, which was the property of the pieces of the

A leaky automobile radiator was such in the ground, at the end of the row of pipes, with its cap just above the surface so that water could be poured into it. Circumstances after cases. On a car, that radiator, could only have inspired profamity; ground connections wet. The ground clamps on the pipes were bright. Pierce said that he put on new ones every few weeks. It became evident that his phenomeal record

became evident that his phenomenal record was not the result of accident.


The aerial is 110 feet long and 26 feet



Walter Pierce going over his ground connections, a pictorial diagram of which is shown on the following page

987

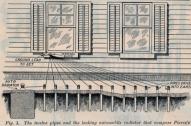swered his letters, but their replies were somewhat indefinite He has many verifications from stations in the United States and Canada, from coast to coast, but he considers nothing as real DX except reception from another continent or its islands.



ground system. The radiator keeps the whole ground system moist.

high; it points N. N. E., with the set at the southerly end. Two glass insulators in series at each end prevented the escape of energy. The wire was of bare copper which, Pierce said, gives better results than tinned copper. He puts up new wire to replace the old every few months, or as soon as corrosion becomes noticeable. The acrial is kept taut, to prevent swinging.

#### ACROSS THE OCEANS

It was still daylight, though late in the afternoon, when I sat down at the receiver. As soon as the tongue of the rheostat touched the first turn of wire, a station jumped at me. So many came in as I turned the knob that I advanced it only an eighth of the way to the maximum setting. These stations were within a radius of about 200 miles.

Pierce took charge of the set and turned the rheostat knob to the maximum position. There was another rheostat at the batteries, adjusted so that it was impossible to injure the tubes by turning the one at the set too far. Almost immediately he brought in 2LO, London, England!

When we tired of tuning in stations, we took off the phones and cut in the loud dence and New York stations came in with volume enough to fill the room and be heard anywhere in the house. Like his phones, his loud speaker is a standard device, of a kind sold in most radio shops. There is not a piece of apparatus in the whole outfit that is of special design or expensive. Pierce is a farm boy, attending high school, and has little money to spend on luxuries. He said he had used the same "B" batteries for two years.

After a night's rest, we rose at early dawn and went back to the set to listen for stations on the other side of the earth-Station 1YA, Auckland, New Zealand, was one of the first to come in. The carrier wave was strong, but the music and announcements were weak. An orchestra was playing. When it stopped, the announcement "IYA, Auckland Station," was heard. This was between 5:35 and 5:37 A. M., Eastern Standard Time, on November 1, 1927. The announcement was logged again at 5:45.

including JOCK, Nagova, and JOAK (no joke!), Tokio, Japan, and 2YA, Wellington, New Zealand, were recognized by their carrier waves. The average broadcast listener may doubt the ability of any person to identify stations by the sounds of their carrier waves; but some may have discovered, as Pierce did, that it can be done, For two years he has operated his set several hours a day, fishing for distant stations. He knows his dials as a navigator knows his compass. He knews the schedules of many of the broadcast stations. He can

A number of stations in the antipodes,

start at zero on the dial scale and tell what station he is going to bring in at each mark, and between the marks. While a station 10,000 miles away was coming in near 4 on the scale, WGY, Schenectady, was working on a wavelength very near it. Pierce separated them, and after seeing him do it, I did. His set increased its selectivity as he added extra ground wires and, as his mother says, he can "adjust the tuning

#### SOME OF THE FOREIGN STATIONS

Among the stations outside of the United States and Canada that Pierce has logged. many of them several times, are:

speaker); 8JQ, Santiago de Cuba; 6HS, Santa Clara; 7BY, Camaguev

Clary 179, Canageres.

Clary 179, Canageres.

Hallis IIII, F. ten us Prices.

Ballis IIII, F. ten us Prices.

Sand Arevier CIAG. Sandage, Odler 90,

John 199, Canager Permandon, Brack

Cong. Massersko, Onemary Permandon, Brack

Alexa, Argentias; COOR, Mastroide, Urquery

CAG. Valgarinia, Cool, P. Danson, Angulia, CAG.

Alexa, Argentias; COOR, Mastroide, Orquery

Argentias; LOW, Bornos Alter, Argentias; CAM,

Argentias; LOW, Bornos Alter, Argentias; CAM,

Argentias; LOW, Bornos Alter, Argentias; CAM,

Canagerias; COOR, Masterdan,

Canagerias; Cooperation COOR, Masterdan,

Canagerias; CAG. Sandage, Masterdan,

CAG. Sandage, CAG. Sanda

(Continued on page 1048)



Walter R. Pierce, Jr., tunes the Radiola III with which he hears broadcast stations in all parts of the world. This set is no longer on the market, and inquiries for its circuit data ... cannot be answered.



Some of the radio noise-makers. Top row: electric flat iron with poor contact or defective resistance; flashing signs or flashers in window displays. Bottom row: electric heating pad, sparking motor, railroad signals, faulty connections in lamp leads.

E would be willing to wager a goodly portion of the munificent weekly stipend that, if you were to inquire casually of a radio fan what caused the fump little noises in his set, he would make one of the two answers; viz: Answer No. One: "Static."

Answer No. One: "Static." The Other: "A leak in that doggone trans-

former on the post in the allegs."
Such a simple disposition of a difficult problem! Surely no other solutions could appeal so strongly to such a variety of numbs. Somehody or other spec there simple must be considered to the surely of the

on the part of a great deal of engineering brains, it was discovered that Grandpapa Statie is innocent of a lot of crimes for which he had been blamed. After a lot more research, these same engineers ascertained that, in most cases, the people who made complaints were in the same class with the dog who sat on his own tail and howled, but was too laxy to move.

It was the consensus of expert opinion that, with the home-brew-noise industry getting along so nicely, natural static might as well be put on a sled and started on the well-known road to oblivion. A man with the hives, you know, doesn't do much kicking over a mosquito hite.

#### INTERFERENCE AND INTERFERENCE

As this sub-title indicates, and as those of us who get more or less enjoyment from listening to radio programs should be fully aware, there exist two kinds of interference. A type which is, happily, confined to the vicinity of large cities is the spirited interference of one broadcast station with an-

other and makes itself known to the listener by a beautiful whistle in the background of the music, instead of the more conventional bass. The only remedy that comes to mind at this moment is either several sticks of well-placed dynamite or aggressive activity on the part of the Federal Radio Com-

On the other hand, if the sounds that float gently out from your loud speaker seem to be a cross-section of a kitchen working overtime frying eggs, with attendant crackles, hums, moans, roars, sputters and what you will-then this is something else again and there is a good chance that the noises can be chased down to their lair and killed. Of course, it would not be right to assume that all the noises come from within the home-for that above-mentioned transformer in the alley might be to blame; but the chances are that, if a little intelligent thought and work is put on the problem, the source of the noises can be tracked down and will be found within your own four

## MAKING INTERFERENCE AT HOME The list of noise-makers that are in the

walls or those of a neighbor.

equipment of the average modern electrically-equipped home is far too long to be here included. However, take heart, radio fars, and read on jfor, although these noise-makers are numerous, yet it is a simple through the properties of electricity, or possess a thick protections, the properties of electricity, or possess a thick protections, the properties of electricity, or possess a thick protections, the properties of electricity or possess a thick protections, the properties of electricity is not provided to the properties of electricity in the properties of the

It should be stated again that "the doggone transformer out in the alley" is usually about as Inuch of a source of radio noises as the munnny of one King Tut recently found in his old family centerry, west of the waterworks in his home-town. To the radio public in general it may seem logical that power companies should burn coal in the power house, at its present prices, just for the fun of pumping current through holes in the lines to ground. But they don't. They would much rather sell electricity than broadcast it.

Some of the real offenders have been classified by the National Electric Light Association, as follows:

Power Cincurs: (1) lines; (2) insulators; (3) lightning arresters; (4) transformers; (5) generators and motors; (6) induction voltage-regulators.

INDUSTRIAL APPLIANCES: (1) are-light circuits; (2) telephone and telegraph lines;

(3) pole changers and converters; (4) street cars and electric railroads; (5) smoke and dust precipitators; (6) motors; (7) sign flashers. HOUSEHOLD APPLIANCES: (1) electric

HOUSTHOLD APPLIANCES: (1) electric pads; (2) violet-ray machines; (3) flatirons; (4) doorbells, light-switches, various small motors.

MISCHLANDOTS (1) X-ray machines; (2) storage-battery chargers; (3) annunciator systems; (4) stock tickers; (5) ignition systems; (6) electric elevators and electric furnaces; (7) moving-picture equipment; (8) high-voltage testing equipment. This list covers in a general way most of

the field of housefold and industrial noise makers; but, if it were not for the lack of space, further classifications might be made; for exomple, under the heading of heating pads might be included all those devices, which are operated by some sort of an electrical thermostatic control; with finitense resistance-wire heaters, and as carring irons, percolators, walle-griddles, etc. Now, as has been suggested, much work

has been done on reducing the output of these non-licensed broadcast stations and in due time the secrets will be unfolded to a panting world and illustrated by rare old Sargents with crosses marking the spot where the body was found. We have in-

# rant Radio Noises



Automatic telephone dials; bad contacts in light sockets, thermostat controls on oil burners, contactors on farm-lighting equipment, dirty commutators on motors, leaky transformers, are among the sources of interference.

timated that the method of bomb-tossing is a bit too crude for this advanced day and age and should be left to those nephews of our National Uncle who get their thity bucks a month for doing just such little odd jobs. We shall try to-shant to Oblivion, Gehema and other way stations the huns, creakles and other, noises that were given

#### RECOGNIZING THE NOISES

to the radio fan for his sins.

Some bright student of the class might at this moment get up on his hind legs and pipe, "But how the-pardon me, how on earth are we going to tell where a hum comes from and where a crackle has its home?" Sit down, Oscar, and incline your car this way and you will get an idea (if

Suppose you hear romping through your loud speaker, a rice, low, deep hum sounding like a note pulled out of a bull fiddle by the long-haired gentleman in the orchestra pit. Such hums, which are sometimes in line carrying 60-cycle alternating current, may also be among those present through the medium of power-gaupty units with defective rectifier tubes or bul filters. A usually bring such a hum to nontern

The unwanted voices of the violet ray and X-ray machines are pitched deeper and have the added characteristic of sounding like a neighbor's winter supply of coal going down the chute into his cellar. Similar to these sounds are those of a wild and undomesticated battery charger.

Another type of grating sound is caused by spark interference, although this has sometimes a high-pitched note accompanying it. It is generally intermittent. Also intermittent is the noise from a thermostatic control, like those of some types of electric tymes.

Crackling noises can generally be traced to defective contactors, loose wiring connections and bad sockets. A crackle with a steady hum indicates a dirty commutator on a nearby motor.

Of course, it is mighty difficult to differentiate between the fine graduations of tones which might mean an entirely different source of interference; but each annovance has, and sticks to the bitter end to, its own net note which we shall soon attempt to describe. The experienced trouble-shooter should know his notes, as well as the piano tuner knows the difference between middle-C and G sharp; but this is small consolation to Mr. Average Listener, whose affronted ears only tell him that his loud speaker is snarling at him. However, one need not be a grand-opera singer or a performer on the fiddle to track down the clusive interference. The methods are simple for the most part.

#### ON TROUBLE'S TRAIL

One of the first things that the trouble shooter should implant firmly, away in the back of his skull, is that the power company has not concected a plot to amony him early time he hears a queer noise in his Jonal gauling fast thrust ruddy in the "jimarads" of a receiver is the cause for bent condenser plates; and plates that books and therefore sometimes apark are every lift as potent a wandered up a street.

And then batteries can play a little tune

all their own. Corroded terminals in jacks and battery elips, corroded socket contacts and tube prongs do their stuff nicely. An excellent imitation of a 50-cycle hum is caused by an open elecutin the audio amplifier. Did you ever hear a defective grid leak fry and sputter? Well, they do. And above all, loose connections will let loose as nice an assortment of noises as has

ever been your lot to listen to.

There has been much published on the subject of trouble-shooting in the mazes of a receiver and we will skip blithely over that

with this admonition: look carefully over your various batteries and socket-power units, connections fore and aft, test your tubes, for contacts and microphonic noises, your switch and jack springs, and the loudsneaker cords.

#### GADGETS AROUND THE HOUSE

If Sister is getting all dolled-up to go to a party and the curing iron, the violet-ray machine, and the flation are all working overtime to add her, and if these various objects are doing their level best to drown out whatever music—if any—is tricking out whatever music—if any—is tricking to be load speaker, don't speak you can be allowed to be a superior of the control of the

After sister has succeeded in waking up here by friend, who has here waiting "just five minutes"—has it ever happened to you?—turn off all the trouble makers and then turn them on one by one and see which one is making all the fuss. If one kicks up a rumpus, first inspect the light socket from which the appliance is getting its power. The contact in there may be lad.

Of course, some cases may not be so

simple to trace and it may be necessary to resort to a small portable set using a loop antenna so that its directional properties can be used. But let this word of caution sink in: be sure that the trouble is not in your own house before you go snooping around some neighbor's domicile.

Suppose that you have traced the trouble to a motor which is merrily sparking; in most cases this is due to dirt on the commutator, causing the brushes to make had contact and resulting m a spark jumping to them. This will m time pit the commutator, and this result will not help to reduce noise. First clean the motor, and

if the iron frame of the motor is not con-(Continued on page 1044)

# What Constitutes Tone Quality?



A Clear Explanation of What Sound Really Is, How It Is Produced, and Why Similar Notes on Different Instruments Sound Differently



By Robert Neil Auble

UCH has been printed in the last few months, in radio journals and radio advertising elsewhere, concerning the quality of tone to be expected from a given loud speaker or a particular radio set. Until about a year ago the whole emphasis had been placed upon the merits of the various circuits, the methods of coupling various stages of amplifiers, and such other technical matters of radio design. From a selling point of view, the change in emphasis has been wise; because very few users of radio sets nowadays care to spend any time in mastering intricate principles of design; on the contrary, they want the manufacturer to build a dependable radio at a price within their means.



As the vibrating reed motres toward C (1) a condensation is produced at C and at the same time a rarefaction is produced at R. As the reed returns to its first position (11), the air is condensed in the region previously rareful, and ararfed at the point volver it was condensed, and the point volver it was condensed. Condensations and varietaclions used careact, Condensations and varietaclions used through the air a sound towers, a shoom in III.

If the product is a musical instrument which gives reasonably satisfactory entertainment, the buyers do not complain.

The aslessman who talks circuit and radio design to such non-technical prospects is likely to frighten away his customers; because not only do few men care to admit popularized terminology of radio, but the mention of inductances, potentiometers, et cetera, also leaves the impression with the average man that the set in question is too average man that the set in question is too many possibilities of trouble requiring the services of the expensive expert. The popularity of the property of

t larity of "one-knob" sets, with a minimum of gadgets and thingumbobs, and with the "works" safely concealed beneath a subpanel, has a firm basis in American psychology.

#### THE CRY OF "QUALITY"

A new difficulty for many has been introduced, however, in the phrase "quality of reproduction." Those of us who have

In this article Mr. Auble explains interestingly the physical basis of the rounds which form music and speech and the method of their production; thus pointing out some of the complications which must be dealt with in their transmission and reproduction by radio. Part II will deal with load speakers and show some ingenious novelities.—Eurros.

"grown up" with radio slave long since learned to onjoy radio programs, because, even though the reproduced program may or may not be faithfully like the original, it is sufficiently pleasing in Beeff; so that any the sufficient of the sufficient with the sufficient to the sufficient with the sufficient with the displeasure—we marred at what we do get But anories at radio learning but the condunate which is excellent if junged by engineering standards, with the statement, as the sufficient with the statement of the temperature of the sufficient with the statement.

Much of the present-day literature of radio, dealing as it does with the quality of speech and music heard at the loud speaker, wrongly creates the impression that the quality of lone of the music is a particular function of radio devices. Nothing can be farther from the truth.

It must be borne always in mind that radio devices, from the microphone to the

loud speaker, are instruments for the reproduction of sound and do not in themselves, accept as inherent faults in the apparatus itself may bring about changer, have anything to do with quality. Radio music cannot improve upon the original, any more than can any other reproduction in nature. Indeed, the copy is best when it is most nearly like the original, regardless of faults in either original or copy.

Since so much emphasis has been given to this factor of quality of tone, it seems appropriate to explain in general terms what the physical basis of quality is, and to show the part played by radio transmitting and receiving units in modifying quality.



The same note produced by two instruments, showing by waveform the difference in the timbre,

WHAT ARE SOUNDS?

Sounds always originate in the vibration of some material substance, such as a vibrating wire of a piano or a violin, or a vibrating air column within a fute or an organ pipe, etc. As such substances vibrate, the such as the substances vibrate, the substances with the substances of the substances, due to the clastic column at the fair, are carried to the ear; where they preduce a to-and-fro movement of the car drawn and give rise to the sensa-

The height of waves in Fig. 2 indicates londness; their width, frequency or pitch.
Fig. 4 shows the someoster or "monochord," which consists of a wive stretched by lever A across a thin-walled hollow box. The effective length of the twice is varied by moving the bridges b and by moving the bridges b and

bi along the box.

MMMMMMM

SOUNDS IDENTICAL IN
LOUDNESS BUT DIFFERING IN PITCH

mmm

WWWWW SOUNDS IDENTICAL IN


SOUNDS IDENTICAL IN PITCH BUT DIFFERING IN LOUDNESS



tion which we call sound. If the original withrations are perfectly periodic (i.e., if the withrations are repeated at exactly equal intervals of time and with equal intensity) we call the resultant sound a musical sound or tone. If the wibrations are irregular and non-periodic we call the sounds noises. Both musical sounds and noises must be

transmitted by radio and reproduced by receivers. The problem is rendered much more difficult by the fact that noisessounds from drums, cymbals, the consonant sounds in speech, etc .- are exceedingly complex and difficult to reproduce,

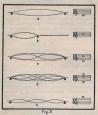Sounds may differ from each other in three respects, viz., pitch, loudness and quality. If the sound waves-the condensations and rarefactions in the air-be represented like water waves, the differences in



Showing some of the simpler ways in which a stretcked toire may vibrate. In a is shown the form of vibration (vibration limits) of a wire sounding only its fundamental note. In b the kalf-segment vibrating gives a tone an is shown vibrating simultaneously to give its fundamental and the first overtone, or second harmonic. In a fundamental, first and second overtones are shown, while in e the second the wire is plucked or bowed at the middle of

inal

1280 1441 1600 1706,6

2048

gni 9th Harmonic

2016

2880

Frequency

Frequency 512 576 600

Frequency

Bundamental

let Harmonie

2nd Harmonie

5rd Harmonio

4th Harmonic

Frequency

Prequency 1556 1728

Frequency

5th Harmonie

6th Harmonic

7th Harmonio 0=

8th Harmonie

Prequency

Frequency



The various patterns formed by particle vibrating plate (Chladni's figures).

pitch and loudness may be shown as in Fig. 2.

It will be observed that sounds differ in pitch when the number of vibrations produced in a given time interval varies. The frequency of vibration for the production of "middle C" (physical pitch) on a piano is 256 vibrations per second, while its octave tone C1 is 512 vibrations per second. Sounds differ in loudness when the force with which the air is disturbed differs. Increasing the force increases the loudness, and vice versa.

#### QUALITY OR TIMBRE

Quality is determined by the manner in which the source is vibrating. It is from difference in quality, or timbre as it was formerly called, that we are enabled to distinguish between musical instruments, or between voices. For example, no one would confuse a clarinet sounding middle C with a piano sounding the same note. The wave forms of middle C for the two instruments are shown in Fig. 3. The pitch of the principal component of the two sounds is the same, and the loudness is the same; but there are characteristic differences in the

> 426.6 480 512

2155.5

2986.6

3413.3 3840 4096

4266,6 4800 5120

tabo 1556

2400

2880

1024

768 855.5

3456 3840 4320 4608 wave form. These differences give the two instruments their distinguishing characters and identities.

If quality depends upon the manner in which the source is vibrating, it is at once evident that the disturbances of the air produced by the piano wire are not like those



produced by the clarinet; even though the two are alike in intensity and fundamental

frequency. To get a more accurate idea of differences

in quality, it is possible to visualize the vibrations of a stretched wire; or the reader may try the experiments with a string on a 'cello or a guitar. The experiments to be described are very simple, but at the same time very instructive. The device shown in Fig. 4, known as a "sonometer" or "monochord," consists of a thin-walled rectangular box about a yard long, upon the top of which is stretched a steel piano wire. The tension upon the wire is produced by means of a weight hanging from the lever A. Two bridges (b and b') are arranged to slide along the box in contact with the wire; thus enabling the experimenter to vary the vibrating section of the wire, within the limits of the length of the box. The tension should be adjusted so that the full length of the wire gives a tone approximately middle C; though this adjustment is not essential to the success of the experiment. If the wire be plucked or bowed at its center a full, rich, mellow tone is produced. Assuming for convenience that the wire has been tuned to middle C, then the tone just heard is middle C. The wire may be seen to be vibrating, somewhat as shown in Fig. 5 at a. This tone is called the fundamental note of the wire and is the lowest tone the wire can produce under the given conditions of

length, tension, etc. (Continued on page 1047)

• The frequencies so marked do not correspond with the frequency of any whole time. In some cases they agree approximately with the half-time. If concen-nace is most perfect when the interval ratios are the smallest whole numbers, it is clear that came of the harmonics will produce disconnece with the fundamental unless they be quickly damped out.

TABLE OF HARMONICS OF THE MAJOR SCALE

682.6

1024

2048

2589.5

2750.6

3413.3

(Physical Pitch)

520 341.3

R

960

1980 1365.3 1934 1706 6 1920 2048



#### Your Radio Entertainment Is Your Receipt

Editor Ranto News. I am very much interested in the article in the November issue, under the caption "Applause." I think that the artists and sponsors of these free programs should know that their programs were received and enjoyed. I have given this matter careful consideration, and find that when the radio listener does write, it is hardly ever that he receives an answer. I have taken this matter up with my friends, and we have come to the conclusion, "Why write, when we never know that our letters are read?" How do we know but that our letters are tossed carelessly aside and never read? In a recent test, I found that after I had written fifteen stations, only one sent me a reply, and that was KGO. Oakland. I have written that station several times, and they sent me a reply each time. I also received a prompt letter of appreciation from a foreign station that I had received. I would rather spend my spare time writing to stations outside the United States and know that they were appreciated, than to write to nearer stations and never receive a reply. I think that if the stations would send a verification card, or even a postcard, probably all the listeners would

> HARRY DUNCAN, 126 South Elm St., Nevada, Mo.

(Unfortunately, most listeners-in, like Mr. Duncan, do not realize the narrow margin on which broadcasting is carried on. A recent broadcast, heard by millions, cost 876,000, of which only a small proportion was received by the broadcasters. Had every family listening in written, it would have been hailed with delight by the sponsors, and would have insured many more free entertainments, of a costly variety, for the radio audience. But, at the same time, to acknowledge every note so received would have cost the stations thousands of dollars more than they received for the program. They can and do answer a few letters of especial human interest, or those that have come a long ways; but it is impossible to write to all their well-wishers. The latter may set down their letters as votes which will be counted for bigger and better programs; but the only returns which should be expected are those which will issue from the loud speaker .- EDITOR.)

#### A Clear Channel for All Stations in Turn?

Editor, Ramo News:

Although we depend mostly on local stations for our reception, most of us occasionally get a hankering to step out and see what we can get. We more often get

NIX than we do DX. And it is all due to the multiplicity of stations. Probably 90% of receivers in use today do not tune close enough to eliminate interference on the present width of wave channels.

My idea would be to create two major channels of about double the ordinary width, clear them of all broadcasting, and then allow them to be used by only one station at a time for one day only, in rotation,

#### A New Addition to RADIO NEWS

NINCE this magazine was established in 1915, it has been been most important in the radio field in the properties of the radio field in 1915, it has been read, and only by the radio anatour, the set builded with the radio anatour, the set builded was the radio anatour, but sep rotation for radio manufacturer, distributors, jobbers and relatives, of great his radio anatour properties, the radio anatour that it has been found necessary to issue a trade section of this magazine, to be known as

#### Radio News Dealers Personal Edition

This section is for the radio trade ONLY, as its entire contents will be of interest to those who are in the radio business, but not to anyone who is deriving his livelihood from other activities. For this reason, it will not be put on sale at the nearsteade, but distributed solely through the mail to the radio trade.

The publishers will be only too glad to end you, without charge, a copy of the new DEALERS PERSONAL BOTTON, who can ado manufacture, distributor, who leader or readiler. For one obtain it only by asking for it—ON YOUR BUSINESS LETTERIFED—and you are cordially invited to do so. See page 1048 of this issue, and

WRITE FOR YOUR COPY

until all stations of a class had had the opportunity of using same. One channel would be for the use of all high-powered stations, say from 5,000 watts up; and the other for low-powered stations, from 5,000 watts down.

This would give every broadcast station the opportunity of being heard occasionally by DX fans; and give DX fans an opportunity of hearing distant stations occasionally if they wish. It would take considerable time to make the rounds of all the stations, but it would be better to be heard occasionally by the DX hound than not at all.

S. A. Fischer, Sutton News, Sutton, Nebraska

(The ingenity of the suggestion is admirable, but its technical prescribedity meanly mit. It takes considerable time to adjust a station to an exact channel, and no high-powered station would desire to leave its assigned, explanelocatively, frequency for this purpose. As for the smallest state assigned, excellent amount of recognition; would be a certain amount of recognition; but it to only by accident that some of them would be a certain amount of recognition; would be a certain amount of recognition; but it to only by accident that some of them would be heart beyond the area in which they are occasionally received today—Korroa.)

# Who Won't Pay for Broadcasting? The Listener!

Yes, we think the worst nuisance is the commercial operator who cannot seem to control his buzzes; and a friend of mine tells me that most of the racket is chatter, like children gasping for words to talk.

J. E. Kitchin's letter in the February

Jack to Nuclean's creek on the electrons below Risans News cater to the commercial and anateur operators when they can sell 100 or 1,000 times the magazines, and get maybe double or triple the advertising to be 1,000 times described to the 1,000 times of the the 1,000 tim

I think the ideal plan for broadcasting would be on this order, about six or eight station chains, about every 50 cycles apart, each having a station in every state and making their programs to coincide so that you could tune in on one chain "classical" music—another "jazs," another operatic, another speeches, and so on. In that way, no chain would interfere with another chain.

As far as paying for the program goes, the R. C. A. or N. B. C. chain certainly gets theirs from radio tubes, storage batteries, giager ale and other advertisements. The first cost of a set is not the last. For, in a battery-operated set, there are new "B" batteries, "C" batteries, tubes, and once in a while new "A" batteries; in the electric sets, new tubes for both set and power unit.

(Continued on page 1081)









Arthur E. Bagley directing the Metropolitan Tower Health class before WEAF'S microphone.

WENTY years ago, if anyone back suggested that a great alarm clock load enough to reach out over thousands of miles, would be heard and beeded by millions some morning in the future, that suggestion would have been repudiated by the general public as a highlymaginative modern fairy story, the result

of some unbalanced mentality.

But now, radio waves carry an audible
good-norning from coast to coast and from
Malne to Florida. The world's largest gymclasses gather around loud speakers in every
state of the union, while even isolated followers of the call of calisthenics stretch
their sleepy bodies up in the cold fastness
of the Canadian woods, in the lonely cabins
of tramp steamers in mid-ocean and in the

# Radio—The Alarm Clock of a Nation

By Julia Shawell

warmer habitations of Panama. More than a million people a day, over vast areas, willingly cut their morning slumbers and devote their stored-up energy to exercises which a few men in a few cities direct.

For more than three years now, radio enhusiasts have been reaching out their arms for better health, bending their bodies for slimmer waistlines, riding imaginary bicycles on the parlor floor to change the pasty, white-faced look to one of rosy checks and brightened eyes.

While station WOR was the pioneer in the idea of the morning round-up for gymnastics, the big chains of the country have adapted and developed the setting-up programs until now those opening broadcasts of the radio day are among the most popular features on the air.

WEAP's hook-up carries the "Metropolitan Health Tower" classes to all parts of the country, while WOR, still active in the earlybird gyn field, has enlisted the Colgate Company to sponsor its classes, holding its sunrise audience with the latest commercial effort to make loud-speaker athletes of its

#### FOUR YEARS' PROGRESS

Arthur E. Bagley, director of the Metropolitan periods on the National Broadcasting Company chains, was the first physicalculture director to break out into the wideopen apaces among the ether waves with his "bodies erect, up and down, right and let, keep smiling everyhody," as the uncounted students of his health cult followed directions, bending and swaying in unison, though a thousand miles divided some of their numbers.

When Mr. Bagley organized his primer school of radio gymnastics he had a limited number of adherents, which grew and grew in size until some indication of its proportions was given in the deluge of mail which swamped his studio. The first broadcasts were in the nature of an experiment, tried out in the late spring of 1924. Would people take the trouble to turn their dials and follow an unseen instructor who was making them work when sleep was so treasured? Mr. Bagley had an idea they would and, as WOR was willing to test out his ideas, the radio gym class had its inception. Almost immediately, requests poured in for further directions, for charts, for individual advice and in commendation of the plan.

Throughout the bleak December dawn, and even in suitry August sumines, these faithful pupils were held and the result were so amazing that the Metropolitan Life Insurance Company, with its 345,000 are some of this horter to better health and to longer lives. Mr. Bagbey then became discrete of this new shood, with large studies in the Metropolitan Tower, which sent out its fast greetings in March of 1928, a very large through the studies of the Metropolitan Tower, which sent out its fast greetings in March of 1928, a very large through the studies of the Metropolitan Tower, which sent out its fast greetings in March of 1928, a very designated to the studies of the Metropolitan Tower, which sent the Metropolitan Tower, which sent the Metropolitan Tower of the Metr

Bernarr Macfadden then took over the WOR classes in conjunction with his activities for physical culture, added an



A part of the "Halth Army," which consists of all shapes, all sizes, all ages and types, that daily rise to do their stuff before the loud speaker.

orchestra to jucite further interest among set-owners and broadcast his theories and his practical ideas for many months. At the end of the year just closed, the Colgate people engaged the facilities of WOR for their own gym classes which have been developing previous programs, trying new suggestions to wake the public early and make them like it.

Since Mr. Bagley became associated with the "Health Tower" classes, more than 400,-000 exercise charts have been sent out to persons who wrote for them. Many of these were to be used in families of from three to ten members. From these figures some idea of the enormous size of the radio gym classes on the WEAF chain alone may be elimosed.

#### WAR ON THE FRONT SALIENT

At one time, the writer directed the gym classes at station WGBS (New York), which started at 10:00 a. m. and were designed for lazy women who just wouldn't get up early enough for the 6:45 or 7:15 classes, and for housekeepers who were too busy getting husbands off to work and children out to school to devote fifteen minutes of a busy period to even health measures. From personal experience, we can write that when a woman decides exercise will make her more attractive, the radio gym class is a proposition already sold to her and, whether she vawns in her downy bed on Park Avenue and slips out to thicklynadded floors or whether she runs in from the kitchen sink and her dishes to turn the dials, she's just as anxious to get that pleased feeling on the scales and to retain or attain attractive lines.

Brokers and boilermakers, clerks and clergymen, salesmen and sailors, fussy bachelors and sport-of-fate husbands, wives who have lost that girlish figure and whole families bent on being healthy, line up together at the call of a single voice, six days a weck—and do they stick? Well, a glance at some of the 400,000 letters in the Metropolitan files would convince the most difficult of the doubting Thomases.

Since his first class, Mr. Bagley has never been a moment late, never been absent a single morning, never broken his schedule. So there's no element of chance in "taking

the sir" for exercise.

Eastly at 6.55 o'clock, every weekday morning, on the N. B. C. stations and the WOR (Columbia) chain, as well as individual stations not allied with either group, the morning chimes or bell announces that the nation is ready for its daily dosen. This health army of all sizes, all types, all shapes and all ages bows its greeting to its unseen teacher and the fam begins. We shape a school of the state of the state of the shiver and shakes off the child zero weather.

Floridians, warm in a sunny clime, evidence more perspiration but no more ambition.

All the healthy rigor that the travelling medicine men used to promise becomes not only a possibility but a fact for those who devote their first waking moments to the radio grm. All the promises which have been made are not rosier than the realization reached by thousands who have written with reactivation to the company of the company of

Fat women take off the accursed pounds, anemic men take on vitality, family groups become energisced, the grouchy breakfast look is wiped off with a smile; for few who stay in line for the class on the air can resist the plea to smile as they work off the slucrish conditions of their systems.

#### ENTHUSIASTIC FANS

The largest family group made up of faithful followers of the gym programs resides outside Newark, N. J. Mother, father and eleven children, two grandchildren and the family dog line up every morning at 7:15 o'clock and "do their stuff" for health?"

The fattest fan who has made herself known to the broadcasters is a 323-pound woman in Michigan, who is slowly but surely



The Metropolitan Life Building in New York City, from the Tower studio of which are broadcast the exercises.

reducing that tonnage and who wrote that she is bent on getting back a figure—even though her husband, who weighs 375 pounds, said she is just a lapful! What a story television would make if it

could be used at 6:45 o'clock on the gym hook-ups! What a conglomerate lineup of humanity would be shown, and how many thousands would have to scurry to cover if they knew that their teacher was watching them!

A United States senator who does his daily dozen wrote Mr. Bagley: "I take your morning health exercises regularly, I thought I was to get something for nothing, (Continued on page 1052)



# Radio Novelties About the Globe



NAVY RADIO MEN GET A CHANCE TO SEE THE WORLD FROM A LOFTY PERCH

Among the jobe not desired by the average man is that of inspector the radio towers at Arlington, Va. Annually the Mayy's experts examine the ammonth steel magets for loose joints, loose boits, rust other deficiencies. The illustration in the center of the page shows moving picture being taken of one of the inspectors walking along the

of the girders high above the countryside. In the lower left phot graph, laken from a point near the base of a tower, looking upwars the small "bempe" along the outer edge are saliers, climbing up as inspecting as they go.

# People and Radio as They Are Seen by the Camera













Radio News for March, 1928



PON a huge indoor stage, in the great Harold Dare motion-picture were armored knights, beautiful ladies in gorgeous costemes, squires, yeomen, serfs, and villains of all sorts, mingled in reckless confusion; for the latest and greatest of Harold Dare super-spectacles was now in the making On a large movable platform stood Harold Dare, clad in a shining suit of mail, megaphone in hand, assisting his most efficient corps of directors to prepare for the great tournament scene. A voice called: "Mr. Dare!"

Dare turned, and saw standing beside the platform, a knight, fully armored and with his visor pulled low over his face. Dare

opened the note he proffered. "I must see you at once, alone. Follow this man. Gloria." Harold Dare spoke to his chief director.

"I shall return in a few moments. Let the picture proceed." He turned and clanked off after the messenger. He was frankly puzzled. This was quite unusual. Gloria, oft his sweetbefore the camera-and, the public

was wont to believe, in real life also-had never before so summoned him. What could this mean? His perplexity increased as his guide led him into the extreme wing of the main office building, in which was located the

studio and equipment of WROT, Harold Dare's own broadcast station. His guide paused before a door marked "Operating Room." Here, Dare knew, was located the major part of the immense equipment comprising WROT. With mounting suspicion, Harold Dare looked at the "She is inside," said the knight, "Inside the room."

Clumsily, Harold Dare's great gauntlet closed about the door-knob. Cautiously be pushed the door open. Yes, there was Gloria, seated in a chair. She wore a strange expression of terror, and Dare saw that she was trembling. He stepped into the room.

He caught a flash of it as it descended upon him and, even as he strove to raise his arms, it pinioned them at his sides.

He found himself imprisoned in a tall cylinder, which enclosed him up to the level of his chin. In her chair, Gloria sat motionless. In the opposite corner of the man, and in his hand he held an ugly automatic

Gloria screamed; but black Dandy Diavolo strode forward and seized her. the girl !" he hissed at a henchman. A vil lainous-looking individual drew forth a neat gag and fastened it firmly in place. moment Gloria was bound hand and foot.

"What does this mean, Dandy Diavolo?" demanded Dare, although he suspected well enough the intent of his captor "It means, Harold Dare," replied Diavolo,

"that you have scorned me too long. Now you must face the consequences!" Gag in hand, he advanced toward the helpless hero. Harold suddenly threw him-

self forward. He tottered - and three brawny henchmen caught the falling cylinder and righted it again. They removed Dare's helmet, gagged him securely, and replaced the helmet.

"Now, my fine fellow," sneered Diavolo, you are going to rue the many times you

have blocked my plans. You have begun to believe that because you triumph over me in every super-spectacle you must in-evitably do so in real life. But you are wrong, Harold Dare. In this episode of your career-and it is to be your lasttriumph is mine!" Diavolo took from a package a large roll

of heavy, flexible copper ribbon. He fas-tened one end of it to a binding post on the end of the cylinder. Looking down. Dare saw that the tube was wound with countless turns of fine insulated wire.

Diavolo unrolled the tape and stretched it from the cylinder over to one terminal of a meter on the transmitting panel of WROT. Another lead he strung from the cylinder, and wrapped the other end of it about a turn of a buge transmitting inductance.

"You may be interested to know, Harold Dare," sneered Diavolo, "that you are inside a great coil of wire, an enormous in ductance, which we have connected to the huge transmitter of WROT. Now let us see if your super-mind can recall some facts regarding induction. Of course you know that when a conductor is placed in the field of an inductance through which current is flowing, currents are induced in the conductor. Because of the resistance of this conductor, the energy thus induced is dissipated in the form of heat. This heating effect becomes more pronounced as

we increase the frequency of the current. So, it is readily imaginable that, if we feed our inductance a large current at a very high frequency, the heat produced in the conductor may become considerable. This phenomenon is the basic principle of the high-frequency furnace, with which metals may be melted-in vacuo, if you wishsimply by the action of high-frequency currents. Now you, Harold Dare, are in the field of such an inductance, and although you yourself are perhaps not a good conductor, your armor will be entirely satisfactory. You, the invincible, will be roasted alive in your armor! And then we Gloria, and I-will leave you to your public.

"That fair female shall rue the day she scorned my advances. I remember well the day our company was out on location, when we both offered to share our lunches with Gloria. I remember well that she refused the cheese sandwich I offered her from the fullness of my heart, and accepted instead the one of roast beef which you handed. her. Very well! If she prefers roast beef, she shall have it; for with the help of my



The car careened and swung into the studio driveway. With a bound it struck the chain stretched across the gate, snapped it, and skidded up the driveway.

radio-frequency oven, you, Harold Dare, shall be merely a great roast of beef!"

As he pronounced these ghastly words,

As he pronounced these ghastly words, Diavolo stepped to the transmitting panel He made sure that the transmitter was disconnected from the antenna. The tubes had been glowing for some moments, and now he threw a switch. In a far corner of the great room, huge generators began to plate-supply voltmeter. He waited until it had reached a maximum; then he began slowly to turn the large fiber wheel which provided a vernier adjustment for the main tuning condenser. Meters sprang to life. He regulated rheostats and adjusted various other controls. Gradually he brought the radio-frequency circuits into resonance The large radio-frequency ammeter climbed

as the output increased.

Inside the suit of armor, Harold Dare felt his hair gradually rise, until it seemed to stand on end. His skin prickled. The armor became perceptibly warmer; his iron-

meshed gauntiets became almost comfortable.

Diavido gave the vernier condenser as final twist, and advanced the filament theostats to their utmost. The meters leaped. Dare felt a surge of warmth. A gentle ticking sound, and a light smoke arose from the tube upon which the coil was warmd. Gloria sat hyportized. Dare sigwarmd. Gloria sat hyportized. Dare sigber own glorious oven size eart a beserching giance toward Diavido; but the archfixed sheart of stone was imperious even to such pitiful appeals. Her eyes filled with tears.

with cars.

The armor was becoming uncomfortable.

Dare's clothing was scorching; the helmet
made his head feel as if it would burne
made his head feel as if it would burne
cound as they expended. A curl of smoke
arone from inside the armor, and trickled
through the open visor of the helmet. Gloria
saw waves of heat ascend, the could feel
them herself. . . She would have screamed,
but the torturing gag stiffed her cries.

Then she swooned.

Yet through all this time of terrible trial and torture, disuntless Harold Dare kept a cool head. He saw that Gloria was unconscious, and gave thanks. She at least was not suffering. A dozen, or more, ideas passed through his mind. He hinneff was passed through his mind. He hinneff was passed through his mind. He hinneff was passed through for him soon, for he had that harence. If he could not summon help. The armor was unbearably hot. He tried to shift his position, and found that he

could move his arms back and forth a few inches. He swung them helplessly. He looked toward the transmitting panel. A needle caught his eye; it was swinging rhythmically back and forth. Unconsciously

he timed its arc.
Gradually it dawned upon him that it
followed the motion of his arms. He groped
aimlessly for an explanation. Changing the
position of his arms seemed to affect the
amount of current flowing in some circuit

Then he found the answer. A wild hope seized him. His movements became purposeful. Energetically he swung his arms, clumsily enough in the heavy armor, but with definite intent.

. . . . .

A government radio field car was nosing deliberately down Hollywood Boulevard. Inside, Aussitant Radio Inspector Merritt sat at the tidy bank of precision receiving instruments. He was checking the wavelength assignments of various broadcast stations, for complaints had come in regarding several small stations in that vicinity.

As he passed down the scale, he came you on a powerful white, as of the carrier wave of a high-powered breadcasting state. He listende, An unsarthly sound it slightly, but its intensity second to fluctuate, so much that the whistle became a verirable warble. What could such action meant Inspector Merritt's joy greeg gin, meant in property of the state of

Yet this was a queer sound. He plugged in an audibility meter, with which to measure the intensity of the signals. The meter swang far across the scale, then see-sawed quickly back and forth. Impatiently the (Continued on page 1939)



Inspector Merritt quickly raised his pistol. He pulled the trigger and the insulator which held Diavolo's R.F. line shat-

tered, letting the bare copper tape fall across a heavy bus wire.

A great arc of dazzling green, and the long ribbon melted.

# This is Station 2LO, London, England, calling



By Dale Pollack

OW many fans can truthfully say that they have actually heard the words above? Or perhaps: "You have just been listening to a piano solo from station IRO, Rome, Italy;" or maybe: "You are listening to an after-dinner concert being broadcast from station JOCK, Nagova. Japan, owned and operated by the Nagoya Radio Broadcasting Company."

How would you like to build a set that will get all these stations and more? And it won't cost you a fabulous sum either; it can be made for less than five dollars. I knew many people who would be willing to pay \$100 to get San Francisco once a Then, too, the average constructorhas all the parts needed in his shop anyway, and need go to no other expense.

The hook-up has been tried and proven, and so you need have no fears that it will not work. I myself have built a half a dozen of them, and not one of them has ever failed to work.

Now you too can pull the bluff with the best of them. You can now argue with the fellow who has that ten-tube superhet. With this marvelous set you have no more static to contend with; and if anyone does not believe it, just let him listen to this marvelous set. As for clearness, selectivity and quality, it has them all beat. Nothing can compare with it. The problem of fading has at last been solved. No more of it with the set described here.

#### A TWO MAN PROPOSITION

Of course, you must think there must be some hitch to it, but I can assure you that there is none at all. In spite of all its qualities, however, it has one rather, it needs two people to operate it. One person cannot run this marvelous set. don't let this make you think that it is complicated; as a matter of fact it has only one tuning control. Even this can be dispensed with, but no one will believe it is a radio set if it has no controls, so we had better place one there. There is one other thing that can hardly be called a control, but which nevertheless is important. It is a push button, such as used to operate doorbells. It does not have to be placed near the set but it is the real control that tunes in the stations

So far you have been kept in suspense as to the hookup of this super-radio set. I am calling it the "Super-Bullodyne," because it is a sure cure for all radio liars. Just have them listen to it once and they will be cured of blowing about their sets forever

#### THE LAYOUT

The extremely simple hook-up, or rather part of it, is shown in Fig. 1. You will note that there is no aerial to be bothered with: even this has been eliminated in the "Super-Bullodyne."

All you have to do is to run a length of double wire (such as annunciator wire, lamp cord, or Christmas-tree wire) from your regular radio receiver to any place in the house that is not within hearing distance of the receiver. (This latter point is very important, as you will shortly understand.)

A small microphone and a flashlight lamp are needed in the attic or cellar, or wherever you run the double wire. There are available on the market a number of small, inexpensive microphones which are ideally suited for use in the "Super-Bullodyne." The entire trick is to connect the microphone to the primary of the st audio frequency transformer in the se without disturbing any of the rest of the amplifier wiring. It may be a good idea to remove the detector tube from its socket, or to leave its filament turned off; otherwise the microphone is likely to be short-circuited through the plate circuit. Make sure that your amplifier tubes light when you have connected the batteries and turned up the

You may be asked some undesirable ques tions as to the number of tubes, the parts, etc. I would advise those who anticipate such queries to throw in a lot of junk; such as spare parts, clock wheels, old tires, wire, or anything to make it look more complicated. Then you can say that you have lost the hook-up, and let them try to trace the circuit. There is another much simpler device to quiet questioners; it takes its most efficient form in the shape of a padded baseball bat. Its operation is obvious. Here is the "modus operandi" of the

Super-Bullodyne. Station your confederate, the indispensability of whom has already been pointed out, at the hidden microphone, to broadcast the program from whatever station you wish. Assemble your friends in front of the "Super-Bullodyne," Whenever you wish to tune in a station, simply press the push button, which will light the signal lamp and warn your assistant. You can readily arrange a suitable code—a certain number of flashes for each stationwhich will prevent confusion. A phon graph in front of the microphone will make

(Continued on page 1061)



#### Wisdom for Radio Widows

A Straight-from-the-Shoulder Talk to the Woman Whose Husband Belongs to the Order of the Sleepless Knights of DX



By Larry Triggs



D X, DX1 Ah! Whisper it softly, you Mrs. Greens, Mrs. Smiths and Mrs. Jonness. Breathe it gently into the chief with the distribution of the you shall see. You who promised to love, you whall see. You who promised to love, honor, and obey your radio-fan husbands, you who darn their socks and bake their favortic pies, you who look to them for favortic pies, you who look to them for the larder runs low and mew frocks when it is spring-let not your hearts! be troubled

with bounty from an ethercal world of jazz bands, bedtime stories and chain broadcasts. You will probably remember that first shrick from the basement the night John

You will probably remember that first shrick from the basement the night John finally got the radio set hooked up. Wonder of wonders! With his own hands he had created the mirade which spanned continents and whilepered back to him what the other half of the world was doing. The and was able to distinguish a jew's harp solo from the station on the other side of town. Think you he slept that night? Fond woman! Then arrived that strained period of ap-

prenticeship which came finally to fruition in John's announcement that he was going to build a set that would get DX. Ah, mystic symbol! Breathe it softly!

You stood, arms akimbo, the fires of rage gnawing at your breast. All those weeks of nagging him to quit fussing and come to bed, or stop fiddling down there and go see what Junior's doing in the attic; all these, were they all to be done over again? Right in the middle on a wonderful concert from BOOB, was John again to spring suddenly from his chair, pliers in hand, to tear the very entrails from the machine in order to correct a slight distortion in the tone? And was he to do it again, and again, and again? And was the radio always going to be in the basement, dismembered, when company came—and with such a good program on from WUMP, too?



#### THE ENDLESS QUEST

Ah yes, fond woman! All these things were coming again and again and yet again. And did you let a little fire kindle in your chest and grow larger and larger, all because you didn't understand DX, or your husband? Ah, tragedy—for John, patient heast.

He wrought this miracle with his own two hands—he who couldn't have fixed a (Continued on page 1042)

You stood, arms akimbo, the fires of rage gnawing at your breast, fussing and fuming at John while he tried for DX.

nor your minds be vexed. For it is a thing which surpasseth understanding, at least for most radio widows.

Tour shoe-store-cierk or bank-president husband had probably never made anything with his hands before in his life, except possible to the store of the store of

#### A STRANGER IN THE HOUSE

But, abl the night John came home with a radio catalog under his arm! Then began that mystic tutelage, that divine ministration from other spheres whereby John became a priest in the temple of vacuum tubes and "B" batteries and wrought with his own hands the miracle; the miracle that gropes in the outer darkness to return laden



questing to the ends of the earth for some faint sign, for some faraway signal, no matter how weak, getting DX and other things.

# The United States—A Broadcast Studio



Forty-Seven Stations Broadcast \$1000-Dollar-a-Minute Program With Microphones at the Four Corners of the Country; 12,000 Miles of Telephone Lines Used in Tie-Up



By Joseph Riley

A STATION hook-up, termed "the greatest mechanical achievement in achievement in the costilest program thus far enjoyment on January 4, 1928. Not only was the program remarkable from an enjoyment on January 4, 1928. Not only was the program remarkable from an engineering standpoint, but it offered to the radio public a gathering of theatrical stars such as seldom has been grouped into sixty.

minutes of broadcasting.
Phillips Carlin, in New York, started of
the lour by introducing Will Rogers, who
has own home in Beverty Hills, California.
The western microphone was then switched
on and, in his own unique skyle, Rogers
of ceronosies. He then introduced Paul
Whitenan and his orchestra (who were
back in New York) saying that Whitenan
was "the man who brought open up and
orchestra." The microphone in New York
City was then switched on the network,

and the wonderful strains of George Gershwin's "Rhapsody in Blue" went out over the forty-seven stations.

At the conclusion of the number, the California microphone was again put on the air and Regers introduced Dorothy and Fred Stone, who were playing at the Erlanger Theatre in Chicago. From a dressing room in the theatre, Stone and his daughter broadcast several songs. Following came a short talk from Detroit by the sponsor of the program, Edward G. Wilmer, president of

Dodge Brothers, Inc.
From California again, Rogers introduced
the man known to thousands for his
"Mammy" songs, Al Jolson, who was in the
heart of the manuny section of the country,
New Orleans. After two or three songs of,
and from, the South, Rogers made his final
talk of the crening, reintroducing Paul
Whiteman, who wound up the program with
two popular jazz numbers from New York.

LONG LINES USED

To bring these widely-separated persons

before the rail ratio antifero, estimated and more than thewty for millions, approximately 12,000 miles of telephone lines were employed. Engineers of the National Broadcasting Company, in conjunction with earliers of the Eld System, which supplied arrangement for several weeks. During the elevelopment of the plans, many complications arose, especially with respect to grant expections arose, especially with respect to grant experimental expects of the plans, many complications arose, especially with respect to grant experimental experimental experiments of the plans, and complications arose, especially with respect to grant experimental experiment

The transcontinental line which carried Will Rogers' introductions was routed through San Francisco, Salt Lake City, Denver, Omaha, Chicago and thence to New

In readiness in case of trouble was an emergency circuit from San Francisco through Dallas, Little Rock, St. Louis, Chicago, into New York. Then, in addition, were the usual telephone lines, required to (Continued on page 1044)





"I bid four diamonds."

"Four spades."
"Five diamonds."

"I double the five diamonds!"
"Redouble!!" And the fight is on!

EN years ago the above dialogue would have meant little if anything to the average man; but today it would be instantly identified by a majority of people as conversation ennanating from a bridge table, whether it were heard on Fifth Avenue, Main Street, or in

the middle of the Sahara Desert

The question might well be asked, "Why this sudden interest in the game of bridge? Taking into consideration many viewpoints, it seems safe to say that, more than to any other factor, the present popularity of the game is due to the broadcasting of bridge games over the radio. Consider for a moment the vast number of people who have listened in to the games for the past two years, and it will require little reflection to come to the conclusion that, even though many radio set owners originally knew nothing whatsoever about the game, they listened in now and then, gradually becoming interested. Bridge is similar to the game of golf in that, once the "bug" has bitten you, there is little hope that you will not become an enthusiast

Another reason why bridge appeals to so many people—and in this respect it is unlike the game of golf—it makes no difference how had a duffer a person is at the game. Even though he knows mone of the many conventions, he can gain a vast amount of pleasure from playing, as the fundamentals of the game are very simple. And then, too, with the examples of expert play brought to him weekly over the air, he can look forward to improving his game, thereby obtaining greater satisfaction from a growing appreciation of its finer points.

#### THE WEEKLY BROADCAST

The games which are put on the air every Tuesday at 10 P. M., E.S.T., from WEAF, its twenty-six associated stations, and fortyseven independent stations, exemplify the correct conduct of hands that have actually been dealt in a game. Wilbur C. White-head, the foremost player in the United States, together with Milton C. Work, a player of the highest rank, choose the hands from actual play and then decide on how they should be bid and played. These two gentlemen take part in every game put on the air, and their partners are players of excellence from different sections of the country. The bridge hands in which these other players will participate are sent in advance to them for their approval of the method of bidding and play.

A great many people have the impression that the games which are broadcast are manufactured handes: i.e., hands especially made up to illustrate different points in bidding and play. This is not done, for a very important reason. In every hand that is dealt there is an inherent probability that the cards will fall, according to a definite multiensitical law, in an order seathers of the control of the control

case the remaining six cards will be divided between the two hands of the opponents, four and two; that all should be possible, four and two; that all should be proposed to the state of the state of the state at a glance, by the way in which the cards or distributed among the four hands, whether they are a "true deal," the result whether they are a "true deal," the result human design. In other words, to broadcast the bidding and playing of a deal in a way that will correctly illustrate certain features, the natural "twast design" must be catually dealing the cards.

#### METHOD OF ILLUSTRATION When, in 1925, it was first decided to broad-

cast bridge games, a great deal of discussion arose, among the originators of the scheme, as to the manner in which the games should be put on the air. John H. Smith, who, with Mr. Whitehead, recently won the bridge championship of the United States, devised the method which was later adopted by the U. S. Playing Card Co., the onsors of the broadcasting of the games. The method is roughly as follows: first, the listeners are advised to have ready a deck of cards separated into the four suits. Then the respective holdings in the four hands are slowly read, the players being designated by the four points of the compass. After the four hands have been read off and the cards arranged, the bidding is made, with the bidder's reasons for each bid explained from the standpoint of his position. Then the play is started, and the

(Continued on page 1049)

# Caring for the Socket-Power Units

Some Valuable Suggestions that will Aid in Securing the Longest and Most Satisfactory Service from Accessories of this Type.



By Charles Magee Adams



OW and again some over-enthusistic and under-informed alesman (and, unfortunately, some
advertising writers as well) can be found
confidently informing purchasers of socketpower units that, as regards care, this equipment "can simply be installed and forgotten."

Conceivably, it can. The driver of a car can also forget to supply his engine with oil and water. But few will think it wise to do so, at least after a first experience; and much the same holds with a radio

socket-power unit.

The amount of attention required by any properly-designed and well-constructed device of this type is trilling. But such attention—intelligently directed and regularly applied—is indispensible. With it, the unit will function satisfactorily and dependably over a long period. But without it, the service supplied will become progressively more unsatisfactory, finally failing altogether.

This care, too—as too frequently is not recognized—must begin with the installation. Many sockel-power units are being brought for receivers already in use, and there is a tendency to fit them into the existing installation in the simplest way, without any thought for their particular requirements. But this procedure often proves to be the cause of unsatisfactory results.

#### VENTILATING THE UNIT

A power unit must be installed with as much consideration for its operating requirements as any other piece of radio equipment; which means, first, that its occution must permit ready accessibility for maintenance, and second, and still meaning important, that it must allow for ample ventilation.


The latter is essential, because all units radiate a certain amount of heat during

this must be carried away if the unit is to be kept at a safe temperature. If it is not, the results may be too-rapid evaporation of electrolyte, damage to rectifiers and filter condensers and, in extreme cases, to transformer windings.

operation. Obviously,

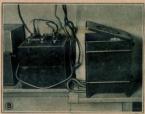Accordingty, if the unit is being installed inside a cohoole cabinet, as is frequently the case, care should be exercised to see that the enclosed space contains a sufficient volume of air to





assure adequate cooling. If it does not, a small opening at the hack (or in some other location that will not be unsightly) may solve the problem without difficulty.

Also, when the unit is located outside the receiver cabinet, say on the floor, it should not be covered for the sake of appearance, or surrounded by other objects, in a way to prevent the free circulation of air. Most of all, if it is placed in the basement under the receiver, particu-

lar care should be

THE WRONG WAT

(A) The wrong way is keep the storage batter and its charger; pile a the loose junk in th house over them, so the they will not have any a circulation at all aroun

(B) The right way, we everything free and clea and raise the lid of the charger, when it is service, so that the ge erated heat can excap Dust and wipe the instruments freewarth.

(C) The easiest and s way of putting the v into an "A" socket-p unit of the kind v employs an electro condenser. Use an dinary pitcher an kitchen funnel. Never taken to be sure it is not near the furnace or any heating pipes which will cause the temperature of the surrounding air to be higher than normal.

The other detail of installation requiring attention is to keep the flexible cord connecting the unit with the lighting-circuit outlet as far away from the aerial and other receiver leads as possible. In some

other receiver leads as possible. In some units, this cord is shelded to prevent induction by the alternating current; but in some it is not, and this precaution will eliminate the excessive hum which might otherwise be caused.

#### FOLLOW DIRECTIONS

When properly installed, the next point of importance is to see that the unit is placed in operation, for the first time, in exact accordance with the manufacturer's directions. This is particularly essential in units employing electrolytic rectifiers or electro-



lytic filter condensers. These require a preliminary period of "warming up" for "forming" the plates; and directions covering this should be followed to the letter. They are specified for good reasons, and satisfactory results cannot be expected unless they are carried out exactly.

Once it is put into service, the most important point in caring for a socket-power unit is, as previously suggested, that this care be regular. A few minutes of intelligent attention at stated intervals (not too long) will, not only keep the unit in a condition for giving better performance, but go



covered by directions accompanying the

mit It will be noted that, with rectifiers of this type, manufacturers often warn against using the hydrometer or syringe employed in adding water to batteries. The reason for this is that the solution used in rectifiers is usually alkaline; with the result that even a slight taint of acid will cause serious damage. Great care should accordingly be exercised on this point, and some means of adding water used, other than that employed in connection with the battery. If the unit employs electrolytic rectifiers

> manufacturer recommends a period of "warming up," similar to that at putting into service, after the unit has stood idle for a prolonged period. This is necessitated by the fact that the plates must be "formed" again, as at the beginning, and such directions should be followed carefully. otherwise a distress-

ing hum will be the result, and possibly serious damages as well. RECTIFIER TUBES In units using filament type rectifier tubes for the "B" supply or "A" charger, failure of these to light is generally depended on as an indication of trouble; but this is scarcely to be recommended. Whenever the charge seems insufficient or the receiver "lacks pep" after six months to a year of operation, it is always well to try replacing these tubes. They will often be found to have deteriorated, though still lighting, as do vacuum tubes in receivers. The gaseous-type rectifier tubes will also require replacement after long use.

Though not actually part of the power unit, it is essential that the "C" batteries be not neglected if these, rather than the socket-power unit, are depended on for negative grid biasing. Because practically no current is drawn from these, many fans regard their life as endless; but, as a matter of fact, they deteriorate merely from age. A check of "C" batteries every few months will assure that the "B" side of the unit is free from excessive current drain and decreased voltage and maintain the tone quality at a high level.

#### UNIT MUST BE SUITABLE Another word of caution seems necessary.

about buying a new receiver to be supplied by a power unit already in use. When this is done, be certain that the unit, particularly on the "B" side, is of sufficient size to meet the demands of the new receiver. This can readily be determined by reference to the milliampere consumption of the receiver and the capacity of the unit: and trouble frequently encountered through overloading may in this way be avoided.

Also, if the receiver and unit are designed for the use of 199-type tubes with filaments in series, the power rheostat should never be turned to a milliampere reading higher than 60. Though this may not seem a definite part of the unit's care, it is so, nevertheless; because turning the rheostat higher overloads the unit as well as the tubes, with results not the best for either.

And finally, do not make a practice of tinkering with the receiver while the power unit is turned on. To be sure, there may be times when adjustments are required with the set "live" and, when they are, strict precautions against short circuits should be taken; such as the use of insulated tools. These are important because, while with batteries such a short-circuit of the "B" power might mean merely a running-down of the batteries; with a "B" supply device it may well mean the burning-out of equip-

(Continued on page 1053)



than several hours of spasmodic attention; and at most the amount of time required is small.

Adding water is an apt example. If the unit employs a storage battery to supply "A" current, it will be necessary to add water to this from time to time. If it is added at regular intervals - say, once a month if that proves necessary—the power supplied will prove much more dependable and the battery's life considerably longer than if it were neglected till the electrolyte level became dangerously low.

CHECK UP ON IT

Another detail requiring attention when a battery is used in checking the charge. Hydrometer readings should be taken before water is added (unless some visual means of indicating the charge is provided. as some manufacturers do); and if the specific gravity falls below the figure specified the charging rate should be increased or the receiver left idle for a day or two. Conversely, if an overcharge is shown the rate should be reduced. The rate itself will probably have to be adjusted to fit the particular operating conditions, which can be done after a little trial.

Distilled water must be added also to electrolytic condensers as well. In the former, it will be necessary to renew the solution after a prolonged period of operation, besides replacing electrodes. These details are KEEP EVERYTHING IN THE RIGHT PLACE

(D) A fine way of causing a lot of troublesome hum in the lond speaker the aeria a 110-volt



YEAR



HEARD ON THE SPEAKER MAGNET FIRST RADIO BUG:



"You've been gone a long time. Where were you?" SECOND RADIO

Bue: "On a little exploring trip to Leslie Carpenter.

RADIO TERM ILLUSTRATED



"A Single-Circuit Squealer"

SIMPLIFIED TEACHER: "Johnny, how do you spell Schenectady?" JOHNNY (Without hesitation): "W G Y."

HOME, SWEET HOME!



"Meeker's wife is such a persistent back-seat driver he's decided to stay home and with the radio." "What good will

that do him? She's an arm-chair tunerin, too." -Gleason Pease.

PRACTICE MAKES PERFECT
FIRST HUBBY: "Is your wife getting much help from the daily cooking hour?"

SECOND HURBY: "Oh, in a way. This morning she got three new recipes while she was letting the pie burn."

BY RADIO (To the Broadcast Artists)

The spot where I would like to be, Is far away by a tropic sea, While all you artists
played for me,
By Radio.

I'd bask all day in the banyon s As the natives danced and the monkeys

Just drinking in your serenade, By Radio.



And while you toiled in a Northern freeze, I'd loll at ease in my "B. V. D.'a." Taking my winter-if you please-By radio.

The only thing I'd ever do, Would be to turn a dial or two, While gladness you'd keep sending through, By radio.

And when the long bright day was done. lieved the sun,

And the tropic moon re-I'd still loaf on and enjoy your fun, By radio.

In fact, 'twould be my chief delight, To stick around in the pale moonlight 'Till the last of you had said "Good Night," By radio. -Roy Coleman.

BLINKS: "The senator's a consist-

JINKS: "PII say he is. He wouldn't even have a wet battery on his radio set!" E Price S -William G.

Mortimer. Game: "Jimpson looks discouraged. Has

he received some sort of a setback?" LEAKE: "Well, the installment man did."



getting much benefit from the Daily Dozen hour?" e tunes it in while

he's eating breakdid appetite.



RADIO RHYMES .....

...... No. 5











TUNING NOW !

NOR MADE THE FAINTEST

#### List of Broadcast Stations in the United States

List of Broadcast Stations in the Officed States										
Radio Call Letter	BROADCAST STA.	Ware (Meters) Pewer (Watts)	Radio Call Letter	BROADCAST STA.	Pewer (Watts)	Radio Call Letter	BROADCAST STA.	Radio Call Letter	BROADCAST STA.	
KDKA	A CONTROLLED TO SERVICE AND ADMINISTRATION OF THE PROPERTY OF	*316 50000	KGEW	Der Merger Cohe   Der Greiche Charles   Ger Christian    Ger Christian    Ger Christian    Ger Christian    Ger Christian    Ger Christian    Ger Christian    Ger Christian    Ger Christian     Ger Christian     Ger Christian     Ger Christian      Ger Christian	*100 100 100 100 100 100 100 100 100 100	KWJJ KWKC KWKC KWKC KWKC KWCC KWCC KWCC	A Comment of the Comm	WDBJ	Roanoke, Va	
REFUX	SCHOOLINE, Associate Associated and Associated Associat	225 15 15 25 16 16 16 16 16 16 16 16 16 16 16 16 16	KJBS KJR KKR KKR KKR KKEX KLI KKLI KKLI KKLI KKLI KKI KKI KKI KKI	and Commission and Co	50 to 28.  50 to 28.  50 to 28.  50 to 29.  150 to 29.  150 to 29.  500 to 29.	hat au	Abburn Ab.  Abburn	WFJC WFKD WFKD WFKD WGBC WGBC WGBC WGBC WGBC WGBC WGBC WGBC	Section   Sect	
KGEF KGEH KGEN KGEO KGEQ KGER	interest of the control of the contr	. 263 800 . 201 50 . 263 10 . 225 12 . 205 100 . 204 50 . 216 100 . 204 10	KUT KVI KVL KVOO KVOS KWBS KWCR	Sloger City, Iowa.  Protection, Ishihao.  Sai Lake City, Utah.  Sait Lake City, Lake City	200 200 200 200 200 200 200 200 200 200	WCBM WCBR WCBS WCDA- WCFL WCGU WCLS WCMA WCOA WCOA	Also démariers, 150 watt)  Kernordas, Wes. 227, 10  Kernordas, Wes. 27, 10  Chivre, 15d, 21  Chivre, 15d, 21	WILL WIDD WIP WIAD WIAD WIAN WIAN WIAN WIAN WIAN WIAN WIAN WIAN	The state of the s	

# What's New in Radio

#### The Electrodynamic Speaker Makes Its Appearance

SPEAKER units of the electrodynamic type have been made available for the first time to the anateur constructor. These units are offered with a small free-edge cone attached, and have been designed so that they may be installed easily in a radio console cubinet, or attached to any satisface builder for realize fully the advantages of power amplification and do so at a comparatively moderate cost.

Electrodynamic speakers differ from others both in principle of operation and in construction. They possess valuable characteristics, found only in this type of reproducers and lack many of the inherent faults of the permanent-magnet type of speakers.

In speakers of the electrodynamic type there is a field winding which must be excited by an external source of direct current. In the magnetic field of this winding a separate moving coil is freely suspended, and the antide frequency currents are passed and the antide frequency currents are passed edge design, is attacked directly to the moving coil. This construction gives great volume and purity of tone, due to a number of factors.

MOVING COLL
MAKEETE BATH

THE COLL
TO FRED CAPPET
TO FRED CAPPET

The above drawing illustrates the interior construction of the new electrodynamic speaker unit with a free-ciae come attached.

The field is of great strength and constancy, and in this field the moving coil is freely suspended. The forces on this coil, which produce the sound, are dependent only upon the current in the coil, and not upon its position in the field; and there is no iron in the armature, to be over-saturated. This results in almost complete freedom from distortion harmonics introduced by the speaker itself.

The drive of the speaker is applied disrectly to the cono. climinating the necessity for a connecting pin which might bend and wirste. The inductions of the cell is exturbed an almost pure resistance-load, resulting in a high power-factor and an impedance which varies but slightly with the frequency curren. The motion of the cell is errors the consequence, the matter is the size of the finite time in the consequence of the consequence of the cell of the consequence, the matter is the cell of the time in the cell of the cell of the cell of the time is the cell of the cel

The freely-floating coil offers other advantages besides the ability to supply great volume without chattering. It is free to



Picture shows external appearance of speaker unit: A, chamois leather insulating cone from frame; B, felt insulating unit from balle; C, tuber cone: D, come abox: E, frame of sheaker.

more an eighth of an inch at a more touch, and is particulty free from the definite reconnecs, which cause the characteristic tiple of other types of speders. The in-pedance of the cell is practically constitute to the cell is practically constituted to the cell in practically constituted to the cell in practically constituted to the cell in practical value of the cell in the

The speaker may be used in connection with radio receivers of any type; but best results are obtained when a power tube such as the 210 is used in the output stage. The unit will not deteriorate with use or age like the permanent-magnet type, as the magnetic lines of force are produced solely

by the current passing through the field coil.

Another important point in connection

with the operation of the speaker is that a baffle is required for best results. This is true of all speakers of the free-edge cone type; as, otherwise, the air waves which are

EFFECTIVE BAFFLE IS DISTANCE ALONG DOTTED LINE FROM POINT A TO POINT B



FLAT BAFFLE BOX-TYPE BAFFLE
Two types of baffles which may be used with
free-edge cone speakers. As the distance AB is
increased, the low-note reproduction is improced.

set up simultaneously by both the front and back of the cone would alternately neutralize and reinforce each other and seriously affect the volume. The illustration shows two types of baffles which may be used with success, the size of the baffle determines the effectiveness of the speaker on low frequencies, but considerable latitude is permissible in thi, construction.

The speaker unit is made in two type, for operation, one with 6 volts D.C., and the other with 110 volts D.C. The 6-volt type requires for the field winding a current of ½-ampere and this may be furnished by the storage battery used for the operation of the receiver. The 110-volt type requires 50 milliampres, which may be obtained by connecting the field ceil of the speaker in place of a fitter ceil in the plate-power unit.

of a more cent in the glane-power in The construction of the speaker is clearly illustrated in the pictures on this clearly illustrated in the pictures on the local power of the form of the proper position within the frame B. The moving coil of the speaker is attached directly to the speaker disphragm at the apex D. B is a thick piece of felt which mechanically insulates the speaker from the buffle after it has been installed.

\*\*Monatorizers.\*\* The Magnarous Company.\*\*

#### New Fixed Condenser Made In Grid-Leak Shape

MANY experimenters have found the design of the standard fixed condenser rather inconvenient from the mechanical viewpoint. In order to install

these units in a circuit, they usually have to be soldered in place and, when it is found necessary to substitute a condenser of different capacity, it is necessary to heat the soldering iron, remove the old condenser and solder a new one in its place.



Standard grid leak clips may be used for mount ing this fixed mica condenser in a receiving set

The inconvenient feature of the standard fixed condenser, mentioned in the above paragraph, has been avoided in a new unit, which has recently been placed on the market and which is illustrated in a drawing herewith. The new condenser is mounted in a glass tube, with metal caps on each end, and resembles a grid leak in appearance. Also, it will fit in a standard gridleak mounting, thus making it easy when desired, to substitute units of various values quickly and without inconvenience.

The new condenser uses mica of a high quality as a dielectric, and its plates are of copper foil. It is ruggedly constructed and cannot change in capacity; it is unaffected by atmospheric conditions as it is sealed in a vacuum.

Manufacturer, Tobe Deutschmann Co.

### Compact Unit Provides "A" and "B" Power to Sets

LARGE majority of those who nave A hitherto converted their battery-operreceivers into electrified or electric sets, which operate from the 110-volt 60cycle house supply wires, were forced to make changes in the wiring. In some cases it was necessary to wire the filaments in series; while in others the use of the new A.C. tubes necessitated a slightly-different



of "A" and "B" power unit with metal removed. Letters refer to apparatus similarly marked in diagram.

circuit. Recently, however, there have been developed socket-power units which may be substituted for batteries without making any changes in the receiver. The unit illustrated on this page is one of the latest designs and provides plate ("B") power as well as filament ("A") power for the tubes

With the unit under discussion, ample power is supplied for the operation of any receiver using eight or fewer tubes of the 201A type. The "A" power circuit has a maximum output of 2 amperes at 6 volts; and the "B" power circuit delivers a cur-rent of 55 milliamperes at a potential of 180 volts. This high voltage makes it possible to use a power tube of the 171 or 112 type in the last audio stage; and the four additional binding posts provide lower voltages for the detector, radio-frequency and first audio-frequency tubes.


The complete unit is mounted in a compact case measuring only 101/4 x 181/4 inches by 71/2 inches high. This is only slightly larger than a set of heavy-duty "B" batteries delivering 180 volts, and the weight of the unit is approximately the same as that of the batteries.

The complete details of the power unit will be found in the schematic wiring diagram. It will be seen that this naturally divides itself into two sections; the "A" power circuit and the "B" power circuit. tue of the voltage drop which takes place across the resistors R1, R2 and R3. R1 is a 6,000-ohm resistance unit, R2 has a resistance of 3,000 ohms, and R3 of 1,800 ohms. A by-pass condenser having a capacity of 0.5 mf. is connected between each



This compact metal case houses a complete power-supply unit for sets using six-volt tubes.

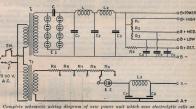of these resistors and the negative lead. The resistor R4 reduces the voltage for the detector tube. In operating a power unit of this type, it is necessary only for the owner to con-



rectifiers in both the filament and plate supply circuits. It will operate sets using eight tubes or less.

Each has a separate power transformer, and the primary windings of these transformers are connected together and to the 110-volt power-supply wires. The switch (SW) connected in the 110-volt circuit controls the operation of both sections of the power unit.

The "A" power device is essentially a unit with characteristics identical to those of a device described previously in this department ("Electrolytic Rectifier and Condenser," pages 596-7 of the December 1927 issue); and those who are interested in a more complete technical description are referred to that article. The circuit employs a step-down transformer (T2); a rectifier (E2) of the electrolytic type; a filter circuit consisting of a heavy-duty choke coil (L3) and an electrolytic-condenser bank; and a voltage-regulator circuit made

up of the fixed resistors R5 to R9. The "B" power circuit is somewhat similar to the standard type, but employs an electrolytic half-wave rectifier which consists of eight small cells connected in series and is by-passed by a 0.2 mf. condenser. The step-up transformer (T1) provides power for the rectifier circuit and the current is filtered by the choke coils L and L2 and the condensers C1, C2 and C3, which have capacities of 4.5 mf., 3 mf. and 6 mf., respectively. The higher, lower and medium intermediate voltages are obtained by virnect it properly the first time and, after that, to add distilled water to the rectifier cells once every three or four months. The output voltage of the "A" power unit need be adjusted only once for a set using a given number of tubes.

Manufacturer, Fansteel Products Co.

### New Resistor Units For Radio **Power Circuits**

A SERIES of accurately-rated wirewound fixed-resistance units, especially designed for radio purposes, has recently been developed. They are well suited for use in plate-socket power units and in amplifier circuits, and possess several new and interesting features,

In the past the constructor has always been confronted with the problem of finding a satisfactory mounting for the resistance units of his power unit or receiver. How-



Wire-wound resistors of this new series are

ever, the mountings specially-designed for the resistors described here are so arranged so that a resistor may be fastened securely in position on a sub-base panel or wooden baseboard with two screws. Also, they are properly insulated so that there is no danger of a short circuit.

The mechanical construction of the resistors is also interesting. The wire is wound on an insulating tube of extreme durability, coated with a special non-vitreous enamel and baked. The baking takes place at a temperature which is much lower than with ordinary usual enamels and, as a result, the fine wire of the unit is uninjured in

the process.

The new resistors are made in two types; a small size, which is 2 inches long and capable of dissipating 71/2 watts, and a larger size 4 inches long and capable of dissipating 15 watts. Both types are 11-16 inch in diameter and available in nine different resistance values between 500 and 15,000 ohms. The current-carrying capacity of the 71/2-watt size ranges from 125 milliamperes for the 500-ohm resistor to 20 milliamperes for the 15,000-ohm resistor; in the 15-watt size it is 175 milliamperes for the 500-ohm resistor and 30 milliamperes for the 15,000-ohm resistor.


In addition to the standard single-resistance sizes, two special tapped resistors of similar type are made for use in power units. One has been tapped to supply intermediate voltages of 221/2, 45 and 90 in a plate socket-power unit, designed to deliver 180 volts under full current load for a 171type tube, and is suited for use in all power units using the 60- and 85-milliampere fullwave rectifying tubes. The other has been tapped to supply intermediate voltages of 45, 671/2, 90 and 135 in a plate socket-power unit, designed to deliver from 400 to 450 volts under full current load, for a 210-type tube, and may be used in power units em ploying 216B and 281-type half-wave rectiflers. The resistor shown in the illustration is of the 171 type

Manufacturer, Daven Radio Corporation.

which sockets receive the detector, the general-purpose, and the power tubes of a receiver. A simple, "foolproof" way of accomplishing this is available in a new line of color-code sockets which have just been placed on the market. The sockets are made with a rich maroon top for use in circuits requiring the use of general-purpose tubes, such as the 201A and 226 types. The detector sockets have a dark green top and are made in both the four- and five-prong types, for the 200A and 227-type detector tubes. In the power

circuits a bright orange socket is used to indicate that a

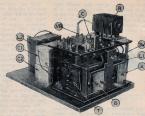tube of the 171 or 210 type is required. In addition to the color-code feature of the sockets, they have other mechanical advantages. The sockets are shock-absorbing and non-microphonic, and the tube-holding element floats, independently of the base, on four perfectly-balanced springs. There is a positive tube-to-terminal connection and



### Homemade "A" Power Unit Uses New Apparatus

PARTS for an "A" socket-power unit of a new design have recently been made available to the radio constructor. new power unit operates on electrical principles which are entirely new and possesses many features not found in other designs.

It will supply ample current for the operation of nine- and tentube receivers using tubes of the 201A type, and is very easy to assemble. It em ploys a new full-wave dry - electrolytic unit in the rectifier circuit; and in the filter circuit high - capacity condensers of

"dry polarized" type are used. The complete schematic wiring diagram

of the unit will be found in these columns. It will be noticed that the 110-volt 60-cycle house current is connected directly to the primary of the step-down power transformer (T) and that a single-pole switch (Sw) is connected in the circuit. A plug receptacle (C) is connected directly in shunt with the primary of the transformer, and this makes it possible to control the operation of the "B" power unit from the switch of the "A" power unit. The output voltage of the power unit is regulated by connecting the rectifier with the desired tap of the secondary winding. A flexible connector (VR) is provided for this

In the power unit full-wave rectification is employed, and a standard bridge rectifier arrangement is used. This circuit is followed by a highly-efficient filter circuit consisting of two high-capacity condensers (C1 and C2) and two heavy-duty choke coils (L1 and L2). One choke coil is connected in series with each side of the line and the condensers are connected across the line at two points in the filter circuit. (Continued on page 1056)

General view of the home-built "A" power unit, with its metal cover removed. The symbols identify apparatus similarly marked in the dia-gram and the description below.

### Socket Identification Made Easy by Color-Code System

A COLOR-CODE standard for tube desments and with this system, which is now gaining popularity, the danger of making a mistake and the hesitation or confusion, which usually accompanies placing tubes in the sockets of a new set, are eliminated. The large variety of vacuum tubes and

circuits now being used has made it impera-

the shock-absorbing feature is not affected by the use of stiff bus-bar wiring in the receiver. The sockets, which are compact in design and of neat appearance, are made of molded bakelite with a black base on which are mounted four binding posts and also soldering lugs. The sockets are made also in strips of five, as illustrated in these

Manufacturer, The Benjamin Electric Manufacturing Company.



An easy method of distinguishing three different types of vacuum tuber, used in modern receivers, provided by the color-code system shown above; the babelle strip above contains six sockets mount in the usual order.

# A Loud Speaker with Linen Diaphragms

Unique Construction Gives Instrument Wide Frequency-Response Range

HROM the standpoints of both construction and performance, the loud one of the nost unusual instruments of its kind the staff of Ramo Nrvs has seen or heard in some time. The speaker, which represents the staff of Ramo Nrvs has seen or heard in some time. The speaker, which pragma is the staff of two square displargam someticed on parallel frames, with spargam someticed on parallel frames, with spargam someticed on parallel frames, with together. The instrument does not resemble even remotely any of the hundreds of comnercially-made loud speakers that Kamo years.

The square vibrating diaphragms are made inherenced interperated after of higher and lines, specially treated after of higher and the same and the state of the able effects of changing conditions of tenserably process, each piece of lines, twenty-and the same and t

accurately determined, and the two points are drawn together and clamped by a hollow threaded bushing with a locking nut on



The curvature of the linen diaphragm is made plain, in this illustration, by the shadows east upon it by the wood bars which hold the

Illustrations on this page courtesy of the

each side. As the diaphragms were stretched quite tight before, they now assume a slightly concave shape, and become so taut that when tapped with a finger they respond rumblingly like a At the point drum. where the centers are clamped, the linen tapers sharply to a narrow bottle neck, about a half inch in diameter. The tension

on the cloth is very great, but the special material used seems to withstand the strain without stretching or tearing.

Two parallel wooden bars, spaced about free indees apart, run across the outer face of one of the square frames. These support a hasky load-spacker driving unit (of the space of the space of the space of the first sheet). This unit is carefully centered, so that its driving pin sides into the bullow bushing exactly at right angles to the plane of the two 24-inch frames; the pin of course, is beleed against the bushing.

### PROOF AGAINST OVERLOADING

From the foregoing description it becomes obvious that the weight or tension of the vibrating disphragms does not act as a vibrating disphragms does not act as a force although it might be imagined that the highly-tant disphragms require a great deal of power to actuate them, even the alightest movement of the drive pin is transmitted in unusually sensitive, and operates with great volume even on moderately strong signals.

The new speaker is capable of handling for more power than is required for all for more power than its required for all for more power to the compact of the example. It was used in emigration with a towastage transformer-coupled audio ampilliter employing two 210-type power tubes a towastage than a first example of the conwast numed in, and a direct example on was made between this speaker and another, of the cone type, of probably the best design more started to ruttle when a certain volment started to ruttle when a certain volme level was reached; whereas this linea disphragm speaker continued to operate the complete of the control of the control of the control of the control of the amplification up to the limit of the capilification.

#### VOLUME WITH QUALITY

The performance of this new loud speaker, as judged by the ear alone, is remarkable for its brilliancy and faithfulness over the whole range of musical notes transmitted



Robert F. Goodwin is shown above, pointing to bushing which draws the two lines diaphragms together. This illustration gives a good idea of the size of the speaker.

by a high-class broadcast soution. Violin music comes through high and clear, without appreciable flattening of the high notes; while the sounds of drums and the low tones of a plano boom forth with clarty to the speaker to the box notes is somewhat disconcerting at first to a hearer uncentioned to such reproduction; but, in a room of favorable acoustic properties (i.e., one furnished generously with rugs, thick curtains and similar echo-killing matching their purious surfaces.)

The actual range of frequency-response of this speaker, according to tests made in the laboratories of the manufacturer, is from 30 to 8,000 cycles. This more than covers the modulation range of the average



### FIG.1

A side view of the new speaker, showing the

broadcast station. The frequency characteristics of the speaker can be altered by means of the four brass rods which hold the wooden frames together, as these rods determine to some extent the tension on the two linen diaphragms.

The flexibility of the wooden frames allows the owner of the speaker to adjust it to his individual musical tastes. Some people like a low-pitched speaker; others prefer a high one.



"Standing By" for "Contact"—A Few Hints on Diagnosing Faulty Operation or Silence in Your Receiver, Before Calling In the Doctor

By L. B. Robbins

HY is it that, in the midst of the finest program you ever listened to, and with the set tuned up to top notch-"A" battery freshly charged, new "B" batteries and everything hitting on all six-the blamed thing suddenly goes dead? It's one of those things difficult to explain, but one of the things that, seemingly invariably happens with company hanging around to criticise or sympathize. Anyway, it's the cause of that universal malady, "The Broadcast Blues." These "Homes of Silence," in such cases, are usually due to some faulty contact in the set, speaker or headphones and it's not so difficult to trace it out, if the job is taken up systematically. Let's see just what can be done to open the program again in the shortest possible time.

First, look at the phones and see if all connections are tight. Are the cord tips in the plug or has one of them pulled out? Take a glance at the connection on the phone itself. Some types have on the outside of the shell a nut which may have dropped off and released the cord. In that

case it's only a small matter to replace the nut and the cord or ind another nut to replace the lost one. When cords are connected inside the shell, unseriew the rubber cap and disphragm and see if the cords are still held tightly by the little contact serews next to the magnets.

The loud-speaker cord should be examined in the same way for loose contacts or open circuits. If the cord itself is thought to be broken, test it out by connecting the two terminals at one end to a pair of dry cells and the other ends to a flashlight lamp. If the latter lights the cord is O.K.

#### TRYING THE TUBES


Next look at the tubes in the set and ascertain if they are seated down in the sockets and are all lighted. If one is unlighted take it out and put it in another socket. If it won't light there the filament may have burned out. The chances are, bowever, that a filament prong was not making contact with the spring in the socket. Press the tube down well and, if it lights and the music suddenly comes on, that was

the cause of trouble. Remove the tube, disconnect the battery leads to the set and then prv up the socket springs slightly with some handy tool until the tube prongs will make positive contact with them. Before replacing the tube brighten up the prongs with a fine file or bit of emery paper. If the tube will not stay down in the socket, look at the bayonet pin in the side of the base, if an old-type receptacle is used. This sometimes works out and there is nothing to hold the tube down in the slot. The only way to remedy this temporarily is to press the tube down and then drive a wooden wedge in between the tube base and the socket, for the time being. A toothpickend will do for this purpose.

If the binding posts of the socket are loose it will be necessary to remove the socket. In this case brighten up the springs, press them up and take up the springs, press them up and take up the play in the springs and binding posts with a a serewdriver and wernet. In sockets of the UX type, the springs sometimes are pushed back by the tube pins and do not make contact with the latter. Examine them carefully for this trouble.

Do not work on sockets or any other piece of apparatus in the set without first disconnecting all battery wires. Neglecting his point may result in indownout tubes, because of a short circuit made by the tool you are working with. And tubes are not cheap, even yet, and often cannot be reticularly, you may be raught with an inoperative set, and no open radio stores to visit for new tubes.

After examining these possible causes of broken contact, look to the jacks; those flat-spring affairs into which the phone plug fits. Here lies a very common cause of trouble. The usual set has from one to three jacks and each one should be inspected thoroughly. The most prevalent trouble is from dirt or scale lodging between the tiny contacts between the springs. The more springs the more contacts; clean between them with a cloth wet with gasoline. Then slide a very fine file (a nail file will do) between them several times, later brushing or blowing out any filings. Test the springs themselves, to make sure one makes solid contact with its neighbor. Insert the phone plug and see if each spring makes positive contact with the halves of the plug shaft and if the other springs make contact with each

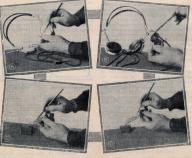


In Fig. 4 is indicated the nut on the rear of a phone that might be loose. Fig. B shows a loose connection at the play. Fig. 6 and D illustrate possible places of poor contact in jucks. Remember that a radio receiver is no better than the poorset contact, and look to the little details that many on much.
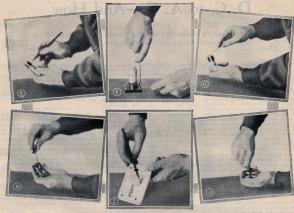
#### THE LIGHTNING ARRESTER

other.

The lightning arrester is seldom thought of in connection with a broken program; but it can cause more trouble than can be imagined, especially in a rain storm. Some-



In Figs. E and G are pointed out possible poor contacts in tubes; in E the "bayonet pin" is pointed out. Figs. F, H and J show how to repair loose or dirty contacts in vacuum-tube sockets. Fig. I points out a place in a lightning arrester where dirt and moisture might cause trouble.

types use open contacts with a carbon button between. If moisture leaks down and lodges between the contacts, it shorts the antenna signals to the ground wire and all you will hear is silence. By using a seaded, vacuum-type arrester this trouble can be eliminated. In the case of a shorted gaptype arrester, remove it and take off the back so that the gap can be wiped dry. Then replace it in as dry a location as possible and seal the removable back with rubber cement. Keeping it inside will, of course, keep it dry; but this is not always possible. Better buy a vacuum type and feel assured of safety, in that direction

With all these possibilities thoroughly gone over, you should have found some one of them to account for the interrupted program. Of course it is assumed you have first ascertained that the particular station has not shut down temporarily due to breakdown, SOS, or some other cause. Turning the dials to some other wavelength will soon determine if the set is working. Just a few trials of the above directions may be the means of again getting "on the air" without having to keep your guests waiting too long "standing by" for "contact".

# Repairing Simple Ailments of Radio Receivers

By Clyde A. Randon
usually results about six months after the

This average radio listener knows very little of the internal functions of his radio set, so when something goes wrong with the cannot supply the proper correceration parts which are sometimes the cause of failure and the expert repairman can usually tell, from the symptoms which cancers, it is the purpose of this article to point out failings and to entitle the proper point out failings and to entitle the proper

A common failing is a gradual or sometimes sudden diminution in loud-speaker volume from stations which ordinarily are quite loud. The expert repairman, when summoned, will first ask about the condition of the batteries. A decrease in volume installation of new "B" batteries and about one month after new drycell "A" batteries are installed in the average set. If you have a small dollar voltmeter you can test they yourself and thus probably save the repairman's wages. If a "B" socket-power mits used one usually does not have trouble from this cause.

The average radio fan imagines that zonething has gone radically wrong when a sinple allment results. As a matter of fact, very little can go wrong in a modern receiver. Perhaps the set has been moved slightly and a wire has become disengaged. The ground connection may have become corredded or the aerial may have blown down. The batteries are usually connected to posts which are plainly marked, "A+," "B-," etc., and one should find little difficulty in replacing the loose wires, if any (see

Often, the bearings on the condensers inside the set have become worm and the plates scrape at certain positions, of the dial, producing peculiar noises in the loud speaker. One can lift the cabitet over a castly determine which condenser is easily the control of the condense of the case of the theory of the condense of the condense of the theory of the condense of the condense of the stator plates; the former should he so bent as to pass freely between the other plates.

(Continued on page 1046)

# D. C. to A. C.-And How



How a Receiver Ordinarily Using D. C. Tubes can be Converted into an Electric Set by the Use of Adapters and A. C. Tubes



HERE is considerable confusion in the mind of the general public as to what constitutes an A.C. radio set. Various interpretations may be made of the degree to which an particular power combination can be considered an A.C. unit: it is not the purpose of this article to discuss this question, for its answer is to some extent a matter of opinion. We will briefly describe, however, what is generally accepted as the nearest approach to alternatingcurrent operation; namely the use of raw A. C. directly on the filaments or heaters of all the tubes in the set. Some people have been led to believe that the use of tubes does away with transformers, "B" power units and the like. Such is not the case, however.

For the benefit of a great many experimenters and home set builders who wish to convert their present battery-operated sets to the use of A.C. tubes, this article covers the changes required in an average six-tube set of the tuned-radio-frequency trees.

#### THE TRANSFORMER

For equipment, a step-down transformer for filament or heater current is the first requisite. The choice of this transformer whiles to use only the separate-leaser tubes of the 22r type; or whether the raw AC-filament tubes of the 22r type; or whether the raw AC-filament tubes of the 22r type; or whether the raw AC-filament tubes of the 22r type; or whether the raw AC-filament tubes of the 22r type; or whether the raw AC-filament tubes of the 22r type; or whether the raw to be used, the transformer should be capable of delivering 1.75 amperes per tube, at 2.5 volts, without any material drop in

voltage; it is preferable to have at least a 15% overload factor above these requirements. If the 226-type is to be used in the R.F. and first A.F. amplifying stages, the transformer should deliver also 1.10 amperes per tube, at 1.5 volts. It is advisable to use for the last audic

It is advisable to use for the last audic stage a 171-type tube, which is operated on raw A.C. at 5 volts. The transformer should have an additional 5-volt winding for this tube.

Unfortunately, A.C. line voltage throughout the country varies a great deal in two ways. The designed standard voltage of the particular distributing system may be 104, 110, 115, 125 volts or some point between; and, under certain load conditions, the actual voltage at any given point also may vary from hour to hour, above or below the standard voltage of the power station. This latter condition is not common in large communities, where the load is handled efficiently. However, the situation is a difficult one from the standpoint of transformer manufacturers, but several have met the problem by designing step-down transformers which will deliver full voltage at the lowest primary potential that may be expected. This, in turn, means that primary taps, rheostats or resistors of some sort will be necessary when the primary voltage is higher than this minimum.

The reader should not, however, gather the impression that the 226- and 227-tubes are extremely critical on filament or heater current; as in fact a liberal percentage of voltage variation is allowed for in the tube design. Indeed, will it be seldom necessary to change the filament or heater resistances to compensate for temporary line-voltage fluctuation, once your particular wavenge voltage is determined and adjusted for.

Another good reason for using a transformer with over-voltage output at the terminals is that, in various converted sets, some may have more voltage drop than others due to the wiring. It is, therefore, considered the best practice to use a step-down transformer with a liberal over-voltage factor.


### PLATE-POWER SUPPLY The "B" supply device may be any good

unit available and does not differ from that used with the lattery-operated sets. Complete "A B C" power packs designed to supply all power requirements for A.C. sets are making their appearance on the market, and will undoubtedly be widely sold. In considering the purchase of these units, care should be taken to see that they meet the conditions previously outlined.

The center-tapped resistors (R4 and R5) may be purchased in the market, or made by winding up with fine resistance wire a decision with tapped in the center. If a second of the control o
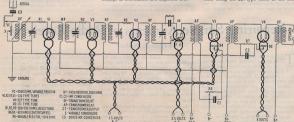
### NEEDED ALTERATIONS The actual rewiring and changes in sets

The actual rewiring and changes in sets to be converted follow in general certain standard practice. We discuss here the average six-tube set, consisting of three stages of R.F., a detector, and two stages of A.F. The accompanying schematic diagram shows the wiring for the conversion when using the 226-type tubes in the R.F.



The schematic diagram shows the wiring connections of a receiver originally designed for D.C. tubes and converted

into one operating with A.C. tubes. X is an optional type of volume control; its range should be 0 to 5 megahmi



Parts used in connection with the new wiring harness: A, by-pass condenser; B, tube adapter for R.F. circuits; C, grid suppressor; D, tube adapter for A.F. circuits; B, center-tapped resistance unit.

and first A.F. amplifiers, the 227-4type in the detector and the III-14ype in the last audio stage. Should the constructor wish to use 227-4tubes in all except the last A.F. stages, the procedure is similar; except that the takes is to be substituted as a connecting point for the center tap of the 227-4tubes. The use of center-lapped resistors at heater terminals of the 227s, with the center lead onging to the cuthods, is also advisable,

The fan who wishes to convert his batteryoperated receiver into a set using A.C. tubes may easily do so, and he will find that there are two methods which he may follow. In one case it is necessary to remove all filament wiring in the receiving set, and then rewire the filament circuits for A.C. tubes. This is a simple operation, but requires some experience in set construction if best results are to be obtained.

For the radio fan who does not feel competent to rewive his set, or who wishes to convert it for A.C. tubes in the least possible time and with the slightest effort, placed on the market simple A.C-stube adapters and harresses. With these adapters it is possible to convert a D.C. set into on using A.C. tubes in a very few minutes, where the possible to convert a D.C. set into vive in the receiver except a few grid wives in the receiver except a few grid

### USE OF A.C. TUBE ADAPTERS

As the adapters are of different types, it is difficult to write a general description which applies to all units. However, each kit is supplied with directions which explain exactly how the installation is best accomplished.

Usually each kit contains one adapter for each tube, and these adapters fit in the tube sockets of the set; while the tubes are inserted into the adapter. These adapters connect the grid and plate prongs of the tubes with the proper terminals of the socket, but insulate the filament prongs from the filament wiring of the set. On the adapters terminals are provided which connect with the filament prongs of the tubes, and the harness is connected with these posts; the harness, which is correctly arranged for A.C. tubes, replaces the filament wiring in the set. In order to light the tubes it is necessary only to connect the free ends of the harness with the proper terminals of a filament transformer.

Arrangements have also been made for installing the extra parts which are required; such as center-tapped resistors, bypass condensers, grid resistors, and biasing resistors. The center-tapped resistors are designed so that they may be correctly connected in the circuit by fastening them to posts provided on the adapter, and the same is true off the by-pass condenses. The 500-olm resistors (Hi, R2 and R3), which are consistent of the constant of

REWIRING THE SET In converting the set without the aid of adapters and a harness, the first procedure is to cut away all previously-installed filament wiring and install the 5-prong sockets, for whatever number of 227-type tubes are to be used. The filament and heater wires should be twisted conductors; the average lamp cord has sufficient current capacity for this purpose. Many sets are equipped with battery switch on the panel; this cannot be used to control the A.C. current unless it happens to be one originally intended for use on 110-volt lighting supply. Should the power switch be installed on the panel, care must be taken to insulate the primary line with the same precautions usually adopted in all appliances connected directly to the house mains. Grid returns of all stages ate brought directly to ground as shown in the diagram. Oscillation control is obtained by use of grid suppressors in the R.F. stages. The correct resistance values for these suppressors may run from 200 up to 700 ohms or over, because of varying circuit and R.F. transformer characteristics; the desired value is the lowest which will keep the R.F. circuits out of oscillations over the entire wavelength range. This method of oscillation control is the simplest for the constructor. Any control system affecting the or volume, which in effect reduces the plate current below the minimum "ripple-voltage point" will not be satisfactory; for, below this critical point, the A.C. hum becomes suddenly apparent. Another procedure for controlling oscillation, which is highly efficient and easily adjusted, is to neutralize the R.F. stages by the conventional capacitive or neutrodyne method. If the set to be converted is a neutrodyne, reneutralization for A.C. tubes will probably be necessarv. Should the set have a coil system depending upon a scarcity of primary turns on the R.F. transformer to make it nonoscillatory, the use of A.C. tubes will increase the tendency to oscillate; in average sets, however, this increase will not reach the spilling point. In general, any method to control oscillation is acceptable, provided the plate current is not thereby reduced materially. By-pass condensers in the R.F. stages are usually essential.

### VOLTAGE REGULATION

In the previous discussion of suitable transformers, the filament or heater-owling situation was brought out. Our conclusions will be a suitable of the conclusions of the conclusions of the control of

For the dealer or service man who expects to convert a number of sets, it is suggested that he prepare strips of resistance units consisting of brass wire wound on fiber or similar material. When the set is converted and ready to install, the correct tube voltages may be determined by finding the proper point of resistance adjustment and permanently soldering or clamping the lead. This adjustment must be made on the fnal set location. Of course, the use of a good low-reading A.C. voltmeter, 0-3 volts, is essential for determining the proper tube voltages; do not use cheap meters, as they are apt to be inaccurate. The dealer or service man should always have a meter of this kind available for A.C .set adjustment; for the individual who converts only one set it would be more economical to borrow a meter for the occasion, as the meter may never have to be used again. Should rheostats be used for the A.C. tubes, special types are necessary; as the rheostats ordinarily used in battery-operated sets are



Illustration courtery Alden Mfg. C.









Dial A controls only the last condenser at the left, while B controls the other six together. The stage shields are marked from S1 to S7.



# An Unusual Nine-Tube Peridyne

Through an Arrangement of Bevel Gears, Seven Tuning Condensers are Controlled by Two Dials; Peridyne Shields Keep Circuits in Resonance



NOTEWORTHY nine-tube tunedradio-frequency receiver, employing six tuned stages with only two tuning controls, through the use of the Peridyne principle of balancing, has recently been constructed. The set employs seven tuning condensers, six of which are mounted on one shaft, while the seventh is controlled separately. This receiver has been designed and built by Mr. Frank Hanus, 2029 East Fortieth Street, Cleveland, Ohio. It is an extremely neat receiver, but quite complicated in mechanical construction, and cannot be duplicated without the use of a rather complete machine shop. For that reason, the circuit


constants are not given here. By referring to the illustration, it can be seen that the two large gears A and B are used for coupling the condensers to the dials. These gears are six inches in diameter and made of cast bronze. Under these gears are two smaller ones, about one inch in diameter, which are rotated by the vernier control knobs which can be seen in the panel view, below the main tuning dials. Because of the size of the smaller gears, considerable vernier action is achieved. The use of these special gears allows the operator to control the condensers directly by rotating the main dials and, when vernier action is required, it can be obtained by rotating the small knobs. This method also keeps the back-lash very small.

ELEMENTS OF THE CIRCUIT

The schematic diagram is not complete, containing only the first and fourth radio frequency stages, and the detector. intervening stages (the second, third, fifth and sixth) have been omitted, since they are duplicates of the fourth stage, audio-frequency also has been omitted, since

have been mounted on the individual shields with the common shaft running through them. Balancing weights have been fastened to the shaft so that a smooth action is obtained when rotating the dials. It will be noticed that holes have been cut. through the tops of the shields, to accommodate the screws controlling the positions

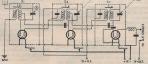) are shown. The mediate stages (5, S5, S6) are exact



it is a standard two-stage transformercoupled unit with no unusual features. It will be noticed that the circuit is primarily a neutrodyne, with total interstage shielding and with the addition of the Peridyne plates over the radio-frequency coils.

EFFECTIVE SHIELD TUNING

The shields are made of sheet aluminum, 4 x 8 x 5 inches. The tuning condensers of the Peridyne shields. This allows adjustment without removing the tops of the shields, and without threading the shield

The front panel is 32 inches long and 81/2 inches high. It has been equipped with a double-reading voltmeter, a control switch and four filament resistors. The switch is arranged so that the filament voltages on the various tubes in the set can be measured. The first filament resistor is used for controlling the filament current on the first R.F. tube. The second one controls the other five R.F. stages; the third the detector; and the fourth the two A.F. tubes.

While this set makes a very neat job and one that any experimenter could be proud of in the line of mechanical beauty, it would be an extremely hard one for the average individual to build; since a considerable amount of special apparatus has been emploved, including several eastings and the special aluminum shields.



The two large dials at the left are the main tuning controls. The four small dials control the various flament resistors.

# Full-Band Tuning in Radio Receivers



A Remarkable New Circuit which Tunes Sharply, Yet



Ru G C'R Rome

HEBUS is a saving which has become almost an axion among radio experimenters, and engineers—that, if see lectivity in a receiver is desired, it is necessary to saverifiee quality, because on the "shiddlends" have to be abaved tool, this taying may become obsolete in a comparatively short time. Dr. Vreeland has developed a radio receiving circuit which permits preat selectivity; yet, at the same time, all the sidebands are amplified equally in this circuit and reproduced in the load

muidal instruments, it is imperative that the "overtone" or "harmonics", as well as the "fundamental" frequencies, he received. As some of these larmonics are of the sixth and eighth order (six or eight times the frequency of the fundamental mote), esclective, for reasons which appear below. Let us assume we have a receiver of the ordinary tuned-radio-frequency type and see how the response curve of such a set appears in an ordingraph. We find that, the matter of a fundamental control of the cont

#### THE SIDEBAND PROBLEM

Just why these sidebands are so important in good reproduction may be, perhaps, not clear to the average fan. Consider for a moment the nature of a modulated radiofrequency wave, such as a broadcast station sends out. Let us assume that we have a carrier wave of 600 kilocycles (a 500-meter wave) which we are going to modulate with speech or music. If the latter is used, we will have the 600-kilocycle wave modulated by frequencies which may be anywhere between 25 and 10,000 cycles, or in some cases even higher. This means that our receiver, in order to reproduce sounds as near like those in the broadcast studio as possible, must amplify a band of frequencies about 20 kilocycles wide, say between 590 and 610 kilocycles (or 600 plus and minus the highest audible frequency which is broadcast, This, in ordinary speech, is the band from 508.2 to 491.5 meters, covering parts of three broadcast channels),

At various times articles dealing with the nature of musical sounds have appeared in Ranno News (see, for instance, page 990 of this issue) and so it will be assumed that the reader is familiar with the fact that, in order to distinguish between the different

SIGNAL WAVE

RESPONSE CURVE

Poll-LL ampliforation over a complete waveland, ut with a tuning sharpness so great as to exclude all other signates, has long been arriently desired by all vails experimenters. The invention of De. Tveeland described invention of De. Tveeland described invention in broadcasting today perturn. Remarkable fielding of reproduction has been demonstrated by an experimental receiver built on this system. As it has not reached the commercial stage, and the proper preparationing of constructional data cannot be given at the present time.—Euron.

(i.e., that a circuit has a definite peak or resonant frequency depending upon the values of it capacity and its inductance) it capacity and its inductance of the control of the control



Dr. Frederick K. Vreeland, the inventor of the band-selector radio receiver.

cycles on each side of the carrier wave, to the great detriment of the music. In Fig. 1 is indicated the amplification of the peak frequency and other frequencies in such a receiver; we see what a relatively small percentage of the broadcast musical notes is passed through the receiver; at 5000 cycles. the reproduction is only a third that of the lowest notes. Yet, if the curve did not have the shape it has (i.e., such steep sides) it would include a portion of the band of frequencies comprising an interfering wave; and two stations would be heard at the same time. Of course it is possible to flatten out the curve so that the peak of the reception covers a greater portion of the 20kilocycle wave; but this in turn makes the sides of the curve less steep and the set less selective.

### WIDENING THE PEAK

The problem then reduces to finding some means that, when introduced into the re-(Continued on page 1053)







SIGNAL WAVE

RESONANT



The Silver Screen-Grid Superheterodyne\*

By Ernest R. Pfaff

This picture shows the new Screen-Grid Superheterodyne mounted in an attractive rullust cabinet. Only two knobs on the front pased are for tuning; one is a regeneration control, one a volume control and one a filament control control.

THE receiver pictured and described herewith is an eight-tube superheterodyne employing three of the new screen-grid R.F. amplifier tubes in the intermediate-frequency amplifier, which is a laboratory-assembled and tested shielded unit, and which effectively clininates all possibility of anything less than peak performance in the lands of even the

most inexperienced builder. The real value of the screen-grid tubes in this receiver can best be realized from the statement that the amplification factor in the three-stage 112-kc, intermediate amplifier approaches 40 per stage, as compared to about 20 per stage for 201A-type tubes. Thus, for the three R.F. stages, the amplification when using screen-grid tubes is approximately 40 x 40 x 40, or 64,000, as against 20 x 20 x 20, or 8,000 gain for the same amplifier using 201Atype tubes. These values of amplification were obtained under conditions of coual apparent selectivity; for it must be borne in mind that, as the sensitivity or amplification of a radio set is increased, the selectivity must go up far faster to maintain the same apparent selectivity in tuning the set. Actually, if the receiving range is doubled, selectivity must go up four times, merely to hold the apparent selectivity constant. Therefore, in designing a screen-grid amplifier, great care must be used to prevent the loss of selectivity from accompanying the increased amplification.

HIGH INTERMEDIATE PREQUENCY In the screen-grid "Laboratory Model" receiver described herewith, not only have the factors of increased amplification and increased selectivity been given careful consideration, but also that of tone quality, so generally neglected or, of necessity, slighted in very sensitive superheterodynes. Through the use of an intermediate frequency of 112 kilocycles, high amplifier selectivity has been obtained and the cutting of side bands is brought entirely within the operator's control. Either he may have medium range, ultra-high-quality reception or, by sacrific ing tone slightly, he can boost the sensitivity of the set to a point where local noise and static, ordinarily very weak, comes in as a roar, and stations not ordinarily heard come in loudly.


Another advantageous feature of the 112-kc. intermediate frequency is that, for all stations below 215 meters or above 455 meters, the receiver is a "one-spot" set; that is, stations outside of the 215—455meter range are tuned in at but one point on the oscillator drum dial. Though stations between 215 and 455 meters can be tuned in at two points on the oscillator dial, by taking 25 grid turns off a standard oscillator coil, the set is made "one-spot" for all stations outside the 215-390-meter band. A further advantage of the 112-kc. intermediate frequency is that the two oscillator dial readings, for those stations that do come in at two dial settings, are widely separated: so that, with the sharp tuning of the regenerative first detector, the set is in operation practically "one-spot." Of course, all stations are received at but one setting of the antenna dial, and either a loop or a short antenna may be used. It is also possible to cut out one of the intermediate amplifier stages and one of the audio stages at will, if desired.
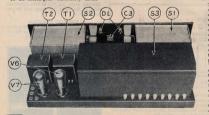
#### SUBSTANTIAL CONSTRUCTION


The set employs a regenerative first-dector circuit (S1) using a 2014-or 200A-type first detector tube (V1), with a place of the constraint of the constrain

Right—This picture clearly shows the arrangement of viving under the steel chassis. Below—General interior view of art with stage shields in place, SI, detector stage; SI, internediate amplifier; TI, TZ, d.F. transformers.





The use of plug-in coils allows different sizes of standard oscillator and antenna colls to be plugged into the set, thus covering all waves from about 30 to 3,000 meters. Following the first detector and oscillator, which may be shielded as shown at S1 and S2 or not, as desired (depending upon whether the set is to be operated in a congested broadcasting center or in the country) is the four-tube long-wave amplifier (S3) containing the three 112-ke, amplifier circuits and screen-grid tubes (V3, V4 and V5) and the second detector circuit and tube (V6). Each transformer and tube is in a separate compartment in the copper shielding, which is 15 inches long, 5 inches wide, and 51/2 inches high, with a cover removable to allow tube insertion and removal. To the right of this LF, unit (which is actually a complete amplifier for time-signal reception), is the two-stage audio amplifier, using a pair of high quality audio transformers (T1 and T2).

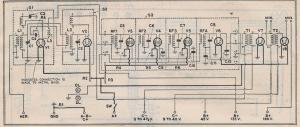

Schematic diagram of the Screen-Grid Superheterodyne. The dotted lines indicate shielding.


amplifier gives uniform amplification to all frequencies between 30 and 5,000 cycles. Above the highest frequency it cuts off to keep down background noise and the alltoo-prevalent heterodyne squeals which are caused by over 600 broadcasting stations being crowded into channels, which would adequately accommodate 95 stations without interference


The entire set is mounted on a pierced steel chassis 10 inches wide,  $1\frac{1}{2}$  inches high, and 23 inches long, to which is attached a 7 x 24-inch metal panel carrying the control knobs. The actual controls are the vernier knobs actuating the two drum dials; an "0n-01" switch (Sw); a regeneration control (C3) for the first detector (the "Sensitivity" knob); a "Gain" control recstat (R3) regulating volume for the three screen-grid amplifier tubes; and a filament rheostat (R2) for the first detector and oscillator.

REALLY "FLEXIBLE" CONNECTIONS

In a number of tests the screen-grid
"Laboratory Model" receiver has been found
to have no equal for DX ability; for it will
reach out from Chicago on a small ten or

twenty-foot aerial, bringing in with loadspeaker volume stations on the east and west coasts that many other receivers will not bring in at all. One LF. amplifier stage can be dropped from the eight take the left compariment of the simplifier (S3) over the partition and elipping it to the top ap of the second take (Vb), whose ellip lead is ignored. So connected and using but two LF, amplifier stages, the set will produce results for distance, tone quality, tained from eller nine and ten-tuke supers.

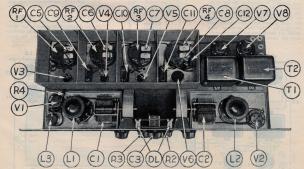

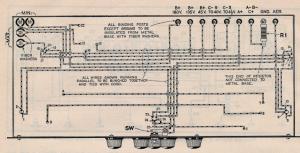

The wiring under the sub-panel, with the connections to be run in a cable, as shown on page 1020.

Even using only seven tubes (if the Sensitivity and Gain knobs are turned up) the set will bring east and west coast stations into Chicago almost like locals on a twenty foot length of wire. Truly, the set is one fully deserving of the name "superheterodyne," for even in the hands of a novice, it tunes in distant station after distant station through a maze of locals with a simplicity that is delightful while an expert an make it run rings around ordinary sets.


The parts used for the screen-grid Laboratory Receiver are named in the list of apparatus which accompanies this article and are all of standard manufacture. It will be found that the different parts bear same symbols as in the drawings and tector and oscillator circuits if the set is to be operated near any powerful broadcast stations. Brass-plate variable condensers of the more expensive type are illustrated in the set, as these allow the dials to turn in the same direction for simultaneous capacity increase or decrease by means of novable shafts. Though the cheaper type made by the same manufacturer are equally

satisfactory, the dials turn in opposite directions for simultaneous oscillator and antenna increase or decrease of wavelengths.

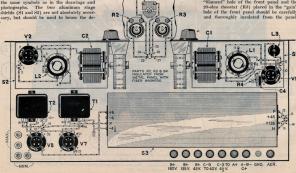
#### PROGRAM OF CONSTRUCTION The construction of the screen-grid

'Laboratory Model" receiver is a simple task, indeed; for the steel chassis and panel are completely and accurately pierced so that the different parts need simply be placed upon them, in the positions in which they appear in the different pictures, and bolted down with machine screws and nuts. A few precautions should be observed, how-

The 6-ohm rheostat (R2) placed in the filament" hole of the front panel and the 20-ohm rheostat (R3) placed in the "gain" hole of the front panel should be carefully thoroughly insulated from the panel,



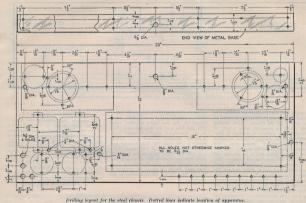Wiring diagram of the parts above the sub-panel. A portion of the front panel is broken away to show the connections on it.




Drumy myone for the steel chassis. Dotted thes marcale location of apparatus,

using a pair of extruded liber washers for each. The "On-Off" withe (Se) need not be insulated from the panel; while it is desirable that the bushing of the midget condenser (G3) shall make good, positive conversable to the state of the st


If variable condensers of the removableshaft type are used, they may be screwed down to the chassis by means of the two mounting feet provided. Both condensers should be put in with their shafts projecting to the right. The two lock collars on the oscillator-condenser shaft should then be loosened and the shaft pushed through to the left so that it projects from the back of the condenser instead of the front; the lock collars being tightened after this operation. If condensers of the standard type are used they are mounted upon the dial brackets which support them entirely; a small extruded brass washer accompanying the dials serves to adapt the small shaft bushing of the condensers to the large hole in the dial brackets. The dial brackets themselves are fastened to the front panel with the drive mechanism slipped into their bushings and projecting through the front panel. The drum scales should be fitted on the con denser shafts to read 100 when the condensers are entirely interleaved, so that readings will increase with the wavelength

The mounting of the different parts upon the chassis is very clearly illustrated in the pictures and drawings. If oscillator and first-detector stage shields (S1 and S2) are used, they are held to the chassis by the different parts mounted in them. It is important to elevate the coil sockets for L1 and L2 above the chassis by means of the %-sinch hollow brass stude slipped over the mounting serves. Terminal 3 of the antenna coil (L1) socket should be to the rear; and terminal 3 of the official terminal 3 of the official terminals of the oscillator coil (L2) socket to the front. The positions of the four tube sockets are clearly illustrated and it should

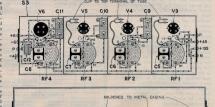be noted that the "A.—" connection of each thus socket is grounded to the chassis by means of a lug under the head of the nearest socket mounting servey. The positions of the audio transformers (TI and T2), choke coil (L3), and time-signal amplific (S3) are clearly illustrated and their mounting needs little explanation, other than



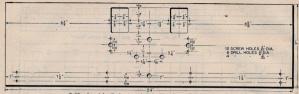R6 R5 R4
Wiring diagram of the top and under dile of the long-wave shielded analytics. The top and under the coupling considerable of the top and under the coupling considerable of the complete, which is a supple of the considerable of the complete of the considerable of the coupling the constant of t



Drilling layout for the front panel of the Silver Screen-Grid Superheterodyne.

to state that the amplifier is held to the chassis by four long 8/32 screws tapped into the corners of its chassis. Each binding post should be mounted, using a pair of extruded fiber washers to insulate it thoroughly from the chassis; with the exception only of the "ground" binding post, which should be grounded to the chassis. The simplest way of doing this is to use one end lug of the 0.57-ohm filament resistor (R1) as a washer for the "ground" binding post, the binding-post screw going through the resistor lug, up through the chassis, and into the binding post. This connection serves to being connected directly to the "A-" binding post (this connection can be seen in the schematic diagram-the resistor should be mounted, not as in the under-view picture, but as explained above.)

#### WIRING

The wiring of the receiver is done entirely with flexible fabric-insulated hook-up switchboard wire, with the exception of the three 'cads, which are put in with bus-bar in spaghetti. One of these bus-bar leads serves to connect post 5 of the antenna coil socket (4) to the stator lug of the midget "sensitivity" condenser (C3); while the other two leads serve to connect posts 1 and 2 of the oscillator coil socket (L2) to post 3 of the antenna coil socket (LI) and the firstdetector grid condenser (C4). All three of these leads should be made of bus-bar in spaghetti, put in in such a way that they are at least %-inch away from the metal. chassis or receiver assembly at any point where they run parallel. All the rest of the wiring, with the exception only of grid and plate leads, should be bunched together as far as possible and, after final assembly and testing, may be laced or cabled, using heavy waxed shoemaker's thread, thus providing a very neat and workmanlike job, as seen in the pictures. The receiver can, of course, be wired with bus-bar in spaghetti throughout, if desired.

The wiring and assembly of the receiver having been completed, all previous operations should be very carefully checked, and the wiring compared with the schematic and pictorial diagrams to make absolutely sure that no errors, which might result in tube burn-outs, or other damage, have been allowed to creep in. This done, the set is ready for operation.

The necessary accessories should be connected to the receiver in accordance with the markings on the binding posts, and all tubes placed in the set. With both filament theoatis. (12 and 13) turned to the left or 'O'!l' position, and the 'On-O'' switch turned on, the two audio amplifier tubes (V7 and V8) and the detector the (V6) in the time-signal amplifier should light. (V7 and V8) and the detector the (V6) turned should be considered to the constant detects (V1 and V2) should light on the constant of the constant value (V1 and V2) should light on the constant value (V1 and V2) should light. The three feedly light should light. The three feedly light should light. The three feedle leads the constant value of the constant value (V1 and V2) and V2 a

NAME OF PART

#### ADJUSTMENT AND OPERATION

To operate the receiver, the filament rhoests (12) should be turned half-way on, the "Sensitivity" know of the midget conciner (Ca) should be turned absolutely all officers (Ca) should be turned absolutely all turned fully on. If the oscillator dial is now rotated, no squeaks should be hearly should they be, it will indicate oscillation of the incremediate amplifier. This would possibly be correct in the case of certain family of the correct in the case of certain family and the concept in the case of certain family and the control of the c

(Continued on page 1060)

MANUFACTURER +

TICT		

C1,C2	2	Variable contensers	.00035 mf. Removable shaft type	1	ALCOHOLD STATE OF STREET	
03	1	Midget contensor	,000075 mf, 17 plates	1	8,9,10	
11,12	2	Plus-in coils	111A true	2	The second second second second second	
ts	1	R.F. choke cell	2,5 millihenries	1 8,9,11,12		
71.72		A.T. transformers	3:1 rette	1 9,11, 12, 13, 14, 15		
91,92	2	Stage entelds	Aluminum - 73 x 33 x 5 inches	0.77		
83	1	T.T. Amplif. (112ke)	2 Stere and detestor (screen grid type)	1	The second secon	
	2	Drum diele	Versier action, sincle tree	-12	Alle States Spanning will	
OT OU	2	Coll sockets	6 Contact true	1		
The state of the s	4	Tube sockets	UX true	1	9, 15, 17, 19, 20, 51, 22, 23, 24, 25	
R1	1	Fixed resistor	-57 Chas (wire wound strip)	2		
12	2	Sheostat	5 chine	2	9, 12, 21, 24, 2, 25, 26, 27, 28, 29	
23	1	Shanstat	20 ehrs	2	9,11,21,24,3,25,26,27,28,29	
04	1	Fixed condenser	.00015 mf. Wice type with cline		3,12,15,16,25,26,27,29,30,31	
Ew .	1	Sattery exiteh	Panel mounting enen type	2	24,26,27	
100	4	Tip tacks			24,26,27	
24 .			2 Xecohes		12, 21, 25, 27, 29, 30, 21, 27, 23, 3	
V1.76		Versum tubes	200A tyre	4	25.36	
12,17	2	Vector tober	201A 177e	14	35.36	
73,74,75	2	Vancum tubes	222 type (spress-prid tube)		35,37	
70	1	Vanuum tube	171 type		35,36	
1000	1	Steel sheets	Plercel, with hardware	8		
277901	1	Frent panel	Piercei ani engravei	5		
-	9	Stading posts	2 10 M	6	9,21,22,25,57	
		Connection wire	Insulated		25, 28, 39	
1/200		1	7	10	10,000	
	24	Control Color	Amplifier 83 is sold as a unit in	1000	Charles Salvanna and	
			completely wired form,	VI.	Sara admits beneficial de	
	-	NUMBERS IN	LAST COLUMN REFER TO CODE NUM	DEDS	BELOW	
1						
4 F. T. Co	not no	ell, Incorporated	2 Carter Feite Company 3 Palymet Menufacturing Comp 3 Van Beern Company 6 Tel Jaharet Programme		Laborateries, Incorporated	
7 Acres W1	ce. Co	EDALT	A Harmarband Excufacturing Commany			
O Allen D	Cer	dwell Company		12 Les	lie F. Mrter Comment	
Pagens	Plest	ris Company	14 Thordarson Eleo, Mig. Company	15 Ele	estrical Research Labe. (forsa)	
		tric Company	17 Presen Electric Company	15 Per	renti, Incorporated	
All-Ann	Cloar	Radio Corporation	20 Airgap Products Company 23 Decimain Flor. Mrg. Corpore	21 Amaga Products, Interporated		
De Ball	NO. 33	ota Company	76 Year Touristant Company	24 Herbert M. Frost, Incorporated		

\* THE FIGURES IN THE FIRST COLUMN OF MANUFACTURERS INDICATE THE MAKERS OF THE PARTS

If you use alternate parts instead of those listed in the first column of manufacturers, he careful to allow for any possible difference in size from those originally used in laying out and drilling the panel and sub-base.

# The All-Electric Everyman Four\*



How to Construct a Four-tube Receiver Operated from an A. C. House Line, using Three of the New A. C. Tubes with a Power Tube in the Last Stage.

By Fred C. Ehlert



HE "Everyman Four" circuit was developed originally for that mammoth body of radio listeners who, living in districts over-supplied with broadcast stations, require primarily a receiver with a high degree of selectivity and yet one that is outstanding in its quality of reproduction. Of course it is realized by all that quality is adversely affected as the selectivity is improved beyond a certain optimum point. Accordingly, it became the task of the designers of the Everyman Four to adjust the two factors until both ends were attained. Strange to say, the

ume obtained from the four tubes. Moreover, since there is no coupling to be considered between primary, secondary and neutralizing circuits, these three circuits, when once adjusted, are sure to be stable and free from cross-reaction as long as the set is used.

It will be noticed also from the diagram that the detector tuning condenser C2 practically "floats" across the inductor; the more usual filament connection to the rotor is missing entirely. Many might think that this arrangement would produce an unstable stage of amplification but, in actual ity of the set. But also they add their part to the ability of this receiver to "go out and get DX." This latter attribute was not one of those taken into consideration by the designers, and it was only after some hundreds of sets had been assembled by enthusiastic experimenters that it becam evident the feature of sensitivity could properly be added to those already to the outfit. Instances have been recorded in which this simple four-tube set had picked up and brought in distant stations which were unreadable on six-, seven- and eighttube receivers.



condensers), C3 (regeneration control), and the volume control at the left of the panel are the only variables needed for the operation of the All - Electric Everuman Four.

ASSEMBLY

In laying out the parts for the All-Electric Everyman Four, the relations shown in the pictorial diagrams should be followed implicitly. As every good radio man knows, it is always possible to alter specifications, if the alterations are carried out according to engineering principles. But it is suicidal to shift coils, condensers and transformers if the builder knows not why he makes the change. The designers could, very possibly, have made a prettier arrangement of the individual items; in fact they tried some others with fair or nearly equal results, but, realizing that simplicity of assembly should be one of the features of the complete apparatus, they made beauty secondary to effectiveness.

selectivity finally obtained practically equals that of the average five-tube receiver embodying two stages of radio-frequency amplification; and the volume is but slightly less than that derived from the best five tubers


Before going into the details of construction of the all-electric "Everyman Four," it would be well to point out still further some of the interesting features of the R F circuit

This set consists of one stage of stabilized radio-frequency amplification, a detector with controlled regeneration, and two stages of high-quality audio amplification. There are four controls, only two of which are commonly used. This makes for simplicity.

The signal impulse from the antenna is fed to the grid of the first tube through a variable-coupling arrangement: this simple device is the only volume control required on the set. In addition, the variable primary can be utilized in extreme cases to increase selectivity.
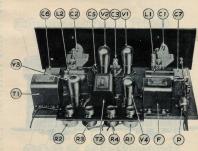
#### A NOVEL R.F. TRANSFORMER

Perhaps the most interesting part of the whole circuit is the unusual form taken by the radio-frequency coil I.2. This coil is a simple solenoid with 66 turns of wire and, from the single winding, come taps for the primary, for the neutralizing condenser and for the tuned detector input. As will be seen from the schematic diagram, the R.F. transformer in the "Everyman Four" is in reality an autoformer; its primary consists of 22 turns and the secondary of 66. This form of inductor insures a high order of signal transfer, which is the principal reason for the extraordinary volpractice, this is not so. Unless the stator of this condenser is improperly placed, there is no hand-capacity, even on the lowest waves to which the set can be tuned. All of these features contribute in their way to the remarkable selectivity and qual-



C1. C2, tuning condensers; C3, regeneration condenser; V1, V2, V3, A.C. tubes; V4, power tube: T1, T2, A.F. transformers: F. output filter: R1, R2, rheostats: R3, R4, potentiometers.

\* Rapto News Blueprint Article No. 49

The antenna coil L1 lies at the extreme left of the baseboard, and the secondary S is supported on a short L-shaped stand. If the baseboard is attached to the front panel at any point other than that shown by the illustrations, the height of this coil support must be changed; as it is essential that the primary coil P match exactly the secondary coil. In other words, the two coils (one fixed and the other movable) must be so arranged that when the coupling is maximum their axes coincide. The distance of these coils behind the front panel is not a vital matter, this being decided usually by the length of the swivel-controlrod of the antenna coil. On the other hand, no harm is done if the coils are brought forward toward the variable condenser, so long as a minimum distance of %-inch is observed.

The coil L2 should be kept at least 8 inches from the antenna coil. If this distance is maintained it is not necessary to alter the axis of the coil. There will then be no reaction even if the coils lie along the same axis.


#### COIL SPECIFICATIONS

If it is desired to wind these coils at home the data will be fr. and of the simplest sort. The coils are wound on forms of formice, 2 inches in diameter. In the case of Li the primary P consists of 14 turns wound in the same direction. It should be seen that the end of the primary and the beginning of the secondary coil are as closeted to the construction of the construction of the to make them. This issues of the possible to make them. This issues the possible to coupling when desired.

The R.F. coil L2 consists of 66 turns tapped first at the 22nd turn and again at the 43rd turn. All coils are wound with

No. 24 D.S.C. wire.

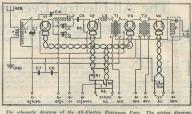Although they play important parts in the operation of the set the location of the neutralizing condenser (C4) and the R.F. choke coil (L3) is not critical. As long as



The schematic diagram of the All-Electric Everyman Four. The wiring diagram, showing the disposition of the parts, is on the opposite page.

SECONANT TRANSPORTED TO THE SECONAL SE

The data for winding the inductors, L1 and L2, will be found in the above sketch. See illustration below for their position.

THE TAP 22 TO THEN

they are placea in such a way as to require no extra leads they will function properly.

The sockets have been placed to give short leads as well as accessibility. It not always best to shift components about with the sole purpose of saving wire; since in some many instances longer leads do no harm whatsoever. Accessibility often means more to the unskilled builder than beauty of arrangement and finese in design.

#### THE AUDIO END


The audio amplification system does not demand a great deal of explaining. Both transformers (TI and TS) were selected because in combination they possess to an those hidden bass notes that give "cound-ness" and beauly to orchestral renditions. Moreover, in so doing they do not cause any particul speech, a trouble which is frequently applied propers. To trouble which is frequently formers. Containing wire of ample size and correst of good iron, these transformers handle well the signal passed on to them. Although not essential to the operation. Although not essential to the operation.

of the "Everyman Four" the use of an output clarifier (F) is advised in order to safeguard the speaker from the high direct current that otherwise would flow through the delicate magnet windings of the unit. So much for the materials located on


So fillulate the materials of the baseboard. The panel comes next. On it are the two 0.005-mf, tuning condensers, CI and C2, the control knob for the antenna compler, and the variable neutralizing condenser C3, through which regeneration is effected. With so few parts on the panel, it is evident that only a few minutes should be required to complete the wiring, once the baseboard has been finished.
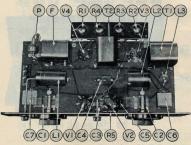
#### A.C. SET DESIGN

In deciding on the tubes to be used, preference was given to the 227-type heated-cathode tubes, because of their greater freedom from hum. This problem is not of such moment when straight tuned-radio-frequency amplification only is concerned; but, in a receiver such as the Everyman play, any residual hum in the play, carried to the R.F. tube is amplified to a point (Continued on page 1984).



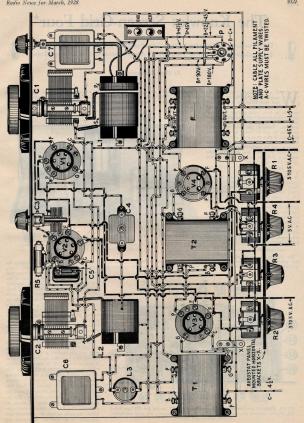13, R.F. choke coil; C4, neutralizing condenser; C6, C7, by-pass condensers; P, cable connector; L1, antenna coupler; L2, plate coil; V1, V2 and V3, Y-type sockets for 22-type tubes; V4, power-tube socket.



# The Knowles Screen-Grid Four\*

0

Constructional Details for a Four-Tube Receiver, which is Simple to Build, and Includes One Stage of Tuned R. F. Amplification with a 222-type Tube

0

By Hugh S. Knowles

W E are continually told that the radio industry is 'nit is infange'' become obsolete. While this would seem to be true, judging from the 'nee'' and 'recultum' of the properties of the and 'recultum' of the properties of the and 'recultum' of the properties of the ception of the tendency, in circuit comlinations, is that of a stage of tuned-radiofrequency amplification with a regenerate detector and an analo-frequency amplifier, and the properties of the properties of the properties of the common of different name—such variation of the properties of the common of the properties of the properties

calling for a new name.
The fact that this circuit arrangement is still very popular, although it has been indicates that it has definite survival value. With the advent of the serven-grid (222-cr in rande-frequency amplification, it is very natural to ask whether this popular circuit arrangement can still the such additional to the control of the servent and the such additional area of the control of the co

old circuit with the expectation of getting greatly-improved results.

FLEXIBILITY OF OPERATION

The receiver we are about to discuss is one which combines the features of this well-known circuit arrangement with the modifications made necessary by the use of the 222 tube. The merits which have been much more difficult in a receiver using five carried over may be summed up in the



T3, output transformer; L4, R.F. choke coil.


word "performance." This is due to the fact that each tube is made to operate at


C1, C2, .00035-mf. condensers; L1, L2, coupling coils; V1, socket for 222-type tube; R2, 15-ohm resistor; R3, grid leak; C4, C5, by-pass condensers; C6, grid condenser; R1-SW, switch and rheostat.

\* RADIO NEWS Blueprint Article No. 50

In performance the receiver combines the features with have made the sets using the 2014-Yepe table popular, and those that the performance of the comparison of the compariso

The antenna coupling may be varied (in the coil L1) to suit the type of antenna used and the amount of interference that prevails in a particular locality. The radiofrequency stage (S1) is tuned separately; which insures maximum amplification. The detector circuit (S2) has a separate tuning control, which may be operated in unison with the R.F. stage control on local stations, but may be more closely adjusted for the reception of distant stations. The iudicious use of regeneration by means of condenser C3 makes the detector stage contribute its quota to both the selectivity and sensitivity of the receiver. This point will be discussed in more detail later.

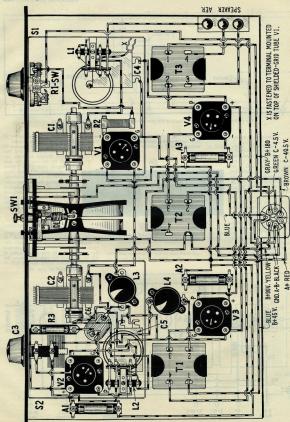

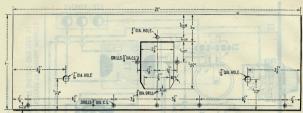

The drilling details for the front panel of the four-fube, screen-grid receiver, illustrated below.

ELEMENTS OF DESIGN

use only the best parts obtainable, to insure corresponding performance, it is imimple matter to portant to build a receiver which is simple

It is a comparatively simple matter to make one laboratory model of a receiver which has exceptional performance; but it is a very different thing to build a re ceiver which may be duplicated by the thousands in the homes of set constructors, not only in parts or appearance, but in performance as well. When this is considered we have a clue to the popularity of the R.F.-stage, regenerative-detector combination. Such a circuit normally has no component parts which have critical values; in other words, it is a production receiver in the sense that it is easy to duplicate and

can be relied upon for excellent results consistently.

One of the most important motives in building a receiver is the economic one. Since the set builder is usually willing to

(W)



C3, condenser controlling regeneration.


and which uses as few components and tubes as possible. This is another important

reason for the survival and popularity of the circuit combination we have in mind. An inspection of the wiring diagram of

the receiver will show that two principal changes are made nocessary by the use of the new screen-grid tube (V1). These are the omission of the balancing circuit, which is a distinct advantage resulting from the low interdectrode capacity (from control grid to plate) and control of the plate of the control of the plate of a transformer to couple the radio-frequency stage to the detector.
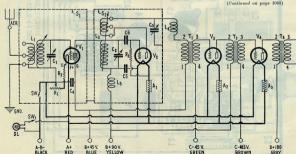
### SPECIAL TUBE CONSIDERATIONS

Although no balancing circuit is used, it is important to minimize the capacity between the plate of the screen-grid tube and the control-grid. In this arrangement, it will be seen that the plate lead leaves the shield compartment within half an inch of



The schematic diagram of the screen-grid receiver described in the above article. The dotted lines indicate the shields enclosing R.F. portions of the circuit.

# The Pacent Distant-Signal Amplifier\*

0

Using the New Screen-Grid Tube in the First Stage,
This New Audio Amplifier Quadruples Amplification

0

By Gerard J. Kelley

HO hasn't been routed out of bed at one time or another to 'bient the Coast'? Few indeed are the Easterners who haven't been coased from between warm covers with the promise of listening to KFI or KHJ. One can't blame any normal radio enthusiast for disturbing fair dreams in his desire to list of the coast of th important being its extraordinarily high "ma" (amplification constant.) The possibilities of this remarkable new tube are many, and a lengthy treatise might be written upon its uses and applications. Experiments conducted towards the ultimate design of this distant-signal amplifier brought out several interesting points.

The 222-type tube is intended primarily for radio-frequency work. In this function, however, it requires special layout of parts, real shielding, and the use of special circuits. To do this with the information at hand, night be a little too much for some builders. As a detector, it has been found quite microphomic in fact, so sensitive to quite microphomic in fact, so sensitive to all the properties of the properties of the sensitive to the properties of the properties of a bit and all the properties of the properties of the obstance.

 as to its ability as a detector could be obtained. Properly used as a first-stage audio amplifier, however, this new tube offers most extraordinary rewards. It is an ideal firststage amplifier of distant signals. This discovery, made while experimenting with the first of these these available, led to table to a new distant-signal amplifier, which is here multilated in its final, perfected and

The presentation at this time will undoubtedly be of special interest to those radio amateurs and broadcast listeners who strice each year to bring in Europe before the weather becomes warm. In the past at limited number of people have succeeded in getting European signals through the detector, only to have them so weak that they are practically inauditible. For those who went better solume on DX work, without

simplified form.

Schematic diagram of the Distant-Signal Amplifier, which utilizes a 222-type tube (V1) in the first stage. Pictorial wiring diagrams will be found on the following pages.

to sweet music three thousand miles away. Sometimes, but rarely, the desire is fulfilled to the full extent. But how seldom!

Many of us. I am sure, have beard the Coast. But the question is, how well have we heard 11? The carrier is there, no doubt about it; but the anisoneous and the about it; but the anisoneous and the and not infrequently, very good imagination are essential to identify the brandcaster. Let's not belittle those persistent operators to be used to be to be used to be to be used to be to be used to

of DAN.

The relet us offer these same distance enthusiats a simple means of briging in farway broadcasting with more votume and power. Here is where the nexty designed distant-signal amplifier proves of creanchable assistance; for it offers more audio amplification in two stages than has every been available to the experimenter, thus far, with the same applied battery voltages. Probably nothing in audio ambient of the same worth-sellig results with such the same worth-sellig results with such

#### USES SCREEN-GRID TUBE

Most radio experimenters have undoubtedly heard of the new 222-type, screen-grid tube and its interesting features, the most \*Rapio News Blueprint Article No. 51

T) R3 T3 R3

T1, T2, A.F. transformers; T3, output transformer; R1, 30-ohm variable resistor; R2, grid leak; R3; amperite; J1, J2, jacks; V1, 222-type tube; V2, power-amplifier tube.


going in for high-priced, claborate amplifying equipment, this simple amplifier is

#### COMPARATIVE AMPLIFICATION

Comparing its total amplification with that of a standard two-stage transformercoupled amplifier, the superiority of the former becomes immediately apparent. The voltage amplification for a two-stage transformer amplifier (transformer ratio 3 to 1, a 201A-type tube in the first stage, and with 90 from the distant-signal amplifier shown in the accompanying schematic diagram.

It is obvious that we have more than four times as much amplification available-with the 222 distant-signal amplifier; or, speaking roughly, on a week DX signal, we should be able to receive the signal with at least four times as much volume on the speaker. Surely an amplifier with this extraordinage, advantage appeals instantly to anyone interested in better distance reception.


It should be understood, however, that the use of the new amplifier is not restricted to DX work; as a matter of fact, this new audio system may be well cumployed with any standard set for both local and distance work. Considering the unusual amplification available, it is apparent that the amplifier should be worked nowhere near its full capacity. On a strong local signal, and with the amplifier soin fall tilt, there

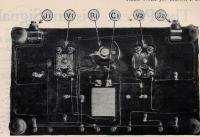


The under side of the horizontal panel of the Distant-Signal Amplifer. The parts here are lettered just as they are in the schematic and wiring diagrams. About one-third of the potentionseter R1 has been shorted, as shown by the white portion of the wire.

is no available output tube which will satisfactorily handle the load. Rather than any gain in this case, a distinct loss in tone quality will result. When properly handled, however, the amplifier gives excellent quality on strong signals; the only adjustment needed is to cut down on the 30-ohm resistor RI (which is a potentiometer connected as shown in the schematic diagram).

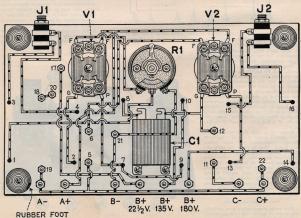The distant-signal amplifier is excellent also for use with an electric-phonograph pick-up. For this purpose, it can be con-



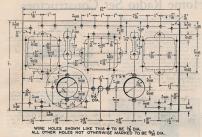The wiring diagram of the under side of the panel is here shown, with numbers and letters corresponding to those given in the list of parts, which may be found on page 1073.



The drilling layout for the only panel used in this amplifier, which is one especially simple to construct.

nected to the receiving equipment in the regular manner, and an adapter placed in the detector socket of the set; or a plug from the pick-up can be run to the input jack of the amplifier, and the receiving equipment left unchanged.

### FEATURES OF THE DESIGN

In starting the design of the distantsignal amplifier some months ago, a number of obstacles were encountered, and were overcome only after considerable work. The first problem centered about the type of coupling device to use in the amplifier. The first Hought was of impedance coupling to work in conjunction with the 22 tube. Investigation showed that there were no available units with an inductance greater than 150 hearies.

Straight transformer coupling was out of the question, inasmuch as no transformer is made with electrical characteristics suitable for work with this new tube.

Finally the idea of autotransformer coupling was considered, and one unit was found that had an inductance of over 300 henries; but this was not enough. After further investigation, the audio transformer (T2) named in the list of parts was selected for use as an autotransformer, not as a regular audio transformer. This choice resulted from the discovery that the transformer maintained a high secondary inductance, about 600 henries, with a high value of current through it. With this in mind, the transformer was selected as the ideal coupling device for the 222 tube, when used as an autotransformer with primary and secondary connected in series.

### CONSTRUCTION IS SIMPLE

Once the problem of coupling was solved by finding a unit with a high value of inductance under high current load, the task of building the complete distant-signal amplifier became comparatively simple. The (Continued on page 1073)

The holes, which are numbered in correspondence with those shown in the diagram opposite, are for the wires connecting the apparatus on the under side of the horizontal panel. Note the simplicity of the wiring.

## Letters from Home Radio Set Constructors

#### A SIMPLE COIL MOUNTING Editor, RADIO NEWS:

I am watching your magazine very closely, building very nearly everything big, just to get some-thing better, you know. That is how I spend my

spare time.

I believe very positively that Mr. F. A. Jewell has the right idea on the audio amplifier. I have mine unit-huilt, and at present am booking it to the Strobodyne circuit just to see what it will do.

Here is a very simple little idea for the novice, to vary the primary coil. I extend the coil and

to vary the primary coil. I extend the coil and mount this device on a separate piece of insulation, using pin jacks if I wish to make it a detachable coil. All the coils I make are space-wound on strict celluloid. If a fellow uses a little patience, he can celluloid. If a resson the make a very next and inexpensive coupler than looks as if it is factory-finished. (See third column).

A. W. DOUGHERTY, A. W. DOUGHERTY, 4350 Lake Park Avenue, Chicago, 111.

### THAT JAPANESE CIRCUIT

Editor, Ranto News:

I thank you for kindly publishing my letter con-cerning the "Crossdyne" in your October issue.

Since I forgot to write the data of the "cross-formers," etc., I have received many letters, about a hundred, from all over the world—Czechoslovakia, nmark, Canada, etc., asking for them.

The Crossformer is a high-frequency regenerative transformer; but quite different in construction from the ordinary R.F. transformers, because the hination of the tickler and the primary. The coils are designed to have low capacity between wind-ings; and, even with the multiplication of regenera-tive stages (as in the former diagram, which showed a triply-regenerative set) this prevents radiation

secondary as well. Thus harmonics, quite different in frequency from the fundamental signal wave, are set up. To remedy this, the inventor of the Crossformer has developed this R.P. transformer, with the especial purpose of producing a receiver adapted to DX.

anispted to DA, The specifications of the transformer are: pri-mary, 15 turns of No. 25 D.C.C. wire on a 2½-inch tube of bakelite or ebonite, 2 inches long. The tickler is wound with 18 turns of the same wire on the same form, at right angles to the primary. A gap of 1/31-inch is kept to lessen the capacity between them. The secondary is wound in "basket" form 3 inches inside diameter, with 57 turns of torm 3 mehes inside diameter, with 57 turns of the same wire. The combination of primary and Sckler is inserted in the opening and fixed with strips of insulation. This transformer, with a .00035-mf, variable condenser, will cover the broad-cast range. It is designed for use with the 201A-type tube; and some modification may be necessary type tube; and some modification may be necessary for use with any other. This information is obtained from the manufacturers, the Mejiro Mfg. Co., Takadamachi, Tokio-fuka, Japan, In my crosselyne receiver, which was diagramed in the October issue, the R.F. choke coils are Samson No. 85, and the tubes either R.C.A. or

MINORU NAKAMURA, Yamate, Oiso, Japan.



The appearance of the "crossformer," a Jap-anese R.F. transformer, in which the primary is wound at right angles to the tickler.

#### AN EXPONENTIAL SUPER-HORN

The articles on exponential horns are very inter-esting to me. I am somewhat of a speaker "nut," having constructed all types of speakers. I set to work and constructed half a dozen borns such as Mr. Millar described in Ranto News for October, Mr. Mutar describes in Ansire own to Con-pley? they all gave excellent results. We have a My beether, who lives in Receiville, Va., has a very powerful raile, and also a powerful unit, be ship it, it was necessary to make it in sections. It is 20 feet long, with five four-foot sections. It is made of beave-board. Each section is nailed tegether and pasted at the corsers with gummed-paper tape. Wooden strips, one-inch square, are nailed to each and of a section; and these are

are nailed to each end of a section; and these are bolted together. The results with this horn are simply wonderful,



Mr. Dey is standing directly in front of his 20-foot exponential horn. Its size may be gauged by comparison with its surroundings. (It is not recommended for use in a port-

I have several telegrams from my brother in regard to the wonderful results he is having with this horn. A five-mile range (over water) is easy. A specially-powerful unit, of course, is required. If the photograph and letter are of interest to anyone, I will be glad to give more details in regard to construction to anyone writing me.

gard to construction to anyone writing me.

J. Bascon Day,

3454 Fort Avenne, Lynchburg, Virginia,

(We are afraid Mr. Dey doesy't know what he ix
his for. Some of our other contributers have discovered something-about the letter-writing ability of

Radio News' readers. However, we would ask that readers avoid writing for details to constructors of a complicated device like this, unless they seriously intend to attempt the construction of one like it .-

#### EXCELLENT WORK WITH THE "PERIDYNE 5" Editor, Ranio News: I am not much on letter writing and, if I had

I am not much on letter writing and, if I had my choice between writing letters and building radio sets, I would prefer building; but this, is about your "Peridyne 5," which I built, as per your instructions in Radio News for December.

As soon as I read the article and saw the Interflex principle was used, I knew it was good; as I

ALARM CLOCK HAIR SPRING CELLUI OID HARD RUBBER OR MICARTA



Mr. Dougherty's variable coil-mounting device is an ingenious bit of wire-twisting. A round-nose pliers and patience are required to make a good job.

built the Interflex when you first published it in 1925. I carried it to San Diego, Calif., on a trip the same year, and built quite a number of these circuits in San Diego. In fact, I hired a man to help me wire these sets, day and night, and every one gave complete satisfaction and is still working

one gave complete satisfaction and is still working. So much for the fatterflex circum; "was built according to your instructions and put to work. Colls and shiefds I mude myself, as I have done since 1921. The circuit is very selective, tuning right and shiefds I station anyone desires; volume and quality are very good. The circuit is very selective, tuning right to the collection of th

then taking same to Smyrna, Del., over Saturday and Sunday nights, the following stations were re-ceived:

and Standay nights, the following stations were reKDKA, Filted Standay, R.K., Derindal, Ore,
KDKA, Bitter Standay, R.K., Derman,
KDKA, Bitter Standay, R.K., Derman,
KDKA, Bitter Standay, R.K.,
KDKA, Milled A.K., RKKA, WHILL, WOK,
KDKA, Milled A.K., KRKA, WHILL, WOK,
KDK, WILL, WILL, KAR, KDK, WALLE, WALL,
WOK, New York,
WOH, WHOMEN, D.M., WK, WARD,
WOH, WEAR, WHILL, WALL,
WOH, Newark, W.R., Springdold, Mane, KWKIL,
WOH, Newark, W.R., Springdold, Mane, KWKIL,
WOK, Newark, W.R., Springdold, Mane, KWKIL,
KUK, WOK, W.R., WOK, W.R., Springdold,
W.K., Springdold, Mane, W.R., Springdold,
W.R., Springdold, W.R., Springdold,
W.R.

The coils I wound as follows: I have two forms

made of wood, three feet long and 2% inches in diameter, cut in half for the whole length, and reated with beeswax. I clamp the form together and cover it with sheet celluloid and wind as many turns of wire as are needed to make a set of three coils. After the winding is finished, I saturate the wire thoroughly with other. This dissolves the colladed and, when the windings are dry, they are self-supporting (as per sample enclosed).

These forms can be made of any diameter and will last forever; but I have found that the 3-inch coll is good for any set. Shorter forms, 31/4-inch and 23/4-inch, are used for primary windings. These can be made to be placed either inside or outside of the secondary. The shields I made from sheet

The condensers and rheostats I used were Pilot; choke was Samson; the high resistor was a Claro-stat, and Amperites were used on the audio tubes.

home, and the crystal was Carborundum, as called for in the original Interface. If your instructions for balancing the set are fol-lowed, no trouble will be experienced by the con-structor; but I found that, as you said, the voltage to the R.F. tubes must be exactly right and using

meters is the best way to know that it is, meters is the best way to know that it is.

I hope you receive other reports as good as this from those who have built the Peridyne, and I am glad you are still catering to the fans who build their own colts, as I think they were the men who made radio popular. There is no more interest shown in them by the newspapers and magazine as in 1922 to 1925, when these papers would show different circuits and the fans would build them, and the oest week build others. I am arer the same interest would be shown and to see it. Whiting you much success with the "Peridyue 5." WILLIAM II, KLERNERGES, 1219 West Eires downer, Philadelphia.

Letters for this page should be as Lebert as possible, for so many are received that all ground the princed. Unless clearly the control of th

ANOTHER VICTIM OF THE MAILMAN

Editor, Ranto News:
Since you published my article on short-wave reception in your October issue, I have had to procure a bigger postoffice box, No. 531 instead of No. 338. Letters come from everywhere asking information; and, as I have no private secretary,

and like a few moments to play with my radio, I wonder if you would not be kind enough to answer my friends in a general way. Since the date of the letter published by you, the Abbé Provencher of Chicottim has constructed a short-wave receiver, using mine as a model. We attribute our success (Continued on page 1983)

### List of Broadcast Stations in the United States

(Continued from page 1009)

TA. \$\frac{1}{2} \frac{1}{2} \frac{1}{



			LIST OF CANA	DIAN BRO	ADCAST CALLS			
CFAC CFCA CFCA CFCA CFCA CFCA CFCA CFCA	Calcary Alta 435 Thromto, Ont. 277 Montreal Calc. 435 Montreal Calc. 4	500 CHGS 100 CHICA 100 CHICA 100 CHICA 100 CHML 100 CHMC 100 CHMC 100 CHMC 100 CHMC 100 CHMC 200 CHMC	Summerside, P. E. I. 208 Townsto, Con. 207 Vancouver, B. C. 411 Confere, Con. 207 Vancouver, B. C. 411 Confere, Con. 207 Vancouver, B. C. 207 Vancouver, Con. 207 Vancouver,	25 CJOR 500 CJOR 200 CJOR 500 CJOR 500 CJSC 500 CJSC 500 CJVC 1000 CKAC 50 CKCD 50 CKCD 500 CKCD	Jethbridge, Alta. 208 See Inland. B. 291 Moore Jare, Sast. 277 Moore Jare, Sast. 277 Saskataton, Sast. 277 Saskataton, Sast. 277 Montreal, Que. 411 Vancouver, B. 411 Hegina, Sast. 217 Ortawa Ogs. 455 St. George Ont. 201 Vancouver, B. C. 411 Red Deer, Alta. 307 Cob'sl. Cost. 283 Toronto, Ont. 384 Toronto, Ont. 387 Cob'sl. Cost. 383 Vancouver, B. C. 412 Red Deer, Alta. 367 Cob'sl. Cost. 383 Vancouver, B. C. 412 Vancouver, B. C.	CKOC	Hamilton, Ont.   341   Searboro, Ont.   911   Searboro, Ont.   912   Searboro, Ont.   913   Searboro, Ont.   913   Searboro, Ont.   914   Searboro, Ont.   915   Searboro, Ont.   915	100 500 500 500 500 500 500 500 500 500



# RadioNews poratories



D ADDO manufacturers are lavited to send to RADIO NEWS LABORADATE of the property of the cold of the

manufactures are published in these paces, and only apparatus which has been tested in the Laboratories and Found of good medicated and execution construction is described. As the service of the RADIO NEWS LABORA-OURLES in the sul manufactures, whether they are advertises or sulvivalent to the substitution of the substitutio

### AUTOMATIC RELAY SWITCH

ubmitted by the S C O Electric roducts, Jackson, Michigan, takes he power line of the trickle charges and the "B" power unit. One lead of the power line is permanently connected to one contact spring of each of the two receptacles built into this device; while the other lead is at-sached to the armature of the relay which closes either the circuit of the

This relay operates, as

CERTIFICATE

from the filament switch of usual, from the filament switch of the radio receiver and is very sen-sitive, as it requires only 0.36 am-pere for its operation. The wind-ing of this relay has a resistance approximately 0.24 ohm, and there-fore, its connection in series with the filament circuit does not affect

sticcably the operating voltage.

the position of a special jumper. The automatic relay switch, which connects to the house line either the trickle charger or the "B" power is controlled from the filament switch of the radio receiver and requires to operate it approximately 0.6 ampere. It has a very small voltage drop across its windings, and is reliable in operation.
AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE F MERIT NO. 2244.





### OF MERIT NO. 1968. "A" POWER UNIT

The automatic "A" power unit Storage Battery Corporation, 508 N.
Capitol Ave. Indiananolis Ind. Capitol Ave., Indianapolis consists of a 6-volt storage consists of a 6-volt storage battery, a trickle charger and an automatic relay switch; all forming a small compact unit enclosed in a sturdy sheet-iron container having a brown crystalline finish. The "A" battery has 5 plates per cell and a 40-ampere-bour capacity. One of the went-plungs is equipped with a small



unit is electrically and mechanically well-designed, and is housed in a strong sheet-iron case with a brown AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2245.

### AUTOMATIC POWER SWITCH

The "Imp" automatic power switch (type No. 115 shown) submitted by the Carter Radio Company, 300 S. Racine Avenue, Chicago, Illinois, is designed to be used in radio receivers



to the power line of either the ti-charger or the "B" power unit.

### snap-switch type and of compact and rugged construction, AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2246,

### RHEOSTAT

The "Hi-Watt" rheostat (type HW6 shown) submitted by the same



most entirely of metal, the amount of insulation being reduced to the minimum. The resistance element is formed of a fiber strip, ½-inch wide, on which a flat resistance rib-bon is wound. The contact arm runs smoothly and provides a good contact with the resistance write. This rheotat has a resistance value of approximately 6 chms owing to its excellent cooling characteristics, and the capable of dissipating continuously is expalled of dissipating continuously 20 watts without overheating.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 2247.

#### FIXED RESISTOR

The fixed resistor shown, submit-ted by the same company, is of the wire-wound type. The resistance wire is wound on a porcelain tube, two inches long and 9/16-inch in diameter, and is covered with a



jury. The average resistance has been found to be very close to its nominal value, the difference being less than one per cent. Rated to dissipate continuously 20 watts, this AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE MERIT NO. 2248.

## BUFFER CONDENSER

mitted by A. M. Flechtheim & Com-pany, 275 Broadway, New York, N. Y., is of the paper type and has

### two sections of approximately 0.1-mf, capacity each, connected in se-





winding of the step-up transformer used in "B" power units using gas-filled rectifier tubes. It is sealed filled rectifier tubes. It is sealed in a metallic can whose external dimensions are 2 x ½ x 1½ inches, and is provided with mounting feet. AWARDED THE RADIO NEWS

### RHEOSTAT

The "Gem" rheostat (type 19 hown) submitted by Herbert rost, Inc., 160 North LaSalle S Frost, Inc.



Chicago, Ill., is of metal-frame on Chicago, III., is of metal-trame con-struction and approximately 1½ inches in diameter. Although small, this rheostat is rugged and of very fine workmanship. All the exposed fine workmanship. All the exposed metal parts are nickel-plated and its general appearance is extremely neat metal parts are nickel-plated and its general appearance is extremely neat and pleasing. The contact arm runs smoothly and makes a perfect con-tact with the resistance strip, which is ¼-inch wide. This rheostat has a resistance value of approximately 6 ohms and is of the one-holeounting variety.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2250.

#### DUPOCTAT The "Gem" rheostat (S 1930



rectifier. Three charging rates (namely, 0.35, 0.5 and 0.8 ampere) may be obtained through changing

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2251.

ADJUSTABLE RESISTOR The shown, submitted by the Mechanical Lab., Inc., 287 North Sixth St., Brosklyn, N. Y., employs as a resistance medium a mixture of graphite and pulverized mira, her-metically enclosed in a small brace container. The longitudinal motion of a special disc inside this con-



very wide range. This instrument may, therefore, be used very suc-cessfully as a volume-control device or in any other place in a radio receiver where an adjustable resistor with a wide range is required. the current-handling capacity of this the current-handling capacity of this unit is relatively small, it is not recommended for use as a voltage divider in "P" power units.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO, 2252.

### SOCKET ADAPTER

The socket adapter shown, submit-ted by the Alden Manufacturing Company, 52 Willow St., Springfield, Mass., permits the use of A.C. tubes Mass., permits the use of A.C. tubes of the 226 type in radio receivers wired for D.C. operation of the fila-ments. This adapter has a built-in UX socket to carry the A.C. tube, at its base with four



standard prongs which fit in any standard UX socket. The grid and plate contact springs of the socket pute contact springs of the socket are connected to the corresponding prougs on the base of the adapter; while the filament springs of the socket are insulated from the beavy prougs of the base, which are in fact dummies. The filament contact springs are extended outside the socket and pages at the context. dummies. The filament contact springs are extended outside the socket and carry at their ends two binding posts which serve to connect them to the leads supplying the low-voltage A.C. The use of this adapter simplifies enormously the problem of electrifying "A" battery.

### FILAMENT POWER TRANSFORMER

TRANSFORMER

The power transformer (No. 4586 shown) submitted by the Dengan Electric Mfg. Co., 2995 Franklin St., Detroit, Michigan, is a step-down transformer and supplies the heating the filaments of A.C. tubes of the 226 and 227 types and of a power tube of the 171 or 112 type. It has three separate windings for current supply at 1½ volts, 2½ and 5 volts. This transformer is of good electrical design and well built. It is



LABORATORIES CERTIFICATE OF MERIT NO. 2254.

# OSCILLATOR-COUPLER

The "Unicouple:" (CU-71 shown) submitted by the Coupler Manufacturing Company, Cleveland, Ohio, is an inductance coil which may be used very conveniently as an oscillatorplate and the grid circuits are wound on a cardboard form 2 inches in diturns of the coupling coil are wound on a bakelite tube, 234 inches in diameter, and 14 inch wide. The housprovided with mounting feet



eter and 1 inch wide. tion with a .00035-mf, condenser, this unit when used in a radio-fre-quency generator covers a band which overlaps the broadcasting

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2255,

### PHONOGRAPH PICK-UP The phonograph pick-up device shown, submitted by the United Air

Cleaner Compan Avenue, Cleaner Company, 9705 Cottage Grove Avenue, Chicago, Illinois, makes it possible to reproduce speech and music from an ordinary phone graph record when used in connection magnetic pick-up unit, attached to a



of a permanent horseshoe magnet, with windings on its two pole pieces, and an armature carrying the phono graph needle. This armature almost closes the magnetic circuit of the unit closes the magnetic circuit of the unit and is held in position by several small pieces of soft rubber. A tel-phone cord, 3 feet long, serves to connect the coils to the amplifer. The volume output is controlled by a Carter potentiometer, approximately 25,000 clams. The support and the swinging arm are made of cause bronze with an attractive Japanese

finish. This unit is sensitive and ery satisfactory in its operation, and easing in appearance. LABORATORIES CERTIFICATE OF MERIT NO. 2256.

### LOUD SPEAKER

The losed speaker shown, submitted by the Aristocrat Corporation of America, New York, N. Y., is an attractive combination of a table lamp and a cone speaker. The base of this hamp is of thack onyx Pulper pottery. The gold-plated two-bulb lighting fixture carries on its top the aluminum base of the speaker unit, which is of



the floating-armature type. The unit's road (driving rod) is centered in a vertical position above the lamp base, and carries a crackle-finish parchment cone which covers the two bulbs, and serves at the same time as a lamp shade. An aluminum casing, consisting of two symmetrical halves, encloses the speaker unit and guides, through a felt washer, the which movement of the reed, which is heavier and more rigid than in most heavier and unit designs. A constant and unit designs. A constant and balance of the lamp shade-disphragm balance of the lamp shade-disphragm the secured. The tone qualities and and its

#### RESISTOR

The resistor shown, submitted by the Eureka T. & M. Company, 42 Walnut Street, Newark, N. J., is carbon as a base. It is shaped in the

# form of a small cylinder, 1% inches long and approximately 5/16-inch

prass cap on each end. This resistor is available in different resistance values, and has a relatively high current-carrying capacity. It may, therefore, be used very conveniently in "B" power units to apoul at cossary voltages, AWARDED THE RADIO NEWS

### "A-and-B" SUPPLY TRANSFORMER

The transformer (No. 463-101 shown) submitted by the Jefferson shown) submitted by the Jefferson Electric Mfg. Company, 501-11 S. Green St., Chicago, Ill., operates on 110-volt, 60-cycle bouse-lighting cur-rent, and is designed to supply (in connection with a full-wave rectifier tube of the 280 type) the entire



a modern electric radio receiver using A.C. tubes of the 226 and 227 types, power tubes in the last stage of the 171 or 112 type. This trans former has five secondary windings; the first three supply 6 amperes at the first three supply 6 amperes at 1½ volts, 2 amperes at 2½ volts, and 1 ampere at 5 volts, for the power tobes. The other two supply 2 amperes at 5 volts for the filament of the rectifier and 125 milliampere at \$20 volts for its plates. All but the first winding are center-tapped mounted on a special bakelite panel attached to the transformer. A cord 6½ feet long, with a plug to fit a standard receptacle of the house-lighting line, is connected to the pri-mary. This transformer is of compact and rugged construction and is sealed in a heavy-japanned-iron shell equipsed with mounting foet. The external dimensions of this instrument are 5 x 5 x 4 inches. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE

power necessary for the operation of

### FILAMENT TRANSFORMER

The filament transformer (type 464-131 shown) submitted by the same company, is a step-down device which operates from the 110-rolt, 60-cycle house line. It has three secondary windings, which supply current at 1½, 2½ and 5 votats; and thus can be used in electrified radio



rent for the filaments of 226- and 227-type A.C. tubes and a 171- or 227-type A.C. tubes and a 171- or 112-type power tube. The 2½- and 5-volt windings are center-tapped; two sheet-iron shells protect the windings from injury. A cord 6½ feet long, with a standard plug, is permanently attacked to the primary and allows direct connection to the LABORATORIES CERTIFICATE OF MERIT NO. 2260.

### ALUMINUM SHIELD

The aluminum box shield shown, submitted by the Aluminum Com-pany of America, 2400 Oliver Build-ing, Pittsburgh, Pa., is designed to



shield the different radio-frequency stages of a radio receiver, thus pre-venting undesirable feed-back and in-terference. Each box is approxi-mately 9 x 5 x 6 inches, and is formed of six aluminum plates 3/32-inch thick, and 4 slotted corner brackets, all held together by means of 8 screws. The shielding properties of this box are very effici AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 2261.

(Continued on bear 1097)





### DEEP, DARK COISES!!



### HERE'S A MYSTERY

### IT'S SO SIMPLE

### A CLASSY SET?

### HARE TO THE PICCOLO PLAYER



### FAST AND FURIOUS

### WOTTA SPEAKER!



### YOU CAN KEEP THEM

# HOW'S IT DONE?

### Contributed by B. Thomas

## CHEESE IT, FELLERS, DE BULLS!

### HABERDASHERS, PLEASE NOTE



### HIGH, WIDE AND HANDSOME

### PAGE GRANDMA



### NEW VACUUM TUBE

### YOU CAN HAVE THIS ONE



### THEY MIGHT BE BOOTLEGGERS





### Conducted by C. W. Palmer

THIS Department is conducted for the benefit of our Radio Experimenters. We shall be glad to answer here questions for the benefit of all, but we can publish only such matter as is of sufficient interest to all.

1. This Department cannot assure more than three questions for each correspondent. Please make these questions brief; if the inquiry is concerning

a circuit other than a standard, published one, delay will be prevented by enclosing a diagram and other necessary information.

2. Only one side of the sheet should be written upon; all matter should be typewritten or else written in ink. No attention paid to penciled matter.

Nectors, diagrams, etc., must be on separate becies. This Department does not nanwer questions by mail free of charge.
 One Editors will be glad to answer any letter, at the rate of 25c, for each question. It, however, questions entail considerable research work, instructs calculations, pattern ferestry, etc., a special charge will be made. Before we answer such questions, correspondent will be informed as to the price charge.

### INCREASING SELECTIVITY (Q. 2268.) Mr. H. Johnson, Long Island City,

(Q. 2268.) Mr. II, Johnson, Long Island Gity, N. Y. writes: "I have a Browning-Drake receiver which is giving me very good results, although the tuning is not as sharp as I would like to have it. I am and because of this I do not want to reduce the size of my aerial to sharpen the tuning. Is there any other method by which I can make my set tune



FIG. Q. 2268

The coil form for use in the antenna unit should be made as shown. A fiber disk should be used, and the wire wound in the slots cut as shown.

sharper without reducing the signal strength and signals from the greater distances than a small signals from the greater distances than a small signals from the greater distances than a small size of the signal size of the size

this is meant that the primary coil is equalize of the income being tunned to the exact frequency of the incoming signal, by means of either a workship conting signal, by means of either a workship conting signal, by means of the conting the conting of the cont

uuned primary produces greater astectivity with some secrifice in volume; leasuse the primary cell, baveing a low inductance value and not being varicoming signal, but depends for its operation upon "shocking" the grid coil at the frequency to which this coil it tuned. The greater the number of this coil it tuned. The greater the number of increase in volume; Blewise, as the number of turns is reduced, selectivity will be more pro-

mounced with a decrease in signal strength. In a particular case, when the antenna coupling coil was cut down from ten turns to one, and this one turn them Saded with a specially-designed the two coupling methods referred to above) the two coupling methods referred to above) the selectivity was as great as if one turn above was used, while the volume was practically the same as used, while the volume was practically the same as the selectivity was about 178 feet long.

#### Construction of the Antenna Coil

From this it will be found that it is possible to use the long, high aerial system, with its resulting high efficiency for intercepting signal energy, yet without sacrificing that degree of selectivity which is generally obtained only by the use of a small antenna-provided that the correct apparatus is

used.

fore thing to do is to built the variable being multi, the schematic details of which being multi, the schematic details of which are above in Fig. 2266A. It consists essentially of a tapped spelerweb cell and a variable of elenser. Great care must be observed when constructing this unit, since a considerable resistance would effectually block the passage of weak signals, used to be a subject to the processor of the subject of the subject to the

The variable air condenser employed should preferably be of the straight-line-frequency type, and the requirements of the circuit are such that this

condenser should have a maximum capacity of ,001 mf. The inductor is of the well-known spiderweb type, since such a coil offers a very low resistance to higher-squeezy currents and is very casy to construct. It consists of 50 turns of No. 22 D.C.C. wire, would through every other slot of ginning. The form used should be made according to the specifications given in Fig. 226.8. No shelline, varnish or other material is used on this coil. After the coil lass been completed, it may be


other muxus.

It is important that this coil shall be placed at right angles to the electrostatic field of the condenser, and also that it shall be out of industries relation to the first coil of the receiver itself. If any coupling should exist between the loading unit any coupling should exist between the loading unit of the control of the contr

The next point is to erect as large an aerial as circumstances permit, bearing in mind that, the higher and freer the aerial is kept, the greater will be the sireal strength.
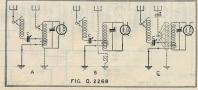
#### Changing Receiver Connections

Assuming that your receiver employs the same direct attents coupling as the commercial Brown-ing-Drake receiver, it will be necessary to remove the two interior lead wirse which connect to the antenna and ground posts. In their place is at tached a spice of copper wire, no smaller than No. 14 and hang enough to reach from the aerial ground post. In order that this wire may not cut into the finer wire of the grid coal, it should be covered with a good grande of spaghetit. The



Methods of connecting the unit to the three most common types of antenna couplers. The first is used in sets with conductively-coupled inputs, the second for semi-aperiodic antennas, and the third for ordinary tuned antenna couplers.

method of connecting this wire is shown in Fig. 2268A: this constitutes the coupling coil through which the received energy is transferred from the loading unit to the receiver. The output terminals of the loading unit are then connected between the sead-in and the aerial post on the receiver.

If your set employs a semi-aperiodic coupler, as in many modern receivers, the changes to be made are very similar. The small coil which is connected between the antenna and ground posts is removed, and in its place is put the single turn of heavy wire. (Fig. Q 2268B.)

In a set which the antenna circuit is tuned (such as a variocoupler set, where the outside winding is connected between the antenna and ground and the rotor used as the main tuning inductance) the primary will have to be unwound and removed. It is not, of course, necessary to dismantle the coupler, but it would not be wise to leave the unuse primary coil in such close relation to the grid coil The single turn of heavy copper wire is wrapped around the secondary and connected to the antenna and ground posts as before. (Fig. Q 2268C). The operation of the unit is very simple,

wave lengths below 350 meters, the switch lever is set on the first point; so that 35 turns of the leading inductance are included in the antenna cir The dials of the receiver are then adjusted to the setting at which a station is known to come in, after which the antenna condenser C is varied until signals are heard. The first dial of the receiver will not read exactly the same as before, because of the changed inductance of the circuit.

### SHORT-WAVE ADAPTER

(Q. 2269.) Mr. R. B. Hughes, San Diego, Calif, writes would like to construct a short-wave un

imilar to the Aero short-wave converter, and use the audio-frequency amplifier in my receiver in kindly publish a diagram and constructional der for building this unit?"

(A.) To convert the receiver, it is necessary sly to disconnect the aerial and ground wires from the receiving set and attach them to the two binding posts of the short-wave converter. detector tube from the receiver and place it in the tube socket of the converter. The cable plug from the converter is inserted in the detector socket of the receiving set. No other tubes are removed nor are the battery wires disturbed, and the loud speaker operates as usual. The tuning is done entirely by the one dial on the converter, The tuning controls on the receiving set are not used,

This converter unit is easy to build and simple to operate. No trick circuit is used and no tricky

The converter is really a short-wave set, co sisting of a regenerative detector with a simple attachment-plug for connection to the audio end of the present receiving set and battery current supply to light the detector tube, now transferred to the converter. This method of connecting the supply to light the detector thos, now transferred to the converter. This method of connecting the two units together consists of a five-conductor cable (two leads of which are not used) and an old yacuum tubals of his served its usefulness otherwise, for the plug. The glass of the naue, broken off and the base cleaned out. Three wires from the cable are soldered into the terminals of the cable one to the "A-," one to the "A-," which the cable one to the "A-," and the cable of the these terminals, hold the tube right side up with the pen towards you; the rear two posts are "A+." and "A--" respectively, and the left front post is the plate terminal). The base of the tube is now filled with some compound, such as that from the top of a discarded "B" battery,

Regeneration is controlled by a 0 to 500,000-ohm resistor, connected across the tickler. A ,00025-mf, variable condenser is used, with a set of three Aero coils, to tune from 15 to 200 meters. A vernier dial is mecessary, as the tuning is sharp. The schematic diagram will be found in Fig. Q



The choke coil is important and must not be nitted. When by-passed with a .002-mf. condenser it will permit the plate lead to enough to reach the receiving set. If a choke coil cannot be easily secured, one can be made by winding 100 turns of No. 26 D.C.C. wire at random on a wooden spool, 1/2-inch in diameter and with a 1/2-inch core

To operate the short-wave converter, select the plug-in-coil covering the wavehand in which you want to receive and plug it into the coil jacks, connect the plug to the rectiving set as previously described, and transfer the aerial and ground leads You may listen either with headphones on the intermediate jack, if your present set is so ar ranged, or use the load speaker as ordinarily con nected. Turn the resistor until the receiver oscil-lates. Tune in a station and clear up the signal by a further adjustment of the resistor or rheostat

#### THE SYNCHROPHASE SEVEN

(O. 2270.) Mr. C. Williams, Salt Lake City, "I would like to obtain copy of the schemati diagram of the Synchrophase Seven receiver. If possible, I would like to have you publish this dia-

(A.) You will find the diagram in Fig. 2270 The designers of this circuit desired a receiver in which the fan need not fear altering the neutralization if tukes were changed in the set. quency-response curve of the average tuned-radio-frequency amplifier shows maximum response on some short wavelength with falling characteristics as the wavelength is increased. To overcome this difficulty, the variable condenser and two re-sistors were placed in the grid circuit of each radiofrequency amplifier tube.

The action of these units is twofold; first, they eliminate the effect of the tube's grid-filament capacity upon the tuned circuit, particularly on the low settings of the tuning condenser, in such a manner that the tubes could be changed without effecting the original resonance setting. Secondly, they control the voltage being fed into the gridfilament circuit of the amplifying tube, so that the radio-frequency input is practically uniform over the complete tuning scale. With this arrangement, and the inherent lack of regeneration in this sys-tem, a high degree of stability of amplification is

The four stages provide ample selectivity and sensitivity and are designed to possess sidehand characteristics with minimized suppression for 1,000 cycles. The detector functions by the grid-leak method, affording maximum sensitivity and selec-tivity. The same compensating system utilized in the radio-frequency stages is resorted to in the detector input circuit, thus permitting the use of any detector tube without unbalancing the tuning system. A non-regenerative detector is used, be-cause the four stages of tuned-radio-frequency amplification give sufficient

The capacities used in the "tone color," to regulate the characteristics of reproduced voice and music, vary from .00008 mf. down.


#### SHIELDING RADIO SETS (O. 2271.) Mr. J. W. Fenworth, Bangor, Me.,

"What is the best metal for use in shielding

(A.) Copper, aluminum and brass are the metals best suited for use as shields. A shield must be of good conducting material so that eddy currents may be formed within its mass. Lead foil and tinfoil have resistances too high to make good shields. Iron

and steel must never be used for shielding high resistance and, furthermore, they introduce mag-netic effects of their own which make matters worse than tefore. Any thickness of metal from No. 6 down to No. 30 gauge may be used satisfactorily

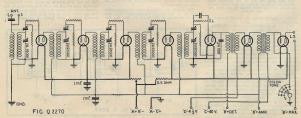The best results will be secured if shields enclosing various radio-frequency stages are insulated circuits in the receiver. On the other hand, the best protection against pickup of outside interference will be obtained with grounded shields If the receiver is equipped with both interstage complete-cabinet shielding, the interstage shielding thus affording almost complete protects



# HOLESALE PRICES

for Dealers, Community Set Builders, General Repairmen and Agents!

CATALOG

Be sure to get this great 128-page book with net prices to the radio trade. Radio Specialty Company is radio's

Radio Specialty Company is radio; a coldest radio parts mail order house in the country, and the new confidential prices to the country, and the new confidence are the lowest of any radio house.

We are ready now to appoint additional agents in all parts of the country. If you are contemplating making big money in radio, merchandise, be sure to get in touch with us at once.

WHEN WRITING TO US, USE YOUR LETTERHEAD

ENLARGED EDITION

RASCO H 14 from Radio's Oldest Mail Order House!

"PASCO"has if

ANYTHING IN RADIO

500 ILLUSTRATIONS



# Wisdom For Radio Widows (Continued from page 1003)

45 Stations Broadcast Bridge Lessons Every Week

Follow Every Play With Ease

Anyoneofthesebridge books will help!

By Wilbur C. Whitehead:
Complete Auction Bridge \$2.00
Auction Bridge Standards 1.50
Auction Bridge Summary 1.00

By Milton C. Work
Bridge Pointers and Tests
Contract Bridge
Contract Bridge
December
19.
Foster's Contract Bridge
100 Bridge Lessons
100 Bridge Lessons
Practical Auction Bridge
2.0
Shertcut to Standard Auction Bridge
Auction Bridge (Annual Magazine). 7.

Prepared by Famous Broadcasters

"Listeners in" need no introduction to Work and Whitehead. They are the most famous of Bridge Broadcasters, and masters of the game.

This is a selection of their best

Many of the plays that did not clear up in your mind over the radio can now be studied at leisure.

Whatever is to be known about Bridge will be found in these books. These are books to fit every need and every purse.

Pick your books now-and be assured that your knowledge will be coming from masters

Each book is well bound, printed in legible type, and contains anywhere from 160 to 500 pages.

Order Direct

CONSRAD CO., INC. 230 Fifth Avenue, New York City exceedance decently before, he evented this ing. You probably liked it at first, thought it was a brilliant addressment, and then, exceeding the legitimate percentage of womakind, you accepted it enthely and conclusively as one energy fat telephone or woman, it is obvious why you give unique woman, it is obvious why you give unique man because John shways had the darmed thing torn to pieces. But, layd—just as if that's not what it was for! I suppose it's an evidence of feninties logic to assume that or the contract of the contract of the conclusion of the contract of the conclusion of the contract of the conclusion of the contract of the contra

Mrs. Jones, did you not know that a gemike flame burns also in your husband's breast, and burns there still—in his, who couldn't properly open a can of tomatoes before?

Ah, the exhaltation that surges through his veins when he turns a switch and hears nusic where there was only ether before! Had you understood this? Had you not seen the wild gleam in his eyes?

THE JOY OF CREATION

He did it, you understand, with his own hands, his own two hands, his very own two hands. Did you not comprehend the subtle significance of that? Thousands had labored before him, for hundreds of years, to perfect and simplify and coordinate physical theories and facts which he himself had never thought of or heard of before. Then, like a visitation from Olympus, the entire mystic scheme of things burst upon his consciousness like the dawn upon a burnished sea. And, lo! he suddenly knew as much about radio as these aged masters who toiled of old. Is that not indeed an endowment? Is that not indeed the gift of magic powers unseen? Did Balboa, or Moses, or Joan of Arc have anything on your husband now?

Ah, Mrs. Jones, fret not when John tears out the raido-frequency gadge to put in a new set of space-wound thingamagigs. Griere not thy out when he disamattes the andio-stage wampus to put in a new pair of giant-transformer dinguess which amplify equally at all frequencies. Tear not the hair when he rips out to her raido and whoosis in between them to make a superheterodyne out of it.

Try hard to understand that what be is obligg. Mrs. Jones, is not meant to aggravate you, but rather to appease these little electric good of his, by amplifying signals at a much higher wavelength than that recrede by the radio-frequency dingletal. It Jones, relices static, and extend DX. (Ah, marred of sound! Breath it softly), Your must not cavil when John uses the bread to to shirtly his colois and condensers; for it reviews laterslage coupling, whatever when the property of the memics.

You must not object when he builds a ten-foot horn out-of papier mache, for it is a horn with principle—a horn with an exponential principle, which is to say it is a horn whose cross-sectional area doubles at equal-intervals along its air-column length. And this, Mrs. Jones, makes for more natural sound, approaching closer and closer to the fundamental wave, where purity alone is to be found. Is this not of the essence of clarity? Well, never mind. Try the next paragraph.

A MAN AND HIS HOBBY

When John explains these things to you, try, oh, struggle very hard indeed to look as if you understood, though indeed you do not understand—as you undoubtedly will not, because, as you are a woman, you don't want to. But you will try to look as though you understand; because if you do not, you will arouse a tiger in your husband's breast. And lady, it will be a deep throaty roar!

Two things will take place if you scorn your husband's admonitions regarding radio: (1) Your husband will say, or at least will think, nasty things about our mental powers. He will probably allege they couldn't be measured in anything larger than a coulomb or an erg; and (2) he will sense your disaffection and will anticipate your calling him away from his tinkering to mash the potatoes or give Junior his bath. This reflection will have the same effect on him as it would on a tiger whose nice, juicy chunk of meat is suddenly and malignantly snatched away. These effects, combined, arise from his intense application to the mystery of ohms, feed-back currents, plates, grids, filaments, inductors, variometers, potentiometers, volts, amperes, milliamperes, kilocycles, grid leaks and condensers. Don't ask me what they are. I only know they are the marrow of his bones, the symbols in his sacred shrine, the little gods in his miracle world to which he does obeisance. To disturb them will start him oscillating in a most fearful manner. And it is not because he doesn't love you,

#### WEEP NO MORE, MY LADY

When you go to bed alone at night, forbear, oh, forbear Mrs. Jones, to finist than he, too, retire, no matter how cold your poor feet may be. For it is at night that DX is abroad in the land. It is then that he communes with the infinite; it is then that he cruises the air, questing to the ends of the earth for some faint sign, for some faraway signal, no matter how weak, that he is getting DX (Breathe it sortly!)

It is his Holy Grall, it is the ultimate recompense for his devoted obtain. To hear stations no one else ever heard beføre is not enough. To hear stations better than anyone else ever heard them before is not enough, although it has its compensations. Dut to hear stations farther away than —that is the consumnate pad, the final reward. And that is called DX, Mrs. Jones (Brestite it softly)

Even if he wakes you up at 3 a. m. with the news that he has Australia, resist the

# What These Have Done YOU CAN DO!

"Since I have been studying with your school I have been appointed chemist for the Scranton Coal Co., testing all the coal and ash by proximate analysis."

"I also have some news for you. I have been made assistant chemist for the concern I am working for."

—A. G. Delwarte.

"I am now cleaner and dyer for the above named company. My salary is almost double what it was when I started the course."

"Your training has opened things to me that other-wise I would probably be years in acquiring. I now enjoy comforts that before I had to do without. It enabled me to have a sconderful little home, a fine laboratory of my own, and gave me a respected position in one of the foremost textile concerns in the country." -J. J. Kelly.

"If it weren't for your course I wouldn't have the tob I've got nost. -George Daynes.

"Since beginning your course of study I have received an increase in my pay cheek, and as I progress my work becomes lighter through a better understanding."

"I am mighty glad I took this course. My salary has been increased several times, and different in-dustrial plants are coming to me for a little addice on different things, netting me a fair side income." —M. E. Van Sickle.

FORTUNES HAVE BEEN MADE

THROUGH CHEMISTRY

THROUGH CHEMISTRY
Altro Nobel, the Swedich chemist who invented dynamite, made so many millions that the income abone from the made so many millions that the income abone from the second of the seco

NOW IS THE TIME TO STUDY

CHEMISTRY Never before has the world scene to a released oppor-mation for the scene of the scene of the scene of the habitation of the scene of the scene of the scene of the laboratories, electrical shops, industrial plants of all kinds, chemistry plays a vital part in the continuous and expansion of the business. In every branch of human scelavor the need for chemists has arisen. Those who will have the adole advantages and greater opportunities afforded while the chemical field is growing and expanding.

#### EASY MONTHLY PAYMENTS You do not have to have even the small

You do not have to have even the small price of the course to start. You can pay for it in small monthly amounts or earn it as many others are doing. The cost is very low, and includes even the Chemistry outfit—there are no extras to buy with our course. Write us and let us explain how you can qualify for a trained tech-nical position without even giving up your present employment.

#### COMPLETE LABORATORY EQUIPMENT

We give to every student, without additional charge, his chemical equipment, including fifty-two pieces of laboratory apparatus and supplies, and fifty-two different chemicals and re-agents. The fitted heavy wooden box serves not only as a case for the outif, but also as a laboratory accessory for performing countless experi-ments. Full particulars about this special feature of our course are contained in our free book, "Opportunities for Chemists."

NAME: ADDRESS.

Don't Wait-Mail the Coupon NOW!

### CHEMICAL INSTITUTE of NEW YORK, Inc.

16-18-R-EAST 30th ST. Home Extension Division 3 NEW YORK, N. Y.

IF you are dissatisfied with your present work, if you wish to earn more money, if you want to get into a profession where the demand for trained men is increasing as the Chemist plays a more and more important role in the industrial life of this country, let us teach you Chemistry.

# You, Too, Can Learn AT HOME

To qualify for this remarkable calling requires elaborate specialized training. [Formerly it was necessary to attend a university for several years to acquire that training, but thanks to our highly perfected and thorough system of instruction, you can now stay at home, keep your position, and let us educate you in Chemistry during your spare time. Even with only common schooling you can take our course and equip yourself for immediate practical work in a chemical laboratory. Dr. Sloane gives every one of his students the same careful, personal supervision that made him celebrated throughout his long career as a college professor. Your instruction from the very beginning is made interesting and practical, and we supply you with apparatus and chemicals for performing the fascinating analyses and experimental work that plays such a large part in our method of teaching, and you are awarded the Institute's official diploma after you have satisfactorily completed the course.

### TUITION PRICE REDUCED

Besides furnishing the student with his Experimental Equipment, we have been able, through the big increase in our student body, to reduce the price of the course. Write today for full information and free book, "Opportunities for Chemists" course. Write toda and free book, Chemists."

#### MAIL THE COUPON FOR FREE BOOK

Clip the coupon below and mail it at once. Your name and address on the coupon will bring you by return mail our interesting free book "OPPORTUNITIES FOR CHEMISTS" and ful particulars about the course and what it



# Greatest of All Great Superheterodynes shown in the New Improved CONSRAD PATTERN

SIMPLE - PRECISE

WHEN you build, build the best and with the best—the Consrad Book Pattern-it will cost no more! When Consrad publishes a pattern of a circuit, it must rank high in the Radio World.

And, of this Strobodyne, none ranks higher-it is the greatest of superheterodynes.

Consrad knows what it is to build sets -knows the sad experience of mistakes caused by confused instructions.

So when this pattern of the great Strobodyne comes to you, it is in the most simple, precise terms possible— easily understood, with all possible chance of doing the wrong thing eliminated.

4 Full-size Blueprints 1 9x12 book

Self-explanatory illustrations Step-by-step Instruction

It is a glorious feeling of accomplishment when the set shines in its finished splendor before you.

### 50c the Pattern

Start Now-Use Coupon Immediate Delivery

230 Fifth Ave., New York, N. Y.

Gentlemen: I enclose 50c. for one copy of the New Official STROBODYNE PATTERN ontaining complete constructional information of all illustrator.

impulse to say: "Well, what of it?" Oh, be not so murderous, so cruel. Bear with him, rather, in this hour of gladness, this moment of divine rhapsody. Try hard, try hard to make the eyes shine and the face illuminate. It will be balm to his poetic soul (otherwise so dull, so dead). For DX is his faith, his hope and his dear desire-his religion. It may burn out after a while, and again it may flame higher. But despair not. It might be worse. He is happy now. You could put crackers in his bed and he wouldn't mind. But treat his DX disdainfully and he will go mad; he will go mad if

you do not grant him his hour of glory. Poison will gnaw within him if you do not understand that, in his soul of souls, he bears you no malice but is simply a radiofan, exultant in his victory over the mundane earth, a giant of power in his own demesne, wrathful as a tiger when disturbed or taunted, but gentle as a lamb and sweet as a June day when he is getting his (say it softly!)-his DX!

Ah, to have understanding, Mrs. Jones, or at least to seem to understand-ah, this is the ultimate charity!

### The United States-A Broadcast Studio

(Continued from page 1004)

carry the program from the New York switchboard, through which the different performers' voices were all routed before they were put on the air from the broadcast stations. This meant thousands of miles of lines from New York to the fortyseven broadcast stations scattered over the country. In short, three transcontinental telephone circuits were required for the broadcast-one to serve the broadcast stations, one to transmit the program of the performers to New York and a third for emergency. It is stated that the cost of putting on


this hour of broadcasting was over \$1,000 per minute; of the total, about \$25,000 went to the artists appearing before the micro phone, \$35,000 to the telephone company and about \$7,000 to the broadcasting company

for the time the stations were on the air. This broadcast, which is one of the most ambitious ever attempted, is said to have been received by one of the largest audiences that ever tuned in on a program. There seems to be no need for broadcasters to fear that sponsors think radio advertising does not pay, when a single company is willing to invest any such amount as was spent for this program. In short, this hour of broadcasting is remarkable from three standpoints, the celebrity of the artists participating, the cost, and the remarkable engineering work that was necessary.
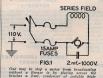
### How To Kill Vagrant Radio Noises

(Continued from page 989)


nected to ground, make this connection. The last of the interference may be killed by connecting a 2-mf. condenser (tested to stand 1,000 volts D.C.) across the brushes. Place the condenser as near as possible to the place where the sparking occurs. See Fig. I.



If the line is over 110 volts and ungrounded the design of the filter should be changed. Two condensers of the same size mentioned above are connected in series, with their common point grounded. This system is then shunted across the commutator, as will be seen in Fig. 2. For very small motors, such as are used in hair driers, vacuum cleaners, soda-mixers, etc., a hightest condenser of 1/4-mf, will do the trick,

In the case of a refrigerator control, furnace control, heating pad, or like device, giving trouble, more than likely sparking is taking place at the thermostat contacts Hook a 1/4-mf. condenser across the input. The result should be silence.

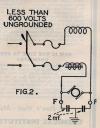Then we have the case of bad contacts Of course the best remedy that we can advise is to fix the contact. But then we just know that someone is going to yelp, "Sup-pose you can't fix it. What then?" If you find for instance, that the delicatessen man



the choke coil consists of 100 turns of No. 18.).C.C. wire wound in a single layer on a 3-ech tube form, H-inch thick and 8 inches long, it is verapped with insulating tape after conding.

# CARBORUNDUM

RID LEAKS

RESISTORS

NOISELESS RECEPTION

Just slip a Carborundum Grid Leak into your set and you won't be long in noticing the difference the improved reception.

For Carborundum Grid Leaks are quiet. They are solid rods of Carborundum that provide an uninterrupted flow of current. There is no noise from arcing. These resistors are dense and they can't disintegrate. Carborundum Grid Leaks are tested at the maximum operating grid voltage, namely 5 volts, and Resistors at 90 volts.

Buy From Your Dealer or Direct ~~ Write for Booklet D-1, "Carborundum in Radio"

THE CARBORUNDUM COMPANY, NIAGARA FALLS, N. Y.

\*\*Link Town Company (Nicolar Mallack) (Nicolar Mallack)

# It's Here~with the latest

The Greatest Call Book of the air

RADIO LISTENERS' GUIDE AND CALL BOOK—50e. Why the circuits, the listed stations, are worth ten times more! For money's worth, remember the name—RADIO LISTENERS' GUIDE AND CALL BOOK! Most complete, convenient, helpful!

Circuits—the very latest—dozens of them—written and prepared for use by experts—all ready to build.

erts—all ready to build. RADIO LISTENERS' GUIDE AND CALL BOOK—50c.

AT ALL NEWSSTANDS OR DIRECT

CONSRAD COMPANY, Inc., 230 FIFTH AVENUE, N. Y. C.

Stations—a wonder index of radio stations of the world, completely listed by call names and cities, with wave lengths and other important data—and special space for dial markings. News—the interesting, illustrated intimacies of the studios which you will thoroughly enjoy.

### New Aero Circuits for Either Battery or A. C. Operation

Proper constants for A. C. operation of the Im-proved Aero-Dyne 6 and the Aero Seven have been udied out, and those excellent circuits are now appathle to either A. C. or lastery operation. A. C. are prints are packed in foundation units. They ay also be obtained by sending 2s for each direct



Tuned Radio Frequency Kit Especially designed for the Improved Aero-Dyne 6. it consists of 4 twice-matched units. Adaptable to 1-A, 190, 112, and the new 240 and A. C. Tubes. .....\$15.00



Aero Seven Tuned Radio Frequency Kit tuneu Radio Frequency Kit Especially designed for the Arto 7. Kit consists 3 twice-matched units. Colis are wound on Bake-ic Tuning range from below 200 to above 300 eters. Adaptable to 201-A, 199, 112, and the new o and A. C. Tubes.

You should be able to get any of the above
Aero Coils and parts from your dealer.
If he should be out of stock order
direct from the factory.

AERO PRODUCTS, INC. Chicago, Ill. over the way is using his sign to put your radio reception on the blink, tell him about it and we will bet another nickel that be will gladly let you hook a 1-mf. condenser across the terminals. Business is business.



A compound filter that silences bell-ringers, so Now suppose that you are located far

away from sign-flashers, street cars and the other poise-makers of the city and that. when you want to get your telephone operator to put through a call to Mary's house, you have to turn a funny crank on the side of the box. That, being attached to a magneto, can do plenty in the way of noise making. In order to have radio reception such as you read about, make a filter of two condensers grounded at their common point and put them in series with two choke coils, one in each side of the line. Consult Fig. 3

As we have said, somewhere in the first portion of this advice, there are many sources of interference, which we have no room to treat of here. We respectfully suggest that, if you are bothered with some ill to which radio is heir, you should consult the "Manual on Interference" prepared by R. J. Casey for the Radio Manufacturers Association. We are indebted to this excellent booklet for some of the suggestions herein given.

### Repairing Simple Ailments of Radio Receivers (Continued from page 1015)

Where a storage "A" battery is employed, the leads to the terminals often become corroded, resulting in poor contact and in clicking or grinding noises in the loud speaker. In neutrodynes, "squealing" often occurs,

which usually means that the radio-frequency stages must be rebalanced. Ordinarily, an expert should do this work and the charges are nominal. Often, if the tubes in the set are changed around, all squealing can be eliminated. Other howls in some sets are caused by

turning the filament or volume controls up too high. One should adjust these until good volume is secured at the lowest possible setting. If the filaments are kept turned on

CONNECTION STRIP

B- B-DEL BAINE B-PWR C+ C

TO ALRIAL

A BATTERY



If reception is poor, see if the speaker connec-tion cord is intact, and if the plug makes good

One can often remedy simple ailments by gently jarring the set. Any wiring that has become loosened will usually thus be discovered.

One listener found that in the middle of a program the volume would often suddenly fall off. This remained unexplained for a long time until one night he chanced to move the lond speaker, and discovered that there was a break inside its flexible connecting cord. The phone jacks often become worn and make poor contact with the loud speaker-plug and crackling noises and variation in volume then result. The loudspeaker cord, being usually subjected to much bending, often develops breaks (see

One should be careful not to touch internal wiring when something goes wrong. but first to inspect thoroughly all outside connections. It is well to remember that 90% of all troubles are easily remedied by the set owner. Isn't it reasonable to say that only those parts which are external and subject to wear are the ones usually found out of order?-Clyde A. Randon.

FIG 1 One of the prime requisites for good reception is a tight connection between batteries and the receiver. Loose connections, whether at the batteries or at the terminal board, are easily too high over an extended period, the tubes employed will become "deactivated;" that is,

### NO USE! SOME CAN PUT THEIR FOOT IN IT

Did you see the item about the fellow who put a billiard ball in his mouth and couldn't get it out?

If you happen to know any radio announcers, ask them to try it.-Ted Cook, in Los Angeles Examiner.



Their high insulating values insure the utmost protection against leaks and losses which often cause poor reception.

Made with Crackle or plain Polished Surface in all regular sizes:

7 x 10, 7 x 12, 7 x 14 7 x 18, 7 x 21, 7 x 24 7 x 26. 7 x 30 inches. Low prices at all

dealers or write to AMERICAN HARD RUBBER CO. 11 MERCER STREET NEW YORK, N. Y.

Makers of famous RADION PANELS

the filaments will cease to function properly and lower volume in the set as a whole will result. One can often remedy this difficulty by changing the tubes around; if the results are no different, the tubes should be tested. One should remember, in changing tubes, that the tube marked "last audio stage" should remain in place, as it performs in this position better than the other can.

#### What Constitutes Tone Quality?

(Continued from page 991)

Now move one of the bridges until the length of the vibrating part of the wire is exactly one-half as long as before. The tone produced will be observed to be an octave higher than the first tone; the frequency of vibration will be exactly twice as great.

Now, having memorized the last tone, move the bridge back to the first position, and pluck the wire at one-quarter of its length. On touching the wire lightly at its mid-point with a feather or the folded edge of a piece of cloth, it will be noted that the fundamental tone is "damped out" or very much weakened, but that the octave tone C is still sounding. Evidently the wire was vibrating in such a way as to produce both the fundamental and the octave tone, somewhat as shown in Fig. 5 at c. Similarly plucking the wire at one-sixth of its length and damping it at one-third of its length gives a still higher note G'. Plucking at one-eighth of its length and damping at onefourth gives a fourth tone C", two octaves above the fundamental. The process may be continued more or less indefinitely, showing that the true condition of the vibration of the wire at any time is very complex; it vibrates simultaneously for its full length, one-half, one-third, one-fourth, etc., with frequencies twice, three times, four times, etc., the fundamental. The complex vibration form gives rise to a whole series of tones above the fundamental, called "overtones" or "partials." The first nine overtones of each of the notes of the major scale (physical pitch) are given in the table, to which reference will be made in Part II of this article, which will appear in the next issue of Radio News.

#### EFFECT OF OVERTONES

It will be also noted that, as the number of overtones is increased (i.e., as the wire is plucked nearer and nearer to the end), the complex tone becomes more and more strident and metallic in character, and at the same time less pleasing to the car. From this fact it becomes apparent that the pleasing character of any tone depends largely upon the quick damping out of certain of the upper overtones. A musician would explain that the sound produced by these overtones (note especially the sixth and eighth in the table) is discordant with the lower tones. If the string is plucked at "nodal points" (those where the wire vibrates least) for the disagreeable discordant harmonics, they are not produced. Since the sixth and eighth harmonics are totally discordant, musicians seek to eliminate them; which accounts for the bowing of a violin string at one-seventh or one-ninth of its length, and the placing of the hammers of a piano so that they strike the wires at nodal points for these two partials.

The study of the manner of vibration of plates and membranes, while it is involved in some difficulty, may also be undertaken by the amateur experimenter. The classical experiments of Chladni, discussion of which will be found in any standard work on acoustics, may be easily repeated. His apparatus consisted of a square plate of glass or metal, supported by a clamp or a bolt through the center, as in Fig. 6. Sounds

# DISTANCE lends ENCHANTMENT

When you buy or build a radio set make sure that it has Copper Shielding. Where long distance reception is desired Copper Shielding is essential. It is a refinement to your set that will enable you to hear the programs of distant stations much more clearly.

Copper Shielded sets give:

improvement to any set.

BETTER RECEPTION FINER SELECTIVITY IMPROVED TONE QUALITY

By virtue of its easy working qualities and its high conductivity Copper Shielding is a decided

# COPPER & BRASS

25 Broadway, New York

Write for your copy of this



There is no cost nor obligation









Experimenter Publishing Co., 230 Fifth Avenue, N. Y. C.

# DEALERS the country over have heard have seen and now acclaim



#### The Modern Business Builder

Radio News DEALERS PERSONAL EDITION—a magazine devoted to the Radio Trade—a personal edition. Supplying to the industry a service that otherwise would be next to imnossible to obtain.

Market Research—Surer Profits Buying Trends—Quicker Turnovers Outlets of Waste—How to Stop Them All the Finer Points of Conducting a Progressive Radio Business

In short, this DEALERS PER-SONAL EDITION is an intimate magazine only meant for dealers containing the current, vital talk of direct bearing and much interest to every dealer.

If you are one of the few who has not become acquainted with the DEALERS PERSONAL EDITION, you must do so at once.

This magazine is doing for the Radio Business what Radio did for many businesses—a complete revolution for the better—with the backing of Radio News.



are preduced by lowing the edge with a violia hour, the pitch of the sound being varied by the manner and place of bowing and by the pointions at which nodal points are produced, by touching the plate with the fingers while the plate is being bowed. Fine fingers while the plate is being bowed. Fine thrown off the portions which are vibrating, collecting over nodal lines. Some of the figures thus obtained are beautifully symmetrical. A few of Chiadmi's sketches are

If the plates he him crough and large crough in dimeric, it will be found that they can respond to an amount infinitely represent the control of the control

tone with a number of overtones.

As the experiments above are continued, and as other more exhaustive investigations are undertaken, it becomes increasingly cer-

tain that the quality of a sound depends upon the number and relative prominence

of the overtones. A clarinet sounding middle C, for example sounds the fundamental together with a certain set of overtones (see Fig. 3). Some of the overtones are strong, some less prominent, and others are so weak as to be scarcely perceptible to the most sensitive musical ear. The sum total of these overtones gives the clarinet its individual character by means of which we identify it. 'f any one of these overtones is removed or weakened, or if any additional tone is sounded to blend with the clarinet's tone, then its individuality is destroyed and we are no longer certain of identification. The reader will recall the sound of a "muted" clarinet for verification of the last statement. The "mute" changes the emphasis

the muted tone is really a new sound. Comparison of the two wave forms in Fig. 3 will show that the fundamental frequencies are the same, and that the intensities are the same. But the partial tones are very dissimilar. Each little kink and curve in each wave is essential, however, to the complex sound.

upon some of the partial tones, introduces

some new ones, and removes others; so that

# Encircling The World With a Two-Tube Set

(Continued from page 987)

Greenland: OGG, Godthaaven. Iceland: Reykjavik. Alasha: KGBU, Ketchikan;

daaba KORU, Kenkikası KODO, Andersoga Fewrey: LD, Chooles EAJI, Calin Spain: Ibl. Mana, Yady; 197, Piyosob, Raghedi Shan, Yady; 197, Piyosob, Raghedi Shan, Yady; 197, Piyosob, Raghedi Shan, Yadyi, Marki, Spain; Sill, Pirussh, İstigamı FPTT, Beris, France; LS, Marki, Sama, 197, Pirus, France; LA, All, Bartelan, Spain; LL, Pirus, France; LA, All, Marki, Sama EAJI, Orden, Spain; Sattgart, Germany; EAJ, Marki, Mary, Spain;

Spain; Bordeaux, France; EAJ25, Malaga, Spain.
Africa: Senegal, West Africa; WAMG, Caper
Town, South Africa; Radio Casa Blanca, Morocco

Asia KZUV, Raguis, Pallirgues Danies, DOK.

Asia KZUV, Raguis, Pallirgues Danies, DOK.

Onka, Japan; DOK, Krist, Japan; KZBO, Ma
Sania, Philippei Bankai, 184, Angeris, KZBO, Ma
Bong, China; TeA, Calonara, Judia; KZM, Ma
Bong, China; TeA, Calonara, Judia; KZM, Ma
Landraina; TeA, Calonara, Judia; KZM, Ma
Landraina; TiR, Sabere, Australia; CiC, Ado
Landraina; TiR, Sabere, Martini; TeC, Sabere,

Landraina; TiR, Sabere, Martini; TeC,

Tanania; MA, Madhoura, Amerila; TeC,

Landraina; China, Martini; TeC,

Landraina; China, Martini; Alexandraina;

derret, New Zamiel; 193, Adalaha, Amerilai,

derret, New Zamiel; 193, Adalaha, Amerilai,

month; in 1927. They and others in the

month in 1927. They and others in the antipodes came in best about 4.30 to 5 o'clock in the morning, when he had to get up to do the milking and other chorn stations were best from 4.30 to 7 P. M., and South American stations from 5 to 11 P. M.

#### THE BEST RADIO NIGHT

During the evening of March 13, 1927, Pierce startled his family by loud whoops of joy. It was one of those rare nights of joy. It was one of those rare nights following: KGR, Honodulu, KGBU, Alsaka, AGM, San Salvador, Central Amerles; CXAD, CAMT and CMAB in Chile, gentina, IzAJ22, Spain; SQLG, Bradit Ride d Janeiro, Bradi (no call letters announced); CWG. Uruguny OAX, Penal Mexico, and PWX, Havans.

Pacific coast stations in the United States came in almost as easily as those near home. Unidentified foreign stations came in on 345, 288 and 307 meters.

345, 288 and 307 meters.
Pierce's radio log, kept with painstaking care for two years, will convince anyone who examines it that it is an authentic record. Many of his records are verified by letters or cards from the stations heard. And there is other evidence almost a strong.

or perhaps stronger.



Pierce holding a receiver which was built by North Kingston High School Science Club

The character and reputation of the family are above question. They live on the homestead where their ancestors settled more than a century ago. The father is a farmer who supports the fine old traditions of a line of forebears with a record stretching back to the days of William the Conqueror. Mrs. Pierce held a responsible position in business before her marriage and is a leader in the Parent-Teachers' Association of the local schools

I met five other members of the family, Fond parents may overgate a boy's achievements, but little brothers and sisters are brutally frank. From "Baby" in the third grade of school to big sister in the Rhode Island State College, they all believe that Brother Walter is a marvel. They too have heard the distant stations and they repeat the announcements and call letters with all the linguistic colloquialisms of Spain, Australia and the rest.

#### Bridge by Radio

(Continued from page 1005)

declarer's partner (dummy) lays his hand on the table, the other three players retaining theirs. As the cards are read off at the station, in the order in which they are played, the listeners play the corresponding cards. Instead of gathering the cards into tricks of four cards, however, each player recovers the card he has just played and puts it either face up or face down, depending on whether his side won the trick or not. This is done in order to keep the hands intact, so that they can be rearranged after the play, when Mr. Whitehead will give further explanation of the bidding and play.

#### WIDESPREAD ATTENTION

Although twenty-seven stations are tied up for the broadcasting of the bridge games direct from New York City, there are fortyseven others which put the games on the air independently. Throughout this and foreign countries, thousands of bridge fans who are owners of radio receivers have clamored for their nearby station to broadcast the games; so that every week an average of seventy-four transmitters are telling the American public how to play a certain hand of the aristocrat of card games.

Many thousands of letters have been received from listeners in all parts of the United States, Canada, and foreign countries, telling how much the bridge games have been enjoyed, and asking that the "advance hands" be sent them. Some of these letters follow:

"Just a line of appreciation from one who is a dub at any card game, but who mjoys any and every game of bridge broadcast," writes D. Kerr, of Omaja, Cuba. "The set isn't functioning as it should, due to faulty transformers, but there are others on the way; so at present I'm getting along with substitutes, but it does not permit the use of a speaker so that the local bridge club can enjoy it. This club has been recently organized and get quite a kick out of playing the advance hands as advertised; and said kick will be complete as soon as we can get an earful of how the experts play it."

From Leicestershire, England, Henry

#### A HIGH-POWERED 10-TUBE MODEL FOR 1928



#### NORDEN-HAUCK **IMPROVED SUPER-10**

"Highest Class Receiver in the World"

This new and advanced design brings to you all the luxury and performance you could possibly desire in a ratio receiver. Absolutely nothing has been emitted to provide supreme reception—a new standard previously unknown. The up-to-the-minute engineering principles found exclusively in the improved Super-10 are comparable to the high compression head and super charger in an automobile engine.

In the Norden-Hauck Improved Super-10 you have -Wonderful Selectivity

-Faithful Reproduction with any Degree of Volume -Signals received at only one point

-Two major tuning controls for all wave lengths

-Wave band 200/550 meters (adaptable down to low waves and as high as 6000 meters with removable coils) Material and workmanship conform to U. S. Navy specifications.

The improved Super-10 is sold complete as a manufactured receiver, or we are glad to furnish blue prints and all engineering data for home construction. Upon request, new attractive illustrated literature will be promptly mailed to you without cost or obligation on your part.

Tear off and mail today-

Your correspondence or inquiry for further information is cordially invited

Write divect to

NORDEN-HAUCK, INC. ENGINEERS

"Builders of the Highest Class

Radio Apparatus in the World" MARINE BLDG., PHILA., PA., U.S. A Cable: Norhanck

NORDEN-HAUCK, INC., MARINE BLEG., PHILA., PA.

D I enclose \$2.00, for which send me, postpaid, complete Blue Prints and operating instructions for the new improved Super-10. DI enclose \$1.00, for which send me Blue Prints of the Model 500 B, C. Power Unit.

Name ..... Address .....







Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 230 Fifth Avenue, N. Y. C.



Strobodyne, Loftla-White Constant Coupled, Qualiford Improved Aristocras, Otiver Lodge, Beel's Super-Hoste Quan, B.-T Power Bis, Hammarhand-Roberto, Dally Ne 4, World's Record Super, Goodwin Aperiodic Dreed of Coupling Coupling of the Coupling of the Coupling of the Model of the Coupling of the Coupling of the Coupling of the MODEL "N" VARIO-DESSER

Teruh, Cuadraformer 6, Bestős 1927, Silver's 2 MODEL - ver-VARIO-DENESER Herometer and usinserst enally experiment of the control of the me, described and single 1.8 to 20 force - merc for

Obtains the proper grid enpacity on Obtains the proper grid enpacity of course, there and interest encourage of the proper course, the proper course of the 
personnel connections. You don't have to remote the connections. You don't have to remote the connection in the X-L. insert remove pressure. Connection is tight and will take. No vibrations can leaves. Releases inst Standard markings, or boxed in complete sets. each, 15 cents.

Investigate the Cootesin Asserboile Carolit. This is accollable to any set and adds a stage without added tuning controls.

X-L RADIO LABORATORIES

2426 Lincoln Ave., Chicago, III.

What.



Phillips Carlin and Graham McNamee broadcasting the playing of a bridge game

Field, 66/X, writes: "You will recall that I received WSAI over here some time ago and I am writing to thank you for your series of bridge games played by Tadio. The booklets are very interesting indeed and today the value of auction bridge, both as a recreation and as a mind-trainer, is al-arcidy appreciated and will be more so, due to your penoner work in this direction."

FROM THE JUNGLES

Simeon Quass, British vice-consul at Corumba, Brazil, writes: "You may be intersted to know that last Saturday I had the pleasure to listen in to a bridge lesson broadcast by WGY of Schenectady. This

unique experience, which certainly has head no precedent in this state of Matto Grass, and I do not think anywhere in Brazil, was made possible by an experimental shortwave set carried by Mr. Francis Gow Smith, of the Explorers' Club, New York, which is making an exploration through the littleknown regions of Matto Grosso."

From Walbidu, Hawaii, A. F. Costa, writes: "I have been enjoying your brigg games since you began broadcasting, but last might I was unable to get bone and mist." It is unable to get bone and mist. Therefore, please send me a copy of the game. I have four or five friends who are just as enthusiastic over your bridge games, and usually come to enjoy them."

# Roasted by Radio

(Continued from page 1001)

Industrial Conference of the C

Filament

Control

TE
"Rheastat

From the "Big, Friendly Radio House"

N<sup>EW</sup> 1928 Book offers fleest, eliminators, accessories at lowest parts, eliminators, accessories at lowest parts, accessor

126 West Lake St., Dept. 12, Chicag

FLECTRICITY

PAY A.C. and D. C.A. THE WASHING, Roddley, or B. placeting, Roddley, or B. placeting, Roddley, or B. placeting, Roddley, or B. placeting, in 2 no. 1, 200.

SCHOOL, of ENGINEERING, White Lodgley, monitors has proposed to the placeting of the placeti

inspector waited for it to come to a stop; but it did not. His brain mechanically began to attempt to translate the movements of the needle into Continental Morse. Inspector Merritt started. Three short

jerks, three long swings, three short jerks— SOS! He seized his pencil. "SOS SOS SOS Harold Dare at WROT SOS SOS SOS Dare SOS Help...". Inspector Merritt waited no longer. He

flung up the window—sprang into the driver's cab. "To the Dare studios—and step on it?"

The great car leaped ahead, with shrick-

The great car leaped ahead, with shricking siren it roared through the heavy traffic, dashed across busy intersections, missing careless drivers and pedestrians by inches, and swung round corners at a sickening speed. Inspector Merritt sat beside the driver and outlined a plan of action.

Ahead appeared the walls of the immense plant of the Dare studios, and the driver let the siren die. The car carcened, and swung into the driveway leading to the main offices. The policeman at the gate dropped his newspaper, rose from his comfortable chair—and dodderd aside as the great car paused not, but with a bound struck the chain stretched across the gate, snapped it, and skidded upon the gravel up to the main office building. The policeman followed at a run. "Come on, my friend!" cried Inspector Merritt. "We may need you too."

the broadcast studio by its lead-in. Through the corridors they raced. At the end of the hall they saw a door marked "Operating Room." Inspector Merritt drew his heavy Army automatic; his companions pulled their revolvers, and stealthly the trio stole down the corridor. Outside the door they halted. They could hear a faint hum of generators.

"Ready!" whispered Inspector Merritt. Suddenly he flung open the door.

With an exclamation, the black-haired arch-villain wheeled and saw that he was covered by three ugly-looking revolvers. Automatically his hands sought the ceiling. Inspector Merritt looked round and saw

Dare. In a flash his quick mind took in the situation. The courageous hero was almost unconscious. Inspector Merritt quickly raised his pict. He pulled the trigger—and the insulator which hed Diavelo's temporary radio-requency line shatered, leiting the bure frequency in the shatered, leiting the bure frequency in the shatered, leiting the bure frequency in the shater of the sha

"How did you do it?" demanded Inspector Merritt, as he and the policeman lifted the long inductance over Dare's head and began to strip off the screen star's armor.

"I really do not deserve such a great deal of credit for it," modestly replied Harold Dare. "I merely recalled that, since my armor formed an absorbing circuit within the inductance, any movement of the armor changed the relation of the two circuits, thus altering the period of the coll. "So, the sale of the coll of the coll. The coll of the coll of the two circuits, and the coll of the coll of the coll of the two circuits, and the coll of the coll of the coll of the transmitter in and out of reconnect. I thus signalled in Continental Morse, hopping that someone might be listening that someone might be listening.

"Very cleverly done," admired the inspector,

At last the hero stood free of the deadly armor. In an instant he was at the side of the beautiful Gloria, cutting the cruel cords that bound her to the chair. Tenderly he lifted her head and removed the gag from the girl's rosebud mouth. Her eyelids flickered.

"Gloria," he cried.

Gloria's eyes opened, she rose unsteadily to her feet, looked wildly around, and, as she swayed forward, Harold Dare caught her in his strong, tender arms.

Fiercely, Dandy Diavolo gritted his teeth.
"Foiled again!" he muttered.

Harold Dare looked steadily at him. "Yes, you are foiled again, as wrong inevitably is foiled."

And the noble Harold Dare and the Pair One went forth to another glorious days.







#### will solve your battery problem

M ORE than a million owners of General Electric battery chargers now enjoy radio programs without ever thinking of run-down batteries.

New low prices
Ent of the Rochise

2-AMP. \$1 4

\$24 5-AMP.
TRUNGAR \$1 0

Guaranteed by General Electric At night, as they switch off the radio they just turn on Tungar [the name of the General Electric battery chargers] . . . in the morning their radio storage batteries are pepped up and ready for active duty.

The Tungar is waiting to give you the same dependable, trouble-free, economical service. It is absolutely dry.

Your dealer can help you. Ask him to show you the popular 2-ampere Tungar that gives both trickle and boost charging rates. It charges "A" and "B" radio batteries and auto batteries, too.





Tungar—a registered trademark—is found only on the genuine. Look for it on the

# GENERAL ELECTRIC



BARON MUNCHHAUSEN'S SCIENTIFIC ADVENTURES, by Hugo Gernsback. In installments J and 4 the wily Baron gives us in detail, a picturesque story and description of his space liyer, his trip to the moon, his landing on the moon, and his views of the earth from the moon.

LAKH-DAL, DESTROYER OF SOULS, by W. F. Hammond, contains good science, thrilling episodes and tense situations, and will remain a vivid memory for many years to come. If you are at all addicted to nightmares, don't read this story at bedtime.

THE MASTER OF THE WORLD, Part II, by Jules Verne. The uncanny appearances and disappearances of the mysterious thing that threatens the safety of the world continue, until Inspector Strock solves the mystery in an extremely unexpected manner.

And many others.



charging business in your community with my Service Station Charger—it's years shead of ordinary chargers—handles 50% to 70% more batteries. I explain everything—start you in a business of your own and put you on the way to big money. Write for FREE BOOK.

C. F. HOLMES, Chief Engineer, Dept. R.N. Independent Electric Works
5116 Ravenswood Avs. Chicago, III.
FREE BOOK-Just Out

#### TRANS MITTING APPARATUS

A Complete Stock at "Chi-Rad" In addition to our regular broadcast apparatus we carry a very good stock of transformers, chokes, grid leaks, high test condensers, etc., for trans-

NEW SHORT-WAVE COILS Specially built by "Chi-Rad." Write for descriptive bulletin and catalog. Dealers and set-builders please use business letterhead when writing for

Chicago Radio Apparatus Co. 415 S. Dearborn St., Dept. RN, Chicago

# What's your trouble Here's the answer to any Radio Roblem that ever existed



Radios Greatest Question & Answer Book

116 Pages-9 x 12 Inches

Be prepared—This means but 50c, and it is well within the means of everyone.

#### 1001 RADIO QUESTIONS AND ANSWERS—50c

THESE questions are the ones arising every day of the year—they are the ones that are costing you money through lack of knowledge. But it is so unnecessary now! This great Question and Answer Book, compiled by the staff of Radio News, probes into Radio and its problems from every angle—and gives answers that have the sweet tinkle of money savel.

Circuits, Amplification, Balancing, Regeneration, Transmission, Set Construction, Operation, Speaker Design, Control, Electrification, Accessory Installation, Antenna Possibilities —there's not a thing about Radio that it misses.

#### 1001 RADIO QUESTIONS AND ANSWERS

50c at all newsstands or direct

EXPERIMENTER PUB. CO., INC. 230 Fifth Avenue New York, N. Y.

#### Radio-The Alarm Clock of a Nation

(Continued from page 997)

but find that I must work for all I get, just as in other activities of life. These classes are better than electric horses, too."

Men who go down to the sea in ships, men who go under the sea, too are numbered among the students. The crew of the submarine V-3 line up for the daily bends and in the Marine Barracks at Quantico, Va-, many followers of the health classes may be found.

From Albany, a barrister wrote that, after exercising for a month, he felt "eight per cent better physically and ninety-five per cent better mentally." Some overweight students have reported losing as much as forty pounds from the exercises.

Men, as well as women, exercise to reduce; but the women stress the woes of wide hips or fat legs, which they are anxious to make more symmetrical, if one is to believe the pleas for personal advice which they direct to the instructors.

#### THE FLAVOR LASTS

An old lady of eighty-one in a Pennsylvania fown has been taking the exercises for one year and in all that time has missed but two mornings. Showing that young women aren't the only ones interested in how their clothes look, this elderly enthusast writes with pepr "My dressmaker thinks my figure has improved wonderfully and my health has kept company."

Filled with irony was this message from a man in Massachusetts who wrote the insurance company: "Keep up the good work. If my health improves much more I will give up my insurance policy."

Judging from many of the letters, the family groups start with one enthusiast who finds it difficult work as missionary among the less interested members of her family. A mother of five children in East Orange, N. J. described her difficulties: "I get up every morning at 6:30 o'clock, start things going and then run into the dining-room where I tune in on the gym classes. I get up the kiddies, but I never could manage my husband, who lays in bed until the last minute. Finally, one morning, I persuaded him and since then I've had no difficulty at all. You should see us all together. From the baby who is four years old and bends his curly-head to touch the floor when you tell us to do it, to the "old man" of the group who is becoming of a much more sunny disposition since taking the exercises, we are all deriving great benefit from our class."

HOW TO DO IT
There are six rules which are most im-

There are six rules which are most important if the listener is to derive any benefit from the exercises and Mr. Bagley lists them as follows: Drink a glass of water before exercising:

Have windows open, top and bottom; Good ventilation is important, but the room should not be too cold;

Have clothing loose at neck and waist; Follow the director's instructions carefully:

If possible, give a full half hour to the exercises every morning.

Doctors all over the East are recommending these gym classes to patients, for all sorts of ills and aliments. Whole clubs make it a rule to devote fifteen minutes or a half hour each morning to the radio calisthenic school.

Realing that, while the early bird may get his audiners of exercising, he has to keep them interested to hold them, all the physical-culture directors of the air try to inject the human note into their instructions and find that a little human between the same and 
While exercise is so important for health, Mr. Bagley and his associates stress the importance of the right kinds of food, of

drinking plenty of milk and of cating slowly.

The morning line-up is no place for a fat person, for he must stand plenty of kidding, which comes through his loud speaker and is directed against excess avoirdupois.

Healthy outdoor exercise and plenty of games are urged to augment the broadcast effort for stronger bodies. Statistics show that, in the past fourteen years, the average span of life has been lengthened five years, giving the lie to the general idea that this world is killing itself off in youth by the wrong kind of living.

The "Health Tower" classes and the WOR group have reached countless numbers of people who never exercised before. Men and women, prevented from leading an active physical life by their jobs and their curvimment, can undo some of the pessible in exercise which meets their needs, sends their blood circulating freely and starts them on their daily duties in good shape. And so the little gym class of the sin,

which was an experiment three and a half years ago, is now one of the most important and far-reaching agencies to aid the health of the entire world. It goes right into the home, requires none of the intricate accessories associated with old-fashioned gymnasiums and costs nothing.

For those of sedentary habits, the first try-outs may result in stiffened muscles which have rebelled against sudden work; but persistency is what is needed and, after a month, health is a habit and radio has done it.

#### Use of a Charger with 4-Volt Battery

TRICKLE CHARGERS, designed for charging 6-volt batteries can be easily adapted to 4-volt batteries without much expense and without any changes in the regular construction. It is necessary only to attach the end of a resistance winding from a 6-ohm rheostat to one of the posts on the charger. The resistance until taken from one of the air-cooled type of rheostat is best for this purpose.

#### Caring for the Socket-Power Units

(Continued from page 1007)

ment, such as transformers, costing several times more than batteries.

From all this it will be seen that the attention required by a socket-power unit, though small in amount, must be intelligent; and, if it is intelligent and if, still more essential, it is regular and systematic, the best of service over a long period can be expected from any of the many standard makes now available. Accordingly, performance proves to be determined quite as much by the user as the manufacturer.

#### Full-Band Tuning in Radio Receivers

(Continued from page 1019)

ceiver, will enable it to be tuned so that it will cover the broadcast wave of 20kilocycle width and, at the same time, be selective. In Fig. 2 is shown the response curve of the set developed by Dr. Vreeland; it will be seen that the peak of the curve is relatively flat with a slight dip in the middle at the carrier-wave frequency and that the sides of the curve are extremely steep, thereby insuring good selectivity. In other words, there is practically equal amplification of all notes up to 10,000 cycles, and above that a sharp cut-off, thereby minimizing the effects of wave interference.

First of all, Dr. Vreeland has developed a band selector. It comprises, in general, a system of reactances so related to each other that they are mutually balancednot merely at a single frequency, as in the case of an ordinary tuned circuit (Fig. 1)but also at any frequency within a given band. At any frequency outside of this band the reactances are not balanced and the unbalanced impedance is high. As a result of this design, the band selector responds to all frequencies within its characteristic band, but is non-responsive to all frequencies outside it. As explained, if the system is correctly proportioned the cut-off at the limits of the band is very sharp.

The elements of a circuit in which such a band selector is incorporated are shown in Fig. 3. It employs two reactive couples X1 and X2, preferably alike, having each a capacity and an inductance that cancel out or balance each other at the same frequency, together with a third reactance X3 which is common to both circuits. The third reactance is small, in comparison with the reactances of the two reactive couples, and may be either inductive or capacitive.

FUNCTIONING OF THE CIRCUIT

At some particular frequency F1 (this being the frequency at which the reactances of the couples X1 and X2 are balanced) the overall reactance of the circuit including X1 and X2 will be zero; current at the frequency F1 will circulate through the branches X1 and X2 without going through X3, and the system will have zero reactance at this frequency.



#### RADIO PATENTS TRADE MARKS

JOHN B. BRADY Patent Lawyer

Ouray Building Washington, D. C.



PATHEX

NEW YORK CITY

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year.

Experimenter Publishing Co., 230 Fifth Avenue, N. Y. C.





POWER UNIT

cones. Operates on "A" battery coormous volume. Most amazina
ormous volume. Most amazina
rou have ever heard from any
nits. Sent C.O.D. PAY POSTMA
tisfactory, return in tea days and
til be refunded.

NSPEAKER RADIO CO., Dept. X
199 Fulton Street, New York

your copy reaching you each month. Sub to RADIO NEWS-\$2.50 a year. Experi Publishing Co., 230 Fifth Ave., N. Y. C


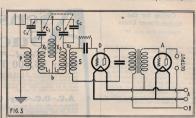


Diagram of a broadcast receiver including a single band selector, X1, X2 and X3.

At any other frequency, the reactive couples XI and X2 will not be balanced within themselves; the result will be a difference of potential between the points a and b. If the given frequency is lower than FI, the reactances of XI and X2 will be capacitive. If, therefore, the reactance depends upon the relation of this inductance to the inductances L1 and L2. If the reactance X3 is a capacity, the band's width is determined by the relation of the capacitive reactance of X3 to the capacitive reactance of C1 and C2.

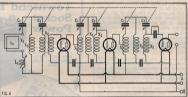


Circuit of a loop receiver in which are incorporated three band selectors, X1, X2 and X3.

X3 is inductive as shown, it will tend to neutralize the unbalanced capacities of branches X1 and X2; provided that their combined reactance is not greater than X3. The width of the band amplified depends primarily upon the relation of X3 to the other two reactances of the circuit. Thus, if X3 is an inductance, the band's width
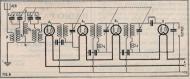
#### EFFECT OF BRIDGING REACTANCE

It is interesting to note the relation of the frequency-characteristic of the band selector to the characteristic of a tuned resonant circuit. When the bridging reactance X3 is removed, the two branches X1 and X2 together constitute a resonant circuit



Schematic diagram of a receiver having a single band selector coupled to an aerial, and a spaced band R.F. amplifier. Ls are the "spacing inductors."

tuned to a certain frequency F1; this being one of the limiting frequencies of the band of the selector unit. (See Fig. 5.) When the common reactance X3 is added again to the circuit the curve takes the band form shown in full lines; the limiting frequency F1 corresponds to the natural frequency of the tuned circuit and the limiting frequency F2 is either below or above this frequency, depending upon whether the reactance X3 is inductive or capacitive.

In Fig. 3 the band selector is shown in use with an aerial; but the circuit may be as readily used with a loop antenna. The capacity introduced into the branch X1 by the antenna is compensated by a fixed capacity Ce in the branch X2. In order to permit compensation for an antenna of any desired capacity without disturbing the frequency-calibration of the system, there is an additional variable capacity Cx, which makes up the difference between the capacity introduced by the antenna and the capacity Cc, so that the balancing of the system is assured. Cx is adjusted until the signal has maximum strength; after which the setting is permanent while the same antenna is used.

#### MULTIPLE R.F. STAGES

The band selector also lends itself readily to use as an interstage coupling element of a radio-frequency amplifier, as shown in Fig. 4. In this arrangement each of the selective elements has, in itself, a substan-tially rectangular band-characteristic. With two or more such units combined in an R.F. amplifier, the overall frequency-characteristic has a similar rectangular form with a sharper cut-off. Increased sensitivity and selectivity are thus secured, with no diminution of the band width. This is in marked contrast to the tuned-radio-frequency amplifier, where each increase in the number of stages narrows the characteristic.

When the various band selector units are made alike, as they may readily be, the whole system, including the antenna selector, is symmetrical and all the elements may be operated by a single control, as is shown. In the band amplifier of Fig. 4 the several stages have different frequency-characteristics which are not rectangular in themselves; but, in combination, they produce an over-all band-characteristic of rectangular form. It should be also noted that, in this case, the cut-off is so sharp that stations can be separated with the greatest ease

#### OTHER VALUABLE FEATURES

An important feature of the spaced-band amplifier is its inherent stability. Since the several circuits are not synchronized, the tendency to regeneration and oscillation is small. Other features include an astatic winding of the coupling coils or transformers, which renders negligible the magnetic coupling between the stages; and mutually-reversed primary and secondary windings, which cause a phase reversal of any external electrostatic couplings, thus putting the potentials of the several stages in such phase relation that they do not cause regeneration. The resultant of these three features is an amplifier of such stability that no capacitive neutralization or balancing of any kind is required; and the coupling transformers may be placed close together without shielding of any kind.

Another variation of the band selector is shown in Fig. 6. The band selector is coupled to the antenna and feeds the amAYear Ahead Build the Wor

#### Low Price, Spectacular A. C. Tube Set

#### Big New York and Chicago Hit!

THE simplicity, dependability, and splendld performance of the A. C. EVERYMANA 4 has made it one of the most popular delute sets excleved. Carton 5. Butler, Technical Haddon Editors of the Chicago Breating American, in his article of January and Chicago Breating American, in his article of January and Chicago Breating American, in his article of January and Chicago Breating American, and the Chicago Breating American, and the Chicago Breating, and the Chicago Breating, volume and distance, with own initial cost and low

Complete List of Quality A. C. Parts-Only \$68.5	15
	2.6
1 Set Everyman Four Colls.	\$5.0
1 7" x 21" Engraved Micarta Panel. 2 Hammarlund .0005 Midline Condensers.	3.7
2 Hammariund 30005 Midline Condensers.	11.0
1 Hammarlund Jr. Condenser (Balancing)	1.7
3 No. 9040 Benjamin Cle-Ra-Tone Sockets.	2.2
1 Benjamin 5-Prong Soeket	.9
7 X-L Binding Posts (Ant. Gnd. B Plus 45, B Plus 90, B Plus 180, Speaker).	
1 10° x 20° x 34° Fritts Baseboard	1.0
1 Muter No. 3300 Supreme Transformer.	.8
1 Muter No. 3320 Supreme Transformer	7.0
1 Muter No. 2700 Clarifler	7.0
1 Muter No. 3710 1 Megohm Grid Leak	5.0
I Muser No. 5/10 I Megonin Grid Leak	.5
1 Muter No. 800 Grid Leak Mounting. 1 Muter No. 201 0001 Bakelite Condenser.	.1
1 Muler No. 301 30001 Bakelite Condenser	4
3 Muter No. 507 Mfd. By-Pass Condensers. 1 Muter No. 508 1 Mfd. By-Pass Condensers.	2.2
2 Muter No. 2750 R. F. Choke Colls.	0.9
1 Muter No. 1900 Variali Condenser	3.0
1 Muter No. 1900 Variali Condenser.	.7
1 Muter No. 2305 1/4 Ohm Power Rheostat	1.0
1 Muter No. 2315 1 GOhm Power Rheostat	1.0
1 Muter No. 2331 30 Ohm Potentiometer. 1 Muter No. 2902 2000 Ohm Power Resistance.	1.0
1 Muter No. 2902 2000 Ohm Power Resistance	. 5
1 Muter No. 2975 750 Ohm Power Resistance.	.0
1 Muter No. 2950 500 Ohm Power Resistance	3
1 Muter No. 3600 A. C. Filament Transformer.	8.5
1 Muter Binding Post Strip, 1" x 6" x 1/4"	.5
1 Muter A. C. Bakelite Control Panel, 2" x 6" x 3;"	1.5
1 Diuter No. 1600 Approved Power Switch	. 5
Total	\$68.9
SPECIFIED PARTS INSURE BEST RESULTS	

#### This Is the Set FOR YOU TO BUILD CAN BE BUILT IN ONE HOUR!

See your Dealer for Everyman 4 paris and full directions for assembly. You may also write Everyman 4, Dept. 827-C, 76th and Greenwood Ave., Chicago, Ill., for folder giving full information

The satisfaction of thousands of fans who have already built be Everyana 4 is illustrated by the Everyana 4 is illustrated by the satisfaction of 
#### Feats of Reception

REPORTED BY BUILDERS IN NEW YORK CITY
A builder of the Everyman 4
in Newark has no troubte in
setting WPG, Atlantie City,
at 3 P.M., with WAAM and
WAAT on the air. Not a
trace of interference. A radio fan on University listens to WBBM, Ch and WTAM, Cleveland, WRNY is on full power

PROFESSIONAL SET




#### MARCH BLUEPRINTS

You can obtain a complete set of blueprints for these receivers direct from RADIO NEWS

THE SILVER SCREEN-GRID SUPERHETERODYNE-Radio News Blueprint Article No. 48...\$1.50 THE ALL-ELECTRIC EVERYMAN FOUR—Radio News Blueprint Article No. 49..........\$1.00 THE PACENT DISTANT SIGNAL AMPLIFIER—Radio News Blueprint Article No. 51. . . . . \$1.00

> Order Direct from RADIO NEWS 230 FIFTH AVENUE, NEW YORK, N. Y.

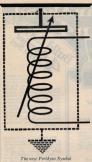MENTION NAME OF RECEIVER AND ARTICLE NUMBER



## PERIDYNE

THE PERIDYNE principle and PERIDYNE circuit, as developed by Hugo Gernsback, Editor of Radio News, is one of the great circuits of the year.

An entirely new principle-so new, in fact, that a new symbol had to be designed for it, is used in this remarkable circuit. The PERIDYNE uses the new shield tuning system, which makes the set unheard of in selectivity and as a distance getter. Thousands of PERIDYNES have already been built, and every user is highly enthusiastic with the results.

The PERIDYNE is a single-dial set, and uses five tubes. It can be operated on batteries or from alternating current. The complete Consrad pattern describing this circuit gives all data, of every sort, how this circuit can be built in a minimum space of time.

The PERIDYNE is a most simple set to build. 50c., enclosed with coupon below, will bring the Official Construction Book, in-cluding 5 full-sized blueprints, and detailed instructions.

> Use Coupon Immediate Delivery

CONSRAD COMPANY, Inc., 236 Fifth Ave., New York, N. Y.

City.....State.....

plifier through its output coil S. A spacedband amplifier of the type just described is employed. In the arrangement here shown the three stages are all structurally similar and the spacing of the waveband is accomplished by the use of fixed "spacing inductances" in two of the stages as shown; or two of the stages may have small "spacing capacities."

In the design of the apparatus due attention must be given to securing a suitable relation between the effective inductance and the effective capacity of the amplifier stages and the same factors of the handselector elements. When this is done the frequency-control curves of the various elements are readily synchronized, so that the whole system may be operated by a single

cation of parts in the unit. The two cables

A and B are for connecting the device with

### What's New in Radio

(Continued from page 1012)

Probably the most interesting feature of the power unit is the new rectifier unit which is used. It consists of a series of couples made up of cupric-sulphide discs facing others of magnesium. The rectifier is clearly shown in the pictures at R. The square fin-shaped copper sections are the heat radiators, and the rectifying discs of the couples make up the solid section which may be seen between the fins. There are sixteen couples in the unit and they are

the "A" posts of the set and the lamp socket, respectively. The switch (Sw) is located on the front panel and the voltage regulator (VR) and rectifier (R) are mounted on the top panel. The choke coils (L1 and L2), filter condensers (C1 and C2), and the power transformer (T) are mounted inside the metal can. Manufacturer, the Knapp Electric Corporation.



forced together under a pressure of almost a half ton. In its operation, a thin film forms on the

surface of the discs in a rectifier of this type. This film functions much like a series of small electrically-charged bubbles; which offer practically no resistance to current flowing in one direction, yet act as an almost perfect insulator to currents of reverse polarity. If, because of an over-load, the film breaks down the unit heals itself; and as a result the rectifier has a normal life of over 1,000 hours. The cells are connected in a series-parallel or "bridge" circuit which gives more efficient rectification and, at the same time, increases the current-carrying capacity of the unit.

The dry polarized type of condenser used in the power unit is the second interesting feature; these condensers operate on much the same principle as the rectifier unit (as they hold a charge one way only) and are an entirely new development. Two such are used in each unit, each having a capacity of approximately 1,500 microfarads and being contained in a case only 2 x 2 x 7 inches. The condensers employ a fabric core to which is cemented one side of the active charge-holding material. The other plate of the condenser consists of a double outer layer of metallic foil. Experiments with condensers of this type show that they improve with age: the total capacity increases and the leakage decreases with continued

The pictures given above show the appearance, mechanical construction, and lo-

#### New Pleated Diaphragm is Used in Fan Speaker

As a result of several months of experiment with various types of loud speakers, a new reproducer has been developed which is neither a horn or a cone. It employs the Loumiere type of pleated-paper diaphragm. 20 inches in diameter, attached at the center to a direct-drive loud-speaker unit. Its unique construction is clearly illustrated in the two pictures given here and the advantages which are gained by the design are not difficult to appreciate.



View of fan speaker with diaphragm installed in the broker position.

From the electrical viewpoint, the new speaker is not unusual; but it is entirely satisfactory. It may be operated in connection with radio receivers employing three or more tubes, and it responds over the full orchestral range with unusual fidelity. It gives good volume for any given signal and provides startling distinctness in radio reception.

Because of the striking resemblance between the folds of a fan and the diaphragm of this instrument, it is known as a "fan speaker." The pleated diaphragm is made of a very tough paper material and is, not only collapsible, but reversible. It is shipped in a knocked-down form to conserve space and packing material, but may be assembled in a few moments without the aid of tools. Also, the diaphragm may be folded up, opened and reversed many times without damage.

A feature of the pleated diaphragm is



The speaker in knocked-down form

that it is artistically decorated with four distinctive designs. A beautiful brown-andgold design has been printed on one side and, on the other, there is an equally attractive silver-and-black design. When the diaphragm is opened, two different designs are available; then, by collapsing the diaphragm and turning it inside out (so that what was formerly the edge becomes the center and the center becomes the edge) two new designs are brought into view.

One picture of the "fanspeaker" shows the unit ready for operation and the other the various parts after they have been unpacked but before they have been assembled. When placing the loud speaker in opera-

tion, it will be noticed that one cord has been marked; this should be connected to the "B" battery side of the circuit. Manufacturer, Fanspeaker Radio Com-

#### New Crystal-Detector Unit Fits in Tube Socket HE black tube-shaped unit, a cross

sectional drawing of which is printed this page, looks like a radio vacuum tube, fits into a tube socket and is used in place of a detector tube; but it is not a vacuum tube. It is a stabilizing- detector unit of the carborundum-crystal type and may be substituted for the detector tube in any radio receiver after slight changes have been made in the wiring. Use of a carborundum stabilizing-detector

unit in place of a vacuum tube in the detector socket of a set provides the receiver with the desirable clarity of a crystal set and, at the same time, retains practically the entire sensitivity of the original receiver. It clears up reception and tends to mini-



Drawing shows mechanical construction of car-borundum-detector unit. P. potentiometer; D, crystal unit; C. fixed condenser.

#### A. C. Connectoralds provide a new and remarkably easy way to convert battery operated

sets to use the new A. C. Tubes NO REWIRING SIGNALS CLEAR

RESULTS ARE REMARKABLE PICKUP IMPROVED

You can now run your battery set with the New A. C. tubes and no batteries at all. Na-ald CONNECTORALDS provide a remarkably easy way to do this, at the same time assuring you of the full efficiency

from these excellent tubes. All you need is a Na-ald A. C. CONNECTORALD kit (No. 905 for 5-tube sets, No. 906 for 6-tube sets, No. 907 for 7-tube sets), Na-ald volume control, any good filament transformer, and "B" eliminator (your present eliminator will do if you are using one).

The Na-ald A. C. CONNECTORALD kits include Y tap resistors. By-pass condensers and midtaps, giving proper C bias for both power and radio frequency tubes.

The harness is so arranged it can be quickly, easily, and neatly connected, regardless of location of tubes.

IMPORTANT-Na-ald A. C. CONNECTORALDS are equipped with a special device for controlling oscillation. Small suppressors or resistors slip into slots in the connectoralds, automatically going into series with the grid of the tube. This feature not only controls oscillation, but gives you any desired amount of sensitivity for your particular locality. The new A. C. tubes with Na-ald Patented A. C. CONNECTORALDS will help you get better quality and greater distance.

Na-ald A. C. CONNECTORALDS work in Atwater Kent. Crosley Bandbox, Kolster, Radiola 16, and practically all other battery sets.







Order your kit today from your dealer or direct.

No. 905-For 5-Tube Sets.								\$	9.00	0
No. 906-For 6-Tube Sets.								. 1	0.0	ä
No. 907-For 7-Tube Sets								.1	1.0	
Na-ald Volume Control									3.0	Į

Also write us for free Na-ald A. C. Booklet. Address Dept. RN1 ALDEN MANUFACTURING CO. Springfield, Mass.

There is a NA-ALD Adapter—Connectorald—Socket—for all tubes, all sets, all purposes



DEBLERS & SET BUILDERS



TOWER PRODUCTS ON SALE EVERYWHERE

#### The BURT Cell

Stabilized Oscilloscope



WARREN r 1 to 10 tubes. Complete with tube. aranteed. Was \$35. Now DIRECT yea, \$21.00. Write: (RREN ELECTRIC CO., Dept. R.N., Peoria, III

#### A Smooth, Positive Volume Control for Circuits Using "AC" Tubes

THE delicate balance of "AC" circuits requires a different method of volume control than that commonly used with



tenere ye seeks tance is the secondary of an R.F. The RX-100 Radiolm in the secondary of an R.F. The RX-102 Radiolm in the secondary of an R.F. The RX-102 Radiolm in the secondary of an R.F. P. The RX-102 Radioln in the secondary of an R.F. Secondary provides volume control and not detune. The same unit has the period of the result of the R.F. Segue, across one of the R.F. Segue, secondary used across one of the R.F. stages.

A Centralab PR-039 Power Rheostat in series with the "AC" transformer will provide accurate voltage control and lengthen the fife of the tubes. Centralab wire wound Potentiometers and Fixed Resistors will prove trouble-free in the power circuits.

Write for full information about these high quality controls. The new "AC" information sheet is now ready for you

CENTRAL RADIO LABORATORIES 19 Keefe Avenue



AT YOUR JERVICE WHITEHALL HOTEL

ST. AND BROADWAY you visit New York. All rooms

rates of \$5 per day for two! A per-fect hotel. Ample parking space and near numerous garages. Exceptional Restaurant

I. McAULIFFE-Res. Manager

earn money and prizes in your spare time. Write Me Today Jim Thayer, Dept. 53, Crowell Publishing Co.



mize extraneous noises, because of the inherently-good rectifying characteristics of this type of detector.

In addition to the advantages named above, use of this detector unit eliminates the plate-battery drain of the detector tube and reduces the detector drain on the filament battery from 0.25 ampere to .025 ampere, the current required by the potentiometer and crystal of the detector unit. The stabilizing detector makes possible also a check to self-oscillation of the radio-frequency tubes, thus controlling howls and permitting peak efficiency over the entire waveband. Also, the resistance of the detector may be made so high that it will have but slight damping effect upon the tuned circuit, with the result that greater selectivity is obtained.

The wiring diagram accompanying this article shows how the carborundum-detector unit may be inserted in a standard receiver, using tuned radio-frequency amplification, a non-regenerative detector, and transformer-coupled audio amplification. In this case short-circuiting the grid leak and condenser is the only important change which it is necessary to make in the wiring of the receiver; but in other circuits, especially those which use a regenerative detector, the change will be slightly more elaborate. In almost all cases, however, the set may be adapted to the new detector in a few minutes' time; and complete instructions are provided with each detector unit.

The drawing shows the mechanical construction of the detector unit. It consists of a small fixed condenser, a crystal unit and a potentiometer. These parts are all lite case, which takes the form of a vacuum tube. The potentiometer may be adjusted by turning the top of the tube until the most satisfactory reception is obtained and then no further attention is required. The schematic wiring diagram shows the connections inside the detector unit

Manufacturer, the Carborundum Com-



Diagram shows how a carborundum-detector unit is connected in the detector socket of a standard receiver.

#### D. C. to A. C.-And How

(Continued from page 1017)

heavy-duty rheostats are already on the market.

We have previously referred to temporary line-voltage fluctuation; this usually occurs at the time when the heaviest load falls on the lighting company's mains. The voltage at the central station may be maintained constantly at a fixed standard, but the drop in various circuits causes this line fluctuation. If this condition prevails, the tube voltage will naturally follow the risc and fall in the main line. The operating characteristics of the A.C. tubes, however, are such that average fluctuation will not affect their operation or life; but, as we have said before, it is very necessary to know just what the average voltage is and adjust for it. In the re-wiring of the set keep the grid and plate leads away from the filament lines as much as possible. A properly-converted set should not pro-

duce A.C. hum audible more than a few inches from the loud speaker. It is suggested that some means of identifying easily the last audio socket be adopted by constructors. The accidental insertion of the 226 tube in this position

will result in an almost-immediate burn out. VOLUME CONTROL

Considerable difference of opinion exists regarding the best method to control volume in A.C. sets. The favorite method in battery-operated sets was to vary the filament temperature in one or more of the R.F.tubes. Although some manufacturers of A.C. sets use this method today on A.C. tubes of the 226 type, it is not considered ideal. The heating of the heavy filament is slow in following the rheostat adjustment, and this naturally introduces a very annoving time-lag. It is particularly noticeable when trying for distant reception.

We have previously discussed the necessity for keeping the plate current of the 226 tube at the minimum ripple-voltage point; this happens to be at about 3 milli-amperes. If the bias on the R.F. tubes can be reduced simultaneously with the filament temperature, this will hold up the plate current and keep out the ripple. Some bias must be maintained at all times, however; as an uneven flow of grid current, and consequent modulation and distortion of the signal, will result without it.

A high variable resistor across the secondary of the first audio transformer has been used by some; but this method is not recommended as it has a tendency to overload the detector. Varying the grid bias as a means of volume control is quite effective on circuits using 227 tubes as amplifiers. but is not recommended for 226s; as this method is apt to shorten the life of the tube. A high variable resistor (100,000 ohms) in the R. F. plate returns will do the job, in a way, but the disadvantages have already been mentioned. It would seem that the most logical procedure in controlling volume is to go to the heart of the matter and control the signal instead of trying to suppress it after it is amplified or rectified. Naturally this must be done in the antenna circuit. The most approved method is to couple variably a semi-aperiodic primary to the secondary of the antenna-coil unit. Unfortunately this is not always easily done in converting sets, as the antenna coil is usually of the fixedcoupling type. If it is at all possible to rotate the primary antenna winding, or secure a similar effect through taps, it is strongly recommended that this be done to obtain best results. A semi-aperiodic an-tenna coil of 8 or 10 turns of wire, wound on a bakelite tube and variable in its relation to the secondary, will work out very

A variable resistor with a maximum of around 5 megolums, in shunt with the antenna coil, will control volume quite satisfactorily. It is suggested that for local or very strong signals the aerial be disconnected entirely from the set; this may be done by means of a snap switch conveniently placed.

A.C. sets give the very best reproduction when the circuits are tuned to exact resonance with the received signal. Any departure from this condition will detruct from one of the most pleasing features of only when the strongest signal is not too loud when the stringest signal is not too loud when the stringest signal is not too name with the volume control at unknimen. Any attempt to control volume by detaining and an apparent lack of selectivity.

#### THE TUBES

Due to the fact that the A.C. tubes of the 258 and 227 types are new on the market, nany experimenters are inclined to be supptial regarding their performance. The actual development of these tubes has been performance has been under observation over a long period. The characteristics of the 258 are approximately the same stars of the familiar 201A types long life may be expected, provided the tubes are open expected, provided the tubes are open correct grid bias is quite essential for the successful use of the 258.

The characteristics of the 227 are such that by using this tube in all stages, except the last A.F., greater signal volume as combe less tendency towards A.C. hum, although a properly designed or converted et using 220 should be practically free from the control of the emitter. The sace of A.C. these is particularly continued to root theroughly the The 22f control of the The 22f (control of the control of the control of the The 22f (control of the control of the theory of the control of the

about 30 seconds to come up to operating temperature. The momentary application of excess heater voltage to accelerate emission should never be tried. The A.C. tubes are operative at 25 cycles as well as at 60 cycles.

#### TROUBLES

Pronounced A.C. hum in the set may be due to several causes; the wiring of the filament lines if not twisted may cause hum. Frequently the "B" supply unit is at fault because of a defective rectifier tube. Should an internal leak develop between the cathode and the heater of the separate-heater tube, hum or noise will result; but this latter condition is of rare occurrence. Unshielded power transformers, if in close proximity to the set, will introduce line disturbances which sound very much like static. When separate-heater tubes have an excessive voltage on the filament, signals will gradually become weaker until, in some cases, they disappear. This is due principally to what is called secondary emission; namely, that caused when the grid gets sufficiently hot to emit (independently) electrons. This will, of course, disturb the stream of electrons and, consequently, the current between the cathode and the plate,



# Guaranteed Socket Power Unit S 3 5 Vo-Day Guarante Charles of the Control of

el [Station W. S. B. C., corned and operated by ] se Changes Your Set Into a Short-Wave Receiver

U.S. upon receipt of \$15 M. O., or C. O. D. postage, upon receipt \$1.00 to guarantee carry charges.

When ordering state k of set so that detailed rections for use may given if necessary. A state type of tubes, such



#### The SUBMARINER

reagactions of that active one by our lawly, this district was a proposal set on contribution between 25 and 68 miles of contributions with sets such as T. It. F., Neutronlyne, Super-It dynn, regenerative sets, and many other types. No solid tubes or hasteries required, who obtained to the region of the set of th

SHORT-WAVE RECEPTION

Is reacted because they penetrate better, and there is state. There are several poserrial stations using the wave to overed by the "Sulinarines" for breadnessing preciains. may also learn code by listening to amateurs from all parts of words. You will have a highly difficient short-wave receiver we

ORDER TODAY

J-M-P MANUFACTURING CO.



PATENTS As one of the object pates

PATENTS As one of the object pates
forms in America we give in
ventors at lowest consistency
results, eridenced by many well known Patents of estimated
conlinary value. Bask Patent-Osses, free, such as the

# The Silver Screen-Grid Superheterodyne

(Continued from page 1024)

decreasing the filament voltage for the 222type tubes until oscillation stops and rotation of the oscillator drum produces no squeals. The receiver may now be tuned at a regular superheterodyne, the Antenna and Oscillator dials serving to select stations. As mentioned previously, stations between approximately 215 and 455 meters will be heard at two points upon the oscillator dial. In preliminary testing, some station between 440 and 460 meters should be tuned in for best response on both dials. It will be observed that while the station can be heard at two points on the Oscillator dial, one point will be stronger than the other. Which of these points is strongest is determined by the position of the oscillatorcoil rotor, which should be turned about 180 degrees in order to make the lower wavelength point (with oscillator-condenser plates least engaged) strongest, and this oscillator-coil rotor should be left set at about 45 degrees with respect to the stator coil. The selectivity of the Antenna dial is determined by the position of the antenna coil rotor; greatest selectivity at least volume being obtained with the antenna rotor at right angles to the stator coil. Antenna selectivity and the sensitivity of the receiver are further affected by the position of the "Sensitivity knob;" this, through the midget regeneration condenser, controls regeneration and oscillation in the first detector and if turned too far in, will naturally cause first-detector oscillation, so that a large number of squeals will be heard in operation. Care should be taken never to use this condenser except on very weak stations, when, after the station is tuned in, it should be turned up gradually to increase signal strength with slight readjustment of the Antenna dial to compensate for the varitions in tuning caused by the Sensitivity con-

If it is desired to operate the receiver as a seven-tube set, omitting one intermediate stage-and this is really desirable except for extreme long-range reception-the first R.F. amplifier stage can very easily be dropped by simply pulling the clip lead in the left-hand compartment of the time-signal amplifier over into the next compartment to the right and clipping it on to the top lead of the second 222-type tube. The clip in the second compartment, ordinarily going to the second tube, should be ignored. Thus the first transformer in the intermediate amplifier feeds the second tube, which, in turn, feeds the third transformer; so that the tube in the first compartment and the transformer in the second compartment (from the left) are simply dropped out of the circuit. It will be found in operation that the tone quality will be somewhat better when using only two intermediate stages than when using three; but the sensitivity in the receiver will be greatest using three stages, and, of course, greater sensitivity means greater noise and stronger signals. The last audio-amplifier stage can also dropped very easily by simply moving the loud-speaker cord tips from the two "maximum" tipiacks to the two "minimum" tipjacks; although this course is not recommended except where an external power amplifier is used, in which case it is best to leave off the second audio stage altogether. An output transformer should be used connected between the output jacks of the set and the loud speaker.

#### FOUR TUNING RANGES

It will be observed in tuning the set that, when using the lower-wavelength heterodyne point of the Oscillator for all signals, both dials will not track. This condition can be remedied by tuning in (say, KYW or KSD) a very high-wave station, and removing turns from the top end of the oscillator coil until the Oscillator dial reading for this high-wave station coincides with that of the Antenna dial. Actually, it may be desirable to remove turns from both oscillator and antenna coils so that KYW or any other 535-meter station will come in with both Oscillator and Antenna condensers interleaved to within all but five degrees of their maximum position. If this stripping of oscillator and antenna coils, which is done in steps of two or three turns at a time, is carried out, it is possible to extend the range of the receiver down so that it will actually go a little below 200 meters. In stripping the coils, only the enamel wire winding at the top end of the stator forms should be touched, the rotors and slot windings being O.K. Generally 10 turns may be removed from the antenna and 25 turns from the oscillator coil.

The receiver will, of course, cover other than the regular broadcast wavelength range, a pair of HIR colds allowing it to pair of HIR colds covering the range of about 30 to 90 meters. Two type 111D colds will cover the range of 500 to 1,000 meters will cover the range of 500 to 1,000 meters will cover the range of 500 to 1,000 meters will cover the set to the range of 500 to 1,000 meters. Will allow the set to tune up to about 3,000 meters. All of these colds are interchanged by large in types fitting the standard cold about 1,000 meters.

For short wavelengths a three-tube regenerative receiver will generally give entire satisfactory results, or even for medium range broadcast reception. It is a simple matter to add a three-contact switch, with all contacts insulated from the frame, on the front panel of the receiver under the detector stage assembly. The lead from post P on the left end of the intermediate amplifier to the R.F. choke coil (L3) should be broken, and the wire from the choke coil led to the blade of the switch. One contact to the switch should go to post P on the left of the intermediate amplifier and the other contact should connect to post P on the right of the intermediate amplifier. The switch then serves to throw the output of the regenerative first detector either directly into the audio amplifier or into the intermediate amplifier. Naturally, when the detector output is connected directly to the audio amplifier, the oscillator tube and all tubes in the intermediate amplifier are unused and may be turned out by an extra pair of contacts on the throw-over switch; or the tubes may be removed from the set,

If any difficulty is experienced in getting the set to function properly in the matter of sensitivity, selectivity, or tone quality, the change above suggested should be made and the lead from the choke (L3) connected directly to terminal P on the right end of the I.F. amplifier. The set should then be operated as a three-tube regenerator, and the results carefully observed, in order that the operator may familiarize himself with the operation of the first detector circuit and the nature of the regeneration control of the "Sensitivity" knob. Naturally, when the intermediate amplifier is added to the circuit, volume, sensitivity and selectivity should increase very much and the oscillator dial would then come into play. In tuning, the oscillator dial should be extremely sharp, requiring only a degree or two at the outside to eliminate practically any station, local or distant. The antenna dial will be broad comparatively, local stations covering as much as 20 to 30 degrees of the Antenna dial when it is rotated alone, and out-oftown stations from 5 to 10 degrees or more.

The real test of the receiver's performance, however, is a comparion against any other standard set—the server-ngrid "Labo-most exceeding the server of the

#### 2LO Calling

(Continued from page 1002)

it possible to supply almost any kind of musical program.

nusical program.

You will notice that this set fulfills all
the conditions set forth at the beginning of
this article. I guarantee it to pull in easily

any station on the earth.



How the microphone is connected in the input circuit of the A.F. amplifier of a receiver.

#### "Scare-Speakers"

R ECENTLY Ranto News described a device for pickling up the conversation of birds. The system is verecent by a Dutch farmer who has installed loud speakers in his orchards, to frighten birds away from the fruit trees. If this method is adopted in England, unkindly suggests a British paper, "a use will be found for those educational talks which we hear so much about."



# Four New Kit Panels!

Bremer Tully Power Six Electric; Karas A-C Equamatic; Karas Knickerboker Four and Tyman "70" front and sub panels are recent additions to the Formica line. There are also available panels for battery sets of the same makes and the World's Record Ten; H. F. L. Nine-In-Line; Magnaformer front and sub panels; Madison-Moore; Melo-Heald; Camfield Nine and many others.

Special panels cut to any size and tubing and rods, etc., is also available for amateur use

THE FORMICA INSULATION COMPANY
4618 SPRING GROVE AVENUE CINCINNATI, OHIO

Any jobber or dealer can get Formica Panels for you



Formica has a Complete Insulating Service for Manufacturers



HAMMARLUND "Midline"

CONDENSER

Soldered brass plates with tie-bars warpless aluminum alloy frame; belbearings; bronze elecle-spring pigtall full-floating, removable rofor abat permits direct tandem compling to other condensers. Made in all stand

Write for Folder
HAMMARLUND MFG. CO.
424-438 W. 33rd St., New York
Canadian Representative

WHITE RADIO COMPANY, Ltd.
41 West Ave. N. Hamilton, Ont.



#### Hammarlund Accuracy Assured

Michael Augelo, the great artist, once said, "Genius consists in the capacity for taking infinite pains." While we are too modest to claim that Hammarland Products are the result of genius, we do insist that they have attained leadership because we fale the point to make them Allow is shown how accurate alignment of Hammarland Condenser plates is assured—firmly anchored in a metal holder, each plate in its own alot, while the thebars and

For Better Radio

PRODUCTS

For Our 32 Page

Radio Instrument Catalog
No. 15-C
EWELL ELECTRICAL INSTRUMENT CO.

#### C. L. PARKER

Ex-Examiner U. S. Patent Office Attorney-at-Law and Solicitor of Patents McGill Building, Washington, D. C. Patent, Trade Mark and Copyright Law



#### TRUVOLT RESISTANCES

IN BUILDING ELIMINATORS AND BOWER CETS

- 1. Unit develops less heat, due to greater radiation surface. This assures long life, with non-
- varying accuracy. 3. Choice of radio designers and
- 4. Made entirely of copper-nickel alloy resistance wire—the finest
- 5. Especially adapted to power devices and electrified sets.
- A full line of Variable, Fixed and Tapped Wire Wound Residances for all radio purposes

Write for complete Free Truvolt Resistance Circular Dept. 12-E, 175 Varick Street, New York, N. Y.

#### YOU CAN SUCCEED IN RADIO-HE DID! Scores of young men like him are

now our grad-uates. There is a constant demand for radio operators. Our course qualifies you in a short time for a splendid, well paying position. Write today for free booklet on our Radio

West Side Y. M. C. A. Radio Institute 319 West 57th St., New York, N. Y.







VERYTHING IN RADIO

# Radio Wrinkles

Final \$50 Prize Award

#### FIRST PRIZE

A Home-Made Loud-Speaker Unit for a Cone

By Oren E. Staubrough

THIS loud-speaker unit may be built almost without cost by the mechanically-inclined radio amateur. It will operate a 36-inch cone-type loud speaker very satisfactorily, and most of the parts required may be found in an experimenter's junk box. All that is needed are a Ford spark coil, a magnet from a Ford magneto, a small bobbin from a buzzer, a piece of soft iron 10 x 3/4 x 1/8 inches, a piece of thin flexible iron 21/4 x 1/32 inches, a brass driving rod, nuts and screws.

In the construction of the unit the first





Two drawings showing complete mechanical de-tails of home-made speaker unit.

step is to break the magnet in two pieces and discard one half. Next, take the half which is to be used in building the speaker unit and determine the north and south poles with a pocket compass. This magnet is  $4\frac{1}{2} \times \frac{3}{4} \times \frac{7}{16}$  inches.

The 10-inch length of soft iron must be cut into three pieces with a hack saw. The first section is 4% inches in length and this is formed as illustrated at B (Fig. 1); the second section is 11/2 inches long and is formed as shown at C; and the third section is used as a mounting bracket for the unit. The last section may be formed after the construction has been completed, and the design which should be followed is shown at G. Winding the loud-speaker coil is the next

problem to consider. Take a bobbin, similar to the one illustrated at E (Fig. 1) and wind it with wire removed from the secondary winding of a Ford spark coil.
As much wire as possible should be placed on the bobbin.

After the directions given in the above paragraphs have been followed out the various parts have been prepared and the unit may be assembled. In Fig. 2 the mechanical details of the completed unit are shown. As the magnet is hard and cannot

#### PRIZE WINNERS

FIRST PRIZE \$25 A Home-Made Loud-Speaker Unit for a Cone By OREN E. STAUBROUGH 2845 Shiver Avenue Indianapolis, Ind.

SECOND PRIZE \$15

Four Jacks and a Tube Base Make a Novel Tester By T. WESTON BROWN Box 122, Carencro, Iowa THIRD PRIZE \$10 How to Build a Simple

Inexpensive Tester By C. W. MAC ELROY 4306 Horrocks Street, Philadelphia, Penn.

This marks the final prize award for Radio Wrinkles. In the future all Wrinkles which are received will be given the same consideration as other articles submitted to this magazine. Wrinkles which are pub-lished in future issues will be paid for at regular stace rates.

be drilled, the various parts must be soldered in place. The 21/4-inch piece of flexible iron strip (A) serves as the armature and is fastened to section B as illustrated Also holes must be drilled in A and B for the adjustment screw D. Now proceed by soldering the various parts to the magnet and the driving rod (F) to the armature. After the speaker unit has been completed it may be connected to a cone in the usual manner; and the two wires from the coil connected to the output binding posts of the set. In order to adjust the speaker, the air gap between the armature and the pole-piece of the coil is changed 4%-



until best results are obtained. This is


accomplished by running the two nuts on the adjustment screw up and down,

#### SECOND PRIZE

Four Jacks and Tube Base Make Novel Tester Bu. T. Weston Brown

THE circuit tester which will be found illustrated here is very interesting and quite useful. It enables the experimenter to test various parts of the circuit, under actual operating conditions, in a very simple manner and without the necessity of making any changes in the wiring of the set. The tester is capable of detecting many faults in a receiver and is also particularly helpful in determining the particular part of the circuit where trouble exists.

To use the tester, a tube is removed from its socket and the tester is subtituted. The vacuum tube is then inserted in the "socketter" on the top of the tester and the receiver is placed in operation. The voltage or current of the various circuits may now be measured by plugging meters into the jacks on the panel of the tester. To determine in 0-though the place of the tester. To deternant in 0-though the place of the tester in 0-though the place of the tester serted in the topmost jack. The jack second from the top is for measuring the plate voltage, and the meter which is connected

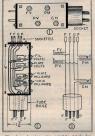

The above drawings give complete details for building and wiring this novel circuit-testing device.

in this position should have a range from 0 to 150 volts. The two lower jacks are for measuring the plate and grid currents of the tuber the same meter may be used for making both of these readings and should be a milliammeter having a range of 0 to 25. The third jack from the top from the top for grid current, and the fourth from the top for grid current.

The construction of the tester is very simple and only a few inexpensive parts are required. The four jacks used are of the midget variety, the two for the volneters are of the single-tested by parts to the construction of the construction of the construction of the control of the construction of the control of the construction of the control of the c

The details of assembly are clearly illustrated in the two drawings, and the wiring is shown in the schematic diagram. Although it is impossible to show this in the
pictures the wires from the plate and grid terminals should be separated as far as a possible. For the wiring, either flexible
wire or bus has may be used; but either should be well insulated to prevent possible short circuits.





CURTAN MFG. COMPANY

Dept. 827-C 154 E. Erie St., Chicago, III.

HOME FURNISHINGS FREE
ON CREDIT - Catalog Free
Over 1400 hospatin in bridge room, didning room, and bedroom 1400 hospatin in Bridge room, graf to pay, 30 days
trial, Write today for free catalog, sur to pay, 30 days
trial, Write today for free catalog, sur to pay, 30 days
STRAUS & SCHRAM Dept, 3573 Chicage, Illinois



# at the crossroads

# Scientific Fact Radio Activity **Inventive Thought** Experiment

everything of note in a matter-of-fact manner

SCIENCE AND INVENTION—at the crossroads of the nation! the crossroads of the nation! Everything of interest and of scientific - Science, Invention,

Chemistry, Astronomy, Electricity, etc. The selected topics in Science and Invention are treated in a nontechnical manner, giving them an everyday appearance and an understanding for all

What is more, a year's subscription to Science and Invention will mean 12 volumes chock full of interesting topics, valuable information, helps for the home and business, and many hours of entertainment.

SCIENCE AND INVENTION A Preview of Modern Scientific Endeavor

on all newsstands 100 pages or more in each issue

If your news dealer has none on hand, the little time spent in writing directly to us will be well rewarded.

EXPERIMENTER PUB. CO. 230 Fifth Avenue New York City

The above paragraphs give general details for operating the tester but the experimenter will, no doubt, discover many different ways in which the unit may be employed to answer his particular requirements.

#### THIRD PRIZE How to Build a Simple. Inexpensive Tester By C. W. MacElroy

OTHER form of tester which is equally as valuable as the one described elsewhere in this department may be made from an old radio headset and a flashlight battery. This tester may be used in a thousand and one different ways, and will be found particularly useful when checking the wiring of circuits and when testing parts for open circuits or short circuits. Also, the tester may be used to advantage when tracing the wiring of a receiver.

The construction of this unit is clearly explained in the drawings and does not re-



A headphone and flashlight battery are the only parts required for building this unit.

quire an elaborate description here. Only one phone is required in the head set and, if two phones are available, one should be removed and a felt pad substituted to protect the ear from the metal of the head set. The battery used is a small flashlight unit of 3 to 41/2 volts, and is fastened to the head set in the position shown with friction tape. The wiring is equally simple and is shown in the wiring diagram. The phone unit and the battery are connected in series and one wire from each is used as a test point.

The advantage of this tester over other designs is that it is entirely self-contained. The battery and the phone are in one unit and this avoids the necessity of having the wiring of the tester unit on the table.


The operation of the tester is very simple and requires but little explanation. The tester indicates when there is a complete conductive circuit between the test points by a click in the phone unit, and the intensity of the click is determined by the resistance of the circuit. Therefore, when testing an instrument, if the test points are touched to two terminals and a click is beard it indicates that there is a connection between the two posts; but if no noise is heard there is an open circuit. Also, in testing a receiver it is possible to locate all parts of the circuit which are connected with the ground by attaching one test point to the ground binding post and touching the other point to all other terminals in

It is often possible to make other tests by comparing the intensity of the sound. For example, when testing an audio-frequency transformer the test points should be touched to the various posts until the two pairs of terminals which connect with the windings are located. It is now possible to determine which pair of terminals connect with the primary winding and which pair connects with the secondary. As the primary winding of the transformer has a much lower resistance than the secondary, the click will be much louder when the test tips are touched to the terminals of this winding.
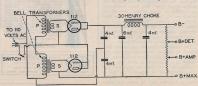
#### A Power-Tube "B" Unit Without a Step-Up Transformer

THE expense of constructing a plate ("B") power unit may be greatly reduced by making use of the circuit arrangement illustrated on this page and, if certain precautions are taken, the system will be found entirely satisfactory and safe. The usual step-up power transformer, which is one of the most expensive items of the average power unit, has been eliminated by using two rectifier tubes in a voltage doubling circuit arrangement. The power from the 110-volt lighting circuit is connected directly to the rectifier tubes, and it is rectified and doubled simultaneously. In this way it is possible to obtain ample power for the efficient operation of receivers using 171-type power tubes in the last audio stage

The complete circuit of the power unit will be found in the illustration. Two standard bell-ringing transformers may be obtained for a small amount from any electrical store. The rectifier tubes are two receiving tubes of the 112 type which are converted into two-element rectifiers by connecting the grid and plate terminals to-



When using this voltage-doubling circuit in a "B" power unit, a step-up transformer is not required

gether. The two 4-mf. condensers con nected in series across the high voltage are the voltage-doubling condensers, and the remaining 6-mf. and 4-mf. condensers are in the filter circuit. All of the condensers used in the unit should be rated for operation at 400 volts. The 30-henry choke is a standard filter-choke coil and the voltagedividing resistor is also of the usual design.

In operation, the rectifier tubes charge each of the two 4-mf. condensers individually at the peak of the A.C. voltage, which is approximately 155 volts. Therefore, as the condensers discharge, the power pack has an output voltage of about 310 volts at no load. Of course this voltage decreases when a set is connected; but this device will usually deliver 180 volts to a 5- or 6-tube set using a 171-type power tube.

When operating a receiver in connection with this power unit, it is necessary to disconnect the ground wire. This is very important, as one side of the A.C. circuit is grounded and, if the set were also connected to the ground, a short circuit might

Contributed by J. R. Balsley.

#### The Knowles Screen-Grid Four

(Continued from page 1030)

regult


the terminal. To prevent any coupling through the common battery, or through the battery leads, a radio-frequency choke

and a by-pass condenser are used. Because of the high plate impedance of the 222-type tube it is important to use a coupling device of high impedance. This is most readily obtainable, without the use of a special coil, by using a tuned circuit such as recommended by the manufacturer of the tube. In some cases a transformer with a 1:1 ratio has been recommended, but this has no particular advantage where the coupling device is used immediately ahead of the detector tube. When such a transformer gives perfect coupling between the primary and secondary, it is similar to the tuned-impedance stage. When increased selectivity is obtained, it is due to looser coupling or to the omission of the grid leak; and this cannot be omitted in the detector stage without making the detector itself much less efficient.

This circuit normally tunes very broadly This is due partly to the fact that the grid leak is connected across the tuned circuit; but principally to the fact that the 201Atype tube must be operated with a positive bias on the grid to secure efficient rectification in the grid circuit (that is, with a condenser-leak arrangement). This positive bias is obtained by connecting the leak (R3) to the positive A filament terminal. Under these conditions the grid attracts electrons and this greatly decreases the grid-to-filament resistance, resulting in loss of sensitivity and selectivity.
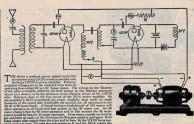
#### EFFECT OF REGENERATION

To insure good quality reproduction the radio-frequency circuits need not pass more than about ten kilocycles. When the tuned circuit "looks into" the detector, the band it will pass depends on the frequency but is from 30 to 60 kilocycles wide; indicating that it contributes little or nothing to the selectivity. Furthermore what is known as the "dynamic" resistance of the circuit



#### ELECTRIC SPECIALTY COMPANY

211 South Street Stamford, Conn., U.S.A.

# Spend the Winter in MIAMI, FLORIDA

Take the time away from the chilling cold and give your family a comfortable winter where every outdoor recreation may be had, including ocean bathing

You can live for less here than at home-stop at

HOTEL

Write for our illustrated booklet and rates H H Mase Proprietor

GRALYNN

A beautiful hotel conducted upon both the American and European Plans Summer Resorts

Churchill Hall and Rexmere Club Stamford, N. Y. Open May to November



have not built or played with a new circuit in three years unless you have built the

cuit employing nine tubes. World's latest-

WANTED

POTTER PRODUCTS CORP 245 Fifth Avenue, New York City



parts modified. Simply connect a few wires. No spect to the control of the contro

ir. Pienty of volume, The set sure is a dandy," B. J. Gillis, Dewrer, Colo. Toleram from M. A., Syracuse, Silms, Lewrer, Colo. Toleram from M. A., Syracuse, Silms-LE Wirling DIRECTIONS

Very easy to wire this set with the instructions we furnish. Just connect a few wires, All you have to do is made to be a set of the 
#### SEND NO MONEY

ask us to send you this great outfit together with as these. We will ship them right away. When they arrive, pay only \$16.65, plus a small delivery charps. (Previge constries and \$15.00 with evder. We pay shipping charpes.)

RADIO COUPMENT CO.

549 S. Wells St. CHICAGO, ILL.

549 S. Wells St. CHICAGO, ILL.



For automatically switching on and off your B Eliminator and Charger, or either, and in addition, automatically switching off your Charger when the battery is fully charged.

With the Full Automatic Voltage Relay it is now practical to utilize the advantages of a high rate charger and at the same time control the switching of the charger as well as the B Eliminator with the switch or filament control on the set.

No. 440

Yaxley Mfg. Co.

Dept. N, 9 So. Clinton Street Chicago, Ill.

RADIO PANELS
BAKELITE—HARD RUBBER

ust, drilled, and engraved to order. Send rough
ketch for estimate. Our Complete Catalog on
anels. Tubes and Rods—all of genuine Baketie or Hard Rubber—usualed on require.

STARRETT MFG. CO.
520 S. GREEN STREET - - CHICAGO

# 

The shield-top of the R.F. amplifier stage removed, with the pencil indicating the top terminal of the screen-grid tube.

is decreased to such a low value that the
222-type tube gives only moderate ampli-

To offset these effects regeneration has been used. The effect of regeneration is to decrease the losses in the circuit or to to decrease the losses in the circuit or to to decrease the moderation it growths merely in bringing this stage up To par, without impairing the quality. In other words, sufficiently and to have the circuit passes to approximately 10 kilocycles. The adjustment is more proposed to the control of the circuit passes to approximately 10 kilocycles. The adjustment is until the decrease no approximately distortion.

When the radio-frequency stages are adjusted so they do not discriminate against the higher audio frequencies, then the problem of good reproduction rests with the audio-frequency amplifier and speaker. A high quality audio-frequency amplifier has been used together with an output transformer, which makes it possible to use the 171- or 1714-type tube in the last stage.

#### CONSTRUCTION

The receiver may very easily be constructed by following the instrument layout and schematic wiring diagrams. The
location of the parts should follow the layout shown on page 1028. In the pictorial
wiring diagram the location of the parts has
been altreed slightly to make the wiring
easier to follow.

A few general precautions will permit the constructor to duplicate the receiver quite easily. If three hours are available in which to assemble the receiver, one of them will be well spent in considering the sequence that is to be followed in the assembly, and in becoming familiar with the various parts and leads. Partially assemble the two shields by

helding the sides together and foreing the corner pieces down about half way. Place the bottom of the shield in what seems to be the proper position and then hold the assembled side walls immediately over it. The shields should be so placed that they are next to the panel and their sides clear the couplings on the drum dial by about

After all the necessary holes are drilled in the panel and drum-dial sides of the shields, these may be securely fastened to the baseboard with the bottom piece in place. An ice piec or similar tool may be used very conveniently to locate the serew holes and to start the wood screws.

Mount the rheostat RI and the variable midget condenser C3 on the panel. The shafts of these two instruments are at shield (ground) potential so they should not be insulated. Solder an 18-inch piece of wire to the "P" terminal of socket VI and another to the "F-" kerminal. These two leads go through the side of the left-hand shield, next to the drum dial. Thread them through the holes provided and mount the socket in the position shown.

#### TUNING-CONTROL MOUNTING

Details for aligning the variable condensers are given in the instructions with the drum dial so they need not be repeated. The condenser CI should be so mounted that its stator plates clear the side of the rheostat RI by about 3/j6-inch. The condenser C2 should be mounted so the frame is ½-inch from the side of the shield.

The location of C2 is quite important, since its frame and rotor plates must be insulated from the shield. They are connected to the "24-49" lead. They are connected to the "24-49" lead. The frame received the shield property of 
be made from its frame to the shield by using a battery with a voltmeter, head-set or speaker. There should be no "click" or deflection of the voltmeter. The sockets and by-pass condensers may

then be mounted. A long lead should be soldered to one terminal of the choke L3. This should be threaded through the hole in the shield, after which the two mounting



screws may be inserted. The two machine screws on the soldering lugs should be removed, to prevent the possibility of one's touching the shield bottom.

#### RUNNING THE LEADS

Flatike rubber-covered wire is used throughout for the wiring. This together with the use of "beef" or direct-line wiring and cabled battery lends, make the wiring very simple. Long lends should be soldered to the state of the

The wiring should progress with a view to completing the coil connections just before the shield is to be assembled. No parts are mounted on the rear side of the shields and these may be added after all the connections have been made. This makes it possible to solder the leads to the coils and other parts more easily.

After the wiring in both salichted computents has been completed the three A.F. transformers (Tt., T2 and T3), the A.F. transformers (Tt., T2 and T3), the profits (A.A. And A3) should be mounted. The ferf-hand shield should have five long perities (A.A. And A3) should be mounted. The ferf-hand shield should have free long perities, (A.A. and A3) should be mounted from the ferf-hand shield should be should be shield as been been founded by the shield should be shield as a ferf-hand shield 
The right-hand shield should have the following external leads: one from the stator plates of condenser C3 to the choke L4; "A.F" battery lead, while goes to A1 (to the right-hand side of the detector to the choke L5 to the whole the choke L5 to the yellow bernald on the cable can be the whole L5 to the yellow bernald on the cable call of the yellow bernald on the cable and the which goes across to the other shield and connects the stator plates of C2 with the "P" terminal of VI. After these leads have been checked, the

audio-frequency amplifier may be wired.

The bottom leads to the cable terminal should be wired first to simplify the soldering.

There is ample room on the baseboard

to permit the use of any type of audiofrequency amplification. If the constructor prefers push-pull amplification a pair of push-pull transformers may be substituted for T2 and T3, and another socket and amperite added.

The amperite used in the last stage will depend on the power tube. The 1A type should be used for all ½-ampere and the 112 type for all ½-ampere tubes.

#### OPERATION

To place the receiver in operation, connect the two "A" battery leads to the cable. Insert the 222-type tube in V1, 201A tubes in V2 and V3 (unless a special detector is used in V2), and the power tube in V4. The filament switch (R1-Sw) should break the connection to all the filaments and

#### A. C. OPERATION!



THE Type 440-A Transformer illustrated is designed for use on 105-125 V. (50-60 cycle) A., and is rated at 65 watts. The following voltages and currents are available:


Price-\$10.00

The use of this transformer, together with the new A. C. tubes, and a dependable plate supply unit such as the General Radio type 445 Plate Supply and Grid Bias Unit, makes the conversion of a battery-operated rever into one operated from the light socket very simple. If you do not care to undertake this change yourself, go to your community set builder. He is well qualified to serve you.

#### GENERAL RADIO CO.

30 STATE STREET

CAMBRIDGE, MASS.

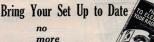

more batteries

THE set owner can now electrify his own set—in a most economical way. Do it yourself! This book will show you how!

## HOW TO ELECTRIFY YOUR RADIO SET

Good, clear, understandable English, with detailed instructions to build the climinator. It discusses the first principles of wave rectification; gives reasons why the electric set is coming to stay; and specifies parts necessary to construct the climinator. Many illustrations showing various eliminators and parts.

Splendid two-color cover—6 x 9 inches.

Get it from the newsstand, or write direct
CONSRAD CO., INC., 230 Fifth Avenue, New York City

# LEARN THE CODE AT HOME



Send &c for Catalog.

THE OMNIGRAPH MFG. CO. 1

THE OMNIGRAPH Automatic Transmitter with the both the Wireless and More Coderight in your own bome—quickly, easily and the pensivery. Connected with Buzzer, huzer an Phone or to Sounder, it will send you unlimite mossages at any speed, from 5 to 50 words mittate THE OMNIGRAPH is not as experiment. For mothan 18 years it has been cold all over the worl

nity adopted by the leading Universities, Colleges and Radio Schools.

Do IT TODAY.

15 HUDSON STREET, NEW YORK CITY

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year Experimenter Publishing Co., 230 Fifth Avenue, N. Y. C.

# Gonner Gabinets

Entire factory stock of Conner Conven-



25%
REDUCTION
Prices NOW
\$26.25 to \$74.75

\$26.25 to \$74.75
Jacobean, Renaissance and Sheraton designs, done in beautifully high-lighted walnut and mahogany. Fronts open down into convenient deaks. Write today for illustrations.

A Conner Cabinet assembles every detail of your receiving set, batteries and accessories, in a scientifically convenient arrangement and encloses everything in an exceptionally beautiful piece of period furniture. You can secure one at this emergency bargain price if you act quickly. Write today for illustrations and details.

CONNER RADIO CABINET CO.
New Albany, Indiana

should control the brilliancy of the 222-typetube. If the rhocotat seems to work satisfactorily complete the battery connections. The small initial space of the blue and yellow leads is due to the current which charges the by-pass condensers. There should be no second spark when it is disconnected and onickly reconnected.

All of the cable markers are correct except that on the yellow lead. This lead should be connected to the "B+90" terminal instead of the "B-."

Connect the aerial, ground and loud speaker and tune in a local station. If the aerial is quite long, the position of the primary of L1 should be adjusted by turning the primary screw (which protrudes through a small hole in the top of the shield) until the primary is near the top of the shield; that is, until the coupling is very loose. If a small indoor aerial is used, the primary should be adjusted so that it is near the secondary. If a very short wire, having a total length of not over 30 feet. is used the connection should be changed so that all of the primary, instead of half of it, is used. The adjustment of the primary will depend on the selectivity and sensitivity wanted. It may be adjusted, while listening to a station, until the desired selectivity is obtained on the lefthand drum

The right-hand drum will be found to tune broadly, for the reasons previously mentioned. To sharpen up this circuit, the regeneration control must be adjusted. Turn the potent of the midget condenser (GG) until the plates are fully meshed. GG to the plates are fully meshed. Set the foot great position may be downward, so that this position may be downward, so that this position may be determined after the shield top is replaced. Set both drums at 100 and adjust the regeneration or tickler coil, just as the primary coil was adjusted, until the set begins to make a hissing noise or otherwise

shows signs of oscillating.

When short-wave stations are tuned in it will be found that the capacity of the midget condenser must be decreased to stop oscillations.

The tuning is done as follows; more both disks, keeping them in the same relative positions and with about the same setting, when a statio · is found, tune the loft-hand drum, which should be quite sharp, until maximum intensity is found. This should be done with the volume control in the "on" position; that is, with no resistance

a local, the volume control may be turned to the left until the volume is moderate. Adjust the right-hand dial and gradually increase the capacity of the midget condenser C3 (make the plates intermesh more completely). It will be found that the setting of the drum must be changed slightly to secure maximum volume, and that the secure maximum volume, and that the tion control is turned too far, the quality becomes poor and there is a pieceing whistle

in the rheostat circuit. If the station is



This handy book should go with every Radio!

Battery Supply Co. upt. N, 227 N, Peeria St., Chicago, II

It is concerned with rac parts—their functions where they are — as their rames. It gives to aymbob used in rac hook-ups, so that y will be able to read a dagram and undeested it. It discusses air was —the sartil—then tally you through every rac part—and finally it actual reproduction.

AND DIO PARTS

will give you a full undersanding of your set. 255

ALL ABOUT RADIO PARTS

5½ x 7½ Inches, hilly illustrated
Get if frees may incustioned or direct

THE CONSRAD COMPANY, INC.
220 Fifth Avenue New York City

#### LIST OF PARTS

01,02 03 04,05	2				MANUFACTURER *
C3		Var. contensers	,00005 ad.	1	Million of the Control of the Contro
	1	Widget condensor	65 mf.	1	4,05,34,48,50,81
	2	Dy-pass contensors	0.5 mf. (paper insulation)	2	14,25,16,17,18,19,20,21,22
061	1	Ortil condessor	,00025 mf, (atem insulation)	. 3	2,7,15,16,17,18,19,20,23
11,72	2	A.T. transferners	3:1 ratio	4	3,5,20,24,25,76,27,28,29,
13	1	Output transformer	1:1 ratio ·	4	20,24,25,26,28,29
12.12	2	Coupling ceils	Auto-couple type	1	TO A SUPPLY OF THE PARTY OF
L3, L4	2	R.F. choke coils	85 millibenry	mo of	4,4,26
11.12	2	Imperites	5 volt, 1/4 envere type	6	
A3	1	Amperite	5 volt, 1/2 onrere type	. 6	
91-0e	1	Deltch-rhosatos	40 ehrs	7	16,17,45
12	1	Fixed resistor	15 ohrs	7	17,28,45
73	2	Ortid leek	E wagotra	18	2,10,15,16,18,19,20,23,34
1/2	1.	Veguue tube	222 type (egreen_grid tube)	9	32,35
72	1	Veguas tube	200A type	9	32,33,34
72	1	Vecuus tube	201A type	9	22,33,34
74	1	Version tube	171 type	9	32,33,34
7	1	Cable plug	T-wire type	7	36,37
51,52	2	Dinge shields	Dunteun	1	bur bishik ceda a
MONE F	1	Drum diel	Souble type	1.2	Collegible St. To.
	1	Leak mounting	Single type	10	15,16,15,19,20,23,34,44
10200	3	Binding posts		. 11	25,43,44
4000 00	4	Sockete	UI type	12	4, 11,25,44,45,45,47,49,49
1000	1	Pront panel	7 x 21 x 1/2 tories	18	40,43,42
200	2	Terminal strip	3 x 3/4 x 1/6 inches	23	40,41,42
CO AAN	1	Baseboard	Total		
		Yookaus wire	Insulated	24	35.30.39

NUMBERS IN LAST COLUMN REFER TO CODE NUMBERS BELOW

Tractes Mendicatacina Chinece I Arbar E. Inchny, Incorporated I Minarta Fahrinatura, Incorporated I Minarta Fahrinatura Company (I Agreem 1987). The Company (I Agreem 1987) and the Company (

1 Date on Vertical Company

1 Date of Refered a Community

1 Interest and Design and Company

1 Date of Refered and Design and Company

2 Date of Refered and Company

2 Date of Refered and Company

3 Hoseand Design Company

3 Hoseand Design Company

5 Dates Technic Company

5 Dates Technic Company

6 Dates Design of Demotics

6 Company Demotics

6 Company Design of Demotics

6 Company Demotics

7 Company Demotics

7 Company Demotics

i Benismin Flectric Mfg.
Dubliler Condenser Carris
Richtes, Incorporated
Flectres, Incorporated
Februarity Incorporated
Februarity Incorporated
Februarity Incorporated
Februarity Compley
Jeffersen Electric Mfg.
Jo. F. Memifesturing Con
Folian Februarity Compley
Folian Februarity Con
Folian Enthalters A. D.
Folian Ent

C. E. Manufesturing Co. (Celt) beldes Naminstaring Company beldes Naminstaring Company belless Satishierd & Duryly Co Hanned State Piber Company berbert H. Front, Incorparated hard & Thomson Manufesturing Co Precise Naminstaring Corporati

\*THE FIGURES IN THE FIRST COLUMN OF MANUFACTURERS INDICATE THE MAKERS OF THE PARTS USED IN THE ORIGINAL EQUIPMENT DESCRIBED HERE.

If you use alternate parts instead of those listed in the first column of manufacturers, be excelled to allow for any possible difference in nice from the originally used in laying out and deliling the panel and sub-base.

which varies in frequency as the drum is rotated. At some intermediate position good volume may be secured without any loss in the quality of the reproduction.

The selectivity of the detector circuit, in all stabe iceruit arrangements, scena particularly poor because no other tuning control is operated from the same drum. If another tuned circuit were operated from the same control and sharply tuned, the "apparent" selectivity would be much better; although the actual selectivity might be the same. The important measure of selectivity is the distance to wold and the selectivity in the distance of the control of the selectivity.

of the over-all selectivity.

In this receiver the over-all sensitivity
and selectivity are quite high and both may
be controlled largely by the regeneration
control. In adjusting the receiver both
control should be rotated together, before
judging that the selectivity is inadequate.
If it must be increased, either more regeneration may be used or the aerial coupling may be decreased as explained before.

Both the selectivity and the sensitivity may be increased when this is necessary by employing the 200A-type detector tube; this may be used with an "A—" return or with the filament end of the leak connected to this terminal. This greatly increases the grid-to-filament resistance of the detector tube and results in sharper tuning and increased sensitivity.

#### The All-Electric Everyman Four

(Continued from page 1026)

where the reception of weak signals is seriously affected. The employment of 297type tubes in the R.F. detector and first audio stages is the most certain method of forestalling this trouble. As the diagram indicates, and as most radio experimenters know, the 227-type has a five-prong base, thus requiring a special socket to correspond.

The standard 171-type power tube is recommended for the last audio stage; although a 122-type semi-power tube may be substituted, with very satisfactory results, if the "B" supply of the builder does not give the desired 180 voits for the first mentioned tube. Although the operation of these new A.C.

takes may not be theroughly understoothold by the average radio builder, there is nothing about them that need cause uncertainty. The girth and plates are connected in the cathode connection is brought out through the socket in the usual way and creating the socket in the usual way and creating the leads connect through the low-resistance leads connect through the low-resistance values terminals of the step-down transformer. But these filament leads must be braided, throughout their length, in order to keep the lima at the lowest value.

In a set as simple as the "Everyman Four" it is not necessary to describe the wiring step by step. The pictorial diagram shows all connections, and if these are made in the proper order the completed receiver must of necessity function properly.



# 90 Volt Power Unit :: \$12.75



Hums, line noises, etc., positively impossible with this new advanced unit. Plun in and forget. Nonacid and noiseless. All detector and intermediate voltages plainly marked. Simpler to look, up the voltages plainly marked. Simpler to look, up the Greater volume and charmes guaranteed. If not theoremie Greater volume and charmes guaranteed. If not theoremie Contact volume and charmes guaranteed. If not theoremie Greater volume and charmes guaranteed. If not the court of the contact of the contact of the contact of the day of the contact of the contact of the contact of the day of the contact of the contact of the contact of the day of the contact of the contact of the contact of the day of the contact of the contact of the contact of the day of the contact of the contact of the contact of the day of the contact of the contact of the contact of the contact of the day of the contact of the contact of the contact of the contact of the day of the contact of the contact of the contact of the contact of the day of the contact of the contact of the contact of the contact of the day of the contact of the c

#### B. HAWLEY SMITH

34 Washington Ave. Danbury, Conn., U. S. A.

NOW-

OW

A Single Drum Dial by National Company with 360 degree Rotation easy attachment and, the Velvet Vernier Quality.—Just ask your dealer for

NATIONAL

TYPE SD ILLUMINATED VELVET VERNIER DIAL NATIONAL COMPANY, Inc., Malden, Mass

NATIONAL COMPANY, Inc., Malden, Mass W. A READY, President

Conis

"Best I ever heard"
Is what you'll say.
land up. Will not burn out.
lous tone and volume. Fully
teed. Easy to mount.
HING TO IT—BUT THE
Unit NEQUALED
Unit Stags
Come Disc. 54.95

Or complete. \$6.9!
For 45 in. Floor Stand add., 1.8i
Beaters Write
FRANK W. WOOD
2100 Gale St., Indianapolis, Ind.
New York
46 Cortlandt St.

New York


6 Cortlandt St.

Chicago

416 S. State St.



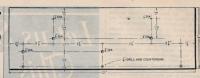The rest instruction excelsed, upon the control of 
ELKAY EQUALIZORS



Drilling details of the front of the All-Electric Everyman Four.

the circuit itself. Attach the aerial post to an aerial at least 90 feet long; one of 1295-foot length should be even better. Use the customary ground connection, with care that it is a good one. Attach the "P" power unit to the proper terminals. Do the same with the "C" battery tops. Flug the AC.

transformer into a nearby light socket and turn up the two rheostats about half way. The tubes will light dimly and no sound will come from the speaker for about 45 seconds. Do not attempt to tune in a station for at least this length of time. A low hum coming from the speaker will first

#### LIST OF PARTS

SYMBOL	Country	NAME OF PART	REMARKS	15	MANUFACTURER *
11	1	Interna empler	Veriable primary (special)	1	
1.2	1	Plate coil	Tapped (apected)	1	
1.3	1	R.T. choke coil		1 2	3,4,10,11
71	1	A.T. Special order	First stops type		4,30,11,12,13,14,15,16,17,38
T?	1	A.F. transformer	Second store type	2	4,20,11,17,17,14,15,16,17,16
9	1	Output filter	Choke renderser type		19,10,19
04	1	Seutralising ours.	15 - 25 mf,	2	3,30
CS.	1	Tixed contensor	,00025 mf.	2	18,81,22,22,24,25,76,27,75,1
05,07	2	Epupass contensors	.5 mf.	2	24,25,26,07,28,29,30,31,32
75	1	Orid lesk	3 merchan	2	19,22,24,25,26,20,29,32,31,1
	2	Orid lerk nount			19,22,24,28,29,14,35
C1,C2	2	Variable contensors	.0005 mf.		4,0,20,11,18,13,19,36,37,38
C3	1	Widget condenser	11 plates, 50 mef.	1 2	4,11,87
R2	2	Mecetet	1/2 ohn		23,27,29
R2	2	Rhesetet	1-1/2 etms	4	23,27,29
82.34	2	Potentioneters	200 shoe		22,19,23,24,27,29,35,29
	1	Tube souket	UX type	4	4,11,17,19,35,89,40,41,42,41
	3	Tube sockets	Uf true		4,11,17,19,35,39,40,61,42,41
72,72,73	3	Yearsm tubes	%-227 1me		34,44,45
V4	1	Versus tube	171 tme		34,44,45
2	1	Ceble omneoter	1-vire		9,23
	1	Front penel	21 x 7 x 3/16 inches		46,47,40
10000	2	Terminal strip	3 x 1 x 3/16 inmes		46,47,40
	1	Decatet strip	27 x 10 x 2/16 inches		46,47,40
	2	Ternier dials	THE RESERVE TO SERVE THE PARTY OF THE PARTY		10,11,12,16,51,50
marin a	1	Sesobeard	Wood - 20 x 9 x 4 inshee	100	10,10,10
SO, ACRES	1	Connection wire	THE RESERVE TO SERVE THE PARTY OF THE PARTY	9	30,35,49,50
W.T.W.	2	Minding posts	THE RESERVE THE PERSON NAMED IN		4.19.20
-	1	Filament transfermer	2,5 volt and 5 volt secondaries		4,10,11,13,61
	1	*B* Peper unit	Sec. voltages: 22,34,67,90 and 180, Any	good 1	one made or menufactured unti-
5257	100	Hist cost our	may be used.		CHARLES STREET, SQUARE,
1 630	1002	non monute cont			CHARLES CO. ST. DOWNERS CO. CO.

NUMBERS IN

COLUMN REFER TO CODE NUMBERS BELOW.

J. Romann's Hern's Actuaring Compaby Barish S. J. Jones
D. Baiden Emminentaring Company
D. Baiden Hendielo Company
D. Parent Hendielo Company
D. Perranti, Incorparated
H. Herticol Research Lake, (Dittal
H. Berticol Research Lake, (Dittal
H. Barish Manufacturing Company
D. Charles Hedde Company
D. Anne Hire Company
D. Anne Hire Company
D. Anne Hire Company
D. Anne Hire Research Company
D. Company D. Company
D. Company D. Resid Observators
D. Company D. Company
D. Company D. Resid Observators
D. Residence D. Reside

Polymer Minimizaturing Company Enter Reido Occasive Size Bire Company International News. Co. (COMPANY) Damided Reido Mondardering Co. Orbert M. Pratt, Incorporated Minimization Products Company A. T. Caustingum, Incorporated Minimization Company The Minimization Company

\* THE FIGURES IN THE FIRST COLUMN OF MANUFACTURERS INDICATE THE MAKERS OF THE PART

If you use alternate parts intend of those listed in the first column of manufacturers, be careful to allow for any passible difference in size from those trun copyright, test is, that is, that is,

be noticed; but, as the tubes heat to their proper temperature, this hum will gradually disappear.

Finally, when the 45 seconds have clapsed, rotate the two tuning dials to approximately 50 on their scale. Set the antenna coils at maximum coupling (primary close up against the secondary). Now waggle the two condensers C1 and C2 simultaneously back and forth until a station is heard. If the station comes in with a squeal alter the setting of the neutralizing condenser C3, which is also the regeneration control. A point will finally be found at which the station will come in clear and loud. Retune slightly to get squarely on the station's wave, and regulate the volume by swiveling the antenna coupler. And, as a last bit of advice, turn the flaments of the A.C. tubes as low as possible without losing signal strength. This will help tremendously in getting your money's worth from the tubes

Since the filament of the power tube V4 also is worked direct from a transformer tap, it is necessary only to switch off the current from the light socket when the period of listening-in is over.

Once the proper heating temperature of the A.C. tubes has been worked out, through varying the two rheostats, it should not be necessary to touch them again. But, unfortunately, in some portions of the country the voltage on lighting lines varies within wide limits-particularly during those hours when many consumers are drawing on the power station for energy. If a distinct fading of all signals is noticed, this is a pretty certain sign that the voltage being supplied the tubes has dropped below a point where the heaters are sufficiently supplied. A slight touch on one or both rheostats then becomes essential.

#### An Emergency Repair of a Burnt-Out Transformer HE primaries of audio-frequency trans-

formers sometimes burn out when the plate circuit is opened suddenly. In cases like this, possibly the best method for repairing the damage is to obtain a new transformer and to be more careful in the future. However, if a variable high resistor, of approximately 500,000 ohms maximum, is connected across the primary terminals of the broken transformer, this stage may be converted into a resistance-coupled amplifier, and the set may be used in this manner until the new transformer is procured.





Engineer Dobe Div. 10-03 Chicago, Ill.

# Radio's Finest Book of Hookups

WHAT more could you ask?—150 of the very finest, selected hookups most popular today. Each one completely explained and fully illustrated so that a complete receiver can be constructed from the information. No out-of-date bookups-all the finest and best in common



use today. 64 pages, illustrated. Large size, 6 x 9 in. Don't miss this opportunity —All Radio and news dealers have fresh copies Now. If there is no dealer near you write us direct, enclosing 25c.

THE COPY

If your dealer cannot supply you, write direct

THE CONSRAD CO., INC., 230 Fifth Ave., New York City

#### Get Your Copy Now!



# Practical Radio Advice

for all!

Set Construction-The New Shielded LR4. The Loftin-White Constant-Coupled Receiver, The Radio News Batteryless Receiver, Superheterodynes, Neutrodynes, dozens of circuits of all sorts, with diagrams and complete instructions for building.

Construction of batteries

Construction of Loudspeakers— from ship model to 36-in. cone type.

The construction of anything in Radio-from dials to wave trapsthe most modern methods

Radio Helps of every sort, concerning every radio part-Trans-formers, Tubes, Shielding, Amplification, Alleviation of Static, How to Install Radio Equipment Permanently, etc., etc., etc.,

#### Radio News Amateurs' Handibook 116 pages-fully illustrated

It took Radio News to put this in-valuable Radio Book before the public. It contains a series of selected articles from Radio News, by the most eminent of Radio Experts.

25c

SOLD EVERYWHERE

If your dealer has none on hand write directly to

EXPERIMENTER PUB. CO., INC. 230 Fifth Avenue New York City

#### Australian Broadcast Stations

By Raymond M. Bell and E. R. Midelev

SINCE reception of the Australian broadcast stations has become possible in nearly all sections of the United States, interest in them has been aroused. One of the most interesting factors is the difference in time. The stations in Sydney and Melbourne are 15 hours ahead of our Eastern Standard Time. When it is 9 p. m. in Sydney, it is 6 a. m. the same day in New York. Although the Australian stations can be received any month in the year, March and October seem to be the best months. The stations of Australia are divided into

two classes; Class A stations receive revenue from the license fees charged all owners of receiving sets. Class B stations are not so favored. The list is as follows:

CLASS A CLASS B 3LO is the most popular Australian sta-

tion, with 2FC a very close second, and 2BL easily in third position. All other Class A are considered equal, with 5DN and 2UE the best of the B class. This is the approximate order of the stations as regards the service they give. 2BL and 3LO are very good on long distance. 2BL ap-pears to be received better in the United States and Canada, while 3LO is picked up better in Asia. In spite of this, 2FC holds the record, having been picked up in Labrador, and also in England on test. 4QG is good on long distance,

Crystal reception, still common in Australia, is good up to 200 miles from each station, depending on weather conditions and set. 2FC and 2BL commence broadcasting each morning at 7:00 a, m, and continue with a few breaks until 11:30 p. m. Other "A" stations commence at noon (local time). An Australian station rated at 5,000 watts has an output of about 2,500 watts (U. S. rating). During the past year Australian stations have relayed 2NM, PCJJ, 2XAD, 2XAF, WLW, 2LO, Berlin, Paris, and Daventry.

Among the stations received in Australia, besides New Zealand and United States, are: JOAK 375 meters, JOBK 385, JOCK 360, Japan; 7CA 370, 7BY 357, in India; and Radio-Manila KZRM 413.

Outstanding amateurs in Australia are 3BY, 38W, 3EF, 3BU, all in Melbourne, and 7UX, in Hobart. These experimenters broadcast on 200-300 meters.

The best New Zealand stations are:

1VA Auckland 2VA Wellington 3VA Christchurch 4VA Dunedin		420 3000 306 500
Wellington's 2YA	is a new s	tation. New
Zealand is about 1,5		
tralia, and is an hou	r and a h	alf earlier in

Adelaide is half an hour later in time than Eastern Australia; Perth is two hours later. All the other stations are, as stated, 15 hours ahead of New York's Eastern Standard Time.

#### A Good Position for the Volume Control

It is often found, when receiving sets incorporating power tubes are used for local recention, that the volume is excessive. The usual method to reduce this volume is to turn down the filament current on one or more of the tubes in the set; but, this sometimes produces distortion and unnatural tone. Possibly the simplest method for controlling the volume without harming the quality is the utilization of a fairly high resistor in the plate lead of the last R.F. tube. This method controls the volume effectively without introducing any noticeable distortion.



asic circuit employing nine tubes. World circuit—the SUPER-HILODYNE—radical

WANTED

.State.......RN-228

POTTER PRODUCTS CORP. 245 Fifth Avenue, New York City

#### The Pacent Distant-Signal Amplifier

(Continued from page 1033)

illustrations accompanying this article give

proof of the compactness and simplicity of the entire unit. Careful attention should be paid to the hook-up of the 222-type tube in the circuit, as well as to the layout of parts, and to small details such as the shield over this tube. The shield, incidentally, is essential as well as novel in form. It is required for two reasons: to allow of the speaker being placed in back of the amplifier; and to suppress the tendency of the tube to howl slightly. It further provides protection for the tube against shocks which might result

in the filament touching the inner grid and burning out. The shield consists of the lower part of a metal beverage shaker purchased at the ten-cent store. It serves the purpose admirably and costs only a dime. It is held in place over the 222-tube by means of short studs, secured to right-angle brackets fastened to the bakelite horizontal panel.

#### CONSTRUCTION OF AMPLIFIER

Lav out and mount the parts as shown in the illustration. Pay particular attention to the matter of battery voltages indicated in the schematic diagram. The bias on the 222-type tube is about 34 of a volt when about 27 volts is applied to the control grid. The control grid is the inmost one, which is brought out to the terminal on top of the tube; in this circuit it is used as a "space-charge" grid. (For detailed explanations of this function see pages 896 and 897 of Ranio News for February, and page 763 of Radio News for January.)

NAME OF PART

Shesetat

Ortd lead

Vacuum tube

4 Subter feet 1 Beverage shaker


Pecent Flectric Company
Tobe Deutschmann Company
E. E. Phy Namufacturing Company

At I medic Laboratories
Fart & Regemen Menuing Co.
C. F. Manufacturing Co. (LeCo)
Tyrone Flectic Congrey
Texter Manufacturing Company
Texter Manufacturing Company
Texter Manufacturing Company
Dobline Condense Corporation

Fixed contense Jacks

Orid leek clips Dub-tree panel

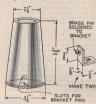This %-volt bias is secured by means of the potentiometer placed in the filament lead of the 222-type tube and connected as shown in the schematic diagram. A slight change is necessary in the 30-ohm rheostat



-SHIELD FOR TUBE VI~ DIMENSIONS SHOWN, ARE THOSE OF AN ALUMINUM BEVERAGE SHAKER, WHICH CAN BE PURCHASED

An aluminum shaker, such as that shown above, with two L-shaped slots, makes an excellent shield for the screen-grid tube.

(R1) to adapt it for use here. The arm is the separate connection and the two ends of the resistance strip have been brought out on separate screws, one of which leads

17,23,24,25,26

27,28,29,21

20,21

9 10,11,12,38

Rediall Company Sangeno Fleatric Company Jone Tire Corpory Asson Tire October & Dugsty Co.
Dissons Heat-Fiber & Dugsty Co.
Dissons Heat-Fiber Company
Assoc Probates, Incorporated
DataClaim This Dorporated
Forcast, Incorporated
Forcast, Incorporated
Forcast, Incorporated
Forcast, Incorporate
Points Memblacturing Co.
Asson Facility Company
John E. Bust & Depany
Deven Exits Company
Deven Exits Company

17,18,29,30,31,19,58

#### electrify your set the easy practical Knapp way ....



The Kit completely assembled with a metal cover in place. Operates on 105-120 volts AC. 50 to 60 cycles.

#### Knapp & Power KIT No expensive short lived AC Tubes, no

troublesome re-wiring, no annoying hum. Increase instead of decrease the efficiency Power gives you music instantly at the snap of a switch. This absolutely dry "A" Power is not in

This absolutely dry "A" Power is not in any way a battery combination ... not something to add to your battery ... it is the most efficient "A" Battery Eliminator ever designed. It supplies unfailing "A" current to any set using 201-A or 6 volt tubes, regardless of number.

Magic Silence

So silent is Knapp "A" Power, that you can place a pair of head phones directly across the output and not be able to detect This is made possible by the efficient Knapp filter system, consisting of 2 over sized chokes and 2 condensers of 1500 microfarads each. A new discovery makes these amazing capacities possible in the small space of 2x2x8 inches!

Absolutely Dry Absolutely Bry
There is not a drop of moisture in this absolutely dry
unit. The condensers are baked so that not a drop of
moisture remains. The unique, fully patented, solid,
full-wave rectifier is absolutely dry. No water mascied no alkali no tabes no electorytic
section. Nothing to get out of order. Nothing that

Assemble in Half an Hour

The Knnpp "A" Power Kit is ao casily assemble that within half as hours for you receive it, you have it in operation, have it in operation, have it in operation. Everyth supplied, even to the acrews, wire, drilled baselon and metal cover. It is no complete, that even a p is supplied no that a "B" Riminator may be operated in the complete of the com

Big Profits for

#### Set Builders

Our president, Mr. David W. Knasp, is offering the so builders of America, for a limited time cally, a mosey-axise, profit-making plan which is unique in the annais of radio. Send the coupon today, before it is too late.



**Knapp Electric Corporation** Port Chester, N. Y.

MR. DAVID W. KNAPP, Pres. napp Electric Corporation 3:1 Fox Island Road, Port Chester, N. Y.

Send me complete information regarding the Knapp

\* THE FIGURES IN THE FIRST COLUMN OF MANUFACTURERS INDICATE THE MAKERS OF THE PARTS USED IN THE ORIGINAL EQUIPMENT DESCRIBED HERE.

If you use absenue parts instead of those listed in the first column of manufacturers, he careful to allow for any possible difference in size from those prisonally used in larger out and drilling the panel and sub-base.

LIST OF PARTS

REMARKS (Connected as autoformer)

0.25 to 0.5 megolyns 5 volts, 1/2 supere

272 type (screen\_grid tube)

7 x 12 x 3/16 inches

NUMBERS IN LAST COLUMN REFER TO CODE NUMBERS BELOW

Cornish Nice Corpany Formice Insulation Company General Fadio Company

Silver Marchall, Incorporated Silver Marchall, Incorporated Brancer Dally Manufacturing Co. Markers W. Frest, Incorporated Henisein Elex. Mfr. Company Jacobs Mireless Carporation To Jur Products Company

Enternational Posts, Co. (CURRENT Radio Corporation of America American Part Dubber Company

...................



NOW!—Lowest-Priced \$
Quality Tube "B" \$ Eliminator - -

nee 1921 Ferbend Products have en famous for outstanding ality and long-life efficiency lowest prices—prices "Within with of All."

85 MIL. TUBE es up to 180 volts on any set

OR ACIDS

30 Days' Trial

#### to the film.ent, the other to the battery. The arm connects to the "F-" point of the input transformer.

With the 30-ohm rheostat R1 in the filament leg, the voltage applied to the tube is too low: so a section of the resistance wire is shorted by means of solder. The actual resistance in the strip required to secure three volts for filament use is 22 ohms. This gives a potential about 0.3 of a volt low: but it tends to increase the tube life without materially decreasing its efficiency

in the amplifier circuit. The adjustment on the potentiometer is made with the knob in the center of the baseboard, on top, between the two tubes.

Those who want to save much time and experimentation will do well to follow to the letter, directions in regard to the amplifier. Inductance values in transformers are highly important; so are voltages; so is layout of parts. The 222-type tube functions in excellent fashion and the best arrangement is shown here. Many hours of conscientious laboratory work have gone into the development of this new distantsignal amplifier. You can save endless trouble by following the diagram and specifications-and that goes down to the tencent beverage shaker.

#### MOUNTING AND WIDING DARTS

From the drawings and diagrams accompanying this article it should be easy for the builder to construct an amplifier which will immediately duplicate the results secured with the original. The layout shown in the drawings is unusually compact, yet one which calls for no difficult or intricate wiring. If this placement of apparatus and general wiring plan is followed, the top of the completed amplifier will be quite free from wiring.

On top of the horizontal panel mount the three transformers, the two input types and the third the output type. At the rear of the panel go the eight binding posts for battery connections. For convenience in wiring, these may be mounted in the order indicated in the drawing,

The two tube sockets mount near the front of the panel, through which a hole 1% inches in diameter is drilled for each socket; and the socket is mounted from the under side of the panel, with the cushioned receptacle coming about flush with the top.

#### SHIPID IS NUCESSARY

The builder should not regard the shield over the 222 type tube as a useless novelty in any sense of the word. Its use is absolutely imperative; for, without it, when the amplifier is operated there may be heard soneals or stray bowls which are attributable purely to the lack of a shield over the screen-grid tube. The shield shown in the sketch makes about as handy a one as you can get. It costs only a dime at any fiveand-ten-eent store, and does the work just as well as a more expensive one,

The potentiometer, R1, mounts between the two tube sockets and on a line with them. The position of the two fixed resistors R3 and R2 is clearly indicated.

To allow satisfactory mounting of parts under the bakelite panel and to allow clearance for these parts when in place, it will be necessary to use four rubber mounting feet, one at each corner. The use of these also puts a nice finishing touch to the whole job and, since the amplifier is not very

heavy, belos to keep it from slipping or sliding on a slippery surface

Mount the parts under the panel exactly as shown in the pictorial sketch of this part of the assembly. With the arrangement shown, the wiring can be readily kent short and direct, with the finished job a very neat and workmanlike one. Flexible rubbercovered wire will be found excellent for the actual work of connecting the various parts,

#### POINTERS ON OPERATION

While 22 volts and 135 volts are shown for the inner grid and the plate, respectively, voltages of 45 and 180 may also be used, if desired,

By using a higher value of grid leak (1 to 2 megohms) and allowing distortion in the last tube, due to the large signal voltage built up, and the time lag of the grid leak, a very good code amplifier is secured. The maximum value of the amplification

securable is a function of the grid leak of the 171-type tube. When this is high, allowing the full effect of the high inductance used in the plate circuit of the 222-type tube to come into play, the signal voltage becomes greater than the allowable gridvoltage swing of the 171-type tube.

The whole unit is controlled by the inductance of the coupling unit and the value of the grid leak, which forms the shunt circuit for the choke.

While if necessary, a value as low as 25,000 ohms may be used for grid leak with good volume and tone, it is better to employ a leak of at least 150,000 ohms. time lag seems great, due to using a large value of resistance for grid leak, this may be partly overcome by increasing value of bias from a normal of 45 to about 60 volts.

#### The "Screen-Grid" Tube

THE new four-electrode vacuum tube used in several circuits described in is issue, and which was designated in the January and February numbers of Ranto News as the "shielded-grid" tube, will hereafter be known as the "screen-grid" tube in the editorial columns of this magazine. The proper designation of this interesting device has been the subject of much discussion in the Rapio News office, and varying opinions were expressed by the members the editorial staff. The term "screen grid" was finally chosen because the leading tubes of the type are so marked and marketed. "Screening," in British radio parlance, is the equivalent of "shielding."

Readers are advised that in other publications they may see this same tube referred to as the "screened-grid." "shield-grid." "shielded-grid," "shield-plate" or "shieldedplate" tube.

#### FOR SAFETY'S SAKE A note of caution: Some experimenters

have reported unexpected burn-outs of the screen-grid tubes, caused evidently by contact between the grid elements and others. Before putting a new tube of this type into service, it is a good idea to test all the contact pins in relation to each other with a six-volt battery. The filament should light only when the battery wires are touched to the filament pins. If any other connection flashes the filament or if there is a circuit between the screen grid and the control grid or the plate, the tube is defective,



# FERBEND ELECTRIC COMPANY



Write for Other Special Bargains Nose is SPIEGEL RADIO COMPANY

TERMS: 25 P \$100 WILL SAVE YOUR SPEAKER

# The Craftsman Dollar Speaker Filter is Guaran-teed to relieve your speaker of the DC plate current (up to 250 volts). It gives speaker a chance to oper ate at its best. Attached in a second. Send dollar in a second.

CRAFTSMAN RADIO PRODUCTS Newark, N. I. 9 Orchard St.

### **Balkite** Radio Power Units England Products Co., Inc., North Chicago, Ill.



#### The Girl on the Cover ---Caroline Andrews

F a canvass of all the female artists on If a canvass of all the female artists on the air were made, it is doubtful whether e would find a more popular or a more distinguished voice than that of Caroline Andrews, the "Lark" of Major Bowes' "Capitol Family," which broadcasts every Sunday evening through the WEAF chain.

Miss Andrews has a distinguished musical career to her credit, boasting association with such nationally-prominent organizations as the DeKoven Opera Company, Philadelphia Opera Company, St. Louis Municipal Opera Company, and more re-cently, with "The Student Prince" operetta. She really began "backstage" at the age of five, with the opera company in which



her mother was singing. She used a wardrobe trunk for a stage and sang the "Jewel Song" from "Faust," and the "Last Rose of Summer" to the delight of the adult members of the company. It was when the late Reginald DeKoven engaged her for his own opera company in revivals of his famous operas, "Robin Hood" and "Rob Roy," that Miss Andrews reached the rank of prima donna, singing the soubrette role with sensational success from coast to coast. Then, at the Philadelphia Grand Opera season, in a company composed of Chicago and Metropolitan Grand Opera stars, Miss Andrews divided the honors with Florence Easton and Ricardo Martin in "Carmen."

The millions of radio fans who listen-in on the Capitol "Family" look forward to the weekly appearances of Miss Andrews, whose glorious coloratura soprano is equally delightful whether heard in an ambitious operatic aria or a simple, lovely ballad or folk-song.

#### A SLIGHT DIFFERENCE Axx: "Is your neighbor's set portable?"

TENNIE: "No, insupportable."

-Gleason Pease.

#### Australian Short Waves

AMERICAN short waves have been rently the compliment was returned at Schenectady. Both Sydney and Melbourne put frequent broadcast programs on the short waves. Melbourne's 3LO transmits regularly Monday on 36 meters (at hours corresponding to 1:30 to 3:30 P. M. Sundays, Eastern Standard Time) and will be glad of reports from listeners,

#### Japanese Aerial Radio

PUBLIC telephone and telegraph service plane "Naniwago," whose call letters are her name, and whose transmitter operates on the standard 600 and 900 meters. This is the first such service in Japan, if not in the world. The plane is owned by the Nip-pon Koku Kabushiki Kwaisha, or Japanese Aviation Co., Ltd.-T. Yamada.

#### Much Heat Liberated in Power Units

WHEN rectifier tubes of some larger types are used in power-unit cir-cuits, it may be noticed that they heat up excessively. It is a good plan, in such a case to place a piece of asbestos between the tubes and the other apparatus in the power unit to prevent damage. The importance of ventilating apparatus which is generating such a quantity of heat is apparent.

#### "Microphonic" Noises

VERY often in amplifying circuits where "high-mu" tubes are used, a howl is noticed in the loud speaker, which is not changed by adjustments of the receiver. If this happens the tubes are said to be "microphonic." This condition can usually be corrected by moving the reproducer away from the receiver; although it may be necessary to mount the tubes on sponge rubber to dampen the vibrations. are on the market at present several types of shock-proof sockets which are helpful in preventing this microphonic ringing. Exchanging tubes in the sockets is also beloful in some cases.

#### Pepping Up the Veteran Radio Tubes

SIMPLE and efficient method of rejuvenating tubes which have "gone is to turn their filaments up to normal brilliancy and then to reverse the polarity of the "B" battery, connecting its positive terminal to "A+" and its negative to the lead which is normally connected to the "B+". The tubes should be left connected in this manner for a full hour; the filament current should then be turned down to the lowest point and left this way for another

In cases where the tubes are unusually poor, the treatment may have to be repeated. After the tubes have been allowed to cool off, the batteries should be connected in their correct manner. It should be borne in mind that some types of tubes are not suitable for rejuvenation; such are the 200A, and certain power tubes.

MAGNAYOX



# R500 Unit

# Dynamic Power Speaker

#### and power amplifier combination

THE wonderful Magnavox Dynamic Speaker, with a matched power unit, self-contained on steel frame, is ready for installation in any radio set or phonograph cabinet having space available of 14 in. wide and 12 in. high.

Power unit for 105-125 volts 60-cycle A. C. supply. Requires one 316B type rectifying tube and one 310 or 210 type amplifying tube. Can replace last audio tube of set or use all tubes of the set. For use with phonograph electrical pickup head: two additional audio stages recommended between pickup and R500 unit.

Only the dynamic type of speaker can bring out the full qualities of reproduction demanded today. With this carefully matched power unit the combination is the highest grade of radio device. Price \$120 for complete unit less tubes. Write for speaker bulletin.



LOBOY MODEL R500 Unit in handsor cabinet, finished in ri old English brown m hogany. \$165.00 b

The Magnavox Company Oakland, California

#### That British Sense of Humor

JUST about the last kind of receiver I would put in the hands of a boy or enthusiastic beginner is one of these swinging-coil plain aerial affairs," says Thermion, in Amateur Wireless (London). "Yet the B. B. C. scatters these circuits abroad, stamps them with its official seal, tells us that they are the goods-and then becomes worried over an increase in the matter of catcalls, chirps, squeaks, yells, howls, and moans that in some localities accompany its transmissions." Pausing to insert a tongue in a cheek, the Englishman then iibes: "Circuits such as these could not be tolerated for a moment in America."

> Manchuria to Germany HE longest regular radiophonic serv-

ice which has vet been established, is reported in effect since December 2nd between Mukden and Berlin, according to the news bulletin of the Department of Commerce. It does not appear whether this is a single span by radio, or whether there are links of land lines.

WHILE experience with short waves are absorbed by the ground, so that communication beyond a point of visibility is almost impossible, an Indian experimenter will test them between the ground and the workings of a coal mine near Calcutta, in the hopes of perfecting a means of com-munication between the surface and points underground.

What's in a Name?

HERE is a professional distinction between a "journalist" and a "news-aper man." Perhaps something of the kind is intimated in the suggestion to a Melbourne, Australia, station that those who describe sporting and other events in progress as they occur, over the radio, be known as "radiographers." Whether they will rank above or beneath announcers is not stated; but it will doubtless be a moot point.

#### If and When

The Atlanta Constitution wonders whether a radio announcer, when he says his prayers, asks the Good Lord, from force of habit, to "please stand by." Probably he does, and also politely suggests, if the Lord likes his prayer, "to kindly write or wire in and say so."-Washington Post.

For DX Listeners

THE Australian station 4QG, Brisbane, announces "Australia" after its call letters, for the benefit of listeners in America and elsewhere who may be tuning in for distance. As the number of short-wave broadcasts in America increases, a similar precaution may be desirable in this country.

Short-Wave Radiophony S TATION WND, Ocean Township, New Jersey, supersedes 2XG as a call. This station is in transatlantic communication on 13.88 and 46.48 meters.

Presidential Station The radio station aboard the President's vacht, the Mayflower, has the call letters NJV.

#### Day vs. Night Reception

IT is reasonably certain that long-wave daylight radio signals both from distant tations and from those only two or three hundred miles away were stronger in 1927 (when the eleven-year sunspot cycle was near its maximum) than in 1923, when it was at its minimum, according to Dr. L. W. Austin and Miss L. J. Wymore, of the Burean of Standards.

On the other hand, Dr. Greenleaf W. Pickard has shown that at night, in the broadcasting range, signals grow weaker when the number of sunspots increases. Hence it appears that the effect of solar activity on signals is reversed when day gives place to night. This corresponds to the conclusions of the engineers of the Bell Laboratories, that magnetic storms, which are known to be connected with sunspots. weaken medium- and long-wave signals at night and slightly strengthen them in the daytime. The evidence regarding the influence of magnetic storms and solar activity on ultra-short waves is somewhat conflicting.

#### Excuse It. Please!

THE cactus-lined carphones go to Dutch telephone operator for the prize rong-number stunt of the century. A resident of The Hague picked up his phone and asked for a number in Amsterdam, according to Wireless World. After having his ear filled with the usual number of splutters he heard a voice saving "Hello!" or the Dutch equivalent thereof.

"Hullo," he inquired, "is this Amsterdam?" "No," replied the voice, "this is Bandoeng" (on the island of Java.)

The telephone operator had inadvertently switched the subscriber to the input side of the powerful radiotelephone station at Eindhoven, Holland, which communicates with Java and other points on the other side of the world. Isn't that enough to jar a resident of Levden?

R ADIO statisticians who try to determine the relation The Kilowatt as a Measure of Enthusiasm features have a new measuring stick to work with: the kilowatt-hour. According to Arthur Williams, vice-president of the New York Edison Company, New Yorkers burned up 86000 worth of extra electricity the night of the Tunney-Dempsey fight, listening to the radio description of the battle and staying up to read the newspaper accounts that appeared shortly afterward. The extra load carried by the company's generators did not fall off until three o'clock

Broadcasting in Russia HERE are 56 broadcast stations in

the next morning.

the Union of Soviet Socialist Republies, (U. S. S. R.) Of these nine are in Moscow and five in Petrograd. In sending your report cards to these stations don't address them to "Russia;" they will be returned.

Praise from the Master

HE United States has progressed in radio until it is ahead of all the other nations of the world, stated Senatore Guglielmo Marconi on the occasion of his most recent visit to this country, early this winter.



rovides the ideal resistance for B-eliminators requiring fixed resistors of permanent resistance value. Not affected by age, temperature or humidity. Will not deteriorate in service.

# Bradleyohm-E

provides accurate plate voltage control for Beliminators. Used extensively by B. eliminator manufacturers Not affected by ti

# Bradleyleak

grid leak that assures the ideal grid leak value. Easily installed on any



set. Enables operator to get the best possible results with any tube

This pioneer in filament control of radio tubes is still mighty popu-lar. Provides noiseless, step-



less filament control for all tubes. Try a Bradleystat on your next set.



# PACENT No. 322 Distance Signal Amplifier

Pacent Transformers plus Pacent Cushion Sockets plus CX322 or UX322 Shielded Grid Tubes plus Pacent Engineering made possible the design of the

DISTANCE SIGNAL AMPLIFIER Described in Radio News

Pacent Electric Co., Inc. 91 Seventh Ave. New York, N. Y. CONTROL your AC TUBES!

#### World Broadcasting-A British Proposal

ON'T you think it is high time we wakened up from our typically h apathetic attitude towards the infinite possibilities of a system of Empire or even world broadcasting?" inquires the

vivacious "Halyard," who enlivens the pages of Wireless Magazine (London) each month. "I certainly thought so recently when I read through a fascinating article on this important subject in an American radio

periodical." (Modesty forbids us from naming the writer and the magazine; but the readers of our September issue will probably guess .-

EDITOR, RADIO NEWS.) "The writer of the article I have in mind don't you think that we ought to be able to reply with something of the same kind from

this side of the Atlantic? "What about it, then? Shall we go in for a double, treble, or some higher-ble super-station at Daventry which will tell the whole world of the greatness of Britain and the British Empire? We have the Rugby station as some kind of a start for

such a scheme. "As an alternative, we might work out our scheme in terms of beam transmissions from England. There are, or soon will be, efficient beam-transmitters to North America, Australia, South Africa, India, South

America, and Egypt.

"Looking at a map of the world, it seems to me as if we have, in the above-mentioned beam transmissions, the basis of as fine a



said that, when it comes to telling the rest

CLAROSTAT

VOLUME CONTROL

AMERICAN MECHANICAL LABS., Inc. Specialists to Variable Resisters 285 North 5th Street, Brooklyn, N. Y.

......

of the world about the greatness of America and its achievements, radio has as yet a great and important duty to fulfil. "To provide the world with American

broadcast transmissions, this writer put forward a plan for the erection of five superstations of immense power. Four of these stations would be placed at the corners of the United States, and these four corner stations would work on the beam-transmission system.

AN EMPIRE SCHEME "If an American writer can put forward such a fine scheme of world broadcasting, scheme for broadcasting to the whole world as could possibly be devised. "Our North American beams could be

made to cover the whole of North America. Our Australian beam could be made to cover Australasia, our South African beam Africa, our Indian beam Europe and Asia, and our South American beam Central and South America. We should scarcely want the Egyptian beam.

#### WHILE THE WORLD GOES 'ROUND

"George has a beaming scheme up his sleeve. It consists of two twenty-four-hoursa-day-continuous-programme-revolving-beam transmitters, one at the North Pole and one at the South Pole, the stations revolving on the carth's axis so as to throw their beams always along the daylight zone. I can't imagine a radio engineer wanting to live at the North Pole or the South Pole, though."

#### An Effective Regeneration Control

NE of the simplest and most effective methods of controlling oscillation in radio-frequency circuits is to connect a midget variable condenser and a variable high resistor across the grid and plate of the radio-frequency tube. An ideal arrangement consists of a .00025-mf. condenser together with a universal-range resistor, wired in series and connected to the grid and plate terminals of the tube socket. The instruments should be mounted close to the tube, to keep the radio-frequency wiring as short as possible,



#### WANTED

We want direct factory representatives in all territories. Write for details and POTTER PRODUCTS CORP. 245 Fifth Avenue, New York City

# Radio "Bugs"

44 AM sorry," says Entomologist Harry Slive, of West Pittston, Pa, "that in my adventures in Radio Land I did not have my camera with me; but as soon as I returned home, I made a drawing for Ramo News of the most maning animal I saw there; it is hown as the Battery rider is called a vibrator. Its diet consists wholly of full-grown cycles and volts, which it consumes in quantities of 90 of the former.



to 110 of the latter. Sometimes the vibrator holds his charger still, and a battery can approach within a few inches in perfect safety. But this is only when the vibrator is externally indisposed. The vibrator, as you know, is quite a villain in Radio land, and I hope you agree with me that there should be a law passed therein, causing the death or expulsion of every vibrator therein or therefrom."

A pathetic scene is often seen on the highways of Radio Land, a puny, overworked tube pulling a huge loud speaker.



The look of despair on the face of a poor little 199 was noted and put on paper by Brinton Sullivan, of Macomb, Ill. It is recommended that an able-bodied 210 be given the job of pulling, with an equally hefty brother to do the pushing. The ayes have it.

Much conjecture has been occasioned as to the latest output in the form of flivvers.



The special model designed for the use of Radiolanders is illustrated here; and a special type of meter is required for the circuit. The collaborating engineer, Jack Shields of Los Angeles, suggests that this type be known as "Henry's Farad." That will be all from you for the present, Jack. F. C. Houghton, of Newark, Delaware, has an eve for bathing beauties. Here is



a filter hesitating on the beach at Capa City. "A wave met' ren," explains our artist, "but fortunately for her it wasn't a continuous one." The same pen sketches a scene of domestic discord, and comments: "This powerful transformer is especially efficient in amplifying distress signals." We



would say that the transformer is doing very well, but the rectifier seems to be in for a session with the radio doctor.

Another of the strange beasts in the forests of Radio Land is known to zoologists as Phonae Resisticus. He prowls around, especially at night, looking for his prey, commonly called signals—the weaker the better—and when he finds one that seems a long way from home, he pounces upon it. This specimen was captured—



alive-by Robert L. Hood, of Pittsburgh, Penn'a.

Harry K. Shibuya, of Vancouver, Canada, has discovered another nocturnal prowher, whom he identified, after some study, as the common or garden variety of "Tohm Cat." Its capacity to ground is high, and the circuit appears to be a noisy



one. Another study by Mr. Shibuya is an Eliminator in the process of eliminating.

Everywhere Under The Sun

Speed Radio Tubes

A Tube for Every Radio Need

> Test the Superb Quality of the New

SPEED

X226 A. C. Y227 TUBES

> VOLUME NO HUM

Long Life

CABLE SUPPLY CO

31 Union Square, New York

#### MAKE MONEY IN RADIO

Over 4,000 Men Now Making Big Money Through Our Plan

THE CUSTOM-BUILT HI-O SIX is the

THE CUSTOM-MUILT HIG. SIX is a must transtraint events of present year. Designed by 10 of America's shades risked present of present year. The present of th

HAMMARLUND-ROBERTS, INC. 1182 Broadway, Dept. C, New York

> **Hammarlund** - Hi-O'SIX -Associate Manufacturers



CLOVERLEAF MFG. CO.

# ACCOUNTING

are earning more money today because they know Accounting. Send for our 30-page book, "How to Learn Accounting," and the first lesson. Both will be sent free. International Accountants Society, Inc.

Dept. 26 3411 So. Michigan Ave., Chicago, Ill.

Scalers, set builders, opents, Dept. 893A. rawik Co., 129 N. Jefferson St., Chicago, U. S. A.

Pick-up device.

AMERICAN BOSCH MAGNETO CORP.

Massachusette

Its late rider appears to have received instructions to dismount directly from



hindquarters. We surmise also that his first name is Mike.

At the vesper hour, when the Heaviside layer is laying most heavily, strange nocturnal creatures make their appearance from the ionized atmosphere. We thought at first glance that it might be an owl, the bird of wisdom; but closer inspection justifies the assertion of its discoverer that it is the Bat. (Not "A" Bat., however.) Its



polarities, however, are entirely too positive, and we do not feel justified in recommending our constructive readers to "C" this Bat. It was discovered by Marad Serriov, of Palo Alto, Calif.

After these surprises, we feel that it is high time to retire for another month; some of the remaining revelations in our archives might be too much for the sensitive reader to accept at one sitting. But there are more bugs in Radio Land than the average fan has yet dreamed of in his philosophy; at a later date we shall perpetrate the remainder of them.

#### Liquid Air in Radio

SCIENTISTS have discovered that a piece of metal cooled to extremely low temperatures becomes almost a perfect conductor. An English experimenter, Mr. Alan J. Bremner, has announced to his radio society that when the antenna coil of a set is immersed in liquid air, while the strength of the signal is not increased, the selectivity becomes remarkably high. Soon no DX fan's workshop will be complete without a thermos bottle of liquid air.

#### RADIO TERM ILLUSTRATED



"A Phonograph Pick-up,"

ccccccccc .... the dawning Anew field for men

# instructive books



PRICE \$5.00

700 Pages 500 Illustrations

ment, Fabrication and Brating of Controlled 
This book is written in simple, understandable

#### AVIATION ENGINES



TA DACES

# PRICE \$1.25



AVIATION

PRICE \$1.25

Remit by cash, stamps, check, No C.O.D.'s

We Pay Postage On All Books

CONSRAD COMPANY, Inc. 230 FIFTH AVENUE NEW YORK

#### Why Vacuum Tubes Become "Paralyzed"

PRESENT-DAY vacuum tubes, for the most part, have so-called thoriated tungsten filaments, the action of which, even at this late date, is not fully appreciated by the

average listener. The electronic emission of such a filament depends upon the presence of a layer of thorium atoms on the outer surface of the filament. Unlike the oxide-coated filaments found in some tubes, the thoriated tungsten filament is not merely coated but permeated throughout its entire mass with the rare element thorium. During the normal operation of such a filament, the thorium on the outer surface is gradually evaporated, reducing the emission current and, if this action is permitted to continue, rendering the tube short-lived. However, while the heat of the filament serves to evaporate the thorium particles on the surface, it is also boiling fresh thorium particles out of the mass and up to the surface. Thus the surface is being continually replenished. Just so long as the filament voltage is not increased bevond about 10 per cent above the rated value, this evaporation and replenishing process continues at an equal rate, so that a constant layer of thorium is maintained on the surface

When the filament is subjected to an overvoltage, however, the evaporation is excessive, so that the tube consequently becomes more or less paralyzed. Operating these tubes at sub-normal voltages is also liable to paralyze them slowly, as the filament temperature is then so low that the process of boiling out the thorium from the interior of the filament becomes abnormally retarded. Hence it is important that tubes with thoristed-tungsten filaments be operated strictly at their rated voltage.

#### Test Soldered Connections.

FTER soldering a wire to a condenser good plan to give it a strong pull with a pair of pliers to be sure that it is really soldered and not merely held in place by the strength of the flux.

#### 40 Non-Technical Radio Articles

every month for the beginner, the layman and those who like radio from the non-technical side.

technical side.

SCIENCE & INVENTION, which can
be bought at any newsstand, contains the
largest and most interesting section of
radio articles of any non-radio magazine in

existence. Plenty of "How To Make It" radio arti-cles and plenty of simplified book-ups for the layman and experimenter. The radio section of SCIENCE & INVENTION is 20 good that many RADIO NEWS readers buy it solely for this feature.

#### Radio Articles Appearing in MARCH Science & Invention

"S. & I." Three-Tube A.C.D.C. Set—Details Describing How to Build a High-quality, God-Volume Regenerative Sct. Uning The New A.C. Tubes.
"MacLed and the Set of the

#### The Listener Speaks

(Continued from page 992)

blown condensers, etc. The way, therefore, to support these stations should be that every radio manufacturer should pay one mill or whatever is necessary of his sales to the broadcasters, being evenly or otherwise divided. Certainly these manufacturers get enough profits for their merchandise, for some of them have grown into millionaires "overnight"-as radio is only about five years old. Why "sock us guys" any more than we have paid? Being a home set builder. I'll bet radio cost me a thousand bucks in the last five years, on my own sets; and many another "bug" has paid as much or more. And then they (the N. B. C.) have the crust to ask us to pay more-3 to 20 dollars a year. They want "whole hog or none," evidently. D. V. CHAMBERS.

510 West 144th Street, New York City.

(Our reader sets forth quite clearly the position of, probably, a majority of broadcast listeners and set constructors: yet, perhaps, does not attach enough weight to the "other fellow's story." We fear that the commercial operator is unjustly accused; though undoubtedly there is still in existence oldstyle commercial and ship equipment enough to cause annoyance to many listeners. The plan for simultaneous chain broad-

casting has been very attentively considered by engineers; but it is not yet sufficiently developed for general adoption. As to the proposal that an assessment on radio apparatus sales should pay for broadcasting, the cost of broadcasting has evolved far beleast, so costly that the expenses of either run beyond the proposed assessment on radio several times. Quoting an old prov-erb, "the mill cannot grind with the water that is past."

Neither the N. B. C. nor any other American broadcaster has asked for a tax on receiving set licenses, such as governments levy in all other parts of the world for the benefit of broadcasters. The only other alternative is that set owners shall buy radio-advertised goods to an extent sufficient to warrant the advertisers in presenting good programs; just as the purchase of other advertised goods warrants the advertisers in defraying a large part of the cost (sometimes 90%) of publishing newspapers and magazines. As another old proverb says, "Those who pay the piper call the tune"-without adverting to a third, which assures us that "The piper's pay is more kicks than halfpence."-EDITOR.)

#### A Woman's Choice Editor, RADIO NEWS: Every woman fond of music wants to

hear that, of course; but I think, more than that, the woman whose household duties keep her tied up more or less around her own home wants something which will inform her of things outside her home. Something which a woman can be interested in and have to think about later, or discuss, or read about in her spare moments, would be light lectures on various simple but interesting topics.

The subjects might pertain to interesting observations of nature, unusual events of WE RECOMMEND

# ULIRADYDE ELECTRIC

Licensed, manufactured, and sold under rights owned and (or) controlled by R. C. A., Gen. Elec., Westinghouse, and A. T. & T.



Six genuine R. C. A. alternating current tubes, built-in air column loud speaker, genuine walnut cabinet - two-tone finish. No batteries of any kind required. Never before was an all-electric set offered at such a low price.

#### SET BUILDERS AND DEALERS

This is one of the many bargains listed in our new 1928 BUYING GUIDE. SEND for your copy today.

#### Allen-Rogers-Madison

Incorporated 35 W. 31st St. New York City

# FROST-RADIO OFFERS TO READERS OF RADIO NEWS TWO VALUABLE NEW BOOKLETS FREE!

Write for Them
Wite for Them
Wite for Them
Wite for Them
With the Control of the Control
From - Regions within the
form in request. What is to
co a spential within paint
for a proposity within the
form in the control
for a proposity within paint
fo

FROST-RADIO
What they Contain

Build" To secure these two bookto receive the FREE, just fine of the free two bookto receive the FREE, just fine of the free two books on the free two printing your name off the free two free two books will antice to the free two books will antice two free t

HERBERT H. FROST, Inc. 100 North Lafalle Street, Chicago, III. Please send me free your two booklets, as advertised in Rudis News for March.

Name. Street Address. City.

....State.....

# EVERYMAN 4

SERVICE STATION
CUSTOM BUILT
SET ON DEMONSTRATION

SET ON DEMONSTRATION
Wired by experts to your order

We keep abreast of all changes and improvements of this wonderful circuit, including the latest screen grid tubes.

RADIO KIT CO.

22 CORTLANDT ST. New York City.

RAISE BELGIAN HARES

Print Your Own

Gards, Stationery, Circulars, Paper, ecc. Save

Gards, Station

the day and their influence on the public, brief accounts of interesting incidents in the lives of noted men, without going into a detailed account of each year, or any educational topic of human interest.

Marion K. Zerbe, Riverdale-on-Hudson, N. Y.

#### A Guide to Current Reading

I am particularly interested in magazine articles of all kinds and, as I am unable to buy many magazines and would like to know what is of most interest in the month, I have often thought that perhaps our afternoon radio adviser might give us a resumé of several magazines each week. This would cover those most worth while, and from them one could select her magazines for

of several magazines each week. This would cover those most worth while, and from them one could select her magazines for the month.

I hear books discussed, recipes, fashions and, of course, the daily news items; but I never hear a word about magazines and I

surely would appreciate the information.

Mas. J. Paul Ellis,

Delmar, Delaware.

Daylight Reception

Editor, RADIO NEWS:

Your magazine is quite obviously an aweinspiring success among periodicals of our time; the reason is equally obvious. I have before, as the continuing successes appeared in print, thought of writing you; but it's too obvious, and your mail is already heavy.

However, another old subscriber writes, and you defend your policy (page 949 of February Ramo News). Quite so; I too, care nothing for pictures, or even jokes. But I well know what a great game it much limit to the property of the property of the subscriber of the property of the subscriber of the property of the pro

I have just written to Mr. Woodruff (whose letter appeared on pages 872 and 916, of the same February issue), on the subject of daylight reception. WHO at Des Moines, is reporting the noon money market in New York, strong enough (with an aerial) to run the horn off the detector cir-

I turn to WBAP and the announcer says we are being entertained by the Fort Worth Club Orchestra. I go to the back of the house and sake Friend Wife to observe that the music she hears there is from WBAP. I have had Asheville, Annuallio, New Orleans, etc.; WJZ will come through on a loop. The professors' lectures at WSUI, lower Clty (500 watts) come beautifully at

Over three years ago, in a winter shade on the Arkansas side of the Onaria (three 190 tubes), I was listening, with my write. The state of the Arkansas of the State of the Arkansas of the Ar

D. Burkhalter, Route 8, Bloomington, Indiana.

Chicago to England

Editor, Ramo News:

The brief article on daylight reception in

last month's issue is interesting to me, because I have been gathering data for years. I know of a receiver in New Hampshire which tuned in a Chicago station at noon; and I have been told by an employee of a Chicago station that there was a verification that there was a verification that there was a verification of a game of the White See in the Rivisio Isles.

Last December, on a Silver-Marshall Six, I tuned in W.W.U before sunset from a Central Illinois location—the report of which will, in the opinion of most readers, entitle me to a life membership in the Ananias Club. An attendual at W3Z informed one that a program from the properties of the way. I would be propertied the way to be properties of the prop

J. C. Scorr, Plainfield, New Jersey.

SOUTH A ROLLING

#### Short Waves in Java

Editor, Radio News:

The short-wave phone transmitter at Mashar, Java, is now working again regularly with 28 kilowatts on 17.4 meters with the Dutch short-wave phone station PLLI<sub>4</sub>, ISV Ucchesslys and Fridays. As thee stations now come through very well, there will be opened within a few weeks a shortwave phone service between Holland and Java. This will be the longest in the world stating system.

As to heavy tropical static; this is indeed very serious, especially on the higher wave-



willnotbe sitting ontop of this coming Fall Season unless you climb aboard with the

A new basic circuit employing nine tubes. World's latest—macclaimed circuit—the SUPER-HILODYNE—radically new—mu

mand—a sure money-maker for custom set builders-

#### WANTED

OTT	ifth	A	ve	m	ie	ï	N	ē	w		Ÿ	ö	ri		т	ı,	Y	ı								
Gen our p	tan	to	bi	do	1	Ď.		ñ		è		й	'n.	'n	š	ŭ	×		'n	ń		ü				
Vame.																										
Lideres	ŧ.,,						ě.										÷				٠	٠				

We want direct factory representatives in all territories. Write for details and our unusual money-making proposition. POTTER PRODUCTS CORP. 245 Fifth Avenue, New York City lengths, but depends also on the season. On the short waves, however, it is no obstacle. Most of the inland and foreign traffic of the Dutch East Indies is handled by the short-wave transmitters, ANC, AND, ANF and ANH (Laboratory)

> D. HERRI. Bandoeng, Java, Kartiniweg 13.

#### Book Review RADIO PROSPECTING. A portion of a

complete course in practical radio. pages, paper cover, 5% x 8½ inches. Published by the National Radio Institute,

Washington, D. C.

A great deal has recently been published, con cerning the methods of searching for precious ores by means of radio-frequency currents. many people this means of prospecting has seemed to smack more or less of the long-haired gentleman who dispensed snake oil from the rear of a wagon. However, according to the book ods which can be utilized for the locating of iron, copper, gold and other ores without the exp digging. first to be described is called the Equi

Potential method. The fundamental principle used in this method is that an electric field is the help of a telephone receiver, a series of "level lines" is determined upon the surface and, by observing the disturbances in these level lines, it may be determined whether deep-lying ores are present or not.

The Chilson Method is quite like that used in the determining of a ship's position at sea by radio. It embodies the old principle that a trans-mitting station will come in on a loop antenna connected to a receiver strongest when the loon connected to a receiver strongest when the loop is pointed directly at the transmitter. The sig-nals are picked up by a loop receiver at differ-ent points on one side of a supposed bed of orc. If the signals cannot be received, it is indicative that a metallic ore between the transmitter and the receiver is absorbing the radio waves. Then, by triangulation, the exact location of the bed or vein can be calculated.

The Re-Radiation process depends on the prinradio-frequency wave, there will be induced in it similar currents. These secondary currents are traced down with a loop-operated receiver in are traced down with a loop-operated receiver in much the same way as in the Chilson method; except that the ore itself in this case is really a secondary transmitter and not an absorber. For those interested in this phase of radio, this work may be recommended, as the prina way that those having but a fundamental knowledge of electricity and radio can comprehend.

HOW TO OPERATE YOUR RADIO WITH A "B" POWER UNIT. Published by the Modern Electric Mfg. Company, Toledo, Ohio. Free for distribution; 31/4 x 51/2 inches, 14 pages, paper covers.

The above is the title of a booklet issued by its publishers for the purpose of assisting radio fans in choosing a "B" power unit, as well as operating it correctly. It contains a wealth of information on the theory and operation of various types of "B" the theory and operation of various types of "B" power devices. Several of the subjects covered by this booklet are: the principle of operation of the rectifier tube; the types of "B" power units; the correct methods for connecting them to radio sets; correct methods for connecting them to radio sets; determination of power-tube voltage; the correct methods for reducing voltages of power units; a table showing the correct "C" bias for various tubes; and a list of possible difficulties to be encountered when using power units, and their corrections.

rection.

In the first section the theory of rectifier tubes.

In the first section was a constant of the cons

The final section in this booklet deals with the possible difficulties encountered when using power units in radio receivers. Common remedies for squealing, blasting, hum, motor-boating, paralyzed booklet will be of particular interest to all radio booklet will be of particular interest to all radio fans who are operating their receivers from A.C. and power-lighting source; since correct operation of receivers with power units can be obtained only through a knowledge of the operation and character-istics of the power units used.

#### Letters from Home Radio Set Constructors

(Continued from page 1035)

to the shielding panel, use of a Bretwood variable grid leak, low-loss coils of different inductancegrid leak, low-loss coils of different inductance-one new coil for every additional turn-and last, but not least, patience. We being in Europe regularly: London at 4:30 p. m. with load-speaker volume. Three times around 1:00 p. m., we heard a station announcing in a Slavish language, and caught the word "popolisis."

caught the word "popolski."

Both of us use the circuit published in Radio
News for August, 1927, attached to a Kolster
eight-tube set. As you know, this has four stages
of R.F., detector, and three of audio, with one contrel. We use a spring-coil aerial and a really good
ground. On taking the attachment to a friend ground. On taking the attachment to a friend who has a Golden-Leutz set and an outdoor aerial we obtained splendid results there as well. On the other hand, attaching it to a Radiola X, even shortcircuiting the tickler, we falled to bring in a sound. I believe that short-wave experimenting for the present, is the only thing worth while for the

Permit me to present the "Chicoutimiflex." a five Persist me to present the "Unknowlimitex," a hve-tube combination of Roberts' non-oscillating reflex and the first stage of the Jewell Super-Hilodyne. When trying this circuit out with the phones, I got a feeling as if I were looking into the space on the other side of the static level or beyond the Heaviside layer. It was an uncanny feeling of unlimited distance close at hand; and when I started out to get some station, the results justified that

Selective? Well, if you know what that means, I can tune in Montreal regularly. Volume? Enough for a big theatre. Tonality? Beethoven would like a chance to hear it. Distance? Better than anything I know of. Chicago in the day time, the Watch Tower in the morning, with indigestion

have made this a one-control affair, with the A nave mase this a other-control anair, with the oscillator-condenser as a volume regulator. It does not work well on the so-called "B" eliminator. Possibly the Bee is eliminated, but its hum is ever present. If you do not mind my conservatism, all that eliminating business around here, something is humming, and that is the by-pass condenser: is humming, and that is the by-pass condenser; something like a Leyden jar, if you know what I mean. Something with a tremendous kick in it; after you took a good try at it, you would under-stand what we mean by "body-capacity." Yes, sir, the set is working fine, no cutting of the sidebands, with best reception when the moon

J. H. VAN KOOLBERGEN, Chicoutimi, Quebec, Canada,

LOOP AND OUTDOOR AERIAL

Editor, RADIO NEWS:

While not new, the following may interest some. I have a 9-tube loop set and a 7-tube set using an aerial. These are near each other, and I noticed when the loop set was in use, signal strength could be greatly increased when the antenna coil on the other set was tuned to the desired frequency, even though the latter receiver was entirely shut

For greater convenience, I purchased a National antenna tuning coil and condenser, mounted them on a board, connected them to outside aerial and ground, and placed conveniently near the loop set. By tuning this to the incoming signal, greater volume is secured with less battery drain. Roughly estimated, I should say that fully 25% less power is

required, when the antenna tuner is used, Of course, it is easy to see that the loop set could readily be altered to a combination loop-and-aerial tuner; but the above method does the same serial timer; out the above method does the same thing very simply, with no change in the set and with no difference in the dial readings. There are two taps on the coil of the antenna tuner; the long

# CHOUD SPEAKER **OPERATION** from a CRYSTAL

NO "TUBES" - NO "B" BAT-TERIES - NO COSTLY "FLIMINATORS" WITH

#### THE SKINDERVIKEN TRANSMITTER

Simple microphone unit provides a most effective and inarpaistive way to satisfactory speake operation. Easy to build and operate circuit. Exceptive on do this now will be used to be used the diaphragm, the electrical resist ance of the microphose unit will be waried correspondingly and the eurent from the battery, in series with it and the load-speaker, will fluctuate necordingly. Thus the problem of securing sufficient power to actuate the Loud-Speaker is simply and adequated.

he results from this very novel and simple uni The results from this very novel and simple unit will astound you.

The expense of this hookup is trifling compared to elaborate tube circuits that give no greater actuation of the speaker.

Besides this there are many other valuable uses in Radio Circuits for this marvelous little unit. Every builder of Radio sets should have a few on hand.

LISTENING THROUGH WALLS This Unit makes a highly sensitive detectaphone, the real thing—you listen through walls with case. Plenty of fun and real detective work too.

CONDUCTING SOUNI SOUND THROUGH

Make yourself a ministure submarine signaling apparatus like those used during the war. Simple circuit with this microphone unit gives splendid results 12-PAGE INSTRUCTION BOOKLET containing suggestions and diagrams for innumerable uses mailed with each unit.

We Pay \$5.00 in Cash for every new use developed for this unit and accepted and published by us.

#### SEND NO MONEY

Order as many as you want—use the coupon below When the postman delivers your order you merely pay him 95e plus a few cents postage. If you order two units you pay him only \$1.75, plus postage.

PRESS GUILD, INC. 16-18-R-East 30th St., New York, N. Y. R-3-28

Transmitter Units, 95c. plus postage, two units.	for	which	Tw	Ill pay f	he s	postm
Name						

Address.... City.....State....

# BEN/AMIN

Cle-Ra-Tone Sockets

Red Top For Standard UX Typ

GreenTop Anew Five Prong Socket for A. C. Detector Tubes. Especially designed for heavy currents of the control 


One-piece terminal to tube connection. Positive or tacts. Knurled nuts for binding post connections handy lugs for soldering.

At All Radio Jobbers and Dealer Benjamin Electric Mfg. Co. 120-128 So. Sanga 247 W. 17th St. New York

coil gives the greatest volume on short-wave sta-tions, and the short coil on above 400 meters. I the change can be quickly made. With this, the greatest volume is secured by having the variable ondenser fully open on the long-wave stations C. F. Rongers

#### A BUILT-IN HORN

Editor, Radio Ni The number of letters I have received, in regards to the sixteen-foot horn which I constructed and you described in your November issue, is so great that it is impossible to answer them. They come from not only the United States, but all over the world. For the benefit of the writers, I ask you to print the following answers to the

The horn is made of clear spruce boards, 14-inch thick and fastened together with screws; it may be made straight if the constructor prefers, as the only reason for bending or curving a horn is to fit it into smaller space. A Baldwin concert unit was used in mine, with a Bodine twin-eight receiver, a 112 power tube and Amsco output filter. My aerial is 100 feet long, including lead-in; my ground wire is soldered to a copper teakettle buried in the earth. be filled with putty and painted over with white lead. I advise anyone constructing a horn of this avoid using a phone unit which gives a metallic aging sound. R. E. WHEATON,

A REAL "MUSIC MAKER"

In your issue of March, 1926, you published in-structions for making a "Parlor Music Maker," in an article by Volney G. Mathison. I have built a number of these sets, and consider this an ideal receiver. The clarity of tone, volume and DX abilities are unbeatable. I think, to be brought up to date, it deserves further experimentation, the single-winding aerial coil mentioned in the article, however, without getting an adjustment too low on the left-hand dial; so I substituted the old Roberts double coil with the seven-point switch on the primary and a "wig-wag" secondary. This is a life-saver in cutting through when stations are all piled up on one wavelength—as you so often find them. For instance, when WPG, KDKA. WMSG and half a dozen more are all coming in at one time, with the point switch I can cut down to 20, 15 or 5 turns; then advance my left-hand dial to commensate the lessened inductance, and clear up one or the other station.

I make the primary 40 turns, with taps at the first, 3rd, 5th, 10th, 20th and 30th turns. This could be simplified by taking only the 10th, 20th and 30th; as you seldom need to cut further, Recently I built a Roberts 5-tube Resistoflex; this has two R.F. tubes with a resistance coupler be-

tween. I was not satisfied, so threw it back into a "Music Maker," but left the R.F. coupler in. The result was a set of tremendous volume, great: I have picked up KFI several times this fall, good filter circuit helps the set, too. In fact I believe, if you would put this set through your laboratory and bring it up to date, adding choke coils, etc., you would have the last word in a set. The tickler can be used on anything near by; but is a great help in DX. In place of the fan tickler, a Royal high resistor is just as good. My present set, which I'll stack up against any of them, cost at "five-and-ten" prices about \$25,00. T. R. EDSON

6031/2 Third St., Towards, Pa.

#### BURIED ANTENNA FOR SHORT WAVES

filter, Rapio News: ried its hook-ups with success for many years am especially interested in radios that are home constructed, and therefore much interested in letconstructed, and therefore much interested in let-ters from their constructors. I have read many letters telling about success on short waves, and others dealing with distance heard on underground antennas; but never one which combines the two-letters are telling you of my success with the Ranio Nuws "Special Short-Wave Broadcast Re-RADIO NEWS "Special Short-Wave Broadcast Re-ceiver" described by Kendall Clough in the October 1927 issue, when using an underground antenna described in the same issue by H. Winfield Secor. Probably the average B. C. L., when he reads Probably the average B, C. L., when he reads about or hears others discuss the short waves, gets the idea that this reception is only for the amathe idea that this reception is only for the ama-teur who knows the code, and thinks it will not be worth his while to explore these little-known bands. I do not know the code at present, but I assure you I intend to learn it soon; because the fan who does not know the code is missing the cream of the radio recepti

Since November 1 has neard over one insure of and fifty phone dations below 200 meters, and I do practically all my listening on the lower bands. Almost any noon I can tune in 2XAD on 22 meters as load and clear as the best stations heard at night. The most fun I derive from low-wave listening is hearing the "Hams" chew the rag on 180 and 200 meters. These boys are sure a fine bunch and

much sport can be had from reporting their sig-nals and receiving their QSL cards. I have a special card printed, which I fill out and send to them; and they in turn send me a card telling me about their station, etc. I have about a hundred OSL cards which I have received to date. (A list of stations ranging from Canada to Texas enclosed.) The greatest thrill I ever had in reception was when I beard 5SW, Chelmsford, England, on 24 meters at noon, January 10, 1928. It was testing with 2XAD and came in with fair volume. They with 2AAD and came in with tair vosume. They also broadcast some music, which was in turn re-broadcast by 2XAD on 22 meters. It sure was interesting to hear two great countries linked to-

SELECTIVITY WITH THE "PERIDYNE"

The "Peridyne Five" is running as I write this letter; the time is 10:00 p. m., WJZ and WEAF are both on, and my W. E. speaker is bringing in WJR, with no cross-talk, and plenty of volume. I just came away from WBBM and WLS. (now get me right); WBBM is along-side of WEAF. dials, and still I cut out WIIN clean on one side, and cut out WMCA on the other. Some selec-tivity! I also bring in WSM, WBS, KMON WBAL, any time from 8:00 p. m. daily. Remem-ber, I am going through the New York local sta-tions all the time.

Now let's get back to the set itself; what a "howling success" it was the first time I turned it on. My better half thought the house was is on. My better half thought the house was coming down; but, after gabring with the set for some of the set o

ANOTHER "PERIDYNE" ENTHUSIAST

Editor, Rabio News:
Recently I constructed a "Peridyne Five" receiver, and an now taking the liberty to say that
you have in no way overemphasized the importages and desirability of veriable-global tunions. tance and desirability of variable-shield tuning.

Having stood in awe of shielding in general, I was greatly delighted to find that it is certainly easy to balance a tuned R.F. circuit to its maxi-





Radio's largest kit supply house ESTABLISHED 30 YEARS

> ALL THE LATEST 1928 KITS! HAMMARI JIND 222

Shield Grid-4-Tube Set SHORT WAVE RECEIVER as described in Radio News Price on request

Colle and Shields in Stock "B" Eliminator and Power Pack Parts SET BUILDERS-Send for Our Handy CIRCUIT BOOKLET and CATALOG

Just Off the Press M & H SPORTING GOODS COMPANY 512 Market Street Philadelphia, Pa.



while learning COVNE ELECTRICAL SCHOOL Est.

LOOK!! IT'S FREE!!

DEALERS AND PROFESSIONAL SET BUILDERS
Your BIG NEW 1928 Catalog is NOW READY!
Contains Nationally Known Parts and Kits Send for it New! It's FREE!

S. HAMMER RADIO CO. Brooklyn, N. Y.

iminators, G. E. Bulb, 4 taps, for res capacity. Silent, unfailing. Steel ca \$9.50; fifty-five milliamperes, 5 tap pere SILITE chargers, \$9.00. Rectifi atalog. "A" Eliminator, 2 amp. \$16.50 ro-Chemical Co. of America, Ind

# OPPORTUNITY AD-LETS

es columns.

Ten per cant discount fee à insure twenty-two cents a word for each insertion. Ten per cant discount fee à insure, 20 per cent discount fee control of the con

CIRCULATION LARGER THAN THAT OF ANY OTHER RADIO PUBLICATION EXPERIMENTER PUBLISHING CO., INC., 230 Fifth Avenue, New York, N. Y.

#### Agents Wanted

ilg Meney and fast sales. Every owner buys g lials for his auto. You charge \$1.50; make \$1.33. Te-ers daily easy. Write for particulars and free sampl erican Monogram Co., Dept. 133. East Orange, N. Guaranteed Gesuine Geld Leaf Letters anyone can put on are windows. Large profits, cromous denand. Free mples. Metallic Letter Co., 422 N. Clark, Chleago.

\$40.60 Suits for \$23.50! All one price. Union-made, g about seiling clothing. We guarantee your store are honest and willing to work. Write at

# Business Opportunities

Ways to Increase Increas. 96-page book "Spore-Money Handbook" centains 67 practical and complete to operate spareline business. For overyone who more money. Price only 50c. Constad Company, 210 Fifth Acessue, New York,

ree Book. Start little Mail Order business. Hadwil, 74 Cortlandt Street, N. Y. ets wanted to advertise our goods and distribute free es to consumers; 50c an hour; write for full par-rs. American Products Co., 1502 Monnesth, Cin-L, Ohio.

#### Chemistry

Chemistry at Home. Dr. T. O'Co our full-page ad on page 1843 lostitute of New York, 16 E

#### Correspondence Courses

Detectives Detectives Needed Everywhere. Travel. Experience un cessary. Particulars free. Write, American Detecti-ratem, 2190 Breadway, N. Y.

Electricity

Electric Fun! Seventy stunts, 110 volts, \$1. Cooperco,

For Inventors Inventions Commercialized. Patented or Unpatented

#### Help Wanted

per menth in your home, folding and real.

We furnish everything. Particulars and Adams Mailing Service, K-1292, Greenfield,

#### Help Wanted, Instructions

Earn \$25 Weekly Spare Time, writing for 2 d Magazines. Experience unnecessary. Copyri-flow to write for Pay" Free. Press Report 2, St. Louis, Mo.

Learn Chemistry at Home. Dr. T. O'Coner to our full-page ad on page 1945 Institute of New York, 16 E. 38th

Practical Radio is unusually successfully taught by Kay Instrument Co. Students study at home, us of radio and cam big money. Railway Exchange II., Portland, Oregon.

#### Male Help Wanted

representative to do missionary work ufacturers in New York City territory, i idea of radio designing and engineering iculars, such as experience and reference Co., Inc., 1000 Clinton Av., N., Boche

#### Miscellaneous Inventions Commercialized, Patented or Unputer

Save Mency at Home. You can build many home ties yourself, such as furniture, kitchen utensils, of the material, etc., thus saving many dollars. All con-mitted in the material of things given in 1st the material of the saving many controlled shine Co., Inc., 220, 17th Avenue, New Yorks

#### Musical

Play Plane by Ear. A sound system. Booklet Free.

#### Old Money Wanted

Old Maney Wasted. Do you know that Coin Cellectors of up to \$100.00 for certain U. S. Certis', And high entiums for all rare cediess? We buy all Rinds. Send 4c r Large Celn Felder. May mean much prefit to you. unismatic Co. Dept. 112, Ft. Worth, Yes.

#### Old Coins

Old Coins. Large Spring selling estalogue of coins for sale, free, Catalogue cuoting prices paid for coins, lee William Hessieln, 191 K. Treescott St., Boston, Mass.

#### Patent Attorneys

Patents-Send for form "Evidence of Conception" to igned and witnessed. Form, fee schedule, information for annatier and Allmine, Registered Patent Attorneys, inited States and Canada, 259 Ouray Side, Washingth

Patents—Send drawing or model of your invention 5 necination and instructions. Advice and hocklet fre-phet references. Best results. Presuptness assure-tion E. Colesson, Patent Lawyer, 724 9th Street, N.W. usingsten. Dec.

Patent Sense-Valuable book free. See Lacey's ad, page 050. Lacey & Lacey, 631 F. St., Washington, D. C. dtabilided 1859. Patents secured. Easy terms. Inventors Service Bureau, Box 1648, Washington.

Patents Inventions Commercialized. Patented or unpatented

#### Postage Stamps

Stamp Cellectors—Phillips Monthly Bulletin (illustrate offers over 2,000 special bargains, sets, packets, sing stamps, etc., each issue. Free. Phillips, Box 10: Hartferd, Com.

Printing Outfits and Supplies

Multigraph typewritten letters sell anything. Two does thousand. Miscellaneous printing. Mover Rev Co.

Printing, Engraving and Multigraphing

#### 200 Letterhoads and 100 Envelopes, \$1.10, postpaid. Radio

Are you making money in radio? If not, send for oblet. Co-Operative Radio Doctors, Dept. N, 181 Essex Radie treuble finder. Log and Station Book Dictionary stoald, \$1.00. Chester, Box 494, Ovster Ray, N. V.

#### Radio Equipment

Direct Fastery Sale. Wholesale prices. Trecomplosis arings. Selling direct is you. Here are sense of our complex selling direct is you. Here are sense of our complex selling in the selli

#### Salesmen Wanted

A paying position open to representati Take orders shoes, honlery, direct to weare Permanent. Write new for free book, "Tanners Shoe Mfg. Co., 873 Sc. C. St., B

#### Scenery to Rent

World's Most Beautiful settings for operas, plays, min-strels. Amelia Grain, Philadelphia.

Song Writers Song-Peem writers. Address Monarch, 236 W, 55th

Sang Peem Writers spldress Hibbeler, DTX, 2104 N.

#### Telegraphy oth Morse and Wireless

#### Wanted to Buy

Full Value Paid for Old Gebl, Jewel

readings that create their own static. I know of a C10 super, for instance, with the B return for the 171 shunted around the milliammeter; 28 ma. reading on WJZ, and a slight turn of the rheostat will run the meter to 50 on a less powerful station, cable makes a good condenser for interferarticle as with a condenser, and solder a ground wire on the armor, being sure to tape the ends not in use. It will stand 220 volts A.C. for a lifetime and not blow.

I keep reading in your columns about constant reception of Australia and Japan. There is no reception of Australia and Japan. There is no kick in being in a location where DX comes through night after night. Last night I logged KFRC, San Francisco, which has never before been heard in this locality. Another feather in my p. My DX turns come in getting stations when by are hard to bring in; and this does not in-fere with our regular radio programs. I have they are hard to oring in; and this uses not in-terfere with our regular radio programs. I have had several hopeless tries for Australia; even though I know there isn't much chance before next March, and I really hope to get them at that time.

HERRERT COX.

(Apropos of this blanketing of stations, facts observed by station engineers seem to indicate that there is a station interference which is not due to there is a station interference which is not due to heterodyning, or to straying from frequency, but which is due to high power. This has been no-ticed between stations 20 kilocycles apart, more strongly than between those separated by but a single channel. Investigations are now being made

#### EXCHANGE OF NOTES

Editor, Ranto News: I would like to correspond with fellow experi-menters in radio. I am interested in the following and have notes on hand: distance-getting crystal and have notes on hand: distance-getting crystal sets with volume, underground antenna and counterpoise, elimination of aerials, tuned devices for light-socket astenna, 110-volt tube sets, automobile radio equipment and results. I will exchange leters and notes with any that are interested, for mutual radio progress. LESLIE CARPENTES, 111 LOWIN ST., Burkington, Vermont.

Editor, RADIO NEWS: Idn a young reader of your magazine and a short-wave radio ham, owning a poor short-wave receiving set. I want to exchange letters with amateurs in your country. introduce me to the earnest amateurs,

S. HANDA 56 Kitamisufi-machi, Arabusa, Tokio, Japan.

#### Radio News Laboratories

(Continued from page 1037) POWER-CONE UNIT

POWER-CONE UNIT
The power-cone unit, submitted for test by the
Fanspeaker Radio Company, 199 Fulton Street,
New York, N. Y., employs a powerful electro-magnet instead of the customary permanent magnet used
in most speaker units. This allows the use of relatively-long air gaps; thereby eliminating all possibility of chattering, even when the speaker is possibility of chattering, even when the speaker is working in connection with the most powerful of radio receivers. The electromagnet draws 0.3



ampere; this current is supplied either by the 6wolt storage "A" battery or from a trickle charger, which is operated from the 110-volt A.C. line. The entire construction is large and rugged. entire construction is large and rugged. The entir is shaped to fit into the average cone speaker, and employs a balanced armature. The coil is layer wound and insulated, to withstand voltages up to 200 without using special protective devices. This unit is an excellent reproducer where volume and

AWARDED THE RADIO NEWS LABORA-TORIES CERTIFICATE OF MERIT NO. 2262.

#### Wash Your Aerial's Face Occasionally

A FTER a receiver has been in operation for sometime, it will generally be d that reception can be improved by The best overhauling the antenna system. method, of course, is to put up both a new wire and new insulators; although carbon tetrachloride can be used very effectively for cleaning the insulators. It will be found in some cases, that simply cleaning the soot off the insulators will cause material improvement in the reception.

# An Experimental Push-Pull

WHEN experimenting with push-pull obtaining the correct transformers at short notice. Two ordinary audio-frequency transformers, if of the same type, can be used by connecting their primaries and secondaries in series to form an emergency transformer for this purpose. The con-necting wire between the two secondaries should be used as the center tap; the two transformers so connected are used on the input side of the circuit.

#### Higher Value Rheostats

are Advisable
WHEN 201A-type tubes are used as
detectors, it is advisable to use a filament rheostat of about 30 ohms; because although these tubes are not very critical to changes in filament voltage they are most sensitive at one particular point. A 6-ohm rheostat does not permit the fine regulation of voltage that is obtained with one of higher resistance; in some cases the point at which the tube operates most efficiently is much lower than the rated voltage,

#### LOCATION UNSUITABLE FOR A SUITABLE RECEPTION

First Mouse: "So you're not going to be married here at Station WBQY? Don't you think this nice pleasant basement is suitable for the wedding?" Second Mouse: "No. indeed! I don't

think that any self-respecting mouse should marry beneath her station."



-The Wireless Constructor, London,

# CONVERT Your Set to A.C.!

with the new KARAS A.C.Former

Easy to do-No Remising !



Armazing New Accessory
This manign new kaza accessory, the Ac-Former,
Table Image new kaza accessory, the Ac-Former,
Cable Ilanese or similar harmeses now available.
Cable Ilanese or similar harmeses now available,
now and the same of 
Banish Batteries Forever

Banish Batteries Forever
The Karsa Ac-Forner lanishes lattreis forever. No need for A batteries, Chromer, relays of C hatteries, Chromer lanishes lattreis, Chromer lanishes lattreis, Chromer lanishes lattreis, Chromer lanishes lattreis, Chromer lands lattreis, Chromer lands lattreis, Chromer lattreis, Lat

Mail Coupon for Information

The coupon below brings full information on how you can convert your set to A. C. with the Karas A-C-Former. We sell you every detail—send you complete data. Fill out and mail today. KARAS ELECTRIC COMPANY

4038-C North Rockwell Street, Chicago, Ill.

KARAS ELECTRIC COMPANY 4035-C North Rockwell Street, Chicago, III. Send me complete data on how I can convert my receiver, Media No. having tubes, to A. C. coperation, as advertised in Resido Nons.

Name.... Street Address.....

WHOLESALE RADIO CATALOG

THE HARCO COMPANY The HARCO CO. 1259 02/10-12-10

PATENTS Protect your inventions today. for illustrated nates. and sketch sheet and terms free BRYANT



# Know your Radio Repair your Radio Set yourself--it's easy!

No matter how much or how little you know of your radio receiver, this new "Radio Trouble Finder" book is going to be a big help.

It explains the common and special faults of all the standard receivers of to-day; tells how to recognize instantly, by various methods, where the trouble lies and also gives special simple tests by which you can determine what is wrong with your receiver. Then for each particular fault there is explained the proper procedure for correcting it.

Book Contains 64 Pages Size, 6 x 9, Illustrated Handsome 2 Color Cover

he bought the

25c the copy

Sold on All Newsstands

THE CONSRAD CO., Inc.

230 Fifth Avenue

New York, N. Y.





# 112 Kilocycle

# **Amplifier Catacomb** Screen Grid Tubes

NOW Silver-Marshall offers for immediate delivery the famous 112 K. C. time signal amplifier catacomb, improved and refined to take full advantage of the tremendous amplification possibilities of the new screen grid R. F. amplifier tubes. Every experienced fan and professional set builder knows the

remarkable efficiency of the famous S-M 440 absolutely accurate peaking, and perfect uniformity, and the new 440-SG amplifier, with 1 is high ampetentions, stooderly accurate pooling, and perfect uniformity, and the see 440 SG form from Annu of the International Conference on the Conferenc .05 ampères, 1.53 voits is at only o miliamperes and 4.7 voits of (a.y.) outcery for operation. As unterly concerning the consumption is so low it may be operated on batteries, yet no finer amplifier can be had for use wherever a sharply tuned long wave amplifier is needed. Unconditionally guaranteed against mechanical and electrical defects, the 440-SQ amplifier catacomb stands unequaled in the long-wave amplifier field. Price \$40.00, ready to use, less tubes.

#### All Your "A" Power for \$5.00

That's the story—on matter what your set, you can drow your A batteries and priced at \$5.00. This transformer supplies all "A" power to your present set by priced at \$5.00. This transformer supplies all "A" power to your present set by using a Nandi, Eby, or Carter A. C. this harmes, which enables you to insert A.C. tube in your present bettery at without a single shange to the set. Then the top to the present the A battery and charger, or expensive twenty to forty dollar A





Let Your Ear Be the Judge

A better transformer than the SAI 200 cm<sup>2</sup> be made. It has the hereiret core—it has the control of the said of th

S-M 220's are unconditionally guaranteed to be the finest audio amplifying units available. Buy a pair—let your ear be the judge, and if you've ever heard anything finer you can return them for refund. That's fair enough, isn't it?

The S-M 220 Transformer is \$8.00, and the S-M 221 is \$7.50.

Silver-Marshall, Inc. 848 W. Jackson Blvd., Chicago, Ill. SILVER-MARSHALL, INC. 848 W. Jackson Blvd., Chicago, III.

I enclose 10c for which please send me full in-formation on quality audio amplification, power supply equipment, the new Shielded Grid Sixes, Universal All Wave Tuners, and the 440-8G. I enclose 25c for complete instructions and blue prints for the Shielded Grid Sixes. I enclose 25c for instructions and blueprints for building the All Wave Tuners.

Name	ú													٠	*	٠	•	ä	٠
Address																			
Cuy										S	N	ı	e						

# A BATTERY ELIMINATOR

# Set Owners – Here's Electric Operation

Why everybody wants electric operation— Simply because it forever releases the set owner from the chore of charging and replacing batteries, and permits uniformly better reception.

How to get it-the next question.

If you own a battery-operated set, the answer is simple. Any good "B" unit and an ABOX "A" Eliminator, will electrify your present set. Think of it—no change in tubes—no change in set wiring.

Don't confuse ABOX with so-called "socket power units." ABOX contains no battery, but is a true electric device that will make your set "Electric" in every sense of the word.

Why deny yourself the convenience of electric operation any longer—the endorsement of over 100,000 users is your guarantee.

Send for circulars and free reprints of recent construction article on Abox "A" "B" "C" Eliminator and power amplifier. Use the coupon.

THE ABOX COMPANY

215 No. Michigan Avenue, Chicago, Illinois Please send me circulars and free reprints of construction article on ABOX "A" "B" "C" Eliminator and Power Amplifier.

Name .....

Address

Check here and attach to your letterhead if you are a dealer and want window display material and supply of circulars



G-Volt Abox Eliminator This model will operate any set using eight or less standard 6-volt tubes. Not necessary to change set wiring. Over 100,000 of

\$32<sup>50</sup>



4-Volt Abox Eliminator A new model for sets using 4-volt tubes. Fits Radiola battery compartment. Size 8¾ in. long, 4 in. wide, 6¾ in. high. Output—6

\$27<sup>50</sup>

All Prices Slightly Higher on West Coast

The Abox Company