

Equipped with adjustable unit

A matchless reproducer harmonizing with the most refined surroundings. Mahogany sides and top, of rich piano finish, it rivals in rare beauty the highest priced Cabinet models. In tone quality and volume it has no equal regardless of price.

Wherever there are ears that hear there is a Tower Quality Product to Fit your Taste and Pockethook.

SOLD BY GOOD DEALERS FROM COAST TO COAST

TOWER MFG. CORPORATION 98 BROOKLINE AVE. BOSTON, MASS









WORLD'S GREATEST LOUDSPEAKER VALUES

RADIO NEWS

Publishers of "Radio News," "Science and Invention,"
"The Experimenter" and "Moter Camper & Tourist."
Editorial and General Offices: 53 Park Pl., New York City

H. GERNSBACK, President. S. GERNSBACK, Tressurer R. W. DEMOTT, Secretary, MEMBER: AUDIT BUREAU OF CIRCULATIONS



VOLUME 7

CONTENTS NOVEMBER. 1925

NUMBER 5

In Our Next Issue

The Resenerative Interflex. A further development of the new real single-control radio receiver circuit developed by Mr. Hugo Gernsback. To the good features of the first designs is added that of regeneration.

Is Lightning A.C. or D.C.? A much mooted question the present writer, Henry Hull, has some ideas really worth noting.

Multiple Grid Vacuum Tubes. Multi-grid vacuum tubes have attained wide popularity in Europe, but are practically unknown here in America among the B. C. L.'s. An article by Theodore H. Nakken describes the application and use of these highly efficient tubes.

A New Phenomenon of the Aurora Borealis.

The renowned Aurora is continually doing things to mystify us. Here is a new one that the writer has discovered, dealing with the effects of the Aurora on long telephone lines. . . .

The KIROVOX. An exposé of an instrument claimed to be a panacea for all

In This Issue

The Raytheon Rectifier. By Joseph Riley 613 Sound Photographs and Their Reproduction. By Theodore H. Nakken 614

The Counterphase Circuit., 616 Straight - Line Frequency Dials By Sylvan Harris 618

The Four Types of Audio Amplifiers. By Sylvan Harris 620

R.F. Selector and Radiation By B. B. Minnium 624

Activities of the Radio News' Laboratories. By the Director 626

With The Amateurs. The Radio Beginner. By A. P. Peck 628

Awards of the \$50 Radio Wrinkle Contest 630 Radiotics 632 Standard Hook-Ups 633

New Radio Patents. By John B. Brady 635 RADIO NEWS LABORATORIES 636

Correspondence From Read-

I Want To Know. By R. D. Washburne 639

By Hugo Gernsback 585

Radio and Movies Now Radio With the Rice Amazon Expedition. By T. S. McCaleb 588

Editorial.

The Inventions of Reginald A. Fessenden Radio - Controlled Automo-bile. By Herndon Green 592

Cover Picture Prize Contest 593 WRNY Starts Broadcasting By Charles D. Isancson 599

Plastic Radio By the Kluth System. By Dr. Alfred Gradenwitz 601 The Life and Work of Lee

Hot Cathode Metal Vapor By Dr. C. B. Bazzoni 604

A Crack 40-80 Meter Set By E. W. Thatcher 605 International Radio 606 Esperanto Broadcast Les-

By James Denson Sayers 607 New Designs In Radio Receivers.
By G. C. B. Rowe 608

A New Two-Range Re-ceiver. By Sylvan Harris 610

Static and Weather Fore-casting. By S. R. Winters 612

New England Advertising Representative T. F. Magrant, Park Square Building, Boston, Mass.

RADIO NEWS is for usin at all necessitable in the United States and mesons agents S. I. Wise E. G., of Pines Vert., Astroncy, Beigings, HOW TO SUBSCHIME FOR HADIO NEWS. Said your pane, and ministen to Experimentar Publishing Co., 30 Fars Planc, Now York, Man (1997) And Co. (1997) And Co. (1997) And Co. (1997) And CO., the EXTERIMENTER and MOTOR CAMPER & TOURIST. WHIS EAVIS AND TRAINS. The SUBSCRIPTION rate for HADIO NEWS is \$ point. II numerous actions are a consistent of the companion of the compan CHANGE OF ADDRESS. Neify us at fer in scheece as possible. It requires serious veits to make an address change on our record. Always vittle coarry.

ON EXPERATION of year calculations of year calculations of year calculations of a serious control of the coarry of the

Detroit Advertising Representative Roy Buell, Donovan Bidg., Detroit, Mich.



Gets 200 to 600 meter Stations coast to coast" "A great big beautiful set"

Vow only



ilt like - looks like - performs like a \$200 set! sered Brose



Notice!

The Powerful New

MAHOGANY CABINET FIVE TUBE SET IN BEAUT

Let the testimony of its many users everywhereas voluntarily reported to us in writing-convince you that a Miraco Ultra-5 actually is unsurpassed for selectivity, long dis-tance range, clear tone,

loud speaker volume and beauty—combined with economy and simplicity of times the price. Send coutimes the price. Send couproof and reports of users

which leave no doubt that the Miraco Ultra-5 gets programs coast to coast as well as from foreign countries.

Completely built, carefully tested and

factory guaranteed by one of America's oldest and most successful makers of quality sets, the Miraco Ultra-5 illustrated above (latest im-proved model for 1926) ity, long distance reception, ch and volume have been amazi increased—"B" battery cons



OtherMiracoLong Distance Sets \$1375 up

All the Proof you want is waiting for You!

ad coupon

MIDWEST RADIO CORPORATION

Pioneer Builders of Sets

404-H East Eighth Street Send free literature, SPECIAL OFFER and all par () Agent () User () Dealer.

ADDRESS



AGENTS!

XYZ

Y. M. C. A. Radio Institute ... 646

Yaxley Mfg. Co............650, 724

Radiall Co.692, 734

Radio Association of America...656

Radio Cabinet Co......738

Radio Corp. of America......641 | Zenith Radio Corp................651

Page |

Page

INDEX TO ADVERTISERS

Page

	The Control of the Co	SPRING -	
A	Cutler-Hammer Mig. Co. The	I The second	Radio Foundation, Inc688
	Cutler-Hammer Mig. Co., The, Back Cover	TO PERSONAL	Radiogem Corp., The718, 749
Aalco Radio Labs644		Jacobs, C. E	Radio Industries Corp719
Acme Apparatus Co	D	Jewell Electric Instrument Co690	Radio Institute of America 741, 747
Aeme Products Co733		Jones Radio Mig. Co., Inc.,	Radio Mast Co718
Aero Products, Inc741	D X Instrument Co682	Jos. W718	Radio Parts Co
Aerovox Wireless Corp716	Daven Radio Corp656		Radio Specialty Co715
Alden Mfg. Co	Dayton Fan & Motor Co., The 693	K	Radio Units, Inc. 740
All-American Radio Corp673	Delta Electric Co694		
Allen-Bradley Co., 752, Inside Back Cover	DeWitt LaFrance Co., Inc706	Karas Electric Co655	Randolph Radio Corp., 642, 662, 721, 732, 738, 743
	Diamond Electric Specialties	Kelleradio, Inc	642, 662, 721, 732, 738, 743
All Radio Co644	Corp	Kellogg Switchboard & Supply	
Ambassador Sales Co734	Corp711	Co	Rola Co., The
American Appliance Co676	Duplex Condenser & Radio	Kimley Electric Co	
American Bosch Magneto Corp., 580, 581, 699	Corp720	Kinley Radio Co732	s
American Electric Co644		Klosner Radio Corp733	8
American Hard Rubber Co743	E	Kodel Radio Corp., The,	Saturn Mfg. & Sales Co., The731
American Radio Engineers678		578, 579, 737	Saal Co., H. G
Amplion Corporation of America 678	E. I. Co696	Korach Radio Co652	Scanlon, Everett . 731
Amsco Products, Inc662	Eagle Radio Co	1 20 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	Service Battery Co 717
Andrews Radio Corp679	Economy Radio Sales Co654	L	Shontz & Co., Inc., H. B., 746
Antennaphone Co	Electrad, Inc	L	Silver-Marshall, Inc. 700
Apex Electric Mfg. Co744	Electrical Engineers Equipment	Lancaster & Allwine	Simplex Radio Supply Co. 740
Arrow Battery Co	Electrical Products Mig. Co666	Lincoln Radio Corp676	
Atwater Kent Mig. Co647	Electrical Research Laboratories .735	Lincoln Typewriter Co., Inc648	Smith Typewriter Sales Corp 706
	Electric Specialty Co700		Southern Toy Co690
S HEET IN THE PARTY	Plantala Ctorona Pottora Co		Spartan Electric Co744
В	The	M	Standard Aerial Base Co747
B-C-L Radio Service Corp740	Elgin Radio Supply Co726	M & M Co., The	Standard Radio Co
B-C-L Radio Service Corp40	Elite Stationery Co728	MacFadden & Co., Inc716	Star-King Co648
Bakelite Corp	Erie Fixture & Supply Co682	Mack Laboratories644	Starrett Mfg. Co706
Barawik Co	Evans & Co., Victor J718	Manhattan Knitting Mills 650	Sterling Mfg. Co., The737
Barkelew Electric Mig. Co., The.661	Express Body Corp708	Martin Co., The Glenn L658	Super Products Co652
Bastian Bros. Co		Martin-Copeland Co 686	Sylvania Products Co701
Belden Mig. Co681	p	Midwest Radio Corp571	
Bell Mfg. Co		Miller Rubber Co., of N. Y723	T
Benjamin Electric Mig. Co694	Fahnestock Electric Co658	Montgomery Ward & Co683	
Black Bros. Co720	Fansteel Products Co., Inc709	Morrison Labs., Inc706	Telephone Maintenance Co642
Bluebird Tube Co670	Federal Mail Order Corp700	Mozart Grand Co., The727	Thomas Battery Co
Bodine Electric Co	Ferbend Electric Co739, 744	Multivider Co	Thordarson Electric Mfg. Co657
Boice, W. B. & J. E680	Fink, Ben W	Murdock Co., Wm. J691	Tower Mfg. Corp569
Brady, John B	Fishwick Radio Co	Music Master Corp732	Trego Radio Mfg. Co726
Branston, Inc., Chas. A680	Fitch Radio Corp703	Muter Co., Leslie F728	Trimm Radio Mfg. Co70+
Brant Battery Co	Formica Insulation Co., The 675	Mydar Radio Co642	Tuerk Míg. Co
Brown Co. W. C	Frost, Inc., Herbert H739	all to bestifiction a triple of the	
Bremer-Tully Mig. Co575	Furnell Mig. Corp., The698	N	п
Bristol Co., The		ANY OWNER OF COUNTY AND ADDRESS OF THE PARTY	U
Brownlie & Co., Roland740	G	Nagel Electric Co., The W. G 646	Union Fabric Co750
Buescher Band Instrument Co648	G & S Radio Research Lab714	National Airphone Corp744	U. S. Tool Co.: Inc. 674
Butts, Inc., C. W	Gale Radio Labs652	National Carbon Co., Inc645	Utility Cabinet Co650
	Gearhart-Schlueter Radio Corp732	National Radio Instituté573	Utt-Williams Electrical Products
c	Gem Tube Co	National, State & Local Tubercu- losis Asan, of the U. S746	Co692
	General Electric Co	Norden-Hauck, Inc702	
C. E. Mfg. Co., Inc714	Goertz & Co., August712		v
California Radio Minerals664	Golden-Leutz, Inc672	0	V
Camfield Radio Mfg. Co733	Gold Seal Products Co., Inc689	Correct Concession of the Conc	Valley Electric Co646, 685
Cannon & Miller Co., Inc704	Goodman, L. W	Ohio Stamping & Engineering	Van Ashe Radio Co724
Carborundum Co., The702	Goodrich Rubber Co., The B. F. 669	Co., The	Vesco Radio Co658
Carter Radio Co712	Gould Storage Battery Co., Inc.,	Omnigraph Mfg. Co., The668	
Chaslyn Co., The652		Owen, Richard B722	
Chelsea Radio Co668	Goyer Co., The	Ozarka, Inc	W
Chemical Institute of New York, Inc	Grewol Mfg. Co741		
Chicago Electrical Devices Co739		P	Wade Mig. Co., Inc
Chicago Salvage Stock Stores682	H	With the control of the second	Walbert Mig. Co695, 713
Chicago Stock Gear Works750	Hammarlund Mig. Co654	Pacent Electric Co., Inc737	Walker Co., The Geo. W684
Clark & Tilson, Inc740	Hammarlund-Roberts 576, 577	Pacific Radio Mig. Co648	Washington Jewelry Co716
Cleveland Engineering Labs. Co., The	Hanscom Radio Devices728	Parker, C. L	Werner Radio Mig. Co., P. F., 750
The662	Hatfield & Son, H. D	Pathé Phonograph & Radio	Western Radio Mfg. Co722, 735
Colytt Laboratories731	Heath Radio & Electric Mir.	Corp	Westinghouse Electric & Mig. Co
Como Apparatus Co724	Co	Pfanstiehl Radio Co	Weston Electrical Instrument
Consrad Co., Inc., The. 730, 736, 748	Henninger Corp., A. F740	Phenix Radio Corp582, 583	Corp
Continental Fibre Co., The 720	Hommel & Co., Ludwig700	Pilot Electric Mfg. Co721	Willard Storage Battery Co653
Crain Bros. Radio Shoppe680	Hughes Electric Co., Benjamin743	Potter Mig. Co678	World Battery Co724, 728
Crescent Braid Co., Inc726	Hull & Co., S. W	Press Co., The646	X-L Radio Labs
Crescent Radio Supply Co733			
Crosley Radio Corp., The697	I	R	V V 7

Illinois Radio Co.........745, 750

Interstate Electric Co.......734

International Correspondence Schools

Crowe Name Plate & Mig. Co...642

Cruver Míg. Co......718

Culver-Stearns Mfg. Co......654

Cunningham, Inc., E. T., Inside Front Cover

Earn 50 to 200 a Week in RADIO

You can! Hundreds of ambitious men are already earning thousands of dollars in this wonderful new industry—you, too, can get your share. Mail coupon below for Free Book which describes fully the amazing money-making opportunities in Radio and tells you how YOU can earn from \$5,000 to over \$10,000 a year.

THE astounding growth of Radio has created thousands of big money opportunities. Millions of dolars were spent during the past year on Radio, and thousands of young men are needed right now to meet the everincreasing demand of work.

Men are needed to build, sell and

install Radio sets—to design, test, repair—as Radio engineers and executives—as operators at land stations and on ships traveling the world over—as operators at the hundreds of broadcasting stations. And these are just a few of the wonderful opportunities.

Easy to Learn Radio at
Home in Spare Time

No matter if you know nothing about Radio now, you can quickly become a Radio expert, by our marvelous new method of practical instruction—instruction which includes all the material for building the latest up-to-date Receiving Sets.



PAY INCREASES OVER \$100 A MONTH
I am averaging anywhere from \$75 to \$150 a month more than I was making before enrolling with you. I would not consider \$10,000 too much for the course.
(Signed) A. N. LONG, Greenburp. Pa.

DOUBLES SALARY
I can very easily make double
the amount of money now than
before I enrolled with you. Your
course has benefited me approximately \$3,000 over and above
what I would have earned had I
mot taken it.

T. WINDER, Grand Junction, Colo



PROM \$15 TO \$80 A WEEK
Before I enrolled with you I
was making \$15 a week on a
farm. Now I earn from \$2,000
to \$4,420 a year, and the work
to \$4,400 a year, and the work
to \$4,000 and I believe the
before. Since graduating a little
over a year ago, I have eago, I alway
almost \$4,000, and I believe the
silve to the service of the servi

Scores of young men who have taken our course are already earning from \$75 to \$200 a week. Merie Wetzel of Chicago Heights, Ill, advanced from lineman to Radio Engineer, increasing his salary 100% even within taking our course! Emmett Welch, right after finishing his training, started earning \$300 a month his training, started earning \$300 a month servenses. Another graduate is now an operator of a broadcasting station—PWX of Havana, Cuba—and earns \$250 a month. Still another graduate only 16 years old, is averaging \$70 a week in a Radio store.

Wonderful Opportunities

Hardly a week goes by without our receiving urgent calls for our graduates. "We need the services of a competent Radio Engineer." "We want men with executive ability in addition to Radio knowledge to become our local managers." "We require the services of several resident demonstrators"—these are just a few small indications of the great variety of opportunities open to our graduates.

Take advantage of our practical training and the unusual conditions in Radio to step into a big paying position in this wonderful new field. Radio offers you more money than you probably ever dreamed possible—fascinating, easy work—a chance to travel and see the world if you care to, or to take any one of the many Radio positions all around you at home. And Radio offers you a glorious tuture!

The National Radio Institute is one of America's Ploneer Radio Schools—established in 1914. Our course is an absolutely complete one which qualifies for a government first-class commercial license. It trains you for bigger paying jobs in Radio.



Send for FREE RADIO BOOK

Learn more about this tremendous new field and its remarkable opportunities, Learn how you can quickly become a radio expert and make big money in Radio.

We have just prepared a new 32-page booklet which gives a thorough outline of the field of Radio—and describes our amazing, practical training in detail. This Free Book, "Rich Rewards in Radio," will be sent to you without the slightest obligation. Mail coupon for it note!

For a short time we are offering a reduced rate to those who enroll at once. Act promptly and save money.

National Radio Institute Dept. 13NB Washington, D. C.



NATIONAL RADIO INSTITUTE, Dept. 13NB, Washington, D. C.

Pl	ease s	end m	e with	tout the	slight	est obligation
our	Free	Book,	"Ric	h Rewa	rds in	Radio," and
ull	detail	s of	your	special	Free	Employmen
ervi	ce. 1	'lease	write	plainly.		

avice.	Piense	write	piainty.	
ame				

RADIO NEWS READERS' BUREAU

Time and Postage Saver

I N every issue of RADIO NEWS you undoubtedly see numerous articles advertised about which you would like to have further information. To sit down and write an individual letter to each of these respective concerns, regarding the article on which you desire information, would be quite a task.

As a special service to our readers, we will write the letters for you, thus saving your time and money.

Just write the names of the products about which you want information, and to avoid error the addresses of the manufacturers, on the coupon below and mail it to us. If the advertiser requires any money or stamps to be sent to pay the mailing charges on his catalogue or descriptive literature, please be sure to enclose the correct amount with the coupon.

We will transmit to the various advertisers your request for information on their products.

This service will appear regularly every month on this same page in RADIO NEWS.

If there is any Manufacturer not advertising in this month's issue of RADIO NEWS, from whom you would like to receive literature, write his name, address and the product in the special section of the coupon below.

TEAR ALONG THIS LINE

DO NOT USE TH	HIS COUPON FOR TECHNI	CAL QUESTIONS	If Catalogue
NAME	ADDRESS . (Street — City — State	List here specific article on which you wish literature.	-4 somelet
100			2/4
Lea this space if you derive i	nformation from a manufacturer w	hose advertisement does not appear in thi	s month's issue
se this space if you desire i			
NAME	ADDRES (Street — City -	SS – State)	
NAME	ADDRES (Street — City –	SS — State)	
NAME	ADDRES (Street — City –	- State)	
NAME Your name	ADDRES (Street — City –	- State)	

FARTHER AHEAD THAN EVER



B-T EUPHONIC

"Pleasing to the Ear"

In addition to surpassing merit as an audio amplifier, the B-T "Euphonic" brings to Radio the first constructional improvement in many years. Movable legs that snap into place in either position allow mounting either side up, above or below your baseboard. The result is shortened leads—no crossed wires and consequent elimination of the howling and distortion often caused thereby. The Euphonic will add luster to the already shining shield of Harry A. Bremer, its designer, who built his first wireless apparatus just 20 years ago.

Two Radios 2.2 to 1, \$5.00 5.9 to 1, \$5.75



The B-T Tuning Control

The Tuning Control is another original example of B-T ingenuity. Better action and better appearance tell the story. Reads in degrees, wavelengths or call letters. Price \$2.50



B-T Lifetime Condensers

All the world knows and recognizes the outstanding superiority of B-T "Lifetimes" Concipinal design. The bearing alone is enough to win your approval. None other even approaches it.

L. 600,0025 (for B-T B an ke wunt SL-600,0025 (for B-T B an k



The Original B-T Nameless Receiver

The original B-T Nameless was about two years abend of its time. It's only now that the correctness of its principles are coming to be properly appreciated. Thousands will build the Nameless this season, and tens of thousands will build and enjoy the unequalled "Counterphase". Six tubes, including three of radio frequency, with only two tuning controls. Long-distance loud-speaker reception with short indoor antennas.

Sold as 5 or 6 tube kits or complete receivers.



The B-T Universal Socket fits both large and mail UX tubes and all UV except the old tyle 199 without an adapter.
The contact tells its value. Look once and ou'll choose it. Price 75c

you'll choose it. Price 75c

☐ Send free circulars

□ Send "Better Tuning," 10c enclosed
 □ Send information on complete receivers.

Name

The oversize 8th Edition of "Better Tuning" is the best dime's worth of radio information you ever read. Send for it today,

reet

State

BREMER-TULLY MFG. CO. CANAL AND HARRISON STS. CHICAGO ILL

Approved by ~ ten leading manufacturers

THE new Hammarlund-Roberts receiver is the united achievement of ten leading engineers, endorsed by ten of the best-known radio manufacturers. No one man's or one group's conception of five tube possibilities but the composite of the leaders' convictions.

This concentration of the leaders upon one purpose—the perfection and intense application of tried and proven radio principles—has produced new results. Results so vital and so valuable that they put the Hammarlund-Roberts far beyond your expectations of performance.

In designing this new standard of efficiency, the consulting engineers had at their disposal the finest parts the market affords—regardless of cost—they were not handicapped in building to a price.

The outstanding merit of the original Roberts Circuit was its use of regeneration (the equivalent of two stages of radio frequency) in combination with proper tube neutralization. This

hitherto unattainable combination provided maximum range, sensitivity, perfect tone and easy, non-critical tuning. It banished the former bugbears of radiation. Ten of the country's leading engineers collaborated on still further refinements and elaborations of this popular circuit. This union of principles, opinions and experiences has clarified hitherto cloudy points. The ideals of all these experts have been pooled in this one model radio receiver.

These ten leading manutacturers offer to the American public greater value than ever before. A radio receiver constructed throughout of the latest, most efficient part designs at a price within the means of every one. A five tube receiver that equals the Super-Heterodyne in selectivity and volume. A receiver so simple in design that anyone can build it from the instructions in the "Hammarlund-Roberts Construction Book." You will wonder at this new simplicity; this new efficiency; this new saving.

Write for this most complete book.

Associate Manufacturers

All-American Radio Corp. Hammarlund Mfg. Co., Inc. Alden Manufacturing Co. Radiall Company Carter Radio Company Dubilier Condensers Union Radio Corp. International Resistance Co.

HAMMARLUND-ROBERTS, 1182-C Broadway, NewYork

ROBERTS

Write for this most complete book giving complete details on assembling, wiring and operating the Hammarlund-Roberts receiver. Moss to Band the
Hammarlund
ROBERTS
ROBERTS
RECEIVER

25c



\$60 85 Cabinet Extra

The All-American Radio Corp. contribute the Rauland Lyric Transformer to the efficiency of this new receiver.

The Emblem of Worth in Radio

The Best that Radio Offers



If the LOGODYNE Big Five excelled only in performance it would not be a KODEL RADIO.

But combining as it does the ultimate in good performance, a tone as mellow and true as a rare old music instrument, a cabinet artistry worthy of the old masters the LOGODYNE Big Five expresses the perfection required of the entire KODEL RADIO line-the best that radio offers.

Free Send for the new edition of our free booklet "The Secret of Distance and Volume in Radio". Gives helpful interesting information on radio operation.

THE KODEL RADIO CORPORATION 501 East Pearl Street Cincinnati, Ohio

WKRC









KODEL "Gold Star" Models— Radio's greatest set values; Three Tube "Gold Star" Model, \$30

Two Tube "Gold Star" Model .. \$20 One Tube "Gold Star" Model... \$12 "Gold Star" Crystal Set \$ 6

Owners of Kodel Broadcasting Station WKRC on the Alms Hotel. Send for program.



The slow 2-ampere battery charger is as obsolete today as the old one-lunger of 1903

Buy nothing but an up-to-date 5-ampere charger!

The New Improved

5 AMP A & B
GOLD SEAL
HOMCHARGER

\$1950



Charges 150% Faster!

Better Because:-

New micrometer adjustment, hinged lid, and carrying handle. No bulbs to buy or break.

Can be used anywhere—contains no acids or other harmful liquids to spill.

Approved by underwriters trouble-proof, shock-proof and fireproof.

Beautiful cabinet in maroon and gold.

Free Write for new edition of our instructive booklet on radio operation "The Secret of Distance and

It takes only one-third as long to charge a battery with the New Improved COLD SEAL HOMCHARGER. The big, healthy 5-ampere charging rate does away with the long bothersome waits that were necessary when the obsolete slow 2-ampere charger was the best that radio offered

The New Improved GOLD SEAL HOMCHARGER charges 150% faster—will charge your battery overnight! And it charges both A and B batteries without additional equipment.

Don't let anybody sell you a slow 2-ampere charger they are obsolete—out-of-date. You need a modern charger with a full 5-ampere rate. Insist on the GOLD SEAL HOMCHARGER.

The Kodel Radio Corporation

501 East Pearl Street Cincinnati, Ohio

WKRC

Owners of Kodel Broadcasting Station WKRC



Radio News for November, 1925

RADIO

BOSCH RADIO BACKGROUND

The American Bosch Magneto Corporation is in position to build radio products of unapproachable quality. This organization comprises skilled electrical engineers, workmen experienced in precision manufacture, a world wide service and distributing organization all backed by plant, tools and equipment especially designed for the manufacture of precision electrical apparatus.

Bosch quality is world famous.

This is the incomparable background of Bosch Radio Products the Amborola Receiving Set, the Ambotone, and the Junior Ambotone Reproducers—all reflecting Bosch quality in design, manufacture and performance.

A M E R I C A N B O S C H
MAGNETO CORPORATION
SPRINGFIELD - MASSACHUSETTS



A Lacault Development

Tho the radio-wise, the mere fact that the designer of this new kind of receiver is R. E. LaCAULT is a sufficient recommendation. This famous technician has frequently lead the forward march of radio. His popularity is founded on the recognition of his intense practicality. He is no mere theorist! He never misleads, never entangles with useless technicalities. He perceives the requirements of the average radio user and designs in strict accordance with these practical requirements. The result is always complete satisfaction. This new type receiver is the realization of Lacault's fondest ideals of radio reception.

Specifications

Gircuit—The new ULTRADYNE Model L3- employs six vacuum tubes of the task as voll, one-quater ampace type. The first three function as radio frequency amplifiers, the fourth as detector and the last two as audio frequency amplifiers. Operation has been simplified by using automatic filament control in place of rheostats. The first two stages of radio frequency amplification are tuned while the third stage is fixed.

Selectivity—A special resistance system of stabilization prevents these circuits from oscillating a resonance points. More than this, the system causally increases the selectivity of the set without any loss in efficiency. Though the set is to highly selective, there are non-of the "critical tuning characteristics" common to so many receivers, due to the use of straight-line wave length common to so many receivers, due to the use of straight-line wave length condensers. The lever system of control provides a vernier action of a new order.

Marched Land Stouker and Amblifer Unite—Distortion has been eliminated.

by striking an equality in the impedance of the load speaker unit and the plate to filament impedance of the utils. The two work in perfect harmony with each other. The new ULTRADYNE is designed to use either an indoor or an outdoor aerial. For most purposes an indoor wite is sufficient. A section of lamp cord run around the moulding of a room is very satisfactory. Cedistrac—The calibrate 152 thinches long, 18 indees high and 14 indees deeper, Space is provided for the "B" batteries on the inside. Binding posts on the rear of the vacuum the socket subbase take the aerial, ground and "A" hattery connections which are run through holes in the back of the cabinet. The wood is a rich, bowen color, andee up of freely makepany vener and decearated with two-tone line cuttings. DCCO finished to guarantee the feel hold seeker form, is a saturary thorce color and is slowed by a small relation of the load seaker, form, is a saturary thorce color and is slowed by a medium.

Guaranteed To protect the public

Mr. Lacault's personal monograms scal (R.E.L.) is placed on the assembly fock-bolist of all genus for the scale of the sca



ULTRADYNE


PHENIX RADIO CORPORATION

of dull gold.

114 EAST 25th ST., NEW YORK

No Dials-No Panel-Built-in Loudspeaker

A New Conception of Radio

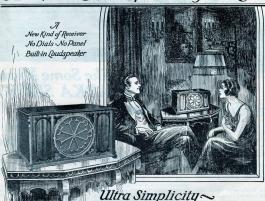

Ultra Simplicity~ Tastefully Unobtrusive

This new kind of radio-musical instrument marks the mastery of technicalities to the point where the whole range of radio's resources are literally at your instant command.

The ULTRADYNE, Model L-3, supplants the usual "laboratory machine." It is a new artistic tablepiece that makes the entrance of radio into the well-appointed home unobstrusive, inconspicuous. It represents the triumph of art over mere

The ULTRADYNE is worthy of the place of honor in the most luxurious

The ULTRADYNE, Model L-3, fulfills everything that the critically-minded have demanded of radio. Why wait any longer, why deny yourself the infinite treasures of radio? The ideal has at last been attained.

Skepticism will vanish if you will allow your local dealer to demonstrate this new modern radio receiver.

f Folder on Request

\$13500

ULTRADYNE

UENIX BADIO CORBODATION

II4 EAST 25th ST., NEW YORK

Beauty in Ione-Beauty in Design



Satisfies Every Owner-

In radio, when one selection does not please, you simply tune it out and pick up another broadcasting station. If it is a matter of unsatisfactory volume or tone in your instrument then it becomes an entirely different matter.

You have certain very definite ideas in mind as to what you want your radio to do. Will you allow us to make a few suggestions regarding a plan whereby you can settle the radio question?

Select the instruments which you think might answer. Have a demonistrating instrument brought to your home. Let each salesman, in turn, make the necessary battery connections. Let him tell you how to operate it but do all the tuning yourself.

You'll buy the instrument then, based on your own operation. You'll size up each one for

- —ease of tuning
 - -distance received
 - -volume
 - -tone
- —selectivity —price.

There still remains one very important question to settle—the matter of service. No matter what anyone tells

you sometimes little things may go wrong. The best radio salesman often knows nothing of correcting radio troubles—satisfy yourself.

Our Ozarka representative in your community will gladly put an Ozarka in your home for such a test. More than this, you will find that he is a thoroughly trained mechanic on our instrument. He has gone through a complete course of study under Ozarka Engineers, the men who designed and perfected the Ozarka.

3187 such men today can correct any trouble which may ever occur on any Ozarka instrument—more men are being factory trained daily. You wouldn't buy an instrument blindly then don't buy service the same way. Any radio instrument is only as satisfactory as the quality of service behind it.

Our Book No. 200 shows the full Ozarka line from \$75.00 to \$197.50, complete with all accessories.

A Few More MenareNeeded

In a great many counties we have the permanent and profitable business of his own because he has an instrument that will more than meet all competition. More than this, he is trained to back up his sales with the kind of service that counts.

Many well established Ozarka representatives started by giving us only their spare time—their evenings. If your county is open you can do the same.

The investment in cash is very small.

The investment in time necessary for study is considerable. It requires patience, but the results have enabled many men to get out of the salary and time clock class.

Any previous sales experience is helpful but not necessary. We can and will teach you how to sell.

Send for 64 Page Book—
"The Ozarka Plan"



This book is entirely too expensive to be sent out on postal card requests. It will be sent FREE to any man who mails the coupon below and who is really anxious to improve his condition. Tell us about yourself—ask for Ozarka Plan No. 100 and don't fall to give

OZARKA 122 Austin Avenue E

Gentlemen: Without obligation - feed book "Ozarka Instruments No. 200" and name of Ozarka representative.

Name.
Address.
City
County
State.





Gentlemen: I am greatly interested in the FREE book "The Ozarka Plan" No. 100, whereby I can sell your radio instruments. Name.

Address. City.
County. State.

EDITORIAL AND GENERAL OFFICES, 53 PARK PLACE, NEW YORK

NOVEMBER, 1925

WHO PAYS FOR RADIO BROADCASTING?

By HUGO GERNSBACK

TOW that radio has become quite stabilized, not only in the set NOW that radio has become quite stabilized, not only in the set building and parts manufacturing industries, but in broad-casting as well, we very often hear the question: "Who pays for broadcasting?" The public wonders, and asks all sorts of questions, and has all sorts of ideas. In fact, no end of rumors are afloat about broadcasting in general.

Radio broadcasting may be said to fall into two classifications: non-commercial broadcasting and commercial broadcasting. The n-commercial braodcasting is done by individuals or organizations which broadcast without direct monetary gain, although there is,

as a rule, an indirect gain of some sort.

When a newspaper or a publisher of magazines owns a broadcast station, it is usually operated with the idea of increasing the circupropaganda. If a church or educational institution is doing non-commercial broadcasting it is with the idea of gaining as many listeners as possible, in the hope that the listeners will sooner or later "come into the fold." This, in other words, is simply propaganda.

If a department store owns a broadcast station, obviously its use is simply that its listeners will be impressed by the name of the

store that operates the station.

The non-commercial broadcaster has a ticklish job, insofar as he can not put over his propaganda in a crude and undignified manner. Suppose a large department store has a broadcast station. How long would listeners stand for it if the department store were to praise its wares in almost every sentence? Nothing like this, of course, ever us wares in aimost every sentence? Nothing like this, of course, ever happens. The department stores, the newspapers and other non-commercial broadcasters are usually content just to get their publicity into the aimouncement, which may take the following form: "This is Station WXYZ, the John P, Doe Department Store. Our next selection will be—""." selection will be-," etc.

Few broadcast stations resort to the use of direct advertising f their wares, although it seems to be ethical with newspapers to or their wares, aithough it seems to be ethical with newspapers to call attention to certain news as published in such-and-such a news-paper. News, in other words, is supposed to be a different kind of commodity from a cake of soap or a pair of silk stockings. On the other hand, it seems to be ethical for broadcast stations owned by department stores to institute prize contests occasionally in which well-known merchandise is given away to broadcast listeners.

All in all, the non-commercial broadcaster has not any easy job acing him. The broadcast station is usually charged up to adverfacing him. tising by the bookkeeping department, and only a certain sum is appropriated, which, as a rule, is not exceeded. The station, having no income, cannot go out and hire artists, so all the broadcasting of the non-commercial stations must be done by volunteer artists, who themselves are broadcasting for the publicity which they get from so doing. This, as a rule, works out harmoniously. The public, on the one hand, gets an excellent program by good artists, while the artists themselves get the advertising which they need. This is the reason why the non-commercial stations do not have to resort to any great amount of "raw" advertising over the air. As matter of fact, a first-class station never does and never should. With the commercial stations, the situation is totally different. A commercial station is one which broadcasts for gain—quite frankly so. It solicits advertising from corporations and the form that the advertising takes is now well known. For instance, let us say, a manufacturer of electric batteries wishes to advertise its name to many thousands of radio listeners. The form that this advertising takes nowadays is somewhat as follows:

"This is Station WZXY, broadcasting the Everlast Battery Co Ams is Station WAAY, proadcasting the Everlast Battery Cor-poration Symphony Orchestra." The advertising is contained in this announcement and if it is repeated week after week it must sooner or later impress the listener that the Everlast battery must be a good battery, although the batteries themselves are never mentioned by name. The manufacturer of the battery knows that he must follow this up with the printed advertisement, and that the broadcast advertising is simply the forerunner to create good will and a "homey" feeling toward this particular battery.

The battery manufacturer in this case not only pays the broadcast station for the length of time he uses the station, but he has to pay the orchestra or artists as well. There is usually no fixed price for the artists or the orchestras, while there is a fixed price for broadcasting, as shown in the following paragraph. These happen to be the charges of one of the greatest commercial broadcast sta-tions in the country—WEAF, of New York.

This station charges from \$150 to \$500 per hour, depending upon the use to which the station is put, the nature of the program, hour of the day, etc. These are charges just for the one station If, however, the entire net of 14 allied stations is tied in for one program from WEAF, the charge is approximately \$2,500 per bour. This is exclusive of the cost of the entertainers and other incidental

expenditures.

It will now be seen that the commercial broadcaster has a certain advantage over the non-commercial one, in that he can pay top prices, if necessary, for talent, and on account of this the public gets an excellent program. Also, for that reason, it does not mind the little advertising which makes the broadcasting possible. in America particularly, is rapidly becoming used to this sort of thing and no longer objects to the slight advertising feature over the air, because it knows that this is a world where you cannot get something for nothing and if you wish to listen to an excellent program some one in the end must pay for it. That some one in the end is, of course, the public. There is a lot of foolishness being pandered about that broadcast

listeners do not pay for the programs. They certainly do in one way or another, sooner or later, even though they do not realize it. For instance, if you are a broadcast listener and have heard, all For instance, if you are a broadcast Instener and have heard, all summer long, the Goldettone Cord Orbelstra, and are in need of an automobile tire, sooner or later, this name will probably stick in your memory and you will ask for a Goldettone Cord 'Tre. It will therefore be seen that eventually you will pay your share of the broadcasting expense, which is as at is should be. If you derive pleasure from the excellent programs you receive night after might, day after day, you naturally do not feel that you should get all this proposed to the control of the programs of the proposed of the programs of the proposed of for nothing. When you buy a newspaper, or when you buy a magazine, you get

such publications at a reasonable cost for one and only one reason; namely, the advertisements contained in such newspapers and such publications. The reader, nowadays, knows that he could not buy phonications, the reager, nowadays, knows that he could not buy his morning paper for two cents, nor his monthly magazine for twenty-five cents, if it were not for the advertising that these publi-cations carry. The advertising, in other words, makes it possible or the newspaper and magazine to be sold at a reasonable price We do not object to the advertisements in these publications, be we know that without them we could not get such a wealth of text and editorial matter.

Therefore, if your broadcast station gives you a wealth of "text and editorial matter," meaning entertainment, music, speeches, and what-not, all free of charge, without your having to pay any money whatsoever, why object to the little advertising that of necessity must go out on the air to make such entertainment possible?

In Europe they still have the idea that every broadcast listener In Europe they still have the idea that every broadcast listener must be taxed a certain sum in order that the broadcast stations may live. That this policy is foolish is best shown by the fact that there are some 600 stations in the United States alone, while all Europe does not boast of more than about 125. Besides this, there are at least a hundred times more broadcast listeners in this country than in Europe.

Radio and Movies





The above is our illustration reproduced from the September, 1919, issue of RADIO NEWS, giving Mr. Hago Geraback's prediction made [o. 1926] decide broadcasting was known in the sames that we have it today. This shows his conception of the scheme whereby the artists of a Grand-Despays could watch their action on one screen while the same picture was being shown in simultaneously in movie houses all over the country, sade our radio could be acted to pict up the view.

By COLEMAN GALLOWAY

EVEN years ago Hugo Gerusback predicted in Rano News synchronization of the radio with moving picture, linking the 'silent drama' with the human voice over the air. Talking picture, the flue attempted, but never made commercially successful. A musical comedy was produced, but the result was mechanical and left the audience dissatisfied.

was prounced, out the result was infechanical and left the audience dissisting Gernshack's prophesy was fulfilled; the talking picture had become a reality. In 15 theatres crowds sat almost bewildered, so uncany seemed to be the perfect synchronization of the lip movements of the actors on the picture screen with the voices broadcast through the receiving sets on the stage.

Acting in collaboration with the Metrocoldsyn-Magre Corporation the Lost Angelter Examiner and Station KTI, Los Angeles, the Committee and Station KTI, Los Angeles, section with a feature film a special film in which two stars, Norma Shearer and Lew Shearer's home and flashing from there to the studio. The action begins in the star's Shearer's home and flashing from there to the studio. The action begins in the star's and being remined by her moder that she is due to appear at the KTI station with Mr. Cody. She calls for Mr. Cody, and they

The film showed them at the microphones of the KFI station, wherein Miss Shearer pretends fear of the instruments and persuades Mr. Cody to make the first speech.

The picture had been carefully rehearsed and all the accompanying dialogue was

broadcast during the filming. No effort was made to present an elaborate play. The only effort was to show that it was possible to synchronize voice with the movement of the player's lips, and the experiment was an indisputable success. The promoters proved

The prophecy made by Mr. Hugo Germback, editor, in an article in the Sept. 1916, issue of Ravicle in the Sept. 1916, issue of Ravicle in the Sept. 1916, issue of Ravicle in the Sept. 1916, issue, the September, 1919, issue, that at that have reprinted here from our September, 1919, issue, that at that the September 1919, issue, that at the Ravicle in the September 1919, issue, that at the Ravicle in the September 1919, issue, that at the September 1919, issue, that at the Even 1919, issue, that at the September 1919, issue, the September 1919, issue, that at the September 1919, issue, the September 1919, issue

their point. With the exception of one or two instances in different houses where operators became nervous the results were remarkably satisfying to all concerned. In one theatre an operator overspeeded the projection machine, with the result that projection machine, with the result that been run through, an incident that brought the audience much amusement.

Fifteen theatres in Southern California were linked in the experiment, the operators running the projection machines with a hand crank, and wearing head-phones tuned in on the broadcast station, which gave them the metroone time-setting cues for starting the film. The speed of the film was gauged by a metronome before each op-

The cues for the actors were run on a special film in the broadcast studio with the picture, the rays being shot through a glass screen, so that they were enabled to time their voices to the movements of their lips on the screen. The glass partition prevented the noise of the projection machine from carrying over the microphone.

from carrying over the microphone.

Receiving sets employing power amplifiers were used in the theatres, and in spite of the summer weather exceptional reception was reported in all instances. One feature of the presentation which appealed to all audiences was the absence of distortion and the fact that the voices as broadcast did not sound cramped.

Now that inventors are announcing the control of radio waves, it may be possible soon for a group of theatres to present any length film story to their individual audiences over specially-tuned sets without making the same slow available to others who have not paid for the service. The demonstration of the conference of the conference

An interesting phase of the radio-motion picture synchronization experiment is the

Are Now Linked



fact that it represents one of the first attempts at co-peration between motion picture concerns and the radio industry. Radio has had considerable opposition from some of the leading producers, and the introduction of general broadcasting evoked a storm of protest from producers who feared that it would tend to harm the picture industry.

One of the biggest concerns on the West Coast prohibited actors under contract from appearing before the microphones of any broadcast station.

But that attitude is disappearing in the face of the realization that radio is something more than a novely, and has come to stay. It will not keep people from the

theatres, and there are great possibilities for co-operation between the two industries. The latest experiment is only a surface and commercial combination of broadcasting and pictures. Succeeding experiments will go further in demonstrating the practicability of Mr. Gernsback's scientific prediction (Conlinued on page 740)

Radio with the Rice Amazon Expedition

By T. S. McCALER

R ADIO News is indeed proud to print herewith the first record of the personal and radio experiences of T. S. McCaleb,
who kept the Rice Expedition in touch with civilization even while they were on ground never before trod by white
men, at the headwaters of the Amazon River.

NE of the outstanding features of the Hamilton Rice expedition to South America in 1924-25 was the successful radio communication of the expedition with the various points

588

in the civilized world.

Regardless of practical experience and
knowledge of combating the elements of the
wilds, an expedition cannot plan every
preparation for supplies to maintain them
for an estimated period of time to reach a
goal, the position of which is merely calculated and the intervening territory unknown.

Many causes that delay progress occur and radio can be used to send a request for additional food supplies and medicines. With radio the party can keep its base or headquarters informed of immediate discoveries, of its progress and of its necessities.

quarters morned of infineducte discoveres, of its progress and of its necessities.

Office while the party may be only 100 miles from civilization communication by mail to keep those interested in the welfare of the members of the party informed may require many monthe. This news, welcome as it is, is not gastifactory, because of the time which has elapsed. But, with radio, word may be sent and received in a few word may be sent and received in a few

There exists in the United States a wonderful system of reliable communication that connects every city and hamlet with practically any part of the world. This system is maintained by an organization composed of men and boys of all professions, who find a great interest in reaching out into space with a remarkably small amount of energy from apparatus often designed and constructed by themselves.

These amateurs are organized into the American Radio Relay League, which soon will become an international association composed of radio amateurs throughout the world.

It was this organization that kept the Rice Expedition in touch with the world, by heeding its request for assistance when the original scheme of communication with the Brazilian radio station at Manaos failed because of adverse atmospherical conditions and the

use of long waves.

To Dr. Manuel S. C. Barros, Districto

Fifty-watt tubes are scarce in the unexplored regions of the Amazon River at the equator. Here is the method Mr. McCaleb used to make five-watt tubes pinch hit for their larger brothers.



Radio Telegraphico at Manaos, great credit is due for his untiring efforts, ability and kind co-operation in aiding in the original communication system.

FAILURE OF LONG WAVES

After interruption on the long waves occurred the writer got into communication with 2CVS in New York City, who voluntered to maintain a schedule each night so that communication could be resumed with the outside world. This method was a tree mendous time-saver when compared to the earlier process of radio communication from the base station to Manaos, thence to New York via cable.

After several nights of reliable communication with 2CVS in New York, adverse weather conditions caused an interruption and stations ICOT, Braintree, Mass.; 3ATE, Baltimore, Md; 8ES, Akron, Ohio; 5SK, Fort Worth, Texas, and 2AKF all periorned excellent service. Later, a contion 2MC at New York, who every efficiently kept a mighty volume of two-way traffic moving.

Other schedules were also maintained with IER, Wellsley, Mass.; 1AF, Harvard University; 1YD, Norwich University, Vermont; 8PL, "h wnee, Ohio; 2BR, New York; 5TD and 4JR, Gastonia, N. C., working through 3BZ and 3ADB, Philadelphia; 3CDV and 3BTA, Gladion, Pa., and 3BFS, Providence R. I.

delphia; 3CDV and 3DLFA, CHARUMI, A.M., and 3BES, Providence, R. I.
With these stations in the East and stations 6OL., Stamford University, Calif., and 6AWT and 6CHL, San Francisco, in the West, both coasts of North America were directly connected by radio with the expedi-

OTHER STATIONS

Later, ICMP, 2BY, 1PL, 4GW, 9BW, 8OV, 2AAN, 1SF, 1ARY, 3ADG, 3OQ, 5SD, 2BRB, 9AZP, 2BQU, 2CJJ, 2BQZ and others rendered a great service by accepting messages from persons in the States for the expedition and receiving expedition messages for the United States, not to speak of many times when they stood by for other traffic.

The greatest distance covered was 'that in exchanging signals and conversation with New Zealand station, 2AP, located at Wellington, at a distance of approximately 8.80 worked on Christmas night and the writer, after bidding Mr. Collier, operator of the New Zealand station, a Merry Christmas subtenly resiliced that New Zealand station, as Merry Christmas subtenly resiliced that New Zealand had to the composite side of the International Date Linc.

Mr. Gerald Marcuse of Station 2NM, at Catesham, near London, was the chief English station to connect with the expedition. His station handled several long messages from Dr. Rice to the Royal Geographical Society.

Station 2AG, owned by Mr. S. R. Runyon and located at Yonkers, N. Y., established a record by receiving a message from an individual in New York and telephoning the reply back, which had been received from the expedition in approximately eight minutes from the time the message was filed.

THE PLANE

During a period in the dry season when the water was rapidly falling, the advance party had penetrated a considerable discover. The airpane, with its plot, Lieut, and the airpane, which is plot, Lieut, the aerial photographer, Capt. Stevens, were awaiting word when a flight could be made to meet the party and for vital information to meet the party and for vital information. Without these reports it has now the property of the party was camped and, in landing, might have run into



Though Mr. McCaleb gave the Indians the best in American broadcasting, they were unenthusi astic, for they could appreciate no music more complicated than a tom-tom beat.

rocks below the surface of the wahave resulted in a serious mishap. The plane being used was of the scout type with the engine supported above the head of the pilot on a single strut. Any considerable jar would cause the engine - to come falling onto the might be classified at least as unpleasant, Asit was the radio link between the advance party and the base kept the pilot well

herewith

informed of the conditions he would have to meet. conditions he would have to meet.

The equipment at the base radio station located at Boa Vista on the Rio Branco (Lat. 2 deg. 49 min. 18 sec. N. Long. 60 deg. 39 min. 55 sec. W. The only way the reader can find this exact spot in an atlas is by the aid of these measurements.) consisted of a transmitter using eight 50-watt tubes to generate a power of 400 watts for communication with Manaos, 400 miles south, a wave-length of approximately 3,000 meters. A number of photographs of the portable station and some of the apparatus used at WIS and brought up to the portable station by the writer for use in direct com-munication with the United States after

the base had been closed down are shown There are several interesting points in mection with the short wave receiver and transmitter which will be interesting to the his radio experience, to deal with the diabolical tropical static.

The transmitter, instead of following the

plan, is built upon the tuned plate The accompanying hook-up will show at a glance just how the thing was arranged The inductances-and most of the set, for that matter-were constructed out of parts of the long wave set and spares carried to the base station. One of the photographs, in particular, is interesting. Long before the time set for the return of the party, the large tubes, 50-watters, began to show signs Not wishing to leave disintegration. things entirely at the hands of chance, the small 5-watt tubes were arranged in series to furnish the necessary power. By soldering them to the circular ring, very good results were obtained. This particular method of mounting kept the effective inductance maximum output was registered in the antenna meter.

The receiver is novel. A description of the hook-up will show where the deviation from normal occurs. The static conditions were such that the standard hook-up sorely tried the operators by the atmospherics. The stunt described here was then tried. Instead of coupling the antenna and ground directly to the tuning inductance of the radio fre-



uency tube, as is ordinarily done - the complete set consists of one radio detector and one audio - the antenna was connected directly to the plate of the detector and then coupled to the radio frequency tube by the tickler.

An added decrease in static is obtained by using a very low antenna, possibly only 10 or 20 feet above ground, and very Both these decrease the signal strength, but at the same time they decrease the static more, resulting in a net advantage.

> T HE past year has seen the use of radio in two very important expeditions, viz., the Rice expedition to the headwaters of the Amazon in possibly the wildest region still unexplored. and the MacMillan Arctic expedition. A glance at the accompanying article will give the reader some idea of the advantages gives the hardy explorer radio which he has never enjoyed before. His personal danger is lessened by one hundred per cent, which is no mean consideration in itself, beside the other advantages. But read the article-Editor.

The construction of the receiver and the transmitter are both plain as to mounting and supply. The photographs will describe them thoroughly. The original gas engine, which was to

have been the primary source of power, was a small air-cooled motor-bicycle engine that flew to pieces due to the centrifugal force. An outboard canoe motor was belted to a small generator which furnished power for charging the 12-volt, 80-ampere-hour stor-age battery. This supplied the dynamotor for the transmitter, which had an approxi-mate power output of 25 watts. John E. Wilshusen, the airplane mechanic, acted as "engineer" when it became necessary to float the generator and battery together for in-



The radio appa us which made



At the base station things were more elaborate. Here are two views of the base station.

creased power. Upon signal from the operator the engine was shut down for re-ception. This method was not necessary at all times, since the battery had sufficient charge for one and one-half hours' com-

TROPICAL DIFFICULTIES

At the next semi-permanent camp the portable station was again erected in the midst of the thickest jungle. But at this which was a little further north and west there were hills more than 1,000 feet high that entirely surrounded the camp. During terrific tropical storms no difficulty was exerienced in communicating with a number of New England and Eastern Seaboard stations, as well as one Canadian.

An incident worth mentioning took place one night during the transmission of a mes-sage from one of the advance camps. The operator, holding the message in his left hand under a small flashlight lamp that was supported in an empty batter tin, turned lead-in. It was supported on an insulator attached to the improvised table where the apparatus was set up. Seeing nothing, he continued to transmit the message. For no apparent reason he turned his head for a second only, to see a faint outline of a snake lying motionless on the lead-in. The message transmitted, the operator picked up a large-bladed pocket-knife from the table, shut down the dynamo and, holding the knife at the proper angle between his thumb and forefinger, took one quick slash and decapitated the snake, at the same time holding his station for an O.K. of his message. This closed the evening's traffic, as it was the last message on the hook. After examining and photographing the snake, it was found to be a jararaca, a very poisonous type, but it was a small one, only 40 inches long. It was probably attracted to the camp by the hum of the dynamotor.

PHENOMENA

Contrary to results showing decrease in received signal strength during daylight, the signal from LR at 10 A. M. on several occasions proved to be approximately equal in strength to the night (Continued on page 747)

he Inventions of Reginald A. Fessenden

PART XI

590

HE income of our little company, known as the Stanley-Kelly-Chesney Company, was to be derived from three things, from the lighting plant and street railway, the manufacture of transformers, and from developments of new inventions made by the laboratory. Whittle-sey, the treasurer, father of "go to hell". Whittlesey, and Hines, the business manager, were both good men.

INSULATING ROCK CUP

In connection with the street railway an interesting thing was noticed which explains some at least of the poor radio reception areas. An extension was made three or four miles north of Pittsfield but no current could be got through the motors. After making all the usual tests without locating the "bug" Chesney connected the motors direct to the feeder and used the trolley wire as return, and the car ran all right. It road was in a cup of non-conducting rock, four or five miles in diameter whose edges rose to the surface, as shown in Fig. 1. It was necessary to run cables from the rails over the edges and ground them outside,

pecially if the reflector threw such that

patents 1,158,124 Oct. 26, 1915, and British pat., 2,995 1908,) so that they would be reflected up and not be absorbed by the ground, as shown in Fig. 2 or com-bining both exactly as I show them eswhen it reached the Ken-

method should appear in the January 1, 1925, article, but this was accidentally omit-ted and the method and apparatus will be more fully described later. TRANSFORMER INSULATION

My first job was to work out a new method of insulating the transformers. Pre-

In the course of Fessenden's traction work, it was found that a section of the road was located in a cup of conducting rock as show matically at the right. establish proper ground con-nection, it was necessary to lead a cable over the edges of the rock layer. The insulat-ing layer was actually four or five miles in diameter

Insulating

nelly-Heaviside layer it would be wide and reflected from a large area, larger than the ionephs' average size, as shown, there would be little fading. Patent applications for this new "Fessenden Wave" system were filed, and later, in April, 1924, its use was sugviously shellacked or japanned paper or cloth had been used, but these were hydroscopic and deteriorated with age. The first transformers we made up were insulated with my catalyzed linseed oil and with a flexible var-nish made from that and the Zanzibar conal and proved much superior to the old ones as regards burn-outs and could be worked at a

higher temperature. But some years before, I had run across a peculiar kind of asphalt, found only in Utah, and called Uintahite. This was not soft like ordinary asphalt, and did not turn to a thick viscous paste when heated but remained hard almost up to its melting point, which was very high, about 400 degrees Fahrenheit. For these reasons there was no commercial use for it. This was exactly what was wanted for my purpose, for the main diffithe cotton fibres are hollow (as shown in Fig. 3) and unless the insulation is so fluid that it penetrates into these little tubes the ends of some of them, lying on the outside of the covering, will lead in moisture and spoil the insulation, as shown in Fig. 4.

So various percentages of Uintahite were tried with catalyzed linseed oil, and a mixture found which would just not soften at the highest running temperature. Then this was combined with the vacuum boiling method I had been using for condensers, the transformers being boiled in the compound in an old sugar vacuum pan. I well remember my pleasure when after attempting to break down the coils without success, one

Fig. 2. According to Fes


senden, if waves were ra diated from a horizonta antenna and reflected up so that the bram reaching the Kennelly - Heaviside layer would be wide and large area, fading would be considerably reduced. In the illustration, (a) is the antenna, (b) the reflec-tor, (g) the Kennelly-Heaviside layer, and (ff) edges of the reflected beam.

Dr. Kennelly later told me of a similar experience he had had with grounding a trans-atlantic cable, so such cases are probably not FESSENDEN HORIZONTAL WAVE SYSTEM

It may be said here that there are good prospects that fading and poor radio reception will be overcome in the near future. Be tween 1900 and 1906 a good deal of work was done on this and the results published in the Electrical Review. London, May 18, The existence of the Kennelly-Heavyside layer was definitely proved, its height measured and given as 100 miles, and the av-erage size of the "ionephs" or clouds of ionized air forming its lower surface as between ½ to 3 miles, and a curve of the trans-mission between Scotland and Massachusetts for January, 1906. The fact that transwas aeolotropic was noted and a relation between the magnetic variation curve and that of the absorption given. Later extained by using several frequencies simul-taneously, and this was published in the Electrician. London, December 19, 1919, But about four years ago it was found that by sending out horizontal waves, i.e., waves

gested in the General Electric Co., and the system was written to accompany the first of these articles, in November, 1924, and it was planned that formal announcement of the

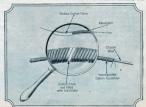Figs. 3 and 4. Cotton fibre is hollow and the insulat-ing oil penetrates this ca-pillary tubing. Fessenden found that this penetration is not always complete and some cotton fibres will remain unimpregnated with the result that they will absorb moisture and spoil the insulation. (The dia-grams, of course, are not accurate pictures cotton fibre)



was sawed across with a back saw and brought me, with the cut surface showing like the section of a submarine cable, This and the silicon steel for low hysteresis and the condensers were my conresis and the condensers were my con-tributions to the transformer end of the business. But the main part of the success was due to C. C. Chesney. He was an ex-tremely able designer and had worked out some formulae which were very valuable,



Fig. 5. Fessenden's electrolytic condenser, con-sisting of sheet iron plates (a), in an electrolyte of bicarbonate of soda (c), contained in iron ves-sel (b), was similar to the arrangement shown above. The plates of each cell were 1/32 of an inch apart.

one for example that gave the minimum loss to be when the hysteresis losses were equal to the resistance losses. He designed trans-formers which had only a small fraction of idle current and all-day loss that the best previous transformers had had, and at lower cost. This and the improved insulation gave the company a splendid reputation and a rapidly increasing business.

HIGH TENSION POWER LINES

Chesney was also the first to see that the ew methods of insulation threw open a wide field for long distance transmission at high voltages. He persuaded Stanley to let him try to work at 15,000 volts (1,000 and 2,000 been the previous standard practice) and installed an experimental line and trans formers for that voltage on the Whittlesey estate, which worked perfectly and resulted in fresh contracts.

ALTERNATING CURRENT MOTOR DE-VELOPMENT-ELECTROLYTIC CONDENSER

The alternating current motor was not a I think now that it would have been, but for the fact that we were trying to develop a commutator type (i.e., one which was really a D.C. motor run on A.C. and with its fields excited by A.C. so that the torque was always in the same direction), to operate at the then standard frequency of 133 cycles. When we came down to 25 or even to 50 cycles, it ran very well. We low hysteresis silicon steel for fields, so the field losses were not too high We got rid of substantially all of the self induction of the armature by Kelly's compensating winding, which is still used. To eliminate the sparking at the brushes we tried at first vacuum boiler condensers, and when we found that so many were re-quired, on account of the low spark voltage, that the cost was prohibitive, I invented new type, the electrolytic condenser, consistsheet iron plates in bicarbonate of soda, about a thirty-second of an inch apart shown in Fig. 5 which worked very and was extremely efficient, showing hardly any rise in temperature after a long To get high starting torque, for cerrun. To get high starting torque, for cer-tain classes of work, we used an enclosed carbon-mercury are whose property of rec-tifying had been discovered some years be-fore by, I think, Du Moncel and which might find a use even today, if properly built so that the mercury vapor could not escape. But the standard frequency was 133 cycles and there was no sale for motors to run on 25 or 50 cycles.

When using the electrolytic rectifier noticed a curious property it had of suddenly losing its ability to act as a capacity and of suddenly regaining it, and that this change could be produced by a spark dis-charge in the neighborhood. This might be worth investigation as an audio fre-

quency or high frequency amplifier. ELECTROSTATIC WATTMETER

Another job was the design of an insulation for fine wire for the winding of the measuring instruments for the high tension work. While on this, the number of turns and cost seemed so unnecessarily great that it seemed there should be some other way, Calculation of the electrostatic forces in-volved, friction of pivots, etc., showed that an electrostatic wattmeter would operate practically, so I built one, shown in Fig. 7, which worked well but has never come into commercial use, possibly because it is more convenient to measure the energy delivered after it has been transformed to the lower working voltage.

The method used for insulating the fine wire. Nos. 32 to 36, was to first clean it wire, Nos. 32 to 30, was to first clean it thoroughly by passing it through baths of alkali and alcohol; then through a dilute shellac solution, and then through the cata-lyzed linseed oil and Zanzibar copal and lastly through a long heated drying tube. But the speed had to be slow and some years later the method was superseded by another using a nitrocellulose compound (which, however, was apt to flake off) and still later by the present enamel method, the name of the inventor of which I should like to know as it is an extremely important improvement over the old methods.

MULTIPLEX TELEGRAPHY BY RESON-ANT CIRCUITS

While with the Westinghouse Company we had installed the electric power plant for the Altoona works of the Pennsylvania

contains a number of formulae which should be of interest to those engaged in this line.

After the lecture Dr. Dudley and others brought up a difficulty they had been having on their railroad telegraph lines, due to the large number of stations in series, and asked

if it could be solved. Of course most of the work on the A.C. motor development at the laboratory had been done with resonant circuits and it oc curred to me that by working the line multiplex with different frequencies and tuned circuits the difficulty could be overcome. Dr. Dudley approved and some of the instruments back with me to Pittsfield and made some tests which were successful, but Stanley very rightly decided that there would be no money in that line of work. So I took the system to an old friend of mine, in the transatlantic cable business, Mr. C. Cutriss, who had himself made some improvements in cable appara-He gave me a very courteous hearing. while I explained my method of working cables multiplex by low frequency tuned A. C. signals, and then said, "Mr. Fessen-A. C. signals, and then said, "Mr. Fes den, I think your system would work. we do not want it. Every one of our cables has cost us \$3,000,000 and we have to earn dividends on them and the greater part the day they are hardly worked at all But if you can invent something which will prevent all cables from sending more than four words a minute, we will give you a serious, but I saw his point, that high speeds of working were not wanted, and dropped the matter for some years, until 1914, when it was proposed again but turned down.

INCANDESCENT LAMP FILAMENTS Most of the time was spent on making

Fig. 7. The filament string galvanomet-invented by Fessenden. Instead of a moving coil, this gat-vanometer makes use of a vibrating g o l d wire. The galvano-meter is capable of re-cording frequencies up to 50,000 per second.



Railroad and what might almost be called the usual offer of superintendent of motive power had been received from Dr. Dudley who, with his brother, (connected with the New York Central Railroad) did so much for railway development, and an invitation to deliver a lecture at Altoona before the Pennsylvania Railroad engineers. The sub-ject they chose was the design of telegraphic apparatus but as delivered covered vider field. It was later published in the Journal of the Franklin Institute, "Electro-magnetic Mechanism, with Special Reference to High Speed Telegraphy," June, 1900, and

In working on measuring instrumen high tension currents, Fessenden invented electrostatic watt meter. It could indicate ower directly in the high tension circuit.

incandescent lamos with filaments coated the mixture of thorium and cerium which Welshach has invented for incan-descent gas mantles. Stanley had the idea that if this were used as a filament coating the lamps would give much more light and my efforts to prove to him that the effect was a catalytic one as shown by the effect of the small percentage of cerium, were ineffectual. Of course, I did my very best to make the idea work, but equally of course without result.

VISIT TO ENGLAND RE HIGH POTEN-TIAL TRANSMISSION

When it was clear that the Welsbach coating would not operate, and the trans-former work was completed. Stanley wished done there in high potential transmission work, especially by Ferranti. Ferranti was one of those engineering geniuses who ap-pear every now and then, but too much in advance of their age. Like Brunel for ex-He had seen that the right way light cities was from a large centra station outside of the city and had built a large station at Depford and designed and built great dynamos and was sending current into London on concentric 10,000 volt mains. Looking it over it did not seem wolt mains. Looking it over it did not seem adapted to conditions in the U.S. at that time, and I so reported to Stanley, adding that I was going to investigate the new (Continued on page 712)

Radio-Controlled Automobile By HERNDON GREEN

Radio is to control a car in transcontinental tour. The system, which is extremely simple and effective, is fully described here.



THE DIAGRAM

A glance at the wiring diagram given in an accompanying illustration will show the circuit in its simplest form. Some of the amplifying relays are left out in order to simplify the circuits.

The two transmitters are of the usual 10-watt type, using storage battery supply for the filaments and plates. They are housed in the tonneau of the control car together-with the power units. The keys controlling them are placed on a small shelf at the right side of the dash.

The receivers are the usual type, employing loop and radio frequency with two audio stages. Since it will seldom be necessary to work over a distance of more than sev-


eral hundred feet, the receivers do not need (Continued on page 656)

Above is shown the two cars used in the transcontinental tour by Mr. Francis P. Houdina. The from car has no driver but is controlled by ra-dio from the second dio from the second car. Note the transmitting antenna and the receiving loop.

OME weeks ago the daily press he alded the first accident which befell an automobile proceeding on its way up Fifth Avenue, New York. The car was a strange affair. In the tonneau was the most complicated collection of radio sets, relays, circuit-breakers and other electrical apparatus, one can imagine. Closely followtwo radio transmitters and an operator When the keys were pressed in the second car, the first one changed its course, blew its horn or blinked its lights. In short, the second car was controlling the one in front

The mechanical and electrical end of the apparatus is simple in the extreme. There are two transmitters and two receivers. One operates on 178 meters and the other on 103 meters. The longer wave transmitter actuates the selector switch, which picks one circuit of the many and closes it for opera-tion. However, the battery current is not connected to the particular controlling de-vice until a dot is sent out on the second transmitter. This puts into operation the exact circuit selected by the first transmitter. Thus, if it is desired to throw out the clutch, the selector switch is first moved to the point which will select the circuit at-tached to the clutch motor, and when the action is desired, the second key is depressed. closing the battery circuit, operating the motor and so throwing out the clutch.

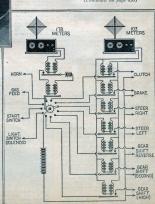Above is the receiving loop and the re-lay devices which operate the motors and solenoids which control the car. At the left can be sent the variable conden-sers which tune the receiver. At the right is a simplified hook-up showing how the radio impulses oper-ate the various agen-tet the various agenate the various agen



Can You Find the 34 Mistakes on Our Cover?



OW that everyone is following the craze, and buying radio set policy of Rapio News for some time to give as much information about sets as possible. This is particularly for those persons who have never used sets before. Every year a new crop of set users comes along, and they must, as a matter of course, learn how to use their sets.

inclined now to the their sees, around for this month's Rauso Niews cover, we told Mr. Howard Brown, our well-known artist, that we winted a painting of a standard 3-dail and the sees of the sees of

\$300 Prize Contest

Cash Prizes

First Prize\$	100.00
Second "	75.00
Third "	50.00
Fourth "	25.00
Fifth "	10.00
Sixth to 13th Prizes,	
each \$5.00	40.00

Total.....\$300.00

did! He did it up "Brown." He showed us the customary preliminary pencil sketch, which looked fine, and so we gave him a direction sheet on which we indicated the connections and all the usual details.

Within a week the cover was duly delivered by messenger, with a note from the artist saying that he had left on his vacation was to our Bling. We looked it over, and it certainly did look good to us. However, our lives, and the more cloudy we impacted to the look good to us. However, we became. Evidently Mr. Brown had been in a terrific hurry when he painted the over, because by the time we recovered from our shock use found that he, had made no Ize as this may seem at first imspection.


But it had come so late that we found

(Continued on page 654)



England's New **Broadcast** Station, 5XX



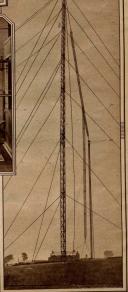


Radio Used As Fire Fighter




The Fire Department of Amsterdam, Holland, has adapted radio, not only for signaling the central station when a fire occur, but also to keep day turns informed as to the propriest made in fighting the configuration. The transmitting and receiving equipment is housed in a truck with a special body, which is driven to all important fires so that the central station can be in direct communication with the fire fighters consulting. Each of these trucks is supplied with many of the city, drawn to a state of 11.000. These mays are 93% by 7 inches indicates by-



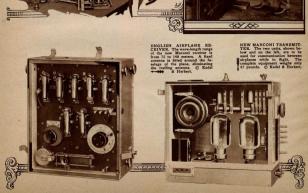




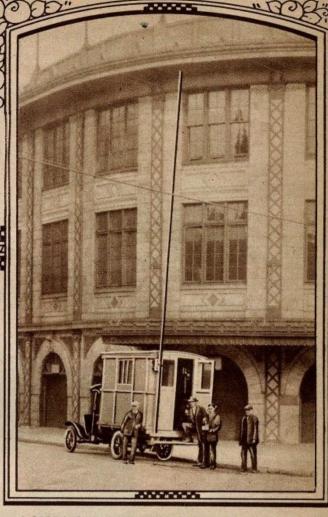

A COLLAPSIBLE ANTENNA. The antenna of the portable relay station used by KDKA as a pick-up station. The antenna is a collapsible jointed copper rod of the vertical oscillator type and is shown in the above photograph attached to the truck that houses the station.

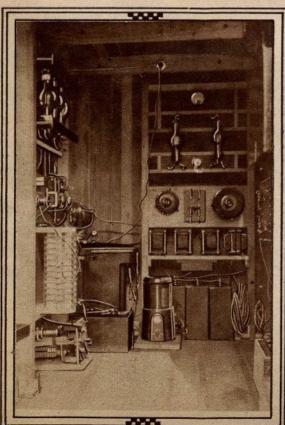WATCH-CASE CRYSTAL RECEIVER. One of the unique sets that was entered in the Radio News Home-Built Set Contest is shown above. The wires shown are the antenna and ground leads, a condenser is in the cover of the case and the taps of the coil are brought out on the face of the watch. The phone tips fit into small jacks at the bottom of the case.




REAR VIEW OF THE K D K A R E L A Y TRUCK. The supports for the antenna are behind the left door and the antenna is slung under the floor of the truck.

INTERIOR OF THE KDKA TRUCK. The transmitter is a quarter KW. set, the power being obtained from a 110-volt lighting circuit and stepped up to 2000 volts D.C. The transmitter, which operates on a wavelength of 35 meters, has relayed programs 20 miles from the station.





Radio Abroad

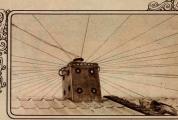

ONE OF THE GROUND PLATES OF STATION SXX. The newest of England's broadcast stations has a unique ground. Surrounding the station are plates, buried as shown in the

THE LEAD-IN TRUNK ON TOP OF THE STA-TION. The ring surrounding the trunk is the terminal of the ground plates. This system of counterpoise is considered one of the best known.

5XX. This photograph, taken from the top of one of the 500-foot antenna masts, shows clearly the ring of thirty-five ground plates surrounding the station. The lead-in from the antenna may be seen in the middle of the picture.

RADIO USED TO BEOADCAST WEL-COME TO THE PERINCE OF WALES. During the travels of His Royal Highness radio played an important role. At Durban the speech of welcome of the Mayor to the Prince was put on the six. The latter may be seen just to the left of the microphones.

REPURE TO

VENILE. Ramo has invaded the canals of this city and gondolas are being equipped with receivers as an added inducement to ourists. The gondola on the right is one of the first to be so equipped. © International Newsreel.

6-1(05)-0

WRNY Starts Broadcasting Innovation

By CHARLES D. ISAACSON Program Director WRNV



CONTRACTOR OF THE PARTY OF THE Above: Dr. Chas.



Miss Anita Browne



I. van Cleft Cooper.



Miss Lorna Lee

(EDITORIAL NOTE: The new Program Director is known all over the world as organizer of concerts for the masses, having reached more than 5,000,000 people face to face—as lecturer, au-thor and newspaper man.

T is going to be the greatest fun of all the things I have ever tried to do, working out this new plan of broad-

Yesterday, you might say, I went for the first time to an improved microphone and could scarcely believe myself as to what could scarcely believe myself as to what was happening. Yesterday, you might say, when I first told my friends that a man only thirty miles away had heard me, they said to me: "Dream on, dream on." First, there is broadcasting, and then there

First, there is broadcasting, and then there must come system in broadcasting. To me radio is a combination of theatre, concert hall, opera house, unversity, town hall and field of sport. Eventually there is no question but that certain stations will be known

tion but that certain stations will be known for certain things, just as magazines are known in certain fields.

But, in the meantime, it will be the plan of WRNY to get away from the haphazardness of broadcasting and so to organize out time on the air that our listeners will know now, and tomorrow and months to come, at any moment.

at any moment.

In order to do this, WRNY has divided its program into music, the other arts, the theatre, literature and other educational subjects. These departments have been subdivided so that in music we find grand opera, light opera, oratory, song literature, chamber music, wolfin courses, etc., and, of course, the best of the popular music.

In literature, or dat and eggs, poetry and

In literature, we have fiction, poetry and serious writings, old and new. There is a sculpture department, courses in history, geography and science, and so on. The plans will work out something like this:

The plans will work out something like this: If you tune in on WRNIY Monday, you will always find popular dance music, folk Always on Monday there will be poetry and painting and history and geography and travel, but Tuesday, on the other hand, will be a night for light opera and orchestral concerts, and just a word or so on architec-

ture.

If you are of a studious turn of mind, you will soon learn that always on Tuesday you can find lectures on law and history—and so it will go on all through the week. Wednesday will be dedicated to songs, fiction, history and sculpture, and Thursday, the more popular music with certain concert

Friday will always be known as grand opera and band concert night, and the night of unusual novelties. I do not want to tell the whole story here. Rappo News has already of unusual novelties. I do not want to tell use whole story here. Rano Nxws has already published a little booklet that gives a plan and outline, which will be mailed to you upon request. The staff of WRNY is now at work on a bir broadcast book that you will want to have in your possession, be-off broadcasting of any station in history. It will tell you at least six months in ad-

vance how to follow everything you want to know.

In order to carry out this tremendously ambitious program, WRNY is about itself an excellent company.

about itself an excellent company,
In the grand opera department there will
be associated regularly such noted conductors as Clementi De Macchi, Salvatore
Avitabile, Louis Aschenfelder, E. D. d'Avigneau. Both Mr. De Maschi and Mr. Avitabile have conducted throughout Europe
and America and Mr. Aschenfelder has
turned out some of the greatest singers.
D'Avigneau conducted the California grand D'Avigneau conducted the California grand opera company and brought Leoncavallo, the composer of "Pagliacci," to America. One organization that is now being prepared for WRNY is a complete chorus and or-

chestra.

The light opera department will give such performances as "Patience," "The Mikado," "Tales of Hoffman," etc. An organization (Continued on page 735)





xandre Zeitlin will broadcast a series of talks on sculpture Tuesdays at 8:30 P. M.





Plastic Radio by the Kluth System

By DR. ALFRED GRADENWITZ*

Another method for producing stereophonic effects in radio reception is interestingly described below. The effect is produced at the receiving, instead of the transmitting station.

POSSIBLE SOLUTIONS

In the October issue of RADIO NEWS an article submitted by Ludwig Kapeller entitled "Radio Stereophony described the method of obtaining stereophonic or binaural reception of electrically con-ducted sounds, which has been put into actual use in Berlin. The method described employs two separate microphones, two separate radio transmitters and receivers, and two independent telephone receivers. This is an expensive method at best, but the system described in this article is worthy of a trial by our readers, as it can be re-produced at relatively low cost.

The stereophonic effect is accomplished, not at the transmitting end, plashed, not at the transmitting end, as in the previous method, but at the receiving end, where a certain difference in phase between the currents in the two telephones is caused, to produce the binaural effect. This is done in a simple manner by means of a special vari-ometer of very high inductance.

—Editor.

enjoyment comparable to that of direct listening. Is it possibly because our

most important sense organ, the eye, is ex-

cluded from co-operation, or is it due to slight defects inseparable from even the best reproduction? The true cause has

lately been found to be a defect similar to that of one-eved vision.

to be due mainly to the co-operation of the

two eyes, each of which, on account of their

right ears might receive slightly different acoustic impressions, just as in direct listening, the right ear, in accordance with the distance separating the two ears, receives a slightly different impression from the left

A conception of space, in fact, is known

inconsiderable distance, receives a

reproduction?

UR readers have possibly wondered why even the most perfect broad-casting of music fails to convey an

If two microphones separated by a corresponding distance were used as sound re-corders, two separate lines of conductors being relied upon to lead the microphone currents to the left and right head-phones respectively, a sound would be heard in exactly the same manner as though the two ears were substituted for the microphones; i.c., this arrangement would convey a perfectly natural, plastic (that is to say, three-dimensional) impression. If, on the other





Fig. 1. Simple circuit illustrating an arrange-ment for setting up a phase displacement from 0 to 360 degrees using a variocoupler.

hand, the two lines of conductors between the microphones and telephones respectively are replaced by two radio transmitters and receivers, the same phenomenon would occur,



posed on electric waves. Inasmuch as two microphones installed at a short distance apart are able to record the phase difference required for a plastic acoustic picture, the vibrations recorded by the two microphones could be superimposed on a single train of The waves issuing from electric waves. the radio transmitter would then carry the receive it. However, inasmuch as this phase difference is communicated simultaneously to both head-phones, both ears are bound to receive the same acoustic picture, thus ex-cluding any actual plasticity. In fact, the electric waves generated by the two microphones respectively and carried by the same train of broadcast waves would have to be disentangled so as to cause those corresponding to the first microphone to be re-ceived by one and those recorded by the second microphone by the other head-phone While this process in theory would seem to be quite feasible, it has not yet been carried out in actual practice.

THE KLUTH METHOD A German radio engineer, Mr. H. Kluth of Nauen, has devised a process based on a

phase displacement of the waves striking the broadcast receiver, the transmitter being, as usual, operated with a single microphone. A shifting in phase of high frequency vibrations as obtained in a radio receiver could, with relative ease, be obtained with the aid of a variometer free to rotate through 360 degrees. The circuit of Fig. 1 illustrates a simple arrangement enabling a phase displacement from zero to 360 degrees to be obtained in accordance with the actual ment were used in connection with the radio receiver it would entail the use of two vacuum tubes (Fig. 2), causing the original high frequency current and that shifted by a fraction of a phase to be supplied to head-This arrange-

slightly different visual picture of its surroundings. That even our sense of hearing is connected with conceptions of space has so roundings. resulting in a perfectly plastic acoustic pic-Another solution of the problem could be far been mostly left out of account, though the mutual distance of the two ears, which is about 81/4 inches, is bound to bring a sound coming from the left, for instance, a little later to the right than to the left ear, so that the acoustic perceptions corconceived of in theory as follows: Micro-phone vibrations are known to be superimphones 1 and 2 respectively. This (Continued on page 720) responding to the two ears, in spite of our remaining unconscious of the slight difference in time, are bound to differ from one another. Just as our sense of vision fuses the left and right eye impressions into a single plastic picture, hearing amalgamates the acoustic perceptions corresponding to the left and right ears respectively into a single plastic conception, which is further accentuated by individual sound differences Broadcasting, on the other hand, will con-vey to our left and right ears respectively (by the intermediary of the two headphones) perfectly identical oral impressions, resulting in a flat and shallow sound picture devoid of any plastic perception.

Endeavours have therefore been made to devise some means by which the left and

*Berlin Correspondent Ranto News. **See Ranto News, Greober, 1925, issue, "Stereophonic Radio,"



The Dife and Work of Lee DeForest





Above is shown Dr. Lee DeForest with his latest invention, the phonofilm, on which he is now working. The picture above was taken in Germany shortly after he had put the device into workable form.

CONCLUDING INSTALLMENT

Twenty of the property of the control of the contro

the DeForest organization was working at the speed, everything was being pushed to the limit. What experimentation was done, the property of t

One of the outstanding developments of this period was the motorcycle station unit, a photograph of which is shown in one of the accompanying illustrations. This was one of the first mobile sets to be perfected

which could be said to have attained really commercial efficiency and dependability. And then in the spring of the following year, while still engaged in the war work,

And then in the spring or the boundary of the boundary of the boundary of the lymns as the usually thought of by the lymns as the broadcasting, as such. From the Columbia Photograph laboratories in 38th street as the first regular broadcast program. It command the columbia produced the laboratories in 38th street as the first regular broadcast program. It command to the laboratories in the laboratories are produced to the laboratories and a public mercing in the half-com on the roof of the Hotel Astor, where a number cost in the laboratories in the laboratories and a public mencing in the laboratories and a public mencie to a standard receiver and auton amplifier. The program came in addition to the telephone receivers there

In addition to the telephone receivers unterwas a loud speaker on a side table. This was not a commercial instrument, since at the control of the control of the control of the not, as yet, reached a point where they were necessary. The instrument used was composed of a horn and standard receiver unit. Its reproduction was not all that could be asked in the way of acoustics.

The following morning the daily press heralded the feat far and wide and in the usual lurid terms. As DeForest had forseen for at least six years, a start had finally been made toward the development of radio as an actual public service which time, other savants in the field placed no credence in this prophecy.

After the first successful attempt from the Columbia studio, results were so promising that the scheme was continued. Artists who were engaged to make records also appeared before the microphone. From

time to time other interests were added to the program and before many months had passed letters began to poor in praising the the program of the property of the property of the program of the property of the property of the program of the property of th

timed, radio dances began to be the thing. Many were held in the metropolitan district with the aid of loud speakers. All of them the throught letters to the broadcasting station are considered to the control of the station, reports came in from the middle West and regular reception in Buffalo, New York, was common. The work continued until April of the next year, when the government closed all next year, when the government closed and control of the war.

Those who have been following this series will remember that all this phone work was

when the continues that an time process were continued to the continues which served as a carrier for the voice modulation. The Heising system of modulation had not yet been brought out and the DeForest system employed the grid method of impressing the voice current in the continues of the cont

have made a much quicker advance into our made a much quicker advance into our and the consequence and the

DeForest began again to spend his squre time working at his own ideas. The Nary was anxions for some improvements in which we have been a superior of the control of the control of the control of the which Wenhelt had discovered in 1994, and thought it a good idea to incorperate it in the filaments of their tube, this decreasand after some necessary experimentation like feature was innorporated in the De-Forest tubes made for the Navy. It was the control of th

U. S. ENTERS WAR

As soon as the United States made its entry into the war, DeForest was called into the service. Since the beginning of the Unpleasantness, airplanes had taken a very important place and were constantly becoming more indespensible to the various combatant forces. The one great difficulty with them was that encountered in communication to and from moving craft. The adapsancessful us to the time De Forest tackled

Biography recorded by W. B. Artin of Radio News, under the personal direction of Dr. DeForest. Copyright, 1925, by E. P. Co.

the problem. He designed and built a comtransmitter and receiver, the power of which was drawn from a generator operated by an air propeller attached to the outside the fuslage.

A great number of these sets were built or the service and performed their duty rell. What an improvement this was over the previous method may easily be recognized when it is called to mind that the only means available before was the use of huge white sheets which could be seen by the pilot, with a shutter arrangement so fixed as to enable the ground men to make dots and dashes by alternately making the sheets visible and invisible.

During the remainder of 1916 and 1917 DeForest continued in the service of the government and finally brought out the VT 2, which is the practical basis for the present-day 201-A type tube. These found

great favor in use and swiftly became the standard of the service. Another experiment which has never been

Another experiment which has never been brought to final form, since the Armistice did away with the near which gave the desired and the second of the secon short-distance work.

A few years ago, after the conclusion of the war, this type of set was the subject of much experimentation among the amateurs. However, in this age of trans-oceanic comnication with five watts or so of power, it has fallen into the limbo of spark transmitters and the other developments which were so important in the babyhood of the

DeForest was still in Paris at the time of the Armistice, and, with the remainder of the population, found himself slightly daft at the announcement of the long-awaited conclusion of the four-year conflict. Being in the thick of it for longer than a great many of his compatriots, it is forgivable that he possibly showed a bit more enthusiasm and release from strain than they.

THE EPISODE OF THE FLAG

the world for four long years at last ended? Of course, there should be a celebration—

riotous, mad even DeForest and Darby—Samuel E. Darby, the attorney who had on occasion fought for DeForest's rights in almost every pos-sible court, who had once, even, prevented DeForest's tasting the weary, dark waters of the Hudson river while in a fit of depres-sion—DeForest and Darby started out to give their taut nerves the long-waited release. Down the Boulevard St. Germaine they went and then across toward the Champs Elysees. The crowd all about was Champs Elysees. The crowd all about was in gala attire and the holiday spirit was rampant. Flags everywhere. DeForest was away from home. He wanted an American flag. Hadn't the Yanks been responsible for most of it? Was he not a Yank? He had to have a flag. Seven shops were visited and all the keepers were sorry, very sorry, but they had sold the last American flag

Well, if he couldn't buy one, there was only one thing to do. He had to have one. It was settled. There were tickets for the Folies Bergère and it was highly improper for him to go without a sign of God's own country to show the Audience. Ah, here was the chance, a nice dark corner and three flags in that third-story window—the French, the Union Jack and, boy, there was the old Stars and Stripes! DeForest told Darby his intention. The latter tried to dissuade him but it was a simple waste of dissuade him but it was a simple waste of breath. So up he climbed—up the stone facing of the building to the window ledge on the third floor. The thing was going successfully. A slight tug brought the flag free from its support. DeForest climbed down with a whoop. And there was where he made his mistake. A gendarme saw the process and, hearing the whoop, came full speed after the culprit. The chase was short and led to a police court. The cool cell behind the court room, how-

ever, did not dampen DeForest's spirits. There was a slow dragging of time, however, and finally Darby was able to get a hearing for his client, in spite of the general disruption of schedule on account of the disruption of schedule on account of the merry making. The judge was austere— until Darby presented DeForest's card. His Honor, it seemed, followed scientific research to some extent and knew of "the





hour or more clapsed between the first break of the news and the time he rushed out into the streets with the remainder of the pop-ulace. For the first few minutes after he reached the street, he seemed fairly sane. However, as the full meaning of the event became more clear in his mind, the momentousness of the occasion was borne more fully upon him.

One thing was absolutely certain. must be some sort of celebration. Was not History being made? Was not the long nightmare which had strained the nerves of





Dr. DeForest in a business pose, appears with his helpers in the at the stud

great American radio man who has so much helped the France." He was dismissed with an admonition to steal no more flags-but keep the one he had.

Then to the Folies Bergère. The show was a riot. No one followed his lines. The cast was in the same mood as the audience. DeForest had a box. Finally toward the Deforest had a box. Finally toward the end of the first act, there came a story of an American Doughboy. At the end, the actor cried "Vine les Edats Unist" Deforest could wait no longer. He arose in his box and cried: "I'll say so!" and waved the flag above his head. There were many of his compatriots in the audience it seemed, for they arose to their feet and began to sing, shout and yell. In a word, DeForest stopped the show for America.

A few days later, his work completed and the last details settled he returned again to New York to take up his work where he had left it, more than a year before. First, however, he took a three months' vacation

Back again at the grind, he began to cast bout for openings for his broadcasting about for openings for his broadcasting scheme. The old High Bridge station was opened and the former programs resumed It was only a short time until the radio inspector for the New York district began to question the right of a station to broadcast. The matter was called to DeForest's attention. DeForest could not see why a duly constituted and licensed station might not broadcast, so long as it observed rules laid down in the radio law of 1912.

In the end the inspector had his way and the High Bridge station cut off the power and ceased its daily programs.

Shortly after this, the Intercity Radio Company, which had an installation atop the World Tower in Park Row, invited the DeForest Company to continue their work at the World. The

invitation was accepted with pleasure and in a short time DeForest was again broadcasting. Another novelty was added to the program in the form of a sort of a vaudeville bill. Vaughn De-Leath was one of the principle performers and after-ward made a great hit on made a great hit on the legitimate variety stage through the aid of her training before the microphone and the reputation it had brought her. Meanwhile, while he had kept this work going he had established another station for the Toronto

(Continued on page 750)

By DR. C. B. BAZZONI*





N the last issue of Radio News I de-scribed certain general features of vacuum tube operation in an article on "Hot and Cold Cathode Tubes as Rec-tifiers and Detectors." I there pointed out that, although the vast majority of the tubes that, although the vast majority of the tunes used in radio have hot cathodes and are pumped to as high a vacuum as possible so as to employ the "pure electron discharge," there are nevertheless on the market a con-siderable variety of tubes, some with hot and some with cold cathodes, in which a sufficient amount of gas or of vapor of some

604



metal vapor tube is here used as a detect is the filament: C, the collector, and the liquid metal anode.

sort has been introduced to alter the tube characteristics in a fundamental way. plate current in such tubes is largely a gas ionization current. Tubes in this latter class frequently seem most curious to the amateur, since he is not familiar with their appearance nor with the principles which underlie their operation. The editor of Radio News has consequently thought that a description of the theory of such tubes, illustrated by references to applications in particular cases would be of interest to RADIO NEWS' readers. In this article I shall speak only of hot-cathode, gas (or vapor) filled tubes, leaving cold-cathode, gas-filled tubes for subsequent treatment.

NEED FOR MORE SENSITIVE DETECTORS It will be recalled that the pure electron discharge of the high vacuum tubes of the 201A and 301A types, being readily and accurately controllable, renders these tubes superior for amplification work in which lack of distortion of the signals is a primary requirement. Such tubes, however, have comparatively very low sensitivity as detec-tors. The importance of obtaining some device with a higher detecting sensitivity


than that of high vacuum, three-electrode tubes is really very great. The present popthan that of high vacuum, unce-treessouthes is really very great. The present popular use of radio is to be traced to the general introduction of "regenerative reception" which is, in principle, a circuit arrangement for increasing the detection sensitivity of three-electrode tubes. A tube hooked up in a regenerative circuit has a high detecting efficiency, but here sensitivity is obtained by a close approach to the production of selisustained oscillations in the set which, unless special precautions are used, may produce destructive interference with neighboring re-ceivers by reradiation. What is wanted is a tube having a higher sensitivity in itself without employing regeneration. Some such device is necessary to the continuation of the growth of radio in service and popularity. GAS-FILLED TUBES

The detecting sensitivity of ordinary tubes can be much increased by introducing into the tubes a small amount of gas which, as explained in last month's article, ionizes at particular plate voltage and produces a sharp rise in plate current partly due to the new electrons (negative ions) thus released and partly due to the neutralization of the negative space charge by the positive gas Tubes of this kind are called "soft ions. Tubes of this kind are called "soft tubes" and are frequently used in the detector stage of radio sets. Tube UV-200 is of this These tubes, to be practical, must contain, however, only very low pressures of If the gas pressure be increased to the point where the detecting sensitivity is a maximum, the device becomes erratic because



In curves A and B the variations in the collec-tor and anode current are shown, giving the resultant effect in curve C.

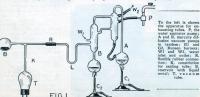of the practically unavoidable changes in gas pressure due to the continual taking up and gas by the metal parts and glass walls of the tubes when the temperature changes. An erratic tube requires continual adjustment of the biasing potential on the grid and is of no use in practice,



It is true that this erratic behavior has been eliminated in certain experimental tubes of the gas content type, stability having been attained by expert care in the preparation of the tubes and by the use of a critical toon of the tubes and by the use of a critical gas pressure—but such tubes have not proven to be reproduceable. By this we mean that it has been impossible to devise a practical manufacturing procedure for making large numbers of these tubes exactly or even nearly alike. Each tube requires individual expert attention and adjustment in the making, These remarks show that a practical radio tube for detecting work must be sensitive,



stable and reproduceable on a commercial

Tubes employing ionization have another advantage over pure electron discharge tubes in addition to their higher detecting sensitivity. Once the ionization point is passed, the plate currents through such tubes are very large, perhaps several hundred milliamperes through tubes of the ordinary detector size. These values are reached at plate voltsize. These values are reached at plate voltages of the order of 18 or 20 volts. In order to pass such currents through a high vacuum tube depending entirely on thermionic emission, much higher plate voltages must, on the other hand, be used-from 90 volts up in ordinary practice.

It is, of course, advantageous from con-

siderations of convenience and expense to keep the required plate voltage as low as possible. However, neither of the advan-tages cited can overbalance erratic behavior of the tubes. To make use of these advantages the first necessity is to secure steadiness of operation. We shall see in this article how nearly this result has been attained by the use of metal vapors in the tubes in place

of gases.
When a gas is to be used in a detector tube choice is nearly always made of one of the so-called "noble gases" (the "rare atmos-pheric gases") helium, argon, krypton, neon or xenon. In practice only helium, argon and neon are used. These gases are very inert and therefore do not react with the electrodes or other parts of the tubes. are monatomic-that is, each molecule con sists of a single atom only, which makes them ionize, i.e., break up under electronic bombardment, in a more simple manner than would polyatomic molecules. Their ionization points are relatively high, ranging from 25 volts for helium down to 17 or 18 volts. This voltage value is the drop through which an electron must fall in order to pick up enough energy to knock an atom of the particular gas apart into a negative ion and (Continued on page 728)

A Crack 40-80 Meter Set

ND where is the man who said it couldn't be done? A review of the accomplishments in the field of amateur radio during the past winter would contain such stupendous developments as to stagger the most vivid imagina-Hazy dreams and aspirations of the past have become real experience-and not only that, but everyday experience to a great number of amateurs throughout the entire world. Communication across states, across continents, across oceans, to the antipodes has become the rule of the game. Communication of nearly three thousand miles at noon with less than one kilowatt input has been with clock-like regularity, Through it all, we see growing that everincreasing bond of friendship which comes through community of interest. National, geographical and racial barriers fall before the advance of amateur radio communica-

This great advance in the art owes its existence to such men as John L. Reinartz, who are ever forging ahead, discovering new facts, and opening new fields of investigation. The readers of the Raso Næw will remember his monumental work on twenty-meter transmission.

An article is here presented that will prove of interest to those who wish to experiment on the 40-80 meter wave band.

By E. W. THATCHER

seen that some of the bands have advantages peculiar to themselves and a particular kind of service. The purpose of this article is to present, in as concise a manner as possible, points in the construction and operation of a simple but efficient transmitter and receiver, capable of operation on either the 40-

or the 80-meter band. THE TRANSMITTER

The transmitter employs one so-called 50watt tube in a Meissner type circuit (Fig. 1). The arrangement, planned to reduce the length of the leads in the oscillating circuit, is shown very clearly in the cut (Fig. 2).

The base is removed from the tube and mounted in an inverted vertical position. A small wooden box with a hole cut slightly larger than the tube furnishes the support, while the tube itself rests upon a small piece of sponge rubber. Around the edge of the

box are fastened the condensers, C₀, C₄, C₅ and C₆ all of .002 mf. capacity. The left end of the box supports the grid leak. Thus, all the leads are centered around the top of the inverted tube, and may be made extreme-

by short.

The power for the plate is supplied by a
Transformer which delivers 1,500 volts either
side of the center tap. An electrolytic rectifier, consisting of 40 lead-aluminum cells
in a "bridge" circuit, gives a pulsating unidirectional current which is ironed out by
two shunt condensers of one microfarad

each, and a large fron-orc choke.

The radio (requency chokes are wound of a continuous choice and the radio of telling whether in the individual case the individual case of the radio of telling whether in the individual case the individual case of the radio of the

The plan followed by the writer in making the inductance will prove the solution to one of the problems that always continuous the problems that always continuous the problems of the problem

The leads from the antenna and counterpoise are brought in through a panel of plate glass (an ex-windshield from an automobile, which was secured from the local garage at the cost of \$9.00). Holes were (Continued on page 690)

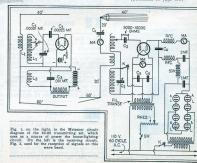


Fig. 4. On the left is the receiving equipment. The inductances are suspended from the horizontal glass rod. Note the fanned plates of the variable condenser.

The wave bands allotted to amateurs have been proven to possess widely varying qualities, but the concordant results of many experimenters makes possible a statement of the general characteristics of each.

BAND	DAYLIGHT CHARACTERISTICS	Fading, bad Atmospheries, very strong		
150 to 200 meters	Range, 0-200 miles Fading, nil Atmospherics, strong			
75 to 85.6 meters	Range, 0-400 miles Fading, nil Atmospherics, nil			
37.5 to 42.8 meters	Range, 250-1,000 miles Fading, nil Atmospherics, nil			
18.7 to 21.4 meters	Range, 1,000-3,000 miles Fading, nil	Range, 4,000-??? Fading, nil		
4.69 to 5.35 meters	Range, ??	Range, ??		

While these figures are far from "hard and fast," they serve to give a basis of comparison on which to work. It can readily be



International Radio



GREAT BRITAIN

Big Ben's Microphone

The microphone which picks up the music of the chimes of this world-famous clock in London is sealed up in a special way in order to protect it against the weather

To assist hearing in

The microphone is wrapped in cotton and then enclosed in a football bladder, the latter being hermetically sealed by means of a rubber solution. The whole affair is then suspended from one of the girders about ten feet above the bells.

House of ords to Have Loud Speakers

the House of Lords, British radio company is to install loud speakers, which are to be camou flaged as gilt-lined tomes to match the array of reference books,

Novel Eng-lish Crystal Detector Resembles Radio Tube

A new permanent de-tector might at first sight be easily taken for radio tube, so great is the resemblance between the Two very sensitive crystals are used in this detector, and it is claimed that no adjustment of any kind is needed. The crystals are carried on two flat springs which press the

Over the whole detector a glass bulb is placed, which excludes all dust and grit. Connection to the set is made by a pin mounting fitted to the ebonite base of the detector. In this way, the detector can be withdrawn or inserted in an instant, and if desired, transferred to another set, just like a tube.



The crystal detector shown here is described above. The photograph is nearly full-size.

The compact and rigid construction allows the detector to be freely handled without fear of disturbing the adjustment. The small size of the device will be seen from the photo; the total height is 25% inches, the diameter of the glass bulb is 5% of an inch

For compact crystal sets, especially of the ortable type, and also for reflex sets, this detector marks a great advance over pre-vious types, and exhaustive tests have shown that the device is all the makers claim for

GERMANY

-C. A. Oldroyd.

Authors'

Rebellion

An authors' rebellion has broken out in Berlin against the broadcast companies, who refused to pay royalties for broad-casting the works of the authors. The re-

volt is headed by the famous playwright, Herr Gerhart Hauptmann, and his colleague, Herr Hugo von Hoffmannsthal.



on the French receiver is unique in that there is a scale provided so that the exact setting of the coils can be logged, making the receiving



ROUMANIA

It is announced that a Lots of Red bill just put before the Roumanian Parliament at Tape in Roumania Bucharest states that all private persons who wish

to possess a radio set must, in addition to applying in person for their license, bring with them their baptismal certificate, a prooof Roumanian citizenship and a statement of their good moral character from a responsible religious leader. Licenses for sets are granted for one year only and the applicant has to pay for the visit of several inspectors before he is allowed to touch his apparatus.



the snow.

NORWAY

roadcasts Ski Events

One of the first events broadcast by the new sta-tion at Oslo was the Na-tional Ski Competition at Holmenkollen, Microphones were carried some ten miles on sleighs and placed just under the ski run so that listeners could hear the sound of the skis on

The induct shown in the ac-companying illus-tration is designed tration is designed especially for square law con-densers. Besides the winding style there is another new feature, which is that the cell is is that the coil is mounted on its plug with a swivel it may be swung to any angle. These English coils are made in inter



European Wave-Lengths

The Technical Committee on Broadcasting has prepared a new international scheme of wavelengths which, it is hoped, will mitigate the present interference experi-

enced by European stations. The older and more important stations will, as far as possible, retain their present wave-lengths, and experiments will be conducted after broadcasting hours to test the efficiency of the new scheme. The results of these experiments will then be considered at a further conference to be held subsequently in Geneva.



AUSTRALIA

Radio Increasing in Popularity their sets

Radio is growing more and more popular in Australia every day, especially in the country districts where farmers may obtain the latest market reports by means of

eir sets.
The Australian broadcast stations are divided into two classes—A and B. The former participate in the money collected from license fees while the latter are run by private firms.

The main class A stations give a nine-hour service daily, using five-kilowatt Aus-tralian-made broadcast transmitters. In this class are:

In this class are:
2BL, Sydney, W.L. 353
2FC, Sydney, W.L. 1100
3LO_F Melbourne, W.L. 371
5CL, Adelaide, W.L. 395
6WF, Pearth, W.L. 1250 There are six class A stations and thirteen

class B licensed in Australia. The radio receiving apparatus used is mainly British or American, although sev-eral Australian firms manufacture complete

sets and component parts. -C. W. Corbin.

353 meters



JAPAN

There are three broadcast stations in Japan: Tokyo, Osaka and Na-gova. At the beginning Radio

Conditions of broadcasting in Japan the Department of Communications issued a strict regulation concerning radio reception. No set may be used unless approved by the authorities. Therefore, it was almost pro-hibitive to import radio apparatus from foreign countries. However, soon after the inception of broadcasting at Tokyo, the regulation was changed and now any set or part may be used without securing permission from the authorities.

Since then there has been a tremendous increase in imported sets and parts, over two million yen having been expended, chiefly in the United States, as Japan has adopted American standards in radio. the other hand, home manufacturers also

were very busy during March, April and May, but at present have become somewhat idle, because of overproduction, and naturally prices have dropped considerably. At pres-ent there are over 40,000 subscribers in the Tokyo district, 25,000 at Osaka and 5,000 at Nagova. Besides these there are an equal number who have not taken out any license. A few other broadcast stations may be erected in the western and northern parts of the country. It is reported that there are over 600 radio dealers in Tokyo and another 400 radio dealers scattered throughout the Empire.



These carriages are so constructed that of different sizes may be substituted.

Esperanto Broadcast Lessons By JAMES DENSON SAYERS*

This is the second of a series of three Esperanto lessons to be broadcast from Station WRNY on 258.5 meters. Mr. Sayers will broadcast this lesson the evening of October 24, 1925.

Comparisons are made in Esperanto as follows:

pli . . . ol, more than: Lakto estas pli nutra ol vino, Milk is more nutritious than wine. malpli . . . ol, less than: Vino estas malpli nutra ol lakto, Wine is less nutri-

tious than milk. la plej, the most. la malplej, the least: El ĉiui liaj amikoj.

Johano estas la plej saga, kaj George da malplej saga, Of (el, out of) all his friends John is the wisest, and George the least wise. ju pli . . . des pli, the more . . . the more: Ju pli li lernas, des pli li deziras lerni, The more he learns, the more he

wishes to learn.

ju malpli . . . des malpli, the less . . . the less: Ju malpli li laboras, des malpli li recevas, The less he works, the less he gets (receives). ju pli . . . des malpli, the more . . . the less: Ju pli li fariĝas granda, des malpli

li estas forta, The larger he becomes the less strong he is. ju malpli . . . des pli, the less . . . the ore: Ju malpli li pensas, des pli li parolas, The less he thinks, the more he talks.

ADVERBS OF TIME Adverbs of time are words that tell when, where or how some action took place. Ili sidas tie, they sit there; si restos hejme, She will remain at home;

Li iros vespere, He will go in the even-Hieraŭ, yesterday; hodiaŭ, today; mor-

Adverbs may be formed from any word Adverbs may be formed from any word whose sense admits of it, especially from adjectives, by means of the adverbial termination e, as bona, good; bone, well; antaŭ, before; antaŭe, previously or formerly; mateno, morning, matene, in the morning; sekvi, to follow; sekve, consequently (lit, followingly). AFFIXES AND CORRELATIVES

Two vastly important parts of the

Esperanto language are the affixes and the ingenuous table of correlatives, es-pecially the former. The root words in Esperanto are comparatively small in number, but their power of variation into almost infinite nuances of meaning add tremendously to the vocabulary. Con-sequently, one knowing about one thous-and of the more frequently used Esper-anto roots should command a vocabulary of twenty-five thousand words, a wider in any national language.

command of speech than ever possessed In any national language.

A few of the more often used affixes will be explained here, but because of the limited space and time on the air, the full list of nearly forty affixes will not be given here. As every affix is a separate and distinct word in itself and can therefore be found in any inexpensive Esperanto dictionary, and as you will each have to acquire some such dic-tionary for further use of Esperanto, it will be easy for you to learn the others. The "Edinburgh" dictionary, which costs only 75 cents, contains a list of the affixes on page IX. As the dictionaries do not always give the table of correlatives, it ill be given here.

Mal—. Perhaps the most important

affix in Esperanto. It reverses the meanmeaning, thus reducing very extensively the number of arbitrary words one must Examples: Bona, goo memorize. bona, bad; dekstre, right, maldekstre, left; helpi, to help; malhelpi, to hinder; fermi, to shut, malfermi, to open; varma, warm: malvarma, cold.

-in-, This suffix indicates the feminine sex: Viro, man, virino, woman; onklo, uncle, onklino, aunt; knabo, boy, knabino, girl; patro, father, patrino,

-ist-. This suffix denotes one who occupies himself or herself in some activity professionally: Jugi, to judge, jugisto, a judge; kanti, to sing, kantisto (kantistino) a professional singer; ku-raci, to cure, kracisto, a physician. —ig— and —ig—. Two much used

-ig- and -ig-. Two much used suffixes. -ig- means to compel or cause suffixes.—ig— means to compel or cause some one or something to do that which the root indicates.—ig— means to become so or such oneself. Thus from ruga, red, we get rugigi, to become red, to blush; klarigi, to make clear, to explain, klarigi, to become clear; sdigi, to cause to be seated, to seated, to set some one; sdigi, to become seated. (Bonvolu sidigi, please be seated.) -eg- and -et- are opposites. -eg-

(Continued on page 738)

TABLE OF CORRELATIVE WORDS

	I Indefinite. Some, any.	K Interrogative Relative What, which.	T DEFINITE. That.	C Collective. Each, every, all.	Nen- NEGATIVE. No, none.
QUALITY Kind of (Adjectival)	Ia Some or Any kind	Kia What kind As	Tia That kind Such, as	Cia Each kind Every kind	Nenia No kind
Morrve Reason (Adverbial)	Ial For some reason Any	Kial Why	Tial For that reason Therefore	Cial For every reason	Nenial For no reason
TIME (Adverbial)	Iam At some time Any time Ever Once	At what time When	Tiam Then	Ciam Each time Every time Always	Neniam Never
PLACE (Adverbial)	Ie Somewhere Anywhere	Kie Where	Tie There	Cie Everywhere	Nenie Nowhere
Manner (Adverbial)	Iel Some way Somehow	Kiel How In what way As, like	Tiel In that way So	Ciel In every way	Neniel No way
Possession (Pronominal)	Ies Someone's Anyone's	Kies Whose	Ties That one's	Cies Each one's Everyone's	Nenies No one's
A THING NOT SPECIFIED (Noun)	Io Something Anything	Kio What thing	Tio That thing	Cio Everything	Nenio Nothing
QUALITY (Adverbial)	Iom Some A little	Kiom How much	Tiom So much	All the quality	Neniom None
Individuality (Pronoun)	Iu Someone Anyone	Kiu Who Which	Tiu That (person or specified thing)	Clu Each Every Clui	Neniu No one Nobody

New Designs in Radio Receivers



By G. C. B. ROWE

Two radio receivers are described below that have incorporated several new features of both electrical and mechanical interest.



In last month's RADIO NEWS we showed our readers a few of the newer designs in radio receivers, and in this present article are two more.

Just as the automobiles, at the beginning, were oscillating from chain to gear drive, or from overhead valves to valves underneath, so radio design is beginning to try the unbeaten paths.

But note that the tendency is toward simplicity of control. In the near future radio receivers will be going down the endless belt in the process of assembly just as the Fords do today.-EDITOR.

HE majority of the receivers that have appeared on the market this fall have had some innovation, in either their electrical or mechanical design. Some of the sets have been vested with new tuning controls and a reduction in their number, others have circuits that are possible only because of the improved apparatus employed, while others are of interest because of the general method of design and manu-

facture. In this last classification belongs the re ceiver shown in the photographs below. The circuit used is basically the tuned radio frequency circuit of Shloemilch and Von Bronk and has six tubes, two stages of tuned radio frequency amplification, detector, one stage of transformer coupled and two stages of resistance coupled audio frequency amplification. The set is licensed to use 88 U.S. Government radio patents that are owned by the U. S. Navy Department.

UNUSUAL FEATURES

Instead of the usual type of wiring using bushar the connections in this set are made with wide nickeled bronze strips, which are fastened securely to the sub-panel by eye-lets. The sub-panel is attached to the aluminum panel at such an angle that it is hori-zontal when the front panel at an angle of 60 degrees. Under the sub-panel are mounted all the electrical parts and above it are mounted by eyelets the six tube sockThe top of the re-ceiver. The strips shown below form tube sockets, elim-inating over twen-ty soldered connec-





The "chassis", or the sub-panel showing the conrs and battery leads.

The panel view of the receiver. This panel is of aluminum finished in black, with silver etching.




pieces of continuous metal take the place of the usual contact strips and connecting wires. All connections that carry plate voltage, as well as the repeating resistance of the two resistance coupled amplifiers, are mounted on one-inch high bakelite insulators. All resistances and condensers in the amplifier unit are directly connected to the strips that serve as the contacts for the tube prongs, thus eliminating leads and soldered connec-

THE CIRCUIT

The circuit, as has been mentioned above, is one employing tuned radio frequency. The condensers that are shunted across the radio frequency transformers are those of the straight-line frequency type, making the ter, as there is a constant difference in log-ging throughout the entire range. Another feature that facilitates tuning is the fact that the head-phones can be inserted into the jack in the plate circuit of the first stage of audio frequency amplification and at the same time the loud speaker may be operating from the sixth tube of the set. This means that it is possible to have the loud speaker in one part of the house and in another part the receiver, which may be tuned without disconnecting the loud speaker. The insertion of the phones in the first stage of audio frequency does not appro ciably impair the volume of the last stage's

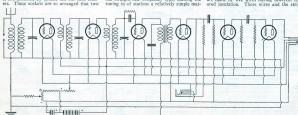The exterior connections of the receiver are made by five wires having different col-ored insulation. These wires and the strips




that are connected to the phone jacks are the only soldered connections in the set. The panel is 28 inches in length and is mounted panel is 28 inches in length and is mounted in the cabinet so that it slopes at an angle of 60 degrees. In the mahogany-finished cabinet there is space provided for 'B' bat-teries behind the sub-panel. The antenna which is recommended for this set is one about 75 feet long, although an indoor antenna may be used. This means that the any type of antenna.

SIMPLIFICATION OF CONTROLS

Another receiver that has new features in both the electrical and mechanical details in both the electrical and mechanical details is shown in the photographs below. This receiver employs five tubes, which act as two stages of radio frequency amplification, detector, and two stages of audio frequency and two stages of audio frequency. amplification.

Instead of using variable condensers to tune the three inductances before the detector tube, as is usual with receivers of this type, the secondaries of the coupler and R.F. transformers are wound in two sections, one on the same tube as the primary and the other on a smaller tube which rotates within the larger one. These three variable secondaries are mounted on a shaft that runs parallel with the front panel and is con-trolled from the front of the panel by the large dial, which operates the shaft by

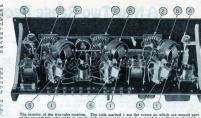

of the accordaries; the parts, 2, are the inductance tandem switches; 3 and 4 are filament rhousatts; the condensers, 5, are the semi-fixed capacities across the secondaries, and the coils marked 6 are the primary and part of the accondaries.

formed by this knob and the finer adjust-ments made by varying the movable secondaries.

The variable condensers that are shown shunted across the secondaries of the radio

same with condensers on the same shaft. MECHANICAL CONSTRUCTION

The sub-panel is at an angle of 90 degrees to the front panel, both of which are of bakelite, and on the sub-panel is mounted all the apparatus. This apparatus is so mounted that there is a minimum of pos-Panel and cabi sible interference and also provision made for the shortest possible connections. The mounting of the tube sockets is unique and tube receiver, the interior of which eliminates microphonic noises to a great extent, if not entirely. On two sides of the sockets there is a brass bushing about 1/4inch high to which is secured a thin strip of insulating material. From the other two sides of the socket are suspended two other strips of the same material, which are inter-woren with the first two mentioned. These strips successfully take up any vibrations that might be transmitted to the elements of the tubes, producing the annoying noises.

The receiver is housed in a cabinet 28x1134 inches. Binding posts are provided for ex-ternal connections at the rear of the subpanel and these connections are made through the rear of the cabinet. Two of the fila-ment control rheostats are mounted on the front of the panel and the other two con-trols are placed inside the cabinet at the


otes that the thr

All the exterior from unsightly Photos courtesy of Kellogg Switchboard and Supply Co.

ondaries that are wound on the larger tube is tapped at nine places, and these taps are connected to three inductance switches. The variable arms of these switches are also connected and controlled from the front of the panel by means of the small knob marked "Wave Zones." The rough tuning is per-


The upper dotted line i

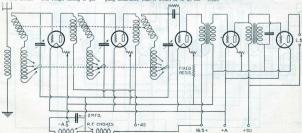frequency transformers and the coupler are variable in form only, as once they are adjusted for any given antenna it is unnecessary to change the settings. By this means it is possible to have but one control for tuning, as it is much easier to operate a gang inductance than it would be to do the



inductances are operated by the same dial, and the same is also true of the three inductance switches. The three variable condensers, after being once adjusted, remain untouched.

A New Two-Range Receiver

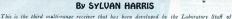



previous issues of Radio News we have presented to our readers several methods of covering the present wave band in such a way as to overcome the difficulties due to crowding of the stations. The first arrangement was presented in the form of the "Three-Range Receiver" in the July issue of RADIO NEWS. The wave range of this receiver was from 140 meters to 600 meters in three steps, so arranged that each step overlapped the other. The change from one step to the other was accomplished by means of one switch of special design. These

610

ranges were: 140 to 240 meters, 220 to 420 meters and 400 to 600 meters. In each of these steps the whole condenser was used, so that by this means not only was a very great wave band covered, but it was covered in such a way as to eliminate

crowding of the stations. The reason for

this is that the whole range is spread over three revolutions of the condenser dial. This

circuit became exceedingly popular with our readers, if the hundreds of letters we have

received from them offers any criterion for

The need for multi-range receivers is ex-plained in the article entitled "Extending the

judgment.

RADIO NEWS. The wave-length range is changed by an ingenious switching arrangement. cast Stations on 150 Meters") it will be necessary to do this in two or more steps. The "Three-Range Receiver" was a three-

circuit tuner. The problem in connection with this circuit was merely the design of a special switch to perform the required functions. The switch as presented in that article, designed by the writer, works very well; it is doubtful if a more efficient arrangement has been presented in the way of circuits for a long time.

THE PROBLEM IN R. F. AMPLIFIERS The problem in connection with radio frequency amplifiers is quite different, as there are several circuits in which the wave range must be split up. They may be split up easily by using a separate switch to tap each R.F. coil, but obviously this does not agree with the modern tendency to make the con-

The arrangement is shown in Fig. 1, which is a sketch of the switches. The construc-tion is very simple, as can be seen from the illustration. The switches are made, in the ordinary manner, of a few switch points, a switch contact lever, a long bakelite or hard

rubber rod, and a few odds and ends. The reason for separating the various switches from one another is obvious to anyone who knows the difficulties that arise in radio frequency amplifiers from inter-stage coupling. If it were not for these R.F. difficulties, it would be feasible to bring all the tan wires into a single switch on the panel, instead of using the three switches, as shown here. Obviously, if this were done, the wires in the various tuned circuits which be very close together and difficulty might be experienced in controlling the tendency toward self-oscillation.





trols as few as possible. The range may be split up easily by using a number of plugin coils of various sizes, but this likewise does not help to preserve simplicity of oper-


The simplest way of accomplishing the desired result, as far as the writer is aware, is by the means described in this article. Each of the tuned R.F. secondary coils is tapped at a convenient point, depending upon how one wishes to split up the range, and all of these tapping switches are controlled

WIRING AND COILS

The wiring diagram is shown in Fig. 2 It will be seen that this is an ordinary five-tube circuit, with two stages of R.F. amplification, electron tube detector, and two stages of audio frequency amplification, with potentiometer control. The switches are plainly shown on the diagram, together with the rod of insulating material which controls

The coils used in the set are ordinary R.F. tuned transformers, which anyone may wind for himself upon a pin-board. The average diameter of the coils is 3 inches, the primary has 6 turns, and the secondary 39 turns of No. 24 D.S.C. wire. The variable condensers used were of the straight-line frequency type, having a capacity of 0.00037 microfarad. The secondaries are tapped at the 15th turn from the grid end of the coils. The general layout of the apparatus may be

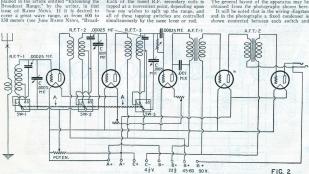obtained from the photographs shown here It will be noted that in the wiring diagram and in the photographs a fixed condenser is



Circuit diagram of the receiver. The three switches are interlocked by the rod shown in broken lines. Note especially the connections of the fixed condensers in each tuned circuit.

the coil. The reason for this can be determined from a study of the two wave ranges which are obtained by means of the tapping switches, when the fixed condensers are not used. Without the fixed condensers the upper range is about 500 meters to 240 meters. The lower range is from about 370 these ranges that the wave-lengths between 370 and 240 meters can be tuned in on either position of the switches.

This is not advantageous, for part of the circumference of the dials is wasted, and it is not possible to take full advantage of the ability of the system to separate the stations on the dials to the fullest extent. For this reason the lower limit of the upper range is raised to about 350 meters by means are then:

Upper range 570 to 350 meters Lower range 370 to 130 meters

It is seen that the overlapping of the two ranges is now only between 370 to 330 meters. This is sufficient overlap from the states of the control of the control of the two the control of the control of the is small enough so that no detriment is offered to the station-separating ability of the receiver.

MANY VARIATIONS POSSIBLE

The idea is subject to many variations, as one may imagine, and furthermore, may be one may interest, and furthermore, which is switching or tapping is feasible. The switching or tapping is feasible. The switches may be every easily tied together by writes or springs, or they may be constituted to the switching of the switching



A diagrammatic view of the above photograph. The fixed condensers are not shown but the construction of the switch is plainly indicated.



sible to make the set cover almost any practical range desired.


The advantages of using arrangements of

this user have seen discussed before in Rxoo News, especially in connection with the articles mentioned above. Not only are the stations spread out over two revolutions of stations spread out over two revolutions of vantages of the straight-line frequency conessers, as outlined in the writer's article on that subject in the August Rxoo Nxos. of course, the system here described is not of course, the system here described is not any type may be successfully used, and it will be found that the stations will be spread a-plenty, even when using the ordinary semi-This receiver has been used for some time This receiver has been used for some time

This receiver has been used for some time by the writer and very satisfactory results have been obtained with it, especially in the way of reducing interference. Interference is generally more noticeable in the large cities where several broadcast stations are located near each other. With this receiver it is a very simple matter to tune out the local stations and receive distant stations.

As shown in the photographs, little space on the baseboard was wasted. It, is, of course, not necessary to use a small a baseboard as points about this receiver is the small space at takes up, in spite of all the apparatus used in it. The layout of apparatus is such that several tuned circuits. The only place where difficulty was experienced was in locating the audio frequency transformers, and for this control of the course of the

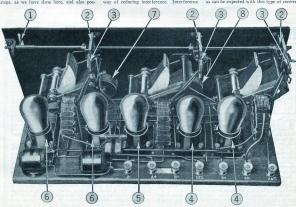The quality of reproduction is very good, and the distance the set brings in is as good as can be expected with this type of receiver.



1, switch lever; 2, switches; 3, fixed .00025 condensers; 4, R.F. amplifiers; 5, detector; 6, A.F. amplifiers; 7, rheostat; 8, potentiometer. S.L.F. condensers are used. Note the long bakelite rod operating the three switches simultaneously.

Static and Weather Forecasting By S. R. WINTERS

DO not think anyone can question that there is a relationship between 'static' and prevailing weather con-ditions," declared E. B. Calvert, Chief of the Forecast Division of the United States Weather Bureau, in an exclusive interview with this writer, in which he dis-cussed the phenomena of atmospheric disturbances as they pertain to radio reception.
"The Weather Bureau," continued Mr.

suggesting that it engage in forecasting indications favorable or unfavorable to reception, based upon weather c The Weather Bureau, however, has taken the position that 'static' is apparently due to causes other than those that might be indicated on the weather map.


"Undoubedly, so many factors are involved that we would not feel justified in engaging in a program of this sort until such time as the Weather Bureau is able to collect sufficient statistical data to have the matter thoroughly studied and investigated, thus having assurance that reliable forecasts of the kind desired can be made. Such an investigation would require considerable expense in the collection of data, the compiling of same, and the personnel for conducting the inves-tigation. At this time the Weather Bureau has not the funds to devote to the project.

RADIO MAY FORECAST WEATHER This government bureau, the largest weather-forecasting organization in the

weather-forecasting organization in the world, is not prepared to deny or confirm the theory that radio instruments in the future may be used in foretelling changing weather conditions. However, the factors are so variable that the crashing noises in the radio receiver cannot be accepted as a reliable index of what the weather will be on the morrow. For instance, during the unusually severe when a cloud as big as Again, the thundering, crashing noises that interrupt the music in your radio receiving set may be attended by an electrical storm in the making. All of which would seem to indicate that "static" is not only a bugbear to radio reception but is extremely erratic in its performances.

The Weather Bureau would contend that "static" is equal to X— an unknown quan-tity. That is to say, while there is a definite relationship between "static" and the pre-vailing conditions of the weather, other factors are involved which befuddle any attempt at a well-defined definition of the causes and actions of this enigma and chief obstacle to radio reception. Even if the origin and factors responsible for "static" were established.

(Continued on page 740)

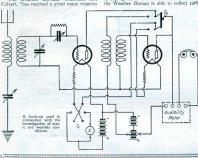

NEXT MONTH—The Regenerative Interflex

What An Ideal Set Should Do NE single, solitary control-NO MORE!

A set your grandmother can operate. Tremendous volume from 3 tubes, equaling or better-

ing most 4-tube sets. No squeals, no howls.

A great distance-getter-1.000 miles under average conditions on the loud speaker.

A set adaptable to all local conditions. Extreme sharpness in tuning, so that you can separate locals

from DX stations. All this and more is accomplished in the Regenerative Interflex fully described in the December issue.

HE radio public has been misled and bamboozled right and left, by radio constructors and publishers who ought to know better, in regard to single-control sets. Right along, this or that article appears, featuring a single control, when in reality the set has as many as seven controls. Perhaps it has a single tuning set nas as many as seven controls. Perhaps it has a single tuning dial, but stuck away somewhere there was a potentiometer, a "tone control," a "stabilizer," several handfuls of rheostat knobs, and what not. These all masqueraded under the name of a "single-control set."

Even if a number of controls are filament rheostats, these are,

Even it a number of controls are filament rhoostats, these are, nevertheless, controls, because in most of these sets no DX can be effected unless the filament voltage is regulated carefully. So we ask the question, "Why dub a 7-control set a 1-control set, when it is nothing of the sort?" Any time, hereafter, when you see such a set labeled with such

misleading name, you will know what to think of it. There has been entirely too much "bunk" and too much deception in sets of this sort. A one-control set should be just what it is called—ONE CONTROL, (ONE DIAL.) AND NOTHING ELSE. You should, by turning the one tuning control, be able "maybe," and without freak conditions. IN OTHER WORDS,
THE SINGLE DIAL SHOULD TAKE CARE OF EVERYTHING. This is the ideal that Mr. Hugo Gernsback has set in

many of his writings and editorials for the past five years.

In the October issue, Mr. Gernsback described the Balanced Interflex, which was the FIRST multiple tube set with but a single control. Good as this set is, which is best proved by literally thousands of letters that are coming in to us now, a still better set is now promised to the radio fan who builds his own. THE REGENERATIVE INTERFLEX is such a big thing that we rish to herald it to you now in advance.

Mr. Gernsback has been working on this set all summer long, and has now designed a regenerative receiver that has a fixed tickler of an entirely new kind, which, once adjusted, need not be touched any more over the entire broadcast range-someth De touched any more over the entire proadcast range—something which has never been accomplished before. In order to do this, a new instrument had to be designed, which is very simple and which can be readily made by anyone. Mr. Gernsback has termed this the Plero-Coupler. It does a variety of things that the usual variocoupler does not accomplish.

Moreover, the particular set in which this coupler is incorpo-rated can be BALANCED TO YOUR LOCAL CONDITIONS, whatever they may be, so that the set will work at its highest efficiency, an accomplishment which was not possible before. So efficient is this new circuit that a one-tube set will work your loud speaker on local stations at a fair volume, while with the 3-tube set also described in the December issue, it is possible to receive stations as far as 1500 miles on the loud speaker under practically all conditions. The set has been tried in operation not only in New York City, but in several other cities as well, in order to make sure that it works under most adverse receiving conditions.

This particular set does not howl or squeal despite the fact that it is regenerative, another great point in its favor. Stations snap in and out with tremendous volume and, best of all, the set is highly selective and easily separates stations that are close together.

The Raytheon Rectifier

Another type of rectifier tube, filled with helium, wnich permits full-wave rectification with one tube.

N THE September issue of Ramo News we described a type of cold-cathode, gas-filled rectifier tube which is new to the American market. ("A New Noon-Filled Rectifier Tube." Ramo article we mentioned the jact that the non tube was only one of a number of new devices applying well-known principles of gas conduction to the problems of ratio. The problems of the problems. The problems of the problems. The problems of the problems o

rest to rigio an extent be used to home and the control bearing a control bearing a

atom is an extremely minute machus can mining four protons, the deements of postive charge, and two electrons, the elemenary units of negative charge. This nucleus are more marked to the control of the context of the control of the control of the two units. Outside the nucleus are two electrons moving our paths not yet entirely charge so that the whole atom is electriccharge so that the whole atom is electricthary that the structure of the context of the control of the context of the control of the context of the control of the electrons. It is found that an electron and Detectors, Ramo Niwes for Cerolor, 125 yet can knock off one or both of the control of the electrons from a helium atom. It drop of about 25 wilds can just knock off one of the electrons from a helium atom. It has been converted into two ions, one negative, the separated electron one of the positive, the residue of

the atom.

Now the conduction of electricity through a gas depends on this ionization. If the gas is not sonized it acts as an excellent insulator, but when ionized it is a first-class conductor. It is very easy to see how conduction takes place through an ionized gas. If the plates A and B are charged positively and negatively, respectively, and ions are formed in the gap between them, the plus



A sucessful "B" battery eliminator comprising the Raytheon tube and associated filter circuits.

Let us suppose that we have a cylindrical the like that shown, containing two metal disc electrodes one inch in diameter metal disc electrodes one inch apart. Suppose the tube contains belium at about 1/100 normal atmospheric pressure. The general construction of the atoms of helium is known to be fairly simple. At the center of each

ions will be drawn to B and the negative ions to A and thus a charge will be transferred from one side charge will be transferred from one side to the desired from the side current will flow across. On the other hard, in the absence of ions, it is impossible for any charge to pass. We see, therefore, that ionization of the gas in a circuit gap is an absolutely necessary prerequisite to conduction




The Raytheon Rectifier.

Courtesy the American Appliance Co.

of electricity access the gap. This recept agreement of the company pollumany formation can be brought about in a number of different ways, as, for example, by passing a beam of X-rays or example, by passing a beam of X-rays or example, by passing a beam of the company of the


(Continued on page 744)

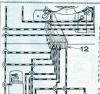

THE BALANCED INTERFLEX CIRCUIT In the article entitled the BALANCED

INTERFLEX FOUR, described by its inventor, Mr. Hugo Gernslack, in the October RADD NEWS, page 442, a mistake in drafting was inadvertedly allowed to go through. This mistake, though annoying, will cause no diagram shown here is the correct one, the arrow pointing to the jack marked "12" indicating where the error occurred. The correction involves merely interchanging the placemal transformer leads (the two bottom

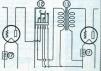To facilitate the use of the full-page layout and the wiring diagram of this circuit, shown on pages 442 and 443 of the October



RADIO NEWS, the small sketches of this jack, shown here, may be cut out and pasted over their proper places in the diagrams on those pages. By THEODORE H. NAKKEN

A unique and novel system of recording sounds on photographic film for subsequent reproduction or transmission by radio. The Gehrke tube used in these experiments is something new to the general reader but has been used successfully by investigators.

N the first article of this series the electric cells in general use, and in particular such a cell of his own invention,

614

called the Luminotron. It seems not at all necessary to dwell any more on the properties of this cell-be it sufficient to say that the cell is of the alkaline type, and that the photo-electric current is not utilized, even if such a current be present, but only the fluctuations of potential of the photo-actinic plate.

From a previous study of the bibliography it became evident at once that if the various problems related to the photo-electric phe-nomena and its applications could have been solved with the photo-electric cells available, they would have ceased to be problems. It is astonishing to learn the amount of labor and patient research, inventive ingenuity and money spent on these problems. Therefore, way of keeping the quality at its highest point was to adjust the "C" battery potential battery potential till the plate current remained steady. When this condition had been attained, there would be movements of the meter pointer only when the amplifier blasted, and this was always due to some other reason than pure amplification. The most important part in the construction of this unit was the com-plete shielding of stages and of the whole amplifier, as otherwise extraneous noises and alternating current hum would drown out all other sounds. Another important consideration for clarity is the use of very out all other large coupling condensers in the resistance coupled stages. The condensers in the amplifier sketched were two microfarads

It was perceived that there are two appli-cations of photo-electric cells which are of the greatest importance: The recording



The Gehrke tube used in making these experiments. Sides: A film strip taken. owing the impres ons created by a playing violin.

Gehrke

the author decided, that if all these carefully worked out schemes remained rank failures, there could be but one reason for this failure: the photo-electric cell. And this was the reason that the cell was made the nucleus of all experiments to follow.

PROBLEM OF AMPLIFICATION

The question of amplification is of great importance, and had to be solved before any other work could be taken on. Various experiments were made with different systems and it was found that resistance coupled vacuum tube amplification promised the best results but too many steps were necessary for good volume. Therefore, a compromiswas made and the final equipment consisted was made and the final equipment consisted of two stages of transformer coupled am-plification and two stages of resistance coupled amplification. The complete diagram of this unit is given in Fig. 1, where it should be specially pointed out that omit-ting the "C" battery both in the transformer and the resistance coupled stages resulted in grievous distortion. It should be stated that the amplifier was at all times so connected that a milliammeter indicated the plate current consumed. It was found that the easiest and reproducing of sound, and the transmission of photographs or copy matter, either by wire or radio.


RECORDING

The first problem to be attacked, however, was the talking and musical film. In other words, how to record sound by photographic means in such a way that minimum distortion occurs both in the actual record-ing and in the reproduction by means of

photo-electric cells. It is easily understood that the reproduction of a photographic sound record is a simple matter once the photo-electric cell and the amplifier are in working order. Fig. 2 is given a schematic representation of the arrangement generally used for this

purpose.

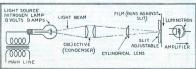The light from a strong electric lamp is concentrated by means of an objective and projected upon a very narrow slit. The width of this slit is determined by the speed at which the film is run behind it, and the maximum number of individual sound frequencies originally recorded. If, for instance, the film were made at a speed of 12 inches a second, and about 4,000 vibrations



The optical system used in these experiments and the source of light for illuminating the luminatron

.

.


.

.

.

.

.

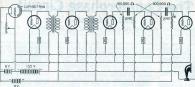

A special amplifier, shown above, was required to amplify the small output of the photo luminotron.

Tube noises and distortion must be kept off the system.

were the highest frequency registered on the film, the slit could have a width of about 1/500 of an inch. In this manner a small amount of light will fall through the slit and through the film, which runs directly and through and through the nim, which runs cirectly behind this slit, and the light, after passing through the film, will then be modulated in accordance with what was recorded on the film. This light is allowed to fall upon the photo-electric cell and acts upon it, giving rise to current fluctuations. These fluc-tuations are amplified and used to actuate a loud speaker. The more natural the record, and the more accurately the cell reproduces the light fluctuations, and the more distortionless the amplifier functions, the more natural will be the reproduction by the loud speaker. Thus it is seen that the success of the film depends first upon the recording, second on the reproducing appa-



The simplicity of the method is shown in this schematic drawing.

The first thing encountered in the recording of the sound is the conversion of the sound waves into some other form of energy -preferably electric current vibrations. After this conversion of the sound waves into microplione currents, we shall, in all probability, feel the necessity for amplifiers for these minute currents, if the sound to be registered is to arrive from a certain distance, and is not projected directly into the microphone.

LIGHT VARIATION

We shall then use the original soundwaves, or their electrical equivalent, either directly or after amplification, to vary the amount of light falling upon a registering film through the same kind of narrow slit as described in the reproducing process. this respect there are several the simplest methods is to use a mirror in such a way that a greater or smaller amount of light from a steady light source reaches the film. One has only to imagine a small, light mirror stuck on the diaphragm of a SPEECH loud speaker telephone or fastened AMPLIFIER to the string of an Einthoven gal-MICROPHONE

suitable manner, or again one can use the string of such a galvanometer a sort of photographic shutter, etc. will be clear that there is an abundance of ways of using electro-mechanical means for this manner of sound recording, and all of them can be made extremely successful, because reproduction has to be done with an ordinary loud speaker. Under present conditions it is extremely


easy to make sound records this way, only have to select one of the programs daily in the air and, instead of receiving it on the loud speaker, the signal received can be used to record the sound by means of simple apparatus indicated above. After such a record has been developed, it can be run off again and again, and be reproduced by means of a photo-electric cell and ampli-

ed by the audio stages of a radio set An entirely different way of recording sound photographically is the use of the cur-rents representing the sound waves to vary the light source itself. In this connection may be stated that the phonograph of future will be an instrument utilizing films as records, and the quality of reproduction will be almost, if not completely, perfect. As will be shown later, there is but one appliance which must be mechanical now. the loud speaker.

USE OF INCANDESCENT FILAMENT

In attempting to modulate the light source by means of the sound currents seems but natural that inventors turned to an incandescent filament, which was caused to glow more or less brightly as varying currents flowed through it. It seems that almost no inventor working on the subject of sound photography could resist this apparently easy and plausible solution. would be possible to name about a dozen or more inventors who have secured pat-ents on a bulb containing a fine filament, the luminosity of which would be caused to vary by speech or sound currents.
(Continued on page 722) The de-

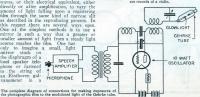Examples of the strips taken by this method are shown at the sides of these pages. The strips are records of a violin.



The Counterphase Circuit

By J. T. Carlton

A two-control receiver employing the toroidal form of coils for coupling the R.F. stages. Several novel features are embodied in the receiver which will be of considerable interest to all.

HE ideal receiver, under present con-ditions as viewed from the stand-point of the broadcast listener, should be capable of operation with extreme ease, selective enough to receive any station without interference from other station, and sufficiently sensitive

insure coast-to-coast reception. must also Such a receiver, moreover, must also function without impairment of the natural qualities of the program to be received; in other words, faithful reproduction of tone

quality is absolutely essential.

To appreciate the basis on which the circuit described herewith is founded it necessary to turn back for a moment to the point in the development of radio frequency amplification where "adding a stage of amplification where "adding a stage of radio" to a regenerative set was considered an accomplishment. Greater range became possible because of the fact that signals primarily too weak to register an effect on the detector tube were strengthened sufficiently for detection

Adding more and more stages became the immediate aspiration of the multitude. troduced, resulting in more efficient apparatus, and a consequent increase in receiver

efficiency and selectivity. WHY "PEED PACK" CIPCUITS OSCILLATE

But unfortunately, as increased efficiency became manifest the difficulty that is com-monly known as "oscillation" also increased It was found that within in importance. the tune of each stage of an efficient lowloss set such amplification would occur that excessive plate energy would flow to the grid of the circuit through the capacity existing between grid and plate elements. The consequence of this feeding back of excess energy was undesirable whistles and howls whenever the receiver was in reasonance or exact tune with a signal,

When in resonance with an incoming sig-

small resistance to the flow of current se up by the signal to which it is tuned; this condition, of course, prevails where the essential components of the receiver are desential components of the receiver are de-signed for high efficiency. When only a small resistance is offered to the passage of a current a large flow will result. As the energy fed into the grid circuit is amplified through the tube, a much stronger signal current results in the plate or output cir-cuit of the tube. When the set is tuned to resonance with the incoming signal the feedback may become excessive, and swamp the signal current. The circuit is then in an oscillatory condition—the undesirability of which is manifest through the whistles and howls that ensue. To maintain the maximum signal current

in the grid circuit we must maintain a condition of reasonance in the tuned circuit, but to allow the use of the low resistance grid trol on the lower wave-lengths, and with the confusion caused by crowding 90 per cent. of the stations on the lower half of the broadcast scale, the futility of any method of fixed control becomes immediately apparent—whether the system employed be neutralization at some mid-frequency or the introduction of enough losses to stop the trouble even on the lower waves. The former method usually results in whistles and screeches at the lower end and weak amplification at the upper, while the latter plan, although it may give favorable results on the high frequencies, usually leaves the er end dead.

With such considerations in mind, Harry A. Bremer evolved a method of control whereby the circuit might be kept at a point just below that of oscillation at all fre-quencies or wave-lengths. It will be remembered that the greatest amount of am-

Photo courtesy of Bremer-Tully circuit we must have means of limiting their

the arrangement of the apparatus in the

Counterphase receiver Note the position of

the tandem conden-sers and the toroidal

energy feed-back from plate to grid so that the signal will not be swamped by whistles and howls. If the tendency to oscillate were uniform at all frequencies the problem could be solved by any of several methods that are

F-FILAMENT END OF SECONDARY

the toroidal coils which are used for coupling the R.F. stages.

plification, free from howls and whistles, is always secured at this point, THE COUNTERPHASE CIRCUIT

The desire was to provide an adjustable compensation for this tendency to oscillate that would allow maximum results at all "Counterphase" circuit now described pro-vides a practical method of controlling three stages of radio frequency amplification with the same ease and efficiency as if only one or two were used


In this circuit on which patents are pending, semi-variable capacities are employed; that is, the ½ to 30 mmf. condensers are once adjusted and remain fixed thereafter.

The means employed to secure the necessary variations to provide for controlling the oscillation tendency is at once new, simple and ingenious. In a condenser when the capacity is decreased the tendency to oscillate is increased. If we introduce a resistance in series with the condenser we will counteract this tendency. Each stage of amplification except the first, which is not difficult to stabilize, has its grid and plate circuits with like and reverse phase wind-ings respectively coupled by fixed capacities

Each stage is easily adjusted so as to prevent oscillation at any frequency by varying the series resistance. Decreasing the series resistance increases the tendency to oscillate, thus governing the amount of reverse phase energy necessary to suppress oscillations at the high frequencies.

An outstanding advantage of this method lies in the fact that there is no detuning effect noticeable, as a result of which it is possible to tune three radio stages as well if there were any practical reason for desiring to do so.

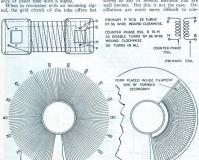as the detector with but two tuning controls instead of four. Indeed, it is possible to go on adding more stages of radio frequency, It is possible that a single control might



be used if one were satisfied to accept the approximations which must always follow when an attempt is made to combine too many functions in one unit. In the writer's many functions in one unit. In the writer's opinion, no normal, two-handed person wants a radio set with only one dial to turn, and has operated either kind of set rather than afterward.

afterward.

Considered as a whole, the efficiency of the Counterphase circuit is no doubt increased because it is unnecessary to introduce any kind of losses into the grid circuit, which is thereby allowed to remain

in a low resistance condition.

The plate circuit inductances are wound in reverse phase to the primary windings of the same circuit. This reverse winding is coupled to an inductance which is in like phase with the grid winding, resulting in a reverse current opposing the plate current sufficiently to retard the flow of current from plate to grid. The values of the two auxiliary inductances are sufficient to feed enough reverse phase energy for the sunpression of oscillations at any frequency within the broadcasting range.

A NEW IMPROVEMENT

The variable resistance, by the way, in-corporates a further new idea. It contains two separate resistance elements on the same Since sensitivity is not required on nearby stations where volume must be reduced, the balancing arm is turned to zero on resistance R-1 before resistance is cut in on R-2 to decrease volume. On the other hand, when sensitivity is required we also want volume, so that the slider arm on R-2 wan, younne, so that the suder arm on R-2 turns back to zero resistance before the other becomes effective. We have, therefore, three stages of radio, a detector and the customary audio stages with but two tuning dials for selecting stations and a variable resistance which needs but slight adjustment to keep the receiver at the maxi-mum point of efficiency on all broadcast The use of a hard detector tube allows all

six tubes to be controlled by one rheostat, and if it is desired this may be placed in side the set, as its particular adjustment may be determined without difficulty, after which it need not be disturbed.

In the schematic circuit R-1 is the resistance that controls the feed-back, and R-2 is a resistance in series with the "B" battery, the effect of which is simply to decrease potential in the same manner in which a rheostat is used in a filament circuit.

Where it is necessary in tuning to cut out resistance in order to suppress oscillations it will be readily seen that turning the knob still further results in cutting down volume, and vice versa. In other words, one resistance arm is always at zero when the other is in effect, and as each rotates about 270



A photo of the Counterphase which employs the circuit diagram shown below.

Photo courtesy the Bremer Tully Min. Co.

there is a total of one and a half turns available between maximum sensitivity and minn volum This newly designed dual resistance



COIL TO HAVE ITO TURNS OF Nº 24 D.S.C. WIRE TO BE TAPPED AT 168-165-155-140 AND 10 TURNS FROM GRID END. NO INSIDE COIL TAPS 1, 2, 3, 4, G, F, & T. NOTE: COIL FOR ANTENNA COIL T A ON COUPLING COILS BETWEEN TUBES T.C.-NOT TAPPED AT 12,3.4. TAPPED ONLY AT T 20 TURNS FROM G.

Specifications of the toroid connected to the

serves a double purpose in that it eliminates one extra control from the panel and sim-plifies tuning. After the station has been selected by the two tuning dials it is only necessary to remember that the resistance knob is turned in one direction to increase sensitivity and volume and in the other direction to decrease them.

Since maximum efficiency at all wave-

lengths is the prime object in this circuit a further refinement is added in the tandem is added to each section of each tandem. make its combined capacity with the main section a trifle greater than the other main unit, and then left permanently in that posi-

By regulation of the second, or panel unit in parallel with the second section it is possible to adjust the capacity to secure exact reasonance between the two It is exact reasonance between the two It is necessary to use the panel "trimmer," however, only when tuning extremely weak signals. For all ordinary tuning it is not

SPECIFICATIONS FOR TOR-OIDAL TRANSFORMERS

Secondary, or outside coil, cross section 1½ inches square, or 134 inches in diameter, if round; 170 turns No. 24 double-covered wire. Core 134-inch tube.

rimary wound on celluloid form made to fit 120 degree inside fila-ment end of secondary consists of 25 turns No. 36 enamelled wire, space wound.

Counterphase winding, 25 turns No. 36 enamelled wire, space wound on same form between pri-

mary turns. Counterphase condenser 1 mmf.

Tuning condensers, double units.

1 mfd. fixed capacities across "B" battery and across "C" battery. .001 mfd. across detector plate to filament.

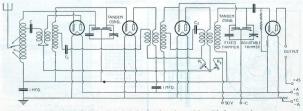


Diagram of the Counterphase circuit, showing how the tandem condensers and the toroidal coils are arranged.

Straight-Line Frequency Dials By SYLUAN HARRIS



The newest thing on the market is the straight-line frequency dial. RADIO NEWS once again gains priority over its contemporaries in giving its readers a first-hand comprehensive view of the subject Mr. Harris' series of articles on straight-line calibration form a complete study of the subject.



Courtery of Radiall Corp.

Courtesy of Bruno Radio Corp

HIS season brings two great developments in radio receiver design, not in the fundamentals, but in the technique. These two developments are in the tuned circuits of the receiver, and are a result of the desire of the users, and the ambitions of the designers, to produce receivers that are more convenient to operate and less dif-

The first of these developments, as everyone knows by this time, is the straight-line frequency condenser. This condenser has been studied in great detail in previous issues of Radio News, beginning with the August, 1925 issue. It will not be necessary, therefore to review here the desirability and convenience of the straight-line frequency characteristic, although it may pay the reader to reread those articles and refresh his memory

on the subject. The next development—the straight-line frequency dial-is a result of recognition denser, and the desire of radio users to out going to the considerable expense of replacing the semi-circular condensers which he already had in his set with the newer type. The straight-line frequency dials are designed to rotate the plates of the semi-circular condenser in such a way that a given speed of rotation for the dial moves the condenser more swiftly on one end and more slowly on the other, so that the S.L.F. characteristics is attained.

THE LAW OF THE S. L. F. DIAL In the previous articles I have written on

the subject of straight-line frequency con densers, I have shown that, in order to obtain such a linear calibration, the capacity of the condenser must vary inversely as the square of the dial setting. In other words, if the of the dial setting. In other words, if the capacity of the condenser at 100 on the dial is 0.0005 microfarad, then at 10 on the dial, the capacity of the condenser should be (10 ÷ 100)2 x 500 or 5 micro-microfarads. At this point it must be remembered that the dial should read 100 when the condenser plates are all the way out, and zero when they are all the way in mesh.



Pinion 2 rotates plate 3, which carries the calibration scale. Pinion 1 moves the sector about the center 6. Pin 4, fastened on sector, thus changes its radius (distance from 8) in arm 5. The smaller the radius the faster the arm (5) revolves about 8, which carries the condenser shaft.

This is the law of the straight-line frequency condenser, and the same law holds true for the straight-line frequency dial. For a semi-circular plate condenser, the capacity of the condenser is directly proportional to the angle through which the plates

are turned.

Now, if the straight-line frequency law is to hold, it is necessary that the capacity C be inversely proportional to the square of the angle of the dial, which, combined with the above relation, requires that the angular setting of the plates be inversely proportional to the square of the dial setting. This, then, is the required law of the straight-line frequency dial. It will be noted that this is the same law as applies to the S.L.F. con-


It is a rather difficult matter to deduce mathematically the shape of a cam or groove which will furnish motion to the condenser plates in accordance with the above law, as the motions in such apparatus involve both rotation and slipping, the combination of which makes the kinematical analysis diffi-Furthermore, the shape of the curve and the premises of the case depend upon the particular mechanical arrangement which is used, and obviously will be different for every individual case. There are a number of mechanical arrangements which may be used to obtain the motion required, which are described in this article.


There are two particular cases in connec-tion with the dials which are being introduced which must be carefully distinguished from one another. The reason for this is that all of them, or nearly all, will probably be called "straight-line frequency" or "S.L.F." dials. Some of the dials will be designed to furnish exactly linear calibrations (of course, forgetting the effect of circuit capacities for the moment) and others will be designed to furnish only approxibrought out more thoroughly as we proceed.

THE CONDENSER MOTION


The particular motion which is given to the condenser plates as the dial is turned is as follows: Starting at a dial setting of 100, when the plates are entirely out of mesh, as the dial

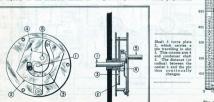is slowly turned, say from 100 to 90, the plates slowly move into mesh. As the dial is turned around further and further, all the



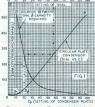

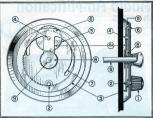The curve shown on Fig. 3 is obtained from the capacity and frequency calibrations above, by following the path.



Vech I turns pini which rotates ag-gear 3. This arries pin 6 in ies pin 6 in Gear 5 oove 7. Gear. iging the angu lar acceleration of arm 4 (a), which turns the condenser shaft at 9.

reading of the S.L.F. dial. Simply follow the nath indicated by the broken lines and the arrows. For instance, if Do, the setting of the plates, is 20, the setting of the S.L.F. dial will have to be 37, as indicated on the horizontal axis at the top of the graph. If this procedure is followed out point for noint, a curve, as shown in Fig. 2, will result. The horizontal axis gives the angular settings of the condenser plates, and the vertical axis gives the dial settings.

This curve is very close to the inverse uare law curve, which was deduced above The only variations are near the ends of the curve, which are caused by the curved por-

THE PURPOSE OF THE S. L. P. DIAL.

Before going into the various mechanisms Before going into the various mecnanisms that will give the required motion of the plates, it may be well to clear up a little misunderstanding that has come to my notice. A correspondent belittled the S.L.F. dial on the score that near one end of the motion



the motion of the dial may be studied from the curves of Figs. 1 and 2. In Fig. 1, the axis at the bottom represents the setting of the plates of the condenser, that is, as if an ordinary, dial were used. In other words, the bottom axis may be taken as representing the angle of motion of the condenser plates. The axis at the left (vertical) represents the

Mfa. Co.

familiar with this curve; because it is linear, the condenser is called a straight-line capacity condenser. The curve BC, on the other hand, gives the values of capacity that are required to make the condenser give a straight-line (or linear) calibration of frequency against dial setting. This has been computed from




the inverse square law, which applies to S.L.F. condensers. The first ten divisions on the dial have been neglected, since, if D is zero, C become infinite. This matter has been explained in detail in the August issue of Radio News, in my first article on the

It is easy to determine from these two curves the relation between the angular setting of the condenser plates and the dial the effect was merely the same as could be for that reason he might just as well use the vernier dial. What he says is true, as far as concerns the separating of stations on the dial, but the same thing is true of the S.L.F. condensers with the specially shaped plates. As the plates are turned out further and further, their area becomes smaller and be obtained by using a so-called vernier con-denser, that is, a small condenser of two or three plates.

In the construction of the S.L.F. dial the mechanical principle illustrated in Fig. 3 is always employed. It is the principle of the lever, as applied to a varying radius of the path of motion of a point fastened to the

(Continued on page 734)



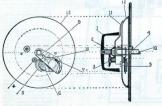





Through a vernier attachment controlled by knob 1, pinion 4 rotates gear 5 and the arm 6. The pin 7 slides in slot 8 in arm 9, which rotates the condenser at charging rates.

Pinion 2 turns circular gear 3, also turning circular gear 7, to which the dial pointer is fastened, at the same time. Elliptical gear 6 is carried ((rigidly) by 3, and rotates elliptical gear, which moves the condenser shaft, at 9, at a variable rate.

The Four Types of Audio Amplification

RU SVI HAN HAPPIS



620

This article is a combrehensine discussion of audio amblifiers. Note that all types are described and their characteristics defined



THERE are, in general, four types of amplifiers, any one of which can be made to operate satisfactorily in amplifying audio frequency currents. The choice of the type to use in a radio receiver depends upon many considerations, and it cannot fairly be said that one type is better than another. This will become apparent as we proceed and it will be seen that the different types of amplifiers are suited to different purposes. It is not well to confuse these purposes, any more than it would be well to confuse the nurnoses of the various types of automobiles. It would obviously not be well to put a truck adapted to heavy hauling into an automobile race, or to use fly-weight runahout in a trans-continental

The four types of audio frequency amplifiers are:


- 1. Ordinary transformer coupled. 2. Impedance coupled.
- 3. Resistance coupled 4. Push-pull.

Types 1 and 2 are very closely allied to each other; in fact, the impedance used in type 2 may be considered as ordinary trans-

he best-known typ amplifier. Thi nplifier uses ordi try transformers fo outling the stage.

TRANSFORMER COUPLED AMPLIPI-

Fig. 1 illustrates the use of the ordinary

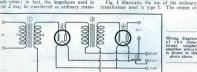

formers having two windings, in which the co-efficient of coupling is unity, and the turns ratio is also unity. The impedance acts as an auto-transformer, the same wing ing acting as primary and secondary at the


00 one tube is connected to the primary winding of the transformer, and the secondary of the of the transformer, and the secondary of the transformer is connected to the input of the next tube. This is the cascade arrangement. L. this arrangement, the maximum amplification per stage (that is, considering the tube

and transformer as a complete unit) is conal to the amplification constant of the tube multiplied by the turns ratio of the transformer. In the transformer, as is well former. In the transformer, as is wen known, the voltage of the secondary bears the same ratio to the input or primary voltage as the number of turns in the secondary bears to the turns in the primary. That is,

$$\frac{\mathbf{v_1}}{\mathbf{v_2}} = \frac{\mathbf{n}}{\mathbf{n}}$$

in which v_1 and v_2 are the primary and secondary voltages, and n_1 and n_2 are the primary and secondary turns. The ratio n_1/n_2 is called the turns ratio of the transformer. is called the turns ratio of the transformer. This step-up of voltage occurs only under certain theoretical conditions, which are never attained in actual practice. However, it follows that the maximum voltage attainable in a stage comprising a tube and transformer is

$$K = \mu \frac{n_s}{n_s}$$

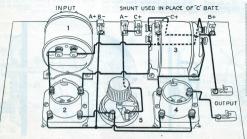


There has been a long-felt meed for a general discus-zion of the various types of amplifiers, which, we feel, has been filled by Mr. Harris' article. The four well-known types are here described in detail, with full instruction on with full Instruction on how to connect them up. There is also included in the article an excellent discussion of the factors entering into the choice of the type of amplifier, for the vorious uses found in radio reception. It is not often that the amateur en-dequor to select the propor instrument for the pur-pores at hand; here is an opportunity for him to be-gin to think about it.

Transformer couplifier. 1—First stage coupling transformer. 2

First stage tube socket. 3—Second stage coupling coupling transformer. 4—Second coupling coup phantom diagram s plainly the compo parts of the amplifier their relation to other.

SHUNT USED IN PLACE OF "C"BATT.

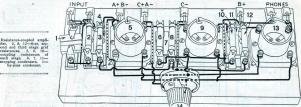

in which K is the total voltage amplification and μ is the voltage amplification constant of the tube.

IMPEDANCE AND RESISTANCE


The second type of amplifier is that which uses an ordinary impedance for the coupling unit between the tubes. This impedance, former, in which the number of turns in both primary and secondary is the same. The turns ratio in this case is unity, so that turns the same of the turns and the same of the same

list above is the resistance coupling. It is, of course, evident that in this case there are no turns to consider, hence no turns rathe, and the maximum amplification obtainments of the control of the

PUSH-PULL AMPLIFICATION

The fourth type of amplifier is the pushpull. This is a system devised by the Western Electric Company for the purpose of reducing the distortion which often results from the curvature of the tube characteristics when the tubes are carrying considerable current. The fundamental circuit connections are shown in Fig. 4. This diagram shows two amplifiers connected in caseade by means of coupling transformers. The two tubes on the right, in spite of the fact that two tubes are employed, represent only one stage of amplification. Little more voltage amplification can be obtained with the push-pull arrangement than with the ordinary transformer coupled amplifier, but

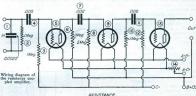transformers. Very satisfactory results are obtained with these amplifiers, but in the old days, before transformers had been developed to the point they have reached today, distortion in the signals received developed quite often. This was generally due to the fact that the transformers would not produce the same amplification at all frequencies. For instance, if a violin were sounding the



it will be found that a much greater plate note

voltage, and hence greater plate current can be handled without distortion, than can be handled by the ordinary amplifier.

APPLICATIONS OF EACH TYPE

The next joint to consider is the proper application of these various types of amplifiers, and their proper use in radio receivers. The most commonly used arrangement is the ordinary cascade amplifier using ordinary note C, which has a frequency of 256 per second, the amplification through the transformer would have a certain value. To reproduce all sounds faithfully, notes of all frequencies should produce the same amplification. Generally they did not, and its found that the transformer curves were as rough as an old cobble rough.

To overcome these difficulties, before any considerable improvements in transformer dotted by the control of th

The figures may vary considerably from these, but the idea is always the same. It will be noted that the effective voltage on the plate is reduced considerably because of the voltage drop in the resistance, and to make up for this effect, it is necessary to to use high values of "By" voltages.

The same ideas hold with regard to the impedance couplings, for impedances cannot be built to have large impedances, and at the same time keep the resistance low. If this could be done, the effective plate voltage



The bread-board layouts on these pages have been made because they show exactly hove the amplifur a complete set. The only difference will be found in the position of the whomen current, which is generally mounted on the ponel. To tell the truth, if may as well be mounted it is reidom necessary to adjust it, provided, of course, that a fiament with its facility in the position of the provided of course, that a fiament with its received in the course of the provided of course, that a fiament with its received in the course of the provided of the provide

 5, 9—autoformers, or coupling impedances. 3, 7, 11—grid resistances. 2, 6, 10—atopping condensers. This type of amplifier is coming more and more into its own as the most perfect in point of truth to the transmitted program.

s has been said above, th

would be the same as the "B" voltage, for a constant current through an inductance produces no voltage dron excepting that due to its resistance.

The push-pull system can be used with the ordinary plate voltages, but if it is desired to get out of the circuit all that is possible it is advisable to use much higher plate voltages. Voltages as high as 150 to 200 volts can be used successfully in pushnull stages.

A COMPARISON

Now, to discuss the four systems from the economic point of view, let us look at the following table:

3 tubes

3 sockets

3 impedances

sockets

3 transformers Large "B" battery

Large "B" battery

Increased fil. current 3 stopping cond.

PUSH-PULL 3 tubes

IMPEDANCE

TRANSFORMER
2 tubes
2 sockets
2 transformers
Ord, "B" battery

2 transformers Ord. "B" battery Ord. fil. current RESISTANCE

3 tubes 3 sockets 3 resistors Large "B" battery do. 3 stopping cond.

3 grid resistors

This table is for the purpose of outlining

the parts required to build the various types of amplifiers, and from it can be obtained a fair idea of the relative cost of each type. I have been applied to the cost of the cost of the cost of each type. See that the cost of the cos

as has been said above, this makes it possible to use higher plates voltages without overloading the tubes.

overloading the tubes.

The first three types of amplifiers eliminate the distortion which arises from the non-linear characteristics of the transformers, but allow the distortion due to curvature of the tube characteristics to remain. The last mentioned type, the push-pull, eliminates this also.

One of the main considerations in connection with amplifiers is the battery drain. In all of the types, excepting the ordinary transformer coupled amplifier, the filament

killing properties of the system. However, transformer compled amplifier, the filament of the system of the system

AUTOFORMER





Above: Wiring diaram of the impednce coupled ampliier. To the left: hoto of the impednce coupled amplier shown in the swo sketches above. consumption is increased 50 per cent. on account of the addition of the extra tube. Likewise, the "B" battery drain is increased, but in the resistance coupled type it is increased far out of proportion to the number of tubes. So far we have said nothing about the

"C" batteries. To obtain good reproduction, it is almost always necessary to use biasing batteries in each stage. These add materially to the quality of reproduction, and at the same time contribute toward economy in reducing the plate current. This is especially true where high voltages are used, either on coupled amplifiers, the grid has is obtained through the grid resistances shown in the diagrams.

Where great volume is desired without distortion, the push-pull system seems to meet the requirements best. This system corrects, at the same time, the distortion resulting from the curvature of the tube characteristic and irregularity of the transformer characteristic. Full advantage of the pushpull system cannot be obtained, however, unless its load factor is kept high; use plate voltages not less than 135 volts, and have a good grid bias of about 4 to 6 volts negative.

The general construction of these four types of amplifiers is shown plainly in the types of amplifiers is shown plants, in various diagrams on these pages. The layout diagrams should be followed very carefully. These have been shown in "bread-board" fashion, but the assembly does not differ materially from the way in which it would really be assembled in a receiver, with the exception of the rheostats, which are generally mounted on the panel. may be well to point out here, however, that it is not generally necessary to adjust these rheostats very much, so for the sake of sim-plifying the appearance of the panel, they may just as well be mounted behind it. Then, once adjusted, it will not be necessary to open the lid of the receiver and readjust them, unless the "A" battery runs pretty To tell the truth, it is just as convenient, in most cases, to do away with the rhostats entirely and use ballast resistances. If an amplifier is assembled properly

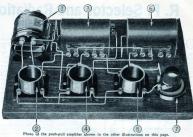

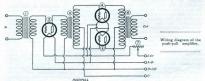

there should be no trouble experienced from audio frequency howling. This should be true whether the transformers are at right angles or not, for most transformers nowa-days are carefully shielded in metal cases. It is well, however, to keep the radio fre-quency conductors well away from the audio end, as considerable trouble may be experi-enced from coupling the audio and the radio frequency stages. Of course, there is no radio frequency current in an audio frequency amplifier; we are referring to the high frequency ampli-

may feed into the amplifiers. It will be found that the push-pull system will give more volume, for a given amount of distortion, than any of the other types, but, as have explained before, there is no economy in building a push-pull stage and then working it at a poor load-factor: that is, we should get all

there is to get out of a stage of push-pull; use voltages up to


fiers or the regenerative detector which

ush-pull amplifier. 1stage input trans-r. 3, 6-input and 3, 6-input transformers 4. 5 ish-pull stage. 4, 5— be sockets for push-pull 150 volts. They may, of course, be worked at the usual plate voltages, but the experi-menter may be disappointed at the resulting volume when he considers that he is using

another tube. The push-pull system has much to i mend it, when properly designed and used as can be seen from the fact that it is used in repeater stations on long distance telephone lines. It is not likely that large teleferior amplifiers.

The resistance coupled units have also much to recommend them, for they practically entirely remove all distortion, excepting, of course, distortion resulting from curvature of the tube characteristic. The difficulty with them is that if they are not handled properly, they are likely to become expensive, in the way of running down the batteries.

There is one other point that should be brought out very carefully and never for-That is, that if there is distortion in the signal currents entering the amplifier, matter what type of amplifier it may be or how good, it is not possible to obtain good reproduction. The fault here does not lie in the amplifier, but in the associated apparatus. For instance, if a regenerative detector preceds the amplifier, and regenera-tive is pushed too near the critical point, distortion will result and this distortion will be passed through the amplifier into the horn, When the term distortionless is applied to an amplifier, it means that it will reproduce faithfully whatever is put into it. It follows, therefore, that if a distorted signal is sent into an amplifier, it would be impossible to get out of the amplifier anything but a distorted signal.

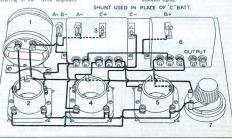

R. F. Selector and Radiation Preventor

NE of the greatest problems with which confinence is the prevention of radiation, or feeding radio or audio frequency oscillations and of radiation of the confinence of the c

624

transgressor in that direction. As a made show that all four types (oscillating R. F. amplifier, oscillating detector preceded by amplifier, oscillating detector preceded by an early of the control of



is with the latter that engineers have con-

The fundamental principle of this system may be easily understood with the aid of this simplified diagram.

It is easily seen that a device which will stop a regenerative set from radiating annoying pusculs and at the same time will supstop a regular state of the same time will see a superity statistic problem. Yet such a
derive has been developed in the form of a
set of the same time to superity states and the input side of the receiver itself. The Isodarad
first comprehensive the amenian and the input side of the receiver itself. The Isodarad
first conservation of the same time to the same onetime antenna, or other energy can pass
from antenna, or other energy can pass
from antenna, or other energy can pass
from antenna, or other energy can
mains constant for all settings of the dial.
When the filament of the tube is cold, energy
tube; when the filament of the tube is cold, energy
tube; when the filament of the tube is cold, energy
tube; when the filament is beated and is
emitting electrons, an amplified copy of the
entity electrons, an amplified copy of the
entity of the same of t

Thus, energy can pass from the antenna to the output of this new device, but cannot pass in the opposite direction. And also when such a stage of perfectly balanced R. F. amplification is interposed between the antenna and the receiving set, any squealing originating in the receiver is solated from the antenna and cannot interfere with the reception of other receivers in the vicinity.


The property of radiation-prevention has wrongfully been claimed for most forms of radio frequency amplifiers connected between antenna and receiving set, the idea stage itself does not oscillate, it will prevent oscillations set up in succeeding stages of the receiver (or in the detector) from reaching the property of the property

TESTS WITH THE SELECTOR

Radiation tests were run by setting up an oscillating receiver connected to one antenna and a non-oscillating set connected as a set of the control of the c

In the development of this instrument, it was noticed that the output coil of

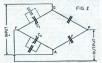the unit was capable of radiating howls originating in the oscillating receiver circuit. For this reason the device has been completely enclosed in a sheet metal case. Incidentally, the use of such a shield




The operation of the circuit depends upon the action of the bridge connection shown here.

permits it to be operated in practically any position with respect to the receiver, and position with respect to the receiver, as the property of the property

be added to any receiver without increasing the tendency toward oscillation.

The new instrument differ from such that the such that the such that the such that trap, as usually connected, admits all except a narrow band of frequencies, at the same time reducing the strength of the desired signal, while this device admits and amplifies only the desired narrow band of frequencies.

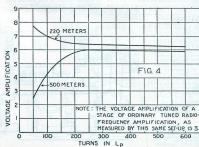
desired narrow band of frequencies. Furthermore, such a decided increase in the strength of the desired signal is



This chart shows how the voltage amplification varies with the number of turns on the plate inductance.

obtained that, in most cases, a station which is inaudible with the receiver alone will, with the assistance of this instru-

will, with the assistance of this instru-ment, give load speaker volume. It is a con-ment, give load speaker volume and Fig. 2 is the all-capacity bridge in-solved. The same lettering is used in both figures. Thus the capacity between denser between points G and P, the grid and plate respectively, of the vacuum plate to the point G and P, the grid and plate respectively, of the vacuum plate to the point A is shown connected between points F and A of the bridge. when once set at the point at which the bridge is balanced, it does not require further adjustment at any wave-length unless a tube having a different value of grid-to-plate capacity is substituted for the tube for which balance was obtained. In Fig. 3, the input inductance L₁ is more than twice the value ordinarily more than twice the value ordinarily employed, resulting in a very high signal voltage across its terminals—and therefore increased signal strength over that ordinarily obtained. The primary inductance is tapped as shown to allow a choice in selectivity for varying conditions of operation. Fig. 3 is the actual

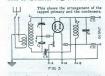

circuit diagram for the type used with sets designed for antenna reception. It will be noticed that the shield marked S is not connected that the shield marked S is not connected directly to the ground, but through a by-pass condenser. While this grounds the shield and the rotor of the twin variable condensers to alternating currents, it removes the possibility of burning out a tube by having the posi-

A commercial form of the instrument, known as the Penetrola.

tive "B" battery lead accidently come in contact with the shield. The matter of which filament lead is grounded and which is connected to B minus lead is determined by the wiring of the receiver itself. Thus this device will function without changes in its own wiring or that of the receiver, with any set, no matter which battery lead is grounded or which is connected to the B minus terminal.

The special output circuit shown in Fig. 3 allows the unit to amplify the incoming signal when feeding into any type of receiver, whether it be of the fixed-tuned primary type (as in the neutrodyne) or a single circuit or looselycoupled type, tuned either with a series or parallel condenser. Cp is so propor-tioned that, with the rest of the output

tioned that, with the rest of the output circuit, it simulates the conditions of the average-sized antenna. This causes the tuning of the first dial of the receiver to be altered but very little—if at all. The output inductance La has been chosen to give the highest possible average gain with various types of receivers. Fig. 4 shows two amplification curves run at 220 and at 500 meters and the inductance of La and at 500 meters and the inductance of La

was chosen from the results of a series of such curves to give the maximum amplifi-cation possible.

FOR LOOP RECEPTION

For use with a set designed for loop reception, type CL has been developed. The circuit of Fig. 5 is employed. Here ane circuit of Fig. 5 is employed. Here the loop is replaced by a very short antenna (20-50 feet long) which, it has been found by experiment, gives a better combination of selectivity and signal intensity and less static. The ground comection may be used as shown or may be replaced by a short length of wire thrown on the floor or running under the carpet. off the note of the state of the difference between the distributed capacity of the secondary of T and that of the loop, thus preventing any marked disturbance in the logging of the first dial of the receiver. In the original circuit, the condensers

The complete wiring diagram of the



on the same shaft and are controlled by the same tuning dial, are of equal size. An improvement which has recently been An improvement which has recently been incorporated consists in the use of unequal condensers for C₁ and C₂. This results in an increase in signal voltage applied to the grid of the tube of 331-3 per cent, as compared with the same circuit using equal capacities for C₁ and

The Penetrola, as this new instrument is called, requires no additional wires, batteries, or connections. It is furnished complete with three cables at the rear for connections.

Results of the Radio Shower Party

WE publish herewith a complete list of the winners of the Rabio News Shower Party which was held from the RADIO NEWS Station WRNY on August 3, last.

There was an unexpectedly large response

to the event, as is shown in the prize list. Due to atmospheric conditions prevailing on the night of the shower, a great many

listeners in distant parts of the country were unable to distinguish clearly the words of Mr. Hugo Gernsback, the Editor, who read the questions which the contestants were to answer. On account of this difficulty, there had to be a rearrangement of the prizes, so that those who did hear the questions and wrote the necessary explanations, fulfilling the conditions of the contest, were awarded the remaining prizes.

The prize-winning list is published below. There were entries from all over the country. However, Mr. W.C. Margaral of Bakersfield, Calif., gets the distance records. There were a number of entries from Ontario, Canada. There is no doubt that the Shower Party

ZONE 1

Prize Winners

26—Thodge R. Sarrya, Lehong, N. H.
227—Thodge R. Sarrya, L. Sarrya, N. H.
227—Thodge R. Sarrya, R. H.
227—Thodge R. H.
2

was a success and it is the hope of those concerned that all contestants will be satisfied with the results and awards. The judges gave their closest attention to the matter and used every effort to see that the awards were made as fairly as possible.

S1—Charler E. Kennedy, East Weynouth, Mass, S2—Jones C. Duder, F. Ell. Rev., Mass. March 20—Jones C. Duder, F. Ell. Rev., Mass. March 20—Jones C. Duder, March 20—Jones C. Duder, March 20—Jones C. Duder, March 20—Jones W. Mainster, Grender, Mass. S2—Jones W. Mainster, Reviewerlik, Mass. S2—Jones S2—Jones W. March 20—Jones S2—Jones March 20—Jones March 20—Jones

ZONE 2

1—Herman Braunstein, Brooklyn, N. Y. 1A—C. W. Bossidy, Auburn, N. Y. 2—Roy Fritts, Auburn, N. Y. 3—Frank J. Lumb, Auburn, N. Y. 4—Phillip G. Shank, Auburn, N. Y. 5—C. P. Bonghion, Binghamton, N. Y. (Continued on page 698)

Activities of the Radio News Laboratories

By The DIRECTOR

In this article the method of testing condensers is simply explained, in order that experimenters may add this interesting test to their repertoire.

VIME was, and not so long ago, that whenever a new-born radio fan went to the local radio dealer to buy a variable condenser to put into the radio receiver he was about to build, he invariably asked for an ump-teen plate condenser. Lo. and behold, new units of capacity were brought into existence by the popularizing of engineers were wont to talk about the capacty of condensers in terms of farads or microfarads, names which paid homage to the neace. But surely he would not rest in peace if he could listen to the way in

626



On the left is the circuit Hartley oscillator and on condenser testing on the right is the

great conceptions of electrostatic capacity ignored or misinterpreted. Well, the point of the matter is that we should not ask an automobile dealer to show snound not ask an automobile dealer to show us a four-wheeled auto or the electrical dealer for a ten-pound motor. We should, most likely, get about as nearly what we wanted as we get when we ask a radio dealer

for an ump-teen plate condenser.

The unit of capacity is not expressed in terms of the number of plates in the con-To tell the truth, it is possible to denser. have a much larger capacity with only two nave a much larger capacity with only two plates than we can ever get in the usual 23-plate variable air condenser. Take the ordi-nary telephone condensers, for instance, These are made of two sheets of tinfoil separated by waxed paper, and the whole rolled up together. In spite of the fact that there are only two what in this there are only two plates in this condenser, it may have as much as 200 times the capacity of the ordinary 23-plate variable air condenser.

WHAT CAPACITY IS

The quantity called capacity is a constant of proportionality connecting the amount of electricity held in a condenser with the voltage impressed across the condenser's termi-nals. In other words, Q = CV

in which Q is the quantity of electricity stored in the condenser and V is the termi-nal voltage. This, of course, is true only in the perfect instrument, under certain con-

From this equation we can define the quantity C, which we shall call the capacity of the condenser. We agree, when Q is meas-ured in coulombs, and V is measured in volte to give the quantity C the name farad, after the great Michael Faraday. (We may get the idea of the coulomb by remembering that when electricity flows in a wire, the current in amperes is equal to the number of coulombs of electricity that pass a given point

in one second.) It has been found that a condenser capable of holding a charge of one coulomb under a terminal voltage of one volt would be enormous in size. This is the condition that would be required to have a canacity of 1 farad. Just think—this would be a condenser 400,000,000 times the size of our ordinary 0.00025 microfarad condenser. So, to get around the difficulty of having to deal with figures in the tenth decimal place, we have come to use, as a convenient unit of capacity, the microfarad, which is one-millionth of the farad. That is, one million microfarads are equal to one farad.

equal to one farad.

The capacity of the ideal condenser, and, for all practical purposes, the actual condenser, does not depend upon the voltage or the quantity of electricity, but upon the physical dimensions of the condenser. It depends upon the area of the plates, the number of plates, the spacing between the plates and the nature of the material between them. formula which enables us to calculate the capacity of a parallel plate condenser is

0.2246 A (n-1) × K microfarads 1.000.000 d

when A is in square inches, and d is in inches. K is a number which depends upon the material between the plates. air, 4 to 8 for mica, 4 to 10 for glass, etc. The letter n stands for the number of plates.

So we see that the capacity of a condenser depends as much upon the size and spacing of the plates as upon their number. Is it wonder that we rarely find two 23plate condensers, made by different manu-facturers, with the same capacity? Hereafter, let us all resolve that we shall no



The testing part of the circuit. The cabinet encloses the standard condenser; the one on the right is under test.

more ask for condensers by the number of plates, but by the number of microfarads. We shall now see how capacity can be measured. There are many ways in which this may be done, but for our present pur-poses there are two methods which are most convenient. The first of th The first of these methods is which is deby means of "substitution," which is de-scribed here, and the other is by means of a capacity bridge, which generally lies be-yond the pocketbook of the average fan.

youd the pockethools of the average fan There is no reason why the average fan cannot make his own capacity measure-ments; with small cost he can do this with a degree of accuracy which is close enough for many of his purposes. All the control of quired is a small oscillator and a variable condenser which has been calibrated; that is, one for which he knows the capacity at a ware all segments. every dial setting.

The oscillator used in the Radio News Laboratory is shown in the photograph. It consists of three units, viz., a coil which is



The characteristic curve of a condenser may be obtained within a few micro-microfarads by the experimenter.

conveniently tapped, a variable condenser and a tube socket. The diagram of con-nections is shown in Fig. 1, and is seen to be the usual Hartley circuit. The tube used is an ordinary UV-201A or C-301A, using about 90 or 100 volts on the plate.

The coil is made of bell wire on a tube

about 3½ inches in diameter. The variable condenser used has a maximum capacity of 0.001 microfarad. With about 50 turns on the coil, and locating the taps about 5 turns apart, this oscillator can be made to emit wave-lengths from about 750 to 75 meters.

This oscillator is often called the driver, and is used merely to supply the energy to the measuring circuit which is shown in This measuring circuit consists of a coil, which may be also made of bell wire on a similar tube, having about the same number of turns as the oscillator coil. The meter shown is a thermo-galvanometer, but if one prefers this may be replaced by a thermocouple and sensitive ammeter. The (Continued on page 696)

Oscillator used in RADIO NEWS Laboratories for the generation of frequencies covering a wave-length band from 75 to 750 meters,



Why Run a Junk Shop? BY INSEPH RILEY

'HY does it seem to be a general impression among those who are not actively connected with the ham radio game that every ama-teur station is nothing more or less than a bunch of junk thrown together in an indisbunch of junk thrown together in an mois-criminate manner and without the least sys-tematic arrangement? Now gather around the table close, boys, and I'll tell you why. Because it is so! True enough, there are Because it is so! True enough, there are some good, up-to-date ham stations that some good, up-to-date nam stations that look almost as though they were really con-structed, but frankly these are few and far between,

The next time you sit down to pound brass, look around you. Probably you will see a tuning inductance hung upon the wall by a piece of string or lying up against the wall and using that as a support. Then you will probably see a couple of fixed conlensers lying on the table a foot or so away

so that you can experiment with its ably this is true, but it is not at all necessary for you to sacrifice the efficiency that sary for you to sacrifice the efficiency that sary nor you to sacrince the emesency that you do by using the junk-shop method. You can do experimental work without being slipshod. Where do you think some of the big research laboratories would be if they threw their apparatus around on the table in any way it happened to fall and tied it together with magnet wire? We would expensive piece of apparatus. thousand volts across a pair of filament by-pass condensers that are only rated at 100 volts breakdown is bad stuff. Regardless of their quality, condensers cost money and, once punctured, are worthless. Let us put condensers of this nature on one side of the financial balance and a few lengths of ber-covered flex on the other side. Which (Continued on bage 694)





from where they ought to be and literally tied to some other part of the circuit by a couple of hunks of magnet wire. Probably the tube is in a precarious position, directly under some heavy piece of apparatus that is likely to fall upon it, diminishing the re-sources contained in your pocketbook by a few odd dollars. If there is any pretense toward system at all, it is probably in the receiver. A good many hams have learned to build their receivers so that they look to use their receivers so that they look like a real piece of apparatus and not like a bunch of junk but—can this be said of our transmitters? No, empathically, no! In the majority of cases it cannot be said. We still persist in throwing our stuff together without seeming to worry about appearances. Everybody wants to reach out further and further and after they have reached the limit of their transmitters, to go beyond that point. As a consequence, a good many of us have forgotten that we are really sacrificing something by using these short-sighted methods.

You will probably answer this by saying that you put your stuff together that way all still probably be using coherers or magnetic detectors at the best won't go, fellows, and the sooner you realize it, the better off you will be, When you build a new piece of appa-

ratus, build it right and provide it with some kind of mounting, so that it can stand on its own feet and not have to lean up against the tube or the wall. Even in making an ex-perimental layout, place the various instruments a close to each other, and in as accessible a position, as is possible. Give a little thought to the work and it will go much more quickly and easily. Then, in-stead of using odds and ends of bell wire or magnet wire to hook the set up, use a few lengths of fairly heavy rubber-covered flex. You can hook up a set just as quickly this way as with the magnet wire and the results will be far superior. Suppose a couple of leads do cross each other. It will do no harm for, in almost every instance, the rubber insulation will prevent sparking. Not so with magnet wire. Trouble will be Not so with magnet wire. Trouble will be encountered, particularly if this wire is carrying radio frequency current in any appreciable quantity. I have personally seen more than one set go out of operation because of an arc formed between two unprotected leads. This is bad business for all concerned and some day may cost you an

THE MONTH'S CROP OF NEW ORA's

2LC-William J. Rooke, 463 East 158th Street, New York City. QSL crds 3HP-George E. Stewart, 220 Collins Avenue, Baltimore, Md. 5 watts C.W.

All crds answd.

3PY—Reassigned to Francis Richard-son, 507 South Orange Street, Media, Pa. 175, 84 and 41 meters. All crds answd. No. 6—5 watts C.W. Crds answd. same day red. 5AUO-Gaston Johnson, 712 East

Mississippi Avenue, Ruston, La. 20 watts, fone es C.W.—150-200. 5AVC-A. E. Williams, 408 South Vienna Street, Ruston, La. 5 watts on

20, 40 and 80 meters. 5OI-Alfred Leitch, Ruston, La. 50

atts C.W.—80 meters.

5APS—W. F. Warrell, Bernice, La.
) watts, fone es C. W.—150-200 meters.
4OY—R. O. Dorset, Spartanburg, S. watts C.W .- 80 meters.

8CW-J. A. Clark, Glens Falls, N. Y. watts C.W.

Swatts C.W. GBWS—Russ. Shortman, 1617 Van Buren Street, Phoenix, Ariz, QSLs answd. 9AZO—Reasisgmed to F. J. Nicholas, Box 484, Savannah, Mo. QSUs quickly answd. QRK mil to watts? 9UI—funior Bishon, Glw West Sireet, Sedala, Mo. Pse QSL mi 20-40-80

meter sigs. QKS.



Getting the Most from Crystal Sets

Ry A. P. PECK

DEDIABLY the most reglected part of the apparatus that will enable us to receive our daily concerts and radio entertainment is that little unit known as a crystal detector and that part of it which makes its operation power are many people using crystal detectors today, but statistics show that this number is much smaller than those using sets employing one opinion, those who have not used crystal detectors or have not done any experimental own with the property of the control of t



A simple crystal set but one that is not very selective is shown above.

biggest and best parts of radio reception. You can get more fun out of working with various types of crystals and detectors stands at less actual expense than from any other experimental work.

ADVANTAGE OF CRYSTALS A crystal detector has a great many advantages. First and foremost, it is inexdetector stands are easy to make. There is no unkeep to a crystal detector, as no batteries are used and there is nothing to de terrise are used and there is nothing to de-teriorate, except possibly the crystal, which may become a little insensitive. It, how-ever, can often be renewed by a method which we will outline in detail later on. Then again, although the range of a crystal detector receiving set is somewhat limited, still when signals are received with it, they are nure and undistorted and music and voice come through with life-like precision. Even though the reception range of a crystal de-tector is limited, still in this day of multitudinous broadcast stations, many of which are operating on comparatively high power, there is always at least one broadcast station within the range of a crystal set in the United States and sometimes there are many

In the metropolitan district many advanced fans have crystal detector receiving sets at hand with which they can listen in on the local broadcasting. From this they get much enjoyment from radio in general and at the same time practice real economy, in that they do not have to use their tube sets for local

reception and thus save on "A" and Fabriers. Cytaid sets are so inexpensive to make and most fans have enough naterial and to make on without further expensions that the set of the set of

The writer's experience with crystal de-tectors dates back to about 1913, when popular favor was divided between several dif-Among these ferent types of detectors. were the old Marconi magnetic detector, microphonic detectors, and a few types of erystal detectors. At this time, of course, there was no broadcasting, such as we know today, and practically the only reception was from amateur transmitters. ship stations and land stations. Today, if someone said that he received over a dis-tance of 1,000 miles with a crystal detector, he might be looked upon, to say the least, as one who stretches the truth. However, in those days 1,000-mile reception from high powered stations was by no means unusual. At the writer's home in central New Jersey he frequently heard the naval station at Key West, Fla., and at more than one time received signals from another high-powered station located at Mare Island, Calif. True, all of these stations transmitted on considerably higher power than the average broad cast station uses today, but, nevertheless, at that time the apparatus used was rather crude in form and this fact quite counterbalances the high power employed. All of the receiving apparatus that the writer used, with the exception of the head-phones, was home-made.

Although, as mentioned above, the range of a crystal detector is somewhat limited, one of these little instruments has brought some surprising results. The writer has personally received broadcasting from station KDKA, approximately 250 miles away, and this on a home-made crystal detector employing a piece of galena. This shows that the old saying that a crystal detector could not be depended upon to receive over more than 25 miles does not always hold true. Under extraordinary conditions on one extremely clear night that was practically free from static, Atlanta, Ga., was received on the same detector. During the winter months this sort of work is not at all exceptional and we could go on to state hundreds of other cases of excellent reception with crystal detectors. However, from those facts given you can easily see that a good bit of excellent work can be done with these somewhat neglected instruments and if you will follow some of the details given below you should have no trouble in duplicating many


SEI ECTIVITY

Usually when a crystal detector set is mentioned for use in broadcast reception. The control of the control of

The first thing to do toward making the crystal set selective is to couple the antenue crystal set selective is to couple the antenue conductively, to the detection circuit, as it usually done in simple sets. Of course, a slight amount of energy is lost in the transference from the primary to the secondary circuit, but selectivity is increased so greatly that these losses may practically be neglected, need to the conductive that the conductivity is increased so greatly make the conductivity in contract the conductivity is increased so greatly that these losses may practically be neglected.

One of the simplest types of inductively coupled test is lifestrated in Fig. 1. Coils L1 and L2 may be a standard type of tuned ands requency amplifying transformer that may haild one yourself in the following manner: Near one and of an insulating tube 33/6 or 4 inches in diameter, wind 5 or 6 turns of the same tube start another coil lawing on the same tube start another coil lawing on the same tube start another coil lawing the secondary and is connected to the variation. The first mentioned winding is consolidated in the control of the c

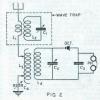able condenser and crystal detector, as shown. The first mentioned winding is connected as L1 in Fig. 1. This type of circuit is extremely simple to control, but in con-



A crystal set is made much more selective by the

gested districts it will be found that the selectivity of it is not all that could be desired.

Thus we must search a little further for a set that will give us everything that we The first consideration is the tuning want of all circuits, rather than only one, aerial and ground system is tuned, selectivity will be increased still further. This can be accomplished by using a variocoupler and connecting it as shown in Fig. 2. The vario-coupler windings are indicated by L3 and L4 and often a series condenser, C4, will be found to be of still greater assistance. This is particularly true if the variocoupler employed is only tapped coarsely or in sections of 10 turns or so. If, on the other hand, this coil is tapped in what is known as units and tens, a variable condenser is always necessary, but will frequently help. The only way to determine this for your own particular set or in your own particular locality is to try the set both with and without a variable condenser.

and the state of t

to receive.

CRYSTAL

WAVE-TRAP CONSTRUCTION

This wave-trap consists of two coils wound very much after the same manner as coils with the coil L1 may be wound directly under L2 von will note that the absorption circuit compaced of coil L2 and combendered in any way. The theory of this instrument is that when two stations are both being heard or by changing the condenser C1. What happens is that you could be condenser C1. What happens is that you can be condensed to the condenser C1. What happens is that you will be condensed C1. What happens is that you can be condensed to the condense C1. What happens is that you desire to eliminate. This circuit that you desire to eliminate. This circuit that you desire to eliminate. This circuit can you could be presented by the condense of the condense when the con

the manufacture of the property of the property of the photograph in Fig. 3. Here the tube containing coil L1 and L2 is mounted on the outside of the ealinet for the very simply of the containing of the collection of the containing the collection of the collection

CRYSTAL

SET SCREWS

set, but nevertheless it is often bothersome. Probably a separation of one foot between the two units will be found sufficient.

The various constants for the circuit aboven in Fig. 1 are a follows: 1 land 1.2 were electrical above and CI has a maximum capacity of 100% and, and CL, 8 fixed capacity of 100% and, and CL, 8 fixed capacity of 100% and a fixed capacity of 100% and 100% and

In case you wish to build a variocoupler yourself to be connected as shown in L3 and L4 in Fig. 2, the following approximate dimensions may be followed. Wind L3, the stator, on a 3½ or 4-inch tube, placing 72 turns of No. 20 or 22 D.C.C. wire on it. Tap this winding every 8 turns for 8 taps and then every turn for 8 taps. The rotor L4 may be wound on a tube or an ordinary ball form that can be bought at any store



A piece of pencil lead or antimony makes an excellent contact for use with galena or silicon.


and should have 40 turns of wire. It is then mounted in any suitable way so that it may be easily rotated in relation to the coil L3. The writer will leave the actual mechanical construction to the individual readers.

SELECTING THE CRYSTAL

Now let us come down to the actual heart of one of these simple recoveris—the crystal of one of these simple recoveris—the crystal of one of these simple recoveris—the crystal of the simple recovering the simple recovery

and choose almosg from.

In the very best way
to do this was to go directly to the source
of supply and purchase a piece of galena,
the total control of the property of the source
of supply and purchase a piece of galena,
then take this home and carefully break it
up into small fragments, obtaining hundreds
a crystal detector saind. Then you can
begin a most interesting series of tests, goof the crystals and sorting them according
to their degree of sensitiveness. Out of all
up the control of the crystal series of the crystal
to the crystal that can bardly be process of
climination again until you have found one
to the crystal that can hardly be beaten by
Then you will probably have in your possession a crystal that can hardly be beaten by
the crystal that can hardly be beaten by
the crystal that can bardly be the control of the
tree of the crystal that can hardly be beaten by
the crystal that can hardly be the control of the
tree of the crystal that can hardly be the control of the
tree of the crystal that can hardly be the crystal that can hardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal that can bardly be
the crystal that can bardly be the crystal t

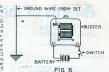

The connections in the diagram above show now a buzzer should be hooked up for testing crystal detector circuits.

is one thing that must be remembered. Do not attempt to landle the crystals with your bare hands. Regardless of how clean they considered the second of the second of the oll present on the surface of the skin and this oil if it gets on the crystal, will form a minute film that may destroy or reduce its secultivacus. Therefore, provide yourself, you can pick up the pieces of mineral and transfer them from one place to another without danger of contamination.

Of course, there are other minerals and crystals worthy of consideration, but for all around use, in a simple crystal set that does not employ vacuum tubes for either radio or audio frequency amplification, galena is hard to beat. Some synthetic and so-called treated galena is very good, but here again it is usually procurable in single small pieces and you may have to buy several before you strike the best one. Silicon, a product of the electric furnace, makes a very good detector but it is not quite as sensitive as galena. It possesses one advantage, however, and that is that it is much more stable because of the fact that a much heavier pressure is used on its surface than on the surface of galena. In the case of the latter, a very light contact must be used at all times and it can plainly be seen that this contact can easily be jarred off. In the case of silicon, however, you can jam a sharp-pointed rod down hard on the surface of the crystal and it will give good results. sort of an adjustment is, of course, hard to loosen and therefore you do not have to adjust the catwhisker or contact as much with silicon as you do with galena. A good many permanent and semi-perman

ent crystal detectors have recently appeared on the market. Most of these are excellent for use in reflex and other sets that use tubes, but they are usually not quite as (Continued on page 650)



A standard type of wave-trap that will increase the selectivity of circuits is shown in the photograph above.

FIG. 4.

A and B show two very good methods of holding crystals in cups so that good contact is made.

SOFT METAL

630

Awards of the \$50 Radio Wrinkle Contest

First Prize

SEMI-FIXED THREE-CIRCUIT

By F. C. RUEHL

One serious objection to the ordinary tickler coil method of regeneration control is the mechanical, not electrical, difficulties and inconveniences encountered. Many of these difficulties may be overcome and the control of the regeneration actually made smoother, by using a fixed tickler coil with a series variable condenser.

The accompanying sketch clearly shows a simple system of this type of regeneration control. S, the secondary, is wound in a manner and style to suit the fan's own re-quirements. P, the primary, should have from 10 to 15 turns and be of such a diameter that it fits fairly snugly inside the secondary, , the tickler, should have a smaller diameter than P, for two reasons: to keep its field



from spreading too much and also to reduce to a minimum its effect on the tuning of the secondary. The number of turns of T should be between 25 and 30. The metal strips, should be of material stiff enough to support the coil without appreciably sagging when the movable coil is near the outer end. The nut, n, should be adjusted to such a position that the inner coil centers properly with the secondary. This adjustment having been determined, solder the nut to the bolt, or use

Second Prize FIVE-CENT EMERGENCY JACKS

By J. V. MORAN

Many constructors of experimental radio is take great pride in seeing just how much sets take given in seeing just now mach of the apparatus that goes into a receiver can be made from spare parts in the junk box. Although the "parts" needed for these jacks are not generally in the radio junk box,



The lowly collar button has at last been applied to radio. They make efficient jacks for phone

they are bound to be somewhere around the house. These parts are nothing more than two collar buttons.

As almost all collar buttons have holes in them, it is only necessary to see whether the tips of the phone cord will fit snugly. the holes are too large, with a pair of pliers pinch the shaft in order to reduce the size of the opening, and if the hole is too small can be easily enlarged by spreading the soft metal with a nail and hammer. Holes having a slightly smaller diameter than that of the smallest part of the button are then drilled in the panel. These holes are then countersunk on the front of the panel so that the buttons will be flush with it. Place the buttons in their holes and twist the con necting leads to the part projecting through the rear of the panel. Then, with a good hot soldering iron, place a ball of solder

are also several other difficulties which could be avoided if proper use was made of a hydrometer. Too often hydrometers are not replaced if broken, and yet there is a very simple method of repairing them and also for making new ones.

On the point of a pin place a piece of cork about the size of the head of a safety match and roll it in melted sealing wax until generous amount is collected on the cork. When the wax has cooled, remove the pin and close the hole by holding the ball of wax over a flame. Then place the wax ball in either an old hydrometer tube or a large medicine dropper, and fill with solution from the charged battery. Sandpaper the wax ball until it just floats in the solution. Then prepare another ball of a different colored wax, but this time put the ball into a solution taken from the battery when it is in a discharged condition. These two balls are then placed in a hydrometer case, as mentioned above. The method of testing with this hydrom-

eter is to draw some of the battery solution



Small balls made of cork and sealing wax can be used for hydrometer floats.

up into the hydrometer, and if one of the balls, for instance, the red one, which can be used to indicate the discharged condition, floats and the other one sinks, the battery needs charging.

asten to S. here with short bolt anut Loosen this nut to slide inner coil in or out.



by suspending the primary and tick-ler coils in this way very fine ad-justments can be made which will Coll leads

just the coupling simply loosen the thumb nut, T, and slide the coil in or out to the proper position and then tighten the nut. The tickler should be so adjusted that oscillation is just possible on the highest wave-length, when the condenser plates are entirely in mesh. One great advantage of this scheme is the ease with which different unit coil combinations may be substituted for long or short wave-length work. That is the leads from the coils may be so arranged that snap clips are used and the changing of coils is very easily effected. Fans who build receivers using this method of coupling will doubtless find it to be one of the smoothest working couplers they have used.

around the shaft of the button, as shown in the accompanying illustration. This will not only hold the jack in place but will provide an excellent contact.

Third Prize HOME-MADE BATTERY TESTER

By LYONEL GOODENBATH

One of the chief parts of a radio receiv ing equipment is the storage battery, and all too often this does not get the attention that it merits. Often it is allowed to remain in a discharged condition, which is very unwise.

Prize Winners

First Prize \$25 SEMI-FIXED THREE-CIRCUIT

THNER By F. C. RUEHL

5215 Tennessee Ave., St. Louis, Mo.

Second Prize \$15 FIVE-CENT EMERGENCY IACKS

By I. V. MORAN 1603 First Ave. N., Seattle, Wash,

Third Prize \$10 HOME-MADE BATTERY


TESTER By LYONEL GOODENRATH Shelby, Mich.

NOTE: The next list of prize winners will be published in the January issue.

AN ANTENNA CLAMP

Although few radio fans realize it, one of the places where there is possibility of extremely large losses is the connection between the antenna and the lead-in. This possible loss may be eliminated by having the antenna and lead-in all one piece of wire, as described below.

The antenna clamp shown in the sketch is made from two porcelain clamps such as are used in house wiring. They should be of the "three-wire" variety, so that the antenna wire can be run through the middle groove and a bushing placed in the two outside grooves in order to prevent the cleats from breaking when pressure is applied to them after they have been placed in position. The antenna wire itself is insulated for about ten inches with heavy rubber friction tape

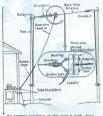

An antenna insulator of this type is both cheap and efficient.

cleats and it is also insulated with the same tape for about twenty feet from the place where it enters the house. The drawing is self-explanatory, and if this system is followed, an efficient antenna should be the re-Contributed by D. E. Phillips.

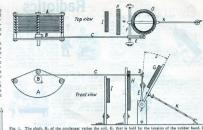


Fig. 1. The shaft, B, of the condenser varies the coil, G, that is held by the tension of the rubber band, K to control the regeneration of the circuit.

AUTOMATIC REGENERATOR CONTROL.

One of the chief tendencies in present-day radio receiver design is the reduction, far as possible, of the number of controls. In the case of regenerative receivers, the constructor, by employing a little ingenuity, can eliminate one more control and still have his set working at the peak of efficiency. The application of this principle to a

tickler feedback set is shown in the draw-ing at Fig. 1. A is the tuning condenser, either 11- or 23-plate. The shaft, shown at half inch, with a set screw as shown. set screw, or to a lug which may be soldered on the shaft, a heavy linen thread, C, is secured and wrapped once or twice around the shaft. The other end is fastened around the shaft. to an arm, E, which is fastened to the tickler shaft, F. A rubber band, K, exerts a con-stant pull on the tickler, G.

The device is set as follows: With the

plates of condenser, A, in full mesh, and

with the thread C in such a position that as the condenser capacity is decreased, or the dial moved toward zero, the arm E is pulled toward the condenser, adjust the length of C so that the arm E is vertical. Then change the position of the tickler coil, G, by varying the angle, J, until the set is at the peak of the regeneration, without being in oscillation. Now try tuning in stations at various wave-lengths. If the tickler is in the correct position on the higher wavelengths, but couples too closely on the lower wave-lengths, causing the set to spill over into oscillation, the arm E is too long; if the coupling is not close enough at the lower wave-lengths, the arm E is too short. With a 1/2-inch condenser shaft the arm E should be between 2 and 21/2 inches long; in order to secure the best position, it is advisable to provide a variable adjustment as shown at D, so that the length of the arm may be readily changed.

After these adjustments have been made, they may be left permanently. If the set is used in a different location, with a difis used in a different location, wi (Continued on page 740)

Radio Set Directory Continued from October Issue Loud Speaker: Sena-

Manufacturer: CON-CERT RADIO-PHONE CO. Batteries: Storage or 1938 Euclid Ave., Cleveland, Ohio

Trade Name: Monotube Circuit: Three Batteries: Storage or Batteries: Antenna: Outdoor Controls: Two List Price: \$12.50

Trade Name: Tritube Circuit: Three Batteries: Storage or dry cell dry cell
Antenna: Outdoor
Loud Speaker: Separate
Controls: Two
List Price: \$35.00

. . . Trade Name: De Luxe Circuit: Tuned radio frequency
Batteries: Storage or
dry cell
Antenna: Outdoor or

indoor Loud Speaker: Sepa-Controls: Three List Price: \$75

Trade Name: Concert Grand Circuit: Tuned radio frequency

Antenna: Outdoor Loud Speaker: Sepa-rate Controls: Three List Price: \$50 . . .

Trade Name: Concert Supreme Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor or loop Loud Speaker: Separate ontrols: Two ist Price \$190.

anufacturer: COS-OPOLITAN PHUSIFORMER CORP., 15-17 West 18th St., New York City

Trade - Name: Cosmo-politan 5-tube panel 7 x 18 Circuit: Tuned radio frequency
Batteries: Either
Antenna: Outdoor
Loud Speaker: Sepa-

Controls: Thr

Manufacturer: DAY-TON FAN & MOTOR Monument and Meigs Sts. Dayton, Ohio

Trade Name: O. E. M. 12. Circuit: Tuned radio frequency Batteries: Dry cell or storage. Antenna: Outdoo Loud Speaker: Sepa-

Controls: Three List Price: \$75.00 Trade Name: O. E. M. 7 Circuit: Tuned radio

Batteries: Dry cell or Antenna: Outdoor Loud Speaker: Sepaontrols: Three

Trade Name: Dayoli Circuit: Tuned ra frequency Batteries: Dry cell or storage Antenna: Outdoor

Controls: Three List Price: \$110.00 rade Name: Day-Fan reuit: Tuned radio

frequency Batteries: Dry cell or orage ona: Outdoor Sepa-Antenna: Outde Controls: One List Price: \$115.00

. . .

Trade Name: Dayroyal Circuit: Tuned radio frequency Batteries: Dry cell or Antenna: Outdo Speaker: Built-in List Price: \$300.00

Trade Name: Dayphone Circuit: Tuned radio frequency Batteries: Dry cell or storage Antenna: Outdoor Loud Speaker: Sepa-Controls: One List Price: \$105.00

Trade Name: Daveraft Circuit: Tuned radio frequency .

Batteries: Dry cell or storage Antenna: Outdo Loud Speaker: Built-in Controls: One List Price: \$145.00

Trade Name: Daygrand Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Dry cell or Antenna: Outdoor Loud Speaker: Built-in rols: One Price: \$195.00

Trade Name: Daytonia Circuit: Tuned radio frequency streries: Dry cell or Batteries: storage Antenna: Outdoor Loud Speaker: Built-in Controls: One List Price: \$300.00

Manufacturer: DE WITT-LA FRANCE

radio Reactodyne R. F. Circuit: Radio frequency Batteries: Storage Antenna: Outdoor Antenna: Outdoor Loud Speaker: Sepa-rate

Controls: Two List Price: \$56 Manufacturer: DIM MOCK-BOGART

RADIO INC. 137th St. and 3d Ave. New York City Trade Name: Ariono'a M-4 Balanced R. F. Circuit: B a l a n c ed radio frequency Batteries: Storage Antenna: Either or without Loud Speaker: None Controls: Two List Price: \$50

Trade Name: Arionola M-4L Balanced R. F. Circuit: Balanced radio frequency Batteries: Storage Antenna: Either or

without Loud Speaker: Built-in 54 Washburn Ave., Cambridge, Mass. Trade Name: Supe List Price:

Controls: Two List Price: \$50

SMACKS OF TAMMANY HALL

Radiotics



WE'LL GO TO BUIND

An Advertisement in the for April offers for sale with one spring gone.
Contributed by Warren D. White,

Milton Pace.

FOR THE THIRSTY

The you happen to see any hamorous mis-prints in the press we shall be glad to No RADIOTIC will be accepted unless the opined original giving the name of the news-paper or magazine is subscutted. We will pay paper or magazine is subscutted. We will pay printed here. A few humorous lines from each corresponder should accompany each RADIOTIC. The most humorous ones will be pointed. Address all RADIOTICs to

Editor RADIOTIC DEPARTMENT.

c/o Radio News.

for Use We nev



The radio section of the Hartford Times (Hartford, Conn.) for August 19 has an article headed "Chart

AND THAT'S TRUE July 19 the Phila-'elphia Inquirer had in inswer to a radio question in which it was told that 'Very little will be gained in distant DECEPTION."

now called a hook-up: Somehody elucidate, willyal Contributed by E. R. Siefkin.

The Wickita (Kan.) Bracon of July 15 in report-ing a speech said that "it

COUNTY by a hast HOOK-UP OF A DO! CITIZENS." Is this of these here political r that due to the influ



ard it. Contributed by Raymond Madill. ALONE AT LAST



ing against the other side of our phones. We shall send in our order at once. Contributed by H. E. Westrate.

THE HEIGHT OF OPTIMISM The Mankato Daily Free Press, Mankato, Minn., for March 2, report March 2, reports, RASH Marujermined cnethe Saturday radio
the Saturday radio
was excellent and "the static was fine." This is a
tic was fine." This is a

-1 and very admirable
We only
little RACK





better-if

The Monte for August ticle on rel "The message ... was picked up by the American Radio DELAY League." Aha! So that's why we have to wait so long for news from the Arctic Ex-

W. D. McClellan.



Contributed by Donald Bond.



innovation. "Say it with flour" and recommend liberal ng during the dinner concert hour.

What an addition it we be to the Burns Agency Contributed A WARNING

QUICK, WATSON, THE NEEDLE!

In the classified ad

The July 28 edition of the alem (Mass.) Evening exist states that "an antenamust be kept clean and well INCULATED."

receive its weekly to buy antennas already "inculat-he Society With Name is on the those who attempt this delicate operation.

Contributed by Charles A. Smith.

OF COURSE! An article on trouble



could a delicate stand the bruta a socker?

Contributed by Henry Willier

The Radio World for July 25 in one of the articles gives the specifications of a very unusual of a very unusual "using No. 24 SOC." advise the baffled set-

of teles to for cless to telestate for socks, size 12. Contributed by Raymond Madill.



The Minneapolis Tribune Minneapolis, Minn., March 22 advertises one-tube radio po cabinet, fits on Ford So-this is where popping

Contributed by R. D. Lewis.

TWO-IN-ONE







NO TUBE SETS NEEDED THERE



On May 24 the Spring-field Republican, of Spring-field, Mass., in relating that some stations were soing to increase their speaker and WBZ's knock them over.

Contributed by Dr. H. S. Thomson.

In the Radio Trouble column of the Boston Daily Advertiser (Boston, Mass.) for August 18, a radio fan states that he "is using a F U R-T U B E neutrodyne



the MacMillan Expedition.

Contributed by Charles A. Smith.

thing that should have used by the A. E. F.

ust day? They should by all means be removed and kept in cold storage till next winter, when they may bring in Alaska or BANGI BANGI ALSO BOOM

New Radio Patents

By JOHN B. BRADY

(1,535,734, D. H. Moss, filed February 9, 1924, issued April 28, 1925. Assigned to C. Brandes, Inc., New York.)
Support for table talkers and method of making the same. The patent shows a method of construction for an electro-magnetic sound reproducer.



The construction of the base and means for mounting the acoustic reproducer therein described in connection with the process of manufacture by which the instruments can be inexpensively produced on a quantity production scale. (1,229,065, J. H. Hammond, Jr., filed December

11, 1916, issued March 10, 1925.)
System of radio control of submarine vessels other movable bodies. A combined electromagnet wave reception system and sound wave




transmission system is illustrated whereby received radio signals are caused to actuate a submarine compression wave sound transmission system for transmitting energy under water for control of sound-receiving devices on board the submarine vessel.

vesset.

(i, \$26,626, C. E. Brigham, filed March 13, 1924, allowed Feb. 17, 1925. Assigned to C. Brandes, Inc., New York.)

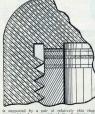Electro-magnetic sound reproducer for randeroception, in which a diaphragm is resiliently supported at its periphery for operation by an electromagnetic operating mechanism. The diaphragm



is supported by a pair of relatively thin rings, one positioned on one side of the diaphragm and the other positioned on the opposite side of the *Patent Attorney, Ouray Building, Warkington, D. C.

diaphragm. The rings are composed of layers of dissimilar material formed integrally with each other and remain in permanent adjustment with respect to the electro-magnetic sound reproducer. This patent covers the Brandes Table Talker.

(1,528,010, C. S. Demarest and M. L. Almquis filed December 31, 1923, issued March 3, 192 Assigned to American Telephone and Telegrap Co., New York.)

Radio signaling system combining the advantages of line wire and radio communication. Some practice receiving circuits are provided for the receiping rate receiving circuits are provided for the receiping current. The arrangement of the receiving circuits is such that a large amplification of the particular detected frequency or range of in quencies, which it is intended to secure, may I received. The patent deserthes a terminal circuit certain control of the provided of th



currents or telegraph signaling currents. The switching means is actuated by signaling currents transmitted over the line for connecting the modulating circuit in desired relation to the antenna system and control circuits.

(1,533,611, W. R. Respess, filed December 22, 1923, issued April 14, 1925. Assigned to New Jersey Research Company, Electrical condenser and method of manufacturing the same, where the metallic armatures are



coated with rubber in solution which, when dry, forms an insulating filament directly upon the conducting plate, permitting condensers to be built up by stacking the conducting plates one upon another.

A NOVEL DETECTOR

(Application date, February, 14th, 1924. No. 233, 782.)
British Patent No. 233,782 granted to the British Thomson-Houston Company, Ltd., and W. F. Boyd, gives details of a crystal detector illustrated by the accompanying diagram. The crystal detector is of a rather peculiar type, the contact being



obtained between the surface of the crystal and a wire helix. Thus the crystal is held in a cup D fixed to a base B, supporting an unright bracket U, which carries an adjusting device. In the modification shown this consists of a rod R provided with a band K facel by means of a probaserse G. The end of the red correl a pretal helix H, the convolutions of which are intimitate constant with the surface of the crystal the helix will revolve and the point of contact will move down the surface. In another modification of the surface of the contraction of the contact of the contract of the contract of the contact of the contract of the contract of the surface of the surface only one portion of wire is used. The contact thus advances at a rate proportional to the size

(1,534,704, J. H. Hammond, Jr., filed Sept. 9, 1918, issued April 21, 1925.) Receiving system for radiant energy, having



separate circuits in which two series of impulses of radiant energy having a prodeterminel phase difference may be utilized to control the operation of selenium cells at a receiver which, in turn, control circuits at the receiving station to selectively actuate the receiving mechanism.

Oratent No. 1,533,372. C. F. Brigham. Ffed June 14, 1924; issued April 14, 1925. Assigned to C. Brandes, Inc.)
Loud speaker for radio reproduction, in which the maximum energy from the electro-magnetic fluctuations is derived by means of a freely floating armature disposed in the magnetic field. The



armature is arranged within the electro-magnetic field and is actuated by the variations in the magnetic flux in such manner that all of the vibrations are effectively employed for the reproduction of signals.

(Patent No. 1,624,413, M. W. Stearns. Filed January 28, 1920; issued January 27, 1925.) RADIO TELEPHONE SYSTEM, in which the same tube circuit functions as a transmitted and receiver. The circuit is arranged for simula



taneous transmitting and receiving. A grounder aerial circuit is provided with a tuning inductance connected thereto and a divided secondary circuit across one portion of which the input circuit of the tube is connected and across the other portion of which the output circuit is connected.

RADIO NEWS LABORATORIES MILITARIA DILIMINI DI

ADIO manufacturers are invited to send to RADIO NEWS LABORATORIES, samples of their products for test. It does not matter whether or not they advertise in RADIO NEWS, the RADIO NEWS LABORATORIES being an independent organization, with the improvement of radio apparatus as its aim. If, after being steated, the instruments submitted. ▲ ▶ pendent organization, with the improvement of ratio apparatus as its aim. II, after being fested, the instruments submitted prove to be built according to modern ratio engineering practice, they will each be awarded a certificate of merit, and a "write-up" such as those given below will appear in this department of RADIO NEWS. If the apparatus does not pass the Laborators results, it will be returned to the manulacturers with suggestions for improvements. No "write-ups" such by manulacturers published on these pages, and only apparatus which has been tested by the Laboratories and found to be of good mechanical and electrical construction is described. Inanumbe as the service of the RADIO NEWS LABORATORIES is free to all manufac-not be accepted by the Laboratories. Apparatus ready for the market or already on the market will be tested for manufactures, as hereitofor, free of charge. Apparatus in process of development will be tested at a charge of \$2.00 per hour required to the control of the control NEWS LABORATORIES, 53 Park Place, New York City.



SPARTAN AUTOMATIC PHONE PLUG

This phone plug, submitted by the partan Electric Corp., 99 Chambers treet, New York City, is shown in te illustration. It works very sat-This phone poar, see, 99 Chambers Spartan Electric Corp., 99 Chambers Street, New York City, is shown in the illustration. It works very sat-isfactorily in radio sets. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 917.



n insulator is provided, through ich the wire is passed. AWARDED THE RADIO NEWS BORATORIES CERTIFICATE MERIT NO. 912.

SIMON WIRE TERMINAL



Simon made of spri merely press that sides, so that t

AWARDED THE RADIO NEWS LABORATORIES CER-TIFICATE OF MERIT NO. 919. THE ORCHESTRION DE LUXE THE ORCHESTRION DE LUXE
This loud speaker, furnished by
F. Bremerman & Sons, 3231 N.
Illinois St., Indianapolis, Ind., was
submitted to the Radio News Labora
aroairs for test. It affords very
good reproduction of radio con-



AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE MERIT NO. 870.

FRESHMAN VERNIER DIAL The dial shown in the illustration as submitted by Chas. Freshman b., Inc., 240 West 40th St., New ork City. This dial is equipped ith a small rubber roller which



AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE F MERIT NO. 915.

EVERSET CRYSTAL DETECTOR DETECTOR

This crystal detector, submitted by
the Everset Laboratory, Box 41
Edgewood Station, Providence, R. L.



is shown in the illustration. It is very sensitive and easily adjusted. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 916.

TUBING AND WIRE CORE The tubing and wire core shown the illustration were submitted the Varilex Corp., Rome, New Yor the Varilex Corp., Rome, New York One type of tubing made is similar to the ordinary spaghetti. Another type consists of a woven braid covered by cotton and celluloid. A third type consists of a tinned bus wire covered with two layers of cot-ton. The whole is then covered with a black insulating material, giving it



WIFE.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 926.

SWITCH
This push-pull battery snap-switch
was submitted by the Millimster Machine Works, 542 West 22d St., Wey
York City. It presents an attractive
appearance on the panel. It is well
built and is equipped with soldering



WOVEN INDOOR AERIAL

WOVEN INDOOR ARRIVAL This indoor aerial, shown in the histration, was submitted by the alley Narrow Fabric Company, 59 heatnut Street, Central Falls, R. I. is a strip of woven metallic braic



AWARDED THE RADIO NEWS ABORATORIES CERTIFICATE OF MERIT NO. 815.

nsformer, submitted Radio Co., 1817 Wile



good volume and quality in audio frequency amplifiers.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 914.

'NIFTY" GROUND CLAMP This ground clamp was the Rabio News La r test by the Amoroso



popes, etc.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 904. AERIAL BASE The aerial base shown in the iHus tration was submitted to the Radi-News Laboratories for test by th





AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 946.

BRANT BATTERY
battery of the standard type,
by the Brant Battery Combig the Brant Brant



The cells are of the lead acid type. The battery has a maximum voltage of 100 volts. It is very sturdily built and leakage is prevented by a built and teasage is prevenied by a special seal of insulating material at the top of each cell. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 869.

PILOT RHEOSTAT

The rhoestal shown in the illustration was submitted to the RADIO NEWS LARORATORIS for test by the Pilot Electrico Mfg. Co., 113-119 Brondway, Broodlyn, N. Y. This rheestat has a rate of resistance of six olums and operates satisfactorily as a filament control in radio re

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 972. LIQUID SPAGHETTI



Radio News Laboratories for test by the Phenix Aircraft Products Co., Williamsville, N. Y. This liquid spaghetti comes in a variety of colors and can be used on bus wires and other bare wires wherever installa-tion is required. It is very easily applied. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 960.

PILOT DIAL This Pilot dial made by the Pilot Electric Mfg. Co., 113-119 Broadway,



N. Y., was submitted to News Laboratories for test.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 943.

PILOT JACK The jacks shown in the illustration were submitted by the Pilot Electric Mfg. Co., 113-119 Broadway, Brook-



lyn, N. Y., to the Radio News Lan-osatonies for test. These jacks are well made and come in a variety of forms from single circuit to the more complicated filament control jacks and double circuit filament control

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NOS. 971 AND 940.

VIBROPLEX DIAL

This dial was submitted by the Vibroplex Co., Inc., 825 Broadway, New York City, to the Radio News Laboratories for test. It is of the



vernier type with a similar knob at the bottom to throw the vernier at-tachment in or out. When thrown one way the dial acts as the ordinary dial: when thrown the other way

advantage is taken of the vernier AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE MERIT NO. 969

TOROIDAL COIL The toroidal coil shown in the illustration was submitted to the Radio News Laboratozius for tes by the Pathe Phonograph & Radio



Company, 20 Grand Avenue, Brook-lyn, N. Y. This toroidal coil is well built and can be used satisfac-torily in tuned radio frequency am-plifiers. Provision is made for primary and secondary coupling.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 952.

ELECTRON TUBE The tube shown in the illustration was submitted to the Radio News Lasonatories for test by the Radio Products Company, 15 Moore Street, New York City. This tube has the



usual rating and operates satisfac-torily as either amplifier or detector, AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 968.

FIAT LOOP The loop shown in the illustration was made by the Radio Appliance La-boratory, 4884-90 North Clark St.,



Chicago, Ill., and submitted to the RADIO NEWS LABORATORIES for test. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 984.

BATTERY HYDROMETER -03/1

The hydrometer shown in the illus-tration was submitted to the RADIO NEWS LABORATORIES for test by the Scranton Glass Instrument Co., Inc., SCRANION, PA.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 961.

TURK POTENTIOMETER This potentiometer was submitted for test to the Raddo News Ladona-rokies by George Turk, 30 Irving Place, New York City. It nots satisfactorily in all radio receivers which require a variable potential for stabilizing.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 944. LITTLE SPITFIRE LOUD SPEAKER LOUD SPEAKER.

This loud speaker, shown in the illustration, was submitted to the Ranon News Lanonarouses for test by the Tower Mfg. Corp., 98 Brookline Avenue, Boston, Mass. It gives very time reproduction with regard to both

quality and volume. It is well made and attractive in appearance. AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 991.

PLUG-IN COILS

TORIES for test. They are of the plug-in type and are mounted in a base similar to the base of a tube. They can be mounted very easily and changed quickly in an ordinary tube

SOCKET.
AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 959.

GRID LEAK The grid leak shown in the illustration was submitted to the Radio News Ladoacroins for test by the Tridot Electric Co., Inc., 16 Hudson Street, New York City. It has a resistance very close to the rated values and operates very satisfactorily in radio receivers.

CONTROL D AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 958.

PILOT CONDENSER PILOT CONDENSER

The condensor shown in this illustration was submitted to the Ranto News Landonarrours for test by the Pilot Electric Mfg. Co., 113-119
Broadway, Brooklyn, N. Y. This condensor has a rated capacity of

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 975.

These coils were submitted by the Zashburn Burner Corp., Kokomo, ad., to the Rapio News Labora-Washburn B



COIL ANTENNA This coil was submitted to the Radio News Landarosius for test by the Tobe C. Deutschmann Co., 46 Cornhill, Boston, Mass. It is of the coollapsible type and operates satisfactorily over the broadcast range of wave-lengths with a .0005 condenser.



AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 957. THOMAS STORAGE BATTERY

THOMAS STORAGE BATTERY
This battery, furnished to the
RADIO NEWS LABORATORIES for test
by the Thomas Battery Corp., 511
West 50th St., New York City,
operates quietly and satisfactorily as
a source of plate voltage for radio AWARDED THE RADIO NEWS
LABORATORIES CERTIFICATE
OF MERIT NO. 885.

PILOT TUBE SOCKET PILOT TUBE SOCKET

This tube socket submitted to the
RADIO NEWS LABORATORIES for test
by the Pilot Electric Mfg. Co., is very
well made and has the added feature
of having the ends of the spring contacts roughened so as to make them self-cleaning.



MAZADA DIAL

This dial was submitted to the ADIO News LABORATORIES by the lazada Radio Manufacturing Commy, 3405 Perkins Avenue, Cleve-



AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 924,

MEISTERSINGER LOUD SPEAKER



This loud speaker, shown in the illustration, was submitted to the Raton Nawe The State of the Raton Nawe The State of the RaNawe The State of the RaAvenue, Boston, Mass. It gives very fine reproduction with regard to hoth quality and volume. It is well made and the RaTon Nawe The Ra-

Correspondence from Readers

Each month readers of RADIO NEWS give their trains or stiles regarding coment hattenings or admining in the radio field in these columns. Many interesting werhal hattles are fought on this horse

ANOTHER INVALID EXPERI-

Editor Ranto News: In the Sentember issue of Rapio News is an account by Thomas J. Howells, entitled "An Invalid Experimenter." I have just

as you say, it has put new life into me. am among the unfortunates who are oo, am among the unfortunates who are Mr. Howells has accomplished.

I am away behind the times in radio.

I am away behind the times in radio.
I am still using a honeycomb coil outfit, but
I have hopes of some day catching up to the
super-beterodyne era. It is one awful iob trying to keep up with the times when one is not able to get around.

I wonder if the radio fans (I mean those

I wonder if the radio tans (I mean those physically normal) can understand in the least just what a job it is to build a set, or even work at one, while in bed. Our friend, Mr. Howells, deserves a gold medal for being so modest about it. There are a hundred and one things which can happen to was mounting some apparatus on a board and I wanted a small brass screw. I lifted a hox of assorted screws over onto the bed to pick one out and just then my arm slipped you think it's a joke, just try it.

I use dry cell tubes, UV-199's, and find
them very good. (Besides, my friends can

come and see me without the dread of heine asked to carry out my storage battery to have it charged!) The one great drawback with the radio game is the fact that the doctor pays more attention to the radio junk than he does to the patient. However, I will spare you my opinion of the medical men

Now, sir, if you haven't any room for this letter, just chuck it, but I should greatly appreciate it if you would send me Mr.
Howells' address; maybe he and I could exchange a few letters.

J. GORDON EDINGTON.

89 Glouster St., Toronto, Canada.

A PLEA FROM RUSSIA

Editor, RADIO NEWS: Russian amateurs will have a friendly

correspondence and more close acquaintance with you! Please send along letters. If you can please send me some radio books magazines and different radio parts, for all I'll be sincerely thankful you, and may paper-money, emited during a revolution and t-cards with Russian views.

With each letter please enclose to belo me pay postage, some International reply coupons, on amount 30-60 cents. All letters and sendings send only by registered post to A. KALACHNIKOFF. Tomsk, Siberia, Russia

Krasnoarmeiskaja St. 66.

ABOUT THE THREE-RANGE RECEIVER

Editor, RADIO NEWS: I have built the three-circuit three-range receiver described in Ranto News for July,

to nut it very mildly. The volume with two stages of audio is tremendous. I receive stations in Kentucky, Missouri and Texas with volume enough to

and to say that the results are gratifying is

be heard all over an eight-room house. And the selectivity is excellent.

prefer the three-range set. Of course, the neutrodyne is more quiet. But the threecircuit three-range set is surely a distance-

Here is a little trick that I find very use-tul: If the outside plate of a variable air condenser is advanced about a quarter of an inch it will give quite a vernier effect, Perhaps some of the fans might be glad of this information

If you should care to publish such information, I will write you again, giving some wonderful set

WILLIAM RAMEY, Cadillac Mich

WELL WELL! Editor. RADIO NEWS:

I seen your International Radio is October Radio News and will you tell me how she works, the Inglish book condenser with the vernier knob k the which has a finer tread (thread?) than what N has yet the both which work off the same skrew shaft ain't it?

I wouldn't bother you like this onli my invalid grandmother (shes the one thats 102 and smokes a pipe in the rotogravure sections of the newspapers) says nothin ever fazed her until this come along and shes had a lotta love affairs too pop tells me and she wants to know how knob k works on the skrew shaft when it has a smaller tread. Yours trooly.

OSKAR WILD.

BRITISH VS AMERICAN RADIO Editor, RADIO NEWS: I have followed the correspondence on the above subject with great interest, and as a British operator of long experience,

ish radio, I should like to be permitted. through the medium of your excellent maga-zine, to draw attention to a few considerations which have been overlooked by your

Comparisons were ever odious, and it is practically impossible to make comparison between British and American radio when the conditions in the two countries are so vastly different. In view of this, it is regrettable that Mr. Bayes, your British cor-respondent, should have expressed himself so forcibly. I am sure that had he not overlooked a few points, he would never have

In any case, Mr. Bayes, hard words never lead one anywhere in a discussion of this sort. In fact, they only lead to individual international bad feeling, which is to be deplored.
Mr. Howe, in your May, 1925, issue, de-

scribes reception conditions on this side of the Atlantic, and on the European side, and his statements are quite correct, as far as they go. However, it is a fact that the United States generally is blessed with better receiving conditions than is Great Brit-ain. Why this is so I do not know, but after very many years of observation I can

after very many years of observation a can testify to that effect.

Mr. Howe says that he can see no reason why British stations should not carry as

well out into the Atlantic in a westerly direction as American stations do in an easterly direction. Neither can I, but I believe Pacific Coast stations are regularly picked un on the eastern seahoard of America whereas eastern stations are very seldon heard on the Pacific Coast Can Mr Howe explain that?

Signals undoubtedly do seem to travel better in an easterly direction, this fact having casting. Difference in time undoubtedly has something to do with it. By the time it is dark enough in the West to get best recention conditions the eastern stations have closed down conditions do not set in

till about 10 P. M. local time (roughly), so that when Mr. Howe was attempting to receive British stations at a distance of some 1.500 miles to the westward, he would be in approximately latitude 35 west where the in approximately latitude 35 west, where the time is two hours and twenty minutes behind Greenwich. As the British stations sign off at about 10:30 or 11 P. M., the latest time (locally) that he could listen for them would be about 8:30 or 9 P. M., when hest recention conditions have not yet had time to become fully established. The same remarks apply to any attempted reception of eastern stations on the Pacific Coast of the United States Many observers who attempt to compare

receiving conditions in various parts of the which though it does not explain everything, is, nevertheless, a factor of considerable importance.

What of the recention of British stations the castward of England? Has Mr. Howe tried it? Personally, I have not been very far east since the introduction of broadcasting, but observations in various parts of Germany, 600 or 700 miles east of England, have shown me that the B. B. C. stations come in many times stronger than they do to the westward. The results, in fact, are roughly comparable with those ob-tained at a similar distance from the eastern tained at a similar distance from the eastern American stations. Reports coming from Egypt, Russia, India and other places in the Orient, indicate that the British sta-tions are received in the East with a detions are received in the East with a de-gree of regularity and strength comparable with the reception of American stations in Great Britain, which seems to confirm my contention that signals travel best in an Mr. Howe is puzzled on the question of

the power used by British stations. This is excusable, and right here lies one of those points of difference which make comparison so difficult. In America, broadcasting stations rate

their power in accordance with the amount of power actually put into the antenna; that is, power output. In England, on the other hand, power is rated according to the input power of the generating plant, and includes the power absorbed by auxiliaries. Western Electric 500-watt radiophone equip ment, for example, obtains its power from a 5-kw. motor generator, which feeds all the auxiliaries, filaments, etc., connected with the set. In Engiatra, called a 5-kw. transmitter.

A. Dinsdale, the set. In England, such a set would be

Senior Operator R.M.S.P. Orduña, Member of the Radio Society of Great

Britain.



Conducted by R. D. Washburne

HIS Department is conducted for the benefit of our Radio Experimenters. We shall be glad to answer here questions for the benefit of all, but we can THIS Department is conficted for the hearful of our Radio Experimenters. We shall be glad to narwer here questions for the hearful of all, but we can a support the configuration of the property of the prope

Mr. Washburne answers Radio questions from WRNY every Thursday at 8:30 P. M.

DE FOREST F-5 RECEIVER

Mr. E. Schaefer, East Las Vegas, New

DeForest F-5 receiver exterior appearance. Note built-in loud speaker (with opening, cloth and grill-work covered). A modern 5-tube set.

reduct by 'the resistances marked R-1 and R-2. Bill the abstraction of these units required after the abstraction of these units required after the abstraction of the particular titles used in the subject of actilitation counted are referred to the subject of activities of the subject of the subject

December, 1924, circuit Q. 2055.
March, 1925, circuit Q. 2094.
March, 1925, circuit Q. 2099.
April, 1925, circuit Q. 2101.
Just, 1925, circuit Q. 2101.
Just, 1925, circuit Q. 2120.
Just, 1925, circuit Q. 2120.
July, 1925, circuit Q. 2127.
July, 1925, circuit Q. 2127.
July, 1925, circuit Q. 2130.
September, 1925, circuit Q. 2142-B,
Q. 2006, 1925, circuit Q. 2142-B,
September, 1925, circuit Q. 2146-B,
September, 1926, circui

It is exclose from the photographs that the most real respect transformers are of the more real respect transformers are of the more real respective transformers are of the appreciable field. The value of the variable construction. The value of the variable construction "loops" for the transformers exact construction "loops" for the transformers of the exact construction "loops" for the transformers of the exact construction "loops" for the transformers of the exact control to the exact transformer to the exact transformer to the exact transformers of the exact transformers to the exact transformers of the exact transformers to the exact transformers of the exact transformers that the exact transformers are transformers to the exact transformers that the exact transformers th

The variable condenses used in the composed content.

The variable by Cercuit are condenses of the content.

The sized leaves the active of the content of t


Q. 2. Would it be possible to apply regenera-tion to the oscillator-detector tube of the Trops-dync? dyne?
A. 2. Regeneration to a sufficient degree is automatically obtained in the circuit, due to the automatically obtained in the circuit, due to the struck when building the set.
Q. 3. On page 1679 of the March, 1925, Ramo to the circuit of the



The "Buzzerdyne." An improved wavemeter, By peculiar electrical action, a pure audio note modulation is obtained.

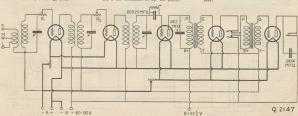A. 3. II your lamp cord is of "twisted pale" (two conductors, insulated and twisted spirally) place your wire, which may be regular insulated to the conductors of the conduct

ULTRA-SELECTIVE CIRCUIT (2148) Mr. Robert E. Schultz, Newport, Ky.,



Schematic circuit of "Type F-5" DeForest radio set. Units "R-1" and "R-2" are termed "anti-radiation devices." They control circuit oscillation. Ground is connected to "A" minus. Grid and plate leads must be short, while battery leads may be bunched like a telephone cable.



Conducted by R. D. Washburne

NIIS Departmen is conducted for the benefit of our Radio Experimenters. We shall be glied to answer here questions for the benefit of all, but we can publish above an anxiety and sufficient to the state of the properties of the state of th

Mr. Washburne answers Radio questions from WRNY every Thursday at 8:30 P. M.

DE FOREST F-5 RECEIVER

Mr. E. Schneier, East Las Vegas, New (2147) Mr. E. Schnefer, East Las Vegas, New Mc., all Maria information can you furrish about the DeForest F-5 receiver incorporating two stages of tuned radio frequency, detector, and two stages of tuned radio frequency, detector, and two suggestions of the receiver of the receiver of the amplification? Desire particularly to know the method used for preventing circuit oscillation, as would be of interest.

A. J. All the information we base available on

se circuit you mention is contained in the accom-anying text and in the illustrations appearing in sees columns. columns, will be noticed that circuit oscillation is con-

DeForest F-5 receiver exterior appearance. Note built-in loud speaker (with opening, cloth and grill-work covered). A modern 5-tube set.

reddet by "the resistances marked R-1 and R-2 in the state of the resistances of these units required after the state adjustment of these units required after the resistance of the resistance

December, 1924, circuit Q. 2055.
March, 1925, circuit Q. 2094.
March, 1925, circuit Q. 2099.
April, 1925, circuit Q. 2099.
April, 1925, circuit Q. 2101.
July, 1925, circuit Q. 2120.
Experimber, 1925, circuit Q. 2142-B.
October, 1925, circuit Q. 2142-B.
Still further means are described

Still further means are described in the text answering questions numbers 2126 and 2127 (July, 1925).

receiver having the F3 circuit are of 2000 and.
The first add requirery transformer has a
mean result found to the first process of the first
mean result found has faile affect upon the did
for, respectively, short, notilism or hang areful,
for, the leading to the short of the first process of the
form of the short of the short of the
form of the short of the short of the
first process of the first of the short of the
first process of the first process of the
first process of the
first process of the
first process of the
first process of the
firs

not the "poriable." School-sold as used. Grid leak value Shock-abovelve sockets are used. Grid leak value Shock-abovelve sockets are used. The "G" potential required for the audio frequency amplifier grids is secured by utilizing the voltage amplifier grids is secured by utilizing the voltage mapping of the secure of the s

Would it be possible to apply reger dyne?


A. 2. Regeneration to a sufficient degree is A. 2. Regeneration to a sufficient degree is desired with the sufficient to the sufficient desired with the sufficient

0.2149

The "Buzzerdyne." An improved wavemeter. By peculiar electrical action, a pure audio note modulation is obtained.

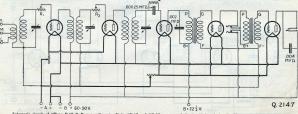A. 3. If your lamp cord is of "vested rapid two conductors, invalated and twisvet spirally) place your wire, which may be regular insulated lell wire, so that it will lie in the seiral groove of each of the place of the place of the place of the cord is covers a lamp cord distance of three feet or more, binding with tape. If the lamp cord is more, binding with tape. If the lamp cord is wire parallel to the light wire for a distance of three feet or more, and bind to the light wire free feet or more, and bind to the light wire for a distance of the cord of the cord

ULTRA-SELECTIVE CIRCUIT (2148) Mr. Robert E. Schultz, Newport, Ky.,



Schematic circuit of "Type F-5" DeForest radio set. Units "R-1" and "R-2" are termed "anti-radiation devices." They control circuit oscillation. Ground is connected to "A" minus. Grid and plate leads must be short, while battery leads may be bunched like a telephone cable.

Q. 1. As I with to build an exceptionally settive et a superselective receiver, one capable it uning very sharply, I am asking you to print a complete receiver diagram, in the "I Want to know" columns, incorporating the special wave 1925, Ranto News ("Selector—A Tuner for the 114"), unless you can suggest a still sharper uning arrangement.

A. 1. You apparently did not notice that circu o. 16 "Standard Hook Ups," September, 192 and Naws ("Selector—A Tuner for the City stures the type of connections you mention. atures the type of connections you mention.


However, we wish to suggest that you try out e new circuit we show as "Q. 2148." It is simmed to be so selective that it will "chop off it of the audio frequency side band." If it will a that, it is selectivity PLUS! Let us make that this business of "side bands" here in a few

words.

The U. S. Government figures on a separation superior of the control of t

Call the way the stations look how they tune in the set

(B) leak may

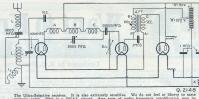

The Ultra-Selective receiver. It is also extremely sensitive. We do not feel at liberty to state maker's name. This is a REAL circuit. Any type of audio frequency amplification may be used, but it cannot be too carefully designed.

design shown. WD-11 or WD-12, C-11 or C-1 or equivalent tubes could also be used with the series arrangement of the filaments. (Should be necessary to say that the "A" potential must be about equal to the sum of the terminal voltage of the tubes used, plus one or two volts more for overcoming connecting where and rheastat resists. of the tubes used, plus one or two volts more too overcoming connecting wire and rheestat resist-ances?) It is up to the experimenter to adapt the circuit to the use of other tubes, such as those of the storage battery type, than the ones listed above. Any deviation from the plans given would be experimental and any forecast of results would be purely theoretical, as no variations have been



A bird's-eye view of one of the sets incorporat-ing the F-5 circuit described in these columns, showing coil and tube-socket layout.


mowing coid and time-socket layout. It tied as yet by our laboratories. An additional stage or two of audio frequency amplification may be added in the usual manner. Only a push-unit power amplifier should really be used.) Care must be extertised in the transformer election, or our be lost. As shown here, the receiver may be used as a standard of comparison of the qualities of other sets, for it is hard to beat this one when Compare death [2]. 248-84, 249-149. roperly built.

Compare detail Q. 2148-A with Fig. 2 appearage on page 532 of the October, 1925 Rabio
lews. This sketch is in the article, "A New
uper-Heterodyne." Here the author gives credit

y meaning and the contribution only to contribute disease.

To Jackson Presider for use of the bridge principles of the contribute of the

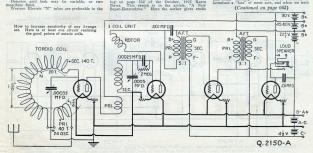brought together insider one tent. 10 is tuned impedance has been used in broadcast vers, but what was necessary to keep the cir from "howling"? Why, it was necessary fuce a "loss" of some sort, and when we ter-



announces three new power tubes reater volume

RCA, concentrating great efforts on the study of vacuum tubes, has developed three important new Radiotrons. They will be widely used in sets of all kinds in the last stage of audio frequency amplification. Their contribution to radio progress is greater power. They mean greater volume on dry batteries-and greater volume on storage batteries. They mean better tone, because they mean volume of sound without distortion.

These new Radiotrons are now ready for general sale, after months of testing.



Radiotron UX-120—A new, powerful amplifier tube that means great volume of tone on dry batteries. \$2.50 Radiotron UX-112-Anew power tube similar to the familiar UV-201-A, but several times as powerful. \$6.50 Radiotron UX-210—A super-power tube, several times as powerful as UX-120. Probably the most powerful receiving tube in existence. \$9.00



AN RCA PRODUCT

RADIO CORPORATION OF AMERICA

NEW YORK

CHICAGO

SAN FRANCISCO

Write forlist of set manufacturers using Crowd Panels, and our interesting folder-"Why the Receiving Set I Buy Should Be Paneled with a Crowe Metal Panel."



CROWE

Etched Metal PANELS Crowe Panels are made of brass and pacity" effects to a negligible mini-

AMONG THE LEADERS already so equipped are the follo ing well-known makes:

MARVELO

Reckley-Ralston BLUE DIAMOND

Grving

HARMONSON

BOSWORTH WORKRITE

Others have been added since this

MANUFACTURED BY

NAME PLATE &

MANUFACTURING CO. 1748 Grace Street, Chicago

I Want to Know

(Continued from page 640)

A research energy desirable.

A research property of the first his PER 72tion 2019. Common O. 1984 with PER 72tion 2019. Common O. 1984 with News. As
to see that the property of the May, 1933, Rains News. As
to see that the property of the see that the property of the see that the property of the



Q. 2148-A How the Wheatstone Bridge principle is in-volved in peanut tube circuit "Q. 2148." This tube is the W. E. 215-A, or "N" tube.

G.L. — Cotil lesk — "Les" is arranged to dile across one end of "Les" is arranged to dile across one end of "Les" is a "Les" in the second of the second on the second of sake:
Q. 1. Why is it that a neutrodyne with three stages of radio frequency amplification has not been put on the market? Woold such a Getube; etc. 1.

A. We consider your inquiry very interest ing. Sets having more than two stages of radio frequency amplification are available, but there are neutrolyses among the lot. Some of the points.

are: Two stages require three falst; these same, at that rate, would necessitize four dish! Tak too much time to tune. One-dial controls are asay, in the Indonatory. When it comes to can-say, in the Indonatory are supported to the result of was ready for the public. It takes a mighty good one-dial set, where the one dial operates two controls, to equal a 2-dial set where either dial has but one control regression of the control supply units will work well with five tubes but poorly on six. Too, the sixth tube means added expense (the tube price) and hattery consumption (if batteries are used) would be more. One more tube means one more



is ideal for coarse or extremely fine tuning, segregating even those stations now so closely grouped on the lower wave lengths; it brings them in with absolute precision. Volume and clarity are matters of course to the Accuratune. Ouickly substituted without alteration of your set.

MYDAR RADIO CO. 7 CAMPBELL ST., NEWARK, N. I.



The Famous Truly Portable TELMACO P-1 Receiver Four Tubes Do the Work of Seven

se peer of pertables in size, weight, case of tuning, sectivity, distance, velums, workmanship and price, rical, bood speaker and batteries self contained, emplets with tubes and batteries. \$125,00 3,00. Receiver only P-I Kit Saves You Money! our offer of the Telmaco P-1 Receiver in kit form has set with enthusiastic reception. This contains all revived parel, and illustrated instructions. \$80.00 complets kit ask your dealer or write us. Descriptive folder free.

Telephone Maintenance Co. 20 So. Wells St. Dept. B Chicago, Ill. ETELMACO:

Quality Radio Exclusively S Established 1918

1926 CATALOG SEND FOR YOUR COPY RANDOLPH RADIO CORP

Insure your copy reaching you each month Subscribe to RADIO NEWS - \$2.50 a year Experimenter Publishing Co., 53 Park Pl., N.Y.C.





A Separate Circuit for Each 40 Meter Wavelength Band!

Kellogg - for 28 years makers of precision telephone instruments and equipment — producers of quality parts since radio began —
Kellogg has perfected a radio receiver worthy to bear the Kellogg name.

In the illustration we visualize this wonderful engineering achievement

In the new WAVE-MASTER there are nine separate circuitsone for each 40 meter wavelength band. Each circuit gives that maximum efficiency heretofore found only in one short section of the dials of ordinary radio frequency sets. Each circuit brings within the range of the tuning dial a different group of stations.

How wonderfully simple tuning becomes! Merely set the pointer to the wave zone in which you are interested and bring in the desired

station with the single Selector dial. This remarkable tuning dial actually has a tuning range of 540 degrees-equal to 11/2 times around a complete circle - over three times the station finding range of any other set.

All other radio frequency sets have variable capacity which must be tuned, usually with three different dials, to balance with their inductance coils.

The WAVE-MASTER'S inductance is not fixed but variable and is easily and quickly tuned, with the one Station Selector dial, to balance the fixed capacities,

Write for full description and complete technical explanation of the Wave Master circuit. Please mention your radio dealer's name.

Kellogg Switchboard & Supply Company 1026 W. Adams St., Dept. K Chicago, Ill.

Radio Dealers and Jobbers The WAVE-MASTER franchise, backed by Kell-resources and our powerful advertising campai is most valuable. Open territory is being clo rapidly. Wire us, or get into Chicago, quick, s

\$275.00

With this Laboratory product anyone on reconditionals them good as now in a few minner? time. Operates on either A.C. or D.C., 110:120 volts—six particles on either A.C. or D.C., 110:120 volts—six particles on either A.C. or D.C., 110:120 volts—six particles on the control of n recondition old,

run

down

Tubes and

than a new Tub fully refunded. re all working t n account of one again. Pays for i e or two to

Laboratories

Chicago

199-Type

MACK LABORATORIES
724 Cass St., Chicago
(enthusen: Lucios 82.85 c
rater usumpa not acceptable)
the Mack Tube Reconstitions
your guanasteed refund plan. Our Guarantee Protects You

A-Type 199-Type

the control of the co



Q. 2148-B Details of cycloid coupler, A-B-C unit, aerial load coil, and recommended instrument layout.

dyne patent, can further royalties be claimed by anyone?

A. 2. The assembled set may be used for conanyone?

A. 2. The assembled set may be used for non-commercial reception, and all will be well, but a license and the payment of a royalty is equired before the set can be sold (technically). However, there can be little harm, I, believe, in disposing of one, or perhaps two, receivers of a certain type, just so the making and selling does not become a just so th habit. Q. 3.

tones one pittle atoms, a design of dependent of the many of the atoms of the atoms



LARGE CONCERT UNIT The Heart of the Speaker

Large size of this unit gives great range with tone of most pleasing quality which, combined with the amplifying properties of the Burns Horn, produces remarkable results. Horn is of distinctive design with pyralin flare in

several handsome finishes. It pleases the eye as well as the ear. Made by

American Electric Company CHIGAGO, U.S.A.



GUARANTEED FOR LIFE Folds to any position-Wires always taut

THE AALCO

LIST PRICE \$15.00

JOBBERS: Write for our proposition AALCO RADIO LABS. 6346 Cottage Grove Avenue CHICAGO

EVERYTHING IN RADIO TRACTIVE PRICES ALL RADIO COMPANY, 417 North Clark St., Ch

Insure your copy reaching you each month. Sub-scribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



646

There's Economy and Satisfaction

in these Valley units You will find both economy and satisfaction in the use of the Valley B-

Eliminator and the Valley Battery Charger. Economy in the B-Eliminator because

it stops forever the expense of buying new B batteries. .

Economy in the charger because it recharges your own storage battery at home overnight at one tenth the cost of service station charging.

And satisfaction in both because, by using them, you need never miss a program on account of low or wornout bat-



THE VALLEY B-ELIMINATOR OPERATES from ordinary light socket; provides a steady, noiseless flow of B current at a constant voltage all the time. With it, there can never be any decrease of signals or frying noises due to low B batteries. Volume is maintained. Reception is uniformly good. For receiving sets of from one to eight tubes. Costs less at the start than wet B batteries. Costs less in the long run than dry cells. Much more sat-



THE VALLEY BATTERY CHARGER IS the only charger needed for all radio storage batteries. Its correct 6-ampere charging rate makes overnight charging a possibility.

The Valley Charger also functions on any lamp socket. It takes about a dime's worth of current for an average charge. Quiet in operation. Most radio dealers handle the Valley B-Eliminator and Valley Charger. Any one of them will be glad to show you these units and explain their advantages.

VALLEY ELECTRIC CO. St. LOUIS, U. S. A.

Valley Electric

nection; both sindings in same direction). The medical probability of the motion that a regular "Mr. or the motion that a regular "Mr. or the motion for the motion of the medical probability of the motion of the



0.2150 The Gimbal Loop. Wave front of broadcast signal travels in vertical plane, while that of some forms of static is said to travel horizontally, enabling one to balance out either, optionally, with a gimbal-mounted loop.

tionally, with a gimbal-mounted loop, rent issue of the Railo Service Bulletin' (refec, free cents per copy; leventry three cents per year, of free cents per copy; leventry three cents per year, of free cents per copy; leventry three cents per year, of the cents of the per cents per year, or an extra per cents per year, or an extra per cents per year, or an extra per year, or any per year, or any per year, or any per year, or any per year, or year, or year, year

INTERFLEX HINTS (2150) Mr. J. Sildman, Kew Gardens, L. I.

(2150) Mr. J. Shlman, Kee Gardens, L. L. Sai, S. Chindla Lorey, S. C. Singhal Lorey, S. L. Sai, S. L. Watter, S. C. Singhal Lorey, S. L. L. Sai, S. L. Sai



Every "Super-Het" owner needs this Voltammeter

Owners of Super Heterodynes or any other sets receiving their "A" and "B" current supply from dry batteries should have a Nagel Combination Voltmeter and Ammeter. Accuracy in readings under any condition and safety against battery drainage are two important features that are embodied in all Nagel pocket-type battery measuring instruments. See your dealer or write The W. G. Nagel Electric Co., 512 Hamilton Street, Toledo, Ohio.

DRY CELL TESTERS AMMETERS VOLTAMMETERS · BAKELITI HOT MOULDED INSULATIONS


Write for Booklet "Opportunities in Radio"

Explains how you may become an expert Radio Operator or Radio Mechanic.

Y. M C. A. RADIO INSTITUTE 158 East 86th Street New York City

Print Your Own rules sent. Write for catalog presses ty THE PRESS CO., Y-72, Moridon, Cor

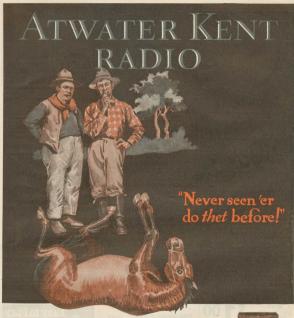Insure your copy reaching you each month Subscribe to RADIO NEWS—\$2.50 a year Experimenter Publishing Co., 53 Park Place N. Y. C.



FARMER in Vermont was trying to sell his A ancient mare as a spirited animal. He led her from the stable and was starting to put her through her paces, when suddenly she lay down, rolled over and died. The farmer was somewhattaken aback. "Well, well," he said. "Never seen 'er do thet before!"

Unfortunately there are radio receiving sets which bear a close resemblance to the old mare. They can often go through their paces. But at any time they are apt

to need first-aid badly. whether it is your first or your tenth, take this advice:

Look at it carefully, inside and out. See workmanlike job. Hear it in operation. Then ask your dealer about the manufacturer. How long has he been in business? What is his reputation?

Do his sets need a lot of service after they are sold? On a judgment of that sort, Atwater Kent

is willing to stand or fall.

Send for illustrated booklet telling the complete wary of Arwater Kent Radio. ATWATER KENT MFG. CO.















How Often Do You Say "I'd Give a Dollar to Get That Station Again?"

Automatic Radio Log Chart

Efficiency is the keynote of Radio half the evening trying to locate your

The Automatic Radio Log Chart enables you to instantly get any station you have ever heard before. The first time you get a station mark down the OF THE WRIST gets your dial readings.

Space provided for logging 180 stations. Eastern stations on one side;

The Automatic Radio Log Chart is simple as A. B. C. Any child can in-stantly understand and operate it. Takes the guesswork out of radio and station you want to hear.

Order Yours Today SENT ANYWHERE IN U.S.

ON RECEIPT OF ONLY

PACIFIC RADIO MFG. CO. 8-10 Centralia State Bank Bldg. Centralia, Washington.

PACIFIC RADIO MFG. CO., RI	X.
8-10 Centralia State Bank Bldg.,	
Centralia, Wash.	
Gentlemen-Enclosed is \$1,00. Send Automitic Radio Log Chart to	-
Name	
Street	
City State	
	=

a single stage of radio frequency amplification. The particular feature of the arrangement was the model of the particular feature of the arrangement was the particular feature of the particular feature of the death of indication, the most troublement ferm of feedback in panh circuits. The schematic circuit amplification of the death of the schematic circuit and of the terror of the death of the schematic circuit and of the terror of the schematic circuit and of the schematic circuit and the schematic circu 19.22, Rason Nows, page 400, may also be collected any, Three shades carried from the first parties of the page 100 miles, and the deep regularities are presented as the static, only now to be the most desirable entire the static, only now to be the most desirable which it is here recommended.

Normality of the page 100 miles are presented as the page 100 miles and page 100 miles are presented as the page 100 miles and page 100 miles are page 100 transformers give exceptionally good results in the Interflex sets.

2. Try reversing the radio frequency trans-former primary connections. Also, try reversing secondary connections. Control of the reversing secondary connections of the reversion of the re-secondary connections of the reversion of the re-secondary connections of the re-secondary connections of the re-cent of the re-ten of the re-ten of the re-cent of the re-ten of the re-cent of the re-ten of th

can be treef, but they are not likely 20 gife a topo-da. Different performance repairs should be tried and reversing the connections conceines 5. An arrial tempt of 65 feet, including lead-ing the control of the control of the con-ing the control of the control of the con-trol one and the circuit, the rails frequency of the trible may have a plate potential of about 55 gife consecred to the cryanic detector (and there-persons are the control of the con-persons of the control of the con-persons of the con-persons of the con-trol of the con-of the con-trol of the con-of the con-trol of the con-on-

t is not used.

7. When adding an audio frequency amplifier, asmall condenser across the primary or secondary of the first audio frequency transformer may im-9. The following Interflex articles have been

9. The following Interflex articles have been published:
"The Interflex" (I dial), RABIO NEWS, September, 1923.
"The Balanced Interflex" (I dial), RABIO NEWS,
"The Interflex Receiver" (I dial), Radio Review, October, 1925, N. Y. Telegram, August 29, 1925. 1925.

10. Note the effect of connecting a small variable condenser (about 5-plate size) from the post-crystal tube grid to "A" minus.

11. Fixed detectors are usually more rugged and are generally more satisfactory than adjustable ones.

ies. 12. Tune very slowly.

TOUGH

First He: "How does your low loss re-ceiver work?" Second He: "It's a TOTAL loss!"

Contributed by Everett Shepard.

THE WORST IS YET TO COME

Europe is receiving American dance music by radio, and so far has been very

ETHERIAL LOVE

My mind becomes a vacuum tube Whene'er I think of you: My heart gets quite ec-static,

Your eyes that flash like unquenched sparks, Break down my high resistance Like a transformed amplifier.

I really think we're both in tune. And ere through life we roam. Suppose you book up now with me, And share my humble ohm.

Contributed by Vernon F. Ashimvall.



Satisfaction Guaranteed or Money Back Cut Prices On All Standard Makes

LINCOLN TYPEWRITER, COMPANY

Boories Leading Independent Typewriter House Dept. 56A 298 Broadway, New York City



Out-performs-Out-lasts-Looks better Numerous tests have shown

out-perform any fixed crystal for distance, volume and quality of tone. For an idea

James Blue Bullet has been under 80 volts on the late steadily for a month. Of other crystals, the

Ask your mearest dealer for a James Blue Builet o send to us direct. Postpaid or C.O.D., \$1.00.

JAMES
2 Side Crystal 50C All sides sessit Two Crystals in one.

STAR-KING COMPANY 200 Davis Street









Speakers-Tubes-Receivers

Each sold under an unconditional guarantee of satisfaction.

Each sold on a restricted territory basis.

Each backed by comprehensive national and local newspaper advertising.

Sylfan Products are manufactured and marketed nationally by an organization of unquestioned integrity and financial standing.



are going to play a part of greatest importance this year.

Sylfan Matched Blue Specials

are without a peer, for quality, performance and long life. Absolutely guaranteed. (Any tube that will light replaced without question.)

Sold in kits of three and five tubes and also singles (to match tubes in kits).

All tube adjustments are made promptly by Baker-Smith offices. Dealers and Jobbers are not expected or asked to make adjustments.



are made on new scientific principles of recreation and amplification worked in such a way that every note of musicevery tone and inflection of the voice is reproduced perfectly. SYLFAN is a speaker you will never be willing to trade. It stands comparison with the most expensive-sells for a sensible price.

501-A Silver Tube for 499-A Peanut type 499 Peanut type. \$2.50 each





Cabinet type \$28

MARKETED NATIONALLY AND EXCLUSIVELY BY BAKER-SMITH CO., Inc.

New Call Building MANUFACTURERS

New York City . . JOBBERS ARE INVITED TO ADDRESS OUR NEAREST OFFICE FOR FULL DETAILS.

Sylfan Receivers

ntly satisfactory in performance—handsome in appearance—sensible in price. Engineering skill and craftsmanship of the highest type have combined to produce Radio Receivers truly remarkable for their tone quality and case of

prefere Radiis Recovers truly transseare to available.

If his such has not yet arrived, and your name and softens to see pleased. If his such has not yet arrived, and your name and softens to our measured of the seed of t









Practicoat



Practicoat



Getting the Most from Crystal Sets

0170101 0010

ensitive as good galena. Furthermore, they to not offer as much field for experimentation and therefore we will not consider them

MOUNTING CRYSTALS

After a good poer of crystal has been selected, direct by buying a quantity as mentoned above or by buying a quantity as mentoned above or by buying a quantity as mentoned above or by buying a quantity and a considerable of the constant o

To avoid this, a soft metal that mets be too the temperature of boiling water double he med for a preminent conformal to the control of the c

A semi-permanent method of mounting restals is by employing an ordinary cup for restals is by employing and ordinary cup for walls should be selected, so that three boles can be drilled and tapped therein. Do this and then server in three pointed thumber of the server in the place a crystal between these three thumbercews and tighten them up so as to make can apply the carbinister or other contact to the exposed surface and can usually find to the caposed surface and can usually find the property of the contact to the exposed surface and can usually find the can be considered to the capital can be used when this mounting is

CONTACTS

The subject of the contact that is to be conused with the crystal and that is to be connected to the other part of the circuit from that to which the cup is connected, receives the contact that you can possibly get is a piece of 14 Larat gold wire of about No. 26 gauge. This can be coiled into a spring formation and the other end fastened in the that it can rest lightly on the surface of the crystal and can be moved over the same.



Premier B Battery Cabinet

Our Premier B Battery Cabinet is a beautif piece of furniture. The B battery companment will take any type B battery. The spa of each B battery compartment is 4½" wie 8½" black and 10" days.



729-10 TO 107 22-60
The tops of these cabinets are figured walnut the emis and B battery pussels are select wal the emis and B battery pussels are select wal of massive molding. Nickel platel plate in the property of massive molding. Nickel platel plate in the plat

We Make 9 Styles of Cabinets for
14 Sizes of Panels.
Send for our 1925-26 line of cabinets at
"Factory to User" prices.
UTILITY CABINET COMPANY
WAUKESHA Phone 721 WISCONSIN





A marvel in design and construction! Coil air cooled, exposed on all sides Adjustable contact sliding lever. No vernier required. One nut mounting.



At all good radio dealers
With Knob, \$1.35
Stehed Dial Plate, 15c extra



Zenith was created for the home

ALL one needs to get the finest radio results from Super-Zenith is good musical taste and a feeling for exquisite tonal values.

So far as technical ability is concerned, the Super-Zenith is so easily controlled that a child can bring in just as many stations—just as quickly—each with the same clear quality of tone—as a radio engineer.

Only a demonstration can make completely evident the remarkably selective character of the Super-Zenith—its clear, sweet tone—its thorough dependability.

Such a demonstration is yours for the asking—in your own home, if you so desire. Simply telephone your nearest dealer.

n Commander Donald B. MacMillan

Again Commander Donald B. MacMillan chooses Zenith for his Arctic Expedition. When human lives may depend upon the reliability of radio performance, only one reason can explain his choice: Zenith has proved to be the best obtainable at any price.



Super-Zeniths are priced at from \$240 to \$2,000. Each instrument is sold under a quality guarantee. Above is shown the De Luxe Spanish model.

Super-Zenith VII . . \$240 Super-Zenith VIII . . 260 Super-Zenith IX . . . 355

Also Zenith regenerative sets (nonradiating) licensed under Armstrong

U.S. Patent No. 1,113,149

Zenith 4R \$100

Zenith 3R 175

Zenith Radio Corporation, Straus Building, Chicago, Ill.



5 times stations!



One man has raised his log one man has raised in log from 12 to 62 stations! An-other, in Seattle, gets Los Angeles in broad day-light! Better volume, sharper selec-tivity, freedom from disturbances, all are vouched for in hundreds of letters Super-Booster owners have sent us.

For selectivity it is positive-ly unequalled. It cuts through interference like a knife, getting the station you want,

The Super-Booster employs an advanced, patented appli-cation of the principle of inductance not embodied in any Hence, with it, you can improve your reception no mat-ter what kind of receiver you

It is a superbly executed mahogany cabinet, 9"x4"x5", placed on or near your re-ceiver. It is very simple to operate and costs only \$12.001 Thousands of Radio News readers have purchased the Super-Booster and these owners write us they would not be without the Super-Booster for many times its cost.

> You should have it NOW. Ask your dealer. If he cannot supply, send a money order for \$12.00 and we will ship direct, charges prepaid. Send your dealer's

Super Products

Manufacturing Co. 9181/2 South Vermont Street Los Angeles, Calif.

sture your copy reaching you each month, scribe to RADIO NEWS — \$2.50 a year, erimenter Publishing Co., 53 Park Place,

Various types of crystal detector stands that will adapt themselves to different contacts magazine and no renetition is necessary here In lieu of gold wire, thin phosphor bronze wire may be used and gives excellent results. In any event, clean the point of the wire periodically by rubbing it once or twice over be surface of a piece of fine sandpaper. will remove any oxide that may have collected and that may tend to make the

Another good little kink that often gives excellent results is the employment of a piece of pencil lead, sharpened to a point and used as the catwhisker. In doing this, the end of the catwhisker wire may be the end of the catwhisker wire may be wrapped tightly around the pencil lead as in Fig. 5 and then the point of the lead may be applied to the crystal. Another good contact may be obtained with a piece of antimony, broken up until a small sliver is obtained and placed in the detector in the same way as the piece of pencil lead shown in Fig. 5. This is particularly suitable with in Fig. 5. This is particularly suitable with silicon and the point should be so arranged that quite a good pressure can be obtained between it and the crystal. You can obtain quite a little knowledge from trying various contacts of this type with different minerals and crystals. Who can tell but that you will nd something that may be of assistance to other crystal detector fans?

CARE OF CRYSTALS

As mentioned above in this article, crystals and minerals should never be handled with the bare hands, but tweezers should always be used. Sometimes, after a crystal has be used. Sometimes, after a crystal has been in use for some time or after it has been added viting the control of the control have accumulated on the surfaces and will usually restore sensitiveness to a great ex-tent. This is a little trick that is worth trying and should be remembered in all crystal work, as it applies to all types of materials that may be used for this pur-

TESTING

Although there are many broadcast sta-Although there are many broadcast stations in operation today and it is very sel-dom that you will not have some station tuned-in, upon which you can test the sensitiveness of your crystal, still, when you are going over a quantity of material in search of a good piece, some sort of test that you can have under your control is to be greatly desired. The simplest way of accomplishing this is by using what is known as a buzzer test. This merely consists of one or two dry cells, a buzzer and a switch or two dry cells, a buzzer and a switch connected as shown in Fig. 6. The contact point of the buzzer is connected to the ground wire of the receiving set and no other connection to the latter is necessary. It is advisable to use a steady high-pitched buzzer as it makes testing much easier and more reliable. Furthermore, the buzzer should be so arranged that it does not make much noise, as otherwise it may bother you when testing. It can be packed in a small box by placing a quantity of absorbent cot-ton all around it. This will reduce the mechanical noise to a very great extent and often will render the buzzer almost and often will render the buzzer almost silent in mechanical operation. All that you have to do to use this test is to close the switch, and listen in on the phones. If the detector is correctly adjusted, you will hear a loud buzz in the phones, but if it is not, move the catwhisker until such a sound is heard. The more sensitive the spot that is neard. The more sensitive the spot that is found on the crystal, the greater the volume of sound that will be heard in the phones. Thus you can quickly tell when you find an extraordinarily sensitive spot.

It may seem to some of the readers that a



TOWN CRIER Radio's Most Beautiful Speaker

You will be delighted with the gorgeous colors . . the handsome, stippled finish, and the novel design of the Town Crier-the Speaker with the voice that thrills. Ask your dealer to show you a Town Crier Speaker. Write today for beauti-fully illustrated circular describing the Golden Polychrome and Green Poly-

List Price \$17.50 GALE RADIO LABS. CHICAGO 2509 Irving Park Blvd.





Easy to Read and Ready to Use The patented Chaslyn Balls show the condition of your Battery. Swim all THREE, Charged FULLY, Sinks the WHITE, Charge still RIGHT, Sinks the GREEN.

Sinks the RED,
Charge is LEAN,
Sinks the RED,
Charge is DEAD. Leading manufacturers of stor-age batteries use the Chaslyn Balls as Charge Indicators. At your dealer, or sent postpaid upon receipt of purchase price.

The Chaslyn Company 3843 Ravenswood Ave., Chicago



MORACH RADIO CO.

Jackson Blvd., Dept. 7.

The Kernch Junior A medification of the "Senice" but possess-tor all its important features-\$12.50.

When You're Talking WILLARDS To Your Customers

You can tell them that because of their power, steady current and freedom from electrical leakage. these very different radio batteries are used by over 200 leading broadcasting stations for standard amplifying equipment.

You can show them that the better job Willards do for the broadcasting station is the same identical job that the batteries in their own radio sets do.

You can give them visible proof that their Willards will be strictly brand new, and in the pink of

WILLARD

BATTERIES

condition when they get them-assurance that with an occasional recharge their Willards will operate like new batteries for years to come.

And when you've made the sale you know it's a clean one -the kind that makes satisfied customers- a sale that will require no service or further attention on your part.

Read about our plan for handling Willard Radio Batteries. It's the very plan you've wished some one would offer you.

Willard Storage Battery Co.

Cleveland, Ohio

The Right Selling Plan for Radio Dealers

Your local Willard Service Station will act as your jobber on Willard Radio Batteries.

This means a quick source of supply of strictly fresh. well charged batteries which you can turn over to your customers in the pink of condition

No servicing problems for you. Your local Willard Service Station assumes the responsibility for service.

Willard Radio Batteries will be advertised more extensively than ever this fall. Have your local Willard Service Station show you

this advertising and explain the details of this new and practical plan for selling radio storage batteries. The advertisements will be signed:

Sales and Service through The Willard Battery men and their Authorized Radio Dealers

Appropriate signs and window cards will identify you as an Authorized Dealer. Booklets and other valuable selling helps will also be fur-

nished.

Your Nearest Willard Service Station is Your Nearest Willard Johher



A STRAIGHT-LINE FREQUENCY ACHIEVEMENT Soldered, non-corrosive brass plates,

R UGGED, compact, sublimely efficient, with all the refinements of 15 years' experience comes the latest Hammarlund achievement -the condenser that distributes stations equally over your dials and solves the problem of critical tuning.

You will recognize many distinc-tive "HAMMARLUND" features of world renown. Others are new -the perfections of advanced engineering and the natural progress of the radio art.

with sturdy tie-bars that insure permanent alignment; one small piece of insulation placed outside of the electro-static field : strong, warpless aluminum frame, grounded to rotor; adjustable ball bearings at both ends of rotor shaft; bronze clock-spring pigtail; single hole mounting; new balancing device; a separate "hand-capacity" shield for use if desired; a quality product at a moderate price.

.0005 Mfd...\$5.00 .0003 Mfd...\$4.65 .000375 " ... 4.75 .00025 " ... 4.50

At the Better Dealers. Write for Descriptive Folder. HAMMARLUND MANUFACTURING COMPANY New York City 424-438 West 33rd Street

For Better Radio PRODUCTS

Rubber Covered Insulators



Neat and efficient. For antenna, good for lead in wires. Small screw starts readily and makes finished job. Great improvement over large, unsightly insulators. Tacy keep of the way. Packed the wires in place and out of the way. Packet 10 in a box, 25c at your dealers or direct from u

CULVER-STEARNS MFG. CO. Worcester, Mass., U. S. A.



THE PRESS

ECONOMY RADIO SALES CO.
Sixth Ave. Dept. A New York
DEAL DIRECT AND SAVE REAL MONEY

good many of the points stressed above are rather small and superfluous and therefore not worthy of consideration. This, however, will not be found to be true because in crystal detector work there is so little energy being handled by the set that every effort must be made to conserve it. Therefore, at tention to detail is most necessary and if you fail to give it, your results will not come up to your expectations and you may be disappointed. Therefore, adhere to the principles laid down and you cannot go far

\$300 PRIZE CONTEST (Continued from page 593)

it necessary to go to press. We tried fran-tically to get in touch with the artist, but he had left no address, so it was a case of making a new cover or running the one with the 34 mistakes. We had no time to make a new one, so we printed the one which you now see adorning the magazine.

As we said before, the set is supposed to be the usual tuned radio frequency set DON'T FORGET THAT! Of course, the usual set nowadays does not have the binding posts on the front panel. These are usually inside. But in order to show the onnections to the reader, we took the liberty of putting the binding posts in front. That is what you might call "poetic license." That is what you might call "poetic license."

This in itself is no mistake, as it was quite intentional.

Some of the mistakes have been so cleverly hidden that it will take you quite a while to puzzle them out. They are not all so easy, by any means. For instance, one of the mistakes is that there is no arrow-head above the left-hand rheostat. That counts as one error. There are 33 more besides this one for you to find. thing is not as simple as it looks, and it takes a bit of ingenuity, logic, and thought to find all the mistakes. We have, therefore, inaugurated a \$300 Prize Contest, with prizes as shown here, which will be paid for the best correct answers. We believe this is the most interesting and absorbing prize us me most interesting and absorbing prize contest we have ever run. Start on it right now, and if you don't find all the mistakes at once, don't get discouraged. Maybe you'll find more of them tomorrow.

BULES OF THE CONTEST

1. Anyone may enter this Contest, with the exception of the employes of the Ex-PERIMENTER Publishing Company and their families

2. Only one set of answers may be submitted by each contestant.

3. All answers must be typewritten or in Penciled matter is not acceptable. 4. List as many mistakes as you can find, using a separate line for each mistake, num-bering the first one "1," second one "2,"

etc., down to "34." 5. Make your answers as short as pos-sible. THE SHORTEST CORRECT ANSWERS WILL BE AWARDED PRIZES IN THEIR CORRECT ORDER.

6. In case of a tie, identical prize-winning answers being submitted by different con-testants, identical prizes will be paid to those tieing for the prizes.

7. This competition closes on November 15 at noon, by which time all answers must have been submitted. 8. Address all entries to Editor "What's

Wrong Picture," c/o RADD Park Place, New York City. RADIO NEWS, 53 HOPELESSLY ETHERIZED

No. 1: "Can't you reason with your No. 2: "No. He's announcer at XPK. and always up in the air."

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year.

Experimenter Publishing Co., 53 Park Place, N. Y. C.



Karas Harmonik Transformers

Amplify Radiocast Music with Absolute Fidelity!

No sooner had Karas Harmonik Transformers been introduced than letters began to pour in from all over the country. Exacting set builders, after many disappointments, found in the Karas Harmonik an audio transformer which really amplified with tremendous volume — and positively without distortion.

"Now I know radio as I never knew it before." So Mr. E. M.

knew it betore. So man, ex-Lubeck of Kokomo, Indiana, ex-reased himself. "Karas Harmoniks bring in every voice and every instrument as distinctly as one could get them in the room." wrote the Rev. Wm. Stellhorn of Columbus, Ohio. "I room, "wrote the Rev. Wm. Stellhorn of Columbus, Olio."

Consider your transformer a real musical instrument. Like a great was a mental instrument. Like a total musical many the control of the control of the columbus of th ment could be picked out with perfect distinctness

These few reports—picked at random from scores of better—bell you more Covincingly than WE can tell you the wins—bell you more Covincingly than WE can tell you the wins—monik Transformers in your new self you build one—or your old set if you keep it. Nothing like it has ever been known before the Karas Harmonik was produced. Nothing approaching it has ever been developed since. Remember, the finest loud speaker card it overcome the shortcomings of defective or inefficient transformers.

Here, for your enjoyment, is an audio transformer, scientifi-cally designed to reproduce through your speaker all of the beauty of Radiocast music—exactly as it is rendered

ras	Elec	tric	Co.,	Chicago,	m.	

Respectfully yours Robert Loos, 1640 N. Leavitt St., Chie in the studio, whether by a soloist or the largest band or

The problem of amplifying high, low and medium audio frequencies to an equal degree has finally been solved. Sonorous base notes pour forth from the speaker in full strength and rich tone quality. The vital harmonics and rich overtones are brought out in their true beauty by this marvel of audio transformers.

All last season, home set builde

tle more for Karas Harmonike than common kinds cost. you want the unmost pleasure that radio has to offer, set a pair of Karas armonik Transformers at once. Whether you are building a new set, so, Or, if you don't care to issaid lithen yourself, any radio repuir man ill do it for you at small expense. Why not make up your mind right we to have the best musle your set is capable of giving?

Karas Electric Co., 4036 N. Rockwell St., Chicago, III.

Name Address.

If you send cash with order we'll send Transformers postpaid,

TRUE TONE QUALITY





e Handbook of Resistance upled Amplification. At Best dio Dealers 25c. Direct by mail,

CLIP THIS COUPON DAVEN RADIO CORPORATIO 138-169 Summit St., Newark, N. J. Please send me the following on Re-sistance Coupled Amplification;

Check one Resistor Manual, 30c is enci Complete Catalog (free).

FOR DEALERS: Send your let terhead or card, or this coupon and we will have our nearest dis tributor communicate with you.

VOLUME was formerly the goal of radio engineers. The blare of discordant trumpets succeeded the tinkling of the harp. The goal had been reached.

But true tone quality is the star we now are shooting at. This ex-plains the phenomenal growth of the demand for resistance coupled amplification. The end of the era of distortion is in sight. Daven engineers have pioneered in resistance coupled amplifica-ation. Daven Resistors and Mountings, Ballasts, Amplifier Kits and Super-Amplifiers are standard everywhere

The Daven Super-Amplifier is the aristocrat of amplifiers. Absolutely no distortion. A revelation to music lovers. It is sold by dealers everywhere, complete, ready to connect with tuner and batteries, for \$15.00.

DAVEN HIGH-MU TUBES

MORE volume of true tone quality is the latest achievement of Daven Engineers.

The new Daven Tube Type MU-20 increases the amplification of the Daven Super to equal or exceed that obtainable with trans-formers. 6 volt, ½ amperc—\$4.00 cach. The Daven Power Tube Type MU-6 for the last, or output stage -85.00.

DAVEN PRODUCTS ARE SOLD ONLY BY GOOD DEALERS

The Sine of Merit RADIO CORPORATION

Resistor Specialists

New Jersey

Newark LITTLE THINGS OF RADIO

I WILL YOU AT HOME IS A RADIO EXPERT

n tube Write Today

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, New York City.

Radio Controlled Automobile

(Continued from page 592)

To understand thoroughly the operation of the car it is best to describe what happens when the car is started and running. pose it is standing parked by the curb. operator in the control car would send out a certain number of dots on the selector transmitter. Each of these dots would move the selector switch forward by one point. This is done through the ratchet arrangement. Each impulse actuates the magnet connected to the ratchet arm. Of course, the operator knows at all times the location of the selector arm and so can send the required number of dots to pick up any circuit STARTING THE CAR

For starting the car he would place it first upon the ignition point. This would directly close the circuit-through an intermediate relay-connecting a solenoid to a battery. This solenoid would pull its armature in, which would, in turn, close the igni tion switch. The operator would then move the selector over one point, which would connect the gas adjustment into circuit ready for operation. However, nothing would happen until he pressed the key to the sec-ond transmitter, which would close the master battery circuit. This action would close the battery circuit connecting the gas solenoid which would, in the same manner as with the ignition, throw the carburetor butterfly valve into the open position. Then another tap at the selector switch

to place the starting motor circuit in position, followed by a second tap at the other key closing the circuit, would start the starting motor. It would continue to rotate as long as the second key was closed. Once the engine was started, the second key could

The clutch is, of course, out and the service brake set. Another movement of selector switch and a tap at the second key releases a brake, while the two keys worked again allows the motor on the clutch pedal to revolve slowly, thus gradually letting the clutch into place and starting the car. Then the operator must think fast. His next step is to set the selector for steer left and press the second key. Through this means he gets the car into the middle of the road. he quickly shifts the selector to the clutch and gives the second key another tap. clears the clutch. All the time the car is going and its path must be watched and the control system held in readiness for an emergency. However, if everything is clear, once the clutch is out, a few more dots on the first receiver sets the selector switch to

circuit which pulls the gear lever back into the "high" position. Then the clutch motor must be selected again and another dot sent so that the engine is connected to the back end. The tuning of the receiver on the radio car is, of course, as sharp as it is possible for them to be made. To the pres-ent no trouble whatsoever has been caused by interfering signals from other stations. As the sets are now arranged, a fairly

the gear shift connector and another dot on the control key connects a large solenoid in

strong signal is needed to cause the relays to operate. From the experiences of the inventor up to the present time there will be little, if any, trouble caused by interference from outside stations actuating the mechanism. And since the power of the transmitters which control the car are of only 10 watts power, little interference to other stations will result from the use of the car.

Alden Sockets Take New Standard Tube Bases

Tune manufacturers announced last summer that tubes were henceforth to have standard bases, making the terminals on all these standard tubes identical, in order that the purchaser of a set may use tubes adapted for use on storage batteries or tubes adapted for use on dry cells without any change

This naturally raised the questions,—"Is there a new Na-Ald Socket to take these standard bases?" And, "Can present Na-Ald Sockets be made to take these standard bases?" The answer to both questions is: "Yes, there is a new Na-Ald Socket and several adapters for new tubes. See next page for illustra-



An easy way to get clearer radio

MANY radio never have put up with disturing never without realizing they could be lessend by heeping contacts clean.

Kny skie in need when you hadd a cut and hadd bists advantage were at seeds No. 46th. Societis. Replace there is your present as if internal or getting cleans railin. Change in No. 46th on the net you hay, if the manufactures has not yet standardized as then the property of the manufactures has not yet standardized as then.



ACINDER, SO Small that you can scarcely see it, is a trifle until it blows in your eye! Until then it deem't teem passible that it could cause so much trouble. By the same token, it doesn't seem possible that a little corrosion on the contacts between tubes and sockers could cause so much trouble in a radio set.

Scarcely any one realizes the extraordinary importance of lean, hight, perfect contact, if you want to get clear radio free from exasperating noises. In all the field of electrical equipment, there is in a single case (except perhaps the much offending doorbell pash button) where ample provision is not made to keep contacts clean. How much sore important it is for the radio set, the most delicase electrical appara-

Na-Ald de Luxe Socket

Is orange to the Luxe observed in the Luxe of the latest and the contacting surfaces come to rest when the transpire, has been down, providing clean, bright, perfect contact in the easiest possible way. The tubes need

provides the easiest possible way to get clearer radio.

These advantages are obtained with the new UX tubes; even with the new UX 199 and UX 120 when used in the Na-Ald 419X adapter.

de Luxe Cushion Socket

This new Na-Ald de Luxe Cushion Socket provides, in addition to clean contact, other features improving your radio. The cushion is a shock absorber, eliminating such vibrations and disturbing noises as those produced by a trolley rumbling past your house, or by your loud seaker.

For the first time these cushion sockets permit the use of hidden wiring, together with direct; positive connections with the same metal that contacts with tube terminals, doing away with the binding posts. Such direct connections help toward clearer radio.

Lowest loss and highest insulating qualities are insured in Alden sockets by using Alden Processed, genuine bakelite. To get clearer radio, use Na-Ald sockets, not only in the set you build but also install them in the set you buy. See next page.

traping but note assets possible way. The tubes need not be removed. No other socket will do this. It best tested circuits.

ALDEN MANUFACTURING COMPANY Makers of the famous Na-Ald Sockets and Dials Dept. K-13, Springfield, Mass.



Plane and "What to Build	
about the new standard-ba	"information, together with information se tubes.
Y.su.	
Seeme	







No 419-X



N. 481-V





Now color adds its charm to the miracle of radio

TET the beautiful warmth and mellow-L ness of blending hues and harmonies of color add to your enjoyment of the miracle of radio. How fitting that the turning of harmoniously colored dials should release the kindred harmonies of sound, which your radio brings you -the thunderous notes of the distant organ, the crashing ensemble of the symphony, mad bursts of passion; all the myriad voices of music that stir the emotions of the heart and uplift it with happiness.

Let color make your set more than an instrument of mechanics and currents. Let it blend in beauty with the most exquisite furnishings of your home. Express your individuality in radio's latest creation -Na-Ald Colored Dials.







Can you tune in quickly? What a difference

a good dial makes

Nothing has been found as easy as the dial for quick, accurate tuning because the eyes are directed to one spot where the numbers appear, thus eliminating the inconvenient and eve-tiring effort of following a pointer around a fixed scale.

The graduations are clear cut and scientifically determined as to length and locations. Good appearance and easy tuning are combined in Na-Ald Super-de Luxe dials.

You can obtain Na-Ald Dials at radio, electrical, and hardware stores everywhere. Be sure you have Na-Ald bakelite dials in the set you build or buy

Send for free "What to Build" information, showing a number of the best tested and selected circuits.

New colored dials give surprisingly handsome appearance

LIKE making a new set out of an old one is the striking and pleasing change brought about by equipping your radio with the new Na-Ald beautifully colored dials, the newest thing out. This improvement is just what is needed to give thousands of sets an appearance in keeping with the decorative beauty of the homes in which they are placed. Imagine how it will improve your set to install garnet, malachite-green (like mottled green and white marble), brilliant tortoise, or grained mahogany dials. Obtainable in regular dials, the new vernier, and the new man-size five-inch dial.

> ALDEN MANUFACTURING COMPANY Manufacturers of Na-Ald Sockets and Dials Dept. K-13, Springfield, Mass.

ALDEN MANUFAI Dept. K-11, Sprin	
	Build information, together with information
about the new stand	land-lensemation, together with more marion
Name	
Name Street	



New! Vernier Dial

AFTER months of engineering and practical experiments, we can now offer you this new Vernier Dial. Every desirable feature is included, combining all the best qualities which a Vernier should have. The mechanism is enclosed in the dial itself and is simple, positive and sturdy. So smooth and positive in operation that to try it is to want it. Even turning the dial farther than it should go cannot injure it.

This Vernier is an Alden Processed Bakelite Dial, with a minimum ar of metal. There is no "live" metal, so the dial does not carry the hand capacity to the panel. It matches the standard Na-Ald Dial so that you can use this Vernier on the critical condenser, and plain dials on the others.

This new Vernier fits all the various condenser constructions. It is attached quickly and satisfactorily and is one of the few Vernier dials that can be used on a condenser with one-hole mounting and on metal panels. No possibility of backlash under any conditions.

New Man-Size Five Inch Dial

ANOTHER new Na-Ald Dial is massively built-five inches in diameter. It has a double knob and provides a comfortable man-size grip. Your fingers do not cover up the numbers. There are 200 graduations instead of the usual 100, and the arrangement of the numerals results in quick, easy reading.

With this big knob and the 200 graduations it is possible to swing from station to station - quickly and accurately. It is generally preferred to the Vernier on sets that do not have critical tuning, such as the neutrodyne.

Both the new Na-Ald Vernier Dial and the new Na-Ald five-inch dial are furnished in the handsome new colors.

uper-de Luxe 3° Dial No. 3034-black 50c; any color \$1.00. Super-de Luxe 4° Dial No. 3044-black 75c; any color \$1.50.

Boxed and matched set of three 4" Dials (No. 3044), and two rheostat knobs (K 3844), any color \$5.00.

5" Dial No. 3054 and Vernier dial No. 6044-in black each \$1.50; brilliant tortoise \$3.00; other colors \$2.50. Colors: black, grain mahogany, mala-



MacMillan received and sent with Thordarson Transformers

KENNEDY KENNEDY Radiadune Radiadune Manstiehl Manstiehl Manstiehl

Thermiodyne GLOBE
Deresnadyne

Deresnadyne ADLER-ROYAL MURDOCK MU-RAD

Valley Silver-Marshall

ULTRHOUNE Newport LEICH

NUNN-LANDON KUSTOMBILT and many others use regions, you too would be very particular to select the best equipment — especially in radio, your sole means of communication.

Thordarson Super Amplifying that year after Transformers — the identical of fine sets—

If you were commissioned to explore the polar

THORDARSON Super Amplifying Transformers — the identical transformers sold by dealers everywhere and used in a majority of quality sets—have been the exclusive choice of MacMillan on his Arctic expeditions.

Surely no greater tribute can be paid to the actual supremacy of Thordarson Transformers, product of the world's oldest and largest exclusive transformer specialists. Faultlessly they amplified programs and messages from great distances on the 1923-1924 expedition — and came back "as good as new." Equally successful was their performance on the last expedition.

The wisdom of MacMillan's choice is further confirmed by the fact

The Thordarson" Autoformer" All Frequency Amplifiers are our latest development. They amplify clearly the lowest as well as the highest notes of an instrument. An adaption of impedances,

that year after year, leading builders of fine sets — makers of fine instruments especially noted for distance and superb tonequalities—use more Thordarsons than all competitive

transformers combined.

In addition to Thordarson audio frequency and power amplifying transformers in his receiving sets, Mac Millan chose Thordarson Transformers for exclusive use in his broadcasting station, WAP, on board the Peary. WAP successfully broadcast the weird voices and instruments of Eskimo entertainers back to civilization.

Thordarsons cost more to build but no more to buy. Dealers everywhere. Interesting bulletins on

amplification mailed free.

Autoformers are \$5 each. Other Thordarson Radio Transformers: Audio Free

quency (subpanel or top mounting ty)
2-1, \$5; 3½-1, \$4; 6-1, \$4.50. Po
Amplifying, \$13 the pair. Interat
Power Amplifying, each \$8. If de
cannot supply, order from us.

THORDARSON ELECTRIC MANUFACTURING CO.

Transformer specialists since 1895**

WORLD'S OLDEST AND LARGEST EXCLUSIVE TRANSFORMER MAKERS

Chicago, U.S.A.

IORDARSON

AMPLIFYING TRANSFORMERS

Standard on the majority of quality sets



FAHNESTOCK CLIPS



tors for every radio pur "THE IDEAL CONNECTOR" FAHNESTOCK ELECTRIC COMPANY
Long Island City, New York



NTRY CIRCUIT bear Atlantic Co., Cuba and Havaii. Our new to assest and cheapest to build. One lon. One tuning central. No selder do it. BOOKLET FREE or comp Vesco Radio Co., OAKLAND, CALIF.

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year.

Experimenter Publishing Co., 53 Park Place, N. Y. C.

Radio Set Directory Continued from page 631

Trade Namé: Arionola Mo Circuit: Tuned radio frequency Batteries: Storage Antenna: Without Loud Speaker: Separate Controls: Three List Price: \$79.75

Manufacturer: THE
W. B. Duck Co.
711 Adams St.
Toledo, Obio
Trace Name: Duck
Bahnced
Gircuit: Tuned radio
frequency
Batteries: Both
Antennas: None
Loud Speaker: Separate

Control: Three List Price: \$100

Trade Name: Duck
Type A-884 De Luxe
Balanced
Circuit: Tuned radio Batteries: Both Antenna: None Loud Speaker: Non Controls: Three List Price: \$125

Manufacturer: ELECTRICAL PRODUCTS
MFG. CO..
69 Sprague St..
Providence, R. I.
Trade Name: Dymac
Selecto-5
Circuit: Dymac Balanced radio frequency Ratteries: Either

Antenna: Outdoor Loud Speaker: Separate Controls: Three vernier, quick acting List Price: \$75 Manufacturer: C O LONIAL RADIO
CORP.
East Ave. and 10th St.,
Long Island City, N.Y.
Trade Name: Colonial
Model 16-5
Circuit: Tuned com-

radio Batteries: Dry
Antenna: Both
Loud Speaker: Sepa-Controls: Three List Price: \$125 Trade Name: Colonial Model 16-6 Circuit: Tuned com-pensated radio fre-

guency
Batteries: Dry
Antenna: Both
Loud Speaker: Sepa-Controls: Three List Price: \$175 . . . Trade Name: Colonial Model 17 Circuit: Tuned combi-nation radio fre-

quency Batteries: Dry Antenna: Outdoor Loud Speaker: Sepa-Loud Sperrate
Controls: Two
List Price: \$58.00 Trade Name: Colonial Model 20-6 Circuit: Tuned combi-nation radio fre-

quency Batteries: Storage Antenna: Both Loud Speaker: Separate ontrols: Thre List Price: \$175 Trade Name: Colonial 21-5 Circuit: Weagant Batteries: Storage

Antenna: Outside Loud Speaker: Separate ontrols: Thr List Price: \$87.50 Trade Name: Colonial
Model 23-5 phonograph panel
Circuit: Weagant
Batteries: Storage
Antenna: Outside
Loud Speaker: Separate Controls: Thr

Trade Name: Colonial Model 24-5 portable Circuit: Tuned combi-nation radio fre-Batteries: Dry Antenna: Both Loud Speaker: Sepa-

rate Controls: Two List Price: \$85 Manufacturer: ELEC-TRICAL RESEARCH LABORATORIES.

2500 Cottage Grove Ave. Chicago, Ill.
Trade Name: Erla Circloid Five De Luxe cabinet
Circuit: Tuned radio frequency, licensed under U. S. Navy paterit
Batteries: Storage
Antenna: Both
Loud Speaker: Sepa-

Controls: Three List Price: \$77.50 Trade Name: Erla Circloid Five De Luxe cabinet
Circuit: Tuned radio frequency, licensed under U. S, Navy Batteries: Storage Antenna: Both Loud Speaker: Sepa-

Controls: Three List Price: \$69.50 Trade Name: Erla Cir-cloid Five De Luxe cabinet Circuit: Tuned radio frequency, licensed under U. S. Navy under U. ...
patent
Batteries: Storage
Antenna: Both
Loud Speaker: Built-in
Controls: Three
List Price: \$142.50

Trade Name: Erla Circloid Five De Luxe
cabinet
Circuit: Tuned radio
frequency licensed
under U. S. Navy patent
Batteries: Storage
Antenna: Both
Loud Speaker: Built-in
Controls: Three
List Price: \$113.50

ELGIN RADIO SUPPLY CO., 270 E. Chicago St., Elgin, Ill. Trade Name: Elgin Circuit: Differential regenerative Batteries: Either Antenna: Both Loud Speaker: Built-in Controls: One List Price \$75

Trade Name: Elgin-Super-Reinartz Circuit: Differential regenerative Batteries: Either Antenna: Both



The SAAL

Soft SPEAKER

brings the best out of your set

SAAL Jr.

The same in every respect as the Saal Soft Speaker except is measures 18% instead of 21% inches in height.

In the Saal Soft Speaker Unit the action of four pole pieces of a powerful magnet are concentrated on a carefully poise connected to the disphragm by a pin. This pin moves the dia phragma with a push and pul The action is extremely species reproducing all consonants and overtones; we the unit can't used as standard by many leading manufacturers of fine producing manufacturers of the results.

YOU may have the best receiver ever built, but the quality of your entertainment is limited by the quality of your speaker. Bring the best out of your set by using the Saal Soft Speaker.

The Sail does not force you to choose between volume and tone quality. It combines volume with a velvet tone. It is not a faid. It is not a trumpet. It is a faithful reproducer of radio programs, properly constructed and shaped for the accurate reproduction of sound. It removes the objection to loud speakers. It has no blare, no blast, no metallic ring.

The Saal Soft Speaker is made to last a lifetime. The neck is of aluminum. The bell is of genuine Bakelite. There is no wood, no tin, no composition. It has nothing to warp, crack or deteriorate. The reproducing unit is of all-metal construction and cannot be harmed or "blasted" by the loudest receiver. It maintains its tone with any volume. There is no adjustment knob to complicate tuning.

In appearance the Saal with its black bell, black crackle throat and graceful lines is the aristocrat of horns. Also furnished with a brown bell and gold or silver stippled throat at\$5 extra. It is guaranteed to give you satisfaction. Hear it at your dealer's

SAAL SPEAKER

VOLUME WITH TONE QUALITY

Manufactured and guaranteed by H. G. SAAL COMPANY, 1800 Montrose Ave., Chicago, Ill.

NO-DIAL 5 Tube Receiver \$980 less accessories

~ and Now a Receiver Without Dials! Simple. trouble-proof, beautiful-New/

Licensed under Blackmore Patents and Patents Pending. Hogan Patent 1,014,002.

NO-DIAL is a new combination of tuned radio frequency and resistance coupling.



The Set for Every Member of the Family

Listen! Sweetly clear, an overture, the prelude to a concert in a distant city floats into the room and fills it. A touch of the finger brings it to you. No need to know about radio-no need to understand its myriad technical terms.

A wonderful instrument is the NO-DIAL, so simplified that it is amazing! There are no dials to twist-none of the trying nervous tension that the adjustment of dials produces-just pure enjoyment. Be you ever so much of a novice, what you must do for yourself with other radio sets-The NO-DIAL does for you.

Scrap the log book—forget past radio disappointments. NO-DIAL is the griefless, worryless receiver you have been waiting for. The entire edge of the cover is a permanent, visible station record. Stations once found and recorded always come in at that same point. It's that simple!

The cylindrical NO-DIAL case is of spun aluminum, absolutely shielding it from body capacity. Finished in beautiful brown mahogany crystalline matching the higher Priced loud speakers.

Tube for tube the NO-DIAL recognizes no superior and on test it has outperformed many higher priced sets.

GUARANTEED

The NO-DIAL is guaranteed against defects in workmanship and material. Place your order now with your dealer if you expect to get delivery. The

demand is exceeding all expectations. Accept no complicated substitutes. Literature Sent on Request

THE OHIO STAMPING AND ENGINEERING COMPANY, Dayton, Ohio, U. S. A.



The Standard Radio Text Book

12th EDITION

264 Pages of Radio-500 Illustrations. Size 6 x 9 Inches-DeLuxe Binding, Genuine Gold Stamped-Round Corners.

PRICE \$2.00

Experimenter Publishing Co., Inc. 53 Park Place New York, N. Y

rate Controls: One List Price: \$55

Manufacturer: THE EQUITABLE RADIO CORPORA TION 300 Madison Ave., New York City Trade Name: Claratone Model No. 124 Circuit: Tuned radio frequency Batteries: Storage Batteries: Storage Little Loud Sptaker: Sepa-rate

Controls: Three Liet Price: \$39 Trade Name: Claratone Model No. 124 L. S. Circuit: Tuned radio

frequency Batteries: Storage Antenna: Either Loud Speaker: Built-in Controls: Three List Price: \$60 Trade Name: Profes-

sional Model No. 124-P Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Outdoor or Loud Speaker: Sepa-

Manufacturer:
CHARLES PRESHMAN. INC.
240-248 W. 40th St.
New York City
and 327 Sc. LaSalle St.
Chicago, Ill.
Trade Name: Freshman Masterphece
Model 5-F-2
Circuit: Tuned radio
frequency frequency
Batteries: Either
Antenna: Outdoor or
indoor (no loop)
Loud Speaker: Sepa-

Controls: Three List Price: \$39.50 Trade Name: Fresh-man Masterpiece -Wodels Jr. 5 Groute: Tuned radio frequency Batteries: Either Antenna: Outdoor or indoor (no loop) Loud Speaker: Bultsin Controls: Three

Trade Name: Fresh-man Masterpicce Model S-F-4 Circuit: Tuned radio frequency Batteries: Either Antenna: Outdoor or indoor (no loop) Loud Speaker: Separate Controls: Three List Price: \$49.50 List Price:

Name: Freshman Masterpiece
Concert Model
Circuit: Tuned radio

Concert Moder
Controls
Cont Trade Name: Fresh-man Masterpiece set of Franklin Console Circuit: Tuned radio

List Price \$75

Trade Name: Fresh-man Masterplece Model 5-F-7

Loud Speaker: Sepa- | Circuit: Tuned radio frequency Batteries: Either Antenna: Outdoor or

Trade Name: Fresh-man Masterpice of Model 5-F-6 with table Circuit: Tuned radio frequency Batteries: Either Antenna: Outdoor or indoor (no loop) Loud Speaker: Built-in Controls: Three List Price: \$82.50

Trade Name: Fresh-man Masterpiece Franklin Console Circuit: Tuned radio indoor (no loop) Loud Speaker: Built-in

Manufacturer: GAROD CORP. GAROD CORP.
124 Adams St.,
Newark, N. J.
Trade Name: Garod
Neutrodyne Type V
Circuit: Neutrodyne
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-

Controls: Three List Price: \$195 Trade Name: Garod

Manufacturer:
GOLDEN LEUTZ,
INC.
476 Broadway
New York City
Trade Name: SuperPliodyne 9
Circuit: Tuned radio
frequency Farrand

patent
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Separate
Controls: Two Trade Name: Plio 6 Circuit: Tuned radio

rate Controls: Two List Price: \$60 Trade Name: Univer-sal Plio 6, 35 to 3600 meters Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa Controls: Two List Price: \$125

Manufacturer: A. H.
GREBE & CO., INC.,
113 West 57th St.,
New York, N. Y.
Trade Name: Synchrophase Type MU-1
Circuit: Tuned balanced radio fre-

Trade Name: Sync rophase Type MU Circuit: Tuned he







"LEAD-IN" INSULATOR

Price \$0.60 No. 612

Spaces the "Lead-In" Wire 5 inches out from

PORCELAIN PEDESTAL



No. 611 Price \$0.50 An insulator with a rigid clamp for the lead-in wire. A pedestal for

RKELEW RADIO ACCESSORIES

> Screw Grip Cord Tips

PIN TIP No. 630 Price 5c each

A PBS EYE TIP No. 631 Expose %" of borr wire. Insert and sorrew "B" locking wire to Price The each "

1/200 FORK TIP No. 632

PORK TIPNO. 632

Price 7/2 e each Sorre Cor 7/2 our sushed at 8/1.

A cord tip that requires no solder, no wrapping of the insulation and no tools other than a pen knife and a small screw driver.

CONFIDENCE

HE annual increase in the number of dealers selling Barkelew Accessories expresses the confidence of the Radio Public in our product.

Special attention is called to the No. 605 Antenna Selector Switch and the Screw Grip Cord Tips. Both items were introduced late last year but will have their best run during the present season.

All radio material is packed in paper cartons and well labeled, making ex-

cellent shelf stock. The design is good, materials are carefully selected and workmanship by

skilled mechanics. Prices and discounts are right for a fast moving line. This means a profitable stock.

For full description of each item, see our new Radio Catalog at your dealer. If he hasn't his copy, we have one for him.

The Barkelew Electric Mfg. Co.

Middletown, Ohio, U. S. A.

MINNEAPOLIS, 1017 Damber Ex. NEW YORK, 157 Chambers St. WASHINGTON, D. C., Mills Bldg DENVER, Denham Bldg.

SAN FRANCISCO, 75 Fremont 8 LOS ANGELES, 443 S. San Ped TORONTO, No. 7 Crang Ave.

No. 605

for Radiola III and III-A

FOUR PHONE POST Radiola III and III-A prongs on this po holes in the face




Connects one to four head-sets in Series to any Radio set using telephone jacks.

OF THE PARTY. FOUR No. 628 Price \$0.50

For binding post mounting. Connects one to four head-sets in series to the more common types of brass phone posts.

Price \$0.05 ea. ole is tinned and half er. Heat and insert

Price \$0.01 ea

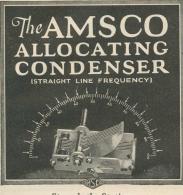

Spreads the Stations Over the Dial-The new

AMSCO Allocating Condenser is the triumphant combination of electrical engineering and mechanical ingenuity. Electrically efficient in un-Each dial degree from 1 to 100 will be found to represent 10 broadcasting kilocycles accurately over the entire scale-"a station for every degree". Mechanically ingenious in correcting the fault of other S. L. F. Condensers-it conserves space! Scientific low-loss construction. Rigidity with light weight.

Made in three capacities—Single or Siamese. Ask your dealer, or write for details of the entire AMSCO Line of engineered radio parts. AMSCO PRODUCTS, INC. Dept. F. Broome and Lafayette Streets, N.Y.C.



ADIO "A" AND "B" BATTERIES give the kind of service that your multi-tube requires. Write for information or ask your deals

The Cleveland Engineering Laboratories Co., 2142 Superior Viaduct, N.W., Cleveland, Ohio

The EAGLE Neutrodyne RECEIVER

is "King of The Air" Write for literature





You must see our new 64-page Catalog before you buy anything in Radio. It's FREE. WRITE RANDOLPH RADIO CORP 159 N. UNION AV. Dept. 2 CHICAGO, ILL

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a yea Experimenter Publishing Co., 53 Park Place, N. Y. C.

Quency Batteries: Dry cell Antenna: Both Loud Speaker: Sepa-Controls: Three Trade Name: Synch-rophase Type MU-1

quency Batteries: Storage Antenna: Both Loud Speaker: Built-in Controls: Three Trade Name: Synch-rophase Type MU-2 Tuned

Manufacturer: GUND-LACH MANHATTAN OPTICAL CO., Rochester, N. Y. Type of Set: Crystal

Batteries: Dry cell Antenna: Both Loud Speaker: Built-in Controls: Three List Price: \$320 less

Manufacturer: THE HALLDORSON CO., 1772 Wilson Ave., Chicago, Ill. Trade Name: Halldor-son Receiver R. F. Circuit: Tuned radio

Manufacturer: W. B. HALLER, 2100 Sarah St., S. S. Pittsburgh, Pa. Trade Name: Hallerio Circuit: Crystal Antenna: Outdoor Controls: Two List Price: \$3

Trade Name: Hallerio 4 Circuit: Crystal Antenna: Outdoor Controls: Two List Price: \$4 Trade Name: Hallerio S Circuit: Crystal Antenna: Outdoor Controls: Two List Price: Complete aerial equipment and phones \$6

Manufacturer: HAL-LOCK & WATSON RADIO CORP., 190-192 Park St., Portland, Ore. Trade Name: "Hako-wat TRS: Circuit: Tuned radio frequency Batteries: Both Antenna: Outdoor Loud Speaker: Sepa-rate

Manufacturer: THE
JEWETT RADIO
PHONOGRGAPH
CO.
Pontiac, Mich.
Trade Name: Jewett
Receiver
Circuit: Fieldless capacity tuned
Batteries: Either

Loud Speaker: Sepa-

Manufacturer:
HONESDALE
RADIO CO.,
c/o The Krantz & Seil Co.,
Honesdale, Pa.
Trade Name: Wayne 4
Circuit: One stage
radio frequency detector, two audio fre-

ist Price: No \$50; No. 2, \$55 Trade Name: Wayne 5 Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

Trade Name: Wayne Antenna: Both Loud Speaker: Sepa-

Manufacturer: 1NDI-ANA MFG, & ELEC-TRIC CO., Marion, Ind. Trade Name: Indiana. Hyperdyne No. 500 Circuit: Tuned radio frequency Batteries: Both-stor-age recomended

Trade Name: Indiana Hyperdyne No. 703 Console Circuit: Tuned radio frequency Batteries: Both—stor-age recommended Antenna: Outdoor or indoor Loud Speaker: Built-in Contro's: Two List Price \$175

Manufacturer:
JOSEPH W. JONES
RADIO MFG. CO.
40-46 W. 45th St.,
New York City
Trade Name: J-65
Circuit: Tuned radio
frequency
Batteries: Dry cell
Antenna: Outdoor
Loud Speaker: Separate Controls: Two List Price: \$65. less

Trade Name: J-80 Circuit: Tuned radio Trade Name: Circuit: Tuned radio frequency Batteries: Dry cell Antenna: Outdoor Loud Speaker: Made to fit upright phono-Controls: Two List Price: \$80.00 Trade Name: J-75 Circuit: Tuned radio

indoor Loud Speaker: Sepa-Controls: Three List Price: \$75 Trade Name: J-85 Circuit: Tuned Batteries: Both



But, What a Difference In the Result —

T HE big loud ticking alarm clock and the small thin noiseless watch are much alike in mechanical principle.

The difference lies in quality of material and workmanship and a scientific refinement in application. Volume in a loud speaker is no longer a distinguishing factor.

The fine point is tone—a clear, natural reproduction of voice or instrumental music attained by the application of the most scientific principles. The Bristol Loud Speaker with its highly developed electromagnetic tone mechanism, non-metallic horns, and long, freely vibrating sound

chambers, gives pure harmony of reception.

Models S and C are equipped with a specially designed diaphragm of broad pitch range. It reproduces not only the low pitched notes but the

high as well.

There are four models, priced at \$15.00 to \$30.00. If not at your dealers, send for Bulletin 3025-S.

A Happy Christmas Suggestion



Size 17 x 10 x 101/4". Beautifully finished mahogany. Full floating wooden horn and

THE BRISTOL COMPANY

Waterbury, Conn.

Bristol AUDIOPHONE Loud Speaker







CRYSTALS. A-1 GET DISTANCE FOR KENTUCKY USER

"A-1 Crystal is sure wonderful. Can hear local reception on Horn-in next room. It is a common occurrence to get KDKA. PITTSBURG (500 miles); WGY, WLS. WTB. WTAM, WOS and others." L. B. D., Covington, Ky.

THE WONDER CRYSTAL

for Reflex or Crystal Set. Sent postpaid, 50c each. 60c C. O. D. CALIFORNIA RADIO MINERALS 904 Oak Grove Avenue, Burlingame, Cal.



ALMOST TOO GOOD TO BE TRUE X-L VARIO DENSERS

MAKE POOR SETS GOOD-GOOD SETS BETTER MODEL N-Capacity range 1.8 to 28 micro-micro-rads, for balance in Roberts two tube, Browning-talks, McMurdo Silvee's Knockout, Neutrodyne and ned radio frequency streudis. Price \$1.00

X-L RADIO LABORATORIES 2426 Lincoln Ave. CH

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year Experimenter Publishing Co., 53 Park Place, N. Y. C.

Loud Speaker: Separate Controls: Three List Price: \$85 Trade Name: JW-90 Circuit: Tuned radio frequency Batteries: Both Loud Speaker: In pho

nograph Controls: Three List Price: \$90 Trade Name: J-195 Circuit: Tuned ra outdoor
Loud Speaker: Built-in
Controls: Three
List Price: \$195 Trade Name: J-175 Circuit: Tuned re frequency
Batteries: Both
Antenna: Both
Loud Speaker: Sepa-Controls: Three List Price: \$175

Trade Name: J-100B Circuit: Tuned radio frequency Batteries: Both Antenna: Both Loud Speaker: Sepa-

Manufacturer: COLIN
B. KENNEDY
CORP.,
2017 Locust St.,
St. Louis, Mo.
Trade Name: Kennedy
Royal Sixteen
Circuit: Balanced
tuned radio fredoor Loud Speaker: Built-in Trade Name: Kennedy Model 15 Circuit: Balanced tuned radio frequency Batteries: Optional Antenna: Both Loud Speaker: Sepa-

rate Controls: Two List Price: \$120 Trade Name: Kennedy Model 20 Circuit: Balanced tuned radio fre-

List Price: \$90

Trade Name: Kennedy Model 6 Circuit: Regenerative detector and three stages of audio am pilification Batteries: Optional Antenna: Outdoor Loud Speaker: Sepa-

Manufacturer:
KLETZEN RADIO
MFG. CO.,
31 Ottawa Avc.,
Grand Rapids, Mich.
Trade Name: KletzenKent Kent Circuit: Armstrong Batteries: Rither Antenna: Outdoor Loud Speaker: None Controls: Two Controls: Two List Price: \$42.50

Trade Name: Kletzen-Wolverine Circuit: Armstrong

Batteries: Either Antenna: Outdoor Loud Speaker: None Controls: Two List Price: \$54.50 Trade Name: Kletzen-Badger
Circuit: Armstrong
Batteries: Storage
Antenna: Outdoor
Loud Speaker: None

Manufacturer: KENMAR RADIO CORPORATION,
Danvers, Mass,
Trade Name: International Babydyne
Model No. 10
Circuit: Regenerative
Butterias. Day cell List Price: \$10

Trade Name: Interna-Trade Name: International Babydyne
Model No. 11
Circuit: Regenerative
Batteries: Dry cell
Antenna: Outdoor
Loud Speaker: None
Controls: One Trade Name: Kenmar Circuit: Tuned radio frequency Batteries: Both Antenna: Both Loud Speaker: Sepo rate Controls: Two List Price: \$85.

Manufacturer:
KODEL RADIO
CORPORATION
507-521 E Pearl St.,
Cincinnati, Ohio
Trade Name: Logodyne
Big 5 Cabinet
Circuit: Tuned radio frequency
Batteries: Either
Antenna: Outdoor preferably
Loud Speaker: None
Controls: Three
List Price: \$90

Trade Name: Logodyne Standard S
Cabinet
Circuit; Tuned radio
frequency
Batteries: Either
Antenna: Either
Loud Spraker: None
Controls: Three
List Price: \$70 Trade Name: Lorodyne frequency
Batteries: Either
Antenna: Either
Loud Speaker: Built-in
Controls: Three

Trade Name: Logo-dync Standard 5 dyne Standard 5 Console Circuit: Tuned radio frequency Batteries: Either Antenna: Either Loud Speaker: Built-in

Trade Name: Kodel Gold Star Circuit: Kodel Batteries: Dry cell Antenna: Either Loud Speaker: Sepa-

Trade Name: Kodel Gold Star Cabinet Circuit: Kodel Batteries: Dry cell Antenna: Both

the New radio battery that is always charged



HERE is something that will be welcomed by all radio fans—a compact "A" storage battery and charger, known as the Exide Radio Power Unit.

This unit is assembled in an attractive metal case, and is kept at all times connected to the ordinary house current as well as to the radio set.

Upon raising a small switch on the end of the unit, the receiving set is ready for use; by throwing it down, the battery is automatically placed on charge. Thus batterycharging, in its most convenient form, practically becomes a part of set operation.

The battery, of course, is an Exide, specially designed for the unit, and has ample capacity for any receiving set—whether that set uses one tube or ten. As there are no moving parts to wear or get out of order, maintenance cost is low.

Finished in a rich mahogany color, the Exide Radio Power Unit is furnished in two sizes—one, for sets using 4-volt tubes; the other, for sets using 6-volt tubes; retailing at \$28 and \$38 respectively—slightly higher west of the Rockies.

There are, in addition, Exide "A" and "B" storage batteries for every requirement, and a rectifier for recharging "B" storage batteries. Inquire of any Exide Dealer or at your favorite radio store.

The Electric Storage Battery Company Philadelphia

Exide Batteries of Canada, Limited, 153 Dufferin Street, Toronto

Exide RADIO POWER UNIT

FOR BETTER RADIO RECEPTION, USE STORAGE BATTERIES



AS LOOKING through plate glass gives a clear eye-picture, so reception from a DYMAC Selecto Five gives a true, clear ear-picture of transmitted sound.

The DYMAC represents something different in set construction -- it's not just a receiver but a fine musical instrument built to render complete and accurate reproduction of tonal values.

The DYMAC is constructed exclusively of time-proved, DYMACmade parts. Cabinet is walnut finish mahogany with ebonized panels.

Its price is \$75. If your dealer can't supply you with a DYMAC Selecto Five promptly, write direct to us. DYMAC Type G Headset (\$5) and Loud Speaker (\$8.50), shown above, will increase your reception enjoyment.

Every DYMAC Product guaranteed one year

Type E Headset, \$3. Vernier Dial, \$1.50 Loud Speaker Unit, \$5. Soldering Set (Standard) \$2.50 Crystal Set (Complete) \$7.50 Sub-panel Socket, 75c.



Electrical Products Mfg. Co. Providence, Rhode Island N. Y. Office: Metropolitan Tower Export Office: Ad. Auriema, Inc., 116 Broad Street, New York City

DYMAC Factory Sales Agents in Principal Distribution Centres

PRIZES FOR YOU

Boys and Young Men-

You can earn dandy prizes and liberal commissions by selling and delivering our popular magazines in your spare time. No experience or money is necessary. We furnish all supplies and tell you just how to start. Write to-day.

E. J. FOLEY, DEPARTMENT RN-11

Experimenter Publishing Company 53 Park Place, New York City

Trade Name: Kodel Circuit: Kodel Batteries: Dry cell Antenna: Either Loud Speaker: Separate Controls: One List Price: \$12

Trade Name: Kodel Gold Star Crystal Antenna: Outdoor List Price: \$60

Trade Name: Logo-dyne Unitrola Uni-versal Phonograph riving set it: Tuned radio Circuit: Tuned radio frequency Batteries: Either Antenna: Either Loud Speaker: Sepa-

rate Controls: Three List Price: \$87.50 Trade Name: Kodel Four-Tube Portable Circuit: Kodel Batteries: Dry cell Antenna: Either Loud Speaker: Bullt-in Controls: Two List Price: \$75

Trade Name: Kodel Two-Tube Portable Circuit: Kodel Batteries: Dry cell Antenna: Both Loud Speaker: Separate Controls: One List Price: \$25

Trade Name: Kodel One-Tube Portable Circuit: Kodel Batteries: Dry cell Antenna: Both Loud Speaker: Separate Controls: One List Price: \$18

Trade Name: Logodyne Panel Assembled Kits
Circuits: Tuned radio
frequency
Batteries: Either
Antenna: Either
Loud Speaker: None
Controls: Three
List Price: \$65, \$50

Manufacturer: LYT-TON INC.. 1120 Lytton Bldg-, Chicago, Ill. Trade Name: Lytton Portable Model 103 Circuit: 1 tuned radio frequency, 2 aperi-odic detector, 2 audio frequency

Batteries: Storage Antenna: Loop Loud Speaker: Built-in Controls: Two List Price: \$195 com-

Trade Name: Lytton
"Compass" Port.
Model 103-A
Circuit: 1 tuned radio
frequency, 2 aperiodic radio frequency
detector, 3 audio fre-

detector, 3 audio fre-quency Batteries: Storage Antenna: Loop Loud Speaker: Built-in Controls: Two List Price: \$225 com-

Trade Name: Lytton Way-O-Dyne No. 201 Circuit: 2 tuned radio frequency complete Batteries: Dry or Batteries: Dry or small storage
Antenna: Outdoor
Loud Speaker: Built-in upright table cabinet
Controls: Two
List Price: \$195, or \$220 complete

Trade Name: Lytton Super-Wav-O-Dyne Model 105 Circuit: 3 tuned radio

frequency combina-Batteries: Dry or storage Antenna: Outdoor Loud Speaker: Sepa-

rate Controls: Two List Price: \$195 less extras, and \$255 in-stalled

Trade Name: Lytton Standard Console Model 100 Circuit: 2 tuned radio frequency Batteries: Dry or stor-Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$195 or \$220 installed

Trade Name: Lytton Concert Console Model 401-A Circuit: 2 tuned radio equency combina Ratteries: Dev or stor-Antenna: Outd Antenna: Outdoor
Loud Speaker: Built-in
Controls: Two
List Price: \$350, or
\$372 complete

Trade Name: Lyttom Duplex No. 99-T Circuit: Duplex reflex crystal detector Batteries: Dry Antenna: Outdoor Loud Speaker: Seps-

Controls: One List Price: \$19.75 less equipment Trade Name: Portable Cabinet Model Circuit: Duplex reflex crystal detector Batteries: Dry Antenna: Wire,

Antenna: Wire, straight antenna Loud Speaker: Separate Controls: One List Price: \$25 less

Trade Name: Lytton Standard Model No. 100 Circuit: Tuned radio frequency
Batteries: Dry
Antenna: Outdoor
Loud Speaker: S

rate Controls: Three List Price: \$75 less ex-tras, \$111 complete, with L. S. tubes

Trade Name: Lytton Wav-O-Dyne Circuit: 2 tuned radio frequency combina tion
Batteries: Both
Antenna: Outdoor
Loud Speaker: Sepa-

rate Controls: Two List Price: \$165 less extras, \$221 installed

Manufacturer: MACK

Manutacturer: MACK

1940 Delancey St.,
Philadelphia, Pa.
Trade Name: The
Mack Sincroflex
(new principle)
Circuit: Sincroflex
Batteries: Both
Antenna: Outdoor
Loud Speaker: Separate
Controls: Two
List Price: \$50

Manufacturer: MAR-TIN RADIO & ELECTRIC CO. 130 West 52nd St., New York City Trade Name: Packard

Circuit: Tuned radio frequency Batteries: Storage

Bremer-Tully Co

Radio drafted Bakelite

so all could listen-in

To make available for everyone, everywhere, the marvel of radio reception, radio engineers required an insulating material possessing a unique combination of properties.

Bakelite alone met the need. It combines high insulation value with strength and light weight. It is easily formed into the many shapes required and will not warp, shrink nor swell. It will not absorb moisture and is unaffected by extremes of heat and cold.

All of these properties and the beautiful color and finish of Bakelite are permanent-unaffected by time, use or climate. So "Radio drafted Bakelite," and today it is used by over 95 per cent of radio set and parts manufacturers.

Make sure that the radio set or parts that you buy are Bakelite insulated, for good insulation is essential to clear reception.

Write for Booklet 24

BAKELITE CORPORATION

247 Park Avenue, New York, N. Y. Chicago Office: 636 West 22nd Street





BAKELITE the special parties of the country of the



THE MATERIAL OF A THOUSAND USES



These new models defy comparison, possessing all the refinements and efficiency of the highest priced sets. The ultimate in selectivity and volume, yet a child of the highest priced sets. can get results. can get results.

The Super-Five with its beautiful mahogany cabinet, rugged bus wiring, handsoldered connections, no unsightly binding posts, and other advanced features,
meets the popular demand for a moderately priced Receiver of highest quality,

o Three Jube Receiver

The only genuine Armstrong circuit 3-Tube Receiver with a dust-proof, fool-proof inside panel protecting the "vitals." Cord connecions to batteries and many other refinements For distance and real tone quality, the equal of many \$100 Sets. See it at your Dealer's.

Other Chelsea Models include the Super-Six. \$60, and the Super-Five with fine Built-in Speaker, \$125.

There's a Chelsea Dealer in nearly every City. If you do not know your Chelsea Dealer, write us for his name and illustrative Circular A.

CHELSEA RADIO COMPANY 179 SPRUCE ST~CHELSEA, MASS

LEARN THE CODE AT HOME WITH OMNIGRAPH



THE OMNIGRAPH MFG. CO., 15 HUDSON STREET, NEW YORK CITY

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year Experimenter Publishing Co., 53 Park Place, N. Y. C.

Antenna: Outdoor Loud Speaker: Sepa-Controls: Three List Price: \$45

MAZ-Manufacturer: M A Z-DA RADIO MFG. CO., 3405 Perkin Ave., Cleveland, Ohio Trade Name: Conson-ello Grand Circuit: Radio fre-Circuit: Read-quency Batteries: Storage Antenna: Loop Loud Speaker: Built-in Controls: Two List Price: \$250

ello Circuit: Radio frequency Batteries: Storage Antenna: Loop Loud Speaker: Sepa-Controls: Two List Price: \$150

Trade Name: Conson-ello Junior Gircuit: Reflex Batteries: Storage Batteries: Storage Antenna: Outdoor Loud Speaker: Separate Controls: T List Price: \$40

Trade Name: Conson-ello Portable Circuit: Radio frequency
Batteries: Dry cell
Antenna: Loop
Loud Speaker: Built-in
Controls: Two
List Price: \$225

anufacturer: METROPOLITAN ELECTRIC CO., METROPOLITAN
ELECTRIC CO.,
811 24th St.,
Des Moines, Iowa
Trade Name: A Meco
Model 2
Circuit: Tuned radio
freguence. Model 2
Circuit: Tuned radi
frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-

rate Controls: Two List Price: \$60 Trade Name: Meco
Model 10
Circuit: Tuned radio
frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-

Controls: Two List Price \$100

Trade Name: Meco Model 6 Semi-Con-Circuit: Tuned radio Circuit: Tuned rause frequency Batteries: Dry cell Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$125

Trade Name: Meco Model 5 Console Circuit: Tuned radio frequency Batteries: Storage Batteries: Storage
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Two
List Price: \$200

Manufacturer: MIN-ERVA RADIO CO., 827 Irving Park Blvd., Chicago, Ill. Trade Name: Minerva Elite Elite
Circuit: Tuned radio
frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Three
List Price: \$125

Trade Name: Minerva Distantia De Luxe

Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

List Price: \$60

Trade Name: Minerva Console Grand Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$255 Trade Name: Minervi

Console Serenade Circuit: Tuned radio Circuit: Tuned radso frequency Batterles: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$200

Manufacturer: MID-WEST RADIO CO., 410 East Eighth St., Cincinnati, Ohio Trade Name: Miraco Ultra Five Circuit: Tuned radio frequency Batteries: Dry cell or Antenna: Outdoor Lond Speaker: Sepa-Controls: Three List Price: \$59.50

Manufacturer: WM. J.
MURDOCK CO.,
347 Washington Ave.,
Chelsca, So. Mass.
Trade Name: Murdock
Neutrodyne No. 100
Circuit: Neutrodyne
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Built-in

Controls: Three List Price: \$100 Trade Name: Murdock Neutrodyne No. 101 Circuit: Neutrodyne Batteries: Storage Antenna: Outdoor

Lond Speaker; Sepa-Controls: Three List Price: \$92.50

Manufacturer: MO-HAWK ELECTRIC CORPORATION 2220 Diversey Blvd., Chicago, Ill. Trade Name: Mohawk Model 100 Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

rate Controls: One List Price: \$100 Trade Name: Mohawk Consolette Model X Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: One List Price: \$175

Trade Name: Mohawl Console Model XII Circuit: Tuned radio

Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Lond Speaker: Built-in Controls: One List Price: \$225.

Trade Name: Mohawk Phonograph Panel Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: One List Price: \$85

Manufacturer: MU-RAD RADIO COR-PORATION Asbury Park, N. J.



DRILL and machine the Goodrich Silvertown Radio Panel with full confidence no special tools are required—it won't break at the edge, crack or chip.

It is made with a full degree of Goodrich skill and rubber knowledge, after long study of radio requirements—the product of a company that has always held quality and service as first considerations.

Science says that rubber is the best material for panels. Then by all means buy the best rubber panel—and that brings you straight to Goodrich Silvertown.

Fifty-five years of rubber manufacturing experience are a guarantee of greatest efficiency in the following products Goodrich has built for radio—

Goodrich V. T. Sockets Spaghetti Tubing
Goodrich Variometers Unwound Battery Mats
Goodrich Radiophone Ear Cushions


The B. F. Goodrich Rubber Company Akron, Ohio

- 1 Easier to drill and machine.
- 2 Better color, lasting luster.
- 3 Lower free sulphur no discoloration.
- 4 Higher softening point no warping.

Silvertown
The Radio Panel Supreme!

POPULAR DEMAND MEETING



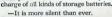

- -It cannot burn out Radiotrons, -It cannot create radio interference.
- -It is ideal for auto batteries-and charges 2 to 6 volt radio "A" batteries, or 24 to 96 volt "B" batteries, in series - all without attachments.



TUNGAR-a registered tradem ark-is found only on the senuine. Look for it on the name plate.

Merchandise Division General Electric Company, Bridgeport, Conn.

GENERAL ELECTRIC



The Tungar is a G-E product developed in the great Research Labora-tories of General Electric.

Two ampere Tungar (East of the Rockies).

\$18.00

Five ampere Tungas

\$28.00

60 cycles-110 yelle

BLUEBIRD RADIO TUBES GUARANTEED to work in Radio Frequency, Neutrodyne, Super Heterodyne and Reflex. WITH BAKELITE BASE

Type 401A \$2.00 Standard Type 409
Type 412

When ordering mention types Shipped Parcel Post C.O.D. BLUEBIRD TUBE CO. cadway Dept.N New York

Special Library of Information

on RADIO PATENTS

and TRADE MARKS

JOHN B. BRADY

Ouray Building Cable address: RADIOPAT

Washington, D. C. Telephone: Main 4806

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year.

Experimenter Publishing Co., 53 Park Place, N. Y. C.

Trade Name: Model A Circuit: Tuned radio Circust: Tuned race frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Separate Controls: One List Price: \$175 Trade Name: Model B Circuit: Tuned radio

Circuit: Tuned rad frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-Controls: One List Price: \$125

Manufacturer: NORTHWESTERN NORTHWESTERN RADIO MFG. CO. 1556 East Taylor St Portland, Oregon Trade Name: Norco (standard cabinet) Circuit: Tuned rad radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-Controls: Three List Price: \$65

Trade Name: Norco
Type D
Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-List Price: \$100 Trade Name: Norco De Luxe Circuit: Tuned radio

Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$150

Manufacturer: OPE-RADIO CORPORA-TION 8 S. Dearborn St., Chicago, Ill. Trade Name: Operadio Portable Circuit: Tuned radio frequency
Batteries: Dry cell
Antenna: Loop or out-Antenna: Loop of door Loud Speaker: Built-in Controls: Two List Price: \$186 com-plete with tube and batteries.

Manufacturer: NU-TONE RADIO CO., INC., S05 Atlas Bldg., Salt Lake City, Utah Trade Name: Nu-Tone N. R. 5-A Circuit: Tuned radio frequency
Batteries: Dry cell
Antenna: Outdoor
Loud Speaker: Sepa-

Controls: Three List Price: \$110

Trade Name: Nu-Tone N. R. De Luxe 25 Circuit: Tuned radio frequency Batteries: Dry cell Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$310

Trade Name: Nu-Tone N. R. 7-A Circuit: Tuned radio Circuit: Tuned radio frequency Batteries: Dry cell Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$180 Trade Name: Nu-Tone N. R. 8-A Circuit: Tuned radio frequency Batteries: Dry cell Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$175 Trade Name: Nu-Tone N. R. 6-A Circuit: Tuned radio frequency
Batteries: Dry cell
Antenna: Outdoor
Loud Speaker: Sepa-List Price: \$145

Manufacturer: PERRY RADIO SUPPLY CO. 218 Washington Blvd., River Forest, Ill. Trade Name: Perasco Keepjie Greuit: Simple single Batteries: Storage or 4ry cell Outdoor dry cell Outdoor Loud Speaker: Separate Controls: One and switch lever List Price: \$25

Trade Name: Perasco PA-III Audio Fre-quency Amplifier Circuit: Two stage au-dio frequency amplifier
Batteries: Storage or
dry cell
Antenna: None
Loud Speaker: Separate Controls: Nor List Price: \$35

Trade Name: Perasco Petit Grand Circuit: Grimes reflex Batteries: Dry cell or storage Antenna: Loop or antenna Loud Speaker: Separate entrols: Two

List Price: \$175 Trade Name: Perasco Type PRD-II Radio Receiver Circuit: Harkness reflex Batteries: Dry cell or storage Antenna: Outdoor Loud Speaker: Sepa-

Loud Spanished

rate
Controls: Two
List Price: \$50 Trade Name: Perasco Two-Stage Type PA-IV Amplifier Circuit: Two stage au-dio frequency ampli-fier

Batteries: Dry cell or storage Antenna: None Loud Speaker: Sepa-Controls: None List Price: \$40

Manufacturer:
PFANSTIEHL
RADIO CO.,
11 So. La Salle St.,
Chicago, Ill.
Trade Name: Model 7
Overtone Receiver
(Pfanstiehl)
Circuit: Pfanstiehl non-oscillating sys-tem tuned radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-

rate Controls: Three List Price: \$140 Trade Name: Pfan-stichl Model 8 Circuit: Pfantichl non-oscillating system of tuned radio trequency

Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-Controls: Two List Price: \$85

after all.

"HOW WELL YOU CAN HEAR" is the only thing that really counts

> Look to your amplifying transformer if your set fails to pass this "quality test"

AS ONE radio fan to another, let's admit a few things.

After all, when a fellow settled back in his easy chair and wants some real entertainment, isn't "How well you can hear" the only real satisfaction in owning a radio set?

Up here at Cambridge we've been making radio transmitting and receiving apparatus since the days when radio was wireless." We've found that the only thing worth

experimenting with is quality-this amplification without distortion. If you would like to test your own or any other set for quality, here's the way to do it. Tune in and at the same time start talking with a

Unless you can understand the voice over the radio with as much ease as that of your friend . . . and without any more effort or concentration . . . then you

are not getting quality . . . you have distortion. For distortion is something more than mere howls and squeals . . . it is anything which prevents you from getting exact, faithful reproduction of the human

> If you find that it requires more attention and effort to hear the radio voice than that of your friend, this is the reason.



distortion. The peculiar characteristics that make your voice recognizable from mine, the sensitive overtones and undertones, have been drowned. The result is a monotone, a droning flatness always difficult to understand.

Yet almost any set can be made to give quality reproduction, if certain precautions are taken.

First of all, look to your amplifying transformers. Here is usually where the trouble lies. Most transformers fail to have the high, flat prolonged amplification curve essential to correctly amplify the sensitive, delicate over and undertones. Hence distortion.

Replace your transformers with Acme Ma-2's which give amplification without distortion and repeat the voice test.

If distortion lies elsewhere, our nearest service station will be glad to aid you in locating and remedying its cause.

Send for this helpful book

THE whole story of distortion and how it can be overcome is carefully and fully explained in a 28-page book, "Amplification without Distortion," the 9th edition of which is just off the presses. Over 200,000 of our friends have already found previous editions helpful. Perhaps this new edition will help you get quality, too. At any rate send for it and see.

Caude Hairns The individuality of the radio it, Acme Apparatus Co. voice has been blurred out by 9th edition of this famous book just

off the press Send for your copy!

ACME ~for amplification

Control releases his or a second	11 - 111
ACME APPARATUS COMPANY, Dep Enclosed find 10c stamps or coin for my out Distortion,"	
Name	
Street	

UNIVERSAL PLIO-6

The Only Set That Tunes All Wave Lengths.

35 To 3600 METERS

R Melbourne 480-WGY 109-2FL Sydney 770-WKAQ San Juan 360-2BL Sydney 350-CPF Amsterdam 2000 Karachi-Bombay-KQP-WGY 1660-6KW Tuinucu 340-Bankok-SP Hilversum 1950-WLW-KDKA 64-KYW-SNO New Castle 400





Six tube, 2 Stages Non-Regenerative Tuned Radio Frequency Amplification, Detector and 3 Stages Distortionless Radio Amplification. Receiving range from 1,000 to 12,000 miles depending upon location, station transmitting, wave-length received and other variable factors. FULL DETAILS NOW AVAILABLE FROM MANUFACTURERS

GOLDEN-LEUTZ INC.

476 BROADWAY : NEW YORK CITY Manufactured under Hopan Patent 1,014,002-Other Patents Pending CABLES "EXPERINFO" NEW YORK



100 AMP, RADIO BATTERY 6 Volt Rubber Case

TWO-YEAR Written Guarantee by THOMAS WITHERBEE Storage Battery Pioneer for 28 Years.

Shipped direct from factory to you. No middlemen's profit—no defays—no grief.

Send No Money

This is an actual 100 amp. Radio Storage Battery honestly built of purest materials by real battery boilders. Solid Rubber Compartment cases—not wood (non-leakable)—will outlast the battery itself. Lead casted carrying handle. Wing binding posts.
Will operate the average 5 tube radio set from three to four hours daily for a month to six weeks. NO DEPOSIT or Advance Payment Required

Simply order—and we will ship by express and you can ex-amine battery at your express office to your heart's content. If you agree will be that it had blacked effect over made—by the you prefer to result with order—deduct 50s. You run no risk as we realize any defective battery during two years. THOMAS BATTERY CORP., 511 West 50th St., New York, N.Y. Trade Name: Pian-stiehl Model 10 Dial Six Overtone Receiver Circuit: Pianstiehl non-oscillating System of tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

Trade Name: Pfan-stiehl Model 8-E Console

Console Circuit: Pfanstiehl non-oscillating system of tmeed radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Bullt-in

Trade Name: Pfan-stichl Single Dial Six Overtone Receiver-Model 10 S-Double Model 10 S—Double Duty Console Greuit: Pfanstiehl mon-oscillating system of timed radio frequency Batteries: Storage Antenna; Outdoor Loud Speaker; Built-in Controls: One List Price: \$200

Trade Name: Planstiehl Single Dial Six Overtone Receiver— Model 10-C—Console Complete Circuit: Planstiehl non-oscillating system of tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: One

PHOENIX RADIO

114 East 25th St., New York, N. Y. rade Name: Ultra-New York, N. Y.
Trade Name: Ultradyne Model L3
Circuit: Tuned radio
frequency
Batteries: Storage
Antenna: Indoor or
Outdoor Outdoor oud Speaker: Built-in List Price \$200

Manufacturer: PORTS MANUFACTURING CO., 3305 E. Belmont Ave., Fresno, Calif. Trade Name: Perkwell

Super 5 Circuit: Tuned radio frequency Batteries: Storage or dry cell Antenna: Outdoor Loud Speaker: Sepa-

rate Controls: Three List Price: \$40 Trade Name: Pormco

Radio Circuit: Tuned radio frequency Batteries: Dry cell or storage Antenna: Outdoor Loud Speaker: Sepa-Controls: Three List Price: \$65

Manufacturer: THE

Manufacturer: THE
PREMIER RADIO
CORPORATION
Defiance, Ohio
Trade Name: Premier
8-A Console
Circuit: Reflex
Batteries: Storage
Antenna: Outdoor or loop Loud Speaker: Built-in Controls: Two List Price: \$350

Trade Name: Premier 7-A Console Circuit: Reflex

Batteries: Storage Antenna: Outdoor or loop Loud Speaker: Built-in Controls: Two Controls: Two List Price: \$290

Trade Name: Premier 7-B Table Type Circuit: Reflex Batteries: Storage Antenna: Outdoor or

Loud Speaker: Sepa-Controls: Two List Price: \$160 Trade Name: Prei 6-B Table Type Circuit: Tuned r frequency Batteries: Storage

Batteries: Storage
Antenna: Outdoor
Loud Speaer: Separate
Controls: Three
List Price: \$100

PRIESS RADIO

CORP.,
633 Broadway,
New York City
Tade Name: Priess
Straight Eight Model
P. R. 4
Circuit: Priess
Batteries: Storage
Antenna: Loop
Loud Speaker: Separate Controls: Two List Price: \$165

Trade Name: Priess Straight Eight Model P. R. 6 Circuit: Priess Batteries: Storage Antenna: Loop Loud Speaker: Built-in Controls: Two List Price: \$275

Manufacturer: RADIO TION OF AMERICA
Bay City, Mich.
Trade Name: "Simpliform" No. 10 Phono-Radio Combination ircuit: Transformed Circuit: Transformes radio frequency Batteries: Dry cell or Antenna: Outdoor Loud Speaker: Built-in Controls: Two

Trade Name: form" No. 11 Phono Radio Combination Circuit: Transformed radio frequency Batteries: Dry cell or cell or Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$200

Trade Name: "Simpli-form" No. 12 Phono-Radio Combination Circuit: Transformed radio frequency Batteries: Dry cell or Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$230

Trade Name: "Simpli-form" 5T-1 Table Model Circuit: Compensated tuned radio frequency Batteries: Dry cell or

storage
storage
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Three
List Price: \$85

Trade Name: "Simpli-form" 5T-14 Console Type of Circuit: Com-pensated tuned radio pensated tuned radio frequency Batteries: Dry cell or storage
Antenna: Outdoor
Loud Speaker: Built-in
Tuning Controls: Three
List Price: \$125

Preliminary Announcement

ALL-AMERICAN RADIO RECEIVERS



ALL-AMERICAN standard; but E. N. Rauland, pioneer in radio and severest critic of ALL-AMERICAN products, shook his head and said "Wait."

And he was wise. If this achievement had not come until next year, it would still have been worth waiting

for. But it is on view at the shows.

Last year it was our pleasure to add
to the family of the "World's

Largest Selling Transformers" an audio
amplifying instrument embodying features hitherto considered impractical.

ALL-AMERICAN Receivers embody, necessarily, all the genuine improvements of the past year in radio receptance of the past year in radio receptance of the ALL-AMERICAN Extension Shortnories. Multistage control through two your disks, without garer, the elimination of "body capacity," the extreme of beauty in tone through Reuland-Lyric, and of distance, power and selectivity through ALL-AMERICAN Straight-Lime Frequency TUSNOS—these are combined more in external appointments.

And yet, All-American Receivers are not high-priced. This is due to the fact that, although only a small number will be produced this fall, the price has been set on the basis of next year's extensive production.

Dealers who realize the significance, for future growth, of handling merchandise of this character, are invited to write their jobbers or the factory for full information, or to visit our booth at the Chicago or St. Loui: radio shows.



ALL-AMERICAN RADIO CORPORATION, E. N. Rauland, Pres., 4207 Belmont Ave., Chicago, U. S. A.

ALL-AMERICAN
Pioneers in the Radio Industry



Mexican Crystals The BEST, bar none. For S Crystal sets, "Silver Ga-S lena." For Reflex sets, 40c Each, 3 for \$1 Special for DePorest, 50c FREE Dealers, write. H.D.HATFIELD & 80N 1761 Vermont Av Hollywood, Calif circuit free with 3 crystals at \$1



W. C. BRAUN COMPANY 34-165, Clinton

Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 65c. Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, N. Y

Trade Name: "Simpli-form" 5T-15 Console Type of Circuit: Com-pensated tuned radio frequency Batteries: Dry cell or Batteries storage Storage Outdoor Loud Speaker: Built-in Tuning Controls: Three List Price: \$150

Trade Name: "Simpli-form" No. 100 Table Type of Circuit: Trans-formed radio frequency Batteries: Dry cell or Batteries: Dry storage Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Three List Price: \$75

Trade Name: "Simpli-form" No. 275 Con-Type of Circuit: Trans-formed radio fre quency Batteries: Dry cell or Batteries: 20., storage Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Three List Price: \$110

Trade Name: "Simpli-form" No. 110 Table form" No. 110 Tab Model Type of Circuit: Tran formed radio fr Batteries: Dry cell or storage Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Two List Price: \$80

Trade Name: "Simpli-form" No. 375 Con-sole Type of Circuit: Tran formed radio fr Batteries: Dry cell or storage Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Two List Price: \$160

Trade Name: "Simpli-form" 5T-215 Com-Type of Circuit: Com-pensated tuned R.F. Batteries: Dry cell or Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Three List Price: \$250

Manufacturer: RAVEN RADIO COMPANY, Cobleskill, N. Y. Trade Name: Raven 5-Type of Circuit: Tuned radio frequency Batteries; Dry cell or storage Antenna: Outdoor Loud Speaker: Sepa-Tuning Controls: Three List Price: \$70 Trade Name: Raven Console Model Type of Circuit: Tuned radio frequency Batteries; Dry cell or

Batteries: Dry
storage
Antenna: Outdoor
Loud Spraker: Built-in
Tuning Controls: Three
List Price: \$170 Trade Name: Raven

Type of Circuit: Tuned radio frequency radio frequency Batteries: Dry cell or Batteries: Day
storage
Antenna: Outdoor
Loud Speaker: Built-in
Tuning Controls: Three
List Price: \$90

rade Name: Raven Superheterodyne set unwired Type of Circuit: -

Batteries: Dry cell or storage Antenna: Loop Loud Speaker: Sapa-Tuning Controls: Two List Price: \$125 Manufacturer: RESAS. INC.

INC.
112 Chambers St..
New York City
Trade Name: Resas
Tone-A-Dyne Com-Type of Circuit: Tuned Type of Circuit: Tuned radio frequency Batteries: Either (stor-age preferred) Antenna: Outdoor or Loud Speaker: Sepa-Tuning Controls: Three List Price: \$60 Trade Name: Tone-A-Dyne
Type of Circuit: Tuned
radio frequency
Batteries: Rither (storage preferred)
Antenna: Outdoor or

indoor Loud Speaker: None Tuning Controls: List Price: \$78 Trade Name: Tone-A-Trade Name: Tone-A-Dyne De Luxe Circuit: Tuned radio frequency Batteries: Either (stot-age preferred) Antenna: Outdoor or indoor indoor Loud Speaker: None Tuning Controls: List Price: \$85

Manufacturer: SHER MAN RADIO MANU-FACTURING CORP. 112 Trinity Place, New York City Trade Name: Clearfield De Luxe Type of Circuit: Tuned amplification Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

Tuning Controls: Three List Price: \$115 Manufacturer: SIM-PLEX RADIO COM-PANY. Rector and Main Sts., Manayunk, Philadel-phia, Pa. Trade Name: "Sim-plex" Type SR5 Type of Circuit: Tuned Batteries: Storag Antenna: Outdoo Loud Speaker:

Tuning Controls: Three List Price: \$57 Trade Name: "Sim-plex" Type Sr.5 De Luxe Type of Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-Tuning Controls: Three List Price: \$65

Trade Name: "Sim-plex" Type SR-8 Sloping Front Type of Circuit: Tuned radio frequency radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-Tuning Controls: Three List Price: \$65

SLEEPER RADIO CORP.,
438 Washington Ave.,
Long Island City,
N. Y.
Trade Name: Sleeper
Monotrat (54)
Type of Circuit: Grimes
Universe Duplex



Good Radio Requires Good Material

T is just as impossible to build dependable radio with poor material as it is to build a good automobile or a good locomotive that way.

Formica panels, base panels, winding tubes, insulating bushings and washers have the qualities that make lasting durability possible.

They have electrical qualities that are more than sufficient for any need-and they combine with them equally essential mechanical strength, resistance to warping, and cold flowing. They never distort in use so that instruments are displaced.

The Formica finish is unequalled in richness and gloss. And that finish is one of the most permanent in the world. It does not discolor, grow dull, check or craze. No ordinary varnish or lacquer can equal it.

These are all things that count. They make or break the satisfaction a radio set will give. And that is why for years the great majority of radio manufacturers have used Formica.

VERI-CHROME PANELS

By the purchase of a controlling interest in the Veri-Chrome laboratories, the financial and production resources of the Formica Insulation Company have been placed behind this remarkable new process for decorating radio panels. Elaborate decorations can be produced much more rapidly and more economically than by engraving. Decorations designed by the leading American artists are offered. Tuning scales may be marked directly on the panel eliminating the standard dial and substituting pointers instead. The reduction in cost is large. Write for prices on complete panels finished in this way in quantity.

Dealers: Formica panels in individual envelopes furnish a line on which dealers make a very satisfactory profit.

THE FORMICA INSULATION COMPANY 4618 Spring Grove Avenue, Cincinnati, Ohio

- 1 Formica is used by nearly all the leading set makers and har for years been used by more set makers than any other material
- 2 Formica is unaffected by weather and time it lasts forever.
- Formica in appearance is the finest of all panel materials and always remains so.
- 4 Formica's electrical qualities of every kind far exceed any
- 5 Formica has high mechanical strength and will not break in use.
- 6 Formics will not sag from heat or cold flow under pressure. It retains its dimensions. Everything you fasten to it stays tight and precisely where you put it. 7 Formica panels are sold in neat craft paper envelopes which assure you that you are getting the genuine.
- 8 Formica is one of the most widely approved materials in radio.

CALES OFFICES

50 Church Street	New York, N. Y.	1026 Second Avenue	Minneapolis, Minn,
9 South Clinton Street	Chicago, Ill.	725 Bulletin Bldg	Philadelphia, Pa.
516 Cayton Bldg	Cleveland, Ohio	708 Title Building	Baltimore, Md.
327 Cutler Bldg.	Rochester, N. Y.	585 Mission Street	San Francisco, Cal.
422 First Avenue	Pittsburg, Pa.	419 Ohio Building	Toledo, Ohio
6 Beacon Street	Boston, Mass.	309 Plymouth Bldg.	New Haven, Conn.
Ef. Calla Obiana	Habana Cuba	Whitney Central Bldg	New Orleans, La.



Hear the Formica Orches traover WLW every Tuesday evening from 9 to 10 Central Standard Time.

RAYTHEON

The new tube that perfects the B-battery eliminator

P URE, resonant, clear tone—reserve power—freedom from worries of all kinds—aren't these the things you have always looked for in a B-eliminator? The things you have never been able to realize?

Here, then, is a tube that makes all these possible—that has immeasurably long life, uniform quality, ample power to run a 10-tube set. The RAYTHEON Rectifier is the result of prolonged experimentation and scientific research. It is the last word in the perfection of the B-battery eliminator, developed by an organization that is in the forefront of the engineering field, and endorsed by radio editors and leading manufacturers

You can buy specially designed B-battery eliminators equipped with the RAYTHEON Rectifier at your dealers. RAYTHEON Rectifying Tubes and specially designed parts for use in building your own B-eliminator are also obtainable from your retailer. Price of tube, \$6.

Look for the RAYTHEON name. It is the mark of quality and your assurance of satisfaction.



Reserve Pomer

Uninterrupted Service

AMERICAN APPLIANCE CO

Cambridge, Massachusetts

Organization Integrity-Honest Merchandising-Truthful Advertising Scientific Research-Sound Engineering-Basic Patents-Substantial Backing

Any Radio Map or Log a Month Old Is

Long Life

Replacements

Unnecessary

Out Of Date Unless It Has a Monthly Supplemental Service THE AIR-LINE RADIO MAP AND LOG

With Patented Movable Mile Scale hasthis Service

AN INDIVIDUAL LOG FOR EVERY STATION If you do not find this the most complete servicable RADIO MAP and LOG published, we will refund your money, PRICE SO CENTS

At your dealers, or sent postpaid. Dealers and Jobbers Write at once

MULTIVIDER CO. St. John & Askew.



keeps prices low. Handsome, convented LINCOLN 4-POINT TAPPED LOOP ductance of the loop. Exceptionally I LINCOLN CENTER-TAPPED LOOP LINCOLN RADIO CORPORATION, 224 N. Wells St., Chicago

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

Batteries: Storage Antenna: Outside Loud Speaker: Sepa-Trade Name: Scout (57)
Type of Circuit: Radio frequency (Juneo)
Batteries: Storage
Antenna: Antenna
Loud Speaker: Sepa-

rate Tuning Controls: Two List Price: \$75 Trade Name: Serena-der (58) Type of Circuit: Juneo Type of Circus,
radio frequency
Batteries: Storage
Antenna: Antenna
Loud Speaker: Built-in
Tuning Controls: Two
List Price; \$100

Trade Name: Super Symphonetic (59) Type of Circuit: Juneo radio frequency. Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Tuning Controls: Two List Price: \$150

Manufacturer: SPLIT-DORF ELECTRICAL COMPANY, 392 High St., Newark, N. J. Trade Name: Splitdorf Sonata Type of Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside antenna Loud Speakers: Sepa-Tuning Controls: Two List Price: \$60 Trade Name: Splitdori Polonaise
Type of Circuit: Tuned
radio frequency
Batteries: Storage radio frequency Batteries: Storage Antenna: Both Loud Speaker: Sepa-Tuning Controls: Three List Price: \$75 Trade Name: Splitdorf

Nocturne Type of Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Both
Loud Speaker: Built-in Tuning Controls: Three List Price: \$150 Trade Name: Solitdorf

Geisha Type of Circuit: Tuned radio frequency Batteries: Storage Antenna: Both Loud Speaker: Sepa-Tuning Controls: Three List Price: \$110 Trade Name: Splitdorf Rhapsody Type of Circuit: Tuned

radio frequency
Batteries: Storage
Antenna: Both
Loud Speaker: Built-in
speaker and compartment for "B" batteries
Turies " teries Tuning Controls: Three List Price: 3410

Trade Name: Splitdorf Mikado
Type of Circuit: Tuned
radio frequency
Batteries: Storage
Antenna: Both
Loud Speaker: Built-in
speaker and compartment for "B" bat-Tuning Controls: Three

Manufacturer: STANDARD RADIO

Trade Name: Standardyne Type of Circuit: Tuned radio frequency Batteries: Storage bat-Antenna: Outside or in-side antenna (not on loop) Loud Speaker: Sena Tuning Controls: Three List Price: \$60

Trade Name: ardyne-Console Model Type of Circuit: Tuned radio frequency Batteries: Storage bat-Antenna: Ontside or inside antenna (not on loop) oud Speaker: Built-in

SONORA PHONO

URAPH CO., INC., 279 Broadway. New York City Trade Name: Sonora Model C Receiver Type of Circuit: Tuned radio frequency Batteries: Storage Antenna: Outside an Loud Speaker: Sepa rate Tuning Controls: Three List Price: \$90

Trade Name: Sonora Model C Highboy Type of Circuit: Tuned radio freewart radio frequency
Batteries: Storage
Antenna: Outside an Loud Speaker: Built-in Tuning Controls: Three List Price: \$90 Manufactures.

STEINITE LABORA-TORIES, Atchinson, Kansas Trade Name: Steinite Type of circuit: Crys-tal tal
Batteries: None
Antenna: Outside
Loud Speaker: None
Tuning Control: One
List Price \$6 Trade Name: Steinite Type of Circiut: Crystal Batteries: Storage Antenna: Outside Loud Speaker: Sepa-Tuning Controls: Three List Price: \$50 and \$60

Manufacturer Manufacturer:
SPIELMAN ELECTRIC CO.,
311 West 59th St.,
New York City, N. Y.
Trade Name: Air Pilot
Batteries: Storage
Antenna: Both
Loud Speaker: Sepa-Trade Controls: Three List Price: \$60

Trade Name: Comet Batteries: Storage Antenna: Both Loud Speaker: Sepa-

Tuning Controls: Three

Manufacturer:
SUN MANUFACTURING CO.,
26th and Maple Sta.,
Louisville, Ky.
Trade Name: Sun
Radio,
Type of Circuit: Tuned
radio frequency reflexed Batteries: Storage Antenna: Outside Loud Speaker: Sepa-

Sun

Tuning Controls: Three List Price: \$75 Trade Name: Radio DeLawe



RADIO 'RITHMETIC

"A" batteries + "B" batteries + RECTIGON = clear radio reception

HARK back to your old arithmetic and those busy boys "A" and "B". They were forever doing "a certain pieceofwork". They 're still inseparable. Nowadays "A" and "B" storage batteries are busy with clear radio reception.

"A" still depends upon "B" and vice versa. Both need to be kept fully alive to do their best work. Both can be kept alive easily and dependably through the use of ome [did you know that?] compact, little device—

The



Westinghouse Rectigon Battery Charge





LL who hear the Amplion are won by its wonderful clearness and deep, full, life-like tone-qualities which have made it the world's largest-selling loud speaker.

The explanation is that The Amplion was evolved by the actual originators and oldest producers of loud speakers.* Long before radio attained general popularity, Graham loud speakers had been adopted-because of outstanding excellence-by the exacting British Admiralty and naval experts of other nations. The Amplion, introduced in 1920, was based on thirty years of successful experience.

Hear The Amplion in comparison with any or all other radio reproducers. Let your ears tell you why it is so widely known as "The world's finest loud speaker." Amplion Loud Speakers, \$12 up. Phonograph units in two sizes. Interesting literature and dealer's address on request.

THE AMPLION CORPORATION OF AMERICA Executive Offices: Suite S, 280 Madison Ave., New York City Canadian Distributors: Burndept of Canada, Ltd., Toronto

The World's Standard Loud Speaker



Potter CONDENSERS

-Prevent "B" voltage fluctuation -Allow undistorted amplification Make possible full bass tones -Improve reception with "B" Supply Units,

Made in 1, 1, 1, 1, 2, 3 and 4 Microfarad sizes At Your Dealer's

POTTER MANUFACTURING COMPANY North Chicago, Illinois

rivaled for clearness of tone, sleed The Amplion. Ask to hear simproved new Amplion Dragon, AR-19, illustrated above.

The supremacy of The recognition and leadership in sales. Partial list of nations in which Amplions are ruling favorites among music-lovers UNITED STATES DOMINION OF CANADA ENGLAND

SCOTLAND VIRELAND NORWAY SW DENMARK WALES SWEDEN HOLLAND BELGIUM FRANCE SPAIN

RANCE SPAIN SWITZERLAND ITALY JAPA SOUTH AFRICA NEW ZEALAND AUSTRALIA

Type of Circuit: Tuned Batteries: Either Antenna: Ossside Loud Speaker:

Tuning Controls: Three List Price: \$100 Trade Name: Sun Radio Type of Circuit: Tuned radio frequency flexed Satteries: Either Batteries: Either Antenna: Outside Loud Speaker: Both Tuning Controls: Three List Price: \$140

Trade Name: Sun Radio & Phonograph Type of Circuit: Tuned radio frequency re-flexed flexed Batteries: Either Antenna: Outside Loud Speaker: Phono-graph and radio com-

Trade Name: Super-Sun Type of Circuit: Radio frequency and special (our own)
Batteries: Dry cells
Antenna: None
Loud Speaker: Sepa-Tuning Controls: Two List Price: \$125

Tuning Controls: Three List Price: \$237.50

Manufacturer: SUN-BEAM RADIO CORP... 350 West 31st St., New York City Trade Name: Akradyne Type of Circuit: Tuned radio frequency, 2 stage each of audio amplification

amplification Batteries: Storage outdoor. Loud Speaker: Built-in Tuning Controls: Two List Price: \$175

Trade Name: Akradyne
Type of Circuit: Tuned
radio frequency, 2
stage cach of audio
amplification
Batteries: Storage outdoor. Loud Speaker: Built-in Tuning Controls: Two List Price: \$215

Trade Name: Akra dyne
Type of Circuit: Three
stage each of audio
amplification and
tuned radio frequency

Loud Speaker: Built-in Tuning Controls: Two List Price: \$475 Trade Name: Akra-Type of Circuit: Tuned

radio frequency, 2 stage each of audio amplification amplification
Batteries: Storage
Antenna: Indoor or
outdoor.
Loud Speaker: Built-in
Tuning Controls: Two
List Price: \$975

Trade Name: Akra-Type of Circuit: Tuned

radio frequency, 2 stage each of audio amplification amplification Batteries: Storage Antenna: Indoor outdoor. Loud Speaker: Sepa-Tuning Controls: Thre

Trade Name: Akra-Type of Circuit: Tuned radio frequency, 2 stage each of audio amplification Batteries: Storage Antenna: Indoor or outdoor. Tuning Controls: Two List Price: \$90 Trade Name: Akra. Type of Circuit: Tuned

radio frequency, 2 stage each of audio amplification atteries: Storage attenna: Indoor outdoor. Loud Speaker: Built-in Tuning Controls: Two List Price: \$110 Trade Name: Akra-Type of Circuit: Tuned radio frequency, 2 stage cach of audio amplification Batteries: Storage Antenna: Indoor or outdoor. Loud Speaker: Built-in Tuning Controls: Two List Price: \$150 Trade Name: Akra-Type of Circuit: Tuned

Type of Circuit: Tumed radio frequency, 3 stage each of audio amplification Batteries: Storage Antenna: Both Loud Speaker: Built-in Tuning Control: Two List Price: \$1,475 Trade Name: Pink-a-Tone Type of Circuit: Tuned

Batteries: Dry cell Antenna: Outdoor Loud Speaker: Sepa-Tuning Controls: Two List Price: \$18.50 Trade Name: Pink-a-Tone Type of Circuit: Tuned

flexed Batteries: Dry cell Antenna: Outdoor Loud Speaker: Sepa-rate Tuning Controls: Two List Price: \$28.50

Trade Name: Pink-a-Tone Type of Circuit: Tuned radio frequency reradio frequency re-flexed Batteries: Dry cell Antenna: Outside Loud Speaker: Sepa-Tuning Controls: Three List Price: \$34.50

Manufacturer:
TELETONE CORP.
449 W. 42nd St.,
New York City
Trade Name: Teletone
R.F. Type of Circuit: Radio Type of frequency
Batteries: Either
Antenna: Outsic indoor (no loc Loud Speaker: Tuning Controls: Thre List Price: \$75 Trade Name: Teletone Tudor Type of Circuit: Radio

Batteries: Either Antenna: Indoo Antenna: Indoor or outdoor (no loop) Loud Speaker: Built-in Tuning Controls: Two List Price: \$200 Trade Name: Teletone Panel Type of Circuit: Radio

frequency
Batteries: Either
Antenna: Indoor
outdoor (no loop)

Insure your copy reaching you each month. Subscribe to Radio New \$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C. Subscribe to Radio News-



And now the final radio set

-the Deresnadyne operating from the light socket

A complete receiver employing no batteries

FOR those who want a radio receiver second to none, both in convenience and performance, the Deresnadyne will settle the question of which set to buy. It is a complete set requiring no added equipment. A set installed by merely plugging in the light socket. A set requiring no attention and always ready to operate at full power. A set which does not choose between tone quality and volume, nor between selectivity and distance, but combines all four qualities of a superlative radio receiver.

The Deresnadyne employs no batteries. It is equipped with a power unit which furnishes all necessary current from the light socket. This unit is an adaptation of one of the most successful power devices in radio. It is entirely noiseless—a permanent piece of equipment, with no bulbs and nothing to adjust, wear out, replace, recharge or renew. It improves reception for it performs at all times exactly as do batteries when these are new and fully charged.

The Deresnadyne includes all accessories except tubes. Its compactness has made possible radical improvements in appearance. The power unit and speaker are included in the cubiner. There is nothing more to buy and no further expense other than household current (110-120 AC 60 oy-120-about 1/10p per hour of actual use. The only connection you need make is the ground wire. Price \$5.65. See it at your dealer's. See also the Deresnadyne II at \$1.25 and III at \$1.85 receivers employing the Deresnadyne circuit but requiring the usual battery and aerial equipment.

Andrews 1
Deresnadyne
Radio Receiving Set





BRANSTON HETROLA



Model R-46 complete with handsome walnut cabinet ready for tubes and batter-ics—\$75.00



Model R-47. Table console type in walnut with self-con-tained loud speaker and bat-tery compartment—\$120.00

The latest development in radio—the HETORUS Coil—illustrated above is now offered to you completely built up in beautiful sets designed for the utmost satisfaction in radio reception.

Two dials only, making for easy tuning y the most inexperienced—all wiring slow the base panel. Increased selectivity, improved tone

and volume, more compact design, and A MARKED DECREASE IN STATIC are

some of the main advantages of this new The HETORUS Coil has no pick-up quality of its own, affording a new and better means of separating closely allocated stations.

It is sold singly at \$2.50 or in a matched set of three at \$7.50. Three coils and three straight line frequency condensers \$15.00. Complete set, wired but without cabinet shown below, \$55.00

Whether you build, rebuild, or buy—use HETORUS coils for best possible results in tuned radio frequency reception. Write at once for full information on this outstanding sensation.

CHAS. A. BRANSTON, Inc.



You Radio Men Need This Lathe! Boice-Crane Utility Lathe

MONEY BACK GUARANTEE W. B. & J. E. Boice, Blick Toledo, O. 2304 Telegraph Avenue : Oakland, Calif.



Aeriola X Crystal Set

Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 65c.

Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, New York

Loud Speaker: Phono graph speaker used. Tuning Controls: Two List Price: \$90

Manufacturer: THERMIODYNE RADIO CORP. 1819 Broadway, New York City Trade Name: Thermio-dyne TF6 Type of Circuit: Ther-Batteries: Either Antenna: Indoor or

Loud Speaker: Sepa-Tuning Control: One master control: One master control List Price: \$150, Cen-tral & Eastern States; \$160, Rocky Mt. & Pacific Coast States Trade Name: Thermio-

dyne TF5
Type of Circuit: Thermiodyne
Batteries: Either
Antenna: Outdoor antenna Loud Speaker: Sepa-Tuning Control: One master control List Price: \$100, Cen-tral & Eastern States; \$110, Rocky Mt. & Pacific Coast

Trade Name: Thermio-dyne CTF6 Type of Circuit: Ther-Batteries: Either outdoor
Loud Speaker: Built-in
Tuning Control: One
master control
List Price: \$275, Central & Eastern States;
\$290, Rocky Mt. &
Pacific Coast States

danufacturer: R. E. THOMPSON MFG. 30 Church St., New York City, N. Y. Trade Name: Thomp-Type of Circuit: Neu-trodyne Batteries: Either Antenna: Outdoor Loud Speaker: Sepa-

Tuning Controls: Three List Price: \$180 Trade Name: Thomp-Type of Circuit: Neu-trodyne Batteries: Storage Antenna: Outdoor Antenna: Outdoor-Loud Speaker: Sepa-Tuning Controls: Three List Price: \$145

Trade Name: Thomp-Type of Circuit: Neu-trodyne Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-

Tuning Controls: Three List Price: \$125 Trade Name: Thomp-

Type of Circuit: Neu-trodyne Batteries: Either Antenna: Antenna Loud Speaker: Built-in Tuning Control: One List Price: \$360

Trade Name: Thomp-Type of Circuit: Neu-trodyne Batteries: Dry cell Antenna: Outdoor Loud Speaker: Built-in Tuning Control: One Loud Speaker: Built-in Tuning Control: One List Price: \$150

Trade Name: Thomp-Type of Circuit: Neutrodyne Batteries: Storage Outdoo Antenna: Outdoor Loud Speaker: Sepa-Tuning Controls: Three List Price: \$125

TRESCO-ATCHIN-Atchinson, Kans.
Trade Name: Steinite
Type of Circuit: Arm
strong regenerative strong regeneral Batteries: Both Antenna: Outside Loud Speaker: Sepa Tuning Control: One List Price: \$6

Trade Name: Steinit Type of Circuit: Arm strong regenerative Batteries: Both Antenna: Outsi-Loud Speaker: Tuning Control: One List Price: \$12.50

Manufacturer: WAL-BERT MFG, CO. 925-41 Wrightwood Ave.,

Ave.,
Chicago, Ill.
Trade Name: Isofarad
Type of Circuit: Balanced capacity bridge
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Sepa-Tuning Controls: Three List Price: \$200 Trade Name: Isofarad,

Jr.
Type of Circuit: Bal-anced capacity bridge Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-Tuning Controls: Three List Price: \$150

Manufacturer:
WELL'S RADIO
MFG. CO.
2708-12 North Ashland
Ave. Chicago, Ill.
Trade Name: Wells
Bear Cat Model V
Gircuit: Radio frequency
Antenna: Outside
Loud Speaker: Built-in
Controls: Three Controls: Three List Price: \$110.00

Trade Name: Wells
Bear Cat Model 50
Circuit: Radio frequency
Batteries: Dry cell
Antenna: Outside Antenna: Outside Loud Speaker: Separate

Trade Name: Wells
Bear Cat Portable
Mouel 500 Model 500 Circuit: Radio frequency Batteries: Dry cell Antenna: Outside Loud Speaker: Built-in Controls: Three List Price: \$110.00

Manufacturer: WEST-ERN COIL & ELECTRICAL CO., 300 5th St., Racine, Trade Name: Radio-Circuit: Tuned radio frequency Batteries: Storage Loud Speaker: Built-in Controls: Three Controls: Three List Price: \$185.00

Trade Name: Radio dyne Circuit: Tuned radio frequency Radiodyne frequency Radiod Batteries: Storage



are dozens of items, each designed especially for some place in your circuit. Our attractive booklet, "Helpful Hints for Radio Fans," describes them all, with diagrams and illustrations. Every

Send for Free Illustrated Booklet

set builder should have this booklet.





NOTHING but the latest—and the best, too! You'll find the We save you money, too! Our enormous buying power permits us to pay spot cash and get rock-bottom best kits for all the latest hook-ups prices. This new catalog illustrates fully described and illustrated in our

Send for your FREE copy, today!

new 96 page "Super" Radio Catalog.

509 SOUTH STATE STREET

CHICAGO SALVAGE STOCK STORES

Dept. RN. CHICAGO, U.S.A.

NA-ALD =

Na-ald DeLuxe Sockets are the only ones Na-aid Delaine Sockets are the only ones with these three exclusive features—lowest loss, lowest capacity and positive side-scraping contact. Send for booklet and laboratory test. Alden Manufacturing Company, Dept. K11, Springfield, Mass.

WADE SQUARE LAW

CONDENSER AND DIAL sizes, complete with 4-inch ve wave .003125 mfd. Radio Frequency, .00025 mfd. Heterodynes .0005 mfd. At your dealers, otherwise send pure price and you will be supplied party WADE MFG. CO., Inc., 1819-A Breadway, N. Y. City

for Improved Reception-D X INSTRUMENT CO.

and describes a complete line of fully

guaranteed parts and accessories



"Lighting Fixtures" READY TO HANG
(Direct from Manufacturer)
supleteely wired including glassware
Send for new Catalogus No. 27
(Just reduced prices)

Special Proposition to Dealers
ERIE FIXTURE SUPPLY Co.
STATION R ERIE PA

Antenna: Inside or outside Loud Speaker: Separate Controls: Two List Price: \$3960 Trade Name: Radiodyne Circuit: Tuned radio

Circuit: 1 u... frequency Batteries: Dry cell Antenna: Outside Loud Speaker: Separate Controls: Three List Prcie: \$110.00 Trade Name: Radio-

dyne Circuit: Tuned radio frequency
Batteries: Dry cell
Antenna: Outdoor
Loud Speaker: Built-in Controls: Three List Price: \$210.00 Trade Name: Radiodyne Circuit: Tuned radio

Circuit: Tunet rans-frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Separate Controls: Three List Price: \$65.09 Trade Name: Radio-

dyne Circuit: Tuned radio frequency
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Separate Controls: Three List Price: \$85.00

Trade Name: Radiodyne Circuit: Tuned radio

Circuit: xono frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$185.00 Trade Name: Radiodyne Circuit: Tuned radio frequency Batteries: Storage Antenna: Indoor or

Trade Name: Radio-Circuit: Tuned radio

Circuit: Aumos
frequency
Batteries: Storage
Antenna: Outdoor and
indoor
Loud Speaker: Separate
Controls: Two
List Price: \$75.00

Trade Name: Radiodyne Circuit: Tuned radio Circuit: frequency Batteries: Storage

outdoor Loud Speaker: Separate Controls: Two List Price: \$100.00 Trade Name: Radiodyne Circuit: Tuned radio frequency Batteries: Storage Antenna: Indoor Antenna: outdoor Loud Speaker: Built-in Controls: Two List Price: \$215.00

Manufacturer: WIL-COX LABS. Lansing, Mich. ide Name: Wilcox Hexaircoil Circuit: Tuned radio

frequency
Batteries: Storage battery preferred
Antenna: Outdoor
Loud Speaker: Separate Controls: Three List Price: \$88.00

Trade Name: Wilcox Circuit: Tuned radio frequency Batteries: Storage bat-tery preferred

Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$140.00 Manufacturer: W-K ELECTRIC COM-PANY.

PANY, 89 Middle Street, Kenosha, Wis. Trade Name: Oriole Model 5 Tuned radio Circuit: Circust: frequency Batteries: Storage Either

Batteries: Storage Antenna: Either or ground wire only Loud Speaker: Separate Controls: Two List Price: \$99.00 Trade Name: Oriole Model 6 Circuit: Tuned radio frequency

frequency
Batteries: Storage battery, and "B" battery compartment
Antenna: Either or
ground wire only
Loud Spraker: Separate Controls: Two List Price: \$100.00 Trade Name: Oriole
M.del 7
Circuit: Special patented circuit
Batteries: Storage
Antenna: Either or ground wire only
Loud Speaker: Separate
Controls: Two
List Price: \$150.00 less

Trade Name: Oriole Model 8 Circuit: Special pat-Circuit: Spec ented circuit
Batteries: Storage
Antenna: Outside antenna and ground
Loud Speaker: Separate
Controls: Two
List Price: \$65.00 less

Manufacturer:
UNITED MANUFACTURING & DISTRIBUTING CO.,
9705 Cottage Grove
Ave., Chicago, Ill.
Trade Name: Unidyne 4
Circuit: Tuned radio frequency Batteries: Storage battery
Antenna: Either
Lond Speaker: Separate
Controls: Two
List Price: \$75.00 Trade Name: Super-Unidyne 4 Circuit: Tuned radio frequency Batteries: Storage bat-Antenna: Either Loud Speaker: Separate Controls: Three List Price: \$130.00

Manufacturer: L. D. VAN VALKENBURG CO., Holyoke, Mass. Trade Name: "Van" Fixed Crystal Re-ceiver

Battery: None
Antenna: Outside
Loud Speaker: No
Control: One
List Price: \$4.00 Manufacturer: YALS RADIO ELECTRIC CO., 1111 Wall St.,

CO., 1111 Wall St. Los Angeles, Calif. Trade Name: Yale Premier Circuit: Tuned radi censed
Batteries: Either
Antenna: Outdoor
Loud Speaker: Separate Controls: Three List Price: \$50.00

Trade Name: Yale-Premier Circuit: Tuned radi frequency — Navy E

censed Batteries: Either Antenna: Outdoor Loud Speaker: Built-in Controls: Three



Gives Your Tuner A Man Sized Voice

N OW—you can enjoy loud speaker reproduction with your favorite tuner.

Using the "Electrad" 3-Step Resistance Coupled Amplifier Kit it's easy and economical to build an amplifier unit. And you will get a clarity and fidelity of tone unequalled by any other amplifying method.

"ELECTRAD" 3-STEP RESISTANCE
COUPLED AMPLIFIER KIT No. 1-C—A
Big \$6.75 value. Contains the necessary Resistor
Couplers, Certified Mica Condensers, Condenser
mounting, Certified Grid Leaks and Resistors,
Nothing else needed except sockets, rheostat and

At all Good Radio Shops or Sent Direct

—Ask Your Dealer, or Write for Folder
on Resistance Coupling Amplification.



"E L E C T R A D"
LEAD-in—Price 40c.
Fits u n d e r locked
windows or doors. No
holes to hore. Quickby installed. 3,000volt insulation. Extra
waterproofing. Meets
the quality standard
set by "Electrad"—

ELECTRAD



"The Six Point Pressure Condenser" THE "Electrad" Certified Fixed Mica Condenser is a revelation in accuracy and design. Ingenious, rigid binding and firm riveting fastens parts securely at Six different points insuring positive electrical contact. Impervious to temperature and climatic variations. Exerts even pressure upon the largest possible surface—can't work loose. Binding strap and soldering lug in one piece. Accuracy and quietens assured always. Value guaranteed to remain within 10% per proposed propose

ELECTRAD, Inc.

428 Broadway

New York City

Also makers of other handy radio essentials—Certified Grid Leaks, Audiohms, Lighting Arresters, Lamp Socket Antenna and many others. Be Prepared to Tune in European Stations During the Trans-Atlantic Test Period This Coming Season

VICTOREEN SUPER HETERODYNE KIT \$33.50 Kit of 5 Coils

Additional Parts Retoreen Super Hetero-

0005 Variable Con-

denser. I-4½ Volt "C" Bat-

tery.
1—7x24-in. Panel.
Base Board 8½x23x½.
Binding Post, Screws, Bus
Bar and Solder Lugs.

on Proping s truly Victoreen Feature.

"P" Bastery consumption is remarkably low-8-10 Milliamps, with Potentioners of the August Potention of the State of the August Potention of the State of the August Potention of the State of the August Potential Potential

former-Neat and Compact

No Oscillations, Howls or Squeals-No Matching of Tubes. Victoreen Air Core Transformers are not merely "matched," but are actually tuned to a guaranteed precision of 1/3 of 1%-another Victoreen feature. Range—Clarity—Volume—Selectivity—Ease of Operation

VICTOREEN MANGANIN RHEOSTATS



The only Rheostats with zero tempera-ture coefficient—no matter how warm the unit becomes the resistance re-mains absolutely constant. Victoreen Rheostats have double the number of turns of wire used on ordi-nary Rheostats—that means twice as No. 20 (20 Ohms)

nary Rucostats—that means twice as fine adjustment.

Genuine Manganin wire used in all

Victoreen resistances.

No. 30 (30 Ohms)

\$1.20 EACH

Potentiometers No. 200 (200 ohms) \$1.50 No. 400 (400 ohms) \$1.50 Noiseless-Beautiful-Convenient-Single Hole Mounting

Ask Your Dealer for a Free Folder and Hook-up of the Victoreen Set-or Write Directly to Us

THE GEORGE W. WALKER CO. 6540 Carnegie Ave. Cleveland, Ohio

Branch Sales Offices Are Located at

50 Church St., New York City
719 Myrmood St., Philaidejsha, Pa.
719 Myrmood St., Philaidejsha, Pa.
720 Church St., San Francisco, Calif.
720 Church St., San Francisco, Calif.
720 Church St., San Francisco, Calif.
720 Sc., Dearborn St., Chicago, Ill.
720 Church St., Wash
720 Church



Price \$1.00

JUST THE BOOK YOU WANTED "Radio News" AMATEUR'S HANDIROOK

Volume No. 1 (Fourth Printing)

Chock full of realise constructive and instructive articles from coveryofty language, which everyone can understand. Sections in coveryofty language, which everyone can understand. Sections in mitters and Account. The Data of the Control of the C

EXPERIMENTER PUBLISHING CO., Inc. 53 Park Place, New York

The Victoreen Kit-

of: 3—"Victoreen" No. 170 R.F. Transformers. 1—"Victoreen" No. 175 Input Transformer.

Either

List Price: \$105.00 Batteries: Storage Antenna: Outdoor Loud Speaker: Sepa-Trade Name: Yale-Trade Name: Yale-Premier Tuned radio frequency — Navy li-censed & Batteries: Either Antenna: Outdoor Loud Speaker: Built-in Controls: Three List Price: \$150.00

Controls: Two List Price: \$98.50 Trade Name: Air-Way Model 62 Circuit: Tuned radio frequency: 4 stages resistance-coupled au-dio amplification Batteries: Storage Antenna: Outdoor Loud Speaker: Built-in

ZENITH RADIO
CORPORATION,
310 S. Michigan Ave.,
Chicago, Ill.
Trade Name: Super
Zenith VII
Circuit: Special Zenith
Batteries: Dry cell or Trade Name: Air-Way Trade Name: Air-Way Model 63 Circuit: Tuned radio frequency; 4 stages resistance-coupled au-dio amplification

ground Loud Speaker: Separate Controls: Two List Price: \$240.00 Trade Name: Super-Zenith VIII Circuit: Special Zenith Batteries: Dry cell or storage Antenna: Outdoor or

ground Loud Speaker: Separate Controls: Two List Price: \$260.00 Trade Name: Super-Zenith IX Circuit: Special Zenith Batteries: Dry cell and storage Antenna: Outdoor or ground Loud Speaker: Built-in Controls: Two List Price: \$355.00 Trade Name: Super-Zenith X Circuit: Special Zenith Batteries: Dry cell and ground Loud Speaker: Built-in Controls: Two List Price: \$475.00 Trade Name: Zenith Circuit: Non-radiating Antenna: Outdoor Loud Speaker: Separate Controls: Two List Price: \$275.00

Trade Name: Zenith 4R Circuit: Non-radiating regenerative Batteries: Dry cell and storage Antenna: Outdoor Loud Speaker: Separate Controls: Two List Price: \$100.00 Trade Name: Super-Ioop Loud Speaker: Built-in Control: One List Price: \$190.00

ADDITIONAL LIST ADDITIONAL LIST:
Descriptions arriving
after close of issue.
Manufacturer: AERIAL ELECTRIC CO.,
128-30 W. Kinzle St.,
Chicago, Ill.
Trade Name: Crystal
Mystery
Circuit: Crystal
Batteries: None
Antenna: Outdoor
Controls: One
Controls: One
List Price: \$10.00

Manufacturer: A I R-WAY ELECTRIC APPLIANCE CORP., 618 Broadway, Toledo, Ohio Trade Name: Air-Way Model G. Circuit: Tuned radio frequency: 4 stages resistance coupled au-dio amplifier

dio amplification
Batteries: Storage
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Two
List Price: \$197.50

Trade Name: Air-Way Model 61-D Circuit: Tuned radio frequency; 4 stages resistance-coupled au-

rate Controls: Two List Price: \$98.50 Trade Name: Air-Way Model 62-D Circuit: Tuned radio frequency; 4 stages frequency; 4 stages resistance-coupled au-dio amplification Batteries: Dry Cell Antenna: Outdoor Loud Speaker: Built-in Controls: Two List Price: \$137.50 Trade Name: Air-Way
Model 63-D
Circuit: Tuned radio
frequency; 4 stages
resistance-coupled audio amplification
Batteries: Dry Cell
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Tyo
List Price: \$197.50

Trade Name: Air-Way Model 41 Circuit: Tuned radio frequency: 2 stages transformer - coupled audio amplification Batteries: Storage Antenna: Outdoor Antenna: Outd Controls: Two List Price: \$49.50 Trade Name: Air-Way

Trade Name: Air-Way Model 51 Circuit: Tuned radio frequency; 2 stages transformer - coupled audio amplification Batteries: Storage Antenna: Outdoor or indeed Loud Speaker: Sepa

rate Controls: Three Last Price: \$87.50 ALL-AMERICAN RADIO CORP.

2650 Coyne St., Chicago, Ill. Trade Name: All-Amax Frade Name: All-Ama Senior Circuit: Reflex Batteries: Storage for "A", dry cell for "B" Antenna: Outdoor Loud Speaker: Not in

Manufacturer: AM-BER MANUFAC-TURING CORPO-RATION. 599 Eleventh Ave., New York City Trade Name: Marv-O-dyne Model T



Radio Receiver



Radio evenings are complete If you have a Valleytone

Appearance

The Valleytone is mounted in a solid walnut gold stripes. It may also be procured in beautiful console models. Special Valley tables with built-in loud speaker may be





Valley table loud speaker You can always count on a full evening's entertainment if you have a Valleytone Radio Receiving Set.

Music with your dinner . . . bedtime stories for the children * * * a play, an opera, or a concert * * * iazz, mammy songs, spirituals . . . the whole range of radio broadcasting can be vours.

With the Valleytone, you can choose your programs by the clock and hear them all the evening through.

For the Valleytone is selective. It will separate and bring in stations only four or five meters apart and will easily separate local and distant stations.

Valleytone selectivity gives a new meaning and puts a new pleasure in radio.

And with the balanced tone of the Valleytone when you hear a station you marvel that any reproducing mechanism can really achieve such faithfulness and such natural results. The superiority of the Valleytone can be demonstrated. The Valleytone thrives on comparison, Wherever it is judged by results and performance, it wins a new owner.

Any authorized dealer will be glad to demonstrate the Valleytone for you.

VALLEY ELECTRIC COMPANY, Radio Division, St. Louis, U.S.A. Branches in Principal Cities

Valleytone Receiving Sets

Valley Battery Chargers

Valley

Valley Electric

Circuit: Two-stage

Loud Speaker to Sepa-

Controls: Three List Price: \$90.00



Tuning Now Made Easy

This has been the choice: "Selectivity-or-Ease of Control." Heretofore, every set builder, every set owner, every set designer, in order to get one of these qualities, has had to sacrifice something of the other. But now you can have ease of control and supremely accurately tuning-have them both, and have them with your present set. The new MAR-CO dial does it! For development in dials has not, as many supposed, reached its limit.

This handsome dial-typical of MAR-CO precision-responds to your slightest touch. There is no suggestion of backlash. It moves smoothly, evenly, and splits a single degree into hairs'-breadth divisions. Several noted set manufacturers have already adopted MAR-CO dials. Circuit designers are specifying them.

Put MAR-CO dials on your present set-or on the new set you buy or build. Till then, you can never know what a difference a dial can make.

MARTIN-COPELAND COMPANY Providence, R. I.

MAR:CO

Join the Chase for Extra Dollars!

You can easily replace those dollars you-by increasing your income. Experiof your spare time each week.

No investment or experience is neces-We teach you and help you in all of your efforts. The coupon below will bring you full particulars about this unusually attractive offer.

---- CLIP OUT-MAIL NOW----

E. J. POLEY, EXPERIMENTER PUBLISHING CO., Box 105, 53 Park Place, New York City.

Nickel

Trade Name: FADA

Loud Speaker: Sepa-Controls: Three List Price: \$125.00

Trade Name: Mary-O-Dyne Model D Circuit: Two-stage radio frequency Batteries: Storage, may be adapted to dry Trade Name: FADA Trade Ivar
"Neutrola"
(Circuit: Neutrodyne
Batteries: Storage or
dry cell
Antennar Ontdoor or
indoor (outdoor preindoor Loud Speaker: Sepaferred)
Loud Spraker: Built-in Controls: Two List Price: \$125.00

Trade Name: Mary-O Dyne Model DC ((Console) Circuit: Two-stage Trade Name: FADA Neutrodyne Phono-graph Panel Circuit: Two-stage radio frequency Batteries: Storage, may be adapted to dry Antenna; Outdoor or

Loud Speaker: Built-in Controls: Two List Price: \$185.00 Manufacturer: AMER-ICAN APPARATUS CO., Richmond, Ind. Trade Name: CN-8 Circuit: Tuned radio frequency Batteries: Dry cell or Trade Name: FADA
"Nentroceiver Grand"
Circuit: Nentrodyse
Batteries: Dry cell or

loop Loud Speaker: Built-in Trade Name: AMACO

indoor (ness, ontdoor)
Loud Speaker: Built-in
Controls: Three
List Price: \$225.00 indoor Loud Speaker: Sepa-Control: One List Price; \$60.00 Trade Name: FADA
Davenport Table
(Console)
Circuit: Neutrodyne
Batteries: Dry cell or Trade Name: AMACO CN-9 Circuit: Amacodyne Batteries: Dry cell or

indoor Loud Speaker: Bald-in Unit built-in

Manufacturer: AMER-ICAN SALES CO., 415 Bryson Bldg., Los Angeles, Calif. Trade Name: "Indian" Portable Circuit: Indian Batteries: Dry cell Antenna: Outdoor or Trade Name: FADA Queen Ann Desk Circuit: Neutrodyne Batteries: Storage or dry cell Antenna: Outdoor or indoor (designed for

outdoor)
Loud Speaker: Built-in
Controls: Three
List Price: \$300.00 Trade Name: FADA

Manufacturer F. A. D.
ANDREA, Inc.
1581 Jerome Ave.,
New York City
Trade Name: FADA
"One Skyty"
(Circuit: Nestrodyne
Batteries: Storage
Antenna: Outdoor or
Indoor (outdoor preoutdoor)
Loud Speaker: Built-in
Controls: Three
List Price: \$275.00

Loud Speaker: Sepa-

ferred)
Loud Speaker: Sepa Trade Name: FADA Beethoven: Grande Circuit: Neutrodyne Batteries: Drg. cell or Trade Name: FADA
"Neutro-Junior".
Circuit: Neutrodyne
Batteries: Storage
Antenna: Outdoor or
indoor (outdoor pre-

Manufacturer: BAT-TERVLESS RADIO CORP. Loud Speaker: Sepa-

1457 Broadway, New York City

When you put UNIPOWER in your set ~ you put an end to the most frequent cause of poor radio reception

NO longer is it necessary for you to put up with the inconvenience of operating your set on dry "A" batteries—or the bother of charging your "A" batteries fail when you want then most. And that today is the most frequent cause of poor radio reception.

You can now equip your set with Unipower and have the thrill of continuous, unfailing "A" power always of the highest quality and refinement, always at full voltage.

What Unipower is

Unipower is a compact, scientifically designed "A" power plant that automatically converts house lighting current into radio power. Unipower is not a battery eliminator and should not be confused with

Unipower comes to you completely wired and assembled—all you have to do is connect two wires to your set and plug in on your house current. Unipower then requires absolutely no attention except the occasional addition of water. Unipower is quipped with an exclusive Balkite charger of special design. Unipower will last you for years, and there are no tubes, bulbs, lamps or weeking parts that require frequent and expensive replacement.

On when it's off - Off when it's on

A unique feature of Unipower is the master-control switch that governs the operation of your entire set. When the switch is ON, Unipower feeds your set rich, quiet power that gives ideal reception, with neither hum nor noise. When the switch is OFF, Unipower automatedly replenishes itself on a low trields charge and with a minimum consumption of current—a few

A new experience for you

Until you use Unipower, you will never know how easily, perfectly and economically your set can be operated. Never again will you go back to dry cells—or bother with a storage battery and charger.

The nearest radio dealer can probably supply you with Unipower—or will be glad to get it for you immediately. The Gould Storage Battery Co., Inc., 240 Park Avenue, New York.

The first cost is the last!

THE NEW UNIPOWER IS QUICKLY AND EASILY INSTALLED—AND FITS COMFORTABLY INSIDE MOST

Unipower's first cost is moderate—and the first cost is the last because Unipower has no tubes, bulbs, lamps or working parts that require frequent and expensive replacement. Unipower will last you for years. Compared with dry "A" battery operation, Unipower pays for itself over and over again.

The standard Unipower operates from alternating current, 110-125 volt—60 cycle. The 4 volt type is for sets using UV-199 tubes or equivalent and retails for \$35,00. The 6 volt type is for sets using UV-201-A tubes or equivalent and retails for \$4,00.0. West of the Rockjee, prices are slightly higher. (Special models, 25-50 cycle are available.)

FREE!

Write for interesting booklet, "Unipower, a triumph in radio power."



Controls: Two List Price: \$16.00

Trade Name: Dietrick-son, Inc. Type 2R-3 Circuit: Regenerative Batteries: Dry cell Antenna: Outdoor Loud Speaker: Sepa-

Manufacturer: ELEC-TRICAL RESEARCH & MFG. CO., Waterloo, Ia.

Control: One List Price: \$100.00 Trade Name: Superior-flex Model P-3 Circuit: Superiorflex— double reflex Batteries: Dry cell or

rate Control: One List Price: \$125.00

storage
Antenna: Outdoor
Loud Speaker: Built-in
Control: One
List Price: \$250.00

Manufacturer: DAVID GRIMES, Inc., 1571 Broadway New York City Trade Name: David Grimes "Empire

Ward's New Radio Catalogue Is Yours Free

This Catalogue represents the world's greatest radio store 333377



Where you buy Radio is equally as important as the set you buy.

Send to Radio Headquarters for the what has been actually tested and ap-

See for yourself what low prices can be made on Radio when it is sold without the usual "Radio profits."

A Complete Radio Manual

This new 52 page Radio Catalogue shows everything in parts, batteries, cabinets, contains a list of stations, a radio log for recording stations. It shows the best of the new sets. One tube sets that give amazing results. Five tube sets with a Write to the house nearest you for your free copy of Ward's new

single dial to turn. Think of tuning in one sta-tion after another by turning a single dial! Every price quoted means a big saving to you. Everything offered is tested by our own Radio Experts; in fact, the best experts compiled this stalogue for you.

Write for this free 52 Page Book, It is yours

Our 53 Year Old Policy For 53 years we have sold only quality merchan-dise under a Golden Rule Policy. You can rely absolutely upon the quality of everything shown in this Radio Catalogue,

Radio Catalogue. Address Dept. 2-R

Montgomery Ward & Co.

The Oldest Mail Order House is Today the Most Progressive Baltimore Chicago Kansas City St. Paul Portland, Ore. Oakland, Calif. Ft. Worth

MILLIAN 0

THE "DOUBLETOROID" COIL

"Hombetoroids" can be mounted at any angle or spaced at any distance, more selective sets possible, since they do not form miniature loop serials. "Doubletoroids" hold static and other disturbances to a minimum since no current from an external source can influence them.

Outstanding Features of the Doubletoroids,

RADIO FOUNDATION, Inc. 25 West Broadway New York



It's Variable

NONOISE GRIDLEAK

Trade Name: "No-Bat-Ry" Carcuit: Super-tuned radio frequency Batteries: Electric cur rent, D.C. or A.C. Antenna: Outdoor or

Trade Name: "Bat-Ry-Les" Console Model Circuit: Super-tuned radio frequency Batteries: Electric cur-rent, D.C. or A.C. Antenna: Outdoor or

Manufacturer: CHAS.
A. BRANSTON, Inc.,
815 Main St.,
Buffalo, N. Y.
Trade Name: Branston
Hetrola V Cat. No.
R45 R45
Circuit: Tuned radio frequency Batteries: Storage Antenna: Outdoor Loud Speaker: Not included

Trade Name: Branston Hetrola V Cat. No.

Greguency
Batteries: Storage '
Antenna: Outdoor
Loud Speaker: Built-in
Controls: Two
List Price: \$120.00

Manufacturer: DIET-RICKSON RADIO CO., Inc., 3rd and Elmond Sts., St. Joseph, Mo., Trade Name: Dietrick-son, Inc. Duo-S Circuit: Radio freindoor Loud Speaker: Separate Controls: Three List Price: \$125.00 Trade Name: David Grimes "Renaissance Model" Circuit: David Grimes Inverse Duplex Batteries: Dry cell Antenna: Outdoor or indoor Loud Speaker: Sepa-Controls: Two List Price: \$85.00 Loud Speaker: Sepa-Controls: Three List Price: \$125.00

Loud Speaker: Sepa rate Controls: Two List Price: \$40.00 Trade Name: Dietrick-son, Inc. Type 2R-4 Circuit: Regenerative Batteries: Dry cell Antenna: Outdoor

Trade Name: David Grimea "Baby Grand Model" Circuit: David Grimes Inverse Duplex Batteries: Dry cell Antenna: Outdoor Loud Speaker: Sepa-rate Controls: Two List Price: \$49.50 TO BE CONTINUED NEXT MONTH

RAILWAVES

Watter: "Do you think radio can be applied to the railways?"
Wayve: "Why not? Wave trains have been used for years."

Contributed by Jack Bront.

THE WORST IS YET TO COME

Tic: "Do your neighbors know that your radio set is portable?"

Toc: "I guess not. They haven't tried to borrow it yet."



One Man Tells Another!

Actual performance has built Gold Seal's popularity

They last twice as long . . . they reach the peak of perfection in reception . . That consensus of opinion has given Gold Seals the call wherever perfect reception, without excuses, is demanded. We have watched them operate under some of the most exacting test conditions, where other tubes failed. But Gold Seals performed in true Gold Seal style.

Winning national recognition purely on their merits is surely proof of the worth of Gold Seal Tubes. It shows, too, that when radio fans find a superior tube, they're quick to tell others. Nothing else could account for the splendid demand for Gold Seals.

.. Engineered and Guaranteed ..

Gold Seal filament is a tube engineering accomplishment destined to revise the radio world's estimate of what fine reception is. And in a splendidly equipped plant, Gold Seal's standards and exhaustive double-tests send each tube out perfect.

If you use a tube rejuvenator, Gold Seals will help you get longer tube life. They can actually be rejuvenated.

A no-argument guarantee goes with every Gold Seal Tube. Your dealer in giving you this guarantee knows it means what it says because he knows the resources of the Gold Seal organization.

Just say Gold Seal to your dealer. You'll get the tube you have waited for. If your dealer is not yet supplied, write us direct. Everywhere \$250

Guaranteed

Manufactured

in All Types A MONTHS PRINT TO PRI

Facts About Tubes

- 1—A tube and its guarantee are only as good as the intentions of the organization behind them.
- 2—Gold Seals are winning on tested merit.
 3—Dealers stand back of them because we stand
- Gold Seal's engineers are radio experts; the Gold Seal plant is a reality and a model of
- Gold Seal plant is a reality and a model of efficiency.

 There were six months of exhaustive experi-
- 5—There were six months of exhaustive experiment before Gold Seal Engineers would permit a single tube to be offered to the public.

GOLD SEAL PRODUCTS COMPANY, Inc. 250 PARK AVENUE, NEW YORK





A Crack 40-80 Meter

(Continued from page 605)

pierced with an ordinary steel drill which mitter might well be added here. In the first place, the antenna was so constructed as to have a fundamental wave-length of 120 a guide in building one to operate in a simi-

lead is connected at a 30 degree angle. The overall length is 80 feet and the fan is stretched 15 feet from the earth.

registered on the antenna ammeter.

For the 80-meter hand the series condens open circuit made to correspond to 80 meters. The closed circuit is brought to

THE RECEIVER

Here again "simplicity is the best policy." The circuit which has given the best results covers the wave bands from 10 to 125 meters. The method of mounting the coils is of

The tuning parts are placed at the back of the board to avoid all capacity effects,

details. It has been found possine, by in-serting a small solder lug on the third, seventh, thirteenth and seventeenth (last) turns, to effectively cover all waves from 10 to 125 meters. The antenna coupling coil is of five and the tickler of eleven turns.

No. 140

INSTRUMENT

1650 Walnut St.

CO.

Chicago

The New MURDOCK

Murdock 204







Murdock 203

Six-tube neutrodyne. Remarkable selectivity and simplicity in tuning make this a truly fine

NEUTRODYNE RECEIVER

NOW-Shielded

More power—greater sensitivity.

These are the outstanding features of this marvelous receiver.

It embodies the newest achievement in neutrodyne construction—the shield.

You'll be amazed at the way it singles out stations—sifts and separates those you don't want to hear.

Murdock 200

Five-tube neutrodyne with loudspeaker and vernier dials. Embodies now improvements that will be extolled by others in 1926. We also offer Murdock 201—the same instrument without 1 o u d



There are opportunities for eager, energetic, enthusiastic merchandisers to become Murdock dealers. Write for information. Every day counts just now. Mail your letter to.

Wm. J. Murdock Co.

night.



MURDOCK RADIO



\$12.50 Beautifully finished in mahogany. Dimensions 30 in. x 8 x 7 in

Like Red Grange Dodging Tacklers

cludes near-by stations, straightarms static, and scores against the far-distant stations that put such a kick into radio reception.

Line up for the 1926 season with Aero-Loop as an essential part of your equipment.

"A Loop Within a Loop", with the inner loop stationary and acting as a "booster" while the outer loop is ajusted by rotating—

Can be used with-or to replace-outside antennae. Sells for \$12.50. Ask your dealer. Shipped direct on receipt of price, express paid, if nor at your dealer's. Be sure to specify the set with which it is to be used. Please give dealer's name.

Write for 12-page Descriptive Diagramatic Aero-Loop Booklet. Your copy Free.

SCOTT SALES COMPANY National Distributors

443 SOUTH SAN PEDRO STREET LOS ANGELES, CALIFORNIA

UTT-WILLIAMS ELECTRICAL PRODUCTS CO. SANTA ANA, CALIFORNIA All are wound with No. 16 D.C.C. wire.
Several receiving antenna systems have been tried at the writer's station. It is interesting to note that the one which has proven the most satisfactory under all conditions is that employing a single wire about 40 feet long, and stretched across the room

proven the most satisfactory thineer all conditions is that employing a single wire about 40 feet long, and stretched across the room the condition of the control of the conbigh, which acts as a counterpoise. This combination has been found to give the greattest signal-stail ratio, which is of great importance in reception, especially over great distances. No actual ground connection is

THE WAVE METER

A wave meter is a first essential in any station, both in connection with the receiver and the transmitter. There is no need for claborate equipment in this line, the simplest

will satisfy just as well.

A variable condenser with a coil shunted across its terminals can be used to measure the frequency of a receiver or transmitter by what is known as the "click" method. This method owes its existence to the ability of a circuit in resonance with an oscillating

In the receiver this resonance is indicated by a click on the phones as the absorption of energy momentarily stops the oscillation in the secondary circuit. When the transmitter is being tested, the absorption causes an increase of the plate current, accompanied by a decrease in the antenna current when the two circuits are 'in tune.' The maximiter is a few to the contract of the

It is not difficult to calibrate a wave meter to a comparatively high degree of accuracy by making use of the standard frequency signals transmitted from time to time by the Bureau of Standards Station WWV, or the Stanford University Station, 6XBM.

The schedules for these stations, and also directions for their use in calibration, are made public from time to time, so no further mention need be made of them.

IN CONCLUSION

The writer has attempted to present an accurate description which will be of value to the entire radio public. Its significance is increased by the probability that within the next few months, the 159-200 meet public the property of the property of the property of the present of the present of the present of the presentation will interest both those who are entering the field for the first time, and those whose experience has been gained on the

TO THE B.C.L: Does radio bold a fascination to you beyond the turning of dials, and the voice of the distant broadcast announce? Haven't you often wished that you could answer back—that you, yourself, could talk to other fans miles away?

TO THE AMATEUR: You already know the thrill which comes from conquer-

TO THE AMATEUR: You already know the thrill which comes from conquering distance with a set of your own construction. The field of "40-80" opens to you even greater possibilities. These bands of the amateur family.

For night and day—summer and winter,

For night and day—summer and winter, a station which can operate on these two waves, and can shift easily from one to the other as is true of the one here described, will be able at all times to cover the greatest distance and maintain the most consistent

ANESTHESIA

Friend: "What a horrible noise comes out of your radio, Jack."

Jack: "Well, if you were just coming out of ether, you'd make a horrible noise, too."

Separates Those Crowded Stations

assions, they are easy to get, clear, perfect in tone. All accomplished with this beautiful dial. So grientifically thought out that is really a revelation advantage of the straight line frequency receiver, but without the necessity and expense of reviring. Gradually change receiver, and though the receiver is the straight line frequency lengths to 2.2 to 1 at high wave lengths to 2.2 to 1 at high wave lengths does the trick. Instantly at ached to any set of straight line frequency. Send for instructions.

RADIALL COMPANY

Dept. T.R.N.-1, 50 Franklin St., New York



TUNE-RITE

The Straight Line Frequency Dial
Made by the makers of Amperite, the Self-Adjusting Rheostat





These unusual advantages increase radio engoyment, Benjamin Super Radio Paris have become the standard for Perfect Results—just as they have become the standard equipment in many of the finest, factory-made radio sees found in the homes of true must levers.

Benjamin Low Loss Long Range Condensers

Straight line type. Spreads the broadcast range on the lower wave lengths, climinating bunching of makes tuning much coster. Minimum insilation is used and leikage must go through long paths costed of strongest field. Unpolashed silver plate finish. Small size of condenser makes it adoptable to any sent regardless of crowding of appearatus on subjunct. Friction disserting of appearatus on subjunct. Friction disserting of appearatus on subjunct of the plate of the strongest control of high ment. Duling resplain formation with each of the significant condenser. Most subject sometimes of the significant condenser. Most subject sometimes are subject to the significant condenser. Most subject sometimes are subject to the significant condenser. Most subject sometimes are subject to the significant condenser. Most subject sometimes are subject to the significant condenser.



Benjamin Tuned Radio Frequency Transformers Low Resistance, Low Distributed Co-



Benjamin Cle-Ra-Tone Sockets



Benjamin Electric Mfg. Co.

There is no better Headset at any Price"



Supersensitive, loud and clear. Reproduces clearly and naturally. Electrically and mechanically as perfect as the highest priced headset. Guaranteed equal in performance to any or all other makes. Tested and tone-matched to the utmost precision. DELTAS are BEST sellers because they are best

Write or wire NOW for full particulars and

DELTA ELECTRIC COMPANY.

150 Delta Block, Marion, Indiana, U. S. A. Lanterns, Auto Spotlights, Auto Ash Receivers, Motor-Blovele Launes, Flashlights and Flashlight Batteries, Why Run a Junk Shop?

is the most expensive? You will save money

Another feature of the junk-shop method

the set is going to work as it did the last time you used it. A slight jar may cause one of the inductances to fall out of posione or more of them may work out of place and fall off. In this way again, your cher-ished adjustment will be lost and has to be Now think of the losses that are found

when slipshod wiring is carried out. Poor connections and fine wire are things to be mean working that distant station that you If you pay some attention to the layout

of the various parts you will again help some part of the radio frequency circuit, the results may be affected. If your A. C. line interact, with part and the control of the interact, with part and the control of the control on the as pure and the control of the control on the as pure as in would be if you kept the two circuits separated. The writer at the control of the control of the control on the C. W. inductance. It was found al-most impossible to clear up the note so that less of the fact that a basisy further force filter was used. A survey of the set soon pointed toward the placement of the girmany.

Probably one of the places where this some ham stations is where a chemical rectiof these important parts of a transmitter made up of any number of odd-sized jars that may be at hand and equipped with nondescript aluminum and lead plates of differ-ent sizes? Often, is undoubtedly the answer. A rectifier of this nature will not work pro-Do not try to cut up aluminum pans and other cooking utensils of the cheaper variety to get your aluminum electrodes. This stuff is N. G. for rectifiers. Blow ness in various things will enable you to do ness in various things will enable you to do
just that, forget certain parts of the set for
a good long time. Some fellows seem to
like to play around with their sets all the
time, even when they are working perfectly,
but usually they only succeed in making things worse. There is no percentage in that

Make Radio DO What You Hoped it Might Do

With every piece of Walbert apparatus you take another great step toward realizing your highest radio expectations. Walbert apparatus is specifically created to erase the deficiencies which may now be baffling you. And just from a description of the action of each Walbert appliance you can see how even the finest present-day radio must benefit from these products.

The Dial that changes old Condensers to S. L. F.



Straight Line Frequency in Condensers has swept Radio. But you can be up-to-date without discarding old condensers. Any semi-circular plate condensers give you perfect S. L. F. characteristics when equipped with Walbert S. L. F. Vernier Dials. You revolve knob and pointer uniformly—Walbert mechanism automatically proportions capacity to broadcast frequencies! No more crowding at low wave lengths. All the fanous original Walbert venier features incorporated in this remarkable S. L.F. dial. \$2.00

Univernier — to put EVERY station on your log



Slow a down your slowest finger-twist twelve times! The ideal ratio—12 to 1. Remember the knob diameter is part of the ratio. Big. centered, Univernier knob preserves the ratio. Picks out stations you now miss. Sharpens stations that now blur. Precise gear clearance prevents jumpy starts or stops. Slippage impossible. No effect on condenser bearings. Simplest mounting. Walbert made it first. It still is first by far. New, convenient, \$1.50 removable logging records along are invaluable. Free with each Univernier. \$1.50

Make your set YOURS

Sure, simple Walbert Lockswitch prevents tampering. No key nuisance. No chance of shock. Phosphorbronze lifetime



Panelite your Set



There is light where your set is, with Panelite. Clear, soft light right on the dials without danger of the house circuit hum.

Easily wired. Tiniest current use. Can also serve as a pilot to warn when set is on..... \$1.00 Gold plated \$1.25

S. L. F. Where You Want It-COMPACTLY



A full inch shorter at least, the Walbert S.L.F. Condenser nevertheless covers the important 90% of the brondcast range with true, straight line frequency characteristics, You really need only that first 90%—so the extra inch of space is worth more than anything else. It is the most practical all-around application of S.L.F. In dust-tight case, with lifetime bearings, spring brass plates, and other highly developed features Walbert S.L.F. Condenser is priced at 10% 33.50

With University 55.000

WALBER

Manufacturing Company, 923 Wrightwood Avenue, Chicago

The// SUPER-HETERODYNE



Here's the finest, most complete book of data and information ever compiled on the Standard Super-Heterodyne.

This is the big book of instruction and information on the various standard "supers" in common use today; a complete, up-to-the-minute, impartial 64page book covering all the builder or user of this type of set might want to This is the very latest of the complete library of Experimenters' Handbooks on radio. These books are complete practical guides to almost every impor-

You can get any of these books at your radio or news dealer or direct from us.

The CONSRAD COMPANY

Sole distributors for the E. I. COMPANY

233 Fulton St. New York, N. Y.

mission, get your set working right and leave

You may say, and it may be true, that you

are obtaining good results with your transfinished job of the installation. cleaned up the apparatus, laid it out sys-tematically and wired it up neatly. I am willing to bet my 50-watter against a pint of vacuum that you would. Try it and see,

And the moral of all this? Maybe you And the moral of all this? Maybe you won't need a moral by this time, but anyway here goes. It you would have good transmission, eliminate the junk-shop method. Plan things before you actually work them out and lay out your transmitter

Activities of the Radio **News Laboratories**

The method of making the measurement

It is evident that the measuring (or pick-

length of the driver must be so adjusted

When this has been done, close the

To bring the circuit back into resonance with the driver without changing the wavepacity of the condenser we are measuring.

precision of the measurement, especially is noun cases, and when we take the difference between the two readings this small capacity drops out. Thus, if C_t is the first capacity reading of the standard, C_a the second, and c the small capacity of the leads, then the capacity of the unknown is

and it will be noted that the small capacity c drops out. The leads may, however, have a slight inductance, and for this reason it is

A Real Long Range Crosley Receiving Set. \$9.75

Do not assume from its very interesting price that this very unusual Crosley set is a toy. Its impressive performance alone entitles it to serious consideration.

Heretofore, the \$10 radio was designed only for local reception. Now the Crosley Pup extends the entertainment radius to 1500 miles under ordinary conditions. Place it beside some costly multipletube set and operate the dials. Both tune through local stations sharply. Both get the same programs with equal case and clarity. Both let you tap the infinite enjoyment coming through the air. There is only one difference-the Pup operates with head phones instead of a loud speaker.

The Pup is the newest Crosley set with a price that reflects the volume-production economies of the world's largest builder of radios. It is substantially constructed and permanent in every regard. Its design is an improvement of the famous Crosley one tube set with which Leonard Weeks of Minot, N. D., heard the MacMillan Polar Expedition while the rest of America listened in vain.

Almost overnight the Pup has become the most popular Crosley set ever offered. It is being bought for youngsters whose curious fingers cannot resist the lure of dials and switches; for the cook, the maid, the old folks back home, and for shut-ins. Traveling men are selecting it because of its easy portability, and radio enthusiasts to have an inexpensive check on their larger sets. Hear it onceand you will own one too!

In addition to the Pup, there is a Crosley for every price and preference. Operating 1, 2 and 3 tubes, these are encased in handsome Crosley-built cabinets and range in price up to the Super-Trirdyn Special which retails for \$60. Each will deliver the superlative performance that has made the word "Crosley" a hall mark of radio perfection in millions of homes throughout the world.

THE CROSLEY RADIO CORPORATION CINCINNATI, OHIO

Owning and operating W L W, first remote



Grosley 3 Tube
52 S. D.
Mahogany finished
cabinet, sloping panel.
Holds all batteries.
\$32.50.



Crosley Super-Trirdyn Regular





strong, U. S. patent No. 1,113,149 and priced from \$9.75 to \$60.00 without accessories. None of the prices quoted include batteries, tubes, headphones, etc. Add 10% to all prices west of the Rocky Mountains.

Crosley De Luxe Combination

Crosley Super-Trirdyn Special



CROSLEY RADIO



IN CONDENSER DESIGN set owner hears—clearly and sharply—sta-tions which he could never hear before to the variance of the could never hear before the ordinary type of condenser. The entire 360 degree dial is absolutely subshe, affording the accuracy of the ineas —the Pursell greatly reduces "static," and other air interferences. Brundl Taper Coil Condenser because it represents the finest condenser workmanship available to day—because it gives to radio reception a facts of the condense of the condense of the condense translations.

A FTER two years of scientific research by one of America's leading experts in condenser engineering, old standards in de-sign have been swept away by a new and

sign have been sweet away by a new and advanced principalle. history has a more Never before in radio history has a more ment been offered. No plates, pears or racks to get out of alignment. No solder, No washers, Kothling to become loosened of the configuration of the property of the configuration of the property of the property of the configuration of the lower half of the disk. As a result the

Manufacturers-Jobbers-Dealers-Wire or Write THE FURNELL MANUFACTURING CORPORATION 889K Broad Street, Newark, N. J.

360° TAPER COIL



appears. With this condenser the measurements may be made as close as one micro microfarad, which is close enough for most

The radio fan may, by this time, begin to wonder where he can get hold of a cali-brated condenser. Precision instruments cost He can, however, if he as a guide in choosing condensers, or merely own condenser by the following method:

Let him use any good variable air con denser having semi-circular plates (which he probably already has) for his standard. He can obtain, either from the advertisecurve of the condenser, and, along the

In making the measurements, the experi-

Results of the Radio Shower Party

Stea Mills.

See Mills.

Story of the Mills of the Mills of the Mills.

Derman Brooklyn, N. Y.

Le Tarri, Brooklyn, N. Y.

Sarke Missiers, Brooklyn, N. Y.

Sarke Missiers, Brooklyn, N. Y.

Sarke Missiers, Brooklyn, N. Y.

Sarker Brooklyn, N. Y.

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year Experimenter Publishing Co., 53 Park Place, N. Y. C.

Another BOSCH RADIO PROPUCT PRICE \$1450

Junior AMBOTONE

Another Bosch Radio triumph. The announcement and immediate nation-wide acceptance of the Bosch Radio Receiver, the Amborola and the Bosch Reproducer, the Ambotone, is now followed by another Bosch Radio product. Bosch now announces the Junior Ambotone.

The Junior Ambotone is a radio reproducer with an unusual tonal quality built to the famous Bosch standard of precision. Following the Ambotone principles of reproduction, the Junior Ambotone gets its mellowness from wood.

The Bosch ability to manufacture to precision standards accounts for the tone quality. The Bosch ability to build with accuracy in quantities accounts for the remarkably low price. The greatest value in radio—the Junior Ambotone—at \$44.50.



AMERICAN BOSCH MAGNETO CORPORATION
Springfield, Mass.



929 PENN AVENUE PITTSBURGH, PA No 10 of a series of 10 1999 R.F. CHOKES "FILTER FACTS Fellow them thru monthly

At the longer wave lengths the filters previously discussed have a double purpose. They thru the small capacity of the windings of large chokes or from stray induction from the set. These should be placed in both the plate and filament supplies. In the filament supply a large condenser,

If you are interested in consistent maximum miles per watt you will be interested in Bul-

ELECTRIC SPECIALTY COMPANY

TRADE "ESCO" MARK

This complete series with other valuable motor-generator information may be obtained in pamphlet form. Write for your copy.

RADIO PARTS CO., LABS., S. AUSTIN BLVD.



Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

Brooklyn, N. Y. drickson, Brooklyn, N. Y. de, Castle Point, N. Y. Elkington, Clark Mills, N. Y. ed, Corning, N. Y.

ington, Pa.
r, Fairmount City, Pa.
crie, Pa. Drumore, Pa.
Drumore, Pa.
xel Hill, Pa.
Dawson, Pa.
ssona, Pa.
ouderspo-

Jr., Daws. Cressona, Pa. Cressona, Pa. Condersport, Pa. Butler, Pa.
bst. Bristol, Pa.
Blossburg, Pa.
Blossburg, Pa.
teiser, Bethlehem, F
isler, Ardmore, Pa.
Allentown, Pa.

ZONE 4

Morrison, Baltimore, Md.
Rogers, Akrom, O.
ey, Barberton, O.
lagher, Cleveland, O.
li, Spencer, O.
fman, Columbus, O.
fman, Columbus, O.
fman, Columbus, O.
fman, Columbus, O.



made than the Sylvania-that is our promise to you, our guarantee.

Aside from this honest assurance, you have the good opinion of thousands of users who know that Sylvanias do deliver more satisfying service, better tone, greater sensitivity, more volume, longer life.

Built into Sylvania tubes is an almost unbelievable degree of accuracy, painstaking skill, sterling quality. Nothing is left undone that will make them the more worthy of your enthusiastic approval. And the fact that they cost no more than other tubes is a very definite reason why you should insist on getting them.


> REHIND each Sylvania tube stands a thoroughly responsible organization, well known and well regarded for many years throughout the electrical world. Its guarantee of complete satisfaction, both to consumers and the trade, means much and will be upheld under any and all conditions.

To Radio Dealers

The rapidly widening circle of Sylvania enthusiasts is making our dealer franchise more and more valuable. Regardless of your present connections write or wire for full particulars now.

A TYPE FOR EVERY NEED OR PREFERENCE: S 01-A, L S-99 Large Base, S 99 Small Base

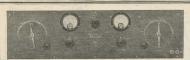SYLVANIA PRODUCTS COMPANY EMPORIUM, PENNA.



MANY MODEL C-10 Super-Heterodyne The Highest Class Receiver in the World

Wave length range 50-600 meters with removable Coils. Panel Dimensions 28 3/16 in. x 8 in. x 1/4 in.

Only two major tuning adjustments.

Total amplification almost 2,000,000 times.

For any Circuit Prompt shipment can be apparatus of the following manufacture:

E. I. S., Inc. General Radio Willard Benjamin Electric
Allen Cardwell
Dubilier
Westen Magnavox
Jewell
Western Electric
Radio Corporation
Music Master
Cutler Hammer
Frost A high powered 10-tube Broadcast Receiver capable of receiving over 3.000 miles under favorable conditions, and having a degree of selectivity far in advance of others.


We believe the Navy Model C-10 represents final superiority over any receiver now being manufactured or even contemplated for broadcast reception.

Attractive illustrated literature gladly mailed upon request. Write direct to

NORDEN-HAUCK, INC. Engineers

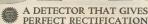1617 Chestnut Street, Philadelphia, Penna.





THE perfect rectification of Radio signals on any Crystal or Reflex Set of course means clear, true, tones and tonal effects. Such reception is possible with the Carborundum Detector Unit. It is a car-

tridge type unit carrying a Carborundum especially created for Radio purposes and one of the inherent qualities of Carborundum is perfect rectification. The Carborundum Detector Unit is fixed, permanent-no adjustments-it

retains its sensitivity indefinitely and will not burn out. It will increase volume, distance and selectivity.

Backed by our guarantee. From your dealer or direct

THE CARBORUNDUM COMPANY, NIAGARA FALLS, N. Y. New York - Chicago - Boston - Philadelphia - Cleveland - Detroit - Cincinnati Pittsburgh - Milwaukee - Grand Rapids

Carborundum Detector Unit

TO THE RADIO DEALER

EXPERIMENTER PUBLISHING COMPANY, 53 PARK PLACE, NEW YORK CITY

Radio News for November, 1925

Service of the control of the contro

ZONE 5

"Thouse McDould, Jr., Fall fere, MassJohns C. Stelder, Maddesser, P.

Middel P. Lechas, Pigmonh, P.

Middel P. Lechas, Pigmonh, P.

Middel P. Lechas, Pigmonh, P.

Lechas, Pigmonh, P.

Lechas, Pigmonh, P.

Lechas, Pigmonh, P.

Lechas, Pigmonh, P.

Lechas, Pigmonh, P.

Lechas, P.

E. Srewart, Daltimore, Md.
A. French, Baltimore, Md.
A. French, Baltimore, Md.
Dye, Baltimore, Md.
Dye, Baltimore, Md.
Dye, Baltimore, Md.
Dye, Baltimore, Md.
Aurier, Baltimore, Md.
Baltimore, Md.
Baltimore, Md.

O. J. Malmanger, Huxley, Ia. George S. Rigby, Media, Pa. Edward Bell, Pompton Lakes, N. J.

Introducing The PICT

The Speaker of Perfect Tonal Values

In the FITCH all the many advantages of the cone-type speaker have been brought to a fuller development.

The double cone has no frame about its edge to restrict free vibration. It is supported at the center only. It has no rubber, metal or felt attached to the edge to kill or distort the tone values.

This, together with the use of two cones of unequal size and angle, gives the FITCH its remarkable clarity and fidelity of tone.

The entire audible range, from the high notes of the soprano to the deep tones of the bass, is reproduced with exceptional uniformity.

The FITCH speaker is a beautiful symmetrical, and artistic ornament, which barmonizes with any setting.

The unit is adjustable. It will not chatter or blast.

See and hear the FITCH at your dealers. If your dealer is not supplied, we can make immediate delivery.





FITCH RADIO COMPANY 105 West 40 th St. ~ New York City

TRIMM Concert \$25



TRIMM

Superior Reproduces HEADSETS Dependable - - - 4.40 PHONODAPTERS
Giant Unit - \$10.00
Little Wonder - 4.50

SPRAKERS Home Speaker - \$10.00 Entertainer - 17.50 Cabinette - -17.50 Chello -30.00

() RIMM Concert reproduces all the tones, from high of violin to low of organ, with perfect fidelity. Easily tone and volume. Volconite horn eliminates scratchy overtones and noises.





as you like it



Cannon-Ball Headsets

ET greater satisfaction out of G vour receiving set. Equip it with Headsets-one for each member of your family.

Clearness and perfection of reception are among the many reasons why you'll enjoy Radio as you like it through a Headset. By reducing the volume, the beautiful notes of music or the words of the speaker

are brought out clearly. And for long distance reception, the Headset is not only reliable but is far more satisfactory.

Buy a good Headset such as the Cannon-Ball. It is extremely sensitive. Its light weight helps to make it comfortable. And it is guaranteed by a well established, reliable manufacturer.

Cannon-Ball \$3.50; Cannon-Ball Junior \$2.75; Grand \$4.75; Cannon-Ball Loud Speaker \$12.50. At your dealer's.

CANNON & MILLER COMPANY, Inc.

SPRINGWATER, N. Y.

RADIO BOOKS AND PATTERNS

The Consrad Company has a complete line of radio books and patterns for ns or operates a radio receiver or transmitter. WRITE FOR FREE CATALOG

The Consrad Company, Inc., 233 Fulton St., New York City,

Hartmann, North Bergen,
Becker, Newark, N. J.
Becker, Newark, N. J.
Ce Muller, North Bergen, N. J.
Kucker, Brooklyn, N. Y.
G. Tapper, Lakewood, N. J.
Merker, Wellsville, N. Y.
W. Smith, Utica, N. Y.
Park, Md. rker, Wensy... V. Smith, Utica, N. & yle, College Park, Md. Rice, Jr. A. Pyle, College Park, Ma. lerbert Rice, Jr. dward Schultz, Bethesda, Md. Paradee, Baltimore, Md. 1 W. Weel, Baltimore, Md. R. Albert, Baltimore, Md.

Con P. Dilling Con Market Billing Van Helm Der Dilling Con Helm Billing Van Helm Billing Va

W. U. Chwiced, constant of the Consider of the Consideration of the

Level Book P. Comment of the Comment ZONE 7



Re*creation is radio's destiny fulfilled



is so excellent it cannot be matched. A genius, he is

Now and again the world applauds an artist whose work

Rola Cabinet Re*creator,

called. solid mahogany, \$46 In the world of radio there are certain reproducers of such outstanding merit they, too, have won the fame of genius. Rola Re*creators, they

The Rola is created for the reecreation of voice and music. From the time the first fine materials reach the hands of the Rola Rola Re*creator-painstaking care and the true craftsman's love for his work color every operation. Assuring precision. Approaching perfection. Small wonder that the Rola alone is called a Re*creator. And

that it charms and captivates all who hear it. The Rola Re*creator is the invariable choice of people who love fine music. Who can be satisfied with nothing less than Rola's realism and sympathetic, truthful performance. Their instant acceptance of the Rola Re*creator is, after all, its final test and highest praise. The Rola Company, 4250 Hollis Street, Oakland, California. Marketed nationally through

BAKER-SMITH, CO., INC. Head Offices, Call Building, San Francisco Branch offices in following cities:

Chicago, 30 North Dearborn





MOCKING BIRD UNIT

\$7.50

All fans remember the pioneer of ad-

You cannot equal the tone reproduction of the Mocking Bird Unit attached to the phonograph. Radio assumes new delights-purity of tone and the remarkable volume (adjustable) are marvelous.

The handsome Mocking Bird Cabinet at \$30 list is a not satisfied.

> MORRISON LABORATORIES, Inc., 339 E. Jefferson Ave., Detroit, Mich.

Morrison

Dealers

Loud Speaker

SEE YOUR TUBES TESTED



Set Mfrs.

There's only one way to be sure your tubes are RIGHT and that's to see them tested before your eyes. Formerly, this was impractical. Tricky curves had to be figured. But times have changed now that the Superadio Dynometer is on the job.

This Dynometer is direct reading. Tells if tube is gassy, underaged, etc. Easy to operate. Positively measures the power of any tube on the market.

Dealers-Write for Details

SUPERADIO KIT NEW-SUPERADIO Reactodyne

DE WITT LA FRANCE CO., INC. 54 Washburn Avenue, Cambridge, Mass.

Boston Representative
Martin, Hartley & DeWitt Sales Co., 99 Bedford St. William A. Welty & Co., 36 So. State St

FORMICA RADIO PANELS

TUBES AND RODS WRITE TODAY for your copy of our new catalog listing and pricing 3384 different sizes and kinds of Formica Radio Panels, 126 differ-ent sizes of Formica Tubes, and 21 different sizes of Formica Robs.

DRILLING-ENGRAVING STARRETT MFG. CO. 520 S. Green St. Chicago, III.



- Louis A. Berchuds, New Brighton, P. L.

- Louis A. Berchuds, New Brighton, P. L.

- Joe M. Kullaky, Minerwille, P. L.

- Low M. Kullaky, Minerwille, P. L.

- Low M. Martin, M. Martin, P. L.

- C. L. Wijhelm, Wilmington, D. L.

- C. L. Wijhelm, Wilmington, D. L.

- C. L. Wijhelm, Wilmington, D. L.

- F. Griffith, Wilmington, D. L.

- F. Saldman, West New York, S. J.

- Saldman, West New York, S. J.

- Saldman, West New York, S. J.

- Cha, E. Schulze, Chica City, N. J.

- Cha, E. Schulze, Union City, N. J.

- Cha, E. Schulze, Union City, N. J.

- Sanger, Hump on C. N. S.

- Sanger, Hump on C. N.

- Sa

ZONE 8

Wm. C. Magargal, Bakersfield, Cal.
Wm. S. Hunter, Goodyear, Com.
Wm. S. Hunter, Goodyear, Com.
P. C. Bonner, Baltimore, Md.
Joseph L. Hultman, Malden, Mass.
Whr. L. Lange, Nevarde, N. J.
E. Bonger, Union City, N. J.
E. Borger, Union City, N. J.
E. Hedrey, Tenneck, N. J.
L. Cannord, Red.
Left-lower, Tenneck, N. J.
L. Stanford, Red Bank, N. J.
L. Stanford, Red Bank, N. J.
L. Stanford, Red Bank, N. J.
W. C. Smith, Pleasantville, N. J.
W. C. Smith, Pleasantville, N. J.

Pfanstiehl Introduces 6-Tube OVERTONE Receiver

With Translucent Station Finder

AST year Pfanstiehl perfected the Overtone Receiver—an accomplishment of the first importance, which radio engineers had vainly attempted hitherto. He did so by eliminating all clashing of radio energy inside the set, thereby insuring a smooth, forward flow of the radio stream from circuit to circuit. The super vibrations of radio energy are thus kept intact, exactly as received, and there is no blurring or marring of the resulting overtones which

This year he went a step further. He still further protected the overtones by an overtone loudspeaker inbuilt and sympathetically adjusted to the receiver itself. Modulation is made perfect. Even through a detached speaker the tone was far superior to any other obtainable in long distance reception. Now it is

Single Dial More Efficient Than Any Multiple Control

His single dial control immeasurably simplifies radio. It will give it a new popularity with the great mass of home users who are inexpert and dislike complicated tuning. It has been made possible by the very same mastery of radio energy in and between circuits which perfected overtone reception. With no leakage of energy to disturb the electrical characteristic of the radio stream on its way through each circuit, THERE ARE NO INEQUALITIES. Each circuit is electrically like every other - ALL tuned by one turn of the Pfanstiehl triple unit condenser.

Without the simple, equalized circuit of the Pfanstiehl system, no efficient one dial control is possible in a radio frequency set. Stray energy and the devices employed to neutralize it create inequalities in the circuits which THEN

REQUIRE SEPARATE TUNING.

It thus becomes apparent how important an advance Pfanstiehl made in simplifying the radio frequency circuit and eliminating all compensating or neutralizing devices. It made possible perfect overtone reception, simple and dependable operation and now-single dial control.

Actual Wave Length GLOWS from Illuminated Dial - No Scale Necessary

An unique feature of the overtone panel in all models is the illuminated station finder disc which revolves with the tuning knob and registers in actual wave-

lengths rather than in arbitrary numbers. The disc is concealed except for a small opening in the panel where the wavelength appears, the disc being translucent and illuminated from behind. Extremely convenient; enables tuning to be done in the dark; shows whether power is on or off; adds a brilliant touch to the panel asstruction, finished like rest of cabinet. Much handsomer than bakelite or rubber. Control and volume dials of inlaid wood. All exposed metal parts gold plated.

An Exclusive Franchise The Pfanstiehl line is sold through are thus protected against unfair competition and price cutting. Whatever good-will the dealer or jobber builds up for Pfanstiehl is the line aggressively with the co-

For further details, address PEANSTIEHL RADIO COMPANY 11 South La Salle Street, Chicago, Illinois

Prices West of the Rockies Slightly Higher









8-A low priced 2-Dial 5-receiving Set, Pfanstiehl quality jout. Price \$85.00 (less acces-

ont SC—Two-dial 5 Tube Rece Set, demountable from consider, permitting use on floor or tab errone Speaker built in. Pri 5 on (less tubes and batteries).

M2 PARTS

Again



Bakelite Coil Form Unwound with rotor, springs and six con-tacts. Price ...\$1.25

Six Contact Bakelite aductance Socket \$1,25

INTERCHANGEABLE INDUCTANCES

Low Loss Coils for any purpose-for all waves from 50 to 550 meters-with SM 306 or 311 (.00035) Condensers. Price-All Types \$2.50.

SEE these and other SM Parts at your Desier's. Circulars sent upon request. SILVER - MARSHALL, Inc.,

Silver-Marshall leads with the finest straight line frequency condensers yet produced. All losses - dielectric, eddy-current, surface-resistance - are unbelievably low. Six sizes both SLW and SLF priced from \$4.50 to \$6.00.

Guyed Sockets
A radically new cushioned socket for all UX or UV tubes except UV 199. Price...\$1.00



116 S. Wabash CHICAGO Avenue



RADIO CABINETS

For your RADIO SET

Get an MBG Cabinet for your set today. Any our cabinets are strongly made from beautifully

Radio Cabinet Department **Express Body Corporation** 42 Lake Street Crystal Lake, Ill.



CONSOLE CABINET

-

Depth Bat. Comp.
10% 10x11x10"
Price \$17.50
fit 6-tube Atwater-

Depth Bat. Comp. 10%" 10x11x36" Price \$20.50 Mounting boards, each 50e Shipped set up complete, one to a cartion.

Prizes For You Boys and Young Men-You can earn dandy prizes and liberal commissions by selling and delivering our popular magazines in your spare time. No experience or money is necessary. We furnish all supplies and tell you just how to start. Write to-day. E. J. FOLEY, Department RN-11, Experimenter Publishing Company, 53 Park Place, New York City

18— Jack Dobon, Rackelli Cerre, N. Y.

18— Jack & W. H.; Killen, Salad Yerk, N. Y.

18— Jack St. H.; Killen, Salad Yerk, N. Y.

18— Jack St. H.; Saladana, N. Y.

18— Jack St. H.; Saladana, N. Y.

18— Jack St. H.; Saladana, N. Y.

18— J. H.; Mandara, P. R. Rachette, N. Y.

18— J. H.; Mandara, P. R. Rachette, N. Y.

18— J. H.; Mandara, P. R. Rachette, N. Y.

18— J. H.; Mandara, P. R. Rachette, N. Y.

18— J. H.; Mandara, J. R. Rachette, N. Y.

18— J. H.; Mandara, J. R. Rachette, N. Y.

18— J. R. Rachette, N. Y.

18— J. R. Rachette, R. R. Y.

18— J. R. Rachette, R. R. Y.

18— J. R. Rachette, R. Y.

18— J. R. Rachette, R. R. Y.

18— J. Rachette, R. R. Y.

18— J. R. Rachette, R. R. Y.

18— J. Rachette, R. R. Y.

18— J. Rachette, R. R. Y.

18— J. Rachette, R. R. Y.

ZONE 10

66—Mr. K. Diversort New York Cry.
67—Mrs. K. Diversort New York Cry.
67—Thomas E. Serkort, S. Willer, Man.
1—I. P. O'Comme, New Hayer, Comp.
1—I. P. O'Comme, New Hayer, Comp.
1—I. P. O'Comme, New Hayer, Comp.
1—I. Serkort, S. Willer, Man.
1—I. Janker, S. Willer, M. S. L.
1—I. Janker, S. Willer, M. S. Will

ZONE 11

I-L. H. Greason, Newark, N. J. 1A—Geo, Jarman, Groveland, Mass. 2—Redford S. Smith, Stratford, Conn. 3—Chas, Livingston, Plainville, Conn. 4—M. P. Kuch, Rockville, Conn. 5—C. F. Riecher, Plainville, Conn.

Equip your set with **Balkite Radio Power Units**

They provide unfailing, uniform current for both circuits



Balkite Battery Charger

Price \$19.50 West of Rockies, \$20 In Canada, \$27.50



Balkite Trickle Charger

Charges both 4 and 6 volt radio
"A" batteries at about .5 amperes.
Usable in 3 ways: (1) As a regular
charger with a low capacity storage harger with a low capacity stors, actively for sets now using dry cel 2). With storage battery sets we tubes, Furnishes more curreharms and by 6 dry cell or 2 storage that the storage for the set of the storage for sets of the storage for sets ontinuous charger for sets ontinuous charger for sets of the storage batter between the storage for sets of the storage for sets or 50 cycles. The storage for sets or 50 cycles or 50 cycles are set of the storage for sets or 50 cycles or 50 cycles.

West of Rockies, \$10.50 In Canada, 815


Equip your set with Balkite Radio Power Units. They improve and simplify radio reception. With their use your current supply is unfailing and always exactly what is required for each circuit. They reduce

the amount of attention you give your set. The Balkite Battery Charger is entirely noiseless in operation. It can be used while the set is in operation.

The Balkite Trickle Charger is especially adapted to sets of small "A" current requirements - any dry cell set, and storage battery sets of few tubes. It enables owners of sets now using dry cells to make a most economical installation.

Balkite "B" II is also well known, It was the outstanding development in radio last year. It eliminates "B" batteries and supplies plate current from the light socket. It fits any set.

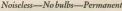The new Balkite "B" at \$35 is especially designed to serve sets of 6 tubes and less. With such sets it will perform exactly as does Balkite "B" II with sets of larger "B" current requirements.



All Balkite Radio Power Units are based on the same principle. All are entirely noiseless in operation. They have no moving parts, no bulbs, and nothing to adjust, break or get out of order. They cannot deteriorate through use or disuse-each is a permanent piece of equipment with nothing to wear out or replace. They require no other attention than the infrequent addition of water. They do not interfere with your set or your neighbor's. Their current consumption is remarkably low. They require no changes or additions to your set.

An"A"battery, a Balkite Charger and a Balkite"B" constitute a complete, trouble-free radio power equipment, one that is economical, unfailing in operation, and eliminates the possibility of run-down batteries.

Manufactured by FANSTEEL PRODUCTS COMPANY, Inc. North Chicago, Illinois

Radio Power Units



U. S. Patent May 27, 2224



Balkite "B"

Eliminates "B" Batteries. Sup-plate current from the light so Operates with either storage tery or dry cell tubes. Keeps circuit always operating at r mum efficiency, for with its us-plate current models.

year.

A new model, designed to serve sets of six tubes or less, Size 8½ in. long, 8 in. high, 3½ in. wide. Occupies about same space as 45 volt dry "B" battery. Operates from 110-120 AC 60 cycle current. Special model for 50 cycles.

Price \$35 In Canada, \$49.50



Balkite "B" II

Price \$55

the Gould Storage Battery Com-pany, is equipped with a special Balkite Radio Power Unit.



"The Song-Bird of Loud Speakers!"

HORN The Horn is made of treated FIBRE that HURN ness, softness, oweretsess. It actually abortly hardly course rounds. It is NON-RESONATING, NON-VIBRATING, IT AMPLIFIES and BEAUTIFIES, and recreates FAITHFULLY and CLEARLY the high notes of the singer, the revest moses of

the crater-and delightful richness of concert music.
ORIOLE is like having a SONG-BIRD in your home.

Usually sells for \$20. We have just 792 of them. OUR PRICE WHILE THEY LAST. \$13.85 Sent on 10.704 Y FREE TRIAL! You pay only \$1 Now! TO TRIAL THE TRIAL THE

\$3 A MONTH

or, if you wish to pay eash, take \$1.00 discount and send \$1265 ORDER NOW! ONLY 782 AT THIS PRICE! SEND ONLY \$1 NOW! MAIL THIS ADV. TODAY



365 Washington Street, Boston, Mass.

Genlemm: Please and me \$13.85 "SONGSTER" Leost-Speak. et actors \$1 Eart payment. If I am atthibid after 10 20.88 "FELALA", I have the privilege of paying for it at the \$12.60 in FULL PAYMENT. deboting \$2.29 and seeding \$12.60 in FULL PAYMENT.

Please write PLAINLY! Tear this Advertisement out now! If you wish to tell us something about yourself, it will be appreciated. RN-11-25

Eliminate Interference

When set up, the Bodine Folding cop is two feet square. The wire is couble-wrapped in green silk and the rame is a beautiful brown mahegany mish. The Bodine casily folds into a box measuring only 5½ x 6 x 18 notes.

BASKET WEAVE

The silk insulated, stranded wire is basket wound, preventing losses and delivering more based of the silk of the

BODINE ELECTRIC 2240 W. Ohio Street

Chicago : : : TII.

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

Radio News for November, 19,

- Linal Leys, New Harry, Com.

- Linal Leys, Ley

Go-Louis Senn, Merr Belleid, Man.

Sour State Weig Garger, N. S., Cas.

1. H. S. Oldinz, New Garger, N. S., Cas.

1. H. S. Control, 1. H. H. S. Cas.

1. Yes and Company of the Control of



Your set at its best always with a **Super-Ducon**

-the "B" Battery Substitute

When guests come in, your set is ready. No run-down "B" batteries—no batteries, being recharged. There's the Super-Ducon plugged into the light socket—ready to deliver a steady, silent flow of current.

It's the perfect substitute of "B" batteries equipped with a specially designed RCA tube (Rectron UV-196) that has an average life of more than 1000 hours. It's a thoroughly efficient device—made and backed by Dubilier, And it keeps your set at its best!

Tested and listed by the National Board of Fire Underwriters.

Dubilier CONDENSER AND RADIO CORPORATION



Price \$47.50

Write for descriptive booklet No. F-3 "The Super-Ducon and how to install-it." 4377 Bronx Boulevard New York City

A Set Is As Good As Its Dials





O BACKLASH is possible in the new Fynur Vernier Control. There are no gears to mesh, so there can be no lost motion, and

If you want the utmost accuracy in reception, and unless you have it you cannot expect the best results from your set, use Fynur dials. and a greater and more lasting satisfaction than any other dial on the market. Simple in construction (can be mounted without dissembling), beautiful in appearance, (black or mahoganite Bakelite). If your dealer cannot supply you, write us.

Your set can be no better than its dials, so have the best set by hav-

AUGUST GOERTZ & CO., Inc. 270-286 Morris Ave., Newark, N. J.

SET MANUFACTURERS will find that Fynur dials will improve the appearance as well as the efficiency of their products. In-

"Flat" Plug CARTER DO

FYNUR VERNIER CONTROL

NEW CARTER ITEMS

Original - Exclusive



A red Pilot light shows when your "A" battery is

"On"-no excuse for going

away and leaving tubes burning. Single hole mounting, quarter turn switch - compact. Simple,



\$1.75

Eliminates shadows and Fits snugly against panel. permits exact readings for the snugly against panel, or logging your dials. Quarknobs and Dials and adds ter turn snap switch come to the appearance of your bined with the light. Persits light to be to the permits light to be to the source. Unsightly tips concealed. if desired when set is oper-

These and other new and original Carter products can be seen at your dealers. Ask him about them.

Volts Battery Drain

MUSSET.

LATEST WHOLESALE MDARD RADIO CO., 108 East 13th, Kansas City, Mo



50-Joseph L. Romes, Jamies, N. Y.

50-Joseph L. Romes, Jamies, N. Y.

50-Richel T. Style Bend Nock, L. I.

50-Richel T. Gender, L. L. I.

50-Richel T. Gender, L. L. I.

50-Richel T. Bertman, P. Forest Hills, L.I.

50-Possible J. Bertman, P. Forest Hills, L.I.

50-Possible J. Bertman, P. Forest Hills, L.I.

50-Possible J. Bertman, P. Forest Hills, L.I.

50-Richel T. Gender, Forester, L. I.

50-Richel T. Gender, Forester, L. I.

50-Richel T. Gender, Richarder, L. I.

60-Richel T. Washer, Richarder, L. I.

60-Richel T. Washer, Asheris, L. I.

60-Richel R. Washer, Asheris, L. I.

60-Richel R. Washer, Asheris, L. I.

60-Richel R. Washer, Marchel R. I.

60-Richel R. Washer, M

The Inventions of Reginald A. Fessenden

steam prime mover, the steam turbine, which Parsons was operating at Newcastle. This I did, and concluded that it would take the place of the steam engine for central station work. A side trip to Cam-bridge was very interesting. J. J. (now Sir Joseph) Thomson was found in his laboratory, the Cavendish laboratory where Maxwell had worked. Thomson showed me some of Maxwell's apparatus, and I saw some of Thomson's experiments on vacuum tubes. I mentioned some work I had done on an electric furnace, in which the graphite transformer and the heat so produced and Then came up the question of the electrowith the electrostatic doublet theory, but just got to work, and I was invited to go along. We came into a dark room

RETURN TO U. S. AND PROFESSORSHIP AT PURDUE

AFPURDUE

1892 was a "panie" year and on returning to the U. S. I found the company in financial difficulties. No part of the expense of the visit to England was refunded to me, the share in the company agreed upon when I resigned my position with the Westinghouse personal expenditures made in connection or what he did be forgotten. He had se-cured Dr. Goss for the Mechanical Engi-neering department, and Goss had made it the best in the world at that time. He next the best in the world at that time. The next wished to develop the Electrical Engineering department. With the appropriation he ob-tained I equipped the electrical laboratories with everything fundamentally necessary for



It IS true!

188 times the energy... and there is absolutely nothing else at all like

PENETROLA

Without Penetrola the signal intensity of WOAI was 11, on the Audibility Meter an impartial precision measuring device. With Penetrola the signal intensity of WOAI jumped above 2000—188 times the signal strength!

Without Penetrola the scientifically measured signal intensity of WCAL was 35, scrambled with WCBD at 29. With Penetrola WCAL went to 2000+ and WCBD to zero—selectivity with a vengeance!

This is just exactly the sort of thing any Penetrola demonstration will show you on any set with any number or arrangement of stages. The wanted station is immensely intensified; interference is overwhelmed by Penetrola. There is so much volume available for the most distant signals that a shorter aerial may be used, curing excess static. Your set is stopped

sexcess static. Your set is stopped from radiating, and is stabilized. It is needless to operate near the oscillation point. And dial readings stay substantially the same. Radio principles known to be of immense promise, but hitherto clausive, are now auccessfully applied by Walbert Penetrola. The widely heralded Isofarad Circuit, latest development of Walbert engineers, is the foundation of Penetrola performance. Here is one tradio appliance literally unduplicated in any way by anybody, because there is no other Isofarad circuit. Nor is there any substitute for Penetrola action, which amplifies ahead of the detector entirely, strengthening signals which would otherwise never be detected! Remembe, signals too weak to detect cannot be amplified by any means placed beyond the detector.

In a few moments any receiver, however costly, can be transformed with Penetrola. Or anyone can quickly assemble the

Penetrola kit and obtain amazing Penetrola results most economically. The Penetrola price buys performance which cannot be obtained with any amount of investment in a receiver alone.

Walbert Made It FIRST

WALBERT

Manufacturing Company, 923 Wrightwood Avenue, Chicago



A DETECTOR

that won't burn out

G & S new SILK CORE DETECTOR will outlive your radio set covers all points of contact and sures constant contact with en-

Adjustable, with spring tension that works-and absolutely in-

ter and other details of manufacture absolutely protected by

\$1.50 at your dealers or send your name and address to Baker-Smith Co., Inc., and we'll tell you where you can get this wonderful detrector. NOT SOLD by madi, except through dealer, jobbers-Address nearest office.

G. & S. RADIO RESEARCH LABORATORY

MARKETED NATIONALLY BY BAKER-SMITH CO., Inc.

New Call Building, San Francisco BRANCH OFFICE ADDRESSES

New York City, 1270 Broadway

Chicago, 30 North Dearbora Street
Dearver, McCiliatock Building
Sait Lake City, Atha Building
Los Argeles, 443 5o. San Pedro Street
Portlands, Ores, Henry Building
Seattle, L. C. Smith Building
Vancourer, B. C., 179 Pender Street, W.



ent Velts... 5.0 8.0 8.0 ent Current. 6.25 .01 .01 .03 Veltage....20 to 120 20 to 80 20 to 80 de with Brass and Bakelite Bases

(E(0

Every tube backed by a guarantee that's backed by a company of established reputa-C.E. MANUFACTURING COMPANY, Inc. 702 Eddy Street, Providance, R.I. Trade Supplied through Jobbers Only!

Jobbers-Write for details and prices. Manufacturers—Ask us about SPECIAL MATCHED tubes.

Serve equally well as radio frequency ampli-

CeCo Tubes make any good circuit better.

Young Man — Turn Your Spare Hours Into Money!

Earn big profits, prizes, and awards selling RADIO NEWS. SCI-ENCE & INVENTION, THE EXPERIMENTER, and MOTOR CAMPER & TOURIST in your neighborhood. We train you as our salesman and pay you liberally for your time. Write at once and we will help you get started. E. J. FOLEY.

THE EXPERIMENTER PUBLISHING CO.,

53 Park Place, New York, N. Y.

the work, paying especial attention to ap mathematical work was emphasized, the students being supposed to enter the senior year with a fair knowledge of differential

A certain amount of time was available A certain amount of time was available for personal scientific work and also where students had no preference of their own as to thesis work, suggestions were made

MULTIPLEX RESONANT TELEGRAPHY
—ELECTRIC ANEMOMETER, THEORY
OF MICROPHONE

The work on multiplex resonant telegraphy was taken up again and carried to a

current necessary to do this depending upon and being a measure of the wind velocity; it was standardized by fastening it to a rotating arm,

Another set of tests was made to de-May, 1897. Other work on this line will be referred to later,

FESSENDEN FILAMENT GALVANO-

Perhaps the most important development was the invention of the filament galvanas though with, say 1,000 turns, there was 1,000 times the force of a single turn, they weighed more than 2,000 times what a single half-turn of straight wire did, also optical calculations showed that the motion it much less sensitive and accurace man me original form above described, which has been used, with gold wire 1/10,000 inch in diameter, for recording each individual wave of wireless messages and for recording fre-quencies up to 50,000 per second and more. It also forms the one type of shutter of late a light beam in one-millionth of a second, and a rapid shutter of this kind is necessary for the operation of the pallo-graph, or "radio-telescope."

A theoretically, and practically important investigation was the experimental verifica-tion of a theorem of Fourrier's, given in his "Theory of Heat," that if a hot body were surrounded by a series of thin sheet metal spheres or boxes, each shell or box would permit only one-third of the heat reaching it to pass outward. This theorem



Revolutionary Method to "Build Your Own"



SHALL WE SEND YOU ALSO New 1925 "Rasco" Catalog No. 12

This Free Book Tells

ON'T EVEN THINK OF BUYING SET OR KIT BEFORE YOU SEE OUR KIT CATALOG

RADIO SPECIALTY CO NEW YORK CITY

Book explains what you want to know

RADIO SPECIALTY CO., Kit Div. 679Y.
245) Greenwich St., New York charge or obligation, the control of the contr

The Unit of Absolute Dependability

MacFADDEN B-POWER GENERATOR

NO ACIDS NO ODORS NO NOISE



Operates on 110 V. 60 Cycle A.C. Current, Turn on the juice and forget "B" battery troubles for life.

Furnishes an unfailing supply of correct B-Power to any set.

Manufactured by an organization of radio engineering and mechanical experts. Sold under a guarantee that really guarantees. Dealers can sell this dependable unit with assurance for continued satisfaction.

IT'S A REAL JOB

MacFADDEN & COMPANY, Inc. 2200 Arch Street Philadelphia, Pa.



To the Radio Dealer:

Let us explain how you can make the sale of our publications a worth while, well paying part of your business. Write now and prepare for the Fall and Winter trade

The Experimenter Publishing Co.

53 Park Place, New York City

was confirmed and other data on heat radiastatic volumeter. In all these investigations, with the exception of that on the multiplex

that time which had defeated Chicago and it fell to my lot to look after

and perhaps more ingenuity was exercised in keeping the team in shape than in the electrical laboratory, for the rules were class work could stay on the team, and if he fell behind special coaching must be ar-ranged for and professors must be persuaded

COLUMBIAN EXPOSITION OF 1893 for the seals of his incandescent lamps, on for the seals of his incandescent lamps, on account of patents. The invention previously referred to, of silicon iron and iron nickel alloys for sealing in wires had been tested and had proved that such seals could be made and would remain air-tight. But Westinghouse nad informed him that he had a particular regard for me and wished, if possible, that I should be offered the newly created chair of Electrical Engineering at the University." A little later a letter was received from Mr. Westinghouse enclosing a check for \$1,000 and stating that he

that Dr. Holland's offer was accepted. On the way to Pittsurgh a stop was made at Chicago, where there was an innection with the Exposition and had the pleasure of meeting Helmholtz, then quite old and apparently a little bewildered by the large scale power installa-tions, Preece, Mascart, Rowland and others and of being appointed with Preece, Sie mens and Kennelly, on the committee on



No Set is Better than its Parts

NLESS each contributing unit performs its task without flaw, the most perfect results can never be
achieved. The amazing excellence of radio performance
is due in no small measure to the contributions of the
Pacent organization of distinguished engineers, who have
provided either first or best, many improvements in radio
receiving sets.

Pacent Parts are now used as standard equipment by forty leading set manufacturers. This fact is a clear indication of the prominent place held by Pacent Parts in the radio field. Whether you buy a set or build one,

look for the Pacent trade mark on every important unit. It is your assurance of highest quality and performance.



Write for our New illustrated catalog.

PACENT ELECTRIC COMPANY, Inc.

You can now choose from forty sets, the manufacturers of which have selected Pacent Parts

Charles Freshman
Co.
Stewart Warner
Speedometer Corp.
Crosley Radio Corp.
Ambler-Holman Co.

Pathe Phonograph and Radio Corp. Ware Radio Corp. R. E. Thompson Mfg. Co.

Ambler-Holman Co.
Bristol Company
Magnavox Company
F. A. D. Andrea, Inc.
Western Coll & Elec.
Co.
Co.

Executive Offices 91 Seventh Avenue

かんしんくん

New York City

Branches:
Washington
Minneapolis
Boston

Chicago Birmingham Pacent

}->\$->\$->\$-Branches:

Branches:
Philadelphia
St. Louis
Buffalo
Jacksonville
Detroit
Pittsburgh

Canadian Licensees: White Radio Limited, Hamilton,

PRECISION MEANS

HARMONY

PERFECT precision in every part reduces loss of energy—

PERFECT precision in every part reduces loss of energy—makes it possible to pick up, and build up, weak signals from far distant stations, and to reproduce such signals with amazing volume, perfect clarity and fidelity to tone.



Model J - 75 S P. \$75

A demonstration proves the superiority of this 5-tube, tuned radio frequency receiver. Encased in rich mahogany cabinet. Price, without accessories \$75.00

JONES PRECISION PARTS

Improve the quality of any home made receiver. Ask your dealer for the genuine precision parts made by Jos. W. Jones, inventor and producer of precision instruments and parts for over 28

JOS. W. JONES RADIO MFG. CO., Inc. 40-46 West 25th Street New York

JOS. NES

Branches: Philadelphia, Boston, Chicago

PATENTS WRITE for our Form

BLANK" before disclosing inventions. Send
model or sketch and description of your lovention for our INSPECTION and INSTRUCTIONS FREE. TERMS REASONABLE. Electrical and Radio Cases a specialty.

VICTOR J. EVANS & CO. 919 NINTH ST., WASHINGTON, D. C.

RADIO MASTS—FLAG POLES
Our dearble, reconsistive matts are units from carreliable to the property of the prope

Insure your copy reaching you each month Subscribe to RADIO NEWS - \$2.50 a year Experimentar Publishing Co. 53 Park Pl. W. V. C.

standards of electrical resistance. The Exposition itself was the most beautiful I have ever seen.

UNIVERSITY OF PITTSBURGH AND ALLEGHENY OBSERVATORY

On one side of the University was the Allegheavy Obervatory where, flanks to the Allegheavy Obervatory where, flanks to the Allegheavy Obervatory where and the Allegheavy Obervatory where the Allegheavy of the Allegheavy of the Allegheavy of the Allegheavy of the State of the Allegheavy of the State of the Allegheavy of the State of the Allegheavy of t

various shapes on long arms rotating on you of a poin, and meaning by very innecesspecial. Langley found that the lift, was a proper or the langley found that the lift, was clearly compared to the large that the lift, was clearly compared to the fair that the innerial of the air had not been taken into account, and the large that plan for mapping the surface of the unit plan for mapping the surface of the large that plan for mapping the surface of the large that the plan for mapping the surface of the large that the rotation welcody of the different pertons of large are large to the large that the large was the large that the large that

On the other side of the University were presented of the Department of the Control of Control

INALD A. FESSENDEN, 45 Waban Hill Road, Chestnut Hill, Mass



There's a Lot of Tuning In the Dial

Fans are logging many new stations that were unavailable before by equipping their

PROUDFOO1

100 to 1 ratio (decimal system) permits iner readings than can be obtained with my other dial. Fits all condensers. 1-9/16x /16 in, metal case contains all mechanism of fix into kinh of 4 kin dial illustration

CRUVER MANUFACTURING CO.



THE SIMPLEST PRACTICAL RADIO SET MADE

\$1<u>00</u>

The RADIOGEM

The imploit radio outili made-set as pearlies as the most openity. A crystal receiving at the you can openit and robo even though you know a considerable about radio. You receive U.ALTOCIEM unassembled, between the a clear conclet, and early construct the set, using on your lands and a stissors. The outilit comprise a construction of the accessors where contact potants, detertin misees take as which to wind the cell, etc., etc. The interesting how compliant gains; and completely of

THE RADIOGEM CORP.

Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park PL, N.Y.C.



De Luxe Model The Marvelous Tone Inexpensive Receivers in Solid Mahogany Cabinets

The combination of Rico Celluweld Low Loss Coils and Variable Condensers is made mechanically perfect. The Coils are welded firmly to the support of the rotor plates, a new principle. (Patents Pending.)

Selective and non-oscillating, the Rico "Auto-Balanced" Tuned Radio Frequency Set accomplished by carefully setting the neutralizing angle of the Coils at the factory; remains permanent due to the Celluweld process.

These and other features are all combined to give the radio buyer the very finest in improved 1925 Receivers.

Type A-RICO-DYNE STANDARD The Rico-Dyne Standard embodies all the features listed

above and is enclosed in a beautiful solid mahogany cabinet. presenting a beautiful appearance in any home,

Type B-RICO-DYNE DE LUXE

any cabinet, but extra space is provided for the wonderful "Melotone" loud-speaker unit and all batteries-what more could one ask?

The Masterpiece of Them All

All Rico-Dyne Receivers are now being equipped with the new Straight-Line Frequency Condensers.



Melotone Unit

The perfect reproducing unit-for loud speakers, phonographs, etc. Has all the qualities of \$10 and \$12 units.

Price - - - \$7.50

Rico-Phones

None Better-Don't pay more-

A headset of real value.

- \$2.50 List



DEALERS-JOBBERS-DISTRIBUTERS

RADIO INDUSTRIES CORP. 131-133-137 Duane Street, New York, N. Y. Export (Ricotrade, N. Y.) Cable Address Bently Code Used



Used by the United States Navy and Signa Corps for over nine years. Dilecto is the strongest, safest radio panel that can be made. Look for the identifying "Re Stripe" that sets apart Dilecto from it

THE CONTINENTAL FIBRE CO.
FACTORY: NEWARK, DELAWARE
Service on Dilecto, also Contex, Conite, and
Vulcanized Fibre, from:

NEW YORK
250 Park Ave.
CHICAGO
Wrighty, Hids.
Pirresult Bank Bidg.
Parkers Bidg.
Parkers

Dilecto (distinguished by its red stripe)



→8(A)> A. C. POLARIZER
Uses Electric Light Current—saves you recharging exect and bother. First small east at Blac is last. Thousands are already existing angularities recommended are already existing angularities.

BLACK BROS. INC.,
Brokenst God H. Ob Hill. Please Brok BLAX to rece

919 Black Bidg., Les Angeles;
Enclassed find \$1.09 bill. Please Rush BLAX to r
Name.

Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

Plastic Radio by the Kluth System

(Continued from page 601)

ment has much to commend it and has been found to work without any hirch, but the setting up of a phase difference has proved to be atterly unable to convey an impression of plastic hearing. The following instance will serve to make this clear:

If the transmitter be operated, say, on a 500-meter wave there would be as much as 600,000 vibrations per second, corresponding to a relatively small number of

It the transmitter be operated, say, on a 500-meter wave there would be as much as 600,000 vibrations per second, corresponding to a relatively small number of accountic vibrations, so that each high frequency vibration would carry only a minute portion of a sound vibration. The arrangement above described will accordingly enable a sound vibration to be shirted at most by a few thousandits of its length.

This falters to obtain an adequate planeshifting by acting on the high frequency shifting by acting on the high frequency problem as devised by Mr. Kluth, &c. a. A haza displacement in he Idephone current. Telephone current, of coarse, have the haza displacement in he Idephone current, and a telephone receiver; for the note A, for instance, it is 4.8. This sound could accordto a libiting of about 100 deepers is quite by a 180-decree plane shifting. However, a shifting of about 100 deepers is quite particularly and the control of the conlaring. The accounts' otheration correspositing to note A is about 20½ inches hearing. The accounts' otheration correspositing to the notal distance of the two eart) possing as a wave-length of 20½ inches correspond degree plane displacement. If on the plane degree plane displacement. If on th

USE OF BEFARATE INDUCTION CUBERSY. As regards, not, the means to be adopted in producing a place displacement in a four current, the most obe adopted in producing a place displacement in a four current, the most obvious would be the incurrent flow. The producing the current flow of the current flow of the current flow, the current flow of the current flow, the current flow of the cur

of the current in the coil of electromagnet B will decrease. On the other hand, when the current in the secretarian return the coil of electromagnet B will decrease. On the other hand, when the current in A is decreasing, membrane M will come close to electromagnet B, causing the current in the latter to augment. In fact, the original telephone current, though with a plane displacement of about 180 degrees is thus produced in electromagnet B. It now the current passing through A is listened to the current passing through A is listened to generated in B through the other head phone, there will still be an impression of



Made according to Bureau of Standards specifications for lowest losses and best electrical characteristics.

space the stations over the dial, while keeping the condenser as small as a straight-line capacity model.

Atumnum stator piate, exactly the same as used in the new DUPLEX Straight Line Frequency condenser, sent on request. Write for one today. Learn the secret of DUPLEX superior construction.

Duplex Condenser & Radio Corp. 52 Flatbush Avenue Extension, Brooklyn, N. Y.



PATENTS If you have an favorities and design to account the state of the state of

and the suide book, "HOW TO GET YOUR STATE AND A STATE OF THE SET THE

RANDOLPH & CO., Dept. 459 Washington, D. C.

"PILOT" CAPACIGRAD Trade Mark Reg. Appl. For

Straight Line FREOUENCY Condenser 13 Plate 300 M. M. F.



PILOT ELECTRIC MFG. CO. Inc., 323 Berry St., Brooklyn, N. Y.

Made By America's Greatest Radio Parts Manufacturer



Elaborate console models with loud speakers built right into cabinets of genuine mahogany and walnut. ALL SETS GUARANTEED. Coast to coast receiving range. Catalog also contains everything in radio supplies,

including batteries, chargers, loud speakers, transformers, condensers, rheostats and any other parts you

may want for improving your set or building a new one.

REMEMBER—WE ARE THE LARGEST EXCLUSIVE RADIO MAIL ORDER DEALERS IN THE WORLD AND CARRY THE BEST OF EVERYTHING IN RADIO. SEND FOR OUR CATALOG TODAY!

RANDOLPH RADIO CORPORATION The Largest Exclusive Radio Mail Order House in the World 159 N. Union Ave. Dept. 11 Chicago, Illinois

You must have our catalog no matter what set or kit you want. Our line is complete and in-

to an eight tube set, kit, or semi-

in our wonderful catalog.

or supplies-any radio data-

No matter what you want in radio - anything from a one tube


Our Catalog Includes complete list of broadcasting stations and general information and facts about our free

GUARANTEE Every article exactly as repre-sented. Every sented. Every efore shipping. omplete satisfaction or noney cheer fully refunded

OUR

Miller

AMPLIFYING HORNS 41 Different Models

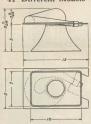

Miller Radio Horns are used on the best loud speakers manufactured,

Radio manufacturers realize that, no matter how good their instrument may be, their efforts are wasted unless the horn they use will amplify, clearly and without distortion, every sound as it is reproduced.

That is why so many of the leading makers of radio instruments use Miller makers of radio instruments use Miller Horns as standard equipment. They know that the unique composition of which Miller Horns are made, is suffi-ciently inert to practically eliminate horn distortion and vibration. They know that there is a Miller Horn scientifically designed to meet their exacting requirements no matter what size their cabinet

Quantity production permits us to sell

The Miller Rubber Co. Akron of N. Y. Ohio



Insure your copy reaching you each month. Subscribe to RADIO NEWS-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, New York City.

practically one-eared hearing, a phase difference of 180 degrees being too great to pro-duce the phenomenon of plastic hearing, while a phase displacement of only 100 de-

phase difference of the current induced in signed on somewhat different lines, its two coils being made up of a large number of windings (10 to 30,000) of thin wire to pro-duce inductive coupling. The arrangement of the variometer will be seen from Fig. 4. ing to the angle between the two coils of the variometer, 1 and k. In order to supply head-phone 2 with a current of the same

Fig. 4. Circuit diagram of the stereophone as developed by Dr. Kluth is shown above.

intensity as the current operating in headin accordance. This arrangement will result in a phase displacement of the current in head-phone 2 of just sufficient magnitude to convey the impression of a plastic acous-

effect similar to the stereoscope in optics and, therefore, has been fitly styled the stereophone. It is readily accommodated in required to obtain a connection with the

mounted at a suitable angle to one another. This stereophone at the present time is the three-dimension broadcasting, entailing as it does, no alteration of the transmitter

Sound Photographs and Their Reproduction

vice seemingly promised success, but it was

to the rapid variations of current and trans-late them into terms of light intensity. caused other means to be sought.

TALKING ELECTRIC ARC One of the first and foremost experimenttalking films, was the German scientist-



sped ready to use! No costly bulbs! No arid fumes is for 116 volt A.C., D.C., or farm plants. Write Kimley Electric Company, Inc. 2665 Main Street Buffalo, N. Y.



To the Man with an Idea I offer a comprehensive, experienced, efficient service for his prompt, legal protection and the development of his proposition, for advice as to cost, search except the proposition, for advice as to cost, search except the proposition, for advice as to cost, search except the proposition, for advice as to cost, search except the proposition of the Booklet of valuable information and form for properly disclos-ing your idea free on request. Write today.

RICHARD B. OWEN PATENT LAWYER en Building, Washington, D. C.

YOUNG MEN-Turn Your Spare Hours Into Money

Earn big profits, prizes, and awards selling SCIENCE & IN-VENTION, RADIO NEWS, The EXPERIMENTER, and MOTOR CAMPER & TOURIST in your we will help you get started. E. J. FOLEY.

The Experimenter Publishing Company

53 Park Place New York City



BURIED TREASURE

can still be found in CHEMISTRY



Good Chemists Command High Salaries



Noted Instructor, Lecturer and Asthurs, Ferragery Pressurer Amerilein Chemical Seciety and a pertical chemical Seciety and a pertical chemical with many well knowarbitectments to his credit. No emity has Dr. Steapes tautch chemic try for years but he was fer man years, engaged for ensurering chemistry work. and you can make yourself independent for life by unearthing one of chemistry's yet undiscovered secrets.

Do you remember how the tales of pirate gold used to five your imagination and make you want to sail the uncharred seas in search of resource and adventure? And then you can be search of resource and adventure? And then you can be search of the search of

What Some of Our Students Say of This Course:

I have not written since I received the big set. I can still say that is far exceeded my anticipations. Since I have been studying with your school. I have been appointed chemist for the Scenaton Coal Co. testing all the coal and ash by proximate analysis. The lessons are helpling me weederfully, and the interesting way in which they are written makes me wait

I with to express my appreciation of your promote peoply to my letter and to the recommendation to the General Electric Ca. I intend to its and to the state of t

So far I've been some than pleased with your course and an still dollen nickey. I have the your course and an still dollen nickey. I have the he your homor graduate this year.—J. M. NOIRK'OS, JIC and JONES AND THE STATE OF THE

one I've studied.—JAMES J. RELLY.
From the time I was having Chemistry it
has never been thus explained to me as it;
now. I am recommending you thinks to me
joint to me as the second of the second part o

friends and let there have have simple your lessons are.—C. J. AMDAIL.

1 am more than pleased. You did right in the size that I am rook go not never successive you.—A. A. CAMERO, so god that I found you.—A. A. CAMERO, and that I found you.—A. A. CAMERO, and the I found you.—A. A. CAMERO, and the I found rook of the I was a second of the I found you.—A. A. CAMERO, and the I find it were thorough than most text books I can secure.—WM, H. TIDINS.

Gas. Co. I appreciate very much the root service of the school when a recommendation was asked for,—JOS. DECKER.



Experimental Equipment Furnished to Every Student

We give to every student without additional charge the chemical conjunction, landsing networks a helice of labor fory negative the conjunction of the conjunction of the land research. These engages the superior and themselves and research. These conjunction is not construct the heavy wooden but rever provided the conjunction of the beary wooden but rever provided the conjunction of the but also as a susted thoratory accessery for performing

CHEMICAL INSTITUTE OF NEW YORK, Inc.

HOME EXTENSION DIVISION II

66-R-WEST BROADWAY NEW YORK CITY

Now Is the Time to Study Chemistry

realth in Chemistry, but the prefession affords congenial moduratest at good salaries to hundreds of thousands who berely follow out its present applications. These appliations are immunerable, touching intimately every business.

are immuserable, teaching instinately every basiness and every product in the world. The week of can hardly be called week at all. It is the keenest and most enjoyable kind of pleasure. The us issuited laborately are filled with thrilling and delightful experimentation, with we alterine

You Can Learn at Home

many ferrited and fineson system of instruction, you can pure stor at home, here yes societies you can be sometimened by the control of the

Easy Monthly Payments

to ere i in small methods international small that you won't feel them, the control of small players and the control of small players a chemical education within the reach of everyor. Write us and let us expelled our play in full—city us the test of everyor. Write us and let us expelled our players in full—city to the test of extending players and the control of the control of

heides furnishing the student with his Experime confusionent, "or are making an additional special after to share while only. You ome it to yourself to find our special it. Write treaty for full information and free code." Opportunities for Chemists." Send the coupon that zow while it is frosh in your mind. Or just

But whatever you do, not today before
is withdrawn.
WAIT—MAIL COUPON NOW! CITY.....

DDRESS

STATE

"As Specified"

by Sylvan Harris in his Push Pull Amplifier illustrated and described in RADIO NEWS.

COMO

The World's Standard
Push-Pull Transformer





Price \$12.50 per pair

Demand the NEW TYPE COMOS with Binding Posts

For maximum volume without distortion nothing can equal a Push-Pull Amplifier in which COMO DUPLEX Transformers are used. Gives "B" Battery and tube economy, with great volume absolutely undistorted.

COMO DUPLEX Transformers have been endorsed by the leading editors of the country, for use in the Cockaday, Roberts, and other of the most popular circuits. These experts know, Need we say more?

COMO APPARATUS COMPANY

Kelley St., Manchester, N. H.

For sale at all leading dealers

RADIO DEALERS

Have you received your copy of our new catalog? If not, write today. New Circuits. New Apparatus.

Dan-Ashe Radio Co.

A COMPARISON OF METHODS
We shall now try to determine which one of the two kinds of records is the most valuable, and why.

inventor, Ernst Ruhmer. Ruhmer claims much rendit for the invention of the so-called talking electric arc, and gave many lectures and experiments with these arcs. He reasoned that if an electric arc can be caused to talk or to give musical recitations, its light should vary in intensity in accordance with the sound waves. Accordingly row sit, and actually obtained a sound record, which he reproduced publicity by means

of sclenium cells.
From an are in the open air to an are in an endoned glass west, with low pressure.
From an are in the open air to an are in an endoned glass west, with low pressure in fact, shortly after the experiments by Rahmer, Prol. Korm, of relephotographic of great perfection over great distances by place-electric methods, proposed to use as the place-electric methods, proposed to use as controlled by an electrically controlled sparse and the property of the proper

in Support of gasous tibe was already unanimously decided upon after investigations on this subject were published by Jacob and the subject was published by Jacob and the subject was subject in given by Gethere on his subject is given in his reason. The Negative Goodpale's carried the subject is a specific form of the which is used quite extensively in Germany will be described in detail. This tube is almost unknown in the United States, and will be described in detail. This tube is almost unknown in the United States, and the English language, except in the case of Plenning work. In analyzing tits type of Plenning work. In analyzing tits type of the subject was also become the subject with the subject with the subject was also become the subject with the subject with the subject was also subject with the subject with the subject was also subject with the subject with the subject with the subject was a subject with the subject with the subject was a subject with the subject was a subject with the subject with the subject was a subject wit

This glowlight can now be utilized in tw distinct ways. In fact, the mechanical recording can also be done in the same dis-

timelty different manner. The first and, I me different manner. The first and, I me did some service to the control of the con

The other type of record is obtained when try not to change the intensity of the light source, but its length, or by mechanical receivable of the change of a kind of very irregular saw with teeth that vary in length constantly. Between the change of a kind of very irregular saw with teeth that vary in length constantly. Between the change of the chan





A combination of Pilot Light and Midget Battery Sweitch. Constantby indicates whether the radio set is "on" or "off." The pilot light bull'seep is furnished in a choice of red, green or amber.

At the bestradio dealers \$1.00—lamp extra
Pilot Light Bracket
Like the Pilot Light Switch, excepting it is
intended for sets already equipmed with a

Panel Light
Neat in appearance. Panel Light, with
jewel in hood. Mounts in single ½ panel





The New Radio Stamp Fad

Here is the DX Radio Stamp Album just like the ones we owned in our youth, in which were placed the rare stamps of the countries for love or money; but the fun of the hobby was the seeking of rare stamps and the eventual possession. So it will be with the DX Radio Stamp Album. There will probably be some stamps you will never be able to own, but there will be many you will be proud to have and be able to show to other scale enthusians. It's an interest, of which a generous supply is furnished with each Album. A dime placed in the hole in the card and sent to the station you heard brings back a stamp for your Album.



given away absolutely free with a subscription to any one of our four magazines: "Radio News," "Science and Invention," "The Experimenter," "Motor Camper and Tourist."

Don't pass up the opportunity to get this valuable premium. With this album, you can keep through the means of beautiful engraved stamps, a certified record of every broadcast station you have heard on your radio set. Your friends will enjoy

The album consists of 96 pages, size 9 x 12 and is bound in extra heavy stiff cover.

log records.

We have acquired 1,000 of these Albums especially for our subscribers. The coupon on this page filled out and mailed to us with \$2.50 will entitle you to a twelve months' subscription

EXPERIMENTER PUBLISHING CO., INC., 53 Park Place, New York, N. Y.

I am enclosing \$2.50 for 1 year's subscription to () "Radio Never,"
"Motor Camper & Tourist" and one EKKO Stamp Album which you will
(Mark to which magazine you wish to subscribe)

NAME

DON'T FAIL TO USE THIS COUPON



T takes but a fraction of a second to detach your headset and attach your loud speaker with this new plug. It comes with the



-a tightly - braided, kinkless, fadeless Cord that permits you to move your speaker from room to room and "listen in" wherever you please. The plug is automatic with no screws to fuss with or lose. It holds terminals securely, yet the slightest pressure on pins instantly releases

PREMIER Cord

complete, with plug ... \$1.75

At your dealer's-or write us.

CRESENT BRAIDCO.. Inc.

Makers of Extension Cords and

Providence, R. I.



Red, for instance, appears mostly as record due to the failure of the film to record faithfully the variations in light in-

This distortion, due to the film, is, of it is apparent that such correction is not at

An equally important consideration against In this respect one can again be sure with the quantitative or saw-tooth record of a uniform intensity of the light, as only the quantity of the same kind of light is going to vary, under the influence of the motion of the film. In general, then, the made his records all in that manner. There seems to be quite a difference of opinion in seems to be quite a uncrence of opmon in this matter, as the German exponents of talking films, Messrs, Vogt, Engl and Mas-solle, use the step-ladder record, and in America exactly the same method of record-ing is advocated by Dr. DeForest, while the Pallophotophone, as made by Mr. Hoxie of the General Encirc Company, is of the the saw-tooth type.

In his own experiments the author used highly polished, flat, nickel electrodes, enimbedding in mica or another insulator. When now a current of sufficiently high



Mechanical Simplicity

Here is the keynote of Elgin populand superiority. With the new Model comes added grace, beautiother striking improvements. A tional equipment, we have

Ideal Under All Conditions

The Eigin embodies every worth-while principle necessary for true Radio enjoy-ment. The 1926 Model is more outstand-ing than ever—a set worthy of your highest approval. Send 2c stamp for complete information.

ELGIN RADIO SUPPLY CO. 207 E. Chicago Street, Elgin, Illinois

Super-Reinartz The Ford of Radio



SEND FOR Guaranteed to Give Complete Satisfaction or Your Money Relunded

PRICE

\$22.50 24.50

C. E. JACOBS, Sole Mnfr.

List Price

MaM Low Loss

Sans Laurentennannan Laure

New 5-Tube TRE

Millions Want This Set!

TREGO RADIO MANUFACTURING COMPANY 1427 Chestnut Street. KANSAS CITY, MISSOURI potential is flowing through this tube, a layer of bluish and highly actinic light appears on the negative electrode. Mirrogen its glowlight, photographs very easily. This layer of light is called the negative glowlight, and careful measurements have shown that its length is proportional to the amount

When an alternating current is applied to the time decrebeds, the light appears alternately upon one or the other of the electronic plants and the electronic plants are always and the electronic plants are the electronic plants are always always and the electronic plants are always always and the electronic plants are always always are always and the electronic plants are always ar

And if one photographs this light through a narrow slit, adapted to the number of frequencies to be accommodated at a given speed of the film, a record results that looks like the films used as border of one of these

poges. The particular pieces of film shown represent the sound waves created by a violin and piano together. As the matter has been presented here it should be clear that the whole processes involved in duplication of the processes involved in that the modulated oscillations are used to excitate the Gehrke tube instead of being radiated into space.

And it will also be clear that any improvement in broadcasting implements will mean an equivalent improvement in the quality of the sound photograph attainable—not only with the method described herein, but with any and all of the sound recording devices that may be pressed into service.

in the present may retrieve the control of the present may retrieve the control of sound waves into electrical energy. Here the choice his between several electro-dynamic microphone, the glowlight mercophone of Dr. Thomas of the West-Porest and, about the best of all the exhectephone of Messay. Vost, Engl and microphone of Messay, Vost, Engl and microphone as yet not published. In an article subsequent to this series the author hopes to deal with the relative mercha and the property of the control of the present t

A second question that vitally affects quality in recording and reproducing is the amplification necessary in both these processes. Of course, here every indication of progress in the broadcast studio means an equivalent improvement in the musical film, just as all improvements in loud speaking question might be stated in the following question might be stated in the following

The photographic sound record is but a broadcast performance made permanent, with all the good characteristics possible in broadcasting, except for the fact that static is completely absent in musical films.

of course, the films may or may not be combined with ordinary motion pieture films on a to make allular material pieture films to a to make allular material pieture. If the coming form of ammentar, since for these films the very manufacture for the films the very manufacture for the films the very manufacture for the films the very considerable for the films that the films that



Introducing "SUPERUNIT JUNIOR"

A little brother to the standard Type A and Type B 'Superunits.

He measures 5 x 10" and he consists of a stage of tuned R.F., the detector and two stages of Thordarson audio.

He has plug-in coils and the standard set of coils which he uses will tune from with the S-C Capacity Element to make a one dial set. Other coils for other wave lengths.

He makes the most efficient set for use with an aerial and there are just 11 connections to complete him.

YOU SHOULD MAKE HIS ACOUAINTANCE!

Price, complete with instructions\$37.50

Materials Needed For a Complete Set

Superunit, Ir." S-C Capacity Element or 2 .0005 condensers

- 2 Bradlevstata Double circuit jack
- Note: No baseboard is re-

Hanscom Radio Devices

Migrs. of the S-C Capacity Element, two control sets Woonsocket, R. I., U. S. A.

STATIONERY PERSONAL. 200 SHEETS and \$1.00

AGENTS MAKE BIG MONEY taking codern



movies. Because one thing is sure: the talk-ing or musical motion picture film will come into its own only after a severe and

Hot Cathode Metal Uapor Tubes

tube circuit must be used across the tube to make it operate as a sensitive detector. voltages are much lower than those used on

USE OF METAL VAPORS IN TUBES performance of gas content tubes, turned

last five years. Some of the results have been published, some have been kept secret. In some cases the vapors have been introduced into tubes containing regulation metal STANDARD PATTERN METAL VAPOR

First let us study the action of a tube of First let us study the action of a tube of regulation pattern into which metal vapor has been introduced. For this purpose an ordinary 201 or 301 tube may be used. The tip is knocked off and a new glass outlet tube tube containing the selected we shall see in a moment. Fig. 1 shows the apparatus needed for this work. It is apparent that few amateurs can undertake such Suitable glass pumps must, however, be bought, and these cost 35 to 40 dollars, LIQUID METALS

For maximum ease in loading the tubes with metal a liquid metal should be used. This requirement limits us to two possibilization voltage of mercury is about 10.5 volts.

The "Windham" Wire Former



A Handy Tool for Electricians, Radio Fans and Mechanics

Retails for \$1.25. Dealers and Jobbers send for full information. Desirable ter-ritory still open.

THE GOYER COMPANY Willimantic, Conn.



12 Sells Lasts Indefinitely—Pays for Itself reaged plates. Order yours today!
SEND NO MONEY Just state mumber of hattacl
send wo will able to
order is received. Extra Offers 4 butterfee linearies all oviolas, \$12.
"May appreciate all the containing hattaclesses. So per cost discount if WORLD BATTERY COMPANY
Wabash Ave., Dept.75 Chic

World

EUREKA DIAL POINTER

to panel.

D-X OWL. The mark of a radio fan. Used as a lapel pin or Dial Pointer, tall being pointed. A sco-ular engraved radio novelty. POLISHED NICKEL OR HEAVY GILT FINISH. Price 15c

C. W. BUTTS, INC., 42 Hedden Place. East Orange, N. J.





The softim-potassium alloy can be prepared by melting together 2d parts of softim metal and 40 parts of potassium netal. These and the parts of potassium netal. These mental regime for the parts of potassium sense and the parts of the part

After the tube has been prepared in the way described it can be put into use in an ordinary receiving set. The lighted filament was a superior of the property of the property of the property of the vapor made up of sodium atoms and potaxism atoms which occupies the bulbs been reached the density of the vapor remains faxed; that is, the number of metal manifest of the property of



A is sodium metal, and on the outside of the tube is H, a heater coil. FF, the filament and C, a collector plate.

Instead of entering into a scientific diving of the property o

Tubes of this kind also amplify well, introducing no distortion, and can be used in amplifier circuits, giving results on a tenvolt battery equal to those of hard amplifier tubes on 45 or 90 volts. It seems, consequently, that the use of the alloy results in



Standardyne Console Model H

List Price, \$135.00

Standardyne

Presents for the new season two distinctive models both embodying the famous Standardyne 5 Tube tuned radio frequency receivers with patented re-acted

Model B5 is smart and trim in its

Model BH is a superb console in genuine mahogany, with the grace and beauty of a thorough-

Both models maintain the Standardyne reputation for performance and dependability.

B5—Pacific and Mountain States \$65.00

BH-Pacific and Mountain States



Standardyne Table Model B5
List Price, \$60.00

Manufactured by THE STANDARD RADIO CORPORATION, Worcester, Mass., U. S. A.

Sole World's Distributor

BEN W. FINK

1123 Broadway

..

New York, N. Y.



-and you can build the finest Radio Receivers Ouickly and Easily

It takes but one or two evenings, using only the simplest tools to construct, at home, any one of the big, popular receivers shown on this page.

All you need is the well known CONSRAD Pattern that covers this particular receiver. CONSRAD Patterns are marvelously simple. You don't have to measure the spacing on the panel board or the placing of the parts. It is all drawn for you on the Blueprints the same as indications are given on a lady's dress pattern.

And you don't have to use 100 different tools to complete the job—just six or seven ordinary tools found in every household. A screwdriver, a pen-knife, a pair of pliers, etc., and you are ready to go a head.

Visit your nearest Radio Dealer, ask him to let you look at some CONSRAD Patterns, select the one you want. Pay the Dealer 30c and you have complete instructions and blaeprints for the construction of the Receiver.

IF VOLK DEALER CANNOT SOPPLY YOU, WITE DIRECT, MENTIONING IT WAS A CONSTRUCTION OF THE PARTY OF THE P

The CONSRAD COMPANY, 233 Fulton St., New York

Consrad

EVERYTHING IN RADIO BOOKS, PATTERNS AND DIAGRAMS

SUPER-HETERODYNE



THE TROPADYNE



THENEUTRODYNE



5-TUBE COCKADAY



THE REFLEX



THE PORTABLE



a distinct improvement in all respects. Of course, such tubes, when used in a regenerradiation disturbances, but in this respect SPECIAL METAL VAPOR DETECTOR

Next, let us turn our attention to one of the most unusual of the specially built tubes employing metal vapor. The vapor in this employing metal vapor. The vapor in this tube is sodium vapor. Sodium is a soft metal, easily scratched with the finger nail,

4 Non-Technical Radio Articles

every month for the beginner, the layman and those who like radio from the non-technical side.

SCIENCE & INVENTION, which can e bought at any newsstand, contains the rgest and most interesting section of also articles of any non-radio magazine

in existence.
Plenty of "How To Make It" radio articles and plenty of simplified hook-ups for the layman and experimenter. The radio section of SCIENCE & INVENTION is so good that many RADIO NEWS readers buy it solely for this feature.

List of Radio Articles Appearing in the November Issue of

"Science and Invention"

A Continuous Broadcast Service
By C. A. Oldroyd A Novel Six-In-One Receiver By L. Ringer

Five Tubes But Only One Tuning Control Hints for the Radio Builder, Part III

By Leon L. Adelman, Assoc, I. R. E.

tively, fairly high, about a red heat, so that to one of the prongs of the socket. FF1 is a tungsten filament supported horizontally of the ordinary tube (although the principle

CIRCUIT CONNECTIONS



Now-Plate Voltage for any Set — and You can afford it.

First Cost Economy now makes it possible for EVERYONE to obtain efficient "B" current supply right from their electric light socket. Now one of the biggest improvements in modern-day radie reception is placed within the reach of all. Think of it! A perfect always efficient source of plate voltage for any set for \$9.751 II marks a revolutionary step forward and will be welcomed by mill-lines of radio enthusiasts.

Ferhend "B" Eliminator

The price of this remarkable new unit is spectacular in more than one way. Besides saving you from \$15 to \$50 it is amazingly low considering the quality and superiority. You may ask "how could it be possible to build such a unit for the ridiculously low price of \$9.75?" True prichanical genius and resourcefulness. About 10 of \$1.50 it is not proceedings and the sourcefulness and resourcefulness. \$9,75?" True mechanical genius and resourcefulness alone are re-sponsible. But the logical way to answer this question is to equip your set at once with this marvelous unit and be convinced.

ASK YOUR DEALER—OR SEND DIRECT

FERBEND Wave Trah Until nation-wide distribution is com-pleted it is possible that your dealer hasn't stocked the MAXMIN "B" Bator C. O. D., plus postage. Remember, superior results are guaranteed or your money back. Be one of the first to own and use the Ferbend MAXMIM "B"

Ferbend Electric

Company 25 East South Water Street Chicago, Ill.

Ferbend Maxmin Guminato

Increase Distance, Volume, Clarity R. N. COLYTT LABORATORIES

565 Washington Blvd., Chicago





ing else to buy. Operates at maximum efficiency at all times on either direct or alternating current, any

Delivers unlim-

Delivers 100 volts to ANY set.

Cost of operation less than 50c a year. It lasts indefi-

All parts are specially designed and only

Unconditionally Guaranteed

to be equal or superior to any eliminator on the market, regard-

FERBEND ELECTRIC CO.

25 E. South Water St., Chicago
Send Postpaid. I am enclosing \$9.75.
Send C. O. D., Plus few cents postage.
Send Literature.

ack and Automatic
or filled by mall proicle absolutely guarRN Mfg. & Sales Co48 Beekman St.
New York, N. Y.



The little instrument that's a BIG help!



Model 506-New Weston Radio Panel Voltmeter

HIS beautiful little precision instrument, handsomely incased in Bakelite, with silver face and dead-black scale, is only 2" in diameter. Mounted on the panel of your set it is the surest way of knowing the actual facts of radio reception. See it at your dealer's. Send for booklet: "Weston Radio Instruments."

> For further information address

Weston Electrical

Instrument Corporation 173 Weston Ave., Newark, N. J.





Write Today For Our 64 Page Catalog of RADIO BARGAINS RANDOLPH RADIO CORP. 159 N. UNION AV. Dept. 2 CHICAGO, ILL. works we may note that actual tests show oscillate over the range of voltages used and HOW IT WORKS

The Experimenter

has come back! If you are one of the one hundred thousand readers of the old ELECTRICAL EXPERIMENTER, you will no doubt be flad to hear that the EXPERIMENTER IN COME back BIGGER AND BETTER THAN EVER.

Experimental Radio

Nothing but experiments, written by the Nothing but experiments, written by the loremost radio authorities, also a mouthly editorial by H. Gernsback. A fine roto-fravar-section to brighten up the magazine. But best of all for you radio readers, is the blg radio section of over twelve pages of some fifty radio experimental articles—and mind you, NOTHING BUT EXPERIMENTS. LIST OF INTERESTING ARTICLES T APPEAR IN THE NOVEMBER ISSUE OF THE EXPERIMENTER

How to Make the Electro Mystic Crystal Globe.

By Phillippe A. Judd.

Electrified Butterfly Lives 25 Years.

By B. Vincent, Southampton, England.

By Loon. L. Adelensa, A. M. I. R. E.

The Luludyne. By Simon Kaho, 2CGX.

Liquid Hydrogen.

Transmitting Photographs By Cable.

The EXPERIMENTER will be on sale at newsstands November 20, 1925.

action long enough to bring everything up positive, by far the larger part of the elec rent to the collector was 100 microamps and was 1,000 microamps and the anode current 1,400 microamps and 340 microamps. It is to be remarked here that the collector cur-rent was always about four times as great





How to Build the SUPER-FIVE

Inclose 25c and you'll have it by return mail

Gearhart-Schlueter Radio Corporation





The KINLEY Tuned Radio Frequency Unit

Send for descriptive circular. KINLEY RADIO COMPANY 45 Elmburst Ave.

current changes with the collector voltage. there is found to be in it a definite "elhow notential increases the anode current only

When the collector is set at this particular voltage and a radio wave is received by the each radio wave that comes in (B, Fig. 5). starts and another when it stops. It is in which does not employ a grid leak and con-

ADVANTAGES OF THESE TUBES To use the sodium tube in the detector

Station 258.5 Meters - 1160 kilocycles is owned and operated by the publishers of this magazine several times every week See your Newspaper for details TUNE IN ON

The two tubes described in this article not are being applied for the most part to pur-

A SCIENTIFIC WONDER

SMITH: I got something good from White's loud speaker last night.

SMITH: I should say. White has a pipe running from it to his still in the cellar. Contributed by Paul S. Powers.

Spectacular Performance

DUOFORMER





Super-Selectivity!

Build the new Duodyne with the Camfield Type 22 Duoformer, and the Camfield Type This circuit—using either dry or storage batteries—is designed for the new power tubes, CX220, or UX120, and CX112 or UX112, and gives a combination of

> Selectivity Sensitivity Volume Tone Quality

never before obtained in a five tube set.

The wavelength range is 150 to 550 meters. Send 25c for "The Duodyne Circuit," a

DEALERS:

If your jobber can not supply you with a complete line of Camfield parts, send us his name and your order direct.



This condenser embodies a new principle of construction, combining every essential and desirable feature in a single unit. Its straight-line action together with the 360° dial, absolutely eliminates the necessity of a yernier. together with the 300° dial, absolutely eliminates the necessity of a vernier.

The Camfield Condenser is enclosed in a trans-parent Dust-Proof Case which prevents the accum-

CAMFIELD RADIO MANUFACTURING CO. 807 Harrison Street

Other Factory Repres

1268 West 115th Street

Baker-Smith Co., Inc., 1270 Broadway, New York City; 30 N. Dearborn St., Chicago. A. S. Lindstrom Co., San Francisco, Los Angeles, Portland, Seattle, Salt Lake City.



CRESCIENT LAVITE RESISTANCES

for Distortionless Amplification 50.000, 100.000 Ohms. Lis seisl Sizes to Order \$2.50 each. iccounts. When Better Resist a. Special Sizes to Order 22.20 each, for discounts. When Better Resist to they will be Crescents.

Co., 1-5 Liberty St., Jamaica, N. Y.

CONDENSERS HEATH RADIO & ELECTRIC MFG. CO., 206 First St., Newark N I

BUILDING A SET?



Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 65c. Experimenter Pub. Co., Inc., Book Dept., 33 Park Place, N. Y



The New TWIN BULB

HANDY (HARGER

Performance

Backs up its Beauty

It's truly a wonder—this new Twin Bulb HANDY. Charges all storage batteries at a fast rate evithent the slightest mois. The "push-pull principle using both halves of the AC wave accounts for the fast economical rate of charge. A special ammeter shows just how fast your ammeter shows just how fast your charge or discharge to make the property of the purpose of the property of the

therefore is particularly adapted to overnight charging. Charges "A" Batteries 4-5 amperes to 6 volt batteries; "B" Batteries up to 120 volts in series. Ask your radio dealer about this new charger.

INTERSTATE ELECTRIC CO.






Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park Pl., N.Y.C.

S. L. F. Dials

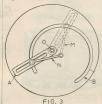movable plates. For instance, suppose a plate, A, which can be rotated about the center, O. This plate has a groove, B, in it, in which travels a pin at the end of an arm, r. The arm, r, has likewise a slot in it, so that the pin can travel up and down the length of the arm.



As the plate, A, is rotated, the pin moves outward from the center, to the positions shown at a, b, c, d. The greater the distance the pin is from the center, or in other works, the greater the radius, r, becomes, the faster will the pin move around the center, O. The actual law of motion of the pin depends upon the shape of the groove, B, and can be made

F(c, g)

The angular setting of the condenser plate varies with the angle of the dial in accordance with the curve above.

Many variations of this principle are possible, as can be seen in the various illustrations on these pages. Sometimes ring-pears and pinious are used, but the design is greatly restricted by these, as the motions are, in turn, restricted by the possible ways of designing gears. The principle represented by Fig. 3 permits of a perfectly linear cali-

Other ways of constructing variable motion dials employ gears of special design, such as elliptical or hyperholic shapes. An acample of the use of elliptical gears is considered to the flustrations. The elliptical gears is considered to the flustration of the



Tone Clarity
Beyond Expectation

Just pull the switch and note the clarity and richness of tone any Amperite-equipped set gives you. Amperite is the automatic rhecatat which does away with hand rhecotats and does away with hand rhecotats and correct transparent of the correct transparent with the correct tran

RADIALL COMPANY
Dept.RNI6,50 Franklin St., N.Y. City

The "SELF-ADJUSTING" Rheastat

AMBASSADOR

Audio Transformer

High, Low and Push-Pull Combined

\$4.50
Low terminals for easy connections. Brass case painted with

deep blue Duco automobile finish. Amplifies without distorting. Write for Free 4-Page Transformer Folder and Hook-ups.

and Hook-ups.

Consigned to Picked Deal

Consigned to Picked Dealers

AMBASSADOR SALES COMPANY


108 Greenwich St., New York

326 W. Madison St., Chicago

22½ VOLT \$2



conducting 21% west rechargeable "B" shour batters, S. Breisles consultation and the last charge statetion of the last consultation and the last charge statetion of 12% with \$12.60; 135 veits \$14.75; 125% with \$1.00; 1135 veits \$12.60; 135 veits \$14.75; 125% with "wither parameted 2 years. Knachbaren kits at till greater tiller generated 2 years. Knachbaren kits at till greater tiller generated 2 years. Knachbaren kits at till greater with the last consultation of the last consultation of the years with the last consultation of the last consultation of the years with the last consultation of the last state of the last with years ratio good catalons to II. H. Strill, 20 years and

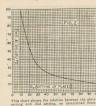

Before closing this article, we must not longest the mecessity of lawing the proper distribution of the properties of the properties of the properties of the part of the part of the conclusive are part of the part of the conclusive are part of the part of th

WRNY Starts Broadcasting Innovation (Continued from page 599)

(Committee from 1-2: err)

is now going forward under the guidance of Mr. Pierre Remington.

Among other are handling the song are handling the song the control of the famous and the following the control of the famous Amelite Galli-Curic. Every other week Mr. Curci and a group of singers will put on a song recital.

The state of the state of the state of the state of the leading song recial groups, below of the leading song recial groups, be lead recorded from the state of the leading song recial groups. The state of the leading song recial groups be leader required by a state of the state

music by the Volga Trio and by J. Van Cleft Cooper, lecturer and singer. Orlando's Concert Orchestra will offer high-class orchestral programs three times

There will be a Classique Ensemble, headed by Thomas Alonji, which will be heard in Sunday night twilight concerts.

The Sadrian Trio will present-old musical comedies which will fit in with the light core of the sadrian trio.

rucci's Orchestra will present some deligh

Rita Maginot is going to play all of the piano classics from A to Z—in just that order. Mathilda Sper will give one of the piano

Build this phenomenal new radio in 45 minutes



The revolutionary Erla Circloid-Five Factory-Bilt Kit as you receive it, Price \$49.50

This new type kit is factory assembled. Ready cut, flexible, solderless leads make it ridiculously easy to wire. Amazing new inductance principle brings results hardly thought possible.

Send for book, Better Radio Reception.

N CW anyone can build the finest of receivers in only a few minutes. No more wire bending or soldering. Merely attach a few ready cut, Rexibe eyeletted leads and the job is done. The finished set is unsurpassed even by the costliest factory-built receiver.

But most amazing is the new inductance principle incorporated in this last word in kits—called the Erla Circloid principle of amplification.

Four vital improvements result from this great discovery, which are not found in ordinary sets.

1. Greater Distonce: Rein *Balloon* Circloids have no external field, consequently do not riflect adjacent coils or wiring circuit. This enables concentration of proportionately higher amplification in each stage, with materially increased sensitivity and range.

 More Volume: Increased radio frequency amplification made possible by Erla Balloon Circloids gives concert volume to distant signals inaudible with receivers of conventional type.

3. Increased Selectivity: Erla Balloon Circloids have no pick-up quality of their own. Hence only signals flowing in the antenna circuit are amplified. Static is greatly reduced for this reason.

Dealers Exclusive franchises are available to pen. Write or wire immediately.

4. Improved Tone Quality: The self-enclosed field of Erla Balloon Circloids eliminates stray feed-backs between coils and consequently does away with mushing of signals and distortion. Tone is crystal clear and perfectly lifelike.

Write for free information on kit—also book See how 45 minutes of fun will give you the

to radio science. Easy as N-B-C to muse Examine it at any Erla dealer's, or send the coupon for full information, illustrations are diagrams free. Also ask for remarkable ne book, "Better Radio Reception," describit the sensational new Circloid principle. Ecose 10c for mailing and postage on book.

ELECTRICAL RESEARCH LABORATORIE 17-B 2520 Cottage Grove Ave., Chicago *Trude Mark Registered.

ELECTRICAL RESEARCH LABORATORIES. 17-B 2520 Cottage Grove Ave.,

Chicago, U. S. A

Send me free informatio
on kit.
Enclose 10c fo
postage for book, "Bette

A. This sign ide
authorized
for distributors.
are equipps
give comp
radio service.

City..... State....

Just the Book You Wanted

"RADIO NEWS" AMATEURS' HANDIBOOK Volume No. 1 (Fourth Printing)

remost radio authorities, in plain everyday language which everyone can understand exclusion include articles on Receiving Sets and Sundry Apparatus, Transmitters and Assouries, Radio Theory, Vacanum Tabe Data, and Praetical Mints for the Amstern. I dow which also serves as a ready reference and should find a place in the Directory and the Company of the Company of the Company of the Company of the Company in the Company of the Company of the Company of the Company of the Company in the Company of the Company of the Company of the Company of the Company in the Company of the Company

Price \$1.00

EXPERIMENTER PUBLISHING CO., Inc., 53 Park Pl., New York

RADIO LISTENERS' GUIDE and CALL BOOK

Radio Set Owners Book.

fall Issue

116 RADIO World's Greatest Book of Information with the Latest Complete List of Radio Stations and Call Letters

Here is the latest and greatest radio book of its kind published for the Broadcast Listener. It is a National Radio Guide Book of the United States in that it gives you, completely and comprehensively, the location of radio stations on the air. It lists all stations of the United States, both Broadcast and Amateur, giving size and location of each station, its wave-length, etc., with ample space for tabling and logging those you receive.

Then just as an Automobile Guide Book tells you how to care for your car, this book explains the complete care of your radio set by explaining the fundamental operation of all principal parts. And also it gives foreign radio stations, time signals and a multitude of

similar, valuable listings.

116 pages filled to the brim with valuable data PARTIAL LIST OF CONTENTS

Selecting a Radio Receiving Set. Reaching the Shorter Wavelengths. How Broadcast Stations Operate. Locating and Eliminating Trouble in

Radio Sets.

All About Radiologs.
The Function and Care of Vacuum
Tubes. Loud Speakers-How to Select Them Fundamental Principles of Radio.

The Care and Operation of Storage Bat-Basic and Modern Radio Circuits. Aerials, Loops, Ground and Lightning

How to Understand Radio Circuits Radio Broadcast Stations of the U. S., Radio Broadcast Stations of the U. S., Special Land and Experimental Radio

Foreign Radio Broadcast Stations, by

American Radio Relay League and Amateur Radio Stations of the U. S., by

Districts. Foreign Amateur Radio Stations Table for Making Time Transitions.

Radio Broadcast Maps of the United Time in All Parts of the World.

SOLD AND DISTRIBUTED BY

The Consrad Company, 233 Fulton St., New York

israc

35c the copy-Sold at all Newsdealers and Radio Stores

IF YOUR DEALER CANNOT SUPPLY YOU, ORDER DIRECT, USING THIS COUPON.

THE CONSRAD CO.,

Herewith find 35c for which send me Fall Edition of Radio Listeners' Guide & Call Book.

the pizno.

Other names in the piano department are Alexander Chigrinsky and Samuel

Louis Stillman, one of the most eminent pianists of today, will be in charge of a series of talks on the epic of the piano.

In the 'cello denartment are names like

have the name of Alexandre Zeitlin, who will lecture on sculpture, and Celeanor Dugas, who will discuss painting. Miss Dugas is an American portrait painter of Dugas is an extract portrait parties of considerable merit. One of the features of the station will be an actual exhibit, to which radio fans are invited, of the paintings and sculpture and architecture of the heads of these departments.

heads of these departments.
Anita Browne, who is head of the Allied Broadcasters, will have the direction of the literary, theatre and fiction departments.

We cannot tell you the whole story in one issue, but if you will follow WRNY you will see what it is we are trying to the whole of the work of the wo

these facts:

Mrs. Brock Pemberton, wife of the famous theatrical producer, and herself a noted artist, will give a new point of view on the costumes of the theatre.

Resta Crowell will carry us through all of the old plays, the great classics of all

There is to be a series on the Kings of Sport, in which the leaders in all fields will

The Society for the Promotion of Ameri-can Aviation will send men well known in the profession to WRNY each week to give

Negotiations are now practically com-pleted which will make WRNY programs the most impressive in the entire field. Not only will the WRNY prospectus tell

that have taken place in each of the depart-As the new regime has just got under

ray, there is nothing much to say except that it was introduced at the Roosevelt Hotel, where its opening was attended by many prominent New Yorkers. Among Hotel, where its opening was attended by many prominent New Yorkers. Among those present were Otto H. Kahn, Hugo Riesenfeld, Dr. Herbert Goldstein, Ben Bernie, Hon. Bird S. Coler, Hugh Kent, J. Andrew White, Father Finn and Dr.

Salt: "How do they determine longitude Op: "They send a signal, see how long it takes to get there—and that gives the long-itude, old son."

Who Takes Care of The Care Taker --of Your Batteries?

Do you have to take care of your battery charger in order to have it properly take care of about Or, do you leave the job entirely to a Sterling Battery Charger?

The Sterling Charger is as simple, safe, and as easy to use as an electric iron. When you set it to work it buckles down to business and silently keeps at it until your battery is chuck full of energy. Nothing to get out of order-no liquids to replenish, nor lamps to replace.

The Model 19 Reactivator charges either "A" or "B" Battery. When charging the "B" Battery there is absolutely no drain on the "A" Battery. The selector switch dispenses with any extra work in changing connections when transferring from "A" to "B" Battery charging, or vice versa.

If its "Sterling" of course its Meter Equipped

The meter indicates the charging rate for either "A" or "B" Batteries, thus assuring you that the charging is taking place at a correct and safe rate of 5 superes for "A" and ¼ ampures for "B".

Storing Combination Chargers are englased in an attractive metal case; also open or closed type for "A" Batteries only.

No. 19 (50 or 66 cycle) No. 950-not enclosed-for "A" Batteries only (50 or 60 cycle) (25 cycle)

> THE STERLING MANUFACTURING CO. 2831-53 Prospect Ave., Cleveland, Ohio Dept. H

ELECTRICAL MANUFACTURERS SINCE 1906



"THE LITTLE SERVICE STATION IN YOUR HOME"



OTHER STERLING EQUIPMENT



Tube Tester





Reactivator



Panel Meters

100 Volt Storage "B" Battery for \$1000!



Everybody can now enjoy the benefits of Storage "B" Batteries-more power, quieter reception, greater economy. Rubber case pre-SERVICE Rechargeable "B" Batteries

in all-rubber cases SO VOLT \$5.50 volts \$1000 VOLT \$12.50

Prices in Canada VOLT 7.75 100 \$14.50 125 \$17.00 SERVICE BATTERY CO. of Canada, 137 Roncesvalles Ave.

Complete

\$14.50

SERVICE

Double-Duty

CHARGER

BATTERY CO. 704 East 102nd Street Cleveland, Ohio

Points of Contact List Price, 50c

List Price, 75c THE BELL "Shockproof" Socket



The 2-in-1 Vernier Dial

List Price Dial, \$2.50



The BELL 3-Phone Plug With this pluz you can book up one to three head sets in series. Philaly marked connections show how to plug in phones without confusion.

List Price, 75c

BELL MANUFACTURING CO. Makers of the famous BELL TIMER

C. L. PARKER McGil Bldg., Wash., D. C. Patents, Trade Marks, Copyrights, Patent Litigation

Young Man-Turn Your Spare Time Into Money! Spatte Tills and awards selling RADIO NEWS, SCIENCE & INVENTION, THE EXPERIMENTER, and MOTOR bood. We train you not move the property of the p

THE EXPERIMENTER PUBLISHING CO. 53 Park Place, New York, N. Y.

Esperanto **Broadcast Lessons**

(Continued from page 607)

denotes a great size or degree, and -et-a small size or degree, of that which the root signifies, as domo, a house, domego, a mansion, dometo, a cottage; ŝnurego, a rope, ŝnureto, a string; monto, a mountain, montego, a huge mountain, monteto, a hill

-il- denotes an instrument by which a thing is done; razi, to shave, razilo, razor; butero, butter, buterilo, a churn; tranĉi, to cut, tranĉilo, a knife.

-an- signifies a member, an inhabi-tant, an adherent of a party, religion, etc. Klubo, club, klubano, a club mem-ber; Londono, London, Londonano, a Londoner; vilaĝo, a village, vilaĝano, a

A RE you interested in motoring, tour-ing or camping? If you are, do not fail to read the November issue of

MOTOR CAMPER AND TOURIST

Here is a magazine that tells you things in connection with your car—things that you never even suspected.

Are you just running around the country or are you getting the full benefit of your car? MOTOR CAMPER & TOURIST shows you the way. On all newstands,

A Loop of the Great West, By Charles L. McCollum.

Seven, Seventeen and Seventy, By J. A. Bond.

The Blue Ridge Mountains of Virginia, By Melvin T. Bunch. Do You Mind Desert Travel?

By Claude P. Fordyce. Sticking to the Open.

By George Law Interesting Detours, By Hattie Mae Hall.

ticiples are:
Present tense end in—anta, (adjectival), —anto, (substantival), —ante, (adverbial):

Past tense -inta, -into, -inte; Future tense -onta, -onto, -onte.

Examples in use: La viro estas paro-lanta. The man is speaking. La paro-lanto, the speaker. Parolante, li eniris la domo, Speaking, he entered the house. La viro estas parolinta, The man has been speaking, La parolinto, the speaker (who has spoken). Parolinte, li eniris la domon, Having spoken, he entered the

La viro estas parolonta. The man is about to begin speaking. La parolonto, The speaker (who is just about to speak, t yet having begun speaking). The passive participles are:

Present tense end in —ata (adjectival), ato (substantival), —ate (adverbial). Past tense —ita, —ito, —ite.

"Picked up Canada, Cuba and Mexicoon this indoor aerial!"




Increased Volume-Greater Selectivity-Less Static!

Throw away your old distance records—let this scientifically designed indoor aerial show you real distance, volume, selectivity—reception at Large Size Has 1000

Feet of Wire! Type IXL EFFARSEE con-tains a thousand feet of copper wire, insulated from moisture and covered with parchment. Can be Type IXL (large) .. \$4.00

Type BXL (small) . . 2.50

FISHWICK RADIO CO. 500 EDWARDS BLDG.,

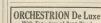



Radio at its BED.

DECHESTRION De Laxe gives you the finest reproduct the destroy of the base told serve the decided the product of the base told serve the decided the base told serve the decided of the base told the base told the base of the bas SUPERB REPRODUCTION

The tone-arm of the ORELECTRION De Luxe is entirely of best wood, from the best countergrow often found in medal or modified plantic speaker totally distingtoned to Luxe is totally distingtoned. ORCHINSTRION De Luxe is I the ideal radia speaker. Desince and perfected by the ideal radia speaker.

RADIO CABINET COMPANY

2123 Olney Street Indianapolis, Indiana
The Orchestrian Loud-Speaker Co., 103 E. 125ch St.,
New York, Eastern Distributors; Haldrids-Parific & Co.,
Parific Boig., San Francisco, Cal., Parific Cost Agents.

64 Illustrated Pages of Radio Bargains! Write for Catalog Today RANDOLPH RADIO CORP

Future —ota, —oto, —ote. La poemo estas lernata, The poem is learned. La batato, The person beaten. Batate, li kriis, Being being beaten. beaten, he cried. La skribita letero, The written letter, Vidite, li forkuris, Having

made by the verb Esti, to be, and a passive participle of the required verb

La pordo estas fermata, fermita. mota, The door is being shut, has been mota. The door is being shut, has been shut, is about to be shut. The preposi-tion used with the Passive is de, by: Mi estas amata de mia patro, I am (being, present time) loved by my father. Ili estos sendataj de sia fratino, They will

All participial verbs, being adjectival, take the plural ending j when the noun to which they belong is plural, as illus-trated in the example above: "sendataj" refers to "ili" the plural subject.

VOCABULARY

preparapor, for, in the in-terest of

granda, large,

menade, to walk ferdeko, deck

floro, flower disvolvi, to develop (disvolvigi, to

de, of, by da, of (referring to

pro. on account of. efekto, effect resendi, repeat, re-

longa, long sur, upon, on aparato, apparatus,

logi, to entice, at-(al-loga, to be

fraŭlino, young lady, Miss aŭskulti, to listen

fari, to do, to make sed, but

READING EXERCISE

Ondoj de senfadena telegrafo kaj telekaj aliaj aparatoj. Ju pli oni lernas Es-peranton, des pli bela kaj alloga ĝi estas. Sidantaj tie en tiu loko kie neniu povis Sidantaj tie en tiu loko kie neniu povis vidi ilin; la juna viro kaj la fraŭlino aŭs-kultis al la muziko venanta el la laŭt-parolilo. Hieraŭ kaj hodiaŭ mi faris nenion, sed mi estas komenconta pre-parojn por iri morgaŭ kiam vi alvenas. El siaj fratoj, ŝi amas pli tiun kies okuloj estas bluaj. Ŝi estas nur knabineto sed frato ankaŭ treege amas ŝin. radio estigas grandega en sia valoro al la mondo. La senfadena tele-grafisto kaj unu el la maristoj de la

ROST-RA

Ask Your Neighborhood Dealer

Improve your receiving set with these high grade FROST-RADIO parts and accessories



FROST-RADIO

FROST-RADIO No. 253-Automatic Cord Tip Jack

FROST-RADIO

FROST-RADIO

No. 501-Jac-Box, complete with cord a

FROST-RADIO

GO to the radio store of your neighborhood dealer and ask him to show you these fine FROST-RADIO parts. Order from his stocks the

are coming. With

on. If you are plan-ing to build a new it these items, and her parts in the

in stock See him today

SPOST-PARIO No. 700-Protector, complete (Pacific Coast prices slightly higher) 50c

FROST-RADIO

Metal Frame Rheostat

FROST-RADIO

314-324 WEST SUPERIOR STREET, CHICAGO NEW YORK CITY CLEVELAND KANSAS CITY LOS ANGELES EXPORT OFFICE: 314 WEST SUPERIOR STREET, CHICAGO



TUBES REPAIRED OR EXCHANGED

ELECTRIC DEVICES CO., De

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



Operates from light socket, Supplies the uniform voltage necessary for perfect reception. Absolutely noiseless, Guaranteed not to set up the slightest hum. No acid to spill. No moving parts to get out of order. Requires no attention. As easy to operate as suriching on a librt. Conven-

sent and dependable. The least expensive plate current supply because of its long life. In bandsome walnut case. Price complete, \$35.

Your dealer can supply you.

The Andrews

Padull who are call.



Improves tone quality. Increases selectivity, range and volume. Losses are negligible. Has exceptionally high ratio of inductance to resistance with minimum

Price and distributed capacity.

Used in well-known receivers such as the Deversadyne and Buckinghom. Can be used in any standard hook-up. Ask your dealer for blue-prints of circuits employing this coil.

Our Technical Dept. will answer inquiries.

Duo-Spiral Tolding Loop



Handsomely finished in silver and malogany. Easily portable. Has long handle and graduated dial. A special model for every circuit. See these standard units at your dealer's

See these standard units at your dealer's or write for complete information.

Radio Units Inc.

Maywood, Illinois
1300 First Avenue
Perkins Elect. Ltd., Montreal, Toronto, Winnipez



YOU CAN GET

Greater reflex or crystal reception if you use BROWNLIE

VERNIER DETECTOR
\$2.00 At your dealer or Direct.
ROLAND BROWNLIE & CO.

Static and Weather Forecasting

(Continued from page 612)

rails intraments could not be accepted as reliable baroneters to weather indications over a wide area, contend meteorologists. Weather forecasting is conducted according to zones or well-defined areas, and users of a content of the content of the

en in progress in one direction only. These variable factors to the contrary, lio equipment is being used, in an experintal way, for detecting storms and the

Radio Wrinkles

ferent aerial, if may be necessary to change the adjustment of the angle J. For an IIthe constants are: Primary, I2 turns; secondary, 65 turns; tickler, 20 turns. For a 23plate condenser: Primary, 10 turns; secondary, 44 turns; tickler, 20 turns; using No. 22 D.C.C. and diamond-waves spelier-web coils. A variable grid leak is desirable, or it a fixed leak, the value should be 7 or 9 megchums

Contributed by M. D. Dansey

Radio and Movies Now Linked

(Continued from page 587)

years ago that "talking pictures," the dream of every theatrical producer, will be a commercial reality.

Grand Opera by Wireless By HUGO GERNSBACK

A RECENT usewayser regor from Calage of the company of the compa

to the orchestra music as well, which is

HENNINGER RADIO

Vizard of Radio

MARVELOUS INVENTIONS
to the perfection of true-coverted R.P. annilitation. These appearance is not appearance of the control o

The POWER PLUS Coil

The resurtable system of weight radiatines the picking up of interferences and absolutely localizes the electromagnetic did in a new among, citing tenenous increase in proceedings of the proceedings of t

POWER-PLUS

Straight Line Frequency Condenser
The Botter and Stater plates of this new POWER-PLL'S confeet centael. Platfall design ellimotate constant resistance and
authoration was recepturated prevents frequency change. Numcount features of design reshort effectiveness never before unreconst features of design reshort effectiveness never before un-

FREE DESCRIPTIVE we will also con Heoninger Felde heed-spa that an

Dealers: Write for dealer felder on these two new specialties
give name of your jebber.

A. F. HENNINGER CORPORATION



Famous Bruno Line
Write us for a Free Catalogue

B-C-L RADIO SERVICE CORP. 218 Fulton Street, N. Y. City

EALERS

omplete stock of nationally known parts
ad accessories. Send for illustrated catag and discount sheet.
Radio Exclusively Since 1921
ARK & TILSON, Inc

thing is that it is not being done now The reason is probably the fact that as year no means has been found to reimburse

But we must give a thought to the man-

At the receiving end, the future un-to-

The underlying idea is not only to give slightest technical difficulty.

Let us say, by way of example, that the opera "Aida" is filmed in its entirety. This may mean a four or five film feature. The opera will be filmed just like any other

Our large illustration shows what hap-pens next. The stars, singers, players, the chorus, orchestra, conductor, etc., are then in front of them is the usual screen. The opera "Aida," which had been filmed before, is now repeated on the screen while microphone in which he or she sings the




NOW you can build a set and have all three tuning dials tune exactly the same—or, you can build a one control set using a gang condenser and know that it's going to work right, AERO Coils are matched! But-the matched feature of Aero Coils is not their only exclusive feature.

Aero Coils are, by electrical measurement and by use tests, the most powerful, most selective and most sensitive inductances ever designed. They will enable your in, with tremendous loud speaker volume, signals you have always had to listen to on head phones.

Build with Aero Coils. You are sure of their superiority because that which makes them so is patent-protected. The Tuned Radio Frequency Kit is \$12.00 complete with circuit diagrams and instructions. At your dealers -or direct, if your dealer hasn't them.

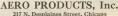Free booklet giving valuable information on radio frequency amplification sent on re-quest. Write now for the "Aero Booklet".



217 N. Desplaines Street, Chicago







ment Commerbook will help sixty cents in stamps or coin or Mexico.

RADIO INSTITUTE OF AMERICA New York City 324 Broadway

UseAERO COILS


The only Air Dielectric Colls Having Variable Primaries In Antennae Circuits 3 Circuit Tuner

Radio Frequency



lective 4-tube, non-radiating set pos-sible to build, Matched - - \$11.00 Wave Trap Unit Also for Crystal Sets

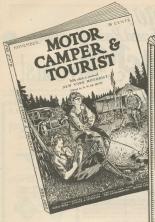Makes an exceptional-ly efficient wave trap for crystal set - \$4.00 Oscillator



Motor Camper & Tourist

has purchased the NEW YORK MOTORIST which is now combined with this magazine.

80 Pages of information for Motor Tourists

35° Everywhere

Subscription, - - - \$3.50 for twelve issues

You can combine your subscription with Radio News; thus, Radio News and Motor Camper & Tourist, 12 issues each......\$6.00

GERMOTT PUB. CO., INC. 53 Park Place, New York, N. Y. Enclosed find \$3.50 for one year's subscription to MOTOR CAMPER & TOURIST (twelve issues).

Sixteen
More Text Pages
Added to

MOTOR CAMPER & TOURIST

Big Increase in the Number of Articles by Noted Authorities and Experienced Tourists

You can get greater pleasure out of any motor trip, see more places of interest and travel with greater comfort and less expense if you read MOTOR CAMPER & TOURIST. Experienced tourists tell you what trails to travel upon, where to stop, what luggage to take along, and to leave home and how to care for your equipment.

More Than Forty Motor Touring Experts Give Advice and Personal Experiences Thousands who have been "over the ground" and who have spent days and weeks on the road have learned by experience the safest, most comfortable and most pleasurable way to camp and tour. These authorities write in MOTOR CAMPER & TOURIST

Timely Trips and Topics of All Kinds One of the features of MOTOR CAMPER & TOUR-IST is the fact that many departments and articles are written especially for the man who is planning an immediate trip in his own car. They give the best trips of the season. In each issue is a complete road

Camping and Touring Equipment and How to Use It

What you take along on your trip is at times just as important as where you are going because a good outfit is half the pleasure of the trip. MOTOR CAMPER & TOURIST gives many, many helpful hints on what to buy and how to buy, and how to use the things you buy.

hints on what to buy and now to buy, and now to use the things you buy.

And then there are many special articles and departments in MOTOR CAMPER & TOURIST of general interest to every man who owns and operates a car. Ask for a copy at your local news stands or use the

THE GERMOTT PUBLISHING CO.,

coupon on this page.

Licensed Publishers - Experimenter Publishing Co., 53 Park Place New York, N. Y. operator, keeps time with the singers, and the singers themselves must keep exact time with the performance as it is unrolled on the screen before their eyes. Insamuch as the identical cast has been fillmed, it will not be difficult for them to keep time with their own performance, as may readily be acceptable to the screen of the screen when the screen of the screen he will home exactly how and when to sing into the microphorain or front of him.

Mail of the microphone go to the wireless telephone station located in the radio room above, and there are, of course, sensitive microphones in the study which pick of the control of the station of the course, the study of the course of the course, and the course of the course that the course of the course of the course for the course of the course of the course of the day and the course of the course of the course of the out over the usual aerial located on top of the bones and are shot out all over the

country instantaneously.

Five hundred to 1,000 miles away—and for that matter all over the country—every moving picture house will have been supplied with the identical film at the stated performance, it having been amonunced days ahead that the grand opera "Alda" will be given at such and such and bour.

Of nourse, where the distances are large, the bour rendering the opera will vary. Thus, for instance, if Scotti were singing in New York and a performance were to start at eight o'clock in the evenings. New at four o'clock in the evening, as at four o'clock in the evening, as an four o'clock in the evening, as a four o'clock in the evening, as a four o'clock in the evening as a matiner, due to the difference of time. Inasumuch as each performances would probably be held only once a month, people would nor middle lincomponent the to the slight, difference the to the slight difference the total processing the slight difference of the slight difference the contraction of the slight difference of the slight differen

Every moving picture house will have its receiving apparatus with its usual amplifiers and anywhere from six to one dozen loud talkers scattered through the house. Exactly at the stated time the moving picture operator will begin grinding away—the operator will begin grinding away—the operator has begun. Simultaneously the distant orchestra will begin playing, filling the house with music.

When the actual performance begins, it will be an easy matter for the operator to keep time with the incoming music. All the needs to do it so grind faster or abover, and insurance as a constraint of the control of t

From a finuscial standpoint it would be good basiness for the opera company, as well as for the moving petture losses, well as for the moving petture losses, and the standard of the movement of the standard of the standard, with handly any expense. The grand opera with an ording off, and the standard of the standard

The writer confidently expects that the scheme will be in use throughout the courter very shortly.

"As efficient as Radion Panels"



The best recommendation for these Radion low-loss parts.

THE very latest developments

in radio are embodied in the
complete line of Radion low-loss
parts, Moulded of Radion-loss
insulation made to order for radio
purposes exclusively—they have the
high-resistant characteristics for which
Radion Panels are noted.

These parts have the wonderful Radion finish, smooth and high-polished. This finish eliminates those losses due to moisture gathering on the surface of ordinary insulation, causing leakage paths.

You can now get Radion Sockets, Dials, the new Radion Loud Speaker Horn, Tubing, Binding Post Strips, Insulators, etc. Radion Panels in black and Mahoganite come cut in standard sizes for whatever set you wish to build.

Send for booklet, "Building Your Own Set," Gives wiring diagrams, front and rear views, shows new set with slanting panel, lists of parts and directions for building popular circuits. Mailed for 10 cents.

AMERICAN HARD RUBBER COMPANY, Dept. All, 11 Mercer St., New York City





binding posts.

The Supreme Insulation
Made to order for radio

N FRANCIS

AMERICAN HARD RUBBER COMPANY, Dept. All, 11 Mercer St., New York City.	
Please send me your booklet for which I encl 10 cents in stamps.	>

Name
Address



FREE—Our 64-Page Catalogue. Filled With Radio Bargains. Write Today! RANDOLPH 159 N. UNION AV. PROL 2 CHICAGO, ILL.



The GOODMAN SHORT WAVE TUNER has been on the market for several years and is still holding its prestige against all comers. Certificate of merit from Rabio News and others.

L. W. GOODMAN, Mir., Drexel Hill, Penna.





SPARTAN BELL \$12.00

Member of the New Improved

PEAKER

two adjustable horn type models: with bakelite base, the Spartan Bell, the Disc Model and the cabinet Consola Modelpriced from \$10.00 to \$25.00.

Every Spartan Speaker represents the best value obtainable at its price. Choose the model that fits your own taste and purse from your dealer.

SPARTAN ELECTRIC CORP. 99 Chambers St. Nam York City

GET A Handy Binder for your RADIO NEWS

Holds and preserves six is-

Price 65c. EXPERIMENTER PUBLISHING CO., Inc., 53 Park Place, New York The Raytheon Rectifier

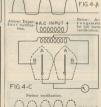


FIG. I A perfectly symmetrical tube does not permit rectifito knock apart, i. c., to ionize, the particular

dition is what we referred to above as the



path for the production of ionization." We now see that it is a simple, common-sense requirement, not in any way difficult to un-derstand. In helium at a pressure of one millimeter of mercury the average path over direction as in the other. If this tube were



Developed for Those

Who Demand the Best "Apex Vernier Dials

Apex Vernier Dials are contracted on exhaustively tested and truly scientific principles and are engineered to the principles and provide coatrol and accuracy casentarity and positiveness sidden encountered and provide coatrol and accuracy casentarity and positiveness added to the principles of t

Apex Rheostat Dials

If your dealer is unable to supply you, order direct from us. APEX ELECTRIC MFG. CO.





of the Air

FERBEND ELECTRIC CO. 25 E. So. Water St., Chicago, III See page 731 for our new "B"

===\\distant====== National Airphone Corp.

MANUFACTURERS OF Somerset-the Ultimate in

Radio Frequency Receivers 18 Hudson Street - New York City

Insure your copy reaching you each month. Subscribe to RADIO NEWS —\$2.50 a year. Experimenter Publishing Co., 53 Park Place, New York

put into an A.C. circuit, both half-cycles of current would pass equally well and no rectification whatever of the flow would

Suppose, now, we have a tube built as in Fig. 3 with one plate, An large area cylinger and the plate of the p

The first step in smoothing out the 'real' valves connected in parallel (Fig. 4C) just as in other cecifiers of all types, so that valves connected in the strength of the strength of the valves of t

It is, of course, desirable to eliminate the "back-current" through the rectifier (the little current loops below the line in Fig. 4A as far as possible, since the ratio of "bac current" to "forward current" determine the percentage of rectification. This en

as small as is practically possible compared with the area of the cathode.

other cuttle and of the same chairman from the mean taken to reduce the effective anode area and in the selection of a scient and the same area and in the selection of a scient another than the selection of a scient and the selection of a scient another than the selection of th

Bigger Radio Bargains Than Ever Before

ERE you are—just off the press—the latest radio catalog and guide, brimful of the best as any proved standard radio sets, parts and kits at savings that will appeal to the thrifty. Profusely illustrated with reliable, guaranteed goods at tremendous savings. Be sure to get your copy before you spend another cent for parts and radio supplies.

EVERYONE INTERESTED IN RADIO SHOULD HAVE THIS GUIDE

It gives information about the newest and most advanced ideas in radio development, describes and illustrates the latest improvements. It will keep you posted on what's up to date. It will help you to build a better set or buy a complete modern one.

Over 100 Hook-Ups

Over 100 latest hookups and information, completely illustrated. Every radio set owner, amateur, beginner and fan should have a copy.

Send the Coupon for Free Copy

You need this book before you spend another cent on radio. Just mail the coupon and free copy will be sent you. Also please include name of a friend interested in radio to whom we can send free copy.





ILLINOIS VG CONNECTORS

No. 1 Series

New Vise-Grip o nectors for eve kind of radia com

No. 3 Cord Tip or soldering. Exsy, quick and positive. Cheapest and best connectors. Only 16e each. Remit.

ILLINOIS RADIO COMPANY Springfield Illinois

Insure your copy reaching you each month. Subscribe to Radio News-\$2.50 a year. Experimenter Publishing Co., 53 Park Place, New York City.



away from the Radio Serv-RADIO TROUBLE

SHOOTER tells you in easy readable English how to locate every radio trouble and how to correct it. If your dealer does not stock it yet, send 25c to

H. B. SHONTZ & CO., Inc. 161 West 64th Stree New York, N. Y



aborhood. IF YOU LIVE IN THE COUNTRY YOU NEED THIS TOOL KIT.

In the event your dealer does not stock it, send your order direct to H. B. SHONTZ & CO., Inc., 161 West 64th St. New York, N. Y.

Three "E" Straight Line Rheostat



ELECTRICAL ENGINEERS EQUIPMENT CO.

The Aristocrat of Rheostats



This limits the conduction to the very tip of the wires, from which the electrons can smoother, cleaner output is said to be ob-



ANODE -2 ANODE I

This shielding protects the dis-

Circuit dia-gram of the "B" battery

The incorporation of the two featurees use of two anodes) gives the tube an outstanding position amongst gas-filled rectifier bulbs for "B" battery eliminators. Since the sare conduction value of tubes of this type of moderate size is limited to a few hundred milliamperes it is evident that they have no application as "A" battery chargers or for similar heavy duty work.

A CORRECTION TO THE HISTORY OF RADIO INVENTIONS

In the July, 1925, issue of Radio News on page 52 under diagram No. 28 the caption should read: "Hartley Circuit. Circuit of 10-meter Generating Set. (By courtesy of



Stamp out Tuberculosis with these Christmas Seals



The National, State, and Local Tuberculosis

YOU CAN GET

FIFE MINUTE INSTRUCTION BOOK

TERE'S a Banjo-Uke that you will be proud to own. Fine workmanship and high grade material have given it rich tone, a neat

looking appearance and it will stand plenty of rough usage. A complete Instruction Book is packed with every Uke. In five minutes the simple lessons in this book can teach you how to play hany of the hits. A few weeks later and you may be known as an expert, welcome at parties, dances, church, lodge and school socials, etc.

lodge and school socials, etc.
We will award hundreds of these
Banjo-Ukes. You can easily earn
one in your spare time. Full particulars mailed immediately on request, No obligation. Write today. E. J. FOLEY

Experimenter Publishing Co., 53 Park Pl., New York

Radio With the Rice Amazon Expedition

*(Continued from bage 589)

signals. Power conditions were the same in both cases. The distance is about 200 miles. The writer had an excellent opportunity to work stations during partial daylibric and work stations during partial daylibric and at Minneapolis, Minn, was worked during absolute darkness at Box Vista. Gradually dawn appeared and then bright dayling the state of the dayling characteristic and the dayling of the dayling of

The station WJS was, at this time, located in a fair clearing and the writer could see plainly the sunrise. As far as could be judged, there was no increase or decrease

in the strength or fading of the signal.

An instance of wave jumping, occurred and in the control of the contr

Joseph Boa Vista, in April, 1925, the writer tried for three nights, calling and listening for United States stations. The final night a station in Philadelphia took all traffic. The records on which the station were logged have been misplaced, but I take great pleasure here in saying that the Philadelphia man saved the day, for we moved the next day on our last leg of the moved the next day on our last leg of the

At the final semi-permanent camp, where the expedition changed from native cances to smaller dug-outs belonging to the Indians, the radio equipment was left behind with

When the party had returned to the other side of the five-mile portage the writer and the airplane mechanic journeyed over to prepare another canoe and send our nunercoss in reaching its goal high up in the Parima Mountains that form the northern boundary of Brazil, forming the border-line between that country and Venezuela.

When the truth in which the efficiency was found to column multitudes of anist and their eggs. They had made home between the effective the ef

But, thanks to the station in Philadelphia, about six messages reached their destination, making known to the world that we were safety on the return voyage after the most

During one very hot night after the rain, when all kinds of insects had found shelter under the canvas roof over the portable set,



A Radio Operator —at Fifteen!

Alfred J. Koenig, the "boy wonder" of radio as he appears today.

ALFRED J. KOENIG worked as an office boy by day and studied radio at the Radio Institute of America by night. At the age of fifteen he received his First Class U. S. Government Commercial Radio Operator's License. Today he is engaged in the transmission and receipt of photomodiograms at the Radio

Thousands of our graduates are now holding successful positions in radio. And YOU can attain success in radio. too.

Corporation of America's station in Hawaii,

Study radio in spare time

Even though you may be employed at present, the Radio Institute of America's Home Study Course in Radio can give you all the knowledge you need to be able to pass your radio license examinations—to ready for your first radio job. This is the world's oldest radio school—conducted by the Radio Corporation of America. For further information, address the

RADIO INSTITUTE OF AMERICA Formerly Marconi Institute Established in 1909

324 Broadway

New York City

CUT HERE

RADIO INSTITUTE OF AMERICA, 328 Broadway, New York City,
Please send me full informations beauty your Home Study Course of radio instruction.

Lam interested in the complete course, including code instruction, which qualities for the U.S. Covernment Commercial or Amsurer Wadio License.

Addres

STANDARD ADJUSTABLE

Fits any pitch of roof.

Eliminates un-

No wind resist-

Price \$2.00

AERIAL BASES

Absolutely protects your building from lightning when grounded.

Lasts a life time. Will not blow

down.

Insist that your aerial be installed with these new Standard Aerial Bases.

Get the best and the cheapest at the same time.

STANDARD AERIAL BASE CO., 227 W. 2nd St., POMONA, CALIF.

Insure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



it was necessary to keep blowing the terminals of the antenna series conduser to prevent the bugs from getting across it and destroying resonance in the autenna circuit immediately a bug touched one of the terminals its body would be cremated and form a short circuit for the high frequency current, which was at high potential through the condenser.

INSECTS

After several months of operating in the open forest, it becomes quite possible to accustom one's self to the many insects, but when they interefere with the actual working of the apparatus, it is of inferent! It is no humorous matter. You crush, mangle and destroy several millions, with the retule until the veil work of the dead ones.

Besides communications, radio played another important role in determining chromotomic properties of the properties of t

The long wave receiver consisted of threthes connected in the usual manner and hat a loop for its collector. Although rathout of the ordinary in constructional detail this receiver worked at all times, despite the drizzling rain and soggy ground on white to free rested. At times, it would require to the contract of t

mosture out of the modelpholes and soly, in the time folick was brought about by the necessity of receiving the non-time size and while under way in a small came has while under way in a small came has a small came to the same time in going ashore, so the apparatus was time in going ashore, so the apparatus was to the same time in going ashore, so the apparatus was to be a small came to maintain maximum significant to the same time in the came, suspering and rotating the loop of the set to maintain maximum significant to the same time to the came, suspering and rotating the loop of the set to maintain maximum significant to the same time to the came, and the same time the came to the same time tim

Boa Vista station but most of the findings must be held for further investigation. However, it can be stated that one im-

portant discovery was of the association of the presence of high winds with an increait atmospheric disturbance. This, no doub directly follows the theory of dust movin at a high velocity giving rise to the atmopheric charges which affect radio receivers.

conditions have no perceptible influence on the reception of wave-lengths below 100 meters. Radio communication from South in the vicinity of 80 meters will not be asreliable during the summer months of North America. This fact cannot be attributed to any definite reason. Very radical conditions the short-wave signals for several days, later permitting them to come through with strength.

At present the author is constructing equinent to be used on a wave-length of 10 a 80 meters for Mr. Henry Field, who is goi to Balboa in the fall. SAVE TIME AND MONE

We have radio Tools of every description for every conceivable set building purpose You will be astonished at the remarkable tools

we have for your work and delighted at our low prices





NO. 201







COMBINATION PLIER

Combination Plier, Wire Cutter, Wire Former and Wrench. Drop forged, slender but exceptionally strong. 6 inches long. No. 202—Combination Plier, Wire Cutter, Wire Former and Wrench. . . 75c

RADIO TOOL SET

rms in the maintest wer, in tools ever made "WANKEE" Tools. It countains the follow-ing: 1 Ratchet Screw-driver, 6% in, long bolding all attachments; 1 Blade, 5½ x ½; 1 Blade 5½ x ½; 1 Countersitis; 2 Socket Wrenches for all countersitis; 2 Socket Wrenches for all counters and from ½ to ½; 1 Wrenche note end 5-16" square or hex. for jack, other ½" hex., etc.

PRICE per set—No. 701. 33.00

SIDE CUTTING NIPPER, LAP JOINT

CIRCLE CUTTER

PRICE—No. 401\$2.60 SCREW STARTER and DRIVER

ELECTRIC SOLDERING IRON

element is of Nichrome, which prevents overheating and assures the desired even temperature. Size of Iron, 10½ in. long. A 4-ft. cord and plug is furnished. PRICE No. 800 \$2.00

HAND DRILL

Especially designed for Radio Work by the makers of the famous "Yankee" Tools. A beautiful balanced, small, powerful drill with beautiful balanced, small, powerful drill with years of the property of the largest drill, mostly immished with drill or tool sets. Length over all, 9½ in. Weight 1½ lbs. Length over all, 9½ in. Weight 1½ lbs. \$2.75 PRICE—No. 302 ... \$2.75

Order all tools by order number. All goods are shipped free of transportation charges to all parts of the United States and possessions the same day as the order is received

MONEY REFUND GUARANTEE

If you are not ratiofed money will be refunded on return of goods,

THE

RADIOGEM CORPORATION

66-R West Broadway

New York, N. Y.

Takes the MYSTERY out of RADIO!



100,000 SOLD

Compiled by HARRY F. DART, E.E. Formerly with the Western Electric Co., and U. S. Army Instructor of Radio. Technically edited by F. H. DOANE.

BE A RADIO expert—it's easy for the 100,000 who own this compact, complete Radio Hand-book. Written in good, plain, understandable language. Crammed full of facts, every one usebook. Written a bound of facts, every one use-language. Crammed full of facts, every one use-ful and important. Explains how receivers and transmitters work, how to build and operate them. Whatever you or your friends want to know, it's here. Will save you many times its

TELLS ALL ABOUT: Electrical terms and circuits, antennas, batteries, generators and motors, electron (vacuum) tubes, most receiving hook-ups, radio and and frequency amplification, broadcast and commercial transmitters and receiving, super-regeneration, codes, license rules. Many other features.

Nothing else like it. Make this extraordinary

INTERNATIONAL CORRESPONDENCE SCHOOLS

Box 3283-F, Seranton, Pensa.

I enlowe \$1..., fee which send me, post-paid, the Handbooks marked X. at \$1 each. It is under-steed that if I am not entirely satisfied I may return them within five days and you will refund

RADIO HANDBOOK, 514 PAGES, \$1

Automobile Brailbook, 314 pages 4 1 Electrical Handbook, 314 pages 5 1 Electrical Handbook, 314 pages 5 1 Electrical Handbook, 324 pages 5 1 Electrical Handbook, 324 pages 6 1 Electrical Handbook, 324 pages 7 Electrical Handbook, 325 pages 1 Electrical Handbook, 325 pages 3 Electrical Handbook, 325 pages 1 Electrical Handbook, 325 pages 3 Electrical Handbook, 3

Build Your Own-

GEARS All Kinds-

The Life Work of Lee DeForest

The station at the World had been op-

For some time there had been a corregan putting the orchestra music from the stalled. Reports of its volume and carry-

THE PHONORILM

He had conceived the idea some years the opportunity to follow it up. However velopments in his private affairs, he de-

Yet he has a great interest in the future "It is only a matter of a few years-the

as a stable and very important part of our cultural life. The change in the program noticeable and we may say that they are

fection of the mechanical and electrical, as well as the artistic, side. From the present, great attention will be paid to the perfection

been overcome by the addition of the voice to the visual entertainment, so that, after all

the home movie may make its presence felt

PERFECT They pull the sodder from the is KELLERADIO, Inc. 821 Market St., San F Sole Distributors

\$ prings you this genuine AMPL-TONE Loud Speaker Unit Ten days' free trial. Your Three Dollars unconditionally returned if at the end of

HEINTZ AND (HOHLMOOS

ten days you are not perfectly satisfied volume and clear re-

graph people spent years perfecting the acoustic Take advantage and use our unit on you UNION FABRIC CO."

(Makers of the French Headzet) DERBY, CONN.



ON FLOATS RUBBER

ILLINOIS RADIO CO.

800 S. 4th St. Springfield, Illinois

RICHARDSON RECEIVERS ACHIEVE RESULTS
Factory and Executive Offices:
Faster Avenue & Hulat Street, Long Island City

Follow these advertisements every month. Reliable advertisers from all over the country offer their most attractive specials in these

Classified advertising rate twenty-two cents a word for each insertion. Ten per cent discount for 6 issues, 20 per cent discount for 12 issues. Name and address must be included at the above rate. Cash should accompany all classified advertisements unless placed by an accredited advertising agency. No advertisement for less than 10 wirels accepted. Objectionable or misleading advertisements not accepted. Advertisements for the January issue must reach us not later than Nov. 1st.

CIRCULATION LARGER THAN THAT OF ANY OTHER RADIO PUBLICATION EXPERIMENTER PUBLISHING CO., INC., 53 Park Place, New York, N. Y.

Agents Wanted

Earn \$10 daily Silvering Mirrors, platfag, refinishing etalware, headlights, chandeliers, bedsteads, Outflit emished. Belanger-Decke Laboratories, 1133 Broadway,

eer York.

Baskrupt and Rummape Sales. Mike \$50.40 daily. W. familihing everything. Distributors, Dept. 213

Business Opportunities

140 profit. No big investment, average mode \$400.1 to one seconds. Representatives wante e. This plan is sweeping the country—write todayour country is gone. Ocarka, 812 Washington Blvd. Sion a week. Mail Order Business. Free beoklet tells how, ample and plans 25c. Free \$3 worth of articles. Gellnar, 4261 Broadway, Chicago, III.

Free Beek. Start little Mail Order Business. Pier, 104 rtland Street, N. Y. We establish any benest man, regardless of inesperience or

no.

Make Møney! 150 Plans FREE! Wolverine Bureau. (D-1) utbezon. Michigan.

\$100 weekly up. We want experienced Badio men to operate branch assembling plants. Parr or whole time. Barfield ald Co. 13 Tiller's Street. Derd. N.R., Brookby, New

Chemistry

Educational ed Correspondence School courses save over half. But entalogue 1600 courses free. Used courses bout ents' Exchange, Dool. A. 47 West 42d St., New Yor

Electric Motors

For Advertisers

Gummed Labels 3000 \$1.00, Catalog 2 cts. MacTag-urt, 1237 Arch, Philadelphia, Penna.

Motion Pictures

Motorcycles, Bicycles

Old Money Wanted

Patents

Patent Attorneys

Total Attendance of Control and Control an

Lenesame—Join our clob—raske acquaintances every-Big illustrated book with descriptions and photos, so stain wrapper for ten cents. Barafide Co., Dept Karsas City, Mo. Radiumart Remeves Warts, Moles, Superfluous Hair, Cosl, voxder and Tattee Marks. Particulars sent free. Radium-et Co., 1416 Cadwallader St., Philadelphia, Pa.

Printing Outfits and Supplies

Print year own cards, stationery, circulars, paner, ote capalete outfits 88.85; 26b Presses 812, \$25; Retary \$150 virth for others, big profit. All easy, rules sent. Writs or catalog presses, type, paper, etc. Press Company, A-13 feriden. Comp

Edison Alkaline Storage "B" Battery elements

edford, Jennsteau, N. Y. Bargains—Zenth Model 3B—4 tube—\$100. tube \$10.0. New sets—guaranteed, if C.O., eccumpany order. Amateur Radio Supply C

Salesmen Wanted

urners, 63 Climax Bidg., Kansas City, Mc Skat Sales Agents Wanted, All or Part land Sone, Metal Polish, etc. Strictly Co

Scenery to Rent

Song Writers

Telegraphy

Telegraphy—Both Merse and Wireless taught the

Wanted to Buy

Value Paid for Old Gold, Joselty, Watcher, crowns, bridges, dental gold, silver, platinu crowns, bridges, delfalle feeth. Pack



Introducing The PICT

The Speaker of Perfect Tonal Values

In the FITCH all the many advantages of the cone-type speaker have been brought to a fuller development.

The double cone has no frame about its edge to restrict free vibration. It is supported at the center only. It has no rubber, metal or felt attached to the edge to kill or distort the tone values.

This, together with the use of two cones of unequal size and angle, gives the FITCH its remarkable clarity and fidelity of tone.

The entire audible range, from the high notes of the soprano to the deep tones of the bass, is reproduced with exceptional uniformity.

The FITCH speaker is a beautiful symmetrical, and artistic ornament, which harmonizes with any setting.

The unit is adjustable. It will not chatter or blast.

See and hear the FITCH at your dealers. If your dealer is not supplied, we can make immediate delivery.







FITCH RADIO COMPANY 105 West 40th St. ~ New York City